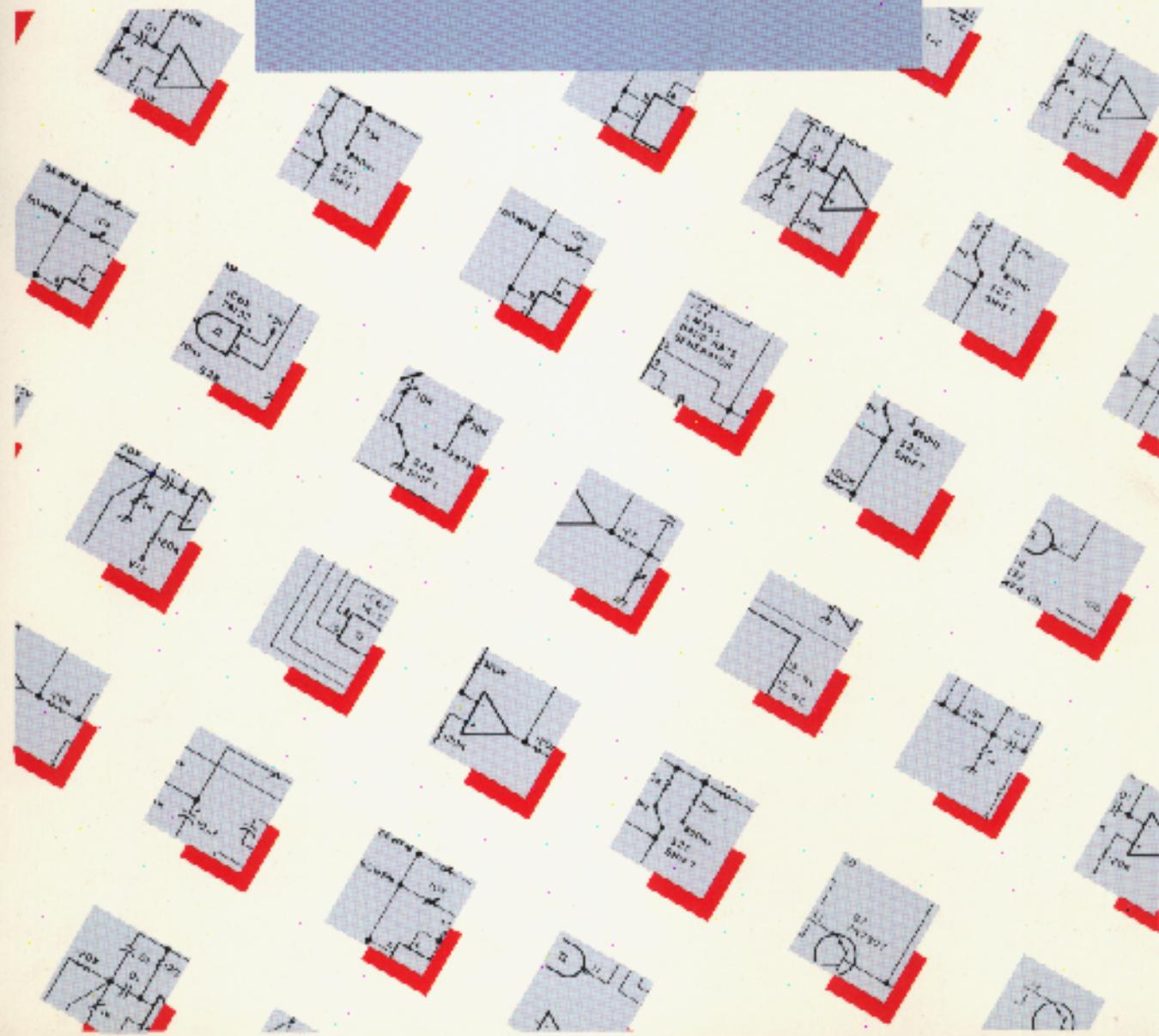


# Encyclopedia of **ELECTRONIC CIRCUITS**

*Volume 2*

Rudolf F. Graf



## **CONTENTS**

---

---

<b>Introduction</b>	vii
<b>1 Alarm and Security Circuits</b>	1
<b>2 Amplifiers</b>	5
<b>3 Analog-to-Digital Converters</b>	23
<b>4 Annunciators</b>	32
<b>5 Audio Mixers, Crossovers and Distribution Circuits</b>	35
<b>6 Audio Signal Amplifiers</b>	41
<b>7 Automotive Circuits</b>	48
<b>8 Battery Chargers and Zappers</b>	64
<b>9 Battery Monitors</b>	74
<b>10 Bridge Circuits</b>	80
<b>11 Burst Generators</b>	86
<b>12 Capacitance Meters</b>	91
<b>13 Circuit Protection Circuits</b>	95
<b>14 Clock Circuits</b>	100
<b>15 Comparators</b>	103
<b>16 Computer Circuits</b>	113
<b>17 Converters</b>	123

<b>18</b>	<b>Counters</b>	<b>133</b>
<b>19</b>	<b>Crystal Oscillators</b>	<b>140</b>
<b>20</b>	<b>Current Meters</b>	<b>152</b>
<b>21</b>	<b>Demodulators</b>	<b>158</b>
<b>22</b>	<b>Descramblers and Decoders</b>	<b>162</b>
<b>23</b>	<b>Detectors</b>	<b>171</b>
<b>24</b>	<b>Digital-to-Analog Converters</b>	<b>179</b>
<b>25</b>	<b>Dip Meters</b>	<b>182</b>
<b>26</b>	<b>Display Circuits</b>	<b>184</b>
<b>27</b>	<b>Drive Circuits</b>	<b>189</b>
<b>28</b>	<b>Electronic Locks</b>	<b>194</b>
<b>29</b>	<b>Emulator Circuits</b>	<b>198</b>
<b>30</b>	<b>Fence Chargers</b>	<b>201</b>
<b>31</b>	<b>Fiberoptics Circuits</b>	<b>204</b>
<b>32</b>	<b>Field Strength Meters</b>	<b>208</b>
<b>33</b>	<b>Filter Circuits</b>	<b>213</b>
<b>34</b>	<b>Flashers and Blinkers</b>	<b>225</b>
<b>35</b>	<b>Flow Detectors</b>	<b>240</b>
<b>36</b>	<b>Fluid and Moisture Detectors</b>	<b>243</b>
<b>37</b>	<b>Frequency Meters</b>	<b>249</b>
<b>38</b>	<b>Frequency Multiplier and Divider Circuits</b>	<b>251</b>
<b>39</b>	<b>Frequency-to-Voltage Converters</b>	<b>255</b>
<b>40</b>	<b>Function Generator Circuits</b>	<b>258</b>
<b>41</b>	<b>Games</b>	<b>275</b>
<b>42</b>	<b>Gas and Smoke Detectors</b>	<b>278</b>
<b>43</b>	<b>Hall Effect Circuits</b>	<b>282</b>
<b>44</b>	<b>Humidity Sensors</b>	<b>285</b>
<b>45</b>	<b>Infrared Circuits</b>	<b>288</b>
<b>46</b>	<b>Instrumentation Amplifiers</b>	<b>293</b>
<b>47</b>	<b>Integrator Circuits</b>	<b>297</b>
<b>48</b>	<b>Intercom Circuits</b>	<b>301</b>
<b>49</b>	<b>Lamp-Control Circuits</b>	<b>304</b>
<b>50</b>	<b>Laser Circuits</b>	<b>313</b>
<b>51</b>	<b>Light-Controlled Circuits</b>	<b>318</b>
<b>52</b>	<b>Logic Amplifiers</b>	<b>332</b>
<b>53</b>	<b>LVDT Circuits</b>	<b>336</b>
<b>54</b>	<b>Measuring and Test Circuits</b>	<b>340</b>
<b>55</b>	<b>Medical Electronics Circuits</b>	<b>347</b>
<b>56</b>	<b>Metal Detectors</b>	<b>350</b>
<b>57</b>	<b>Metronomes</b>	<b>353</b>

58	Miscellaneous Treasures	356
59	Modulator Circuits	368
60	Motor Control Circuits	373
61	Multiplier Circuits	391
62	Noise Reduction Circuits	393
63	Notch Filters	397
64	Operational Amplifier Circuits	404
65	Optically-Coupled Circuits	407
66	Oscillators	420
67	Oscilloscope Circuits	430
68	Peak Detector Circuits	434
69	Phase Sequence Circuits	437
70	Photography-Related Circuits	443
71	Power Amplifiers	450
72	Power Supply Circuits	460
73	Power Supply Circuits (High Voltage)	487
74	Power Supply Monitors	491
75	Probes	498
76	Proximity Sensors	505
77	Pulse Generators	508
78	Radiation Detectors	512
79	Radar Detectors	518
80	Ramp Generators	521
81	Receivers	524
82	Rectifier Circuits	527
83	Relay Circuits	529
84	Resistance/Continuity Meters	533
85	RF Amplifiers	537
86	RF Oscillators	550
87	Sample-and-Hold Circuits	552
88	Sine-Wave Oscillators	560
89	Sirens, Warblers and Wailers	571
90	Sound (Audio) Operated Circuits	580
91	Sound Effect Circuits	585
92	Square-Wave Generators	594
93	Staircase Generator Circuits	601
94	Stereo Balance Circuits	603
95	Strobe Circuits	606
96	Switch Circuits	611
97	Tape Recorder Circuits	613

<b>98</b>	<b>Telephone-Related Circuits</b>	<b>616</b>
<b>99</b>	<b>Temperature Controls</b>	<b>636</b>
<b>100</b>	<b>Temperature Sensors</b>	<b>645</b>
<b>101</b>	<b>Temperature-to-Frequency Converters</b>	<b>651</b>
<b>102</b>	<b>Theremins</b>	<b>654</b>
<b>103</b>	<b>Thermometer Circuits</b>	<b>657</b>
<b>104</b>	<b>Tilt Meters</b>	<b>663</b>
<b>105</b>	<b>Time-Delay Circuits</b>	<b>667</b>
<b>106</b>	<b>Timers</b>	<b>671</b>
<b>107</b>	<b>Tone Control Circuits</b>	<b>682</b>
<b>108</b>	<b>Touch-Switch Circuits</b>	<b>690</b>
	<b>Sources</b>	<b>694</b>
	<b>Index</b>	<b>713</b>

# Introduction

---

---

*Encyclopedia of Electronic Circuits—Volume 2*, a companion to Volume 1 published in 1985, contains well over 1400 not-previous covered circuits organized into 108 chapters. For each reference, circuits are listed at the beginning of each chapter. The extensive index further enhances the usefulness of this new work. The browser, as well as the serious researcher looking for a very specific circuit, will be richly rewarded by the context of this volume. A brief explanatory text accompanies almost every entry. The original source for each item is also given so that the reader requiring additional data will know where to find it.

I am most grateful to William Sheets for his many and varied contributions to this book, and to Mrs. Stella Dillon for her fine work at the word processor. These friends and associates of long standing have my sincere thanks for contributing to the successful completion of this book.

# 1

## **Alarm and Security Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Auto Burglar Alarm
- Multiple Alarm Circuit
- Differential-Voltage or Current Alarm
- Trouble Tone Alert
- Photoelectric Alarm System
- Alarm Circuit

## AUTO BURGLAR ALARM

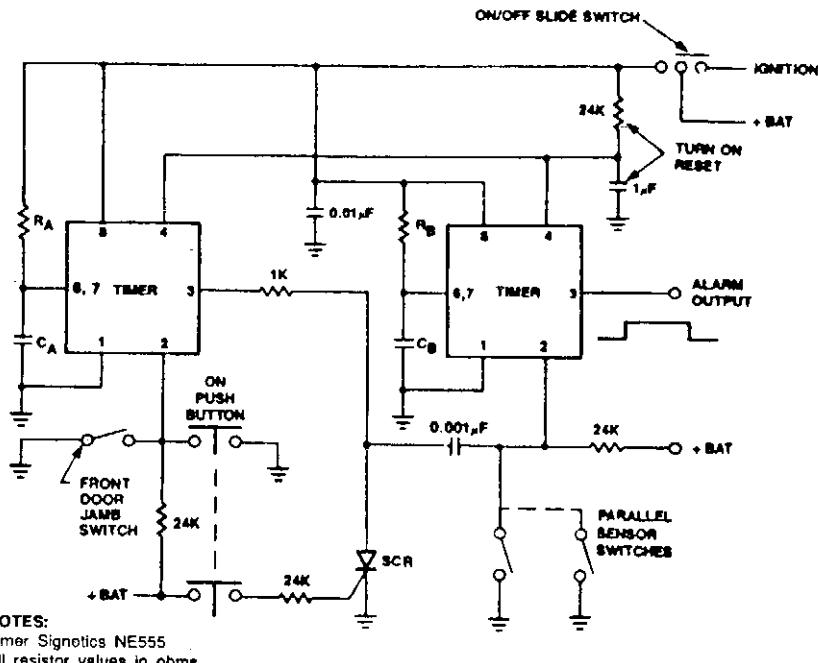


**Fig. 1-1**

### Circuit Notes

Timer A produces a safeguard delay, allowing the driver to disarm the alarm and eliminating a vulnerable outside control switch. The SCR prevents timer A from triggering timer B, unless timer B is triggered by strategically-located sensor switches.

## MULTIPLE ALARM CIRCUIT

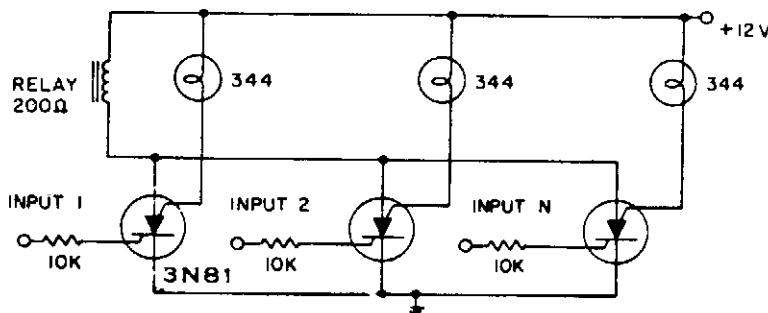

**Fig. 1-2**

### Circuit Notes

Any of several inputs pulls in the common alarm relay with lamps giving visual indication of triggering input. Low resistance lamps decrease input sensitivity.

## DIFFERENTIAL VOLTAGE OR CURRENT ALARM

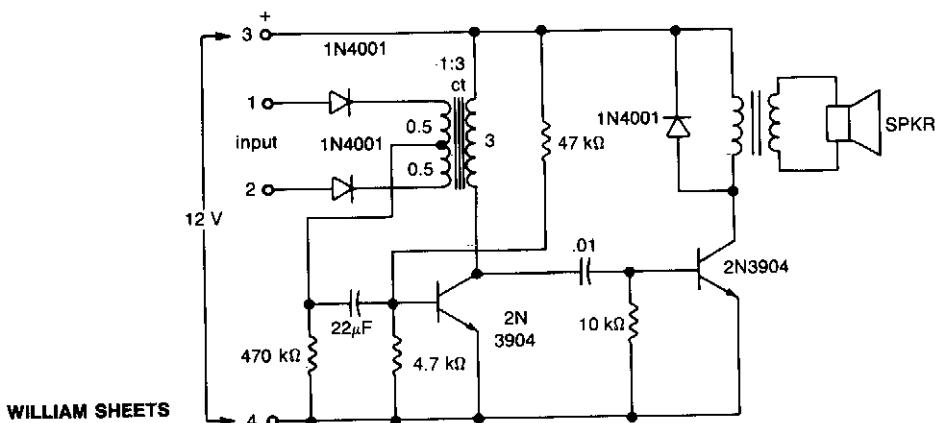


Fig. 1-3

### Circuit Notes

The input may be dc or low frequency ac. The output is a distinctive series of audio beeps or a continuous tone, and occurs only when a selected polarity unbalance is present at the input.

## TROUBLE TONE ALERT


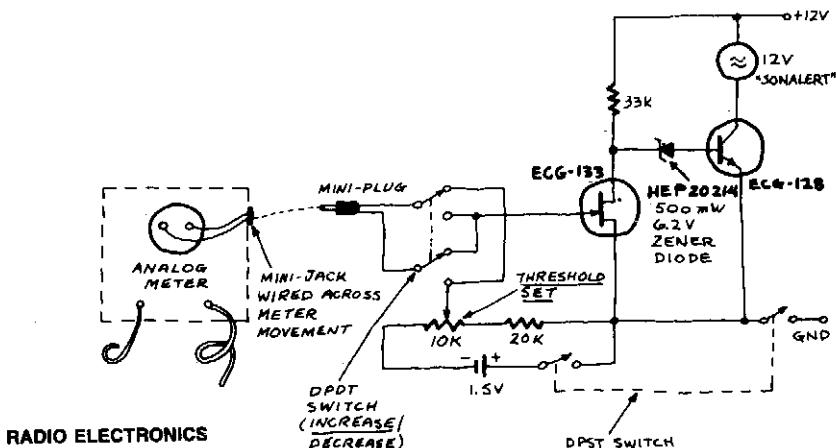


Fig. 1-4

### Circuit Notes

The Trouble Tone Alert is intended for use with analog meters—just wire a “mini” earphone jack directly across the meter movement, plug it in, and you’re all set. This device reacts to the meter-movement driving voltage. It will respond to a change in ac or dc voltage, current, or in resistance. The circuit will respond to an increase or decrease selected by the DPDT switch and is adjusted with the threshold control until the tone from the Sonalert just disappears (with the meter in the circuit being tested, of course).


## PHOTOELECTRIC ALARM SYSTEM

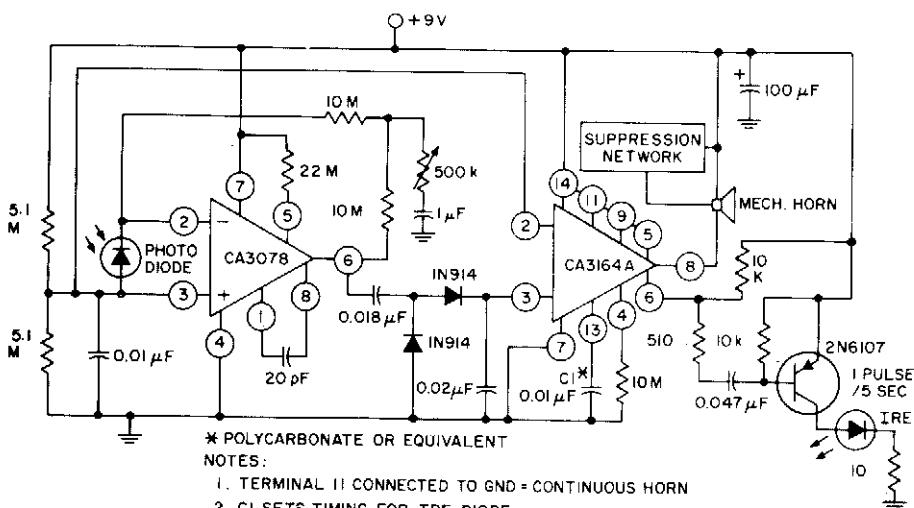

### Circuit Notes

The CA3164A BiMOS detector alarm system and the CA3078 micropower op amp with a photodiode are used as an automatic switch for turning on a night light or sounding a mechanical horn.

## ALARM CIRCUIT

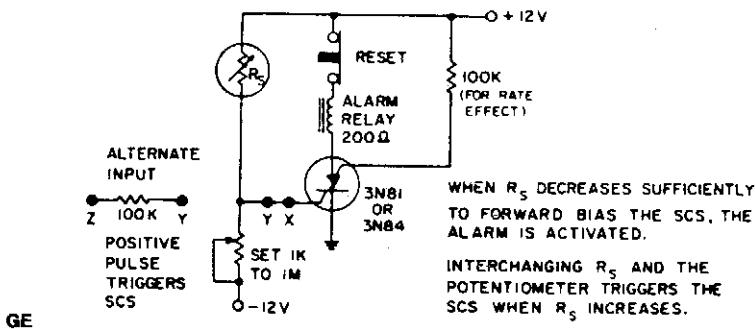

**Fig. 1-6**

### Circuit Notes

Temperature, light, or radiation sensitive resistors up to 1 megohm readily trigger the alarm when they drop below the value of the preset potentiometer. Alternately, 0.75 V at the input to the 100 kΩ triggers the alarm. Connecting SCS between ground and -12 V permits triggering on negative input to  $G_A$ .

# 2

## Amplifiers

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Stable Unity Gain Buffer with Good Speed and High  
Input Impedance  
Chopper Stabilized Amplifier  
Ultra-Low-Leakage Preamplifier  
FET Input Amplifier  
Ultra-High  $Z_{in}$  ac Unity Gain Amplifier  
Logarithmic Amplifier  
Composite Amplifier  
Stereo Amplifier with Gain Control  
Precision-Weighted Resistor Programmable-Gain  
Amplifier  
Power GaAsFET Amplifier with Single Supply  
Linear Amplifiers from CMOS Inverters  
Current-Collector Head-Amplifier

Hi-Fi Comander  
Two-Wire to Four-Wire Audio Converter  
Thermocouple Amplifier  
Low-Distortion Audio Limiter  
Speech Compressor  
Speaker Overload Protector  
Audio Automatic Gain Control  
Voltage Controlled Attenuator  
High-Input-Impedance Differential Amplifier  
Audio Q-Multiplier  
Automatic Level Control  
Pulse-Width Proportional-Controller Circuit  
Op Amp Clamping
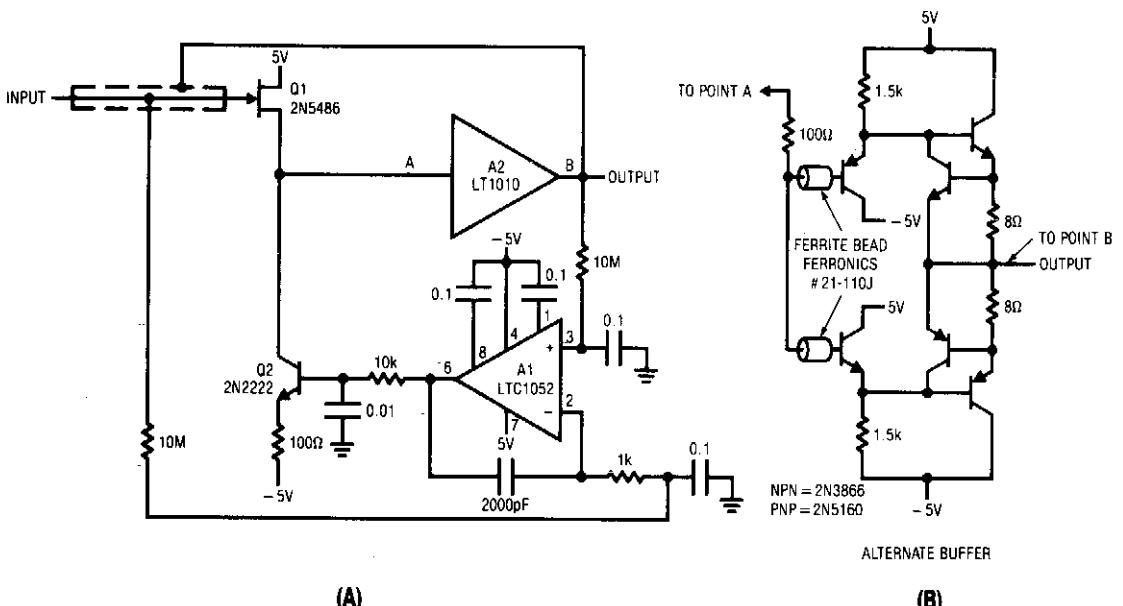
## STABLE UNITY GAIN BUFFER WITH GOOD SPEED AND HIGH INPUT IMPEDANCE




LINEAR TECHNOLOGY CORPORATION

**Fig. 2-1**

### Circuit Notes

Q1 and Q2 constitute a simple, high speed FET input buffer. Q1 functions as a source follower, with the Q2 current source load setting the drain-source channel current. Normally, this open loop configuration would be quite drift because there is no dc feedback. The LTC1052 contributes this function to stabilize the circuit by comparing the filtered circuit output to a similarly filtered version of the input signal. The amplified difference between these signals is used to set Q2's bias and hence Q1's channel current. This forces Q1's  $V_{GS}$  to whatever voltage is required to match the circuit's input and output potentials. The 2000 pF capacitor at A1 provides stable loop compensation. The RC network in A1's output prevents it from seeing high speed edges coupled through Q2's collector-base junction. A2's output is also fed back to the shield around Q1's gate lead, bootstrapping the circuit's effective input capacitance down to less than 1 pF. For very fast requirements, the alternate discrete component buffer shown will be useful. Although its output is current limited at 75 mA, the GHz range transistors employed provide exceptionally wide bandwidth, fast slewing and very little delay.


### CHOPPER STABILIZED AMPLIFIER

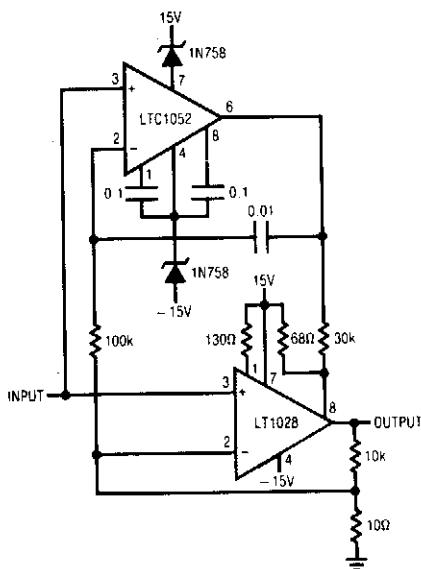

LINEAR TECHNOLOGY CORP.

**Fig. 2-2**

### ULTRA-LOW-LEAKAGE PREAMPLIFIER

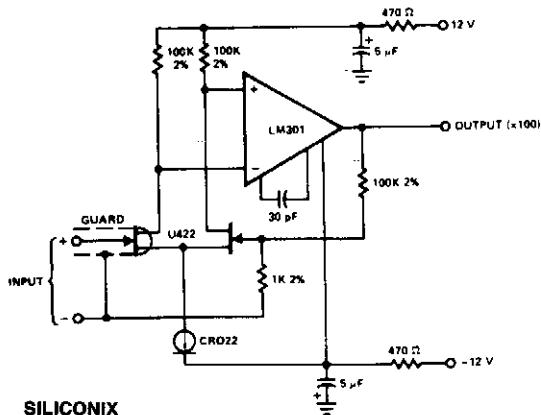


SILICONIX

#### Circuit Notes

The circuit has an input leakage of only 2 pA typical at 75°C and would be usable with 1 M ohm input resistance.

**Fig. 2-3**

### FET INPUT AMPLIFIER

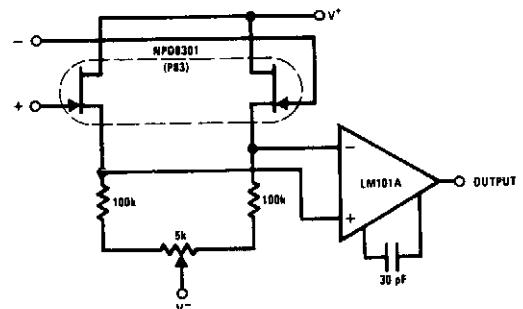


NATIONAL SEMICONDUCTOR CORP.

#### Circuit Notes

The NPD8301 monolithic-dual provides an ideal low offset, low drift buffer function for the LM101A op amp. The excellent matching characteristics of the NPD8301 track well over its bias current range, thus improving common-mode rejection.

**Fig. 2-4**
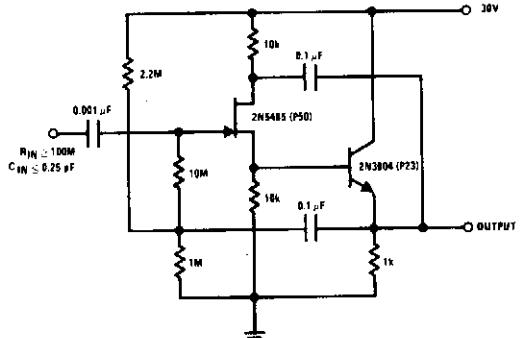
### ULTRA-HIGH $Z_{in}$ AC UNITY GAIN AMPLIFIER




NATIONAL SEMICONDUCTOR CORP.

#### Circuit Notes

Nothing is left to chance in reducing input capacitance. The 2N5485, which has low capacitance in the first place, is operated as a source follower with bootstrapped gate bias resistor and drain.

**Fig. 2-5**

## LOGARITHMIC AMPLIFIER

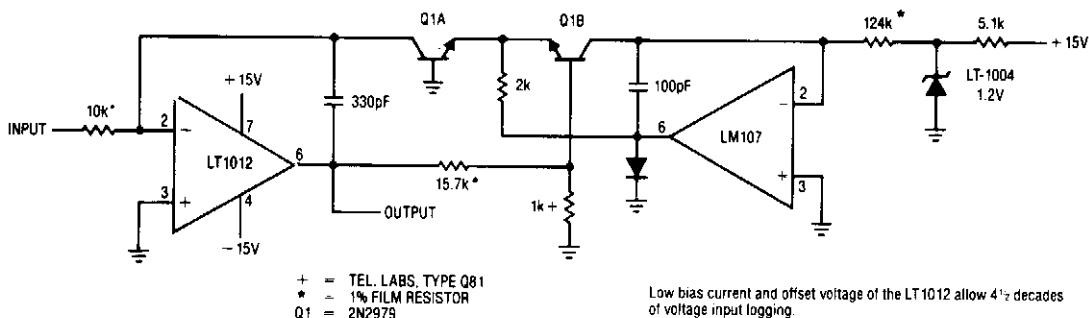

LINEAR TECHNOLOGY CORP.

Fig. 2-6

## COMPOSITE AMPLIFIER

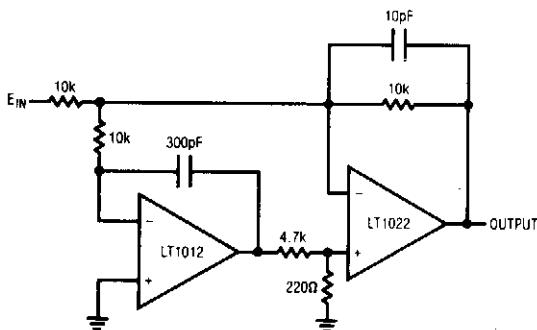


Fig. 2-7

LINEAR TECHNOLOGY CORPORATION

### Circuit Notes

The circuit is made up of an LT1012 low drift device, and an LT1022 high speed amplifier. The overall circuit is a unity gain inverter, with the summing node located at the junction of three 10-k resistors. The LT1012 monitors this summing node, compares it to ground, and drives the LT1022's positive input, completing a dc stabilizing loop around the LT1022. The 10 k - 300 pF time constant at the LT1012 limits its response to low frequency signals. The LT1022 handles high frequency inputs while the LT1012 stabilizes the dc operating point. The 4.7 k - 220 ohm divider at the LT1022 prevents excessive input overdrive during start-up. This circuit combines the LT1012's 35  $\mu\text{V}$  offset and 1.5 V/ $^{\circ}\text{C}$  drift with the LT1022's 23 V/ $\mu\text{s}$  slew rate and 300 kHz full power bandwidth. Bias current, dominated by the LT1012, is about 100 pA.

## STEREO AMPLIFIER WITH GAIN CONTROL

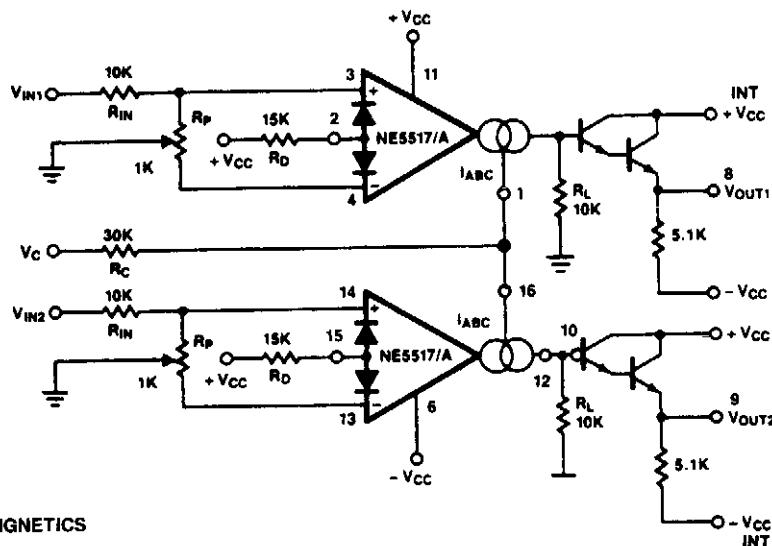


Fig. 2-8

SIGNETICS

### Circuit Notes

Excellent tracking of typical 0.3 dB is easy to achieve. With the potentiometer,  $R_p$ , the offset can be adjusted. For ac-coupled amplifiers, the potentiometer may be replaced with two 5.1 k ohm resistors.

## PRECISION-WEIGHTED RESISTOR PROGRAMMABLE-GAIN AMPLIFIER


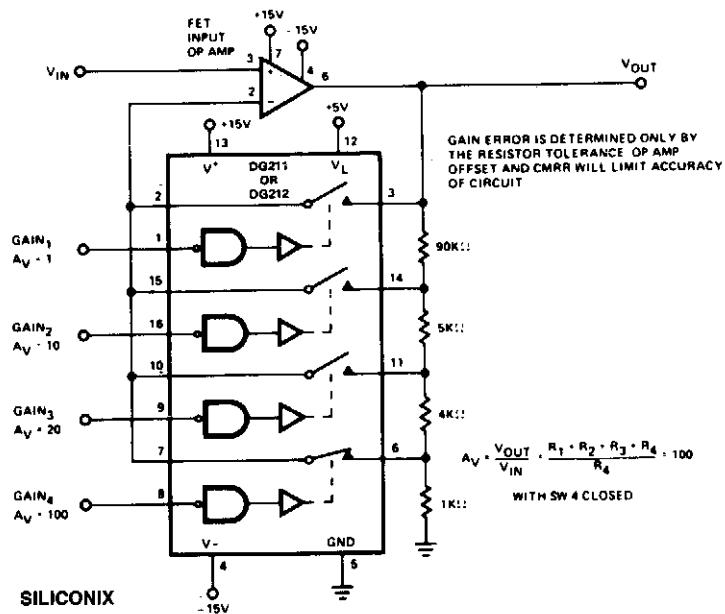


Fig. 2-9

SILICONIX
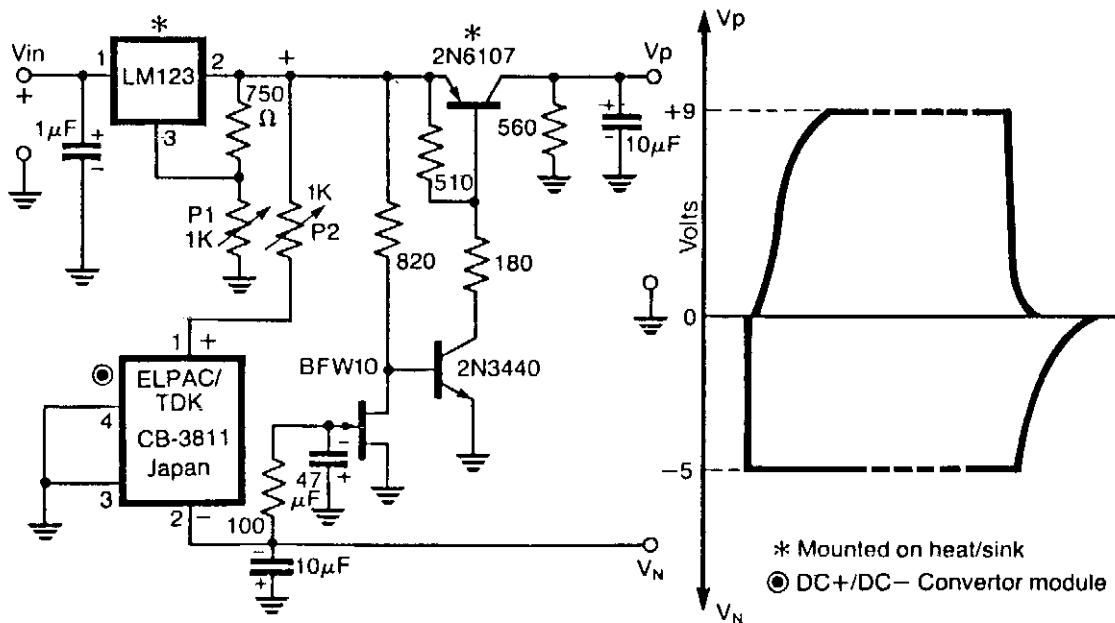
### POWER GaAsFET AMPLIFIER WITH SINGLE SUPPLY




ELECTRIC ENGINEERING

**Fig. 2-10**

#### Circuit Notes

The dual regulator circuit operates from a positive supply, which when switched ON powers the gate first, and when switched OFF shuts off the drain first as shown in the figure. This circuit incorporates the LM123, a three terminal positive regulator and a dc+ to dc- converter, the outputs of which power the drains and gates of the power GaAsFETs in a power amplifier relay. The output of the three terminal regulator drives a dc+ to dc- converter whose output biases an N-channel JFET suitably so as to pull the base of the series pass transistor 2N6107 to a level to turn it on. The circuit will turn off the drain supply whenever the negative potential on the Gate fails.

## LINEAR AMPLIFIERS FROM CMOS INVERTERS

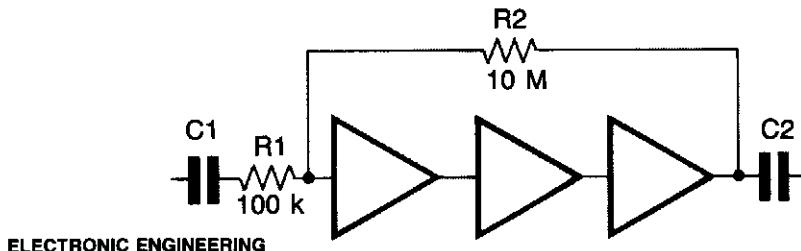


**Fig. 2-11**

### Circuit Notes

CMOS inverters can be used as linear amplifiers if negative feedback is applied. Best linearity is obtained with feedback applied around three inverters which gives almost perfect linearity up to an output swing of 5 V p-p with a 10 V supply rail. The gain is set by the ratio of R<sub>1</sub> and R<sub>2</sub> and the values shown are typical for a gain of 100. The high frequency response with the values shown is almost flat to 20 kHz. The frequency response is determined by C<sub>1</sub> and C<sub>2</sub>. This circuit is not suitable for low level signals because the signal-to-noise ratio is only approx. 50 dB with 5 V p-p output with the values shown.

## CURRENT-COLLECTOR HEAD-AMPLIFIER

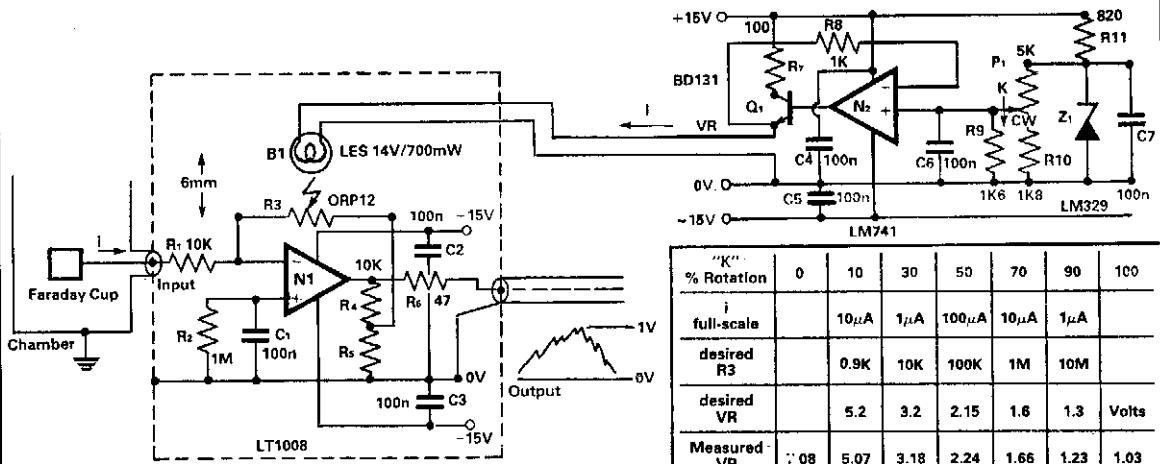


**Fig. 2-12**
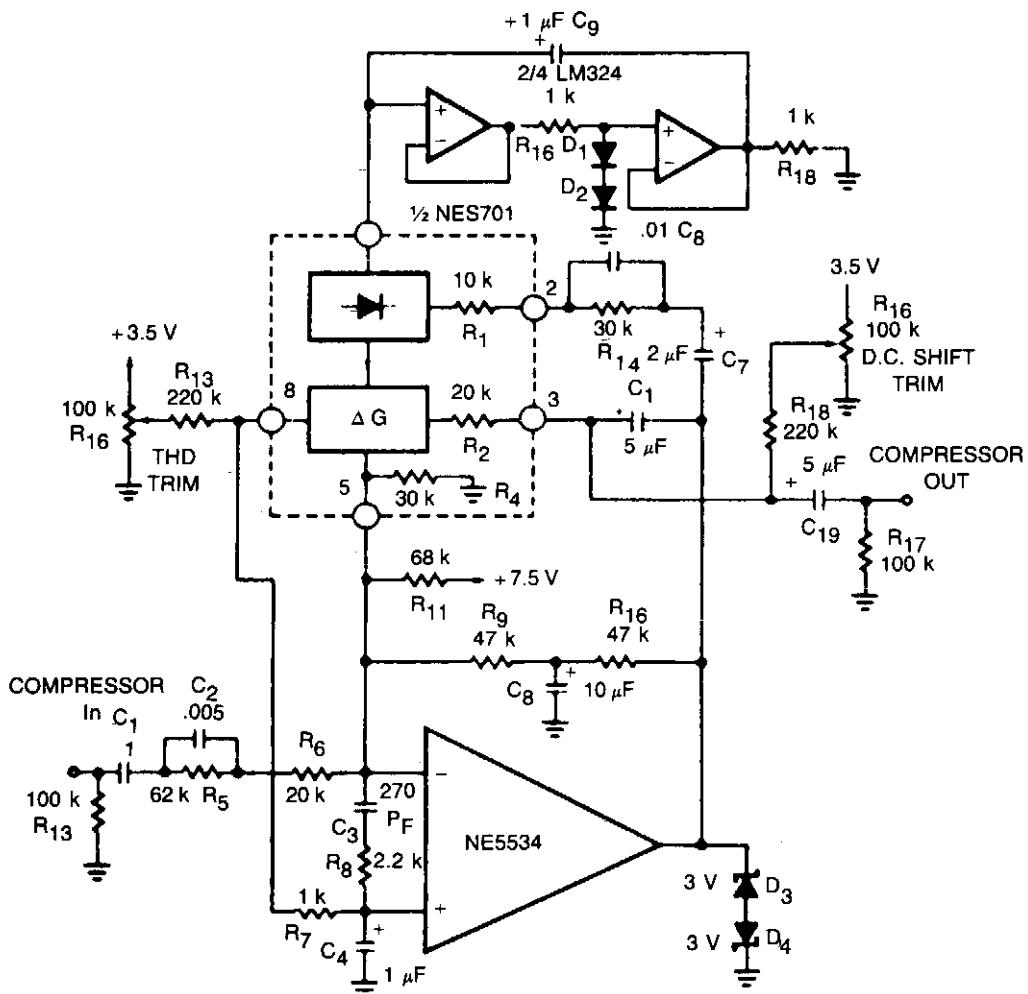
### Circuit Notes

To amplify small current signals such as from an electron-collector inside a vacuum chamber, it is convenient for reasons of noise and bandwidth to have a "head-amplifier" attached to the chamber. The op-amp N<sub>1</sub> is a precision bipolar device with extremely low bias current and offset voltage (1) as well as low noise, which allows the 100:1 feedback attenuator to be employed. The resistance of R<sub>3</sub> can be varied from above 10 M to below 1 k, and so the nominal 0 to 1 V-peak output signal corresponds to input current ranges of 1 nA to 10 μA.

## HI-FI COMPANDER



SIGNETICS


HI-FI Compressor With Pre-emphasis

TC0721S  
**Fig. 2-13(A)**

### Circuit Notes

This circuit for a high fidelity compressor uses an external op amp, and has a high gain and wide bandwidth. An input compensation network is required for stability. The rectifier

capacitor ( $C_9$ ) is not grounded, but is tied to the output of an op amp circuit. When a compressor is operating at high gain, (small input signal), and is suddenly hit with a signal, it will overload until

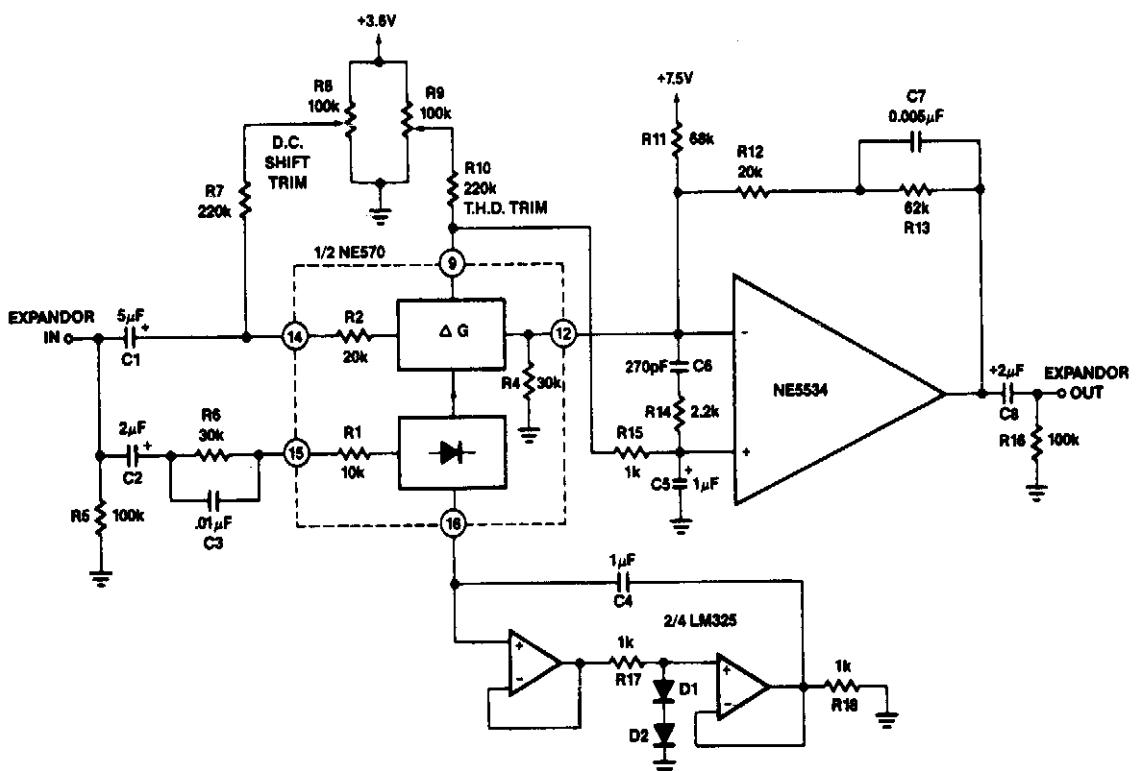

TC07250S

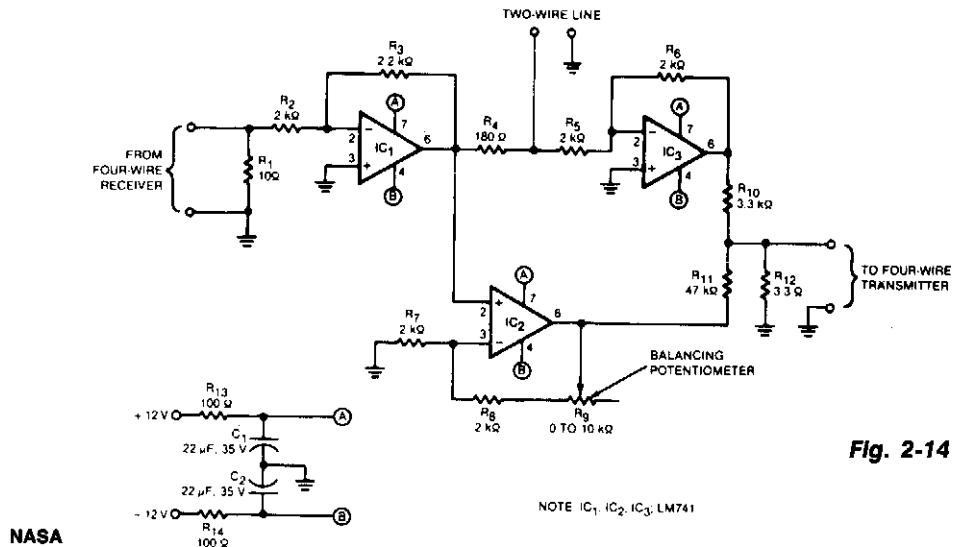
Hi-Fi Expander With De-emphasis

Fig. 2-13(B)

it can reduce its gain. The time it takes for the compressor to recover from overload is determined by the rectifier capacitor  $C_9$ . The expander to complement the compressor is shown in Fig. 2-13B. Here an external op amp is used for high slew rate. Both the compressor

and expander have unity gain levels of 0 dB. Trim networks are shown for distortion (THD) and dc shift. The distortion trim should be done first, with an input of 0 dB at 10 kHz. The dc shift should be adjusted for minimum envelope bounce with tone bursts.

## TWO-WIRE TO FOUR-WIRE AUDIO CONVERTER

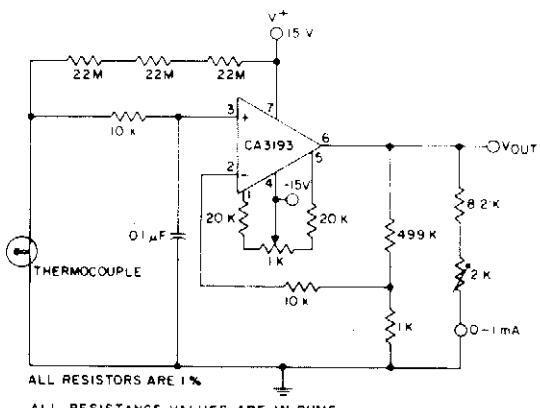


**Fig. 2-14**

### Circuit Notes

This converter circuit maintains 40 dB of isolation between the input and output halves of a four-wire line while permitting a two-wire line to be connected. A balancing potentiometer,  $R_g$ , adjusts the gain of IC2 to null the feed-through from the input to the output. The adjustment is done on the workbench just after assembly by inserting a 1 kHz tone into the four-wire input and setting  $R_g$  for minimum output signal. An 82 ohm dummy-load resistor is placed across the two wire terminals.

## THERMOCOUPLE AMPLIFIER




### Circuit Notes

The circuit uses a CA3193 BiMOS precision op amp to amplify the generated signal 500 times. Three 22-megohm resistors will provide full-scale output if the thermocouple opens.

GENERAL ELECTRIC/RCA

**Fig. 2-15**

## LOW-DISTORTION AUDIO LIMITER

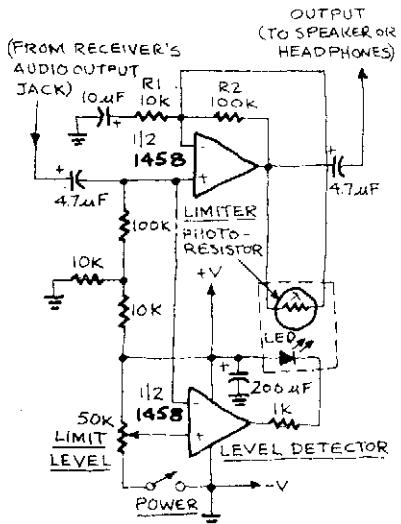

## RADIO-ELECTRONICS

**Fig. 2-16**


Circuit Notes

The level at which the audio limiter comes into action can be set with the LIMIT LEVEL trimmer potentiometer. When that level is exceeded, the output from the LIMITER-DETECTOR half of the op-amp (used as a comparator) turns the LED which causes the resistance of the photoresistor to decrease rapidly. That in turn causes the gain of the LIMITER half of the op-amp to decrease. When the signal drops below the desired limiting level, the LED turns off, the resistance of the photoresistor increases, and the gain of the LIMITER op-amp returns to its normal level—that set by the combination of resistors R1 and R2. A dual-polarity power supply ( $\pm 12$  volts is desirable) is needed for the op-amp.
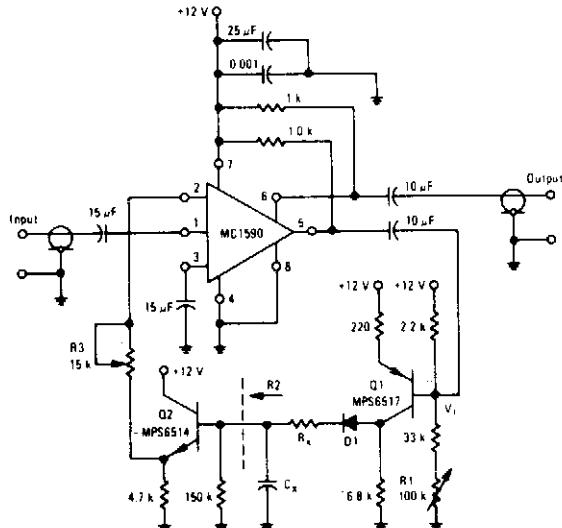
## SPEECH COMPRESSOR

Circuit Notes


The amplifier drives the base of a pnp MPS6517 operating common-emitter with a voltage gain of approximately 20. The control R1 varies the quiescent Q point of this transistor so that varying amounts of signal exceed the level  $V_r$ . Diode D1 rectifies the positive peaks of Q1's output only when these peaks are greater than  $V_r \approx 7.0$  volts. The resulting output is filtered  $C_x$ ,  $R_x$ .  $R_x$  controls the charging time constant or attack time.  $C_x$  is involved in both charge and discharge. R2 (150 K, input resistance of the emitter-follower Q2) controls the decay time. Making the decay long and attack short is accomplished by making  $R_x$  small and R2 large. (A Darlington emitter-follower may be needed if extremely slow decay times are required.) The emitter-follower Q2 drives the AGC Pin 2 of the MC1590 and reduces the gain. R3 controls the slope of signal compression.



MOTOROLA INC.

*Fig. 2-17*

## SPEAKER OVERLOAD PROTECTOR

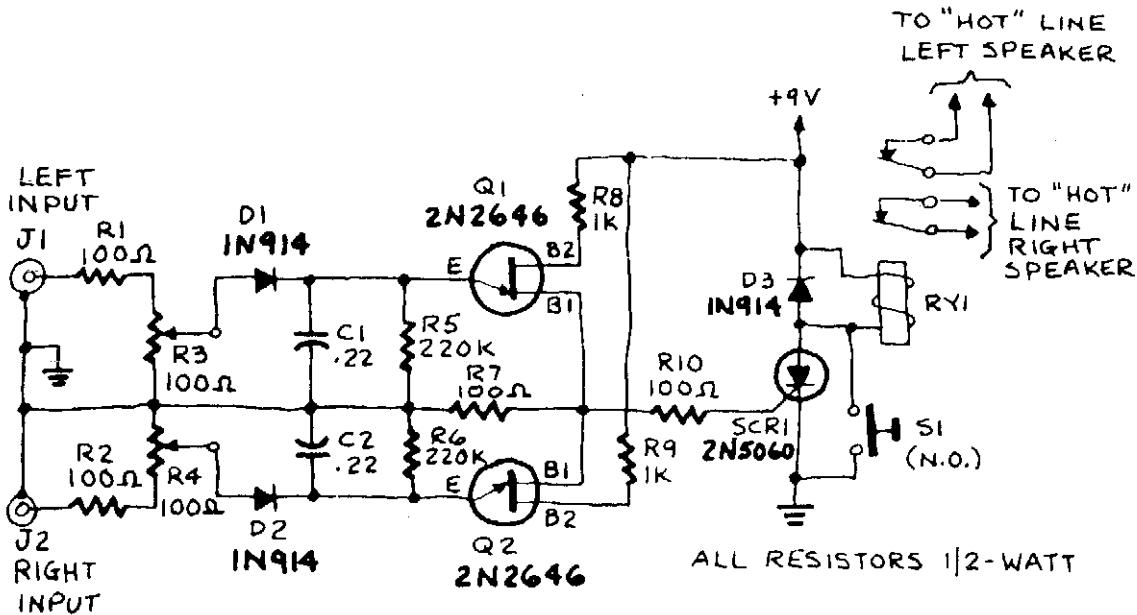


RADIO ELECTRONICS

Fig. 2-18

### Circuit Notes

The input to the circuit is taken from the amplifier's speaker-output terminals or jacks. If the right-channel signal is sufficiently large to charge C1 to a potential that is greater than the breakdown voltage of Q1's emitter, a voltage pulse will appear across R7. Similarly, if the left-channel signal is sufficiently large to charge C2 to a potential that is greater than the breakdown voltage of Q2's emitter, a pulse will appear across R7. The pulse across R7 triggers SCR1, a sensitive gate SCR ( $I_{GT}$  less than 15 mA where  $I_{GT}$  is the gate trigger-current), that latches in a conducting state and energizes RY1. The action of the relay will interrupt both speaker circuits, and the resulting silence should alert you to the problem. Cut back the volume on your amplifier, then press and release S1 to reset the circuit and restore normal operation. The circuit can be adjusted to trip at any level from 15 to 150 watts RMS. To calibrate, deliberately feed an excessive signal to the right input of the speaker protector and adjust R3 until RY1 energizes. Do the same with the left channel, this time adjusting R4. The circuit is now calibrated and ready for use.

## AUDIO AUTOMATIC GAIN CONTROL

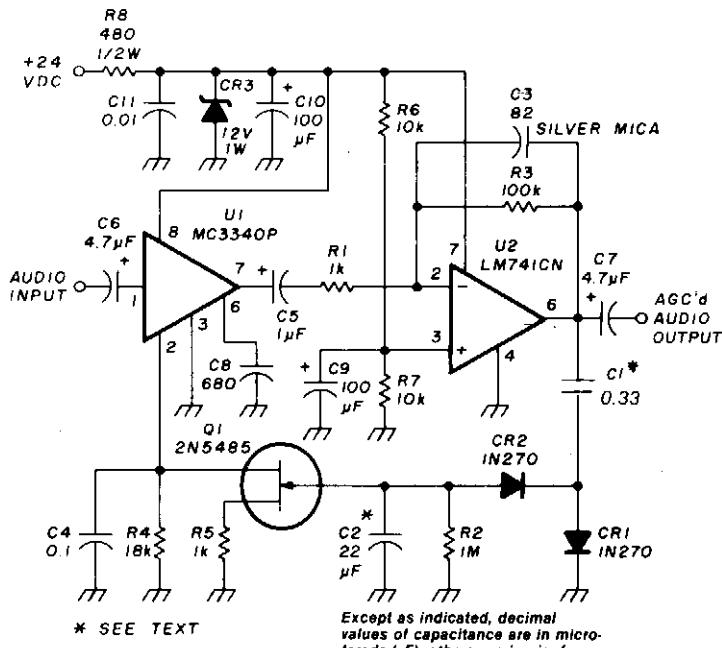

HAM RADIO


**Fig. 2-19**

### Circuit Notes

An audio signal applied to U1 is passed through to the 741 operational amplifier, U2. After being amplified, the output signal of U2 is sampled and applied to a negative voltage doubler/rectifier circuit composed of diodes CR1 and CR2 along with capacitor C1. The resulting negative voltage is used as a control voltage that is applied to the gate of the 2N5485 JFET Q1. Capacitor C2 and resistor R2 form a smoothing filter for the rectified audio control voltage.

The JFET is connected from pin 2 of the MC3340P to ground through a 1 kilohm resistor. As the voltage applied to the gate of the JFET becomes more negative in magnitude, the channel resistance of the JFET increases causing the JFET to operate as a voltage controlled resistor. The MC3340P audio attenuator is the heart of the AGC. It is capable of 13 dB gain or nearly -80 dB of attenuation depending on the external resistance placed between pin 2 and ground. An increase of resistance decreases the gain achieved through the MC3340P. The circuit gain is not entirely a linear function of the external resistance but approximates such behavior over a good portion of the gain/attenuation range. An input signal applied to the AGC input will cause the gate voltage of the JFET to become proportionally negative. As a result the JFET increases the resistance from pin 2 to ground of the MC3340P causing a reduction in gain. In this way the AGC output is held at a nearly constant level.

## VOLTAGE-CONTROLLED ATTENUATOR

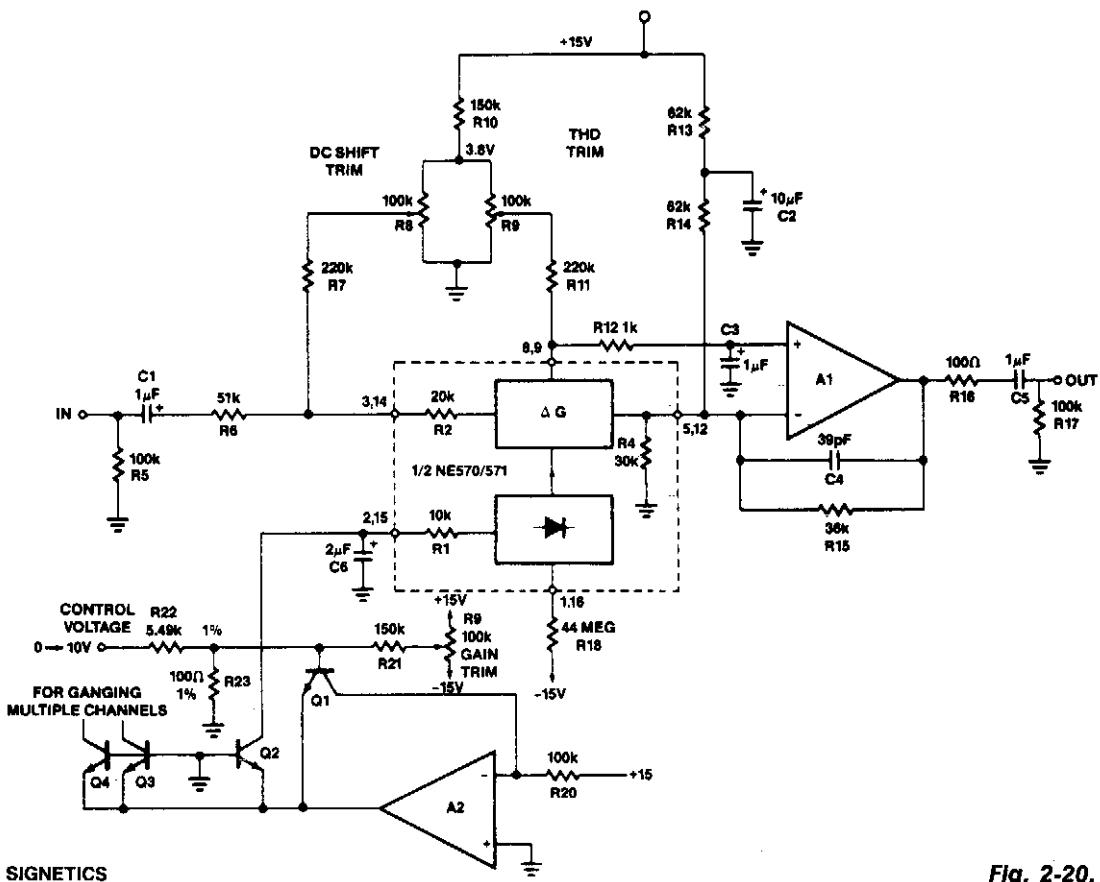


**Fig. 2-20.**
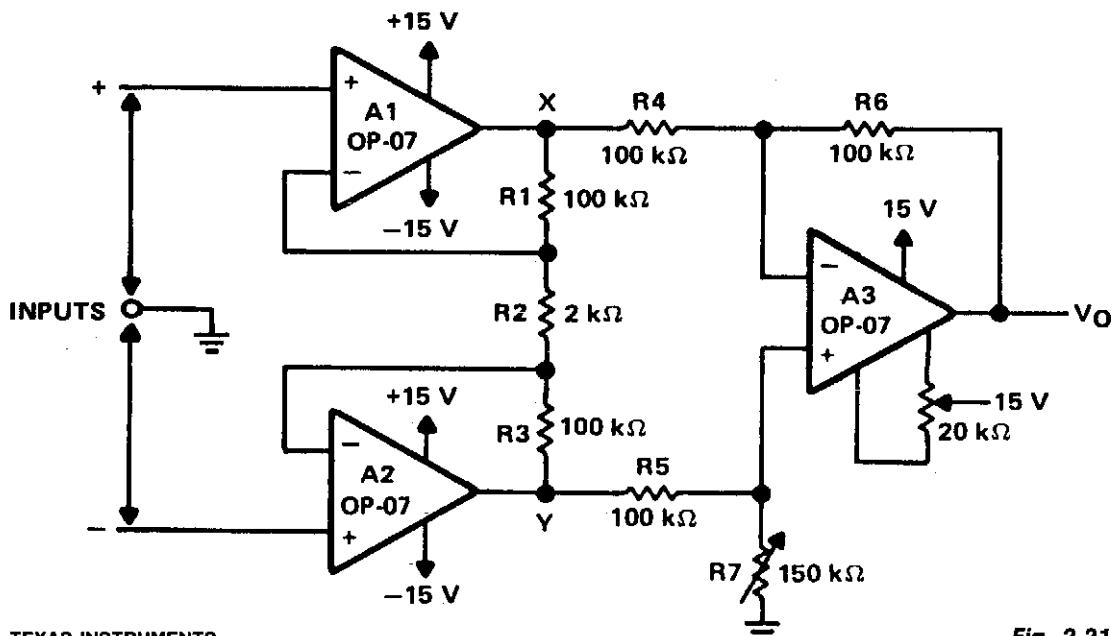
### Circuit Notes

Op amp  $A_2$  and transistors  $Q_1$  and  $Q_2$  form the exponential converter generating an exponential gain control current, which is fed into the rectifier. A reference current of  $150 \mu\text{A}$ , ( $15 \text{ V}$  and  $R_{20} = 100 \text{ k}$ ), is attenuated a factor of two (6 dB) for every volt increase in the control voltage. Capacitor  $C_6$  slows down gain changes to a 20 ms time constant ( $C_6 \times R_1$ ) so that an abrupt change in the control voltage will produce a smooth sounding gain change.  $R_{18}$  ensures that for large control voltages the circuit will go to full attenuation. The rectifier bias current would normally limit the gain reduction to about 70 dB.  $R_{16}$  draws excess current out of the rectifier. After approximately 50 dB of attenuation at a  $-6 \text{ dB/V}$  slope, the slope steepens and attenuation becomes much more rapid until the circuit totally shuts off at about 9 V of control voltage.  $A_1$  should be a low-noise high slew rate op amp.  $R_{13}$  and  $R_{14}$  establish approximately a 0 V bias at  $A_1$ 's output.

## HIGH-INPUT-IMPEDANCE DIFFERENTIAL AMPLIFIER



TEXAS INSTRUMENTS

Fig. 2-21

### Circuit Notes

Operational amplifiers A1 and A2 are connected in a non-inverting configuration with their outputs driving amplifier A3. Operational amplifier A3 could be called a subtractor circuit which converts the differential signal floating between points X and Y into a single-ended output voltage. Although not mandatory, amplifier A3 is usually operated at unity gain and R4, R5, R6, and R7 are all equal.

The common-mode-rejection of amplifier A3 is a function of how closely the ratio R4:R5 matches the ratio R6:R7. For example, when using resistors with 0.1% tolerance, common-mode rejection is greater than 60 dB. Additional improvement can be attained by using a potentiometer (slightly higher in value than R6) for R7. The potentiometer can be adjusted for the best common-mode rejection. Input amplifiers A1 and A2 will have some differential gain but the common-mode input voltages will experience only unity gain. These voltages will not appear as differential signals at the input of amplifier A3 because, when they appear at equal levels on both ends of resistor R2, they are effectively canceled.

This type of low-level differential amplifier finds widespread use in signal processing. It is also useful for dc and low-frequency signals commonly received from a transducer or thermocouple output, which are amplified and transmitted in a single-ended mode. The amplifier is powered by  $\pm 15$  V supplies. It is only necessary to null the input offset voltage of the output amplifier A3.

## AUDIO Q-MULTIPLIER

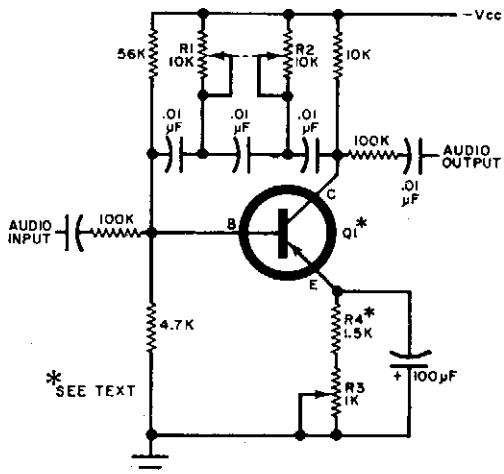


Fig. 2-22

## Circuit Notes

This circuit is for selective tuning between two closely spaced audio tones. The selective frequency is dependent on the value of capacitors and resistors in the feedback circuit between the collector and base of Q1. With the values shown, the frequency can be "tuned" a hundred cycles or so around 650 Hz. R1 and R2 must be ganged. Emitter potentiometer R3 determines the sharpness of response curve. Any transistor having a beta greater than 50 can be used. Select a value for R4 so that the circuit will not oscillate when R3 is set for minimum bandwidth (sharpest tuning).

## AUTOMATIC LEVEL CONTROL


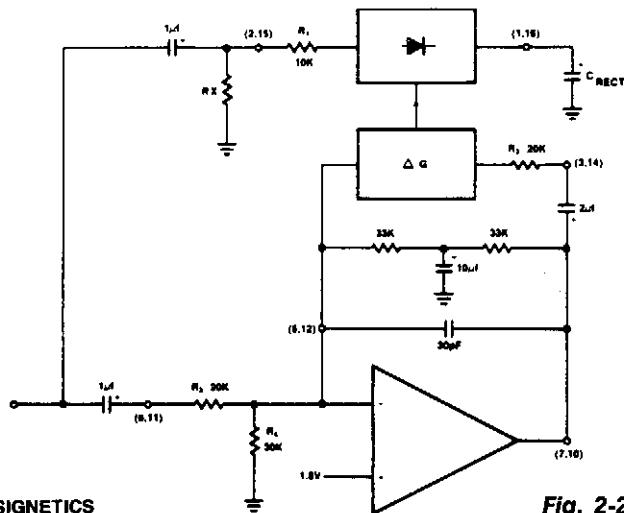


Fig. 2-23

## Circuit Notes

The NE570 can be used to make a very high performance ALC compressor, except that the rectifier input is tied to the input. This makes gain inversely proportional to input level so that a 20 dB drop in input level will produce a 20 dB increase in gain. The output will remain fixed at a constant level. As shown, the circuit will maintain an output level of  $\pm 1$  dB for an input range of +14 to -43 dB at 1 kHz. Additional external components will allow the output level to be adjusted.
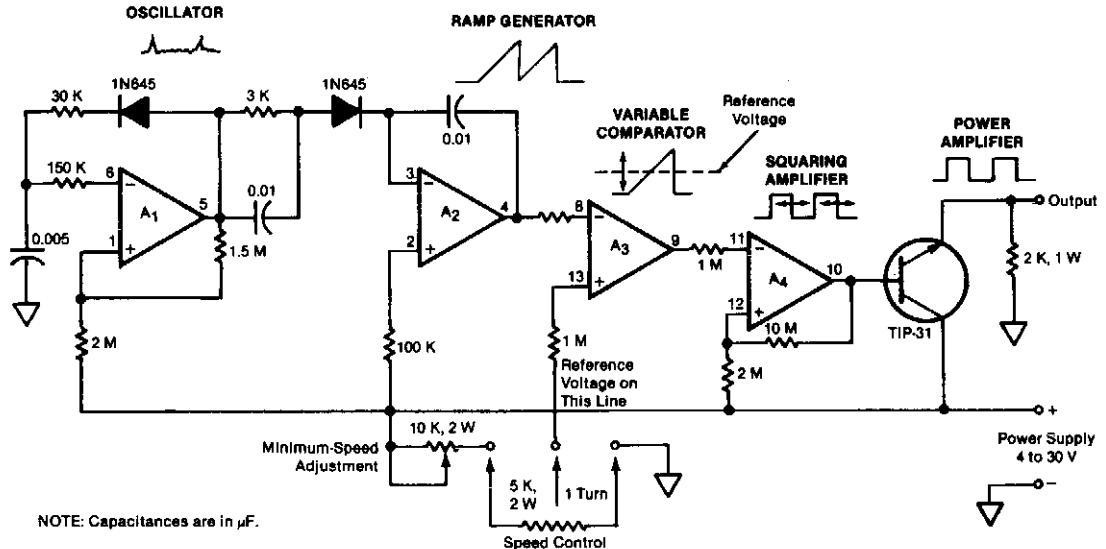
## PULSE-WIDTH PROPORTIONAL-CONTROLLER CIRCUIT




NASA

Fig. 2-24

### Circuit Notes

The quad operational amplifier circuit yields full 0 to 100 percent pulse-width control. The controller uses an LM3900 that requires only a single supply voltage of 4 to 30 V. The pulse-repetition rate is set by a 1 kHz oscillator that incorporates amplifier A<sub>1</sub>. The oscillator feeds ramp generator A<sub>2</sub>, which generates a linear ramp voltage for each oscillator pulse. The ramp signal feeds the inverting input of comparator A<sub>3</sub>; the speed-control voltage feeds the noninverting input. Thus, the output of the comparator is a 1 kHz pulse train, the pulse width of which changes linearly with the control voltage. The control voltage can be provided by an adjustable potentiometer or by an external source of feedback information such as a motor-speed sensing circuit. Depending on the control-voltage setting, the pulse duration can be set at any value from zero (for zero average dc voltage applied to the motor) to the full pulse-repetition period (for applied motor voltage equal to dc power-supply voltage). An amplifier stage (A<sub>4</sub>) with a gain of 10 acts as a pulse-squaring circuit. A TIP-31 medium-power transistor is driven by A<sub>4</sub> and serves as a separate power-amplifier stage.

### OP AMP CLAMPING

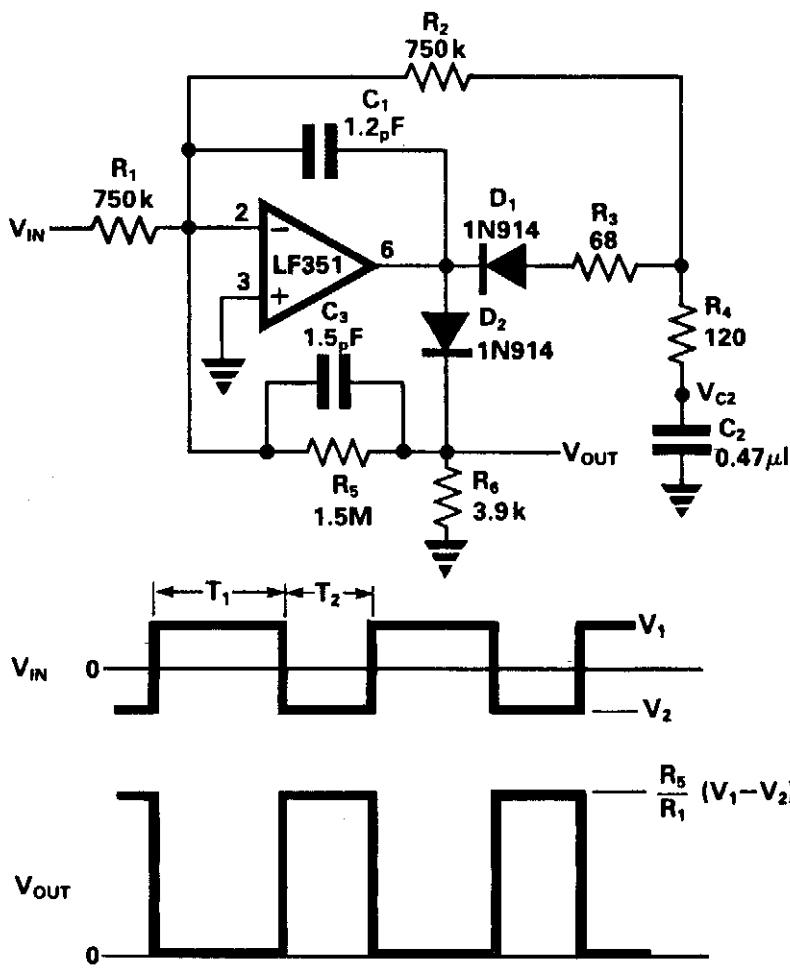

ELECTRONIC ENGINEERING

*Fig. 2-25*

#### Circuit Notes

The circuit clamps the most positive value of the input pulse signal to the zero base level. Additionally, the circuit inverts and amplifies the input signal by the factor of  $R_5/R_1$ . The waveforms are shown in the bottom of Fig. 2-24.

# 3

## Analog-to-Digital Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Successive Approximation A/D Converters
- 4 Digit (10,000 Count) A/D Converter
- 16-Bit A/D Converter
- Inexpensive, Fast 10-Bit Serial Output A/D
- 10-Bit A/D Converter
- High Speed 12-Bit A/D Converter
- Successive Approximation A/D Converter
- Cyclic A/D Converter
- Differential Input A/D System

## SUCCESSIVE APPROXIMATION A/D CONVERTERS

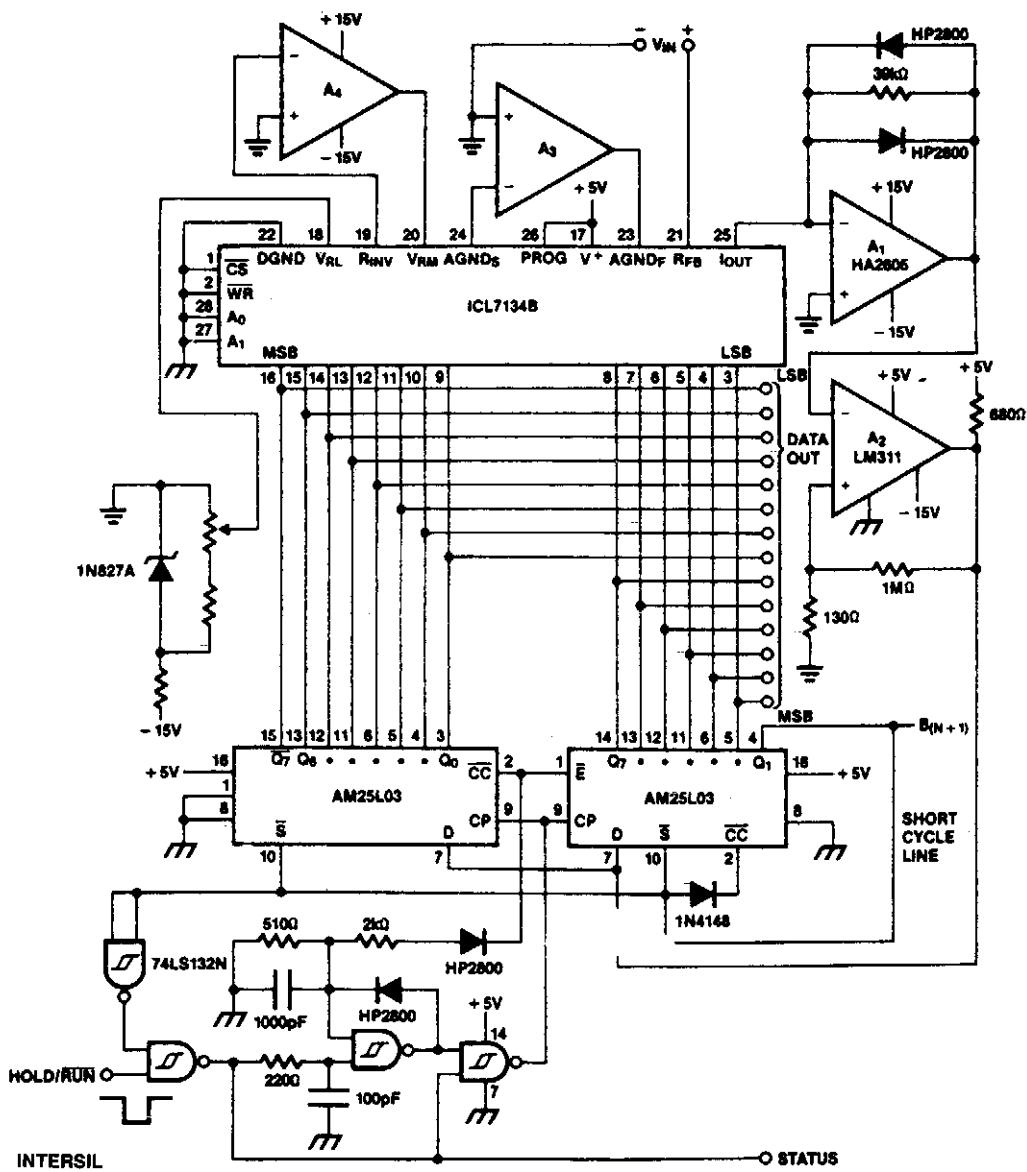



Fig. 3-1

## SUCCESSIVE APPROXIMATION A/D CONVERTERS , Continued.

### Circuit Notes

The ICL7134B-based circuit is for a bipolar-input high-speed A/D converter, using two AM25L03s to form a 14-bit successive approximation register. The comparator is a two-stage circuit with an HA2605 front-end amplifier, used to reduce settling time problems at the summing node (see A020). Careful offset-nulling of this amplifier is needed, and if wide temperature range operation is desired, an auto-null circuit using an ICL7650 is probably advisable (see A053). The clock, using two Schmitt trigger TTL gates, runs at a slower rate for the first 8 bits, where settling-time is most critical than for the last 6 bits. The short-cycle line is shown tied to the 15th bit; if fewer bits are required, it can be moved up accordingly. The circuit will free-run if the HOLD/RUN input is held low, but will stop after completing a conversion if the pin is high at that time. A low-going pulse will restart it. The STATUS output indicates when the device is operating, and the falling edge indicates the availability of new data. A unipolar version can be constructed by tying the MSB (D13) on an ICL7134U to pin 14 on the first AM25L03, deleting the reference inversion amplifier A4, and tying  $V_{RFM}$  to  $V_{RFL}$ .


### 4 DIGIT (10,000 COUNT) A/D CONVERTER

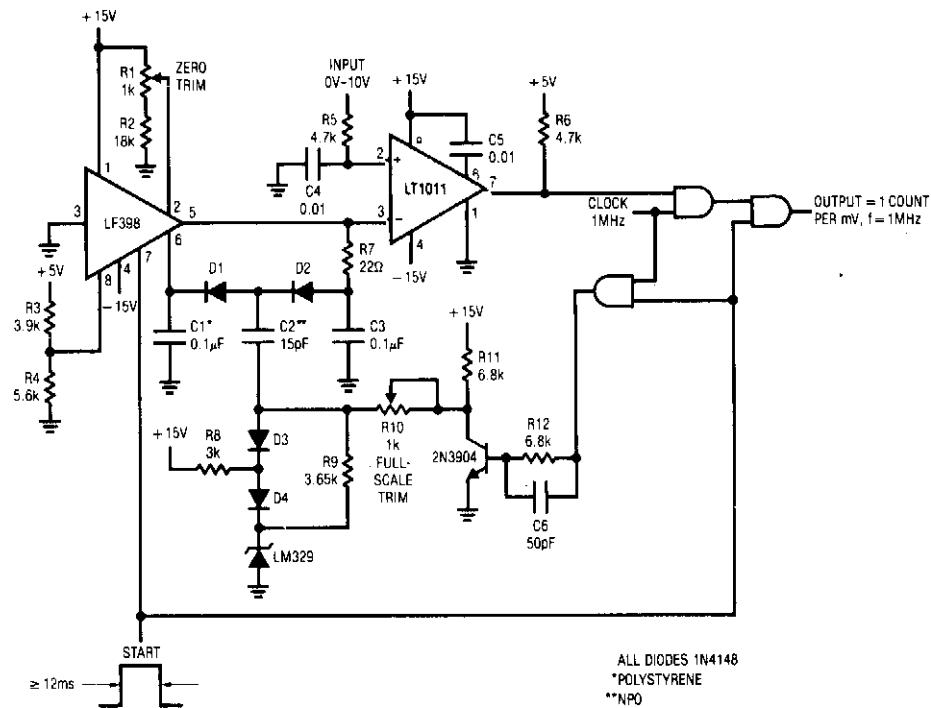

LINEAR TECHNOLOGY CORP.

Fig. 3-2

## 16-BIT A/D CONVERTER

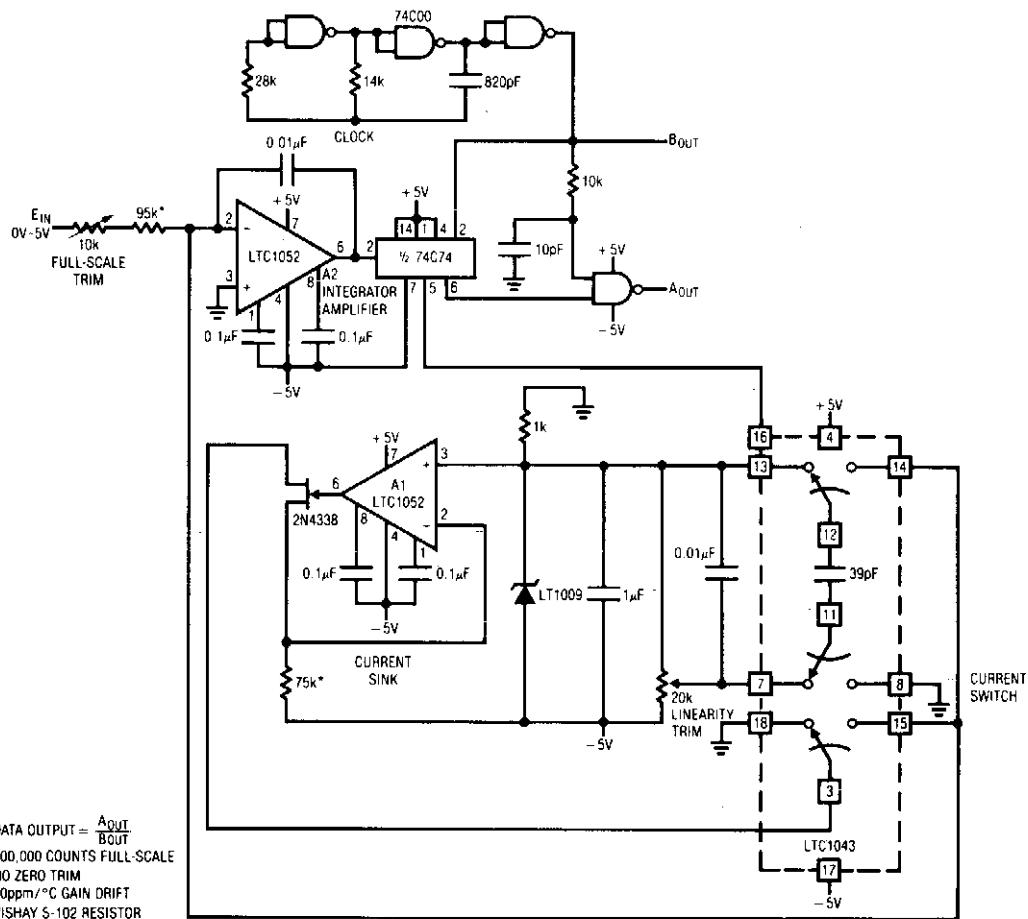


LINEAR TECHNOLOGY

**Fig. 3-3**

### Circuit Notes

The A/D converter, made up of A2, a flip-flop, some gates and a current sink, is based on a current balancing technique. Once again, the chopper-stabilized LTC1052's 50 nV/°C input drift is required to eliminate offset errors in the A/D.
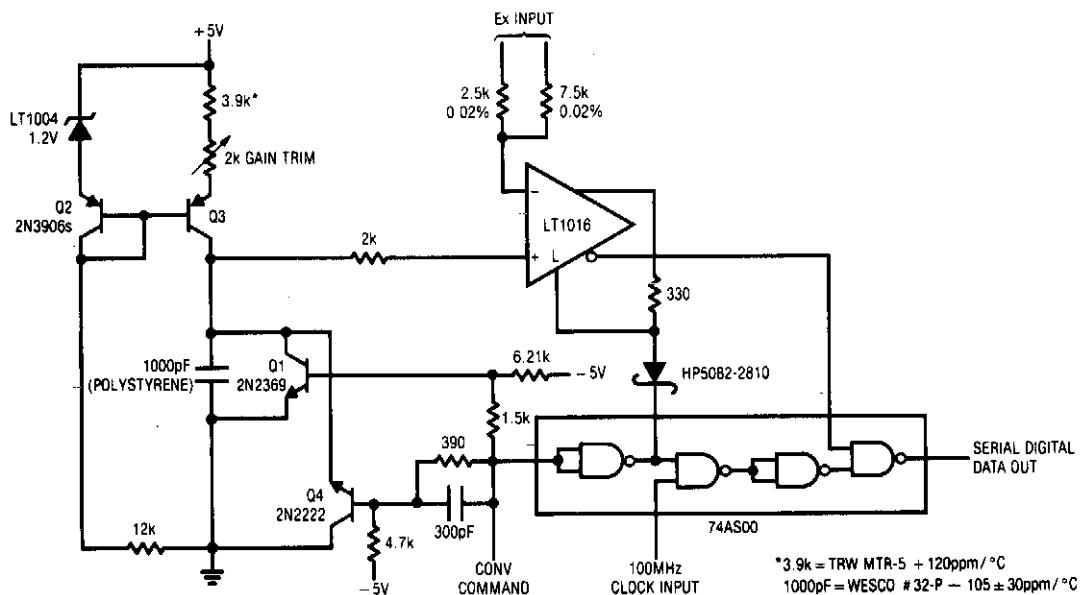
## INEXPENSIVE, FAST 10-BIT SERIAL OUTPUT A/D




LINEAR TECHNOLOGY CORPORATION

**Fig. 3-4**

### Circuit Notes

Everytime a pulse is applied to the convert command input, Q1 resets the 1000 pF capacitor to 0 V. This resetting action takes 200 ns of the falling edge of the convert command pulse, the capacitor begins to charge linearly. In precisely 10 microseconds, it charges to 2.5 V. The 10 microseconds ramp is applied to the LT1016's positive input. The LT1016 compares the ramp to Ex, the unknown, at its negative input. For a 0 V - 2.5 V range, Ex is applied to the 2.5 k ohm resistor. From a 0 V - 10 V range, the 2.5 k ohm resistor is grounded and Ex is applied to the 7.5 k ohm resistor. Output of the LT1016 is a pulse whose width is directly dependent on the value of Ex. This pulse width is used to gate a 100 MHz clock. The 100 MHz clock pulse bursts that appear at the output are proportional to Ex. For a 0 V - 10 V input, 1024 pulses appear at full-scale, 512 at 5.00 V, etc.

## 10-BIT A/D CONVERTER

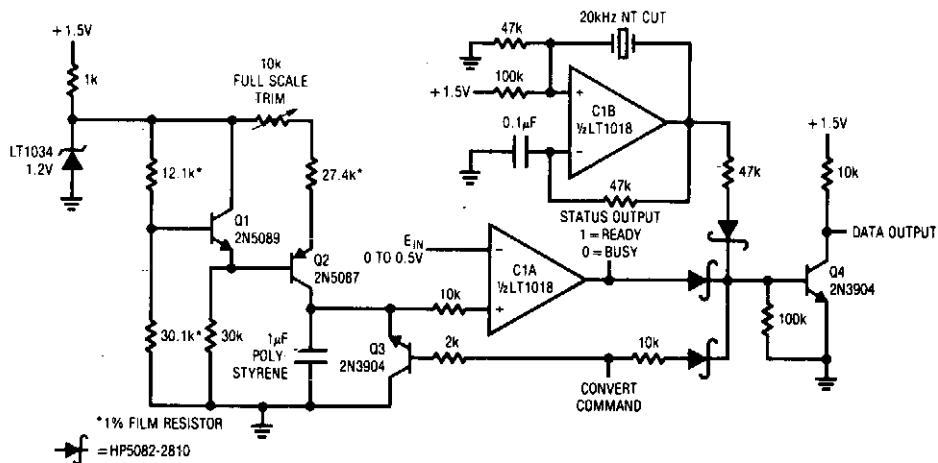


LINEAR TECHNOLOGY CORPORATION

*Fig. 3-5*

### Circuit Notes

The converter has a 60 ms conversion time, consumes 460  $\mu$ A from its 1.5 V supply and maintains 10 bit accuracy over a 15°C to 35°C temperature range. A pulse applied to the convert command line causes Q3, operating in inverted mode, to discharge through the 10 k $\Omega$  diode path, forcing its collector low. Q3's inverted mode switching results in a capacitor discharge within 1 mV of ground. During the time the ramps' value is below the input voltage, CIA's output is low. This allows pulses from C1B, a quartz stabilized oscillator, to modulate Q4. Output data appears at Q4's collector. When the ramp crosses the input voltages value CIA's output goes high, biasing Q4 and output data ceases. The number of pulses at the output is directly proportional to the input voltage. To calibrate apply 0.5 V to the input and trim the 10 k $\Omega$  potentiometer for exactly 1000 pulses out each time the convert command line is pulsed.

## HIGH SPEED 12-BIT A/D CONVERTER

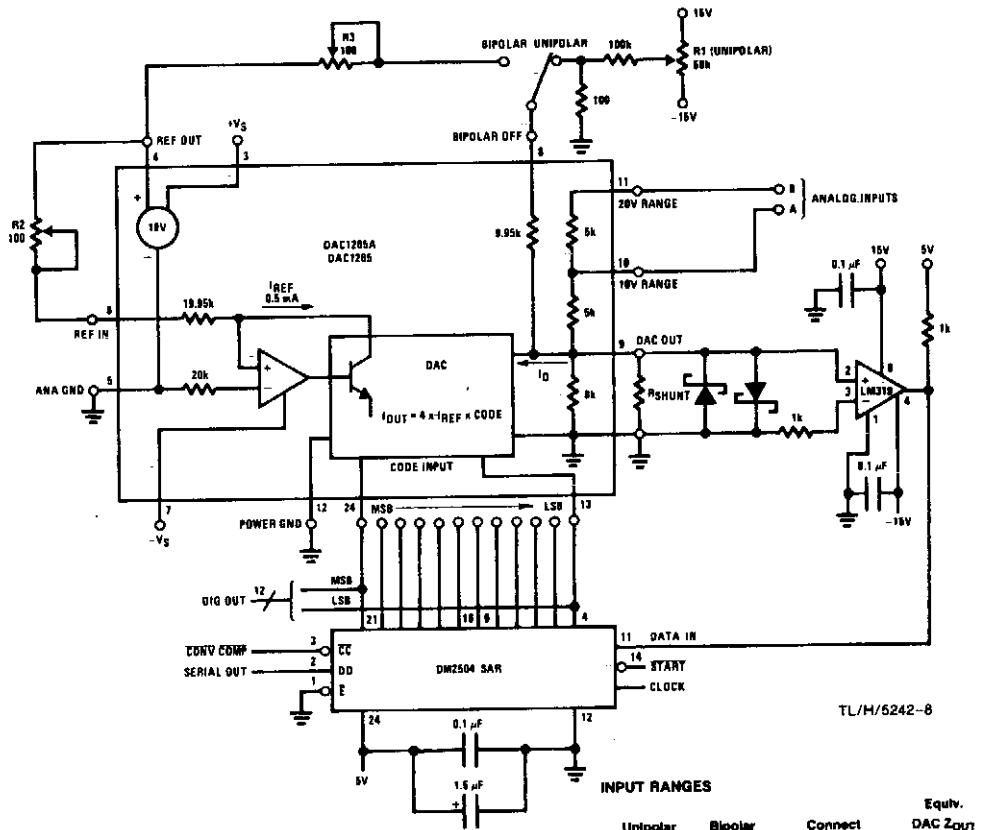

NATIONAL SEMICONDUCTOR CORP.

Fig. 3-6

### Circuit Notes

This system completes a full 12-bit conversion in 10  $\mu$ s unipolar or bipolar. This converter will be accurate to  $\pm \frac{1}{2}$  LSB of 12 bits and have a typical gain TC of 10 ppm/ $^{\circ}$ C. In the unipolar mode, the system range is 0 V to 9.9976 V, with each bit having a value of 2.44 mV. For the true conversion accuracy, an A/D converter should be trimmed so that given bit code output results from input levels from  $\frac{1}{2}$  LSB below to  $\frac{1}{2}$  LSB above the exact voltage which that code represents. Therefore, the converter zero point should be trimmed with an input voltage of 1.22 mV; trim R1 until the LSB just begins to appear in the output code (all other bits "0"). For full-scale, use an input voltage of 9.9963 V (10 V-1 LSB- $\frac{1}{2}$  LSB); then trim R2 until the LSB just begins to appear (all other bits "1"). The bipolar signal range is -5.0 V to 4.9976 V. Bipolar offset trimming is done by applying a -4.9988 V input signal and trimming R3 for the LSB transition (all other bits "0"). Full-scale is set by applying 4.9963 V and trimming R2 for the LSB transition (all other bits "1").

## SUCCESSIVE APPROXIMATION A/D CONVERTER

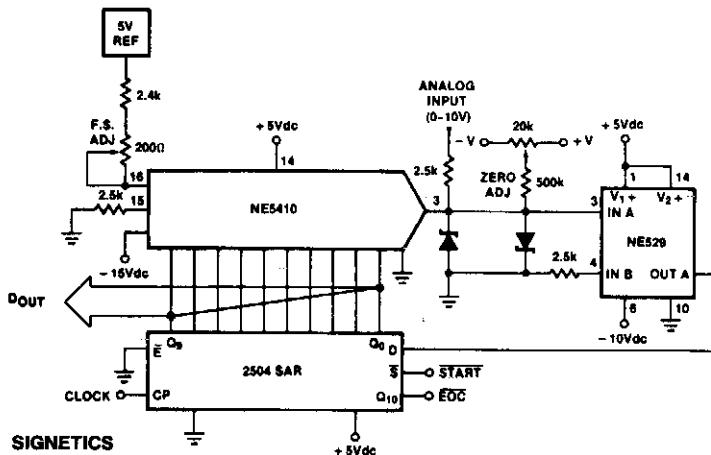


Fig. 3-7

### Circuit Notes

The 10-bit conversion time is  $3.3 \mu\text{s}$  with a 3 MHz clock. This converter uses a 2504 12-bit successive approximation register in the short cycle operating mode where the end of conversion signal is taken from the first unused bit of the SAR ( $Q_{10}$ ).

## CYCLIC A/D CONVERTER


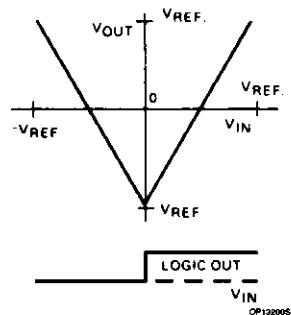
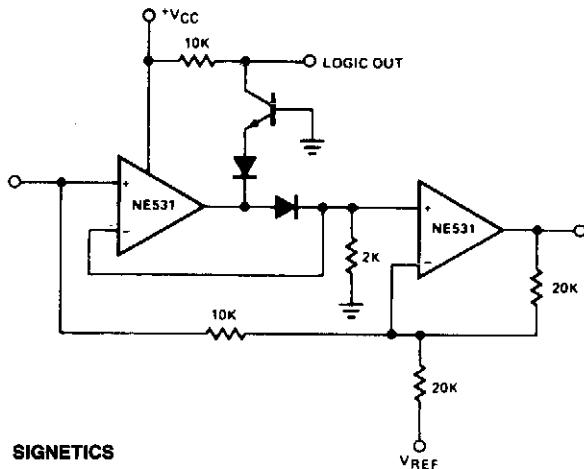


Fig. 3-8

### Circuit Notes

The cyclic converter consists of a chain of identical stages, each of which senses the polarity of the input. The stage then subtracts V<sub>REF</sub> from the input and doubles the remainder if the polarity was correct. The signal is full-wave rectified and the remainder of V<sub>IN</sub> – V<sub>REF</sub> is doubled. A chain of these stages gives the gray code equivalent of the input voltage in digitized form related to the magnitude of V<sub>REF</sub>. Possessing high potential accuracy, the circuit using NE531 devices settles in 5  $\mu\text{s}$ .

## DIFFERENTIAL INPUT A/D SYSTEM

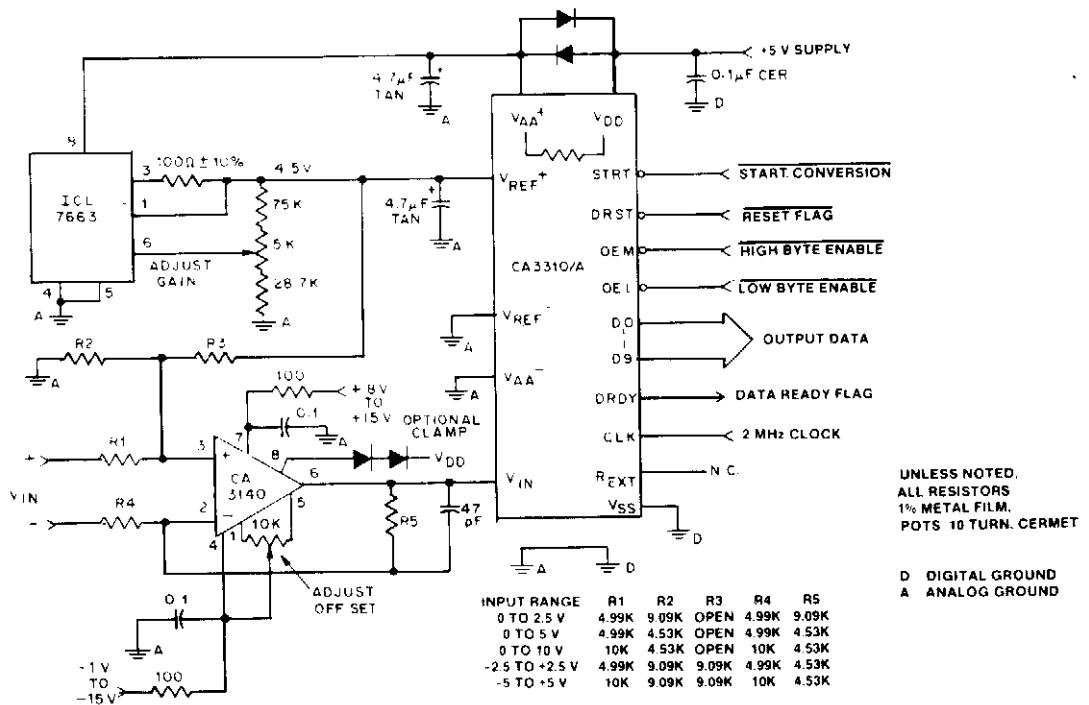

GENERAL ELECTRIC/RCA

**Fig. 3-9**

### Circuit Notes

Using a CA3140 BiMOS op amp provides good slewing capability for high bandwidth input signals, and can quickly settle energy that the CA3310 outputs at its  $V_{IN}$  terminal. The CA3140 can also drive close to the negative supply rail. If system supply sequencing or an unknown input voltage is likely to cause the op amp to drive above the  $V_{DD}$  supply, a diode clamp can be added from pin 8 of the op amp to the  $V_{DD}$  supply.

# **4**

## **Annunciators**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low-Cost Chime Circuit  
Electronic Bell  
Sliding-Tone Doorbell

## LOW-COST CHIME CIRCUIT

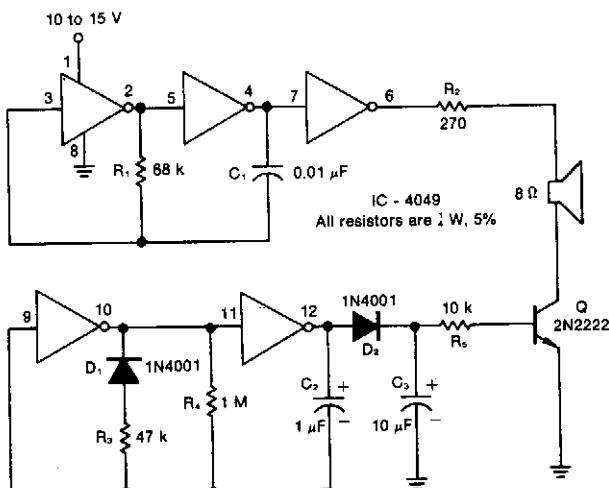


### Circuit Notes

Resistor R1, capacitor C1, and two inverters form a square wave generator, which produces the basic tone. The generator is followed by an inverter that acts as both a buffer and a driver for the speaker. Resistor R2, which has a minimum value of 100 ohms, limits the current and controls the volume. Diode D1, capacitor C2, resistors R3 and R4, and two inverters create the pulse generator that determines the turn-on and decay times of the chime. The decay circuit—formed by D2, C3, R5, and Q—reduces the amplitude of the chime tone exponentially as a function of time.

**Fig. 4-1**

## ELECTRONIC BELL

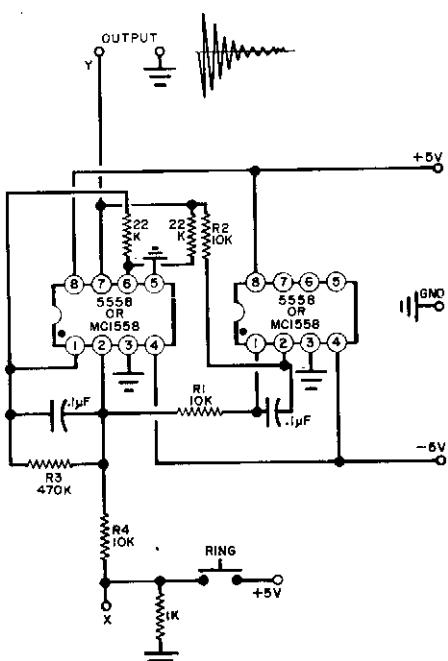

### Circuit Notes

Coarse frequency is controlled by the capacitors which must be kept nearly identical in value to each other for best results. Fine tuning is accomplished with R1 and R2. The decay time is controlled by R3.

**Fig. 4-2**

## SLIDING-TONE DOORBELL

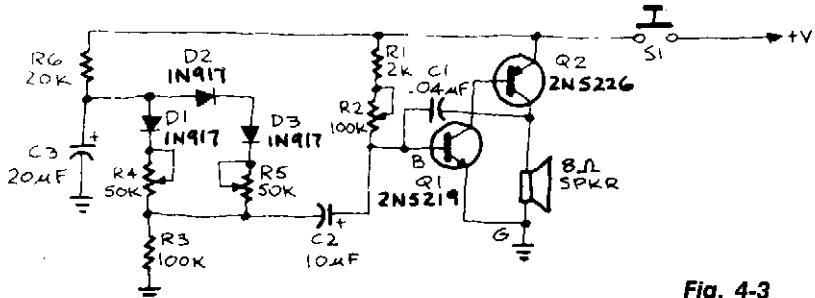


Fig. 4-3

RADIO ELECTRONICS

### Circuit Notes

When the doorbell is pushed, you'll hear a low tone that will "slide up" to a higher frequency. The frequency of the AF oscillator is determined by coupling capacitor, C1 and the value of the resistance connected between the base of Q1 and ground. That resistance,  $R_{BG}$  is equal to  $(R1 + R2) R3$ . First, assume that S1 is closed and R2 has been adjusted to produce a pleasant, low-frequency tone. Capacitor C3 will charge through R6 until it reaches such a voltage that it will cause diode D1 to conduct. When that happens, the value of  $R_{BG}$  is paralleled by R4. Thus, because the total resistance  $R_{BG}$  decrease, the output tone slides up in frequency. Capacitor C3 will continue to charge until the voltage across D2 and D3 causes those diodes to conduct. Then  $R_{BG}$  is paralleled also by R5, the total resistance again decreases, and the oscillator's frequency again increases.

# 5

## **Audio Mixers, Crossovers and Distribution Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Electronic Crossover Circuit
- Sound Mixer Amplifier
- Microphone Mixer
- Low Distortion Input Selector for Audio Use
- Audio Distribution Amplifier
- Four Channel Four Track Mixer

## ELECTRONIC CROSSOVER CIRCUIT

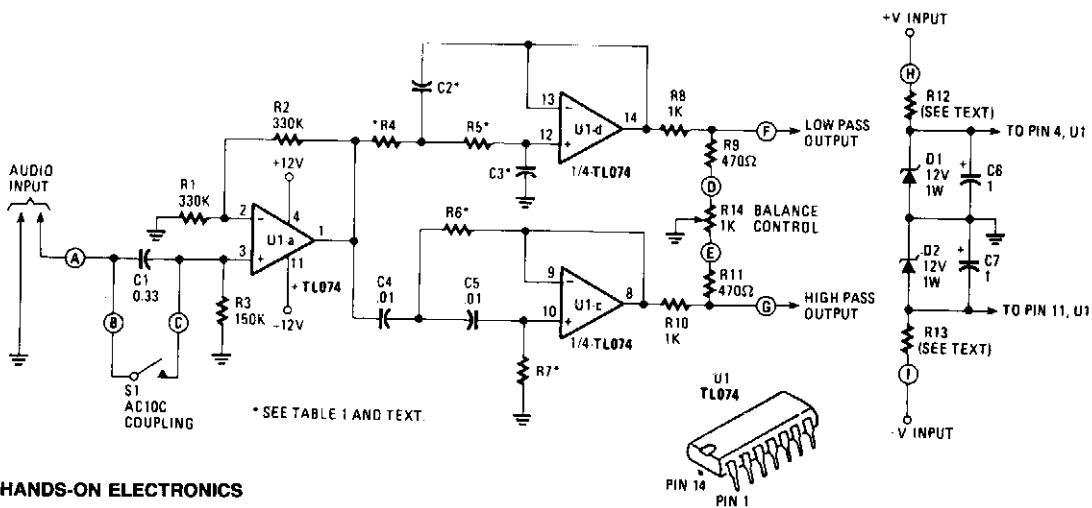


HANDS-ON ELECTRONICS

**Fig. 5-1**

### Circuit Notes

An audio source, such as a mixer, preamplifier, equalizer, or recorder, is fed to the Electronic Crossover Circuit's input. That signal is either ac- or dc-coupled, depending on the setting of switch S1, to the non-inverting input of buffer-amplifier U1a, one section of a quad, BIFET, low-noise TL074 op amp made by Texas Instruments. That stage has a gain of 2, and its output is distributed to both a lowpass filter made by R4, R5, C2, C3, and op-amp U1d, and a highpass filter made by R6, R7, C4, C5, and op amp U1c. Those are 12 dB/octave Butterworth-type filters. The Butterworth filter response was chosen because it gives the best compromise between damping and phase shift. Values of capacitors and resistors will vary with the selected crossover at which your unit will operate. The filter's outputs are fed to a balancing network made by R8, R9, R10, R11 and balance potentiometer R14. When the potentiometer is at its mid-position, there is unity gain for the passbands of both the high and low filters. Dc power for the Electronic Crossover Circuit is regulated by R12, R13, D1, and D2, and decoupled by C6 and C7.

## SOUND MIXER/AMPLIFIER

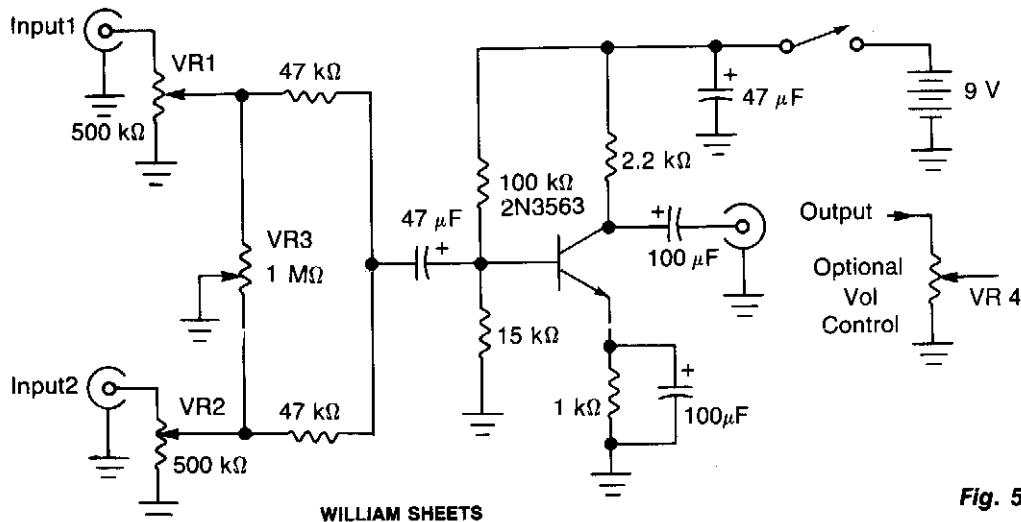


**Fig. 5-2**
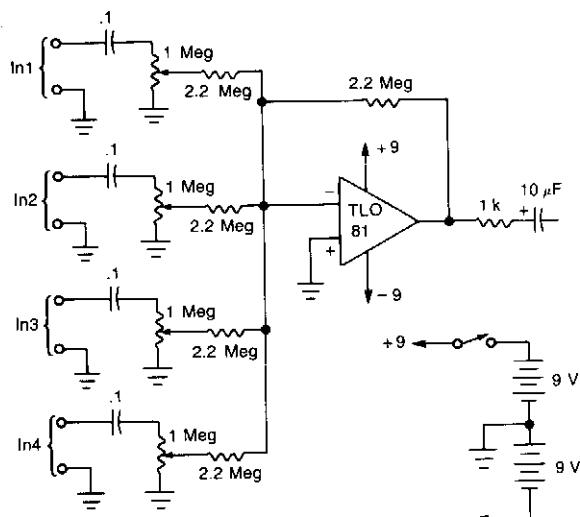
### Circuit Notes

Both input signals can be independently controlled by VR1 and VR2. The balance control VR3 is used to fade out one signal while simultaneously fading in the other. The transistor provides gain and the combined output signal level is controlled by VR4 (optional).

## MICROPHONE MIXER




WILLIAM SHEETS

### Circuit Notes


A TL081 op amp is used as a high-to-low impedance converter and signal mixer. The input impedance is approximately 1 megohm and the output impedance is about 1 kilohm. Two 9-volt batteries are used as the power source. Battery life should be several hundred hours with alkaline batteries.

**Fig. 5-3**
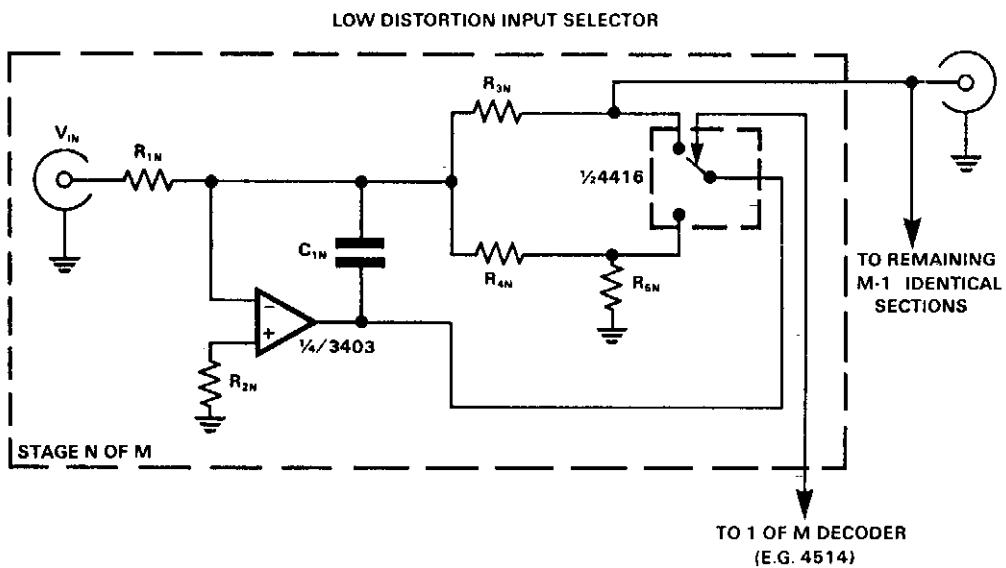
## LOW DISTORTION INPUT SELECTOR FOR AUDIO USE



EQUIVALENT CIRCUIT OF EACH STAGE:

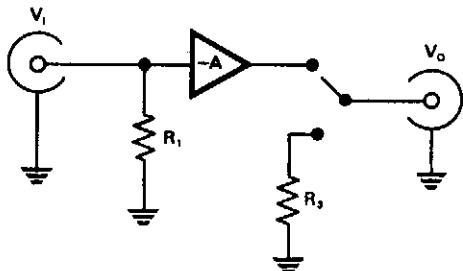

$$R_{3N} = R_{4N} = AR_{1N}$$

$$R_{2N} = (R_{1N} + R_5) // R_{3N} // (R_{4N} + R_{5N})$$

$$\frac{1}{2\pi f_{MAX}} \gg R_{3N} C_{1N} \gg r_s$$

$$R_{6N} = \frac{1}{R_1^{-1} + \sum_{i=1}^M (R_{3i})^{-1}}$$


ELECTRONIC ENGINEERING

**Fig. 5-4**

### Circuit Notes

CMOS switches are used directly to select inputs in audio circuits, this can introduce unacceptable levels of distortion, but if the switch is included in the feedback network of an op amp, the distortion due to the switch can be almost eliminated. The circuit uses a 4416 CMOS switch, arranged as two independent SPDT switches. If switching transients are unimportant, R<sub>5</sub> and C<sub>1</sub> can be omitted, and R<sub>4</sub> can be shorted out. However, a feedback path must be maintained, even when a channel is switched out, in order to keep the inverting input of the op amp at ground potential, and prevent excessive crosstalk between channels.

## AUDIO DISTRIBUTION AMPLIFIER

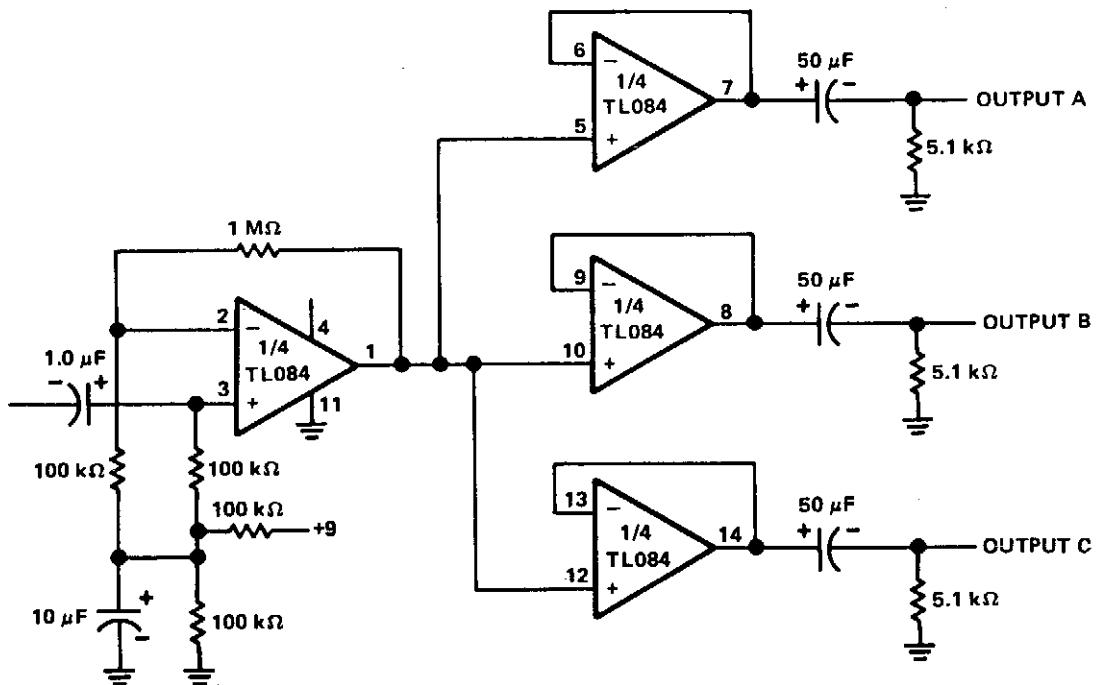


TEXAS INSTRUMENTS

*Fig. 5-5*

### Circuit Notes

The three channel output distribution amplifier uses a single TL084. The first stage is capacitively coupled with a  $1.0\ \mu\text{F}$  electrolytic capacitor. The inputs are at  $\frac{1}{2} V_{CC}$  rail or 4.5 V. This makes it possible to use a single 9 V supply. A voltage gain of 10 ( $1\ \text{M}\ \Omega/100\ \text{k}\ \Omega$ ) is obtained in the first stage, and the other three stages are connected as unity-gain voltage followers. Each output stage independently drives an amplifier through the  $50\ \mu\text{F}$  output capacitor to the  $5.1\ \text{k}\ \Omega$  load resistor. The response is flat from 10 Hz to 30 kHz.

## FOUR CHANNEL FOUR TRACK MIXER

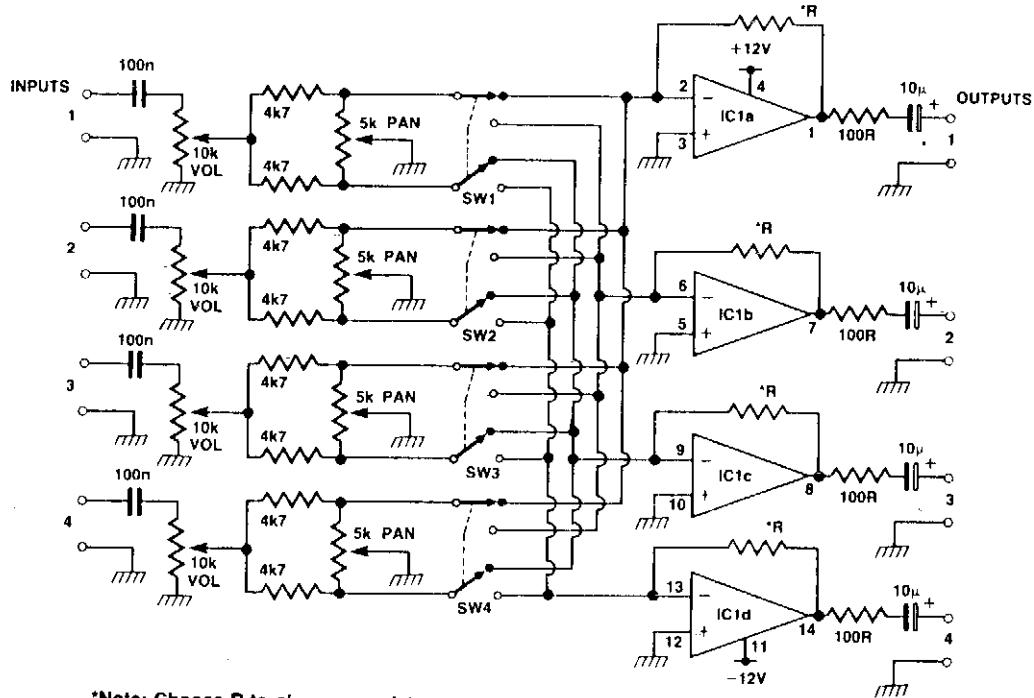

\*Note: Choose R to give appropriate gain.

ELECTRONICS TODAY INTERNATIONAL

**Fig. 5-6**

### Circuit Notes

This circuit can be used as a stereo mixer as well as a four track. The quad op-amp IC gives a bit of gain for each track. The pan control allows panning between tracks one and two with the switch in the up position, and with the switch in the down position, it makes possible panning between tracks three and four. Extra channels can be added. A suitable op amp for IC1 is TL074 or similar.

# **6**

## **Audio Signal Amplifiers**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Auto Fade
- Transistor Headphone Amplifier
- Stereo Preamplifier
- Audio Compressor
- Micropower High-Input-Impedance 20-dB Amplifier
- Stereo Preamplifier
- Microphone Preamplifier
- Volume, Balance, Loudness & Power Amps
- Balance and Loudness Amplifier

## AUTO FADE

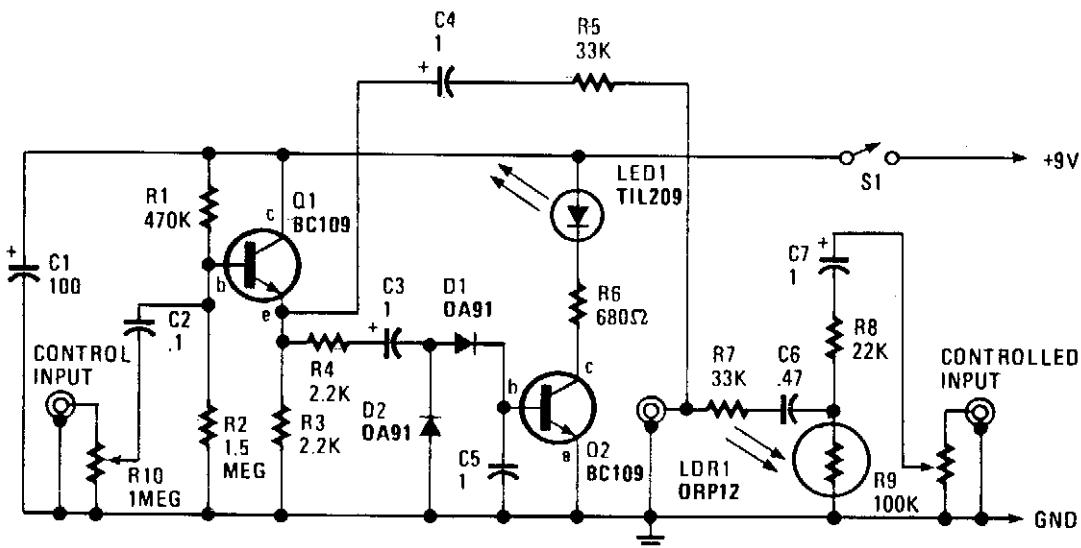


TAB BOOKS INC.

*Fig. 6-1*

### Circuit Notes

The automatic fader drops the level of the background music when the narration comes up. The control input goes through R10, a preset audio level control, to the input of an emitter-follower buffer stage (Q1). The buffer offers a high input impedance and makes sure that the source impedance is low enough to drive the rectifier and smoothing circuit, which consists of D1, D2, and C5. The smoothed output drives a simple LED circuit. R8 and LDR1 form an input attenuator across which the output is fed via C6 and C7 to the output jack. The output at the emitter of Q1 couples to this socket through C4 and R5. R5 and R7 are a passive mixer. With 200 mV or less at the input, there isn't sufficient voltage across C5 to make Q2 turn on. Over 200 mV, Q2 does turn on to a limit, and the LED gets power. That makes the LDR's resistance fall, and signal loss through the attenuator increases. Increase the input to 350 mV rms, and you get a signal reduction of better than 20 dB.


## TRANSISTOR HEADPHONE AMPLIFIER

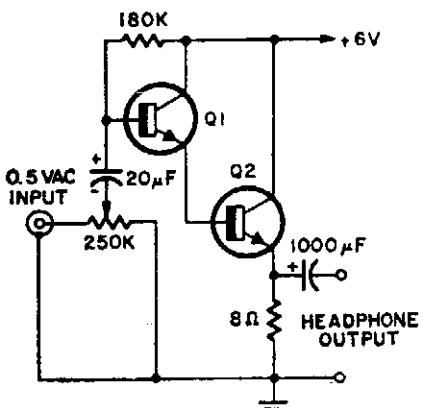

*Fig. 6-2*

RADIO ELECTRONICS

## STEREO PREAMPLIFIER

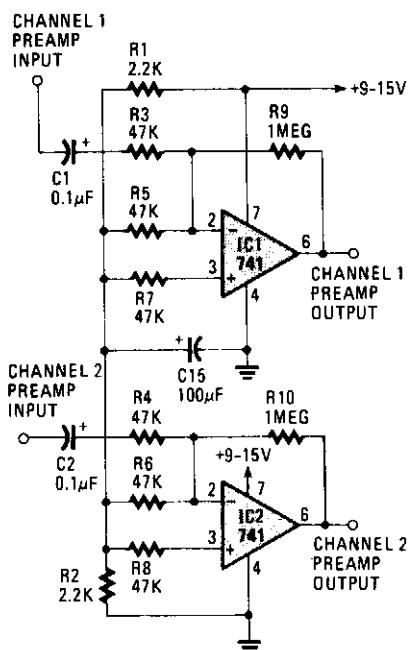


### Circuit Notes

The circuit provides better than 20-dB gain in each channel. A better op-amp type will give a better noise figure and bandpass. In this circuit the roll-off is acute at 20,000 Hertz.

HANDS-ON ELECTRONICS

*Fig. 6-2*

## AUDIO COMPRESSOR

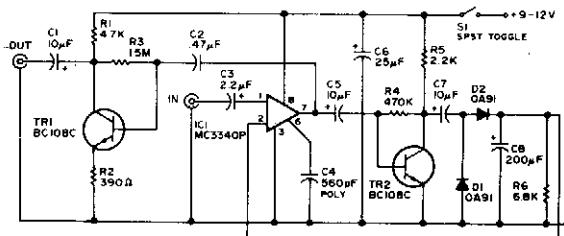

RESISTORS - MINIATURE 1/4W, 5 OR 10%  
CL - 0.66-0.77 ELECTROLYTIC, 16V WKG  
C3 - ELECTROLYTIC, 25V WKG  
C8 - ELECTROLYTIC, 6V WKG  
C2 - TYPE C2B0 (MULLARD)

73 MAGAZINE

Fig. 6-3

### Circuit Notes

A MC3340P is used as a variable gain amplifier. The output of TR2 is rectified and controls the gain of IC1.

## MICROPOWER HIGH-INPUT-IMPEDANCE 20-dB AMPLIFIER

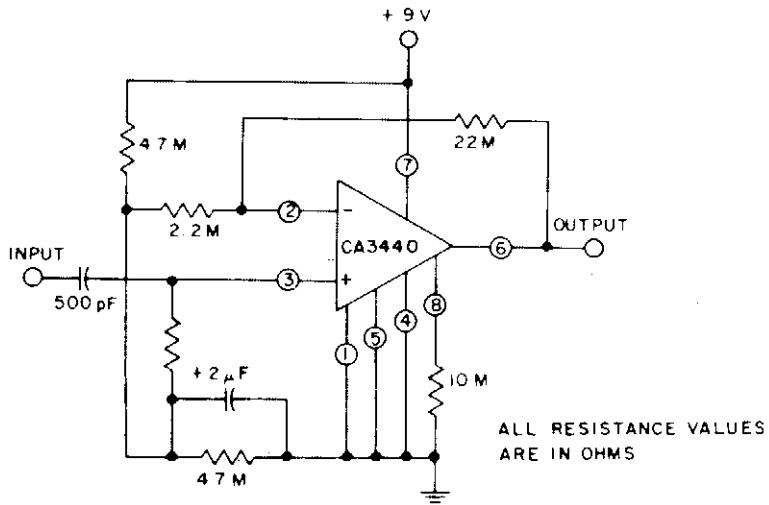


Fig. 6-4

ALL RESISTANCE VALUES  
ARE IN OHMS

$R_{in} > 20 \text{ M}$   
STAND-BY POWER =  $90 \mu\text{W}$     3 kHz    UPPER 3 dB BANDWIDTH  
GAIN = 20 dB  
BW = 20-Hz TO 3-KHz  
SR =  $0.016 \text{ V}/\mu\text{s}$

GENERAL ELECTRIC/RCA

### Circuit Notes

This circuit takes advantage of low power drain, high input impedance, and the excellent frequency capability of the CA3440. Only a 500-pF input coupling capacitor is needed to achieve a 20 Hz, -3 dB low-frequency response.

## STEREO PREAMPLIFIER

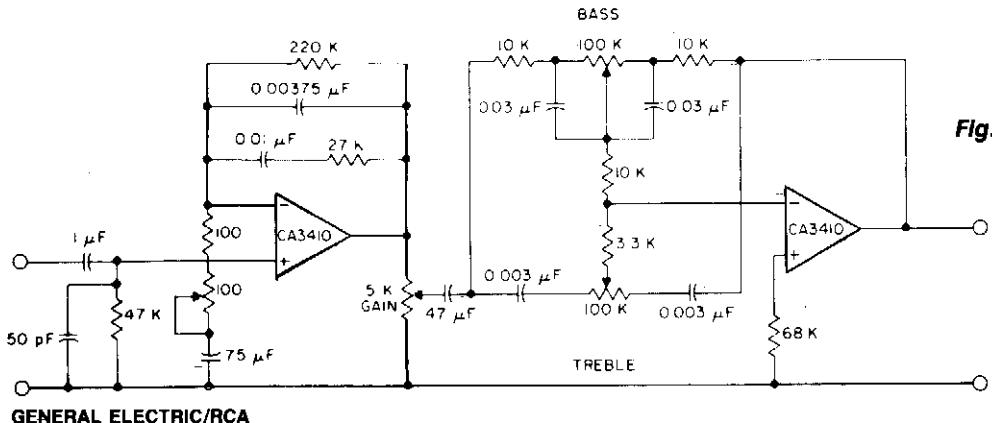


Fig. 6-5

### Circuit Notes

This circuit has RIAA playback equalization, tone controls, and adequate gain to drive a majority of commercial power amplifiers, using the CA3410 BiMOS op amp. Total harmonic distortion, when driven to provide a 6-V output, is less than 0.035% in the audio-frequency range of 150 Hz to 40 kHz. Complete stereo preamplifier consists of duplicating this circuit using the two remaining CA3410 amplifiers.

## MICROPHONE PREAMPLIFIER


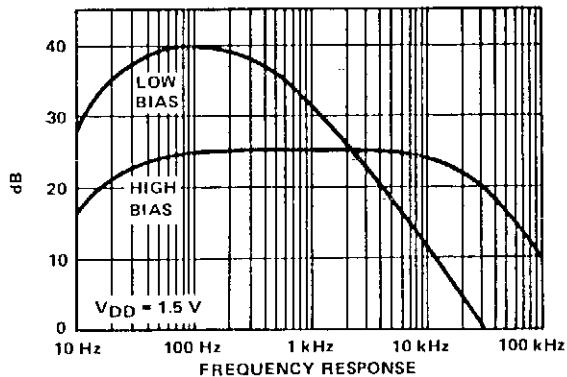
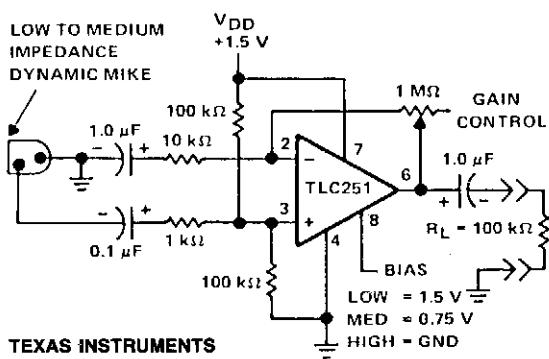


Fig. 6-6

### Circuit Notes

A microphone preamplifier using a CMOS op amp complete with its own battery, is small enough to be put in a small mike case. The amplifier operates from a 1.5-V mercury cell battery at low supply currents. This preamplifier will operate at very low power levels and maintain a reasonable frequency response as well. The TLC251 operated in the low bias mode (operating at 1.5 V) draws a supply current of only 10  $\mu$ A and has a -3 dB frequency response of 27 Hz to 4.8 kHz. With pin 8 grounded, which is designated as the high bias condition, the upper limit increases to 25 kHz. Supply current is only 30  $\mu$ A under those conditions.
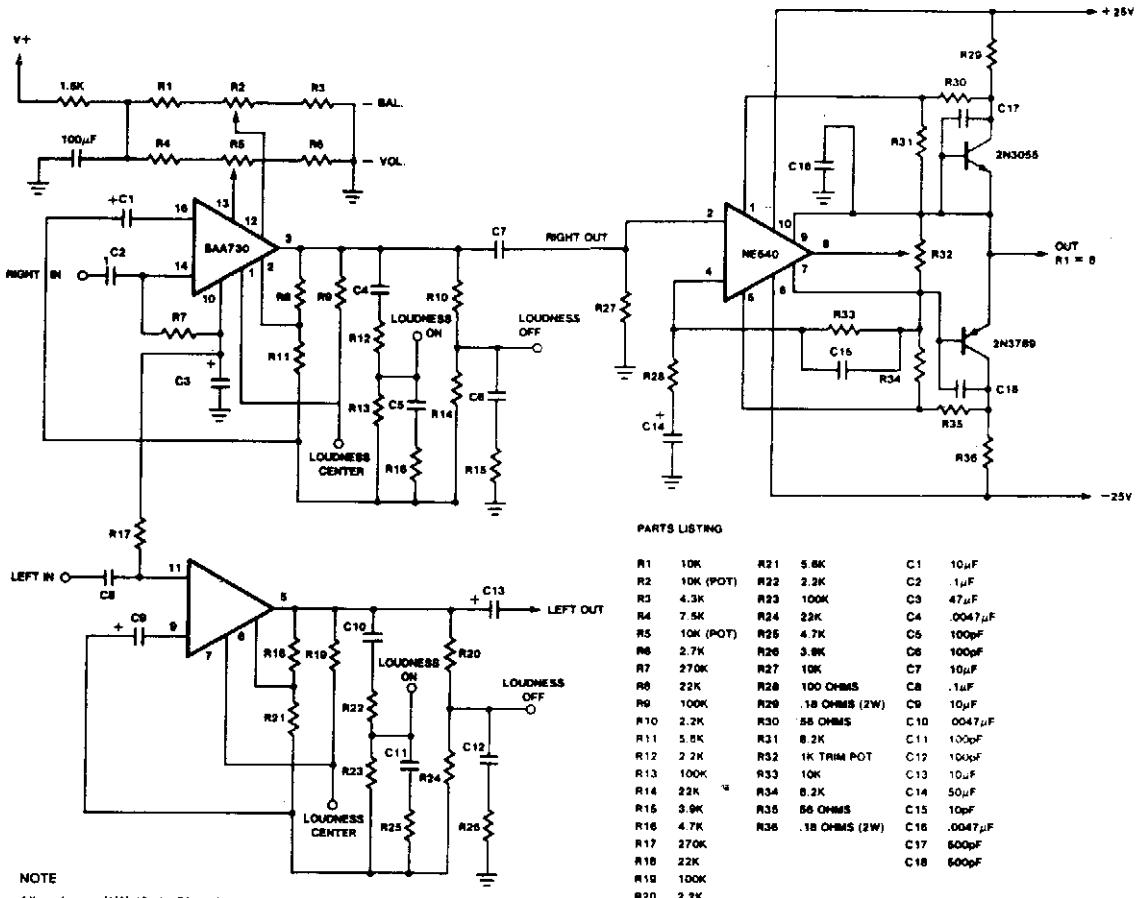
## VOLUME, BALANCE, LOUDNESS & POWER AMPS




SIGNETICS

Fig. 6-7

### Circuit Notes

This circuit should prove suitable as a design example for audio sound application.

## BALANCE AND LOUDNESS AMPLIFIER

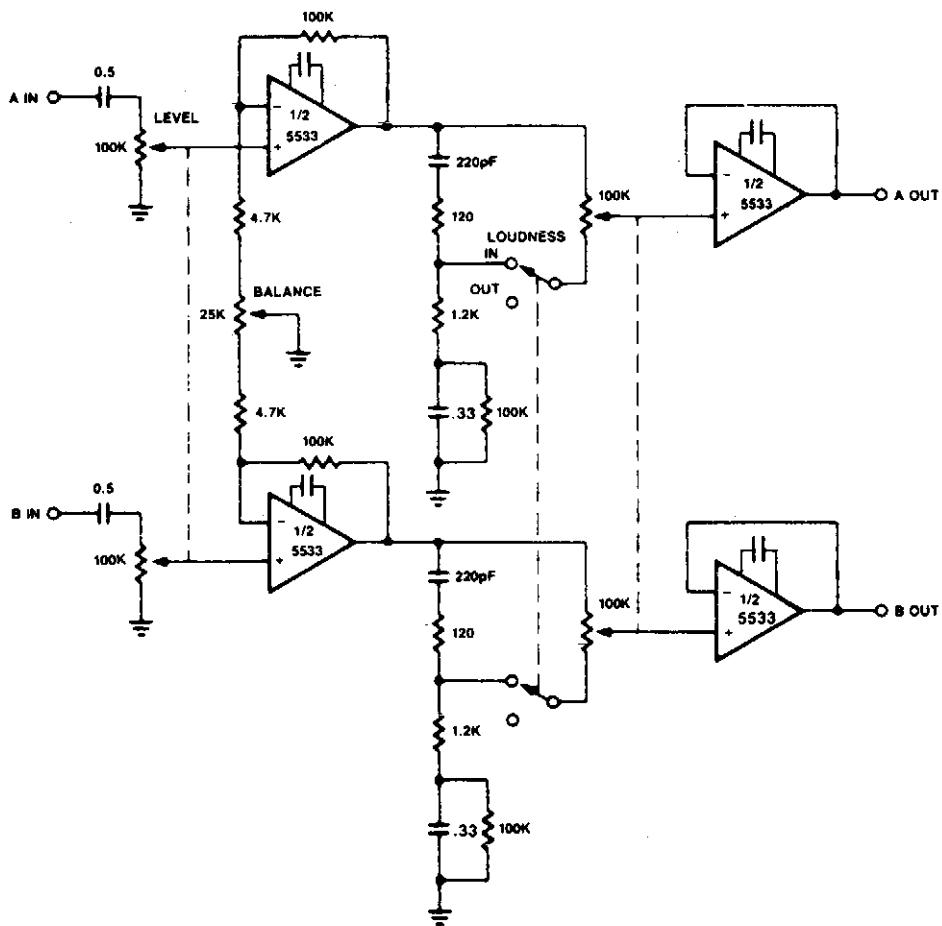

TC06660S

**NOTE:**

All resistor values are in ohms.

SIGNETICS

**Fig. 6-7**

### Circuit Notes

The circuit shows a combination of balance and loudness controls. Due to the non-linearity of the human hearing system, the low frequencies must be boosted at low listening levels. Balance, level, and loudness controls provide all the listening controls to produce the desired music response.

# 7

## Automotive Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Intermittent Windshield Wiper with Dynamic  
Braking  
Immobilizer  
Automotive Exhaust Emissions Analyzer  
Glow Plug Driver  
Garage Stop Light  
Bar-Graph Voltmeter  
Delayed-Action Windshield Wiper Control  
Slow-Sweep Wiper Control  
Automotive Lights On Warning

PTC Thermistor Automotive Temperature Indicator  
Road Ice Alarm  
Headlight Dimmer  
Ice Formation Alarm  
Delay Circuits for Headlights  
Ignition Timing Light  
Digi-Tach  
Car-Wiper Control  
Automatic Headlight Dimmer
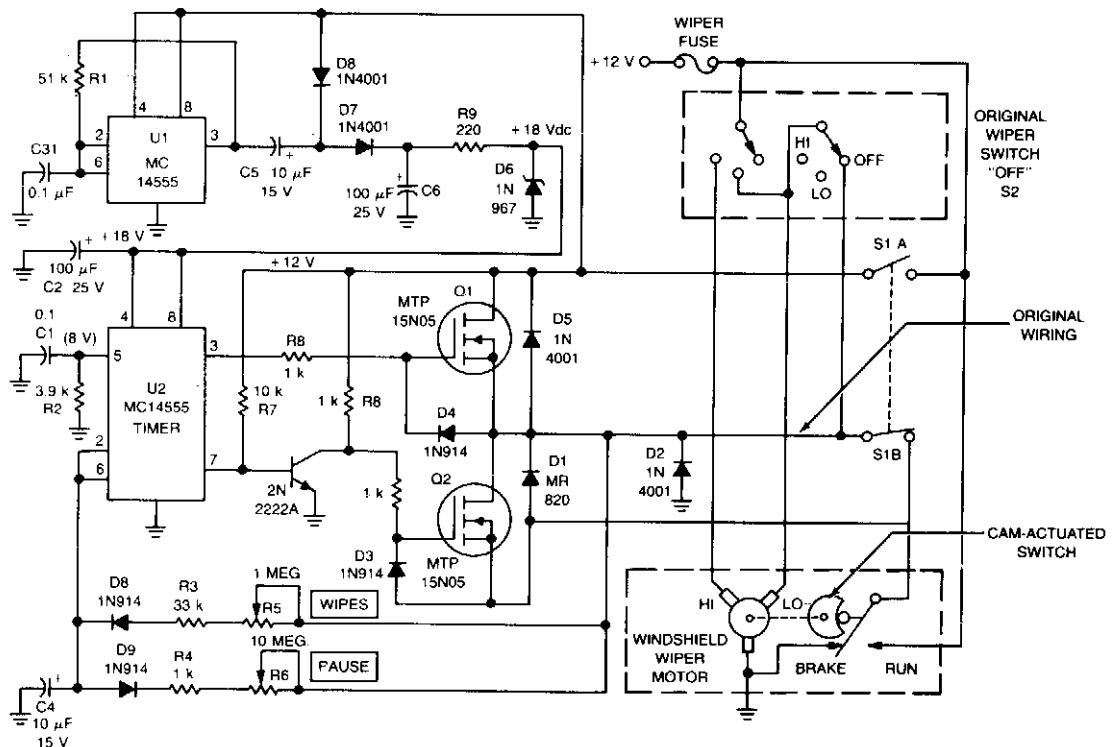
## INTERMITTENT WINDSHIELD WIPER WITH DYNAMIC BRAKING



MOTOROLA

**Fig. 7-1**

### Circuit Notes


The circuit provides a delayed windshield wiping, and dynamic braking of wiper blades when they reach the rest position. This prevents the blades from overshooting, which might cause them to stop at a point where they interfere with the drivers' vision.

With the original wiper switch off, switch S1A turns on the delay circuit and S1B disconnects the original automotive wiring. When S1 is turned off, the original wiring controls the system and the delay circuit is bypassed.

Turning S1 on applies the +12-V battery to U1 which is a voltage doubler that produces +18 V. This higher voltage supply is necessary to ensure reliable turn on of Q1 by multivibrator U2. This arrangement provides about +18 V to the gate of Q1, whose source is +12 V minus the  $V_{DS}$  drop of Q1.

Q1 remains on for a time determined by the WIPES potentiometer. The interval between wipes is controlled by the PAUSE control. When C1 drops below +4 V, U2 fires, turning Q1 on and restarting the cycle.

## IMMOBILIZER

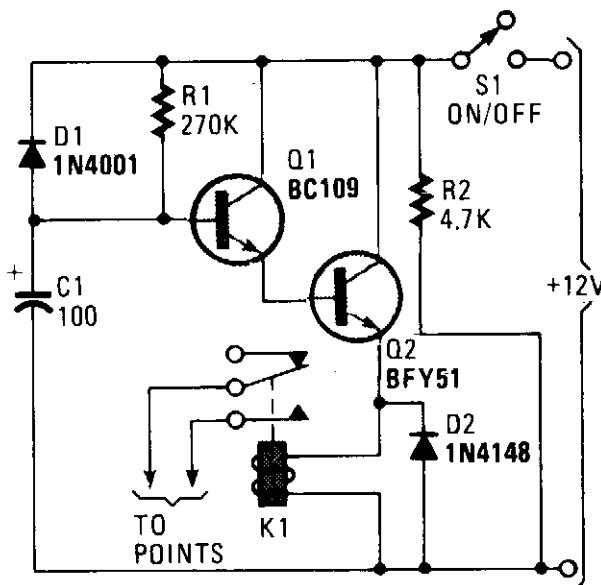


*Fig. 7-2*

HANDS-ON ELECTRONICS

### Circuit Notes

A flip of S1 puts the circuit into action. Power for the circuit is picked up from the ignition switch, and the circuit receives no power until the ignition switch is closed. When power is turned on, capacitor C1 is not charged and the emitter-follower Darlington pair (formed by Q1 and Q2) are cutoff, thus no power is applied to the relay (K1), which serves as Q1's emitter load. The relay's normally-open contacts are connected across the vehicle's points. (At this time, the relay contacts are open and have no effect on the ignition system). C1 charges by way of R1, causing the voltage at the base of Q1 to rise steadily. That creates a similar rise in the voltage at the emitter of Q2. A Darlington pair is used to provide a high input-impedance, buffer stage so that the voltage across C2 is free to rise almost to the full supply potential. Loading effects do not limit the charge potential to just a few volts. Eventually, the voltage applied to the relay becomes sufficient to activate it. The contacts close and short out the points. The ignition system now doesn't act properly and the vehicle is disabled. If the ignition is switched off, power is removed from the circuit and diode D1, which was previously reverse-biased, is now forward biased by the charge on C1. D1 allows C1 to rapidly discharge through R2 (and any other dc paths across the supply lines). The circuit is ready to operate when the ignition is again turned on. The engine will operate, but not for very long. The values of R1 and C1 provides a delay of about 25 to 30 seconds. Increase R1's value to provide a longer delay.

## AUTOMOTIVE EXHAUST EMISSIONS ANALYZER

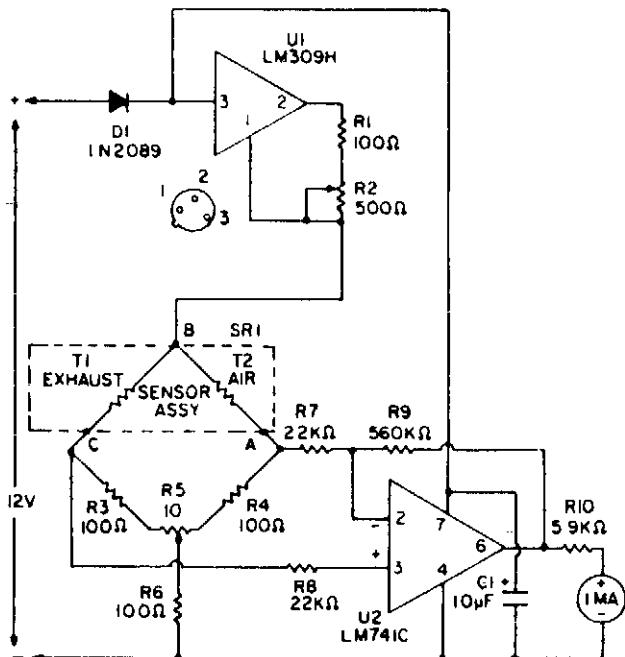

**Fig. 7-3**

**C1**—10- $\mu$ F, 25 volt electrolytic capacitor  
**D1**—Silicon diode, general purpose, IN2069 or equivalent  
**M1**—0.1 ma ammeter  
**R1, R3, R4, R6**—100-ohm 10%  $\frac{1}{4}$  watt resistor (All resistors are 10%,  $\frac{1}{4}$  watt)  
**R2**—500-ohm potentiometer, PC mount  
**R5**—10-ohm potentiometer, front panel mount  
**R7, R8**—22,000-ohm resistor  
**R9**—570,000-ohm resistor

TAB BOOKS, INC.


**R10**—5,900-ohm resistor  
**SR1**—thermistore sensor assembly, part number 100-1648 from Heathkit model CI-1080, Heath Company Benton Harbor, MI, 49022  
**U1**—LM309H 5-volt regulator integrated circuit  
**U2**—LM741TC op amp intergrated circuit  
**Misc.**—PC Board, screws, cabinet, solder, hardware, 10-foot plastic tube, etc.

### Circuit Notes

A bridge circuit contains two 100-ohm resistors (R3 and R4), and two thermistors (T1 and T2). At room temperature the resistance of T1 and T2 is about 2000 ohms. When they are each heated to 150°C by a 10 mA current, the resistance value decreases to 100 ohms. Thus, the four elements comprise a bridge circuit. A characteristic of CO is that it conducts heat away from a thermistor at a different rate than air. One thermistor, T1, is exposed to the automobile exhaust while the other, T2, is isolated in a pure air environment. The difference in thermal conduction unbalances the bridge. A voltage difference is caused between points A and C. A differential amplifier, U1, amplifies this difference and drives the meter with sufficient current to read out the percentage of CO and the air-fuel ratio. A front panel balance control, R5, balances the bridge and calibrates the instrument. Calibration is performed when both thermistors are exposed to the outside air.
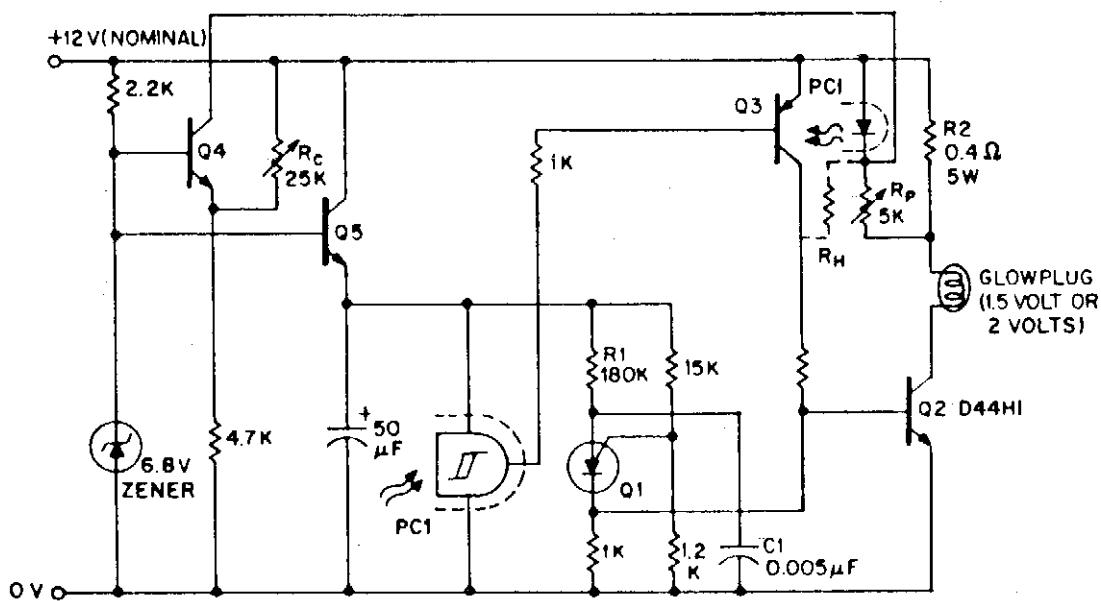
## GLOW PLUG DRIVER

ALL RESISTORS 1/2W EXCEPT AS NOTED OTHERWISE



$R_c$  — SUPPLY VOLTAGE COMPENSATION TRIM.

$R_p$  — PLUG TEMPERATURE ADJUST.

Q1 — 2N6028

PC1 — H11L2.

Q3 — D29E2

Q4, Q5 — D33DI

GENERAL ELECTRIC

Fig. 7-4

### Circuit Notes

Model airplanes, boats, and cars use glow plug ignitions for their miniature (0.8cc to 15cc) internal combustion engines. Such engines dispense with the heavy on-board batteries, H.T. coil, and "condenser" required for conventional spark ignition, while simultaneously developing much higher RPM (hence power) than the compression ignition (diesel) motors. The heart of a glow plug is a platinum alloy coil heated to incandescence for engine starting by an external battery, either 1.5 volts or 2 volts. Supplementing this battery, a second 12-volt power supply is frequently required for the engine starter, together with a third 6 volt type for the electrical fuel pump.

Rather than being burdened by all these multiple energy sources, the model builder would prefer to carry (and buy) a single 12-volt battery, deriving the lower voltages from this by use of suitable electronic step-down transformers (choppers). The glow driver illustrated does this and offers the additional benefit of (through negative feedback) maintaining constant plug temperature independent of engine flooding, or battery voltage while the starter is cranking.


In this circuit, the PUT relaxation oscillator Q1 turns on the output chopper transistor Q2 at a fixed repetition rate determined by R1 and C1. Current then flows through the glow plug and the parallel combination of the current sense resistor R2 and the LED associated with the H11L Schmitt trigger. With the plug cold (low resistance), current

is high, the H11L is biased "on", and Q3 conducts to sustain base drive to Q2. Once the plug has attained optimum operating temperature, which can be monitored by its ohmic resistance, the H11L is programmed (via  $R_p$ ) to switch off, removing base drive from Q3 and Q2.

However, since the H11L senses glow plug current, not resistance, this is only valid if supply voltage is constant, which is not always the case. Transistor Q4 provides suitable compensation in this case; if battery voltage falls (during cold cranking, for instance), the collector current of Q4 rises, causing additional current to flow through the LED, thus delaying the switch-off point for a given plug current. The circuit holds plug temperature relatively constant, with the plug either completely dry or thoroughly "wet", over an input voltage range of 8 to 16 volts. A similar configuration can be employed to maintain constant temperature for a full size truck diesel glow plug (28-volts supply, 12-volts glow plug); in this case, since plug temperature excursions are not so great, a hysteresis expansion resistor  $R_H$  may be required.

**Fig. 7-4 Continued**

### GARAGE STOP LIGHT

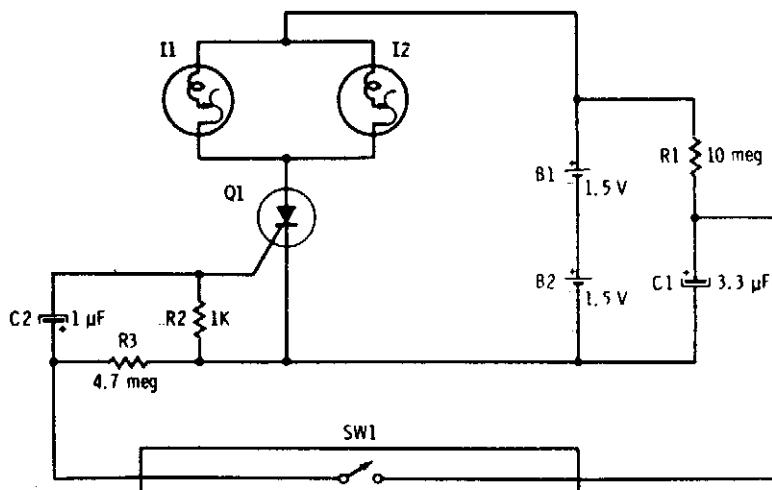

TAB BOOKS INC.


SWITCH - STRIP

**Fig. 7-5**

### Circuit Notes

Capacitor C1 is permanently connected across the 3-volt supply through 10 megohm resistor R1. The capacitor charges (relatively slowly) to 3 volts. The instant switch SW1 is closed, it connects the charged capacitor (C1) in series with C2 and R2. Capacitor C2 starts to charge, placing a positive-going voltage on the gate of the SCR and causing it to turn on. The two parallel-connected "self-flashing" bulbs I1 and I2 turn on. They flash and turn off the SCR and the circuit is off until car is driven off the switch and C1 can recharge.

## BAR-GRAPH VOLTMETER

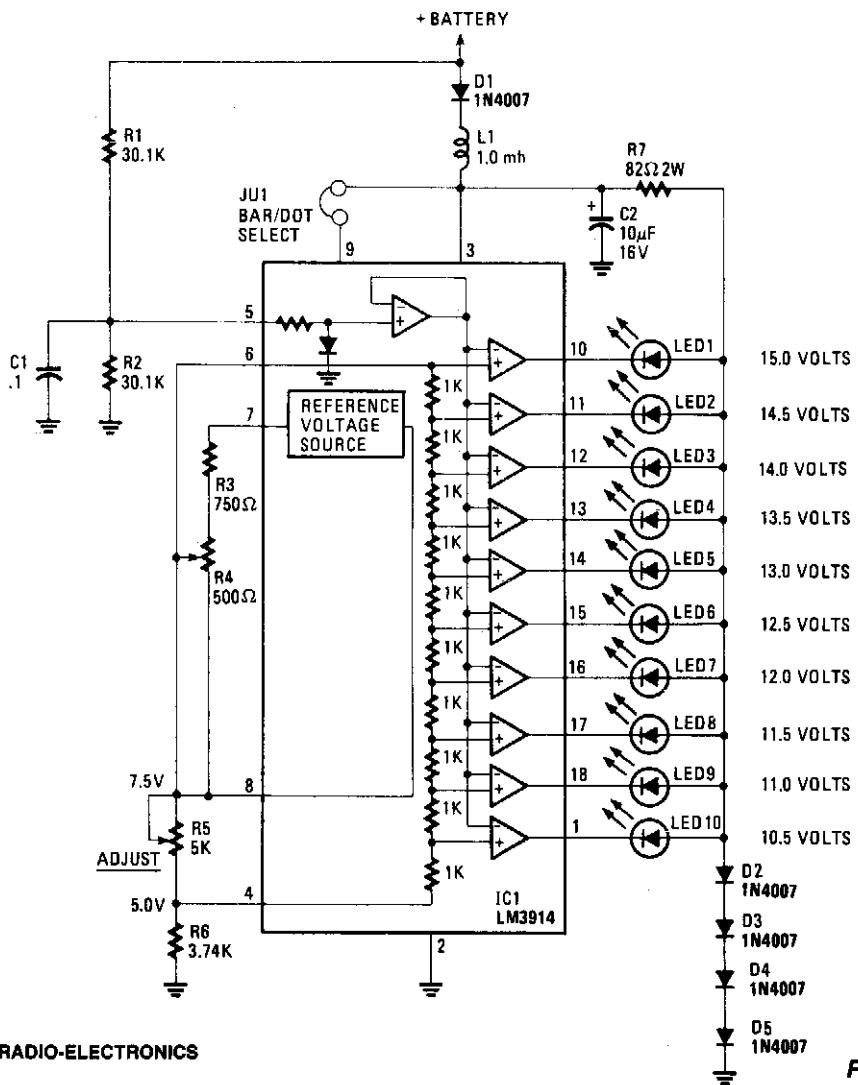

RADIO-ELECTRONICS

Fig. 7-6

### Circuit Notes

This display uses ten LED's to display a voltage range from 10.5 to 15 volts. Each LED represents a 0.5-volt step in voltage. The heart of the circuit is the LM-3914 dot/bar display driver. Trimmer potentiometer R5 is adjusted so that 7.5 volts is applied to the top side of the divider. Resistor R7 and diodes D2 through D5 clamp the voltage applied to the LED's to about 3 volts. A lowpass filter made up of L1 and C2 guards against voltage spikes. Diode D1 is used to protect against reverse voltage in case the voltmeter is hooked up backward.

## DELAYED-ACTION WINDSHIELD WIPER CONTROL


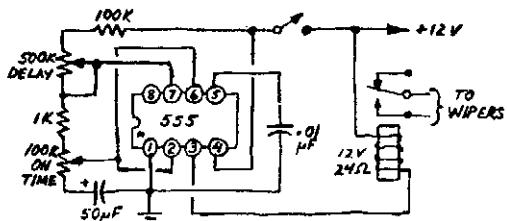


Fig. 7-7

POPULAR ELECTRONICS

## SLOW-SWEEP WIPER CONTROL

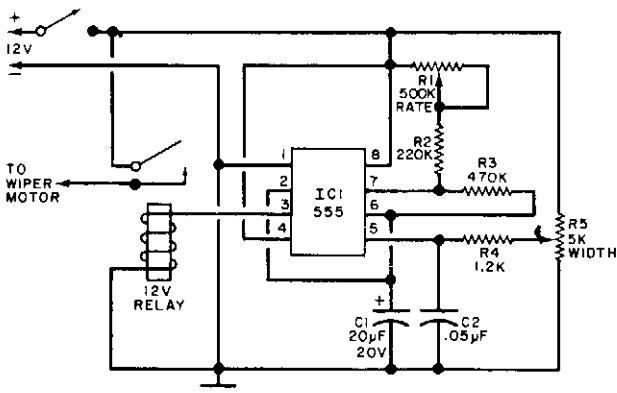

POPULAR ELECTRONICS

Fig. 7-8


## Circuit Notes

The relay which applies power to the wiper motor is actuated at periodic intervals by the timer circuit, closing the wiper motor contacts. Potentiometer R1 serves as the pulse rate control and potentiometer R5 as the pulse width control. These two controls should be adjusted for optimum performance after the unit is installed in a car.

## AUTOMOTIVE LIGHTS ON WARNING
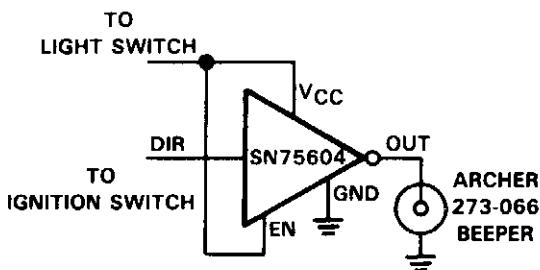
### Circuit Notes


The SN75604, with input control logic but requiring only one supply rail, can be used in the "lights on" sensor and alarm driver. The device V<sub>CC</sub> and enable inputs are connected to a voltage lead from the light switch. The direction control input is connected to a lead from the ignition switch. Only operation of the lights without the ignition will result in the alarm sounding. The beeper used in this application is an Archer 273-066 that will operate from 3 V to 28 V. At a typical 12 V level, it will produce a pulsating tone of about 95 dB at 30 cm. The alarm "on" current is about 12 mA when operating from a 12 V supply.



TEXAS INSTRUMENTS

Fig. 7-9
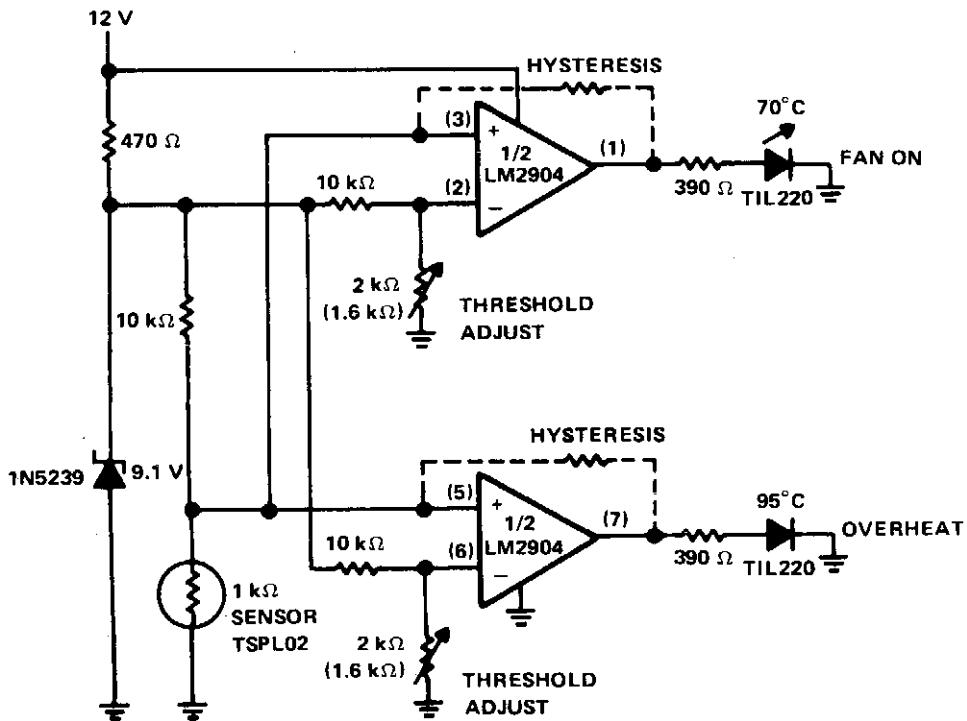
## PTC THERMISTOR AUTOMOTIVE TEMPERATURE INDICATOR




TEXAS INSTRUMENTS

*Fig. 7-10*

### Circuit Notes

The circuit is used to indicate two different water temperature trip points by turning on LEDs when the temperatures are reached. The circuit is constructed around the LM2904 dual operational amplifier powered from the 12 V auto system. The thermistor is in series with a 10 k $\Omega$  resistor from ground to the positive 9.1 V point. The top of the thermistor is tied to both non-inverting inputs of the LM2904. The voltage at these inputs will change as the thermistor resistance changes with temperature. Each inverting input on the LM2904 has a reference, or threshold trip point, set by a 10 k $\Omega$  resistor and a 2 k $\Omega$  potentiometer in series across the 9.1 V regulated voltage. When this threshold is exceeded on the non-inverting input of LM2904, the TIL220 LED lights. The two trip points can be recalibrated or set to trip at different temperatures by adjusting the 2 k $\Omega$  potentiometer in each section. In addition to being used as warning lights as shown here, circuits can be added to turn on the fan motor or activate a relay.

## ROAD ICE ALARM

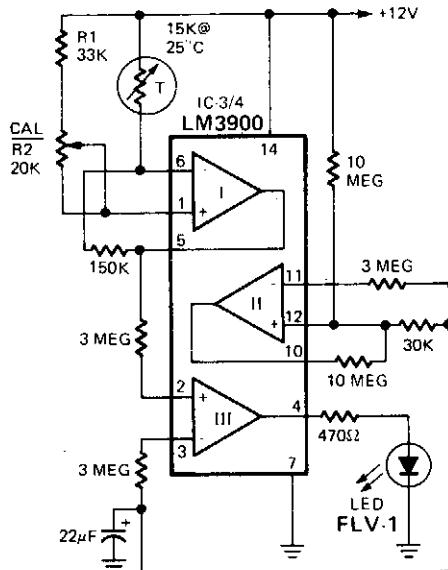


RADIO-ELECTRONICS

*Fig. 7-11*

## Circuit Notes

The circuit uses a thermistor and three sections of a LM3900 quad op amp IC. When the temperature drops to 36°F the LED indicator flashes about once each second. The flashing rate increases as temperature drops to 32°F when the LED remains on. Amplifier I compares the thermistor's resistance to the resistance of the standard network connected to its noninverting input. Its output—fed to the noninverting input of op amp III—varies with temperature. Op amp II is a free-running multivibrator feeding a pulse signal of about 1 Hz to the inverting input of op amp III. This amplifier compares the outputs of op amps I and II and turns on the LED when the multivibrator's output level drops below op amp I. The monitor is calibrated by placing the thermistor in a mixture of crushed ice and water and adjusting the 20 kΩ pot so the LED stays on.

## HEADLIGHT DIMMER

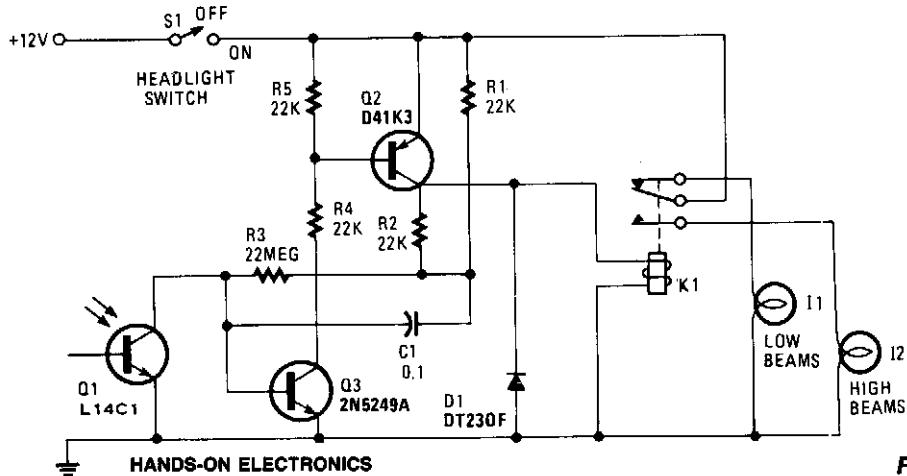


*Fig. 7-12*
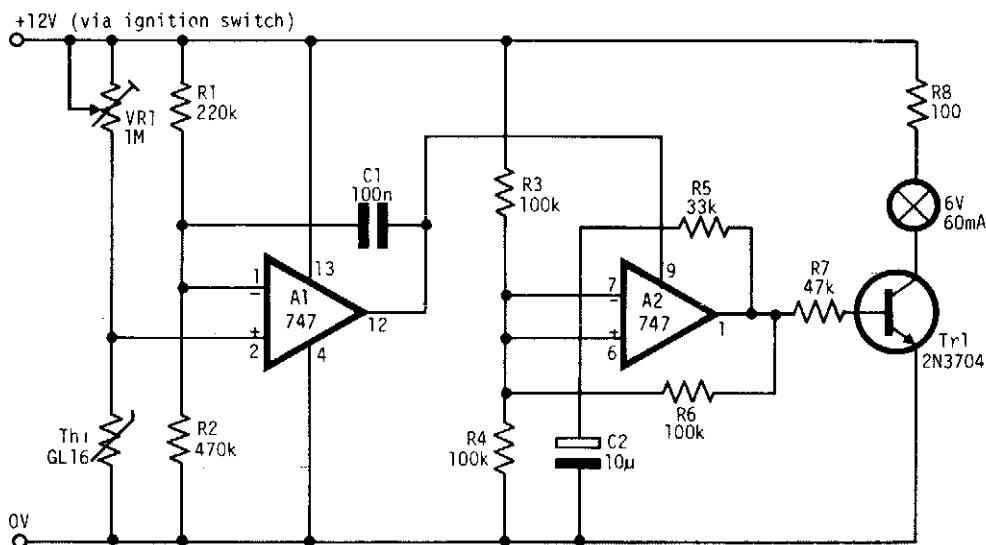
## Circuit Notes

When the lights of an on-coming car are sensed by photo-transistor Q1, things get going. Sensitivity is set by the 22-megohm resistor, R5, to about half a foot-candle. The relay used has a 12-volt, 0.3A coil. The L14C1 is complete with a lens that has a diameter of one inch for a 10° viewing angle.

## ICE FORMATION ALARM




ELECTRONIC ENGINEERING

Fig. 7-13

### Circuit Notes

The circuit warns car drivers when the air temperature close to the ground approaches 0°C, thereby indicating possible formation of ice on the road surface. Op amp A1 is wired as a voltage level sensor. Op amp A2 is wired as an astable multivibrator which, by means of current buffer Tr1, flashes a filament lamp at about 1 Hz. As air temperature falls, a point is reached when the voltage at pin 2 just rises above the voltage at pin 1. The output of A1 is immediately driven into positive saturation, since it is operated open-loop. This positive output voltage powers A2 through its V+ connection on pin 9, starting the oscillator. The thermistor is a glass bead type with a resistance of about  $20\text{ M}\Omega$  at 20°C. VR1 is adjusted so that the lamp starts flashing when the air temperature is 1 to 2°C.

## DELAY CIRCUITS FOR HEADLIGHTS

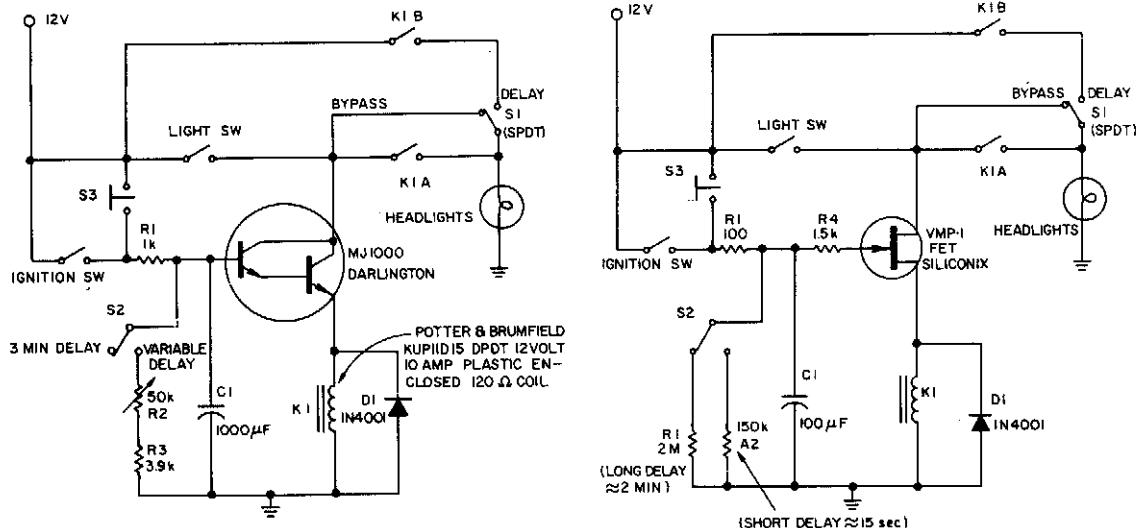

1. Automobile headlights may be kept on up to 3 minutes after you leave the car with this Darlington time-delay circuit.

2. A FET version of the delay circuit allows the use of a smaller timing capacitor,  $C_1$ , for a given delay, and almost instantaneous reset with  $S_3$ ; the Darlington circuit needs almost 2 s.


ELECTRONIC DESIGN

Fig. 7-14

### Circuit Notes

This circuit keeps an automobile's headlights on temporarily. It also will turn the lights off, even if you forget to flip the light switch. The circuit's shut-off delay is actuated only after both the ignition and light switches have been on, and only if the ignition switch is turned off first. If the light switch is turned off first, no delay results. Parking and brake-light operation is not affected. The maximum time out can be up to 3 minutes in part 1 and hours with the circuit in part 2, depending on the relay selected and the value of  $R_2$ . A switch  $S_2$  can be used to permit selection of either a short or long delay. Momentary switch  $S_3$  can restart circuit timing before the time-out is completed. A bypass switch,  $S_1$  removes the delay action.

## IGNITION TIMING LIGHT

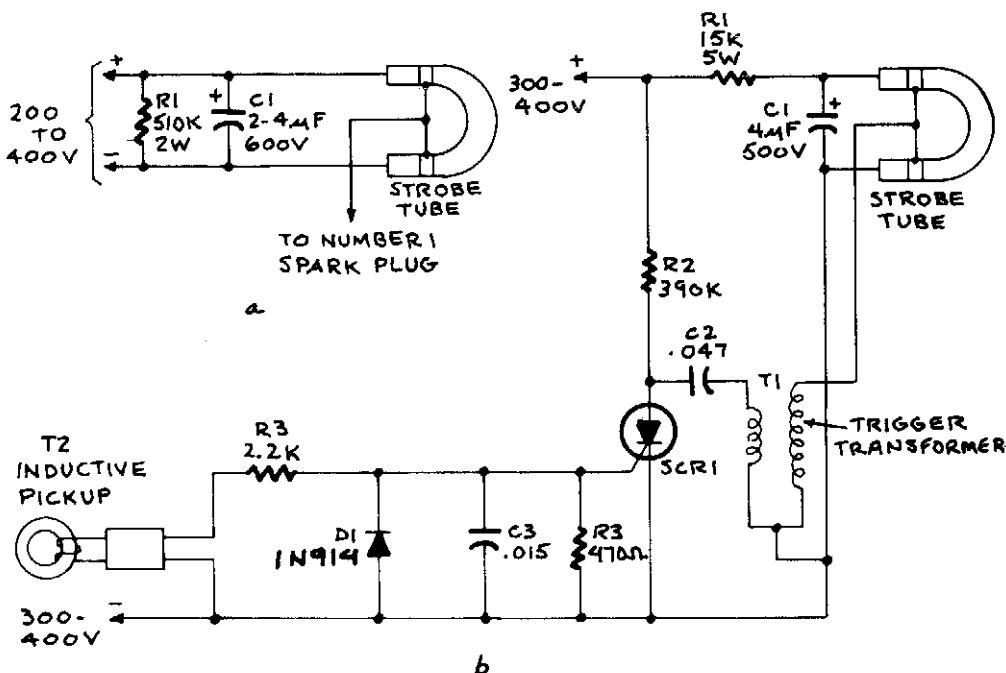

RADIO-ELECTRONICS

Fig. 7-15


### Circuit Notes

Figure A shows the circuit of a direct-trigger timing light. The trigger voltage is taken from the car's ignition circuit by a direct connection to a spark plug. A circuit using an inductive pickup is shown in Fig. B. A trigger transformer is used to develop the high-voltage pulse for triggering. The triggering circuit consists of  $T_1$ ,  $C_1$ , SCR1, inductive pickup coil  $T_2$ , and the waveshaping components in the SCR's gate circuit.

When the spark plug fires, it induces a pulse in pickup coil  $T_2$  that triggers the SCR gate. The SCR fires and discharges  $C_2$  through the primary of  $T_1$ . The secondary of  $T_1$  feeds a high-voltage pulse to the trigger electrode of the flash tube. That pulse causes the gas—usually neon or xenon—to ionize. The ionized gas provides a low-resistance path for  $C_1$  to discharge, thereby creating a brilliant flash of light.

Resistor  $R_1$  limits current from the supply as the tube fires. When  $C_1$  is fully discharged the strobe tube cuts off and returns to its "high-resistance" state. The current through  $R_2$  is not enough to sustain conduction through SCR1, so it cuts off and remains off until it is re-triggered by a gate pulse.

## DIGI-TACH

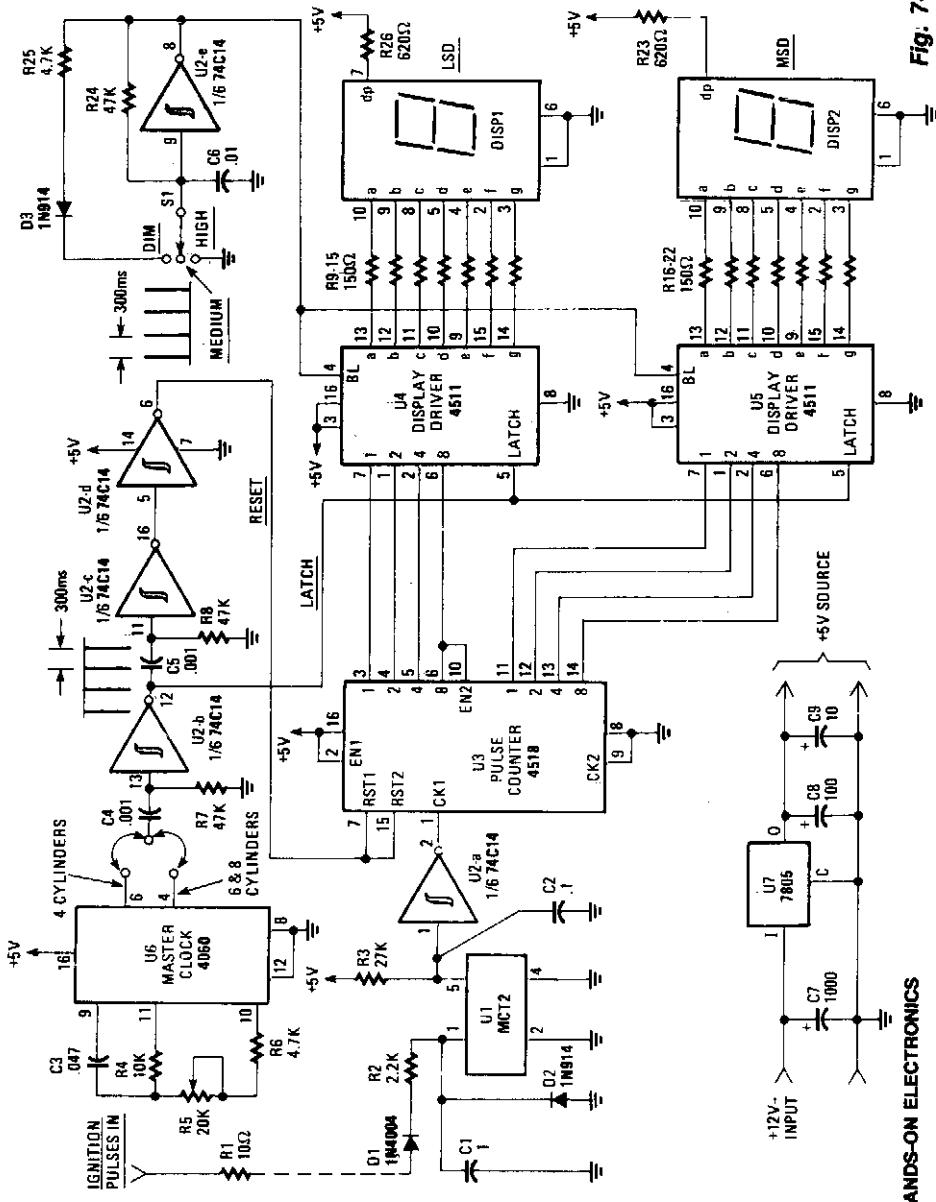


HANDS-ON ELECTRONICS

## Circuit Notes

The Digi-Tach contains a master-clock circuit (UJ6), latch and reset pulse generators (U2-b-U2-d), input signal conditioner (U1, U2-a), pulse counter (U3), display and display drivers (DISP1, DISP2, U4, and U5), and a voltage regulator (U7). As an added feature, Digi-Tach contains a dimmer circuit (U2-e).

Fig. 7-16

## CAR-WIPER CONTROL

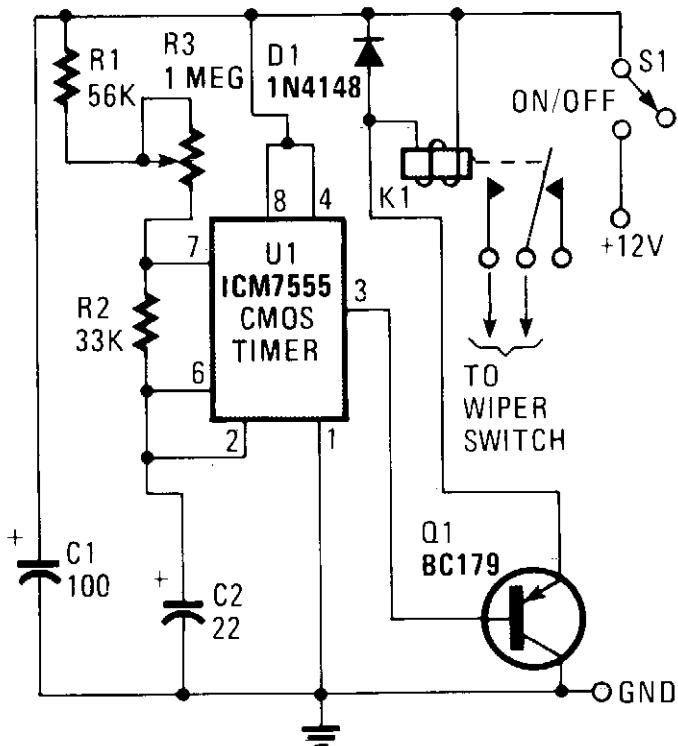


HANDS-ON ELECTRONICS

Fig. 7-17

### Circuit Notes

U1 is configured to operate in the standard astable mode, providing a form of relaxation oscillator. When power is applied, C2 initially charges through R1, R2 and R3 to two-thirds of the supply voltage. At that point, U1 senses that its threshold voltage at pin 6 has been reached, and triggers the timer, causing its output at pin 3 to go high. That high, applied to the base of Q1, keeps the transistor in the off state. Now C2 begins to discharge through R2 to pin 7 of U1. When C2 has discharged to about one-third of the supply voltage, U1 is toggled back to its original state. C2 starts to charge again, as pin 3 of U1 goes low. The low at pin 3 causes Q1—which serves as an emitter-follower buffer stage—to turn on, allowing current to flow through the coil of relay K1. That, in turn, causes K1's contacts to close, applying power to the wipers. The charge time of capacitor C2 is determined by the setting of potentiometer R3. Capacitor C2 should be a tantalum type, and actually, almost any 12-volt coil relay with sufficiently heavy contacts should serve well.

## AUTOMATIC HEADLIGHT DIMMER

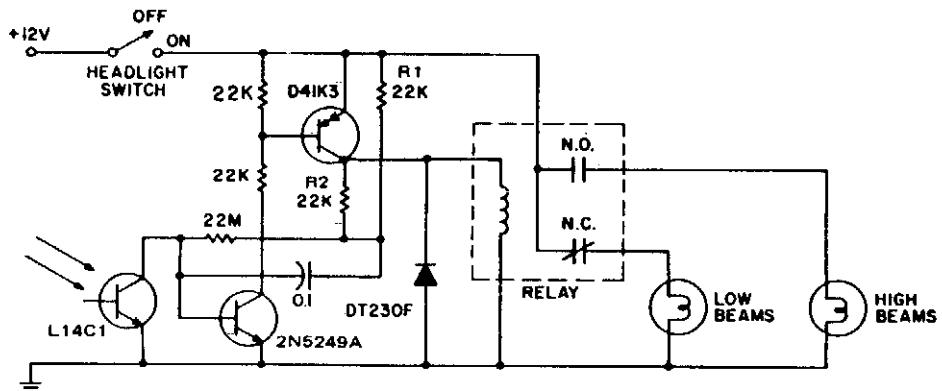

**RELAY:** 12V, 0.3A-COIL: 20A, FORM C, CONTACTS OR SOLID-STATE SWITCHING OF 16A STEADY-STATE 150A COLD FILAMENT SURGE, RATING.

**LENS:** MINIMUM 1" DIAMETER. POSITIONED FOR ABOUT 10° VIEW ANGLE.

GENERAL ELECTRIC

*Fig. 7-18*

### Circuit Notes

This circuit switches car headlights to the low beam state when it senses the lights of an on-coming car. The received light is very low level and highly directional, indicating the use of a lens with the detector. A relatively large amount of hysteresis is built into the circuit to prevent "flashing lights." Sensitivity is set by the 22 megohm resistor to about 0.5 ft. candle at the transistor (0.01 at the lens), while hysteresis is determined by the R1, R2 resistor voltage divider, parallel to the D41K3 collector emitter, which drives the 22 megohm resistor; maximum switching rate is limited by the 0.1  $\mu$ F capacitor to 15/minute.

# 8

## Battery Chargers and Zappers


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Rapid Battery Charger for ICOM IC-2A
- Gel Cell Charger
- Ni-Cad Battery Zapper
- Lithium Battery Charger
- Thermally Controlled Ni-Cad Charger
- Ni-Cad Battery Zapper II
- Battery Charger
- Wind Powered Battery Charger
- Battery Charger Operates On Single Solar Cell
- Versatile Battery Charger
- 14-Volt, 4-Amp Battery Charger/Power Supply


## RAPID BATTERY CHARGER FOR ICOM IC-2A

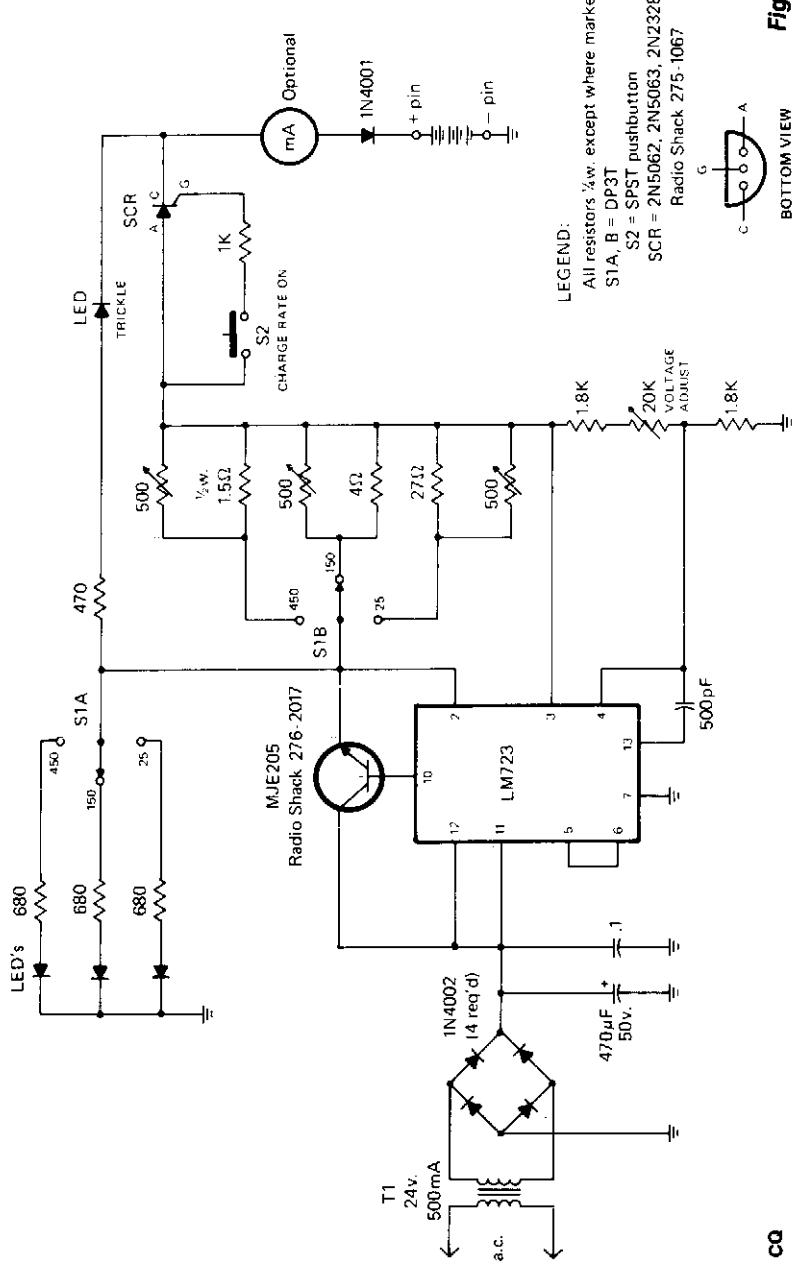

**Circuit Notes**

Rectified and filtered voltage from the 24 Vac transformer is applied to the LM723 voltage regulator and the npn pass transistor set up for constant current supply. The 470 ohm resistor limits trickle current until the momentary pushbutton (S2) is depressed, the SCR turns on and current flows through the previously determined resistor network limiting the charging current. The SCR will turn off when the thermal cutout circuit inside the battery pack opens up.

## GEL CELL CHARGER

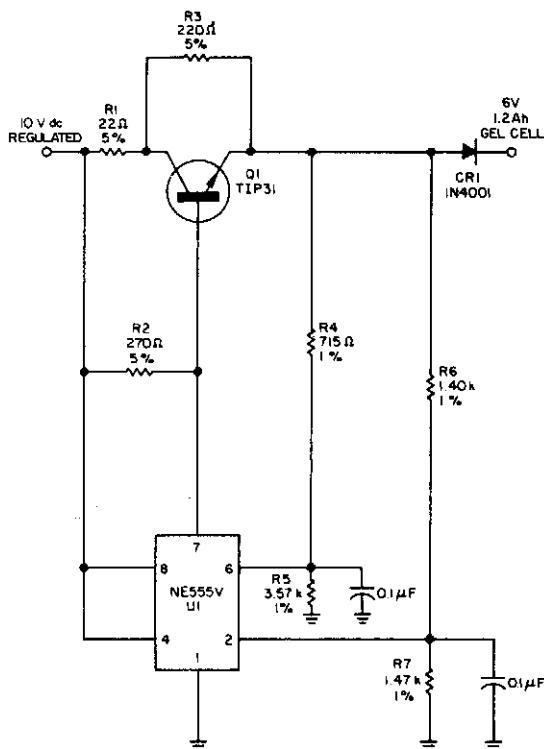

ELECTRONIC DESIGN

### Circuit Notes

This circuit detects a full-charge state and automatically switches to a float condition—from 240 mA to 12 mA.

Fig. 8-2

## Ni-CAD BATTERY ZAPPER

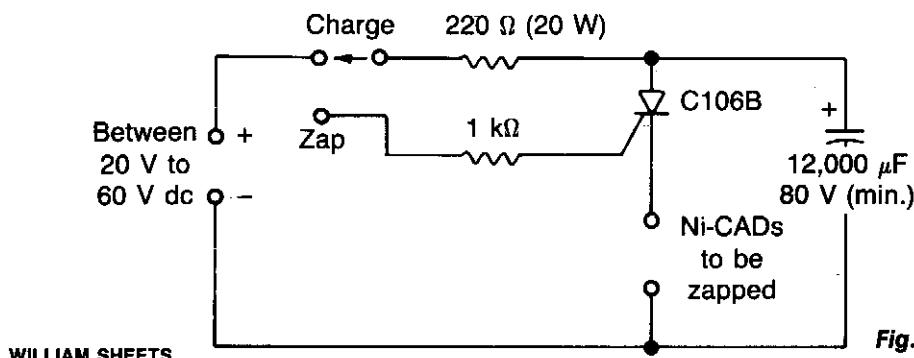


Fig. 8-3

### Circuit Notes

The short in a Ni-Cad battery can be “burned off” with this zapper. Use of the SCR keeps heavy discharge current from damaging switch contacts.

## LITHIUM BATTERY CHARGER


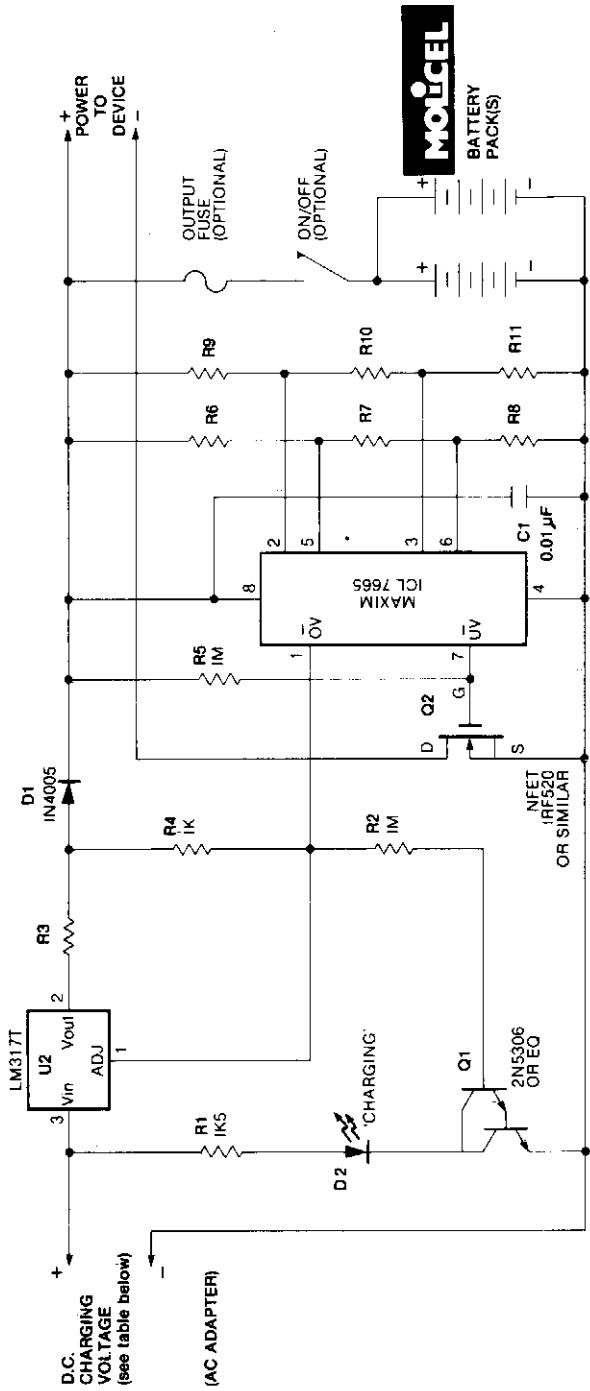


Fig. 8-4

### Circuit Notes

Charging is accomplished with a constant current of 60 mA for AA cells to a cutoff voltage of 2.4 V per cell at which point the charge must be terminated. The charging system shown is designed for multi-cell battery packs of 2 to 6 series-connected cells or series/parallel arrangements. It is essential that all cells assembled in the pack be at an identical state-of-charge (voltage) prior to charging. The maximum upper cut-off voltage is 15.6 volts ( $6 \times 2.6$  V).

## THERMALLY CONTROLLED NI-CAD CHARGER

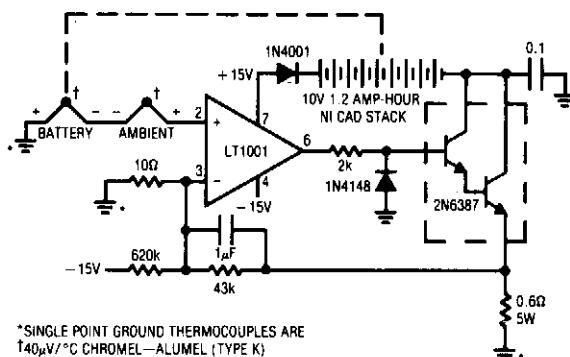

LINEAR TECHNOLOGY CORPORATION


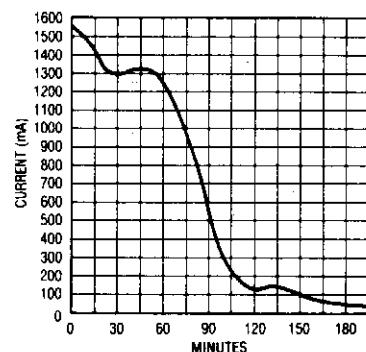


Fig. 8-5

### Circuit Notes

One way to charge Ni-Cad batteries rapidly without abuse is to measure cell temperature and taper the charge accordingly. The circuit uses a thermocouple for this function. A second thermocouple nulls out the effects of ambient temperature. The temperature difference between the two thermocouples determines the voltage which appears at the amplifier's positive input. As battery temperature rises, this small negative voltage ( $1^{\circ}\text{C}$  difference between the thermocouples equals  $40\ \mu\text{V}$ ) becomes larger. The amplifier, operating at a gain of 4300, gradually reduces the current through the battery to maintain its inputs at balance. The battery charges at a high rate until heating occurs and the circuit then tapers the charge. The values given in the circuit limit the battery surface temperature rise over ambient to about  $5^{\circ}\text{C}$ .

## NI-CAD BATTERY ZAPPER II

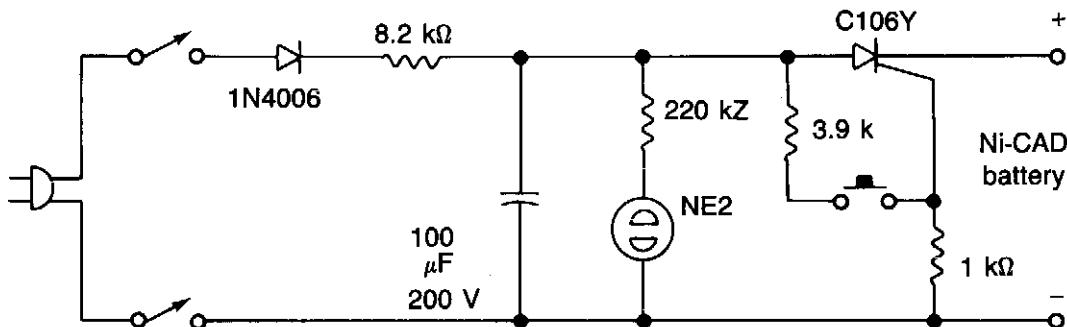


WILLIAM SHEETS

Fig. 8-6

### Circuit Notes

This zapper clears internal short in nickel cadmium batteries by burning it away. CAUTION: The negative battery terminal is connected to one side of the ac line. For safety operation use a 1:1 isolation transformer.

## BATTERY CHARGER

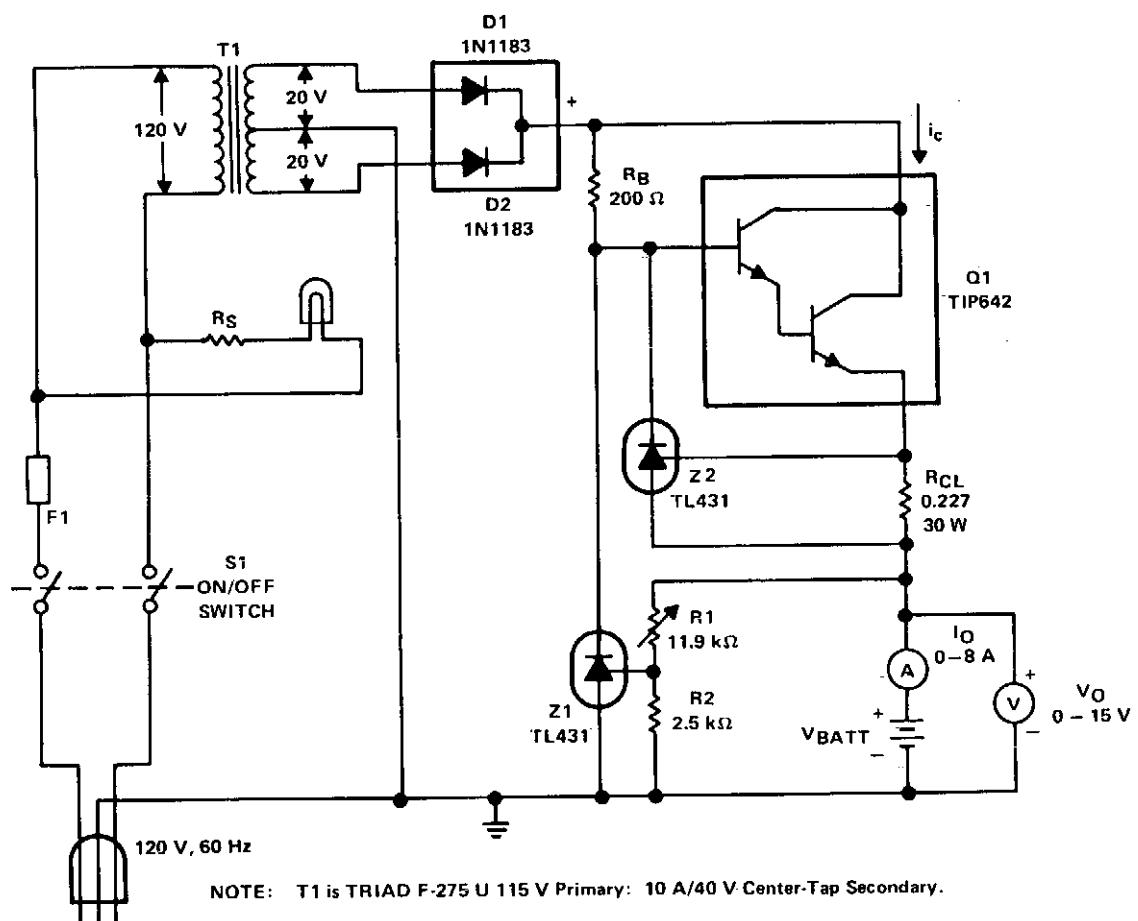


TEXAS INSTRUMENTS

Fig. 8-7

### Circuit Notes

The charger is based on a charging voltage of 2.4 V per cell, in accordance with most manufacturers' recommendations. The circuit pulses the battery under charge with 14.4 V (6 cells × 2.4 V per cell) at a rate of 120 Hz. The design provides current limiting to protect the charger's internal components while limiting the charging rate to prevent damaging severely discharged lead-acid batteries. The maximum recommended charging current is normally about one-fourth the ampere-hour rating of the battery. For example, the maximum charging current for an average 44 ampere-hour battery is 11 A. If the impedance of the load requires a charging current greater than the 11 A current limit, the circuit will go into current limiting. The amplitude of the charging pulses is controlled to maintain a maximum peak charging current of 11 A (8 A average).

## WIND POWERED BATTERY CHARGER

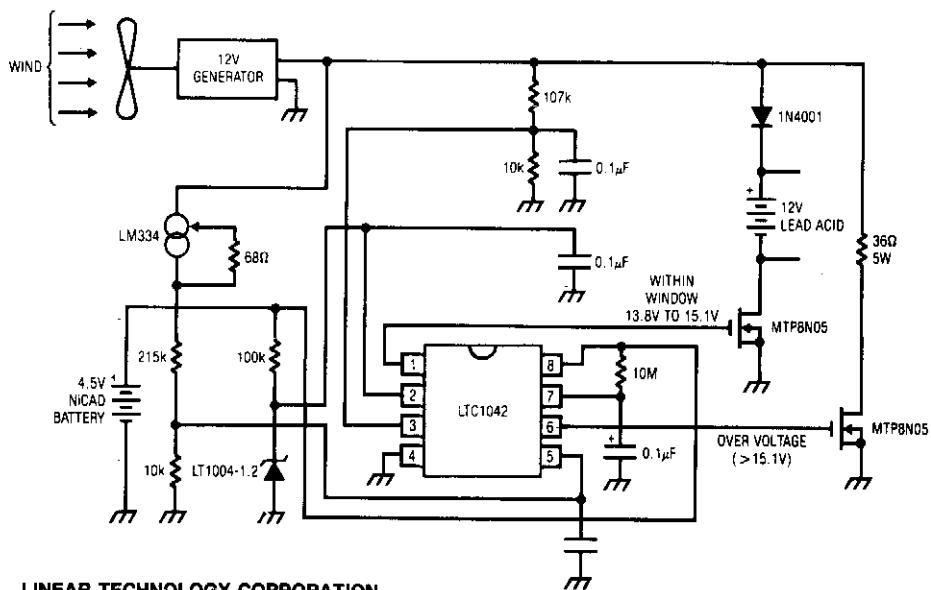

**Fig. 8-8**


### Circuit Notes

The dc motor is used as a generator with the voltage output being proportional to its rpm. The LTC1042 monitors the voltage output and provides the following control functions.

1. If generator voltage output is below 13.8 V, the control circuit is active and the Ni-Cad battery is charging through the LM334 current source. The lead acid battery is not being charged.
2. If the generator voltage output is between 13.8 V and 15.1 V, the 12 V lead acid battery is being charged at about 1 amp/hour rate (limited by the power FET).
3. If generator voltage exceeds 15.1 V (a condition caused by excessive wind speed or 12 V battery being fully charged) then a fixed load is connected limiting the generator rpm to prevent damage.

This charger can be used as a remote source of power where wind energy is plentiful such as on sailboats or remote radio repeater sites. Unlike solar powered panels, this system will function in bad weather and at night.
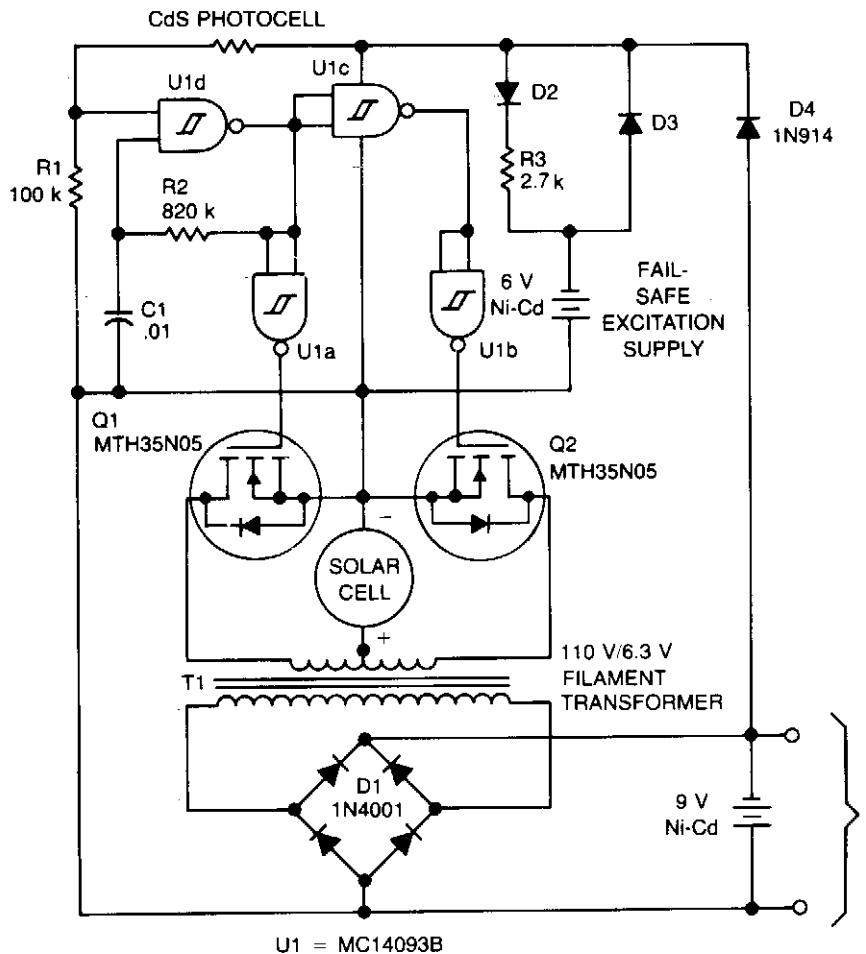
## BATTERY CHARGER OPERATES ON SINGLE SOLAR CELL



MOTOROLA


**Fig. 8-9**

### Circuit Notes

The circuit charges a 9-V battery at about 30 mA per input ampere at 0.4 V. U1, a quad Schmitt trigger, operate as an astable multivibrator to drive push-pull TMOS devices Q1 and Q2. Power for U1 is derived from the 9-V battery via D4; power for Q1 and Q2 is supplied by the solar cell. The multivibrator frequency, determined by R2-C1, is set to 180 Hz for maximum efficiency from a 6.3-V filament transformer, T1. The secondary of the transformer is applied to a full wave bridge rectifier, D1, which is connected to the batteries being charged. The small Ni-Cad battery is a fail-safe excitation supply to allow the system to recover if the 9-V battery becomes fully discharged.

A Cds photocell shuts off the oscillator in darkness to preserve the fail-safe battery during shipping and storage, or prolonged darkness.

## VERSATILE BATTERY CHARGER

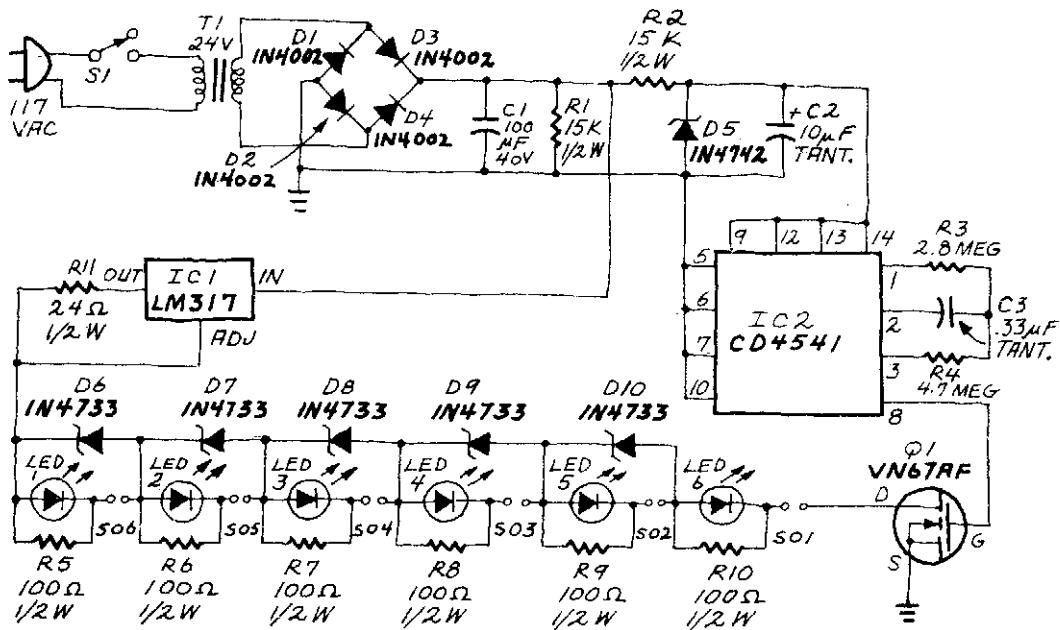

RADIO ELECTRONICS


*Fig. 8-10*

### Circuit Notes

An LM317 voltage regulator is configured as a constant-current source. It is used to supply the 50 mA charging current to S01-S06, an array of AA-cell battery holders. Each of the battery holders is wired in series with an LED and its associated shunt resistor. When the battery holder contains a battery, the LED glows during charging. Each battery holder/LED combination is paralleled by a 5.1-volt Zener diode. If the battery holder is empty, the Zener conducts the current around the holder.

A timing circuit prevents overcharging. When power is applied to the circuit, timing is initiated by IC2, a CD4541 oscillator/programmable timer. The output of IC2 is fed to Q1. When that output is high, the transistor is on, and the charging circuit is completed. When the output is low, the transistor is off, and the path to ground is interrupted.
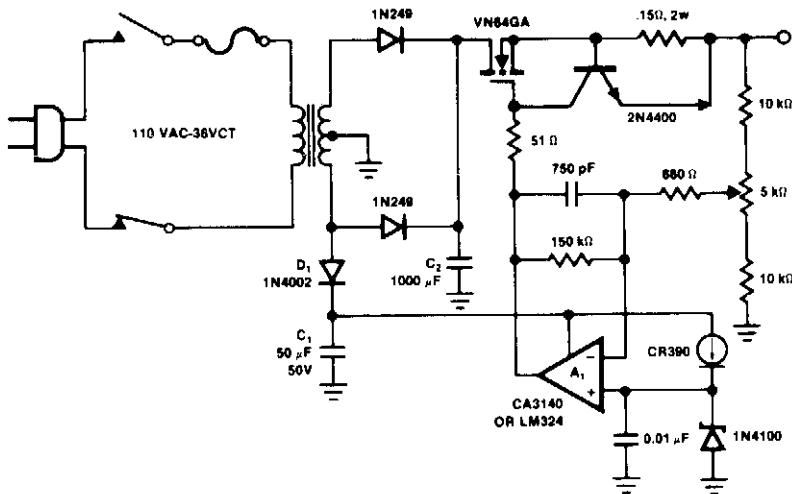
## 14-VOLT, 4-AMP BATTERY CHARGER/POWER SUPPLY



SILICONIX, INC.

**Fig. 8-11**

### Circuit Notes

Operation amplifier A1 directly drives the VN64GA with the error signal to control the output voltage. Peak rectifier D1, C1 supplies error amplifier A1 and the reference zener. This extra drive voltage must exceed its source voltage by several volts for the VN64GA to pass full load current. The output voltage is pulsating dc which is quite satisfactory for battery charging. To convert the system to a regulated dc supply, capacitor C2 is increased and another electrolytic capacitor is added across the load. The response time is very fast, being determined by the op-amp. The 2N4400 current limiter circuit prevents the output current from exceeding 4.5 A. However, maintaining a shorted condition for more than a second will cause the VN64GA to exceed its temperature ratings. A generous heat sink, on the order of  $1^{\circ}\text{C/W}$ , must be used.

# **9**


## **Battery Monitors**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Dynamic, Constant Current Load for Fuel Cell/Battery Testing
- Voltage Detector Relay for Battery Charger
- Battery Status Indicator
- Low-Battery Indicator
- A Lithium Battery's State-of-Charge Indicator
- Step-Up Switching Regulator for 6-V Battery
- Battery Voltage Monitor
- Battery Monitor

## DYNAMIC, CONSTANT CURRENT LOAD FOR FUEL CELL/BATTERY TESTING

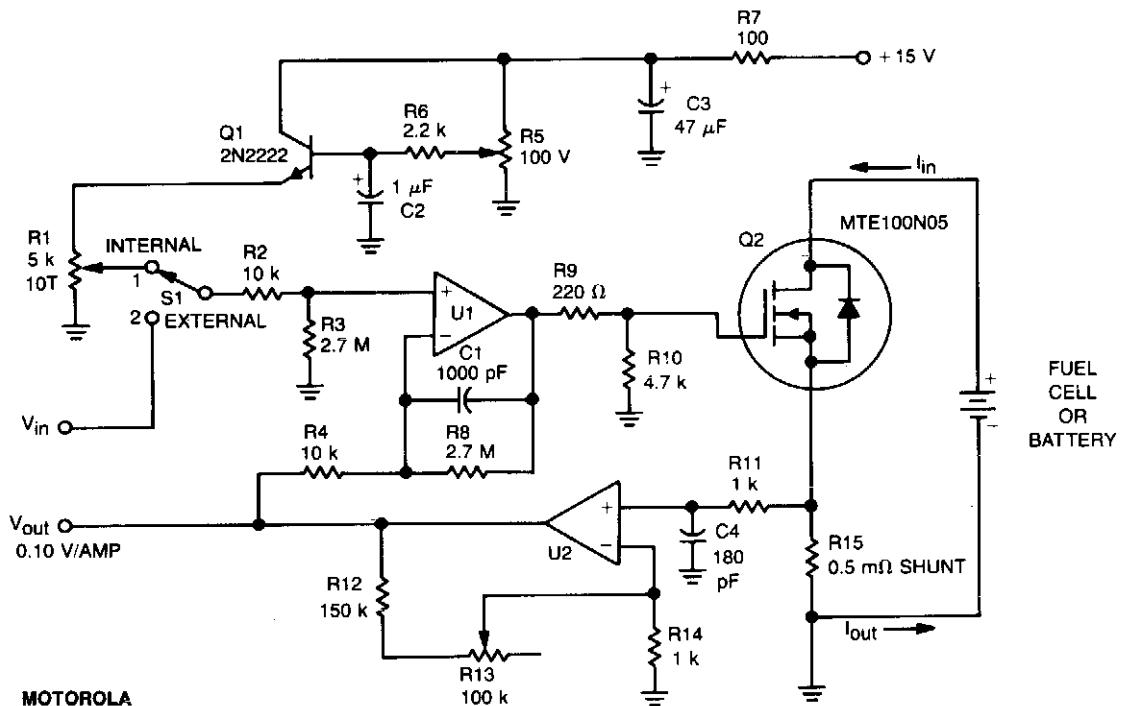

**Fig. 9-1**

### Circuit Notes


This circuit was designed for testing fuel cells, but it could also be used for testing batteries under a constant current load. It provides a dynamic, constant current load, eliminating the need to manually adjust the load to maintain a constant load.

For fuel cell application, the load must be able to absorb 20-40 A, and since a single cell develops only 0.5 to 1.0 V, bipolar power devices (such as a Darlington) are impractical. Therefore, this dynamic load was designed with a TMOS Power FET (Q2).

With switch S1 in position 1, emitter follower Q1 and R1 establish the current level for the load. In position 2, an external voltage can be applied to control the current level.

Operational amplifier U1 drives TMOS device Q1, which sets the load current seen by the fuel cell or battery. The voltage drop across R15, which is related to the load current, is then applied to U2, whose output is fed back to U1. Thus, if the voltage across R15 would tend to change, feedback to the minus input of U1 causes that voltage (and the load current) to remain constant. Adjustment of R13 controls the volts/amp of feedback. The  $V_{OUT}$  point is used to monitor the system.
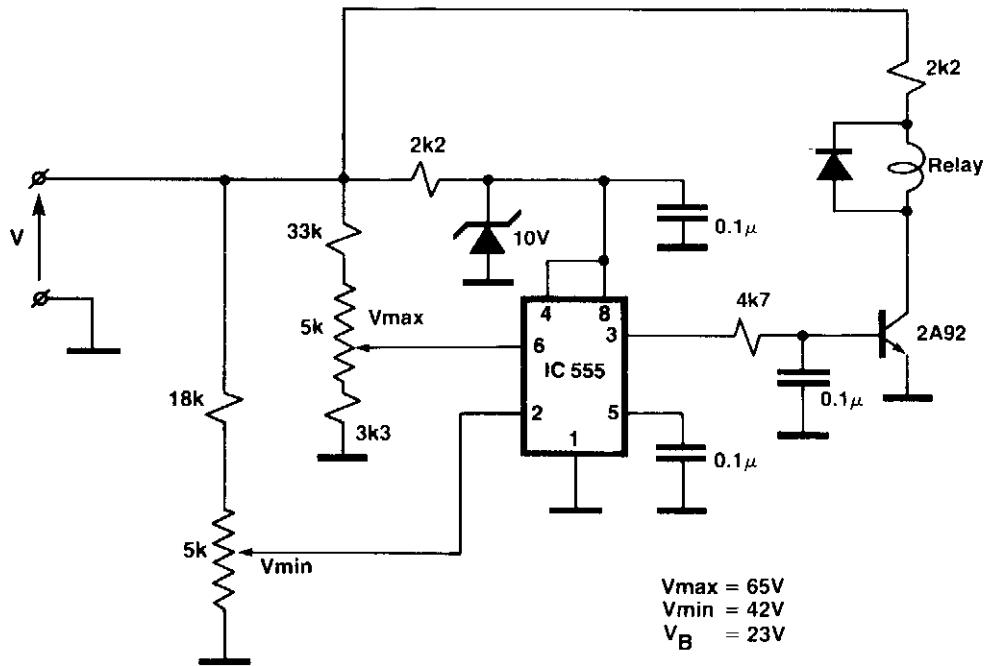
## VOLTAGE DETECTOR RELAY FOR BATTERY CHARGER



ELECTRONIC ENGINEERING

Fig. 9-2

### Circuit Notes

While the battery is being charged, its voltage is measured at V. If the measured voltage is lower than the minimum the relay will be energized, that will connect the charger circuit. When the battery voltage runs over the maximum set point, the relay is deenergized and it will be held that way until the voltage decreases below the minimum when it will be connected again. The voltage is lower than a threshold  $V_B$  (low breaking voltage) the relay will be assumed that such a low voltage is due to one or several damaged battery components. Of course  $V_B$  is much lower than the minimum set point.

### BATTERY STATUS INDICATOR

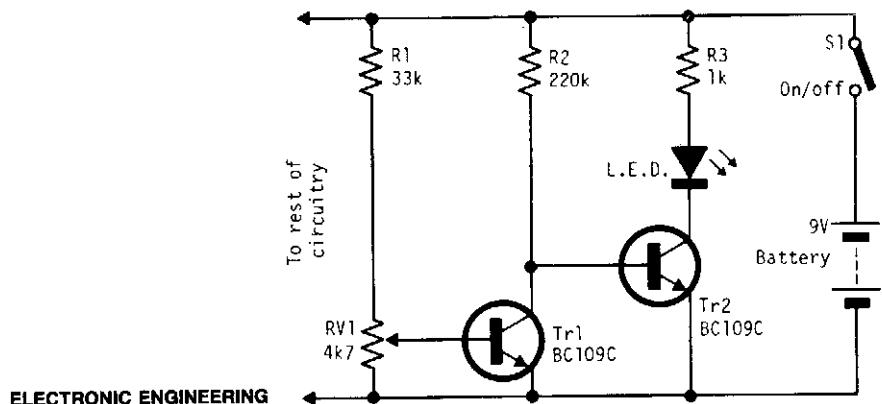


Fig. 9-3

### Circuit Notes

Continually monitors battery voltage during use and consumes only about  $250 \mu\text{A}$  (until the end point is reached). Near the end point Tr1 turns off, allowing Tr2 to illuminate the LED to increase current drain further leading to a distinct turn off point.

### LOW-BATTERY INDICATOR


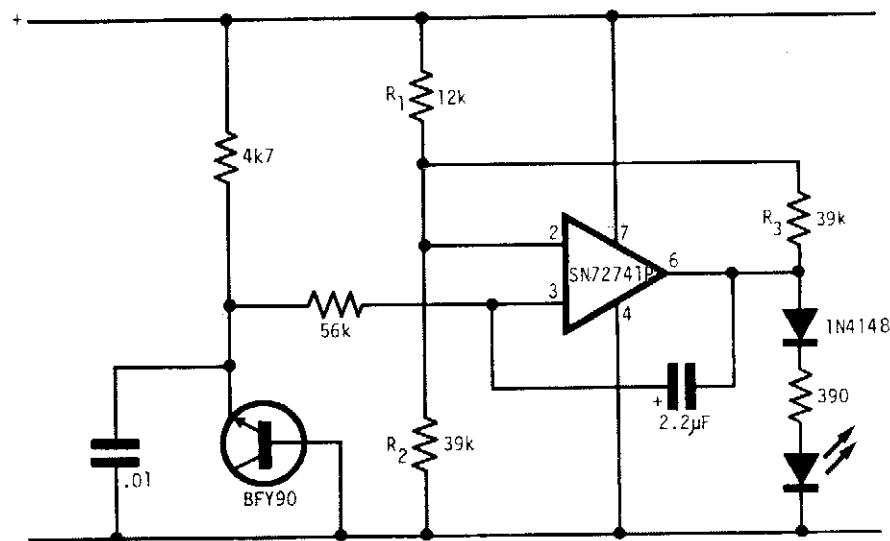


Fig. 9-4

### Circuit Notes

Under good battery conditions the LED is off. As the battery voltage falls, the LED begins to flash until, in the low battery condition, the LED lights continuously. Designed for a 9-volt battery, with the values shown the LED flashes from 7.5 to 6.5 volts.

## A LITHIUM BATTERY'S STATE-OF-CHARGE INDICATOR

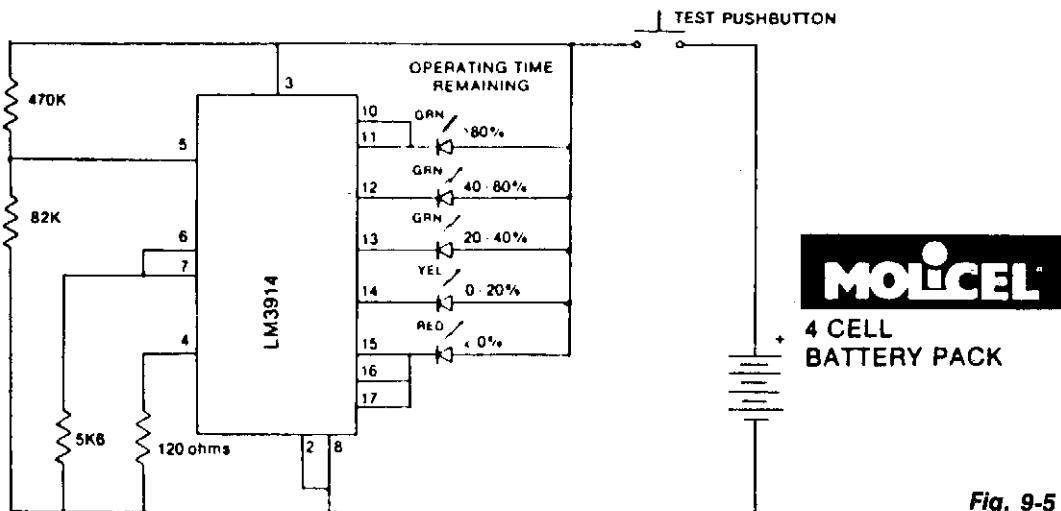


*Fig. 9-5*

MOLI ENERGY LIMITED

### Circuit Notes

State-of-Charge indication of a sloping-voltage discharge can be used as a state-of-charge indicator. A typical voltage comparator circuit that gives a visual indication of state-of-charge is shown. Components identified are for a 4-cell input voltage of 9.6 to 5.2 volts.
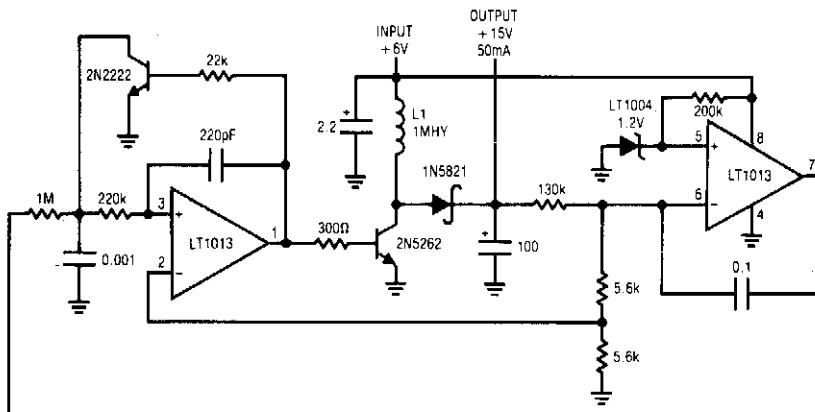
## STEP-UP SWITCHING REGULATOR FOR 6-V BATTERY




L1=AIE—VERNITRON 24-104  
78% EFFICIENCY

LINEAR TECHNOLOGY CORP.

*Fig. 9-6*

### BATTERY VOLTAGE MONITOR

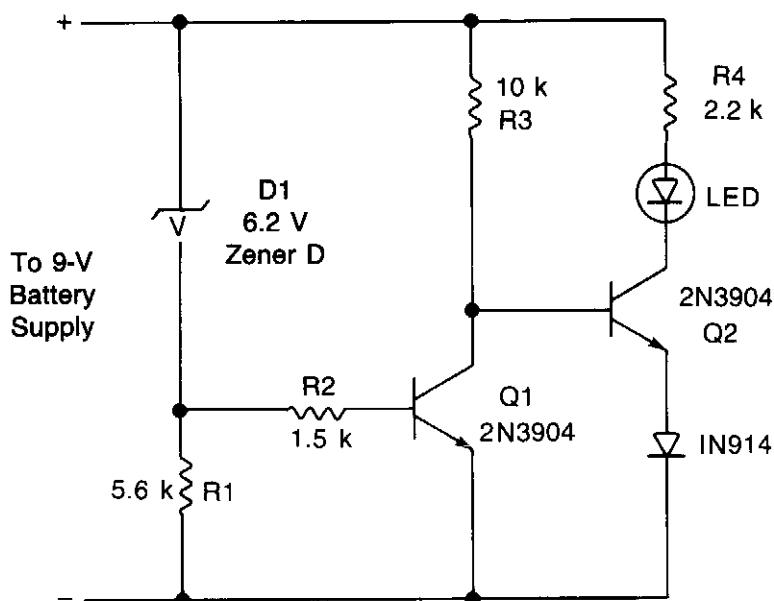


WILLIAM SHEETS

Fig. 9-7

### Circuit Notes

This circuit gives an early warning of the discharge of batteries. Zener diode D1 is chosen for the voltage below which an indication is required (9 V). Should the supply drop to below 7 V, D1 will cease conducting causing Q1 to shut off. Its collector voltage will now increase causing Q2 to start conducting via LED1 and its limiting resistor R4.

### BATTERY MONITOR

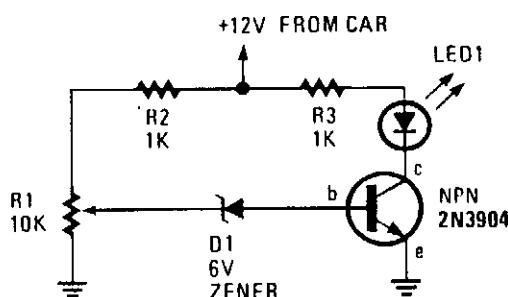

### Circuit Notes

The circuit is quick and easy to put together and install, and tells you when battery voltage falls below the set limit as established by R1 (a 10,000-ohm potentiometer). It can indicate, via LED1, that the battery may be defective or in need of change if operating the starter causes the battery voltage to drop below the present limit.

TAB BOOKS, INC.

Fig. 9-8

# **10**

## **Bridge Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Ac Bridge
- Bridge-Balance Indicator
- Bridge Circuit
- Typical Two Op Amp Bridge-Type Differential Amplifier
- Low-Power Common Source Amplifier
- Amplifier for Bridge Transducers
- Strain Gage Bridge Signal Conditioner

## AC BRIDGE

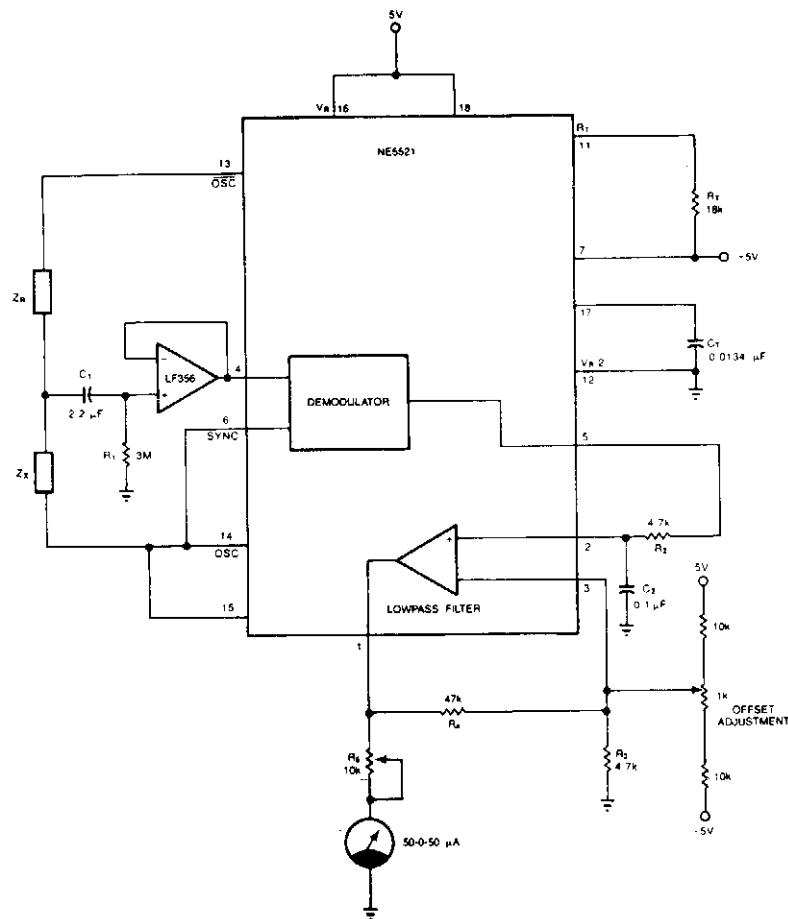


**SIGNETICS**

**Fig. 10-1**

Circuit Notes

The circuit provides a simple and cost-effective solution to matching resistors and capacitors. Impedances  $Z_R$  and  $Z_X$  form a half-bridge, while OSC and  $\bar{\text{OSC}}$  excite the bridge differentially. The external op amp is a FET input amplifier (LF356) with very low input bias current on the order of 30 pA (typical). C1 allows ac coupling by blocking the dc common mode voltage from the bridge, while R1 biases the output of LF356 to 0 V at dc. Use of FET input op amp insures that dc offset due to bias current through R1 is negligible. Ac output of the demodulator is filtered via the uncommitted amp to provide dc voltage for the meter. The 10 k potentiometer, R5, limits the current into the meter to a safe level. Calibration begins by placing equal impedances at  $Z_R$  and  $Z_X$ , and the system offset is nulled by the offset adjust circuit so that Pin 1 is at 0 V. Next, known values are placed at  $Z_X$  and the meter deviations are calibrated. The bridge is now ready to measure an unknown impedance at  $Z_X$  with  $\pm 0.05\%$  accuracy or better.

### BRIDGE-BALANCE INDICATOR

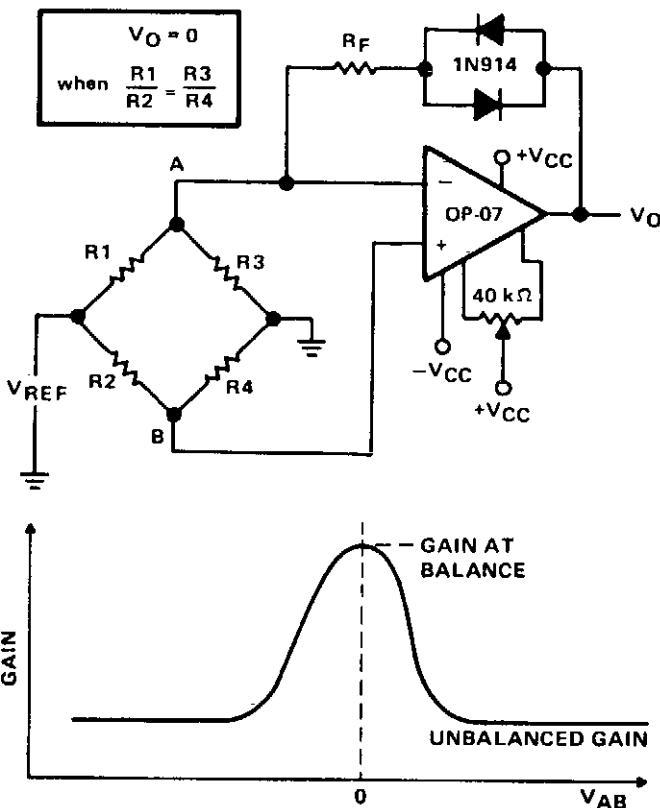

**Fig. 10-2**


TEXAS INSTRUMENTS

#### Circuit Notes

Indicator provides an accurate comparison of two voltages by indicating their degree of balance (or imbalance). Detecting small variations near the null point is difficult with the basic Wheatstone bridge alone. Amplification of voltage differences near the null point will improve circuit accuracy and ease of use.

The 1N914 diodes in the feedback loop result in high sensitivity near the point of balance ( $R_1/R_2 = R_3/R_4$ ). When the bridge is unbalanced the amplifier's closed-loop gain is approximately  $R_f/r$ , where  $r$  is the parallel equivalent of  $R_1$  and  $R_3$ . The resulting gain equation is  $G = R_f(1/R_1 + 1/R_3)$ . During an unbalanced condition the voltage at point A is different from that at point B. This difference voltage ( $V_{AB}$ ), amplified by the gain factor  $G$ , appears as an output voltage. As the bridge approaches a balanced condition ( $R_1/R_2 = R_3/R_4$ ),  $V_{AB}$  approaches zero. As  $V_{AB}$  approaches zero the 1N914 diodes in the feedback loop lose their forward bias and their resistance increases, causing the total feedback resistance to increase. This increases circuit gain and accuracy in detecting a balanced condition. The figure shows the effect of approaching balance on circuit gain. The visual indicator used at the output of the OP-07 could be a sensitive voltmeter or oscilloscope.

### BRIDGE CIRCUIT

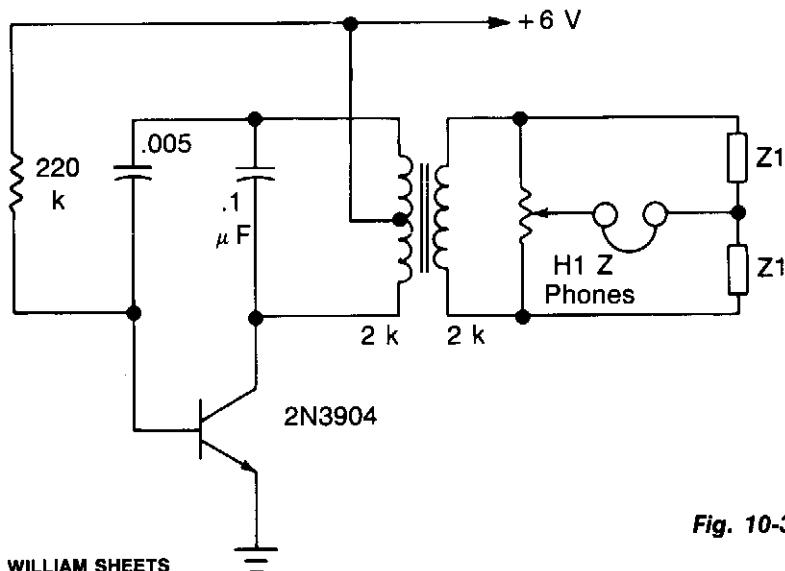


**Fig. 10-3**

WILLIAM SHEETS

### Circuit Notes

The transistor is connected as an audio oscillator, using an audio transformer in the collector. The secondary goes to a linear pot. The ratio between the two parts of the pot from the slider is proportional to the values of  $Z_1$  and  $Z_2$  when no signal is heard in the phones.
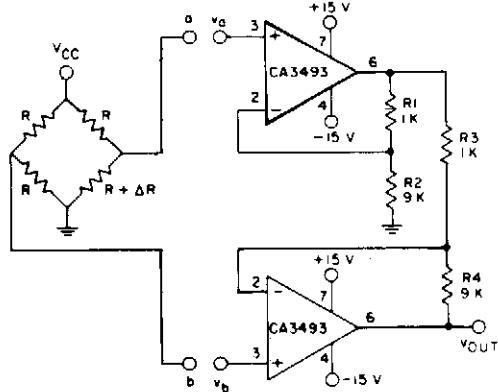
### TYPICAL TWO OP AMP BRIDGE-TYPE DIFFERENTIAL AMPLIFIER



### Circuit Notes

Using a CA3493 BiMOS op amp to provide high input impedance and good common-mode rejection ratio (depends primarily on matching of resistor networks).

$$V_{OUT} = V_b - V_o \left( \frac{R_4}{R_3} + 1 \right)$$

$$A = \frac{V_{OUT}}{V_b - V_o} = \left( \frac{R_4}{R_3} + 1 \right)$$


FOR VALUES ABOVE  $V_{OUT} = (V_b - V_o)(10)$

ALL RESISTANCE VALUES  
ARE IN OHMS

GENERAL ELECTRIC/RCA

**Fig. 10-4**

## LOW-POWER COMMON SOURCE AMPLIFIER

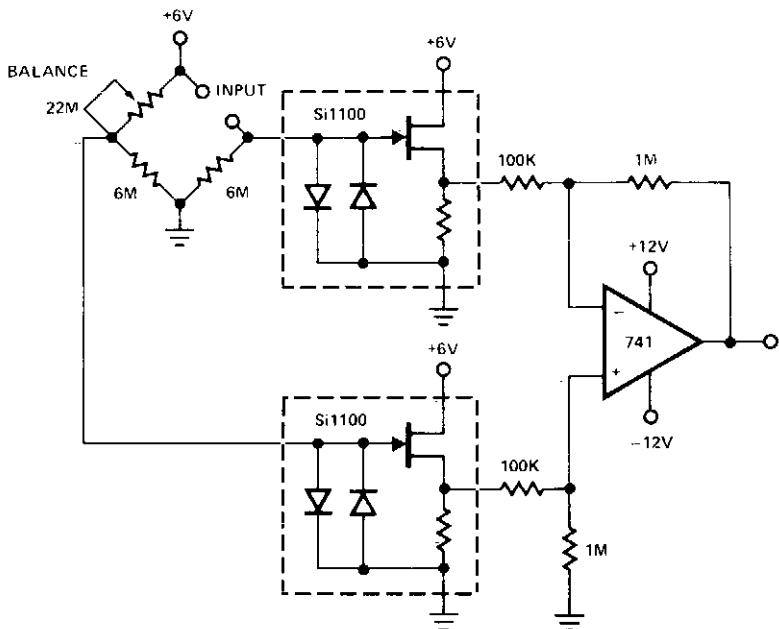


SILICONIX, INC.

**Fig. 10-5**

### Circuit Notes

A circuit that will operate in the 10- to 20- microamp range at a 12-volt supply voltage. The diode protection is available in this configuration. The circuit voltage gain will be between 10 and 20, with extremely low power consumption (approximately  $250 \mu\text{W}$ ). This is very desirable for remote or battery operation where minimum maintenance is important.


## AMPLIFIER FOR BRIDGE TRANSDUCERS

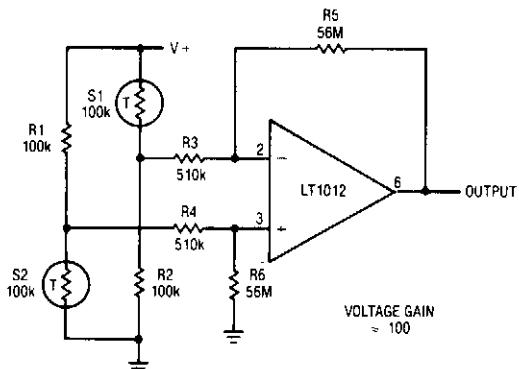

**Fig. 10-6**

LINEAR TECHNOLOGY CORP.
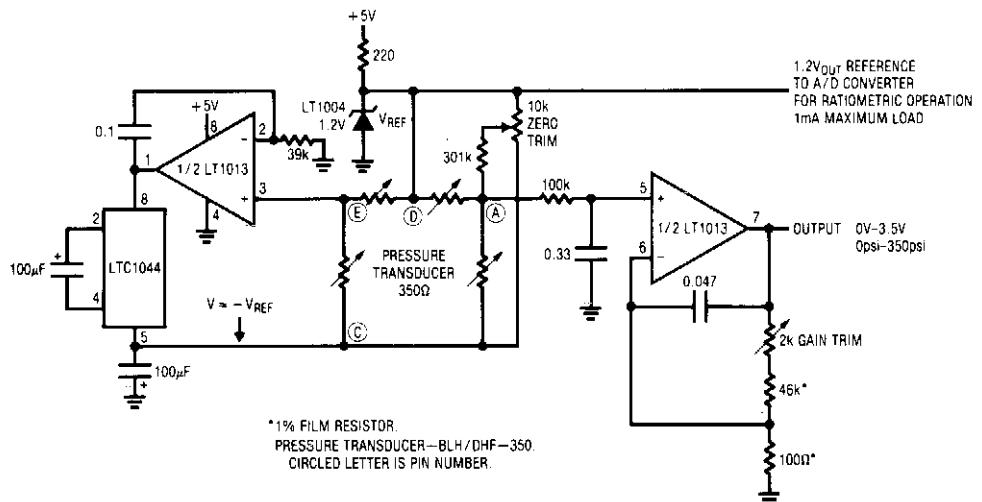
## STRAIN GAUGE BRIDGE SIGNAL CONDITIONER



LINEAR TECHNOLOGY CORP.

**Fig. 10-7**

# 11


## Burst Generators

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Single-Tone Burst Generator
- Square Waveform Multiburst Generator
- Single-Timer IC Provides Square-Wave Tone Bursts
- Strobe-Tone Burst Generator
- Tone Burst Generator

## SINGLE-TONE BURST GENERATOR

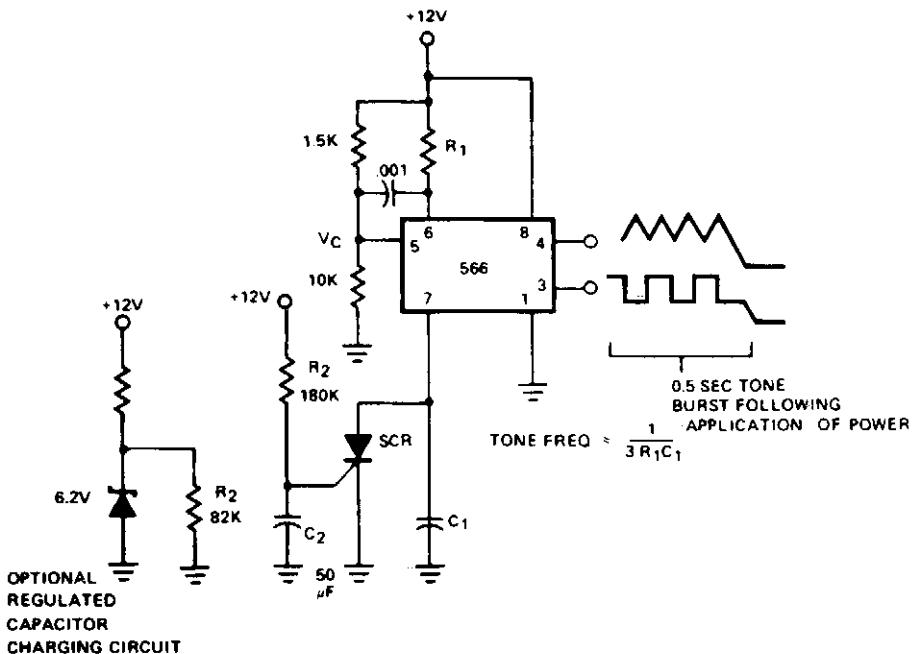

SIGNETICS

Fig. 11-1

### Circuit Notes

The tone burst generator supplies a tone for one-half second after the power supply is activated; its intended use is a communications network alert signal. Cessation of the tone is accomplished at the SCR, which shunts the timing capacitor C1 charge current when activated. The SCR is gated on when C2 charges up to the gate voltage which occurs in 0.5 seconds. Since only  $70 \mu\text{A}$  are available for triggering, the SCR must be sensitive enough to trigger at this level. The triggering current can be increased, of course, by reducing R2 (and increasing C2 to keep the same time constant). If the tone duration must be constant under widely varying supply voltage conditions, the optional Zener diode regulator circuit can be added, along with the new value for  $R_2 R_2' = 82 \text{ k}\Omega$ . If the SCR is replaced by an npn transistor, the tone can be switched on and off at will at the transistor base terminal.

## SQUARE WAVEFORM MULTIBURST GENERATOR

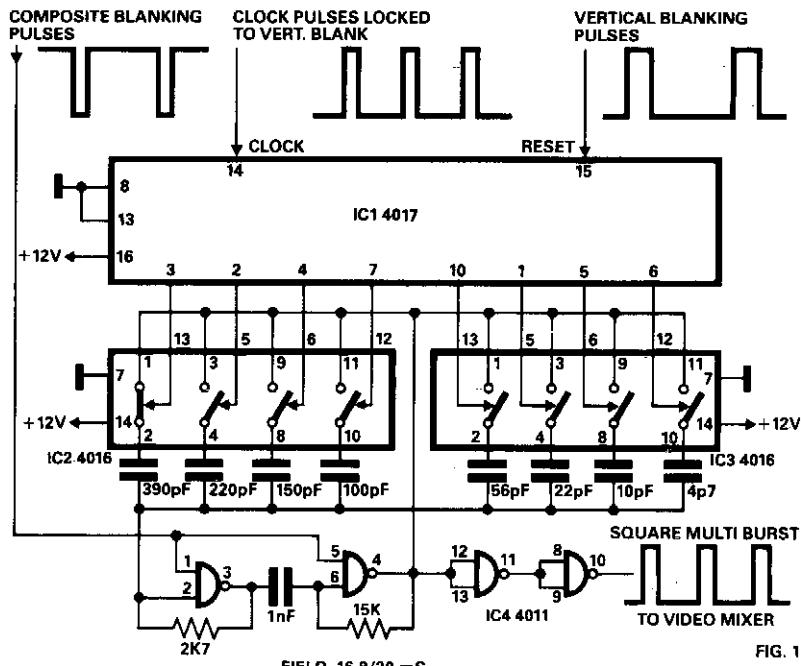


FIG. 1

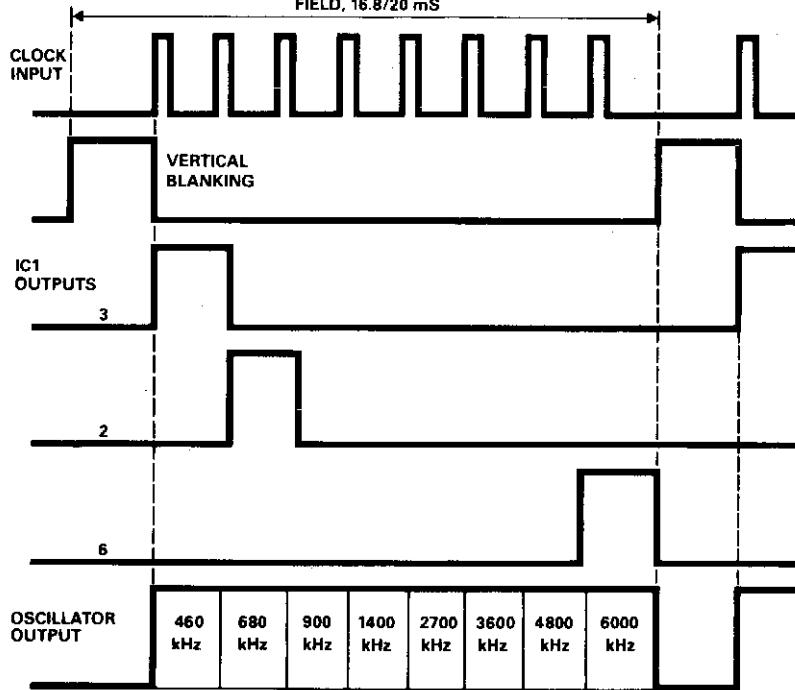


Fig. 11-2


## SQUARE WAVEFORM MULTIBURST GENERATOR, Continued.

### Circuit Notes

The generator described here is intended for multiburst signal square waveform generation and can be used as a device for characterizing the response of TV monitor amplifiers as shown. The circuit is an RC oscillator with NAND gates (IC4-4011), with its capacitor C changed periodically by means of bilateral switches (IC2, IC3-4016). The control inputs of bilateral switches are driven by the outputs of a counter/decoder (IC1-4017) the operation of which is determined by generated clock pulses, so that they occur eight times at half-picture (field). These pulses are locked to vertical blank pulses.

Horizontal synchronization is achieved by means of composite blanking pulses (negative polarization) applied to pins 1 and 5 of IC4. The oscillator frequency changes in the following discrete steps: 460 kHz, 680 kHz, 900 kHz, 1400 kHz, 2700 kHz, 3600 kHz, for the time of one frame. The video signal is fed on a mixer where it is superimposed with a composite sync signal.
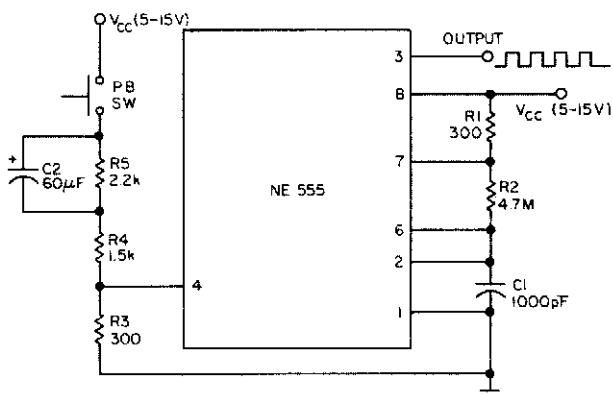
## SINGLE-TIMER IC PROVIDES SQUARE-WAVE TONE BURSTS



ELECTRONIC DESIGN

Fig. 11-3

### Circuit Notes

The tone-burst generator gives a 50-ms burst of 1.5 kHz square waves with each operation of the pushbutton and can source or sink 200 mA.

## STROBE-TONE BURST GENERATOR


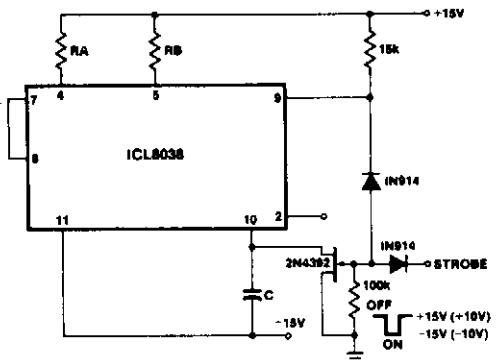


Fig. 11-4

INTERSIL

## TONE BURST GENERATOR

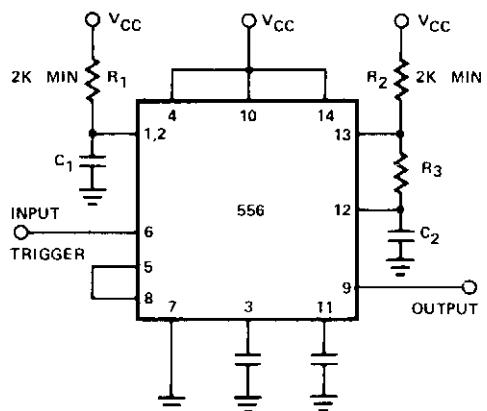

### Circuit Notes

The dual timer makes an excellent tone burst generator. The first half is connected as a one shot and the second half as an oscillator. The pulse established by the one shot turns on the oscillator allowing a burst of pulses to be generated.

SIGNETICS

Fig. 11-5

# 12

## Capacitance Meters

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Capacitance-to-Voltage Meter  
Accurate Digital Capacitance Meter

## CAPACITANCE-TO-VOLTAGE METER

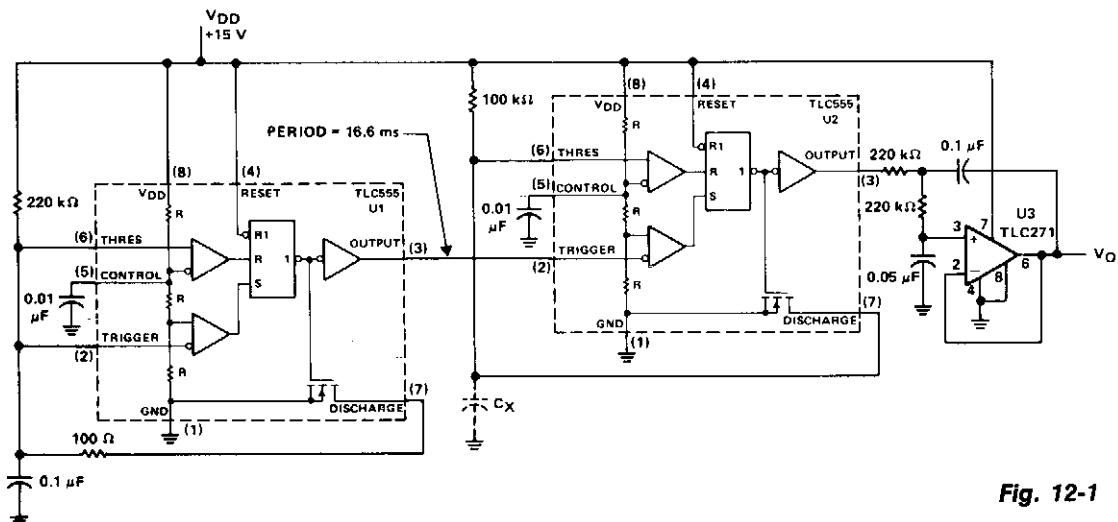


Fig. 12-1


TEXAS INSTRUMENTS

### Circuit Notes


Timer U1 operates as a free-running oscillator at 60 Hz, providing trigger pulses to timer U2 which operates in the monostable mode. Resistor R1 is fixed and capacitor Cx is the capacitor being measured. While the output of U2 is 60 Hz, the duty cycle depends on the value of Cx. U3 is a combination low-pass filter and unity-gain follower whose dc voltage output is the time-averaged amplitude of the output pulses of U2, as shown in the timing diagram.

The diagram shows when the value of Cx is small the duty cycle is relatively low. The output pulses are narrow and produce a lower average dc voltage level at the output of U3. As the capacitance value of Cx increases, the duty cycle increases making the output pulses at U2 wider and the average dc level output at U3 increases. The graph illustrates capacitance values of 0.01  $\mu$ F to 0.1  $\mu$ F plotted against the output voltage of U3. Notice the excellent linearity and direct one-to-one scale calibration of the meter. If this does not occur the 100 k ohm resistor, R1, can be replaced with a potentiometer which can be adjusted to the proper value for the meter being used.

## CAPACITANCE-TO-VOLTAGE METER (CONT'D)

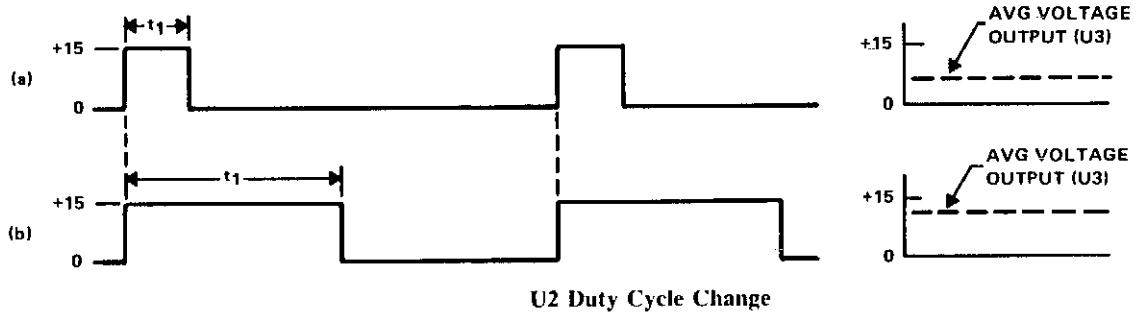

U2 Duty Cycle Change

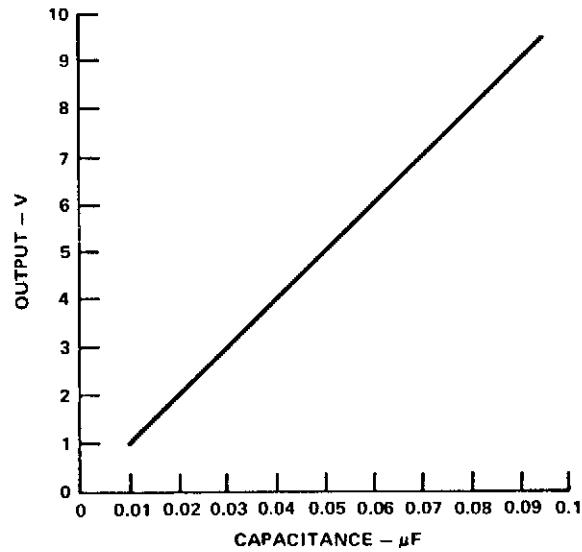

TEXAS INSTRUMENTS

Fig. 12-1

## ACCURATE DIGITAL CAPACITANCE METER

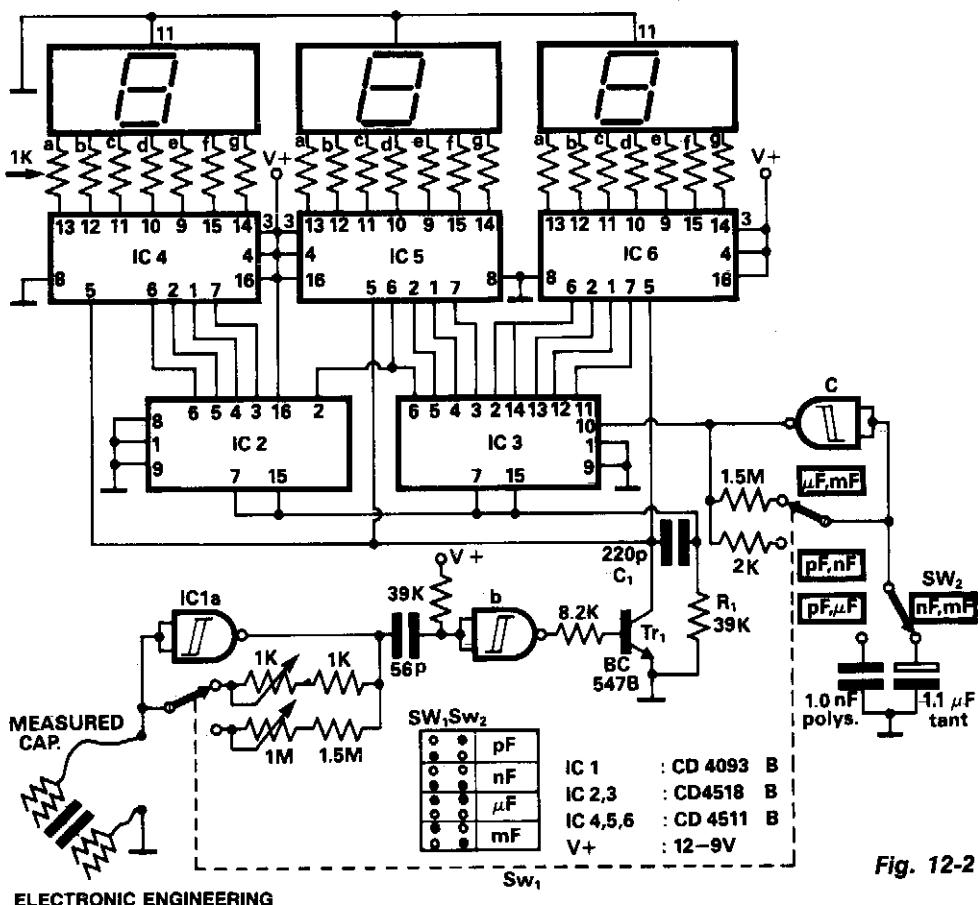


Fig. 12-2

ELECTRONIC ENGINEERING

### Circuit Notes

The principle of operation is counting the pulse number derived from a constant frequency oscillator during a fixed time interval produced by another lower frequency oscillator. This oscillator uses the capacitor being measured as the timing. The capacitance measurement is proportional during pulse counting during a fixed time interval. The astable oscillator formed by IC1c produces a pulse train of constant frequency. Gate IC1a also forms an oscillator whose oscillation period is given approximately by the equation:  $T = 0.7 RC$ .

Period T is linearly dependent on the capacitance C. This period is used as the time interval for one measurement. The differentiator network following the oscillator creates the negative spikes shaped in narrow pulses by IC1b NAND Schmitt Trigger. The differentiator formed by R1 and C1 produces a negative spike which resets the counters. The display shows the number of high frequency oscillator pulses entering the counter during the measurement period.

# 13

## Circuit Protection Circuits


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Overvoltage Protector
- High Speed Electronic Circuit Breaker
- 12 ns Circuit Breaker
- Low Voltage Power Disconnector
- Automatic Power-Down Protection Circuit
- Line Dropout Detector
- Electronic Crowbar

## OVERVOLTAGE PROTECTOR

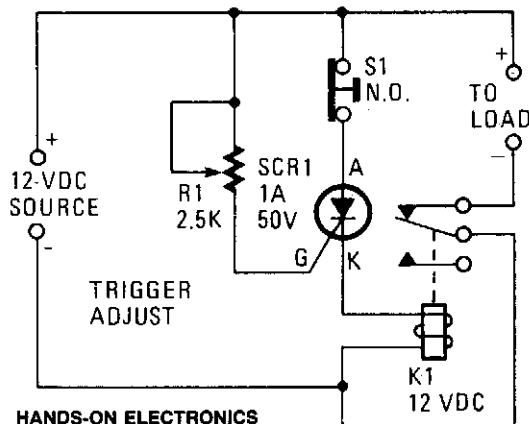


**Fig. 13-1**

### Circuit Notes

A silicon-controlled rectifier is installed in parallel with the 12-V line and connected to a normally-closed 12-V relay, K1. The SCR's gate circuit is used to sample the applied voltage. As long as the applied voltage stays below a given value, SCR1 remains off and K1's contacts remain closed, thereby supplying power to the load. When the source voltage rises above 12 V, sufficient current is applied to the gate of SCR1 to trigger it into conduction. The trigger point of SCR1 is dependent on the setting of R1. Once SCR1 is triggered (activating the relay), K1's contacts open, halting current flow to the load.

## HIGH SPEED ELECTRONIC CIRCUIT BREAKER

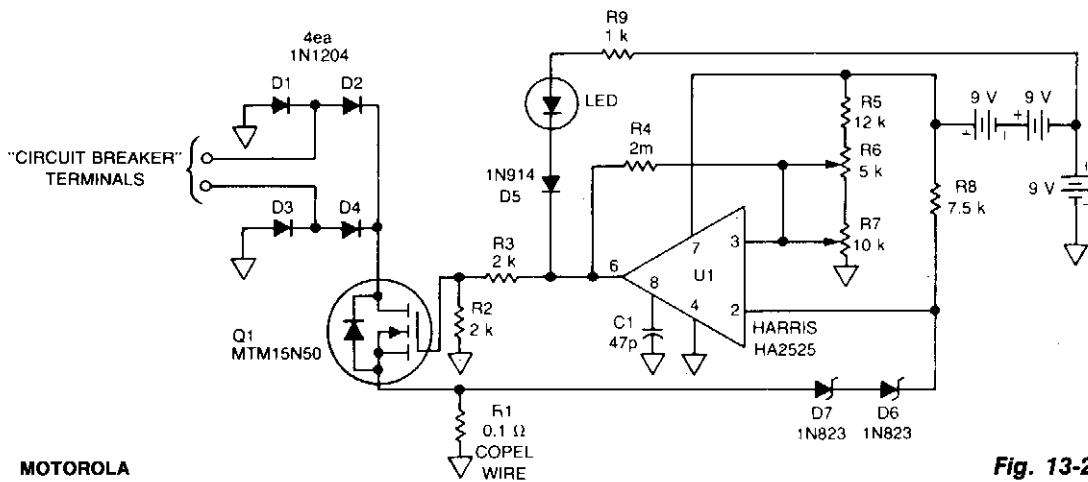

**Fig. 13-2**


### Circuit Notes

This 115 Vac, electronic circuit breaker uses the low drive power, low on resistance and fast turn off of the TMOS MTM15N50. The trip point is adjustable, LED fault indication is provided and battery power provides complete circuit isolation.

The two "circuit breaker" terminals are across one leg of a full wave diode bridge consisting of D1-D4. Normally, Q1 is turned ON so that the circuit breaker looks like a very

low resistance. One input to comparator U1 is a fraction of the internal battery voltage and the other input is the drop across zeners D6 and D7 and the voltage drop across R1. If excessive current is drawn, the voltage drop across R1 increases beyond the comparator threshold (determined by the setting of R6), U1 output goes low, Q1 turns OFF, and the circuit breaker "opens." When this occurs, the LED fault indicator is illuminated.

## **12 ns CIRCUIT BREAKER**

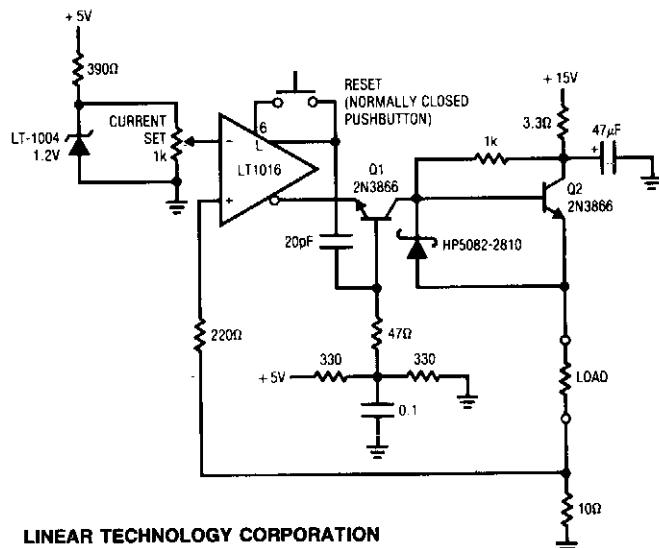

*Fig. 13-3*


LINEAR TECHNOLOGY CORPORATION

Circuit Notes

This circuit will turn off current in a load 12 ns after it exceeds a preset value. Under normal conditions the voltage across the 10 ohm shunt is smaller than the potential at the LT1016's negative input. This keeps Q1 off and Q2 receives bias, driving the load. When an overload occurs the current through the 10 ohm sense resistor begins to increase. When this current exceeds the preset value, the LT1016's outputs reverse. This provides ideal turn-on drive for Q1 and it cuts off Q2 in 5 ns. The delay from the onset of excessive load current to complete shutdown is just 13 ns. Once the circuit has triggered, the LT1016 is held in its latched state by feedback from the non-inverting output. When the load fault has been cleared the pushbutton can be used to reset the circuit.

## **LOW VOLTAGE POWER DISCONNECTOR**


Circuit Notes

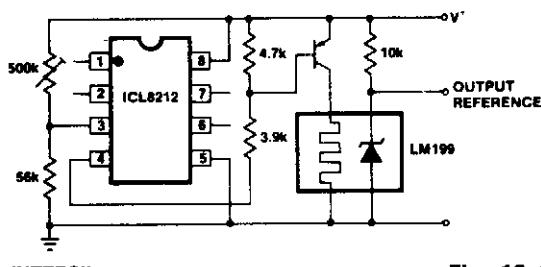

**Fig. 13-4**

There are some classes of circuits that require the power supply to be disconnected if the power supply voltage falls below a certain value. As an example, the National LM199 precision reference has an on chip heater which malfunctions with supply voltages below 9 volts causing an excessive device temperature. The ICL8212 can be used to detect a power supply voltage of 9 volts and turn the power supply off to the LM199 heater section below that voltage.
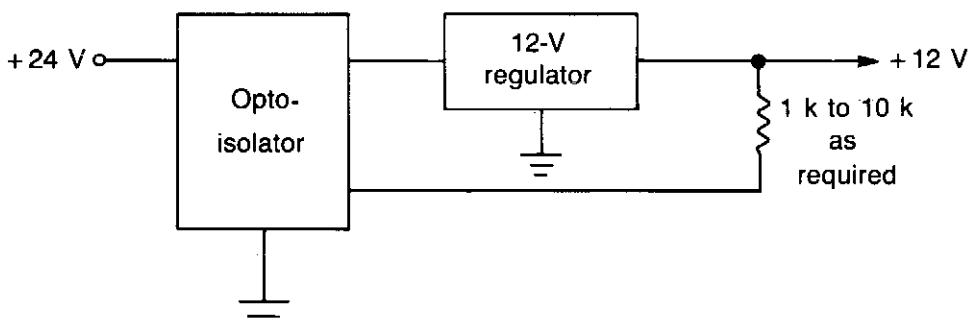
## AUTOMATIC POWER-DOWN PROTECTION CIRCUIT




WILLIAM SHEETS

*Fig. 13-5.*

### Circuit Notes

This circuit is faster than a fuse and automatically resets itself when a short is removed. The normal regulated dc input line is opened and the phototransistor of the opto isolator is connected in series with the source and regulator. Between the output of the regulator and ground is a LED and an associated current-limiting resistor, placed physically close to the surface of the photosensitive device. As long as the regulator is delivering its rated output, the LED glows and causes the photo device to have a low resistance. Full current is thus allowed to flow. If a short circuit occurs on the output side of the regulator, the LED goes dark, the resistance of the photo device increases, and the regulator shuts off. When the short is removed, the LED glows, and the regulator resumes operation.


## LINE DROPOUT DETECTOR

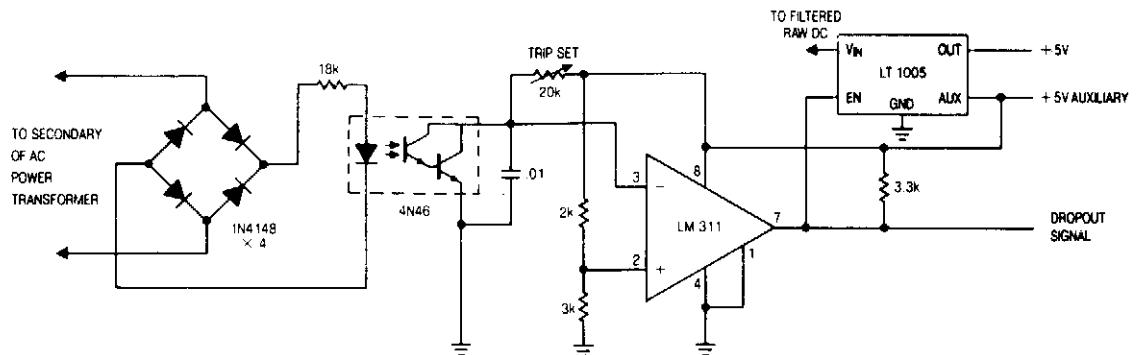

LINEAR TECHNOLOGY CORP.

*Fig. 13-6*

## ELECTRONIC CROWBAR

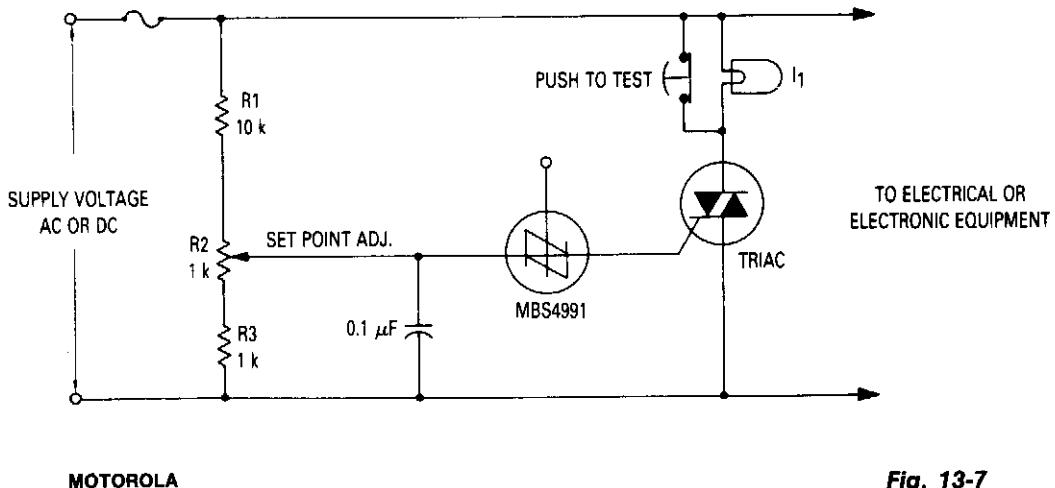

MOTOROLA

*Fig. 13-7*

### Circuit Notes

Where it is desirable to shut down equipment rather than allow it to operate on excessive supply voltage, an electronic "crowbar" circuit can be employed to quickly place a short-circuit across the power lines, thereby dropping the voltage across the protected device to near zero and blowing a fuse. Since the TRIAC and SBS are both bilateral devices, the circuit is equally useful on ac or dc supply lines. With the values shown for  $R_1$ ,  $R_2$  and  $R_3$ , the crowbar operating point can be adjusted over the range of 60 to 120 volts dc or 42 to 84 volts ac. The resistor values can be changed to cover a different range of supply voltages. The voltage rating of the TRIAC must be greater than the highest operating point as set by  $R_2$ .  $I_1$  is a low power incandescent lamp with a voltage rating equal to the supply voltage. It may be used to check the set point and operation of the unit by opening the test switch and adjusting the input or set point to fire the SBS.

# 14

## Clock Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Three Phase Clock From a Reference Clock  
60 Hz Clock Pulse Generator

### THREE PHASE CLOCK FROM A REFERENCE CLOCK


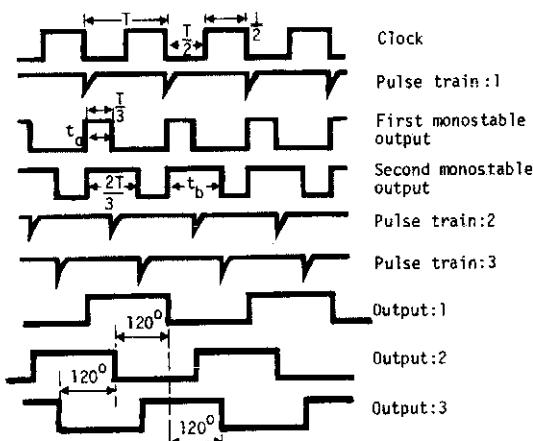


Fig. 14-1

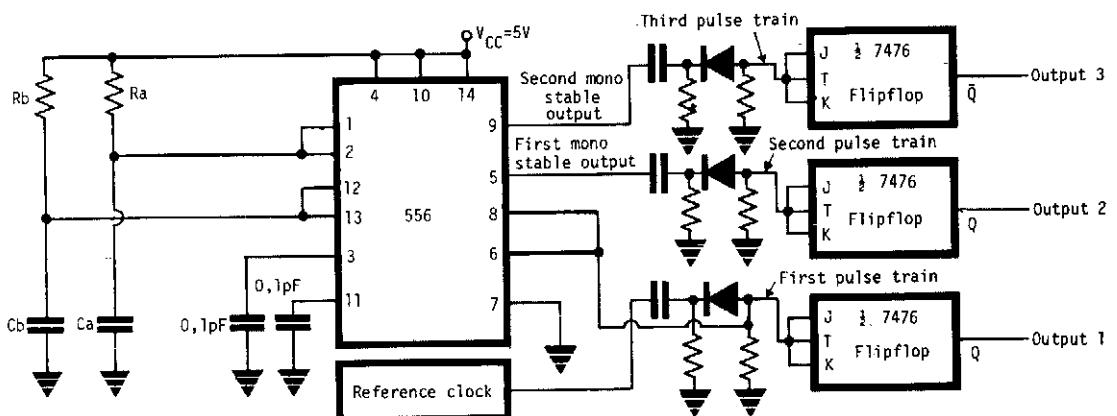


ELECTRONIC ENGINEERING

#### Circuit Notes

The circuit provides three square wave outputs with  $120^\circ$  of phase difference between each other. Reference clock frequency is twice that of the required frequency. This can be obtained from a crystal oscillator with a chain of dividers or by using LM 555 in 50% duty cycle astable mode. If  $1/T$  is the frequency of the reference clock, the dual timer 556 is connected to give two mono-stable output pulses of duration  $T/3$  and  $2T/3$ . The first timer R and C value are adjusted so that  $t_a = 1.1RaCa = T/3$  and the second timer R and C values so that  $t_b = 1.1RbCb = 2T/3$ . For triggering the two monostables a negative pulse train (1st) is derived from the reference clock with a differentiator and a clipper combination as shown. The three pulse trains trigger three JK flip flops giving three phase square wave outputs.

## 60 Hz CLOCK PULSE GENERATOR

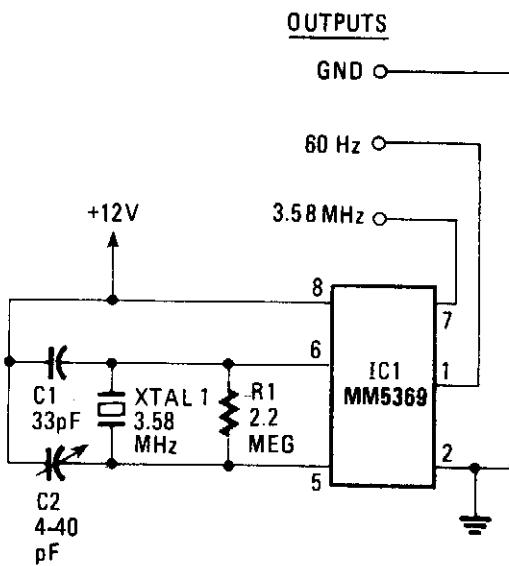

### Circuit Notes

The circuit provides a clean, stable square wave and it will operate on anywhere from 6 to 15 volts. The IC and color-burst crystal are the kind used in TV receivers. The 3.58 MHz output makes a handy marker signal for shortwave bands.

HANDS-ON ELECTRONICS

Fig. 14-2

# 15

## Comparators

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low-Power Comparator with Less than 10  $\mu$ V  
Hysteresis

Voltage Monitor/Comparator

Limit Comparator

Double-Ended Limit Comparator

Low-Cost Comparator and Display

Window Comparator

Comparator Detects Power Supply Overvoltages,  
Catches Glitches

High-Low Level Comparator with One Op Amp  
High-Input-Impedance Window Comparator


Frequency Comparator

Demonstration Comparator Circuit

LED Frequency Comparator

TTL-Compatible Schmitt Trigger


### LOW-POWER COMPARATOR WITH LESS THAN 10 $\mu$ V HYSTERESIS

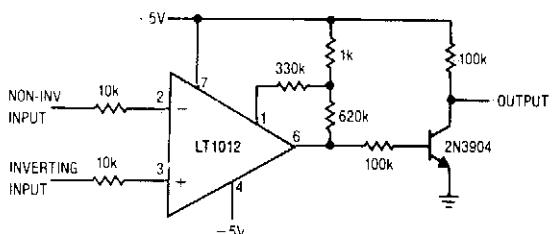

*Fig. 15-1*

LINEAR TECHNOLOGY CORP.

### VOLTAGE MONITOR/COMPARATOR

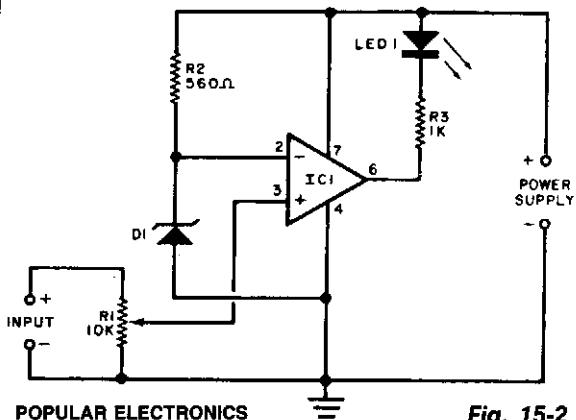


POPULAR ELECTRONICS

*Fig. 15-2*

### Circuit Notes

A portion of the monitored voltage (determined by R1's adjustment) is compared to a fixed voltage obtained from a zener reference network, R2-D1. As long as the monitored voltage remains at or above its present monitor point (determined by R1's setting), the output indicator, LED1, remains dark. If the voltage drops below this level, the LED goes on. D1 is a 3.3-V zener. A 12 Vdc power supply is suitable for monitoring input voltages of up to 12 volts.


### LIMIT COMPARATOR

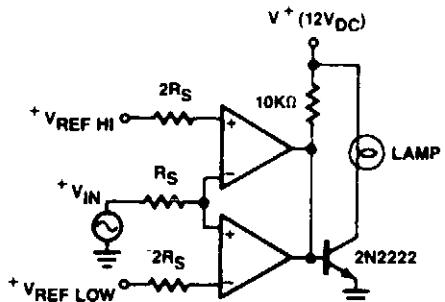

SIGNETICS


*Fig. 15-3*

## DOUBLE-ENDED LIMIT COMPARATOR

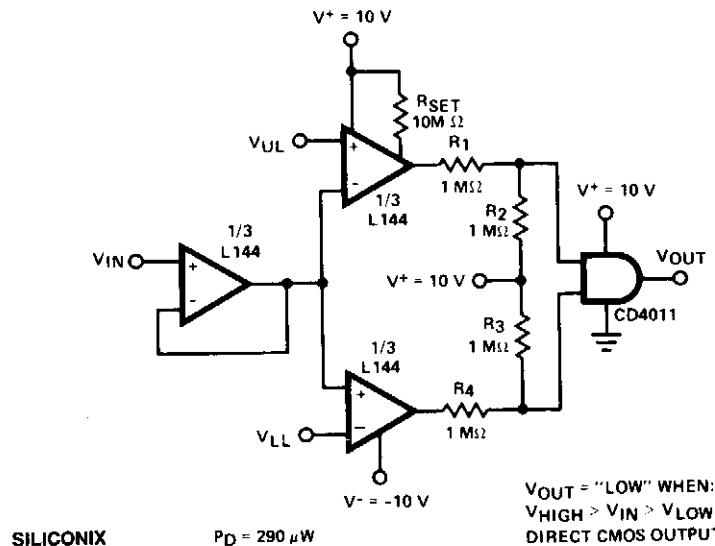

**Fig. 15-4**

## LOW-COST COMPARATOR AND DISPLAY

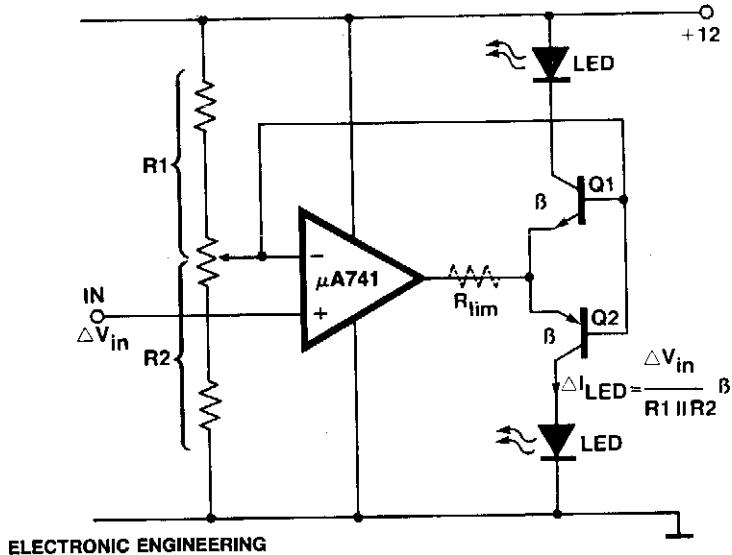

**Fig. 15-5**

**ELECTRONIC ENGINEERING**

### Circuit Notes

An op amp is used as a comparator and a sink for LED current. The output voltage of the amplifier changes about 1.4 V depending on the direction of the current. Only one transistor is on at any time. Maximum LED current is limited to 25 mA by overcurrent protection of the uA741. If LEDs are not capable of carrying such a current or an alternative op amp is used and an additional resistor  $R_{\text{lim}}$  is necessary.

## WINDOW COMPARATOR

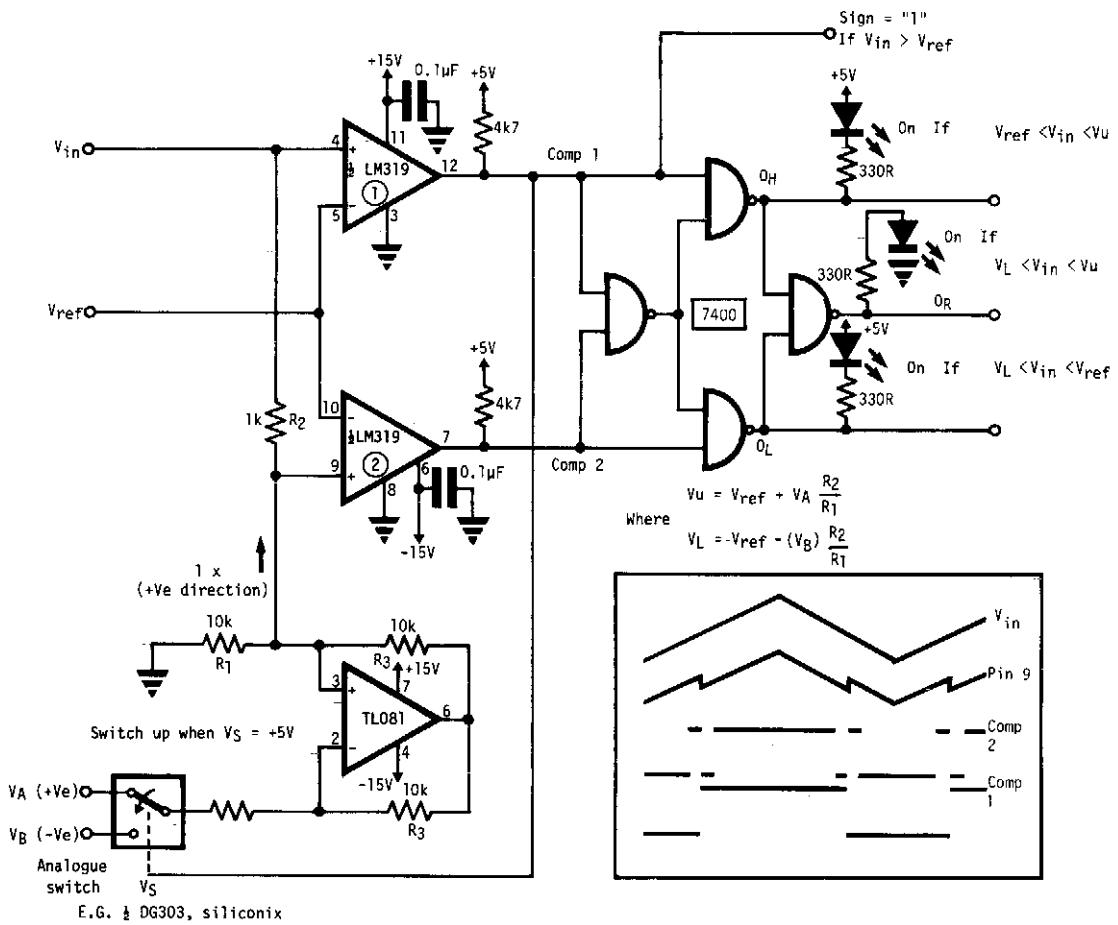


Fig. 15-6

ELECTRONIC ENGINEERING

### Circuit Notes

This circuit provides independently adjustable upper and lower threshold settings, and has sign, in window range, in upper window, and in lower window digital outputs.

## COMPARATOR DETECTS POWER SUPPLY OVERVOLTAGES, CATCHES GLITCHES

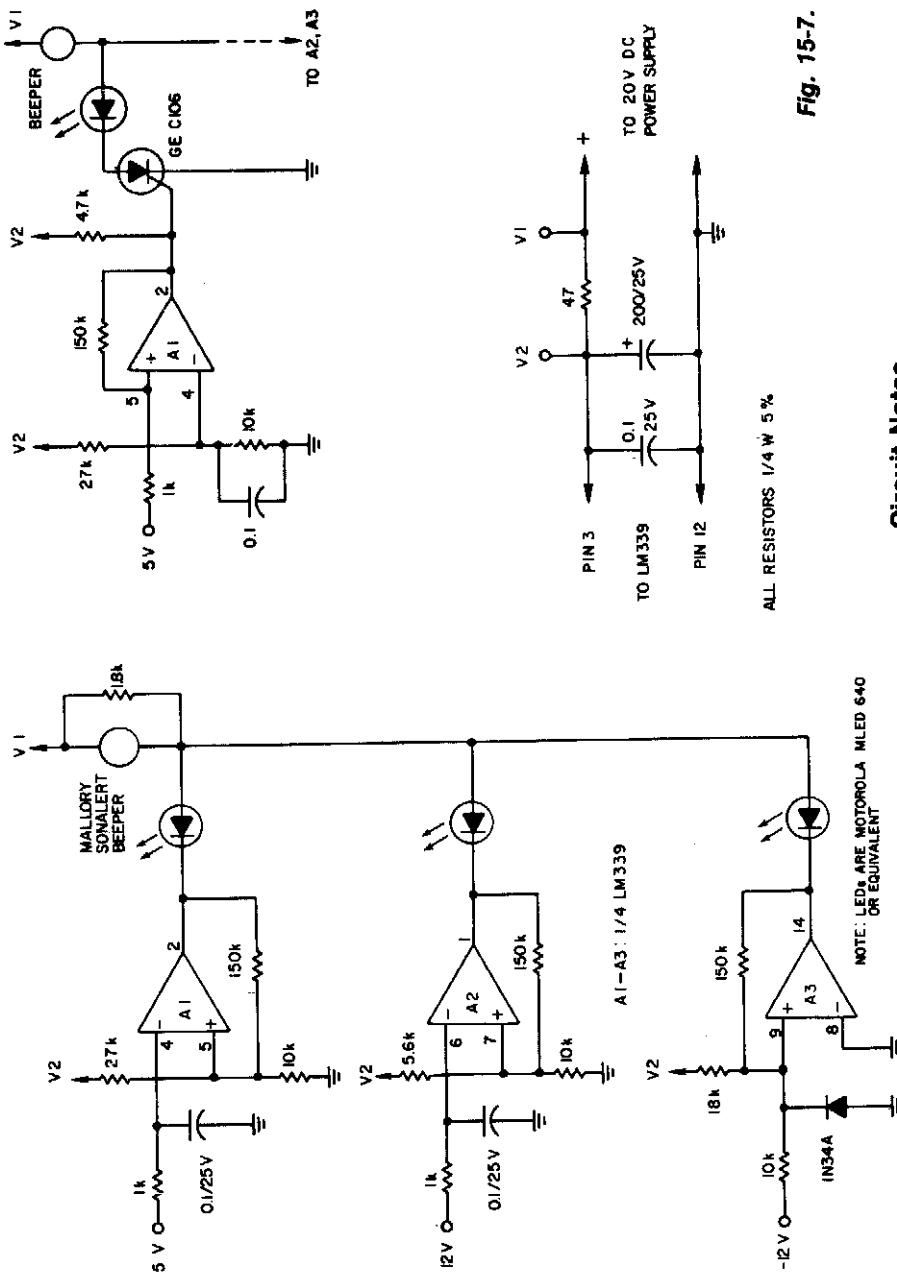



Fig. 15-7.

## ELECTRONIC DESIGN

### Circuit Notes

- (A) To maintain an alarm condition when an overvoltage transient disappears, add an SCR to the comparator circuits. For SCR operation, voltages to the comparator inputs are inverted. (B) The triple-voltage monitoring circuit detects transient power-supply overvoltages. If excessive voltage momentarily appears at the 5, 12 and -12 V inputs, the LED for that circuit lights and the beeper sounds for as long as the overvoltage lasts.

### HIGH-LOW LEVEL COMPARATOR WITH ONE OP AMP

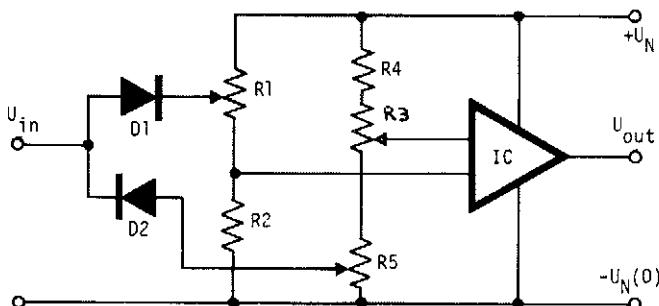


**Fig. 15-8**

ELECTRONIC ENGINEERING

### Circuit Notes

The voltage to be compared is fed through diode  $D_1$  and  $D_2$  to the voltage dividers  $R_1$  and  $R_5$  where the low and high limits are present. When the voltage level of an input signal exceeds the high threshold limit set with potentiometer  $R_1$ , the diode  $D_1$  becomes forward biased and the increased voltage on the inputs of the op amp drives it into positive saturation. Similarly, a decrease of the input voltage at the op amp inputs turns the op amp to positive saturation. Potentiometer  $R_3$  is used for zeroing the op amp in the off state.

### HIGH-INPUT-IMPEDANCE WINDOW COMPARATOR

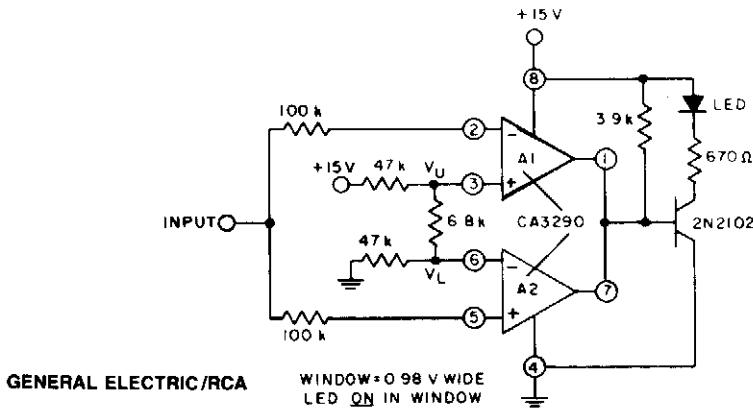

**Fig. 15-9**

GENERAL ELECTRIC/RCA

WINDOW = 0.98 V WIDE  
LED ON IN WINDOW

### Circuit Notes

The circuit uses both halves of the CA3290 BiMOS dual voltage comparator. The LED will be turned "ON" whenever the input signal is above the lower limit ( $V_L$ ) but below the upper limit ( $V_U$ ).

## FREQUENCY COMPARATOR

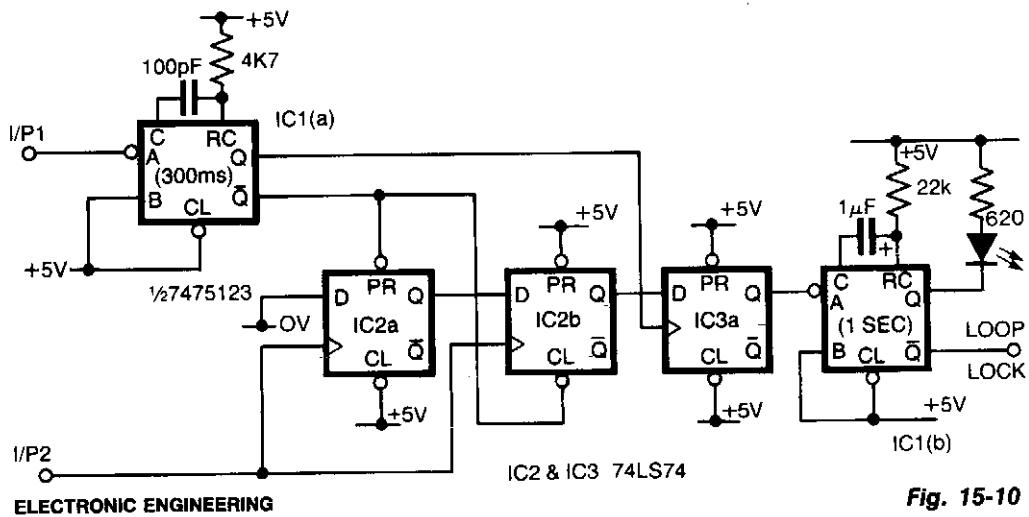


Fig. 15-10

### Circuit Notes

Input 1 is used as a gating period, during which a single rising edge on input 2 will cause a logic 1 output-any other number, indicating non-identical frequencies causes a logic 0 output.

IC1a converts input 1 to a narrow pulse which initializes IC2 which forms a two-stage shift register clocked by input 2. On the first edge of input 2 a logic 1 appears on the output of IC2b and for all subsequent inputs a logic 0 is present. At the end of the gating period this output is latched by IC3 forming the lock output. As this is only valid for one input period a monostable is added to the output to enable, for example, visual monitoring of the output. Either output from IC3 can be used depending on which state is most important. As connected the failure state is indicated.

## DEMONSTRATION COMPARATOR CIRCUIT


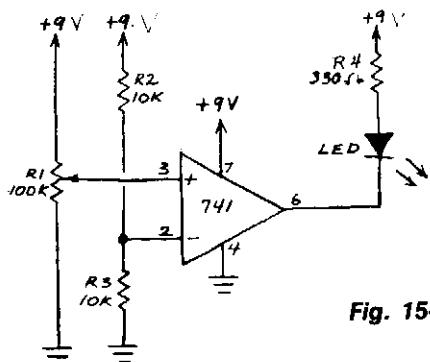


Fig. 15-11

### Circuit Notes

This circuit is an op amp without a feedback resistor. R2 and R3 junction point sets the reference voltage. When the input voltage set by R1 is below the reference voltage the LED glows. If voltage is above reference, the LED goes off.

## LED FREQUENCY COMPARATOR

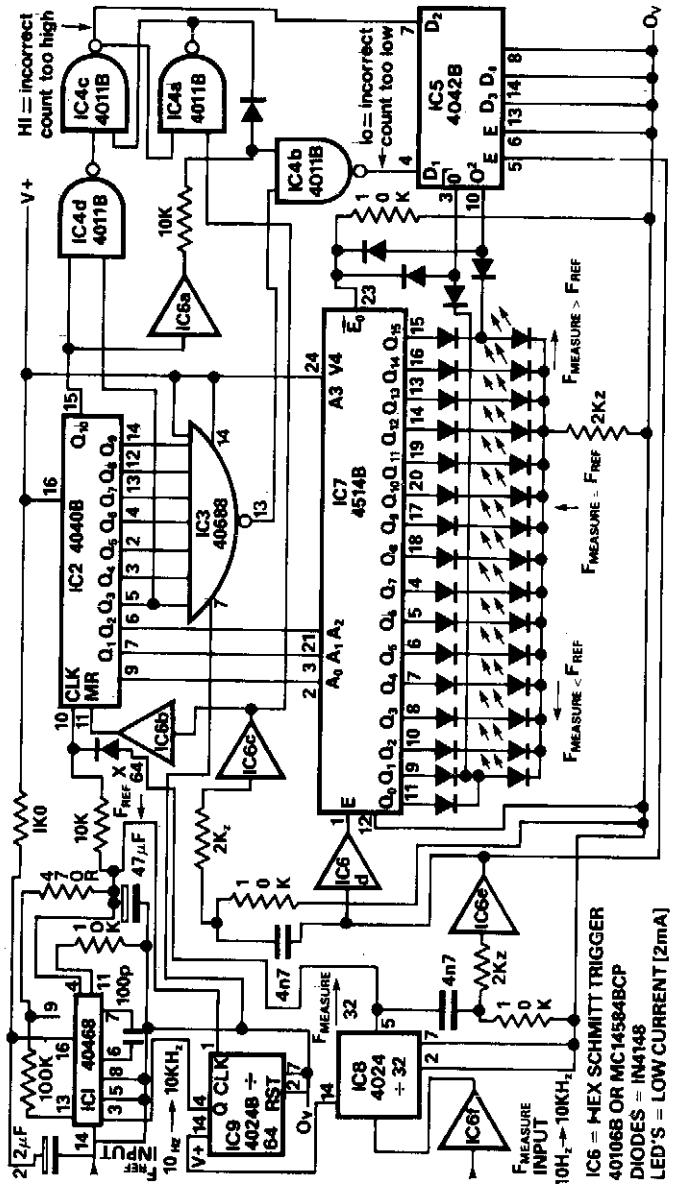

ELECTRONIC ENGINEERING


Fig. 15-12

### Circuit Notes

The circuit provides unambiguous LED + or - bar readout with steps of 0.1%. The reference frequency is multiplied by the PLL (IC1) and divider IC9 to output 64  $\times$   $F_{(ref)}$  and this is then gated by dividing  $F_{(measure)}$  by 32 in IC8 thus is  $F_{(ref)} = (measure)$  then IC2 counts 1024 pulses. Should the count be more than 1031 than the latch IC4c/IC4a is set to indicate count too high ( $F_{(measure)} > F_{(ref)}$ ) and if the count is less than 1017 then IC3/IC4b indicate count too low ( $F_{(measure)} < F_{(ref)}$ ). These signals are latched by IC5 at the end of each period by the latch signal from IC6e.

When the two frequencies are within + or - 0.6% the LSB's of the counter IC2 are decoded and latched by IC7 and displayed on LED's IC6c resets the counter after latching the data.

### TTL-COMPATIBLE SCHMITT TRIGGER

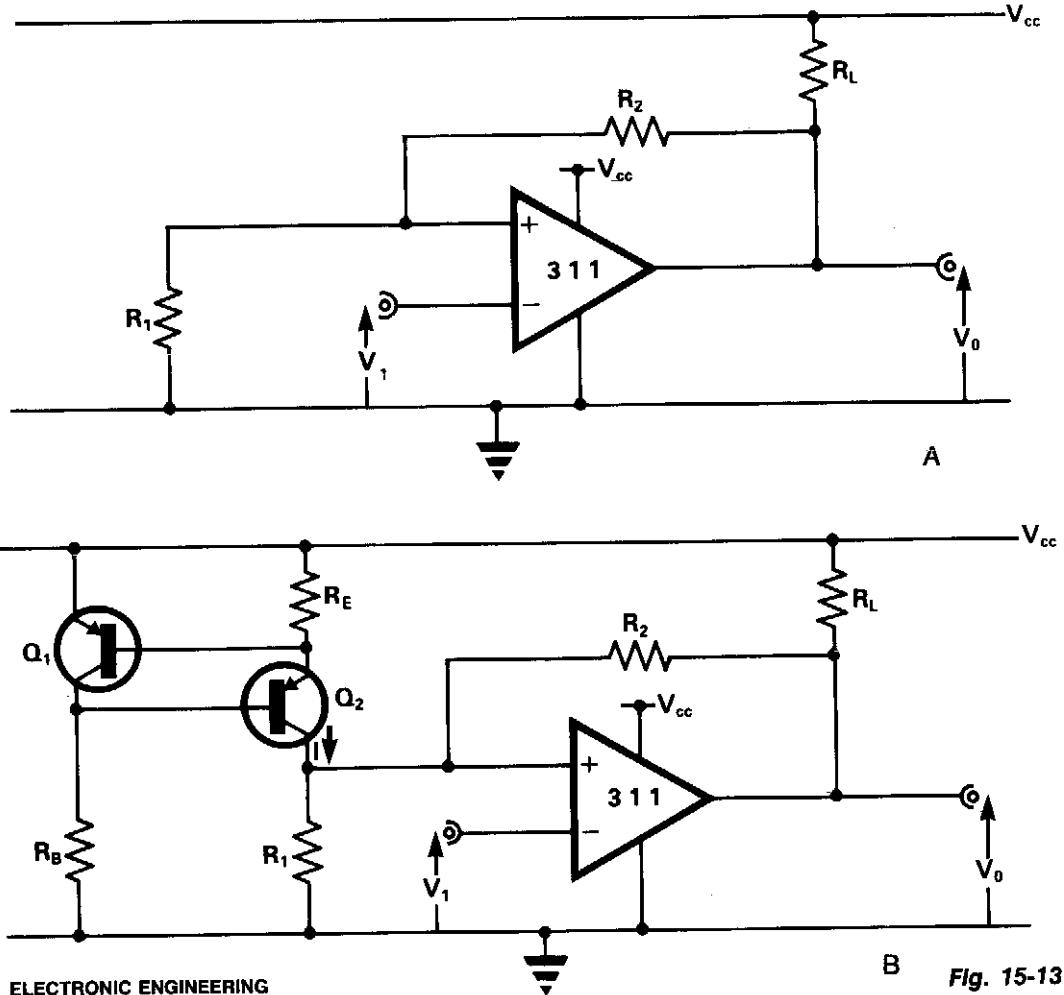

ELECTRONIC ENGINEERING

Fig. 15-13

#### Circuit Notes

The comparator has an output pull-up resistor  $R_L$  and is connected up to operate as a Schmitt trigger using the single rail supply  $V_{CC}$ . The feedback resistors  $R_1$  and  $R_2$  give upper and lower threshold levels  $V_{T+}$ ,  $V_{T-}$ , respectively.  $V_{T+}$  is easily set by suitable resistor selection but there is little independent choice of  $V_{T-}$  because  $V_{T-}$  cannot exceed  $V_{CE(SAT)}$ . In Fig. 15-13B current-source, comprising the transistors  $R_E$ ,  $R_B$  produces a current  $I \sim (V_{EB}/R_E)$ ,  $V_{EB} (\sim 0.65 \text{ V})$  being the emitter-base voltage of  $Q_1$  and  $Q_2$ . Fig. 15-13C shows the results of a practical test using the circuit of Fig. 15-13B, and the following operating and component data:

$$V_{CC} = 5 \text{ V}; R_L = 1 \text{ K ohm}; R_1 = R_2 = 10 \text{ K ohm};$$

$$R_B = 3.6 \text{ K ohm}; R_E = 1 \text{ K ohm} + 10 \text{ K ohm pot};$$

$$Q_1 = ZTX500; Q_2 = ZTX500.$$

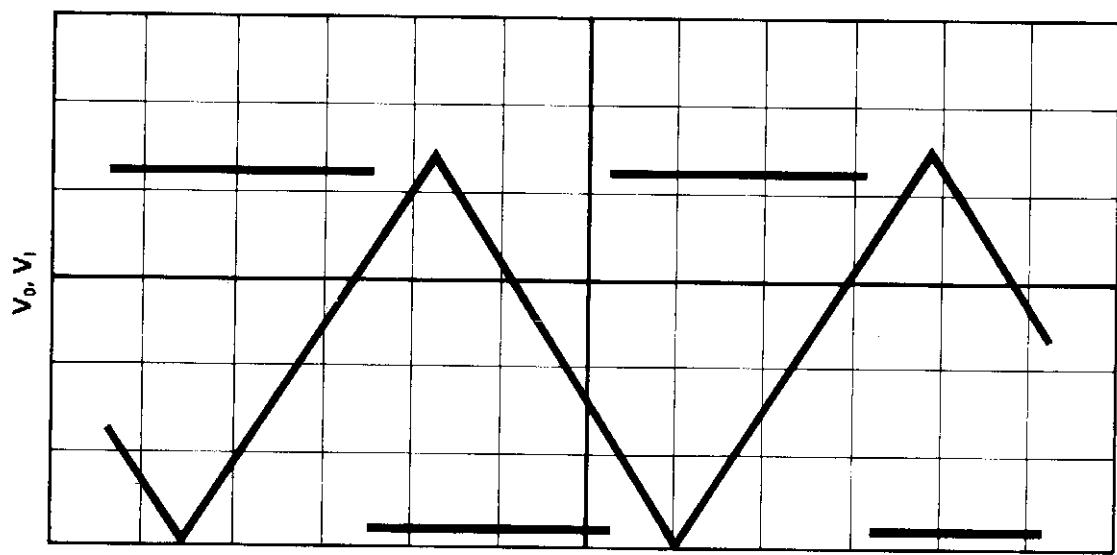


Fig. 15-13 Continued

# 16

## Computer Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- |   |                                    |
|---|------------------------------------|
| 8-Bit $\mu$ P Bus Interface                     | CMOS Data Acquisition System       |
| V <sub>PP</sub> Generator for Eproms            | High Speed Data Acquisition System |
| Eight Channel Mux/Demux System                  | Buffered Breakout Box              |
| Microprocessor Selected Pulse Width Control     | Z80 Clock                          |
| 8048/IM80C48 Microcomputer with 8-Character     | Data Separator for Floppy Disks    |
| 16-Segment ASCII Triplex Liquid Crystal Display |                                    |

## 8-BIT $\mu$ P BUS INTERFACE


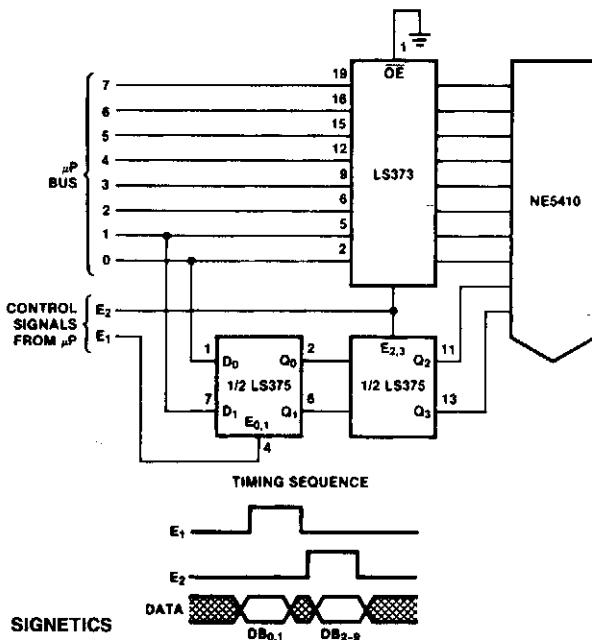


Fig. 16-1

### Circuit Notes

With this double latch technique, valid data will be latched to the DAC until updated with the  $E_2$  pulse. Timing will depend on the processor used.

## $V_{PP}$ GENERATOR FOR EPROMS

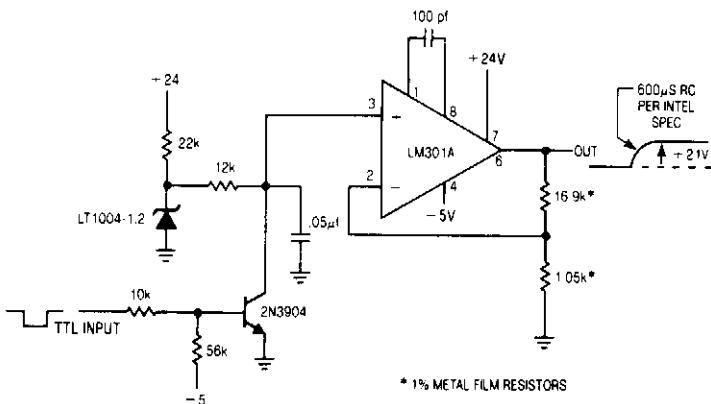


\* 1% METAL FILM RESISTORS

LINEAR TECHNOLOGY CORP.

Fig. 16-2

## EIGHT-CHANNEL MUX/DEMUX SYSTEM

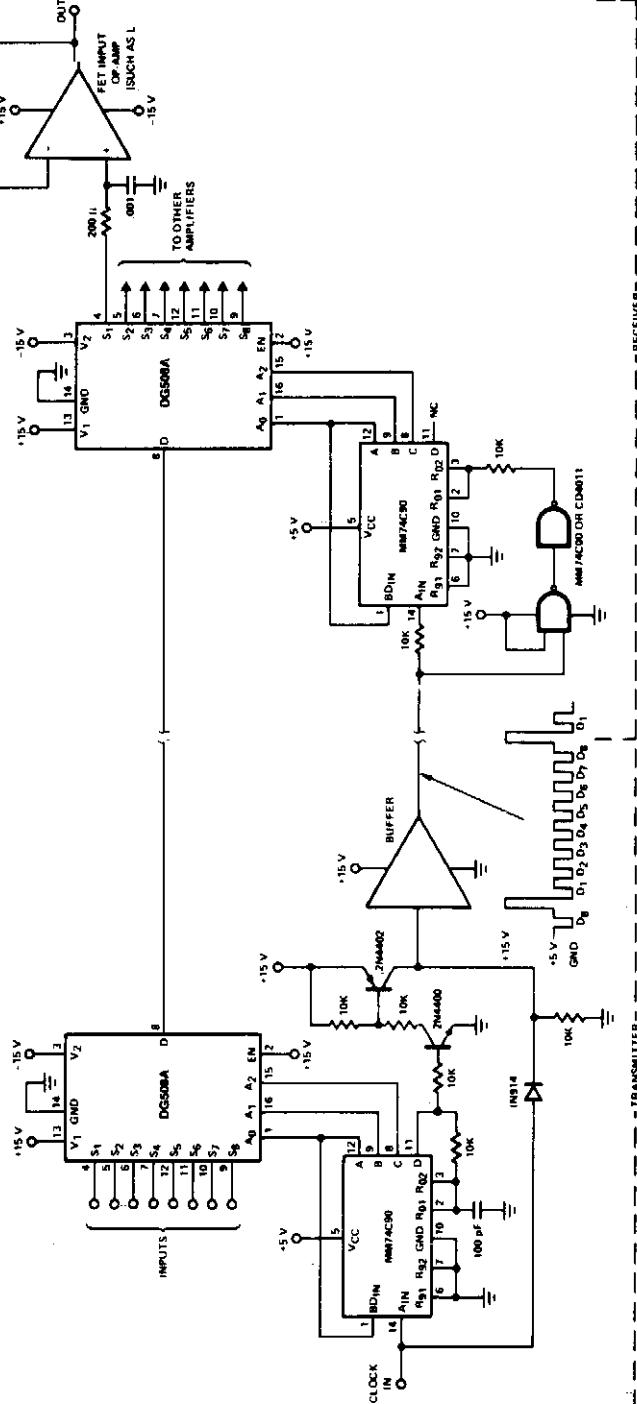


SILICONIX

**Fig. 16-3**

### Circuit Notes

A number of signals may be sent between two points simultaneously by making a slight modification in the receiver circuit. A second DG508A is used as a demultiplexer, allowing all 8 channels to be monitored continuously.
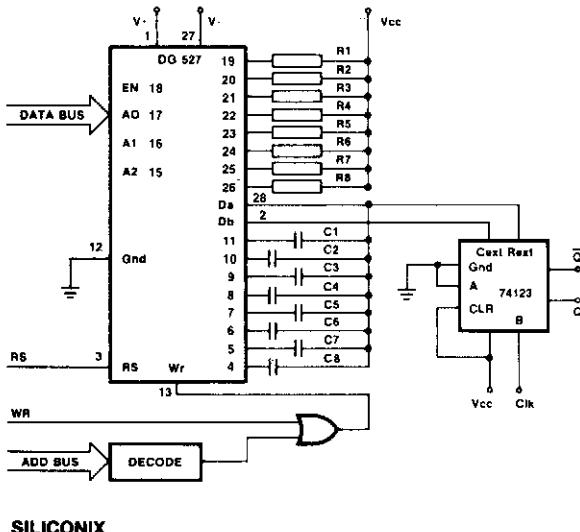
## MICROPROCESSOR SELECTED PULSE WIDTH CONTROL



SILICONIX

Fig. 16-4

### Circuit Notes

Differential multiplexers are generally used in process control applications to eliminate errors due to common mode signals. In this circuit however, advantage is taken of the dual multiplexing capability of the switch. This is achieved by using the multiplexer to select pairs of RC networks to control the pulse width of the multivibrator. This can be a particularly useful feature in process control applications where there is a requirement for a variable width sample "window" for different control signals.

## 8048/IM80C48 MICROCOMPUTER WITH 8-CHARACTER 16-SEGMENT ASCII TRIPLEX LIQUID CRYSTAL DISPLAY


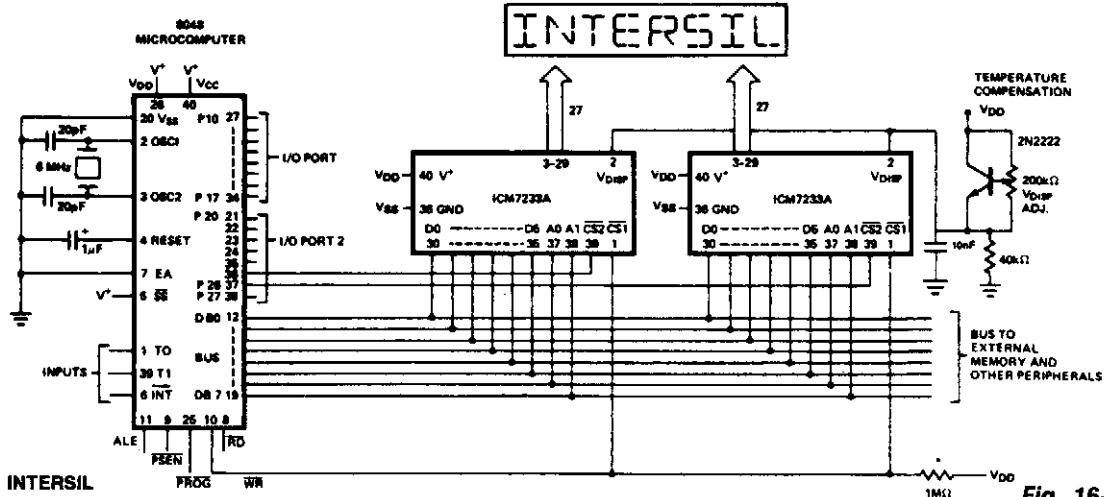
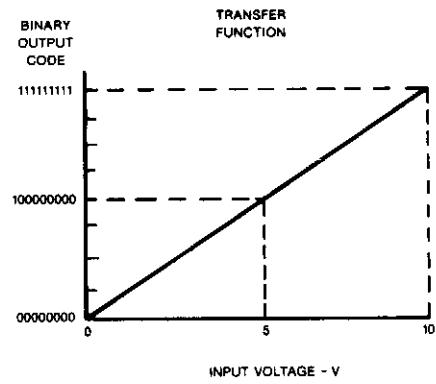


Fig. 16-5

### Circuit Notes

The two bit character address is merged with the data and written to the display driver under the control of the WR line. Port lines are used to either select the target driver, or deselect all of them for other bus operations.

## CMOS DATA ACQUISITION SYSTEM

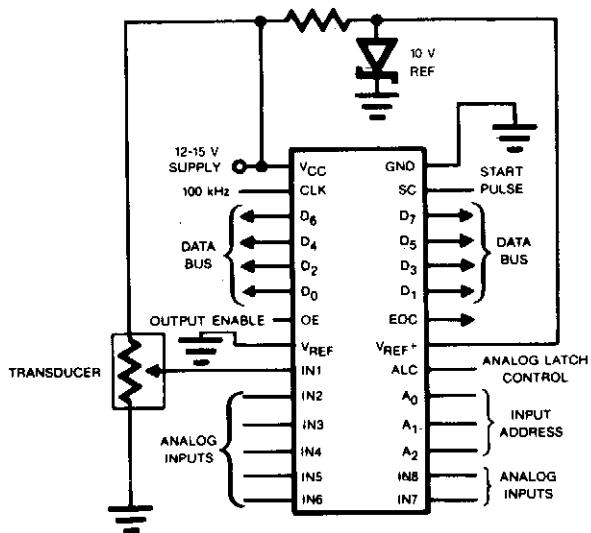

$V_{CC} = 15 \text{ V}$   
 $V_{REF} = 10 \text{ V}$   
 $GND = V_{REF^-} = 0 \text{ V}$   
RESOLUTION = 39 mV  
 $R_{SOURCE} \leq 1 \text{ k}\Omega$

**Fig. 16-6**

SILICONIX

### Circuit Notes

Charge redistribution to achieve A/D conversion. In typical applications, as a ratio metric conversion system for a microprocessor,  $V_{REF^-}$  will be connected to ground and  $V_{REF^+}$  will be connected to  $V_{CC}$ . The output will then be a simple proportional ratio between analog input voltage and  $V_{CC}$ . The general relationship is:

$$\frac{D_{OUT}}{2^8} = \frac{V_{IN}}{V_{REF^+} - V_{REF^-}}$$

Where  $D_{OUT}$  = Digital Output  
 $V_{IN}$  = Analog Input  
 $V_{REF^+}$  = Positive Reference Potential  
 $V_{REF^-}$  = Negative Reference Potential

## HIGH SPEED DATA ACQUISITION SYSTEM


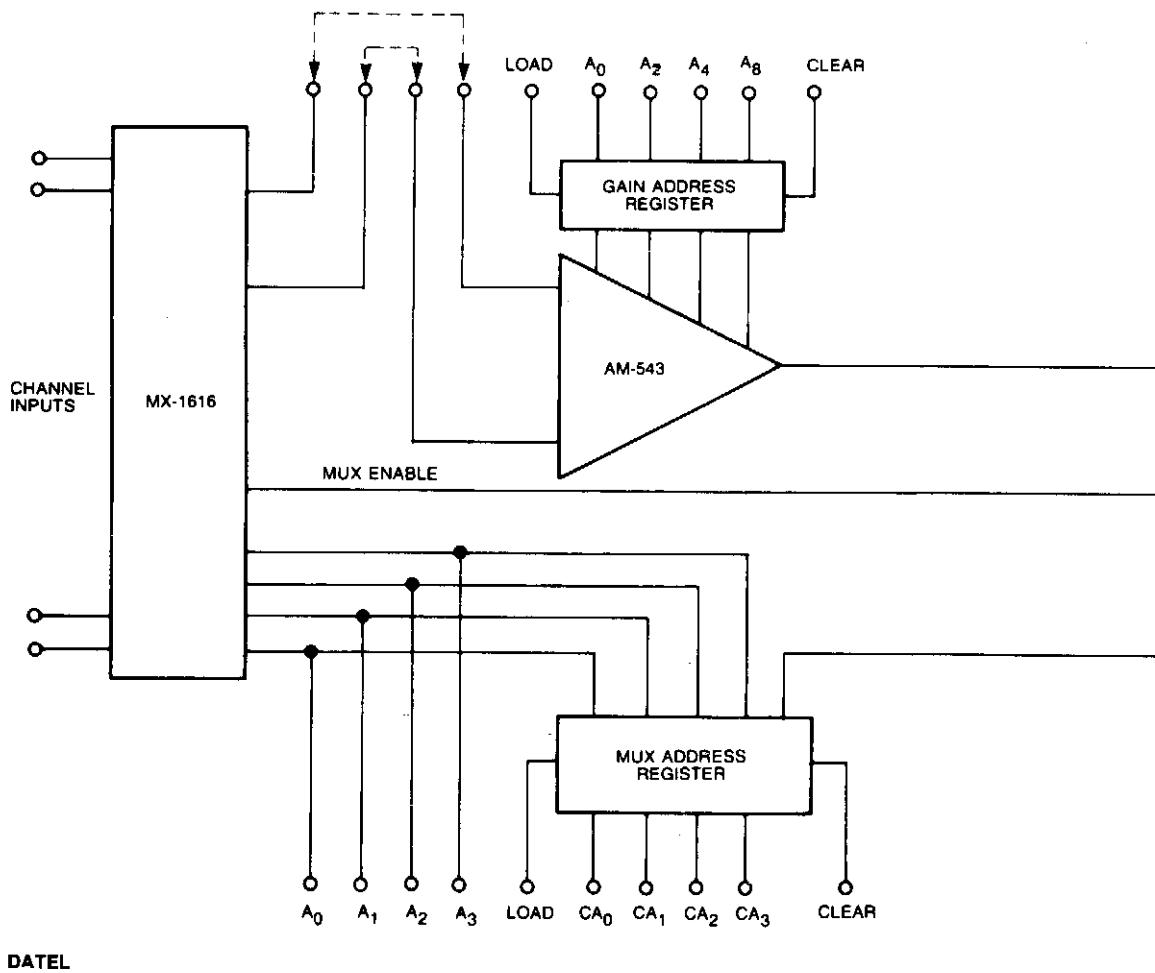


Fig. 16-7
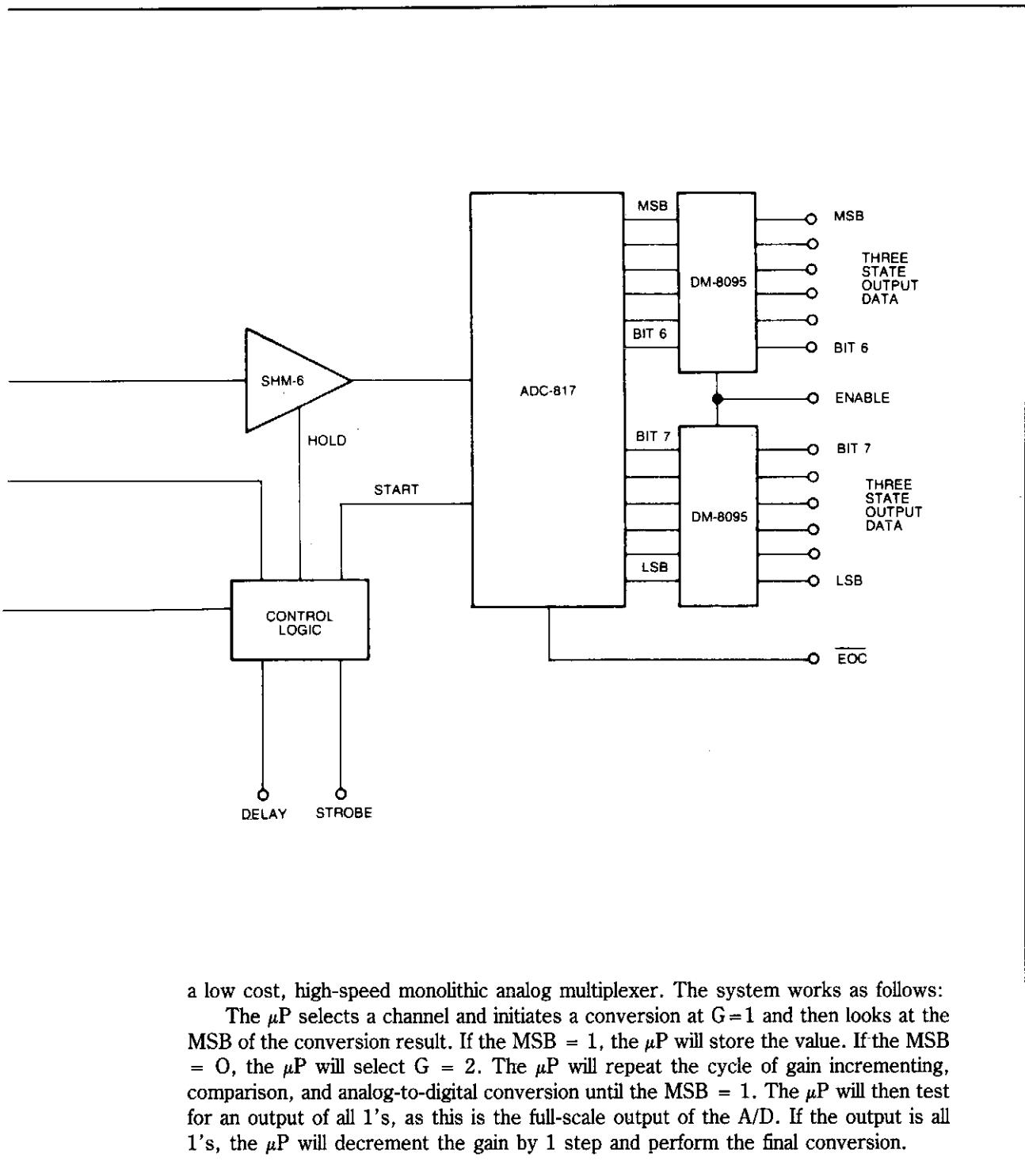
### Circuit Notes

This diagram shows a high-speed data acquisition system with 8 differential inputs and 12-bit resolution using the AM-543. If the control logic is timed so that the Sample-Hold-ADC section is converting one analog value while the mux-amplifier section is allowed to settle to the next input value, throughout rates greater than 156 KHz can be achieved. The AM-543 is used with Datel's ADV-817, a 12-bit hybrid A/D with a 2  $\mu$ sec conversion rate, the SHM-6, a 0.01%, 1  $\mu$ sec hybrid Sample-Hold, and the MX-1616,



a low cost, high-speed monolithic analog multiplexer. The system works as follows:

The  $\mu$ P selects a channel and initiates a conversion at  $G=1$  and then looks at the MSB of the conversion result. If the MSB = 1, the  $\mu$ P will store the value. If the MSB = 0, the  $\mu$ P will select  $G = 2$ . The  $\mu$ P will repeat the cycle of gain incrementing, comparison, and analog-to-digital conversion until the MSB = 1. The  $\mu$ P will then test for an output of all 1's, as this is the full-scale output of the A/D. If the output is all 1's, the  $\mu$ P will decrement the gain by 1 step and perform the final conversion.

## BUFFERED BREAKOUT BOX

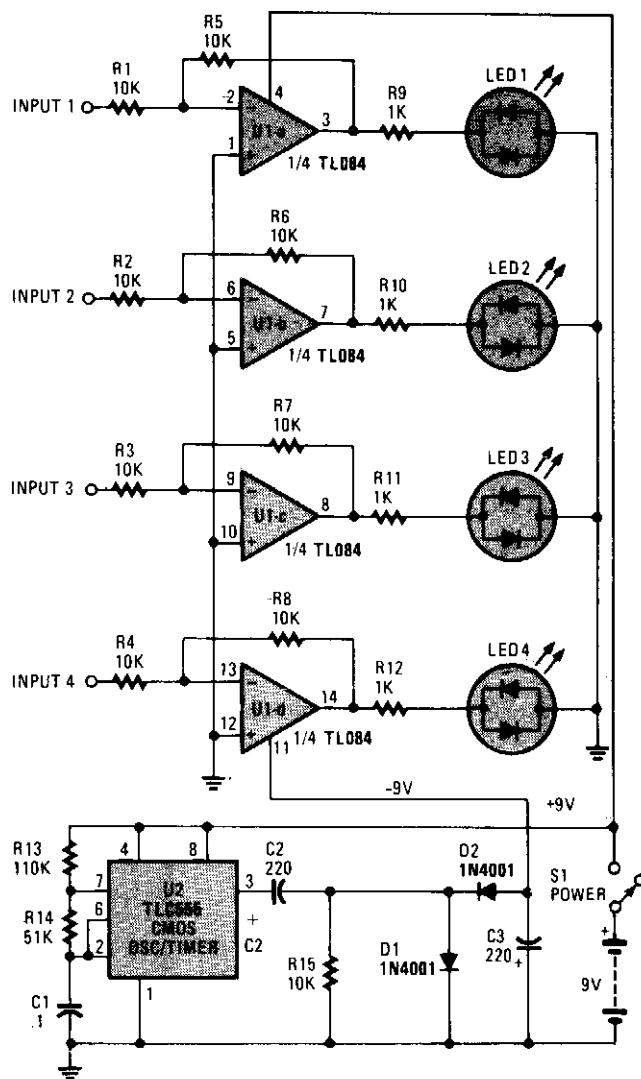


Fig. 16-8

HANDS-ON ELECTRONICS

### Circuit Notes

The monitoring circuit consists of four tri-color LEDs driven by an equal number of op amps configured as gain-of-one inverting amplifiers. Each LED is wired in the circuit so that it glows red when the input to the op amp is high, and green when the input is low. The LED remains off when the input is disconnected from a circuit, when it's at ground potential, and when it's connected to a 3-state output that's in the high-impedance state. Each input has an impedance of 10,000 ohms preventing the circuit

## BUFFERED BREAKOUT BOX, Continued.

from loading communication lines. The op amp requires both positive and negative supply voltages to properly drive the LEDs. Both voltages are supplied by a single, nine-volt battery. The battery supplies the positive source directly. The negative source is supplied via a CMOS 555 oscillator/timer that's configured as an astable oscillator, which is used to drive a standard diode/capacitor voltage doubler. When the 555 is connected to the monitoring circuit, the output voltage is not 18 volts ( $2 \times 9$ ), but a little under nine volts, due to loading. The circuit draws about 16 mA with all LEDs off; with all four on, it draws between 20 and 30 mA, depending on how many LEDs are high, and how many are low. The use of CMOS op amps reduces quiescent current drain considerably.

### Z80 CLOCK

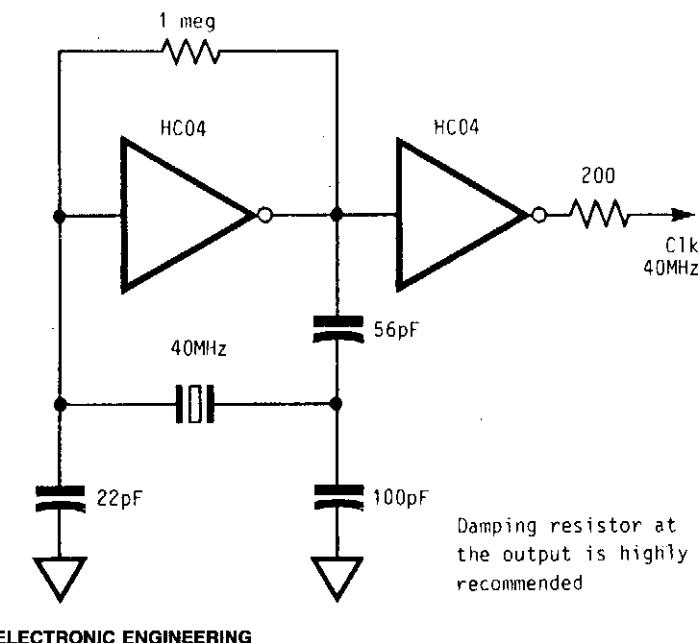



Fig. 16-9

ELECTRONIC ENGINEERING

### Circuit Notes

The circuit will operate reliably from below 1 MHz to above 400 MHz. With  $V_{CC} = 5$  V the output of the second inverter essentially attains a full swing from 0 V to 5 V. Such large logic output levels and broad frequency range capabilities make this oscillator quite suitable for driving MOS components such as CPU, controller chip, peripheral devices, as well as other TTL products. A damping resistor in series between the clock output of the oscillator and the input of the device being driven will remove the undesirable undershoot and ringing caused by the high speed CMOS part.

## DATA SEPARATOR FOR FLOPPY DISKS

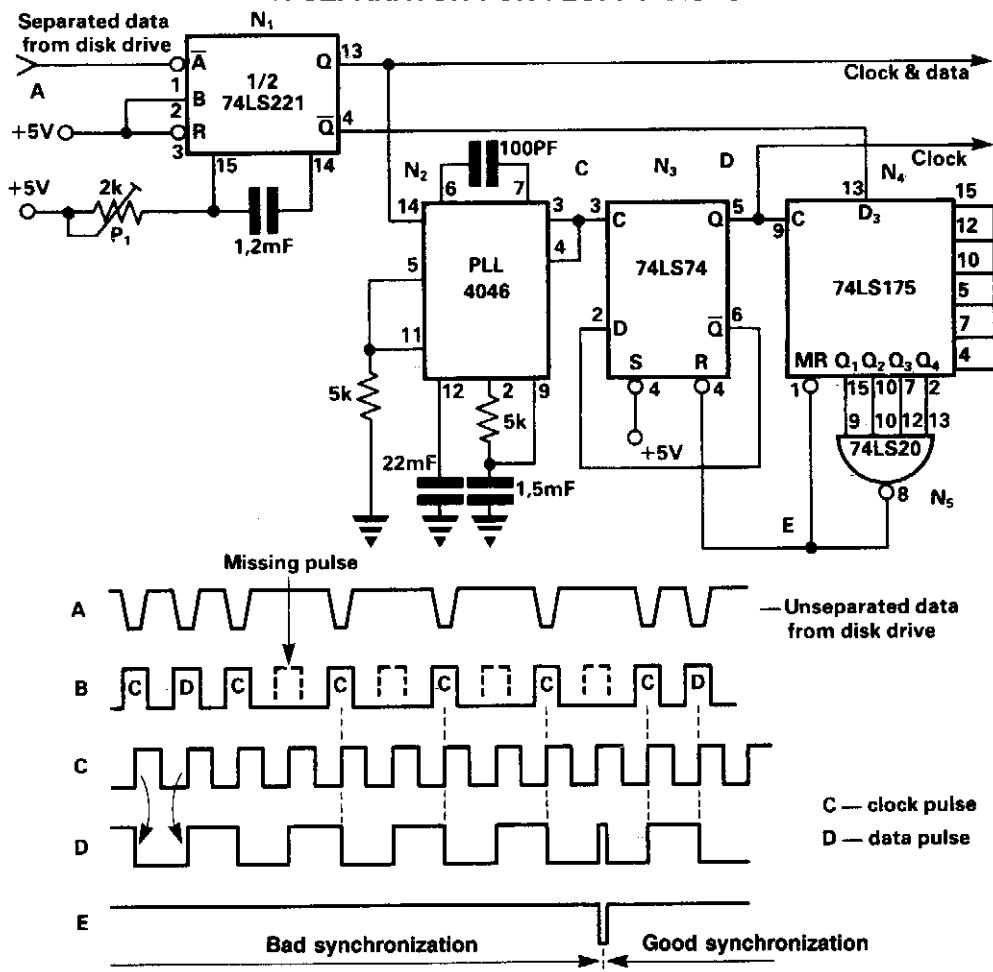

ELECTRONIC ENGINEERING

Fig. 16-10

### Circuit Notes

The data separator is intended for use with 8" flexible diskettes with IBM 3870 soft sectored format. The circuit delivers data and clock (B) and clock pulses (D). These two signals must be in such a sequence that the negative edge of the clock pulse is at the middle of a data cell.

Unseparated data (A) from the floppy unit is shaped with one shot N<sub>1</sub>. Trimmer P<sub>1</sub> should be adjusted so that pulses (B) are 1  $\mu$ s wide. This signal synchronizes PLL N<sub>2</sub> with a free running frequency adjusted to 500 kHz. The output of the PLL is 90° out of phase with its input. D-type flip-flop N<sub>3</sub> is connected as a divider by two and changes state at each positive edge of (C). N<sub>4</sub>, connected as a shift register, looks for four consecutive missing pulses. When this happens, the circuit is resynchronized with (E) so that the negative edge of (D) is in the middle of a data cell.

# 17

## Converters

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Voltage-to-Pulse Duration Converter

Voltage-to-Current Converters

TTL-to-MOS Logic Converter

TTL Square Wave-to-Triangle Converter

A Regulated DC-to-DC Converter

Capacitance to Pulse Width Converter

Current-to-Voltage Converter with Grounded Bias  
and Sensor

Triangle-to-Sine Converters

Precision Peak-to-Peak AC-DC Converter

Photodiode Current-to-Voltage Converter

Self Oscillating Flyback Converter



RMS-to-DC Converter

100 MHz Converter

Precision Voltage-to-Frequency Converter

Bipolar DC-DC Converter Requires No Inductor

## VOLTAGE-TO-PULSE DURATION CONVERTER

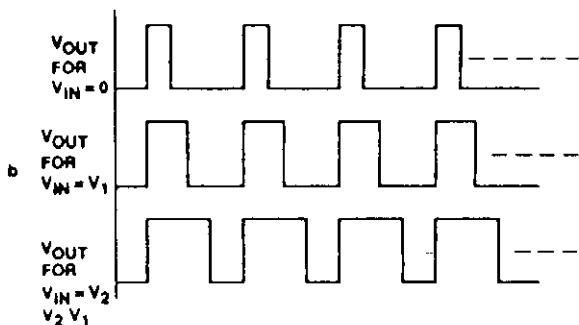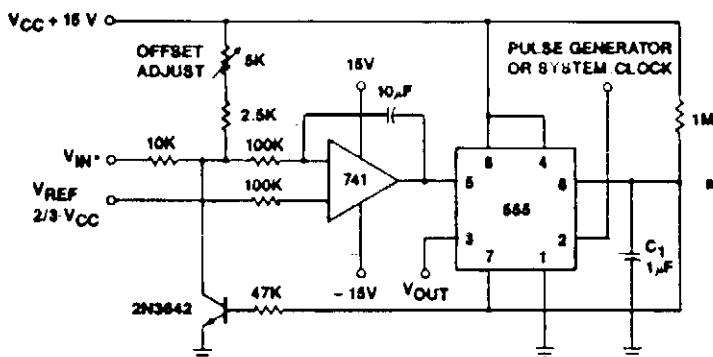

### NOTES:

All resistor values in ohms

\* $V_{IN}$  is limited to 2 diode drops within ground or below  $V_{CC}$


SIGNETICS

Fig. 17-1.

## Circuit Notes

Voltage levels can be converted to pulse durations by combining an op amp and a timer IC. Accuracies to better than 1% can be obtained with this circuit (a), and the output signals (b) still retain the original frequency, independent of the input voltage.

## VOLTAGE-TO-CURRENT CONVERTERS

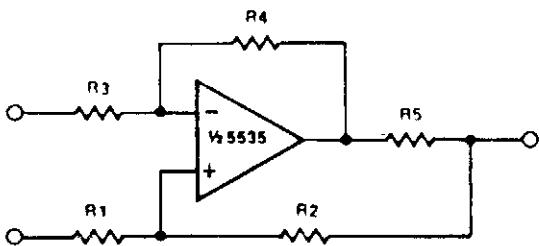

### NOTES:

$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$I_{OUT} = \frac{-V_{IN} \cdot R_2}{R_5 \cdot R_1}$$

SIGNETICS

## Circuit Notes

A simple voltage-to-current converter is shown in the figure. The current out is  $I_{OUT}$  or  $V_{IN}/R$ . For negative currents, a pnp can be used and, for better accuracy, a Darlington pair can be substituted for the transistor. With careful design, this circuit can be used to control currents of many amps. Unity gain compensation is necessary.

Fig. 17-2

### TTL-TO-MOS LOGIC CONVERTER

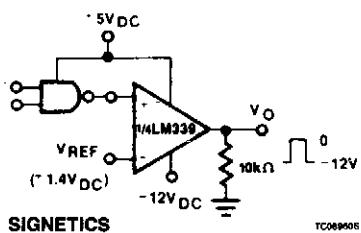


Fig. 17-3

### TTL SQUARE WAVE-TO-TRIANGLE CONVERTER

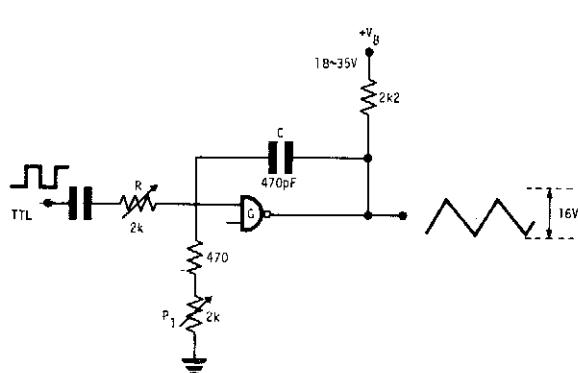


Fig. 17-4

#### Circuit Notes

This fixed frequency triangular waveform generator driven by a TTL square wave generates typically 16-V p-p triangles at frequencies up to several MHz. It uses only one NAND open collector gate, or one open collector inverter as a fast integrator with gain. Careful successive adjustments of R and P<sub>1</sub> are needed. When correct adjustments are reached, output amplitude and linearity are largely independent of the value of V<sub>B</sub>, from a minimum of 18 V up to 35 V. The value of C shown is for 100 kHz; at higher frequencies, it must be reduced in proportion.

### A REGULATED DC-TO-DC CONVERTER

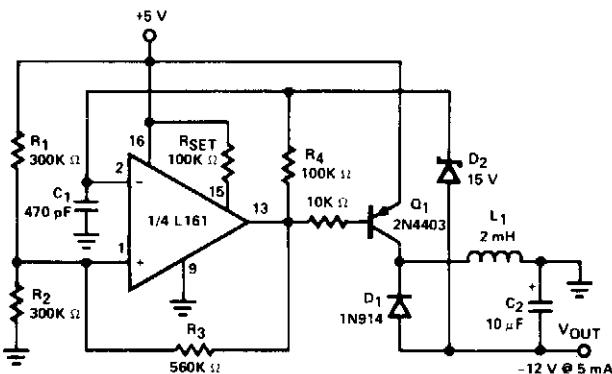


Fig. 17-5

## CAPACITANCE TO PULSE WIDTH CONVERTER

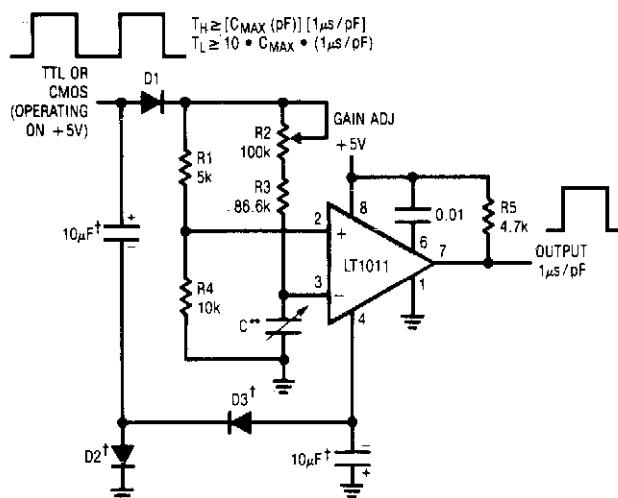


Fig. 17-6

$$*PW = (R_2 + R_3) \left( \frac{C}{R_1} \right), \text{ INPUT CAPACITANCE OF}$$


LT1011 IS  $\approx 6\text{pF}$ . THIS IS AN OFFSET TERM.

<sup>t</sup>THESE COMPONENTS MAY BE ELIMINATED IF NEGATIVE SUPPLY IS AVAILABLE (-1V TO -15V).

\*\*TYPICAL 2 SECTIONS OF 355pF VARIABLE CAPACITOR WHEN USED AS SHAFT ANGLE INDICATION.

LINEAR TECHNOLOGY CORP.

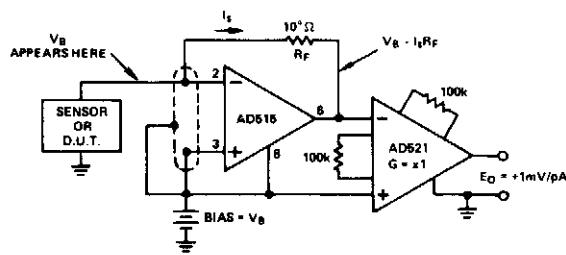
## CURRENT-TO-VOLTAGE CONVERTER WITH GROUNDED BIAS AND SENSOR



ANALOG DEVICES, INC.

Fig. 17-7

## TRIANGLE-TO-SINE CONVERTERS

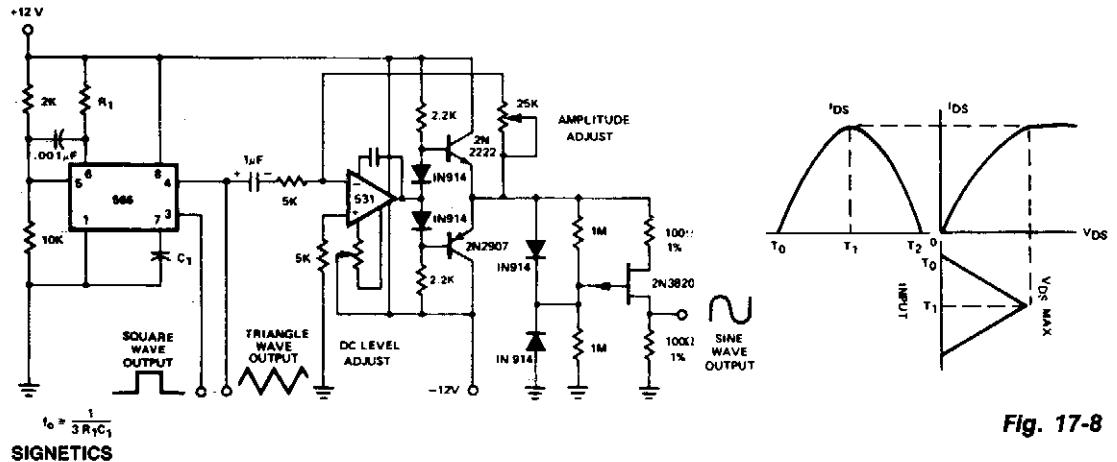


**Fig. 17-8**

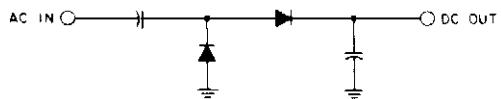
**Circuit Notes**

Conversion of triangle wave shapes to sinusoids is usually accomplished by diode-resistor shaping networks, which accurately reconstruct the sine wave segment by segment. Two simpler and less costly methods may be used to shape the triangle waveform of the 566 into a sinusoid with less than 2% distortion. The non-linear  $I_{DS}V_{DS}$  transfer characteristic of a P-channel junction FET is used to shape the triangle waveform. The amplitude of the triangle waveform is critical and must be carefully adjusted to achieve a low distortion sinusoidal output. Naturally, where additional waveform accuracy is needed, the diode-resistor shaping scheme can be applied to the 566 with excellent results since it has very good output amplitude stability when operated from a regulated supply.

## **PRECISION PEAK-TO-PEAK AC-DC CONVERTER**



## CONVENTIONAL VOLTAGE DOUBLER

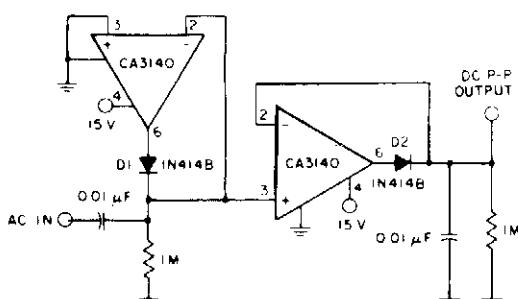

GENERAL ELECTRIC/BCA


## **Circuit Notes**

Using a CA3140 BiMOS op amp and a single positive supply converts a conventional voltage doubler with two precision diodes into a precision peak-to-peak ac-to-dc voltage converter having wide dynamic range and wide bandwidth.

ALL RESISTANCE VALUES ARE IN OHMS

"Reprinted with permission from Electronic Design, Vol. 25, No. 24,  
copyright Hayden Publishing Co., Inc. 1977."

## PHOTODIODE CURRENT-TO-VOLTAGE CONVERTER

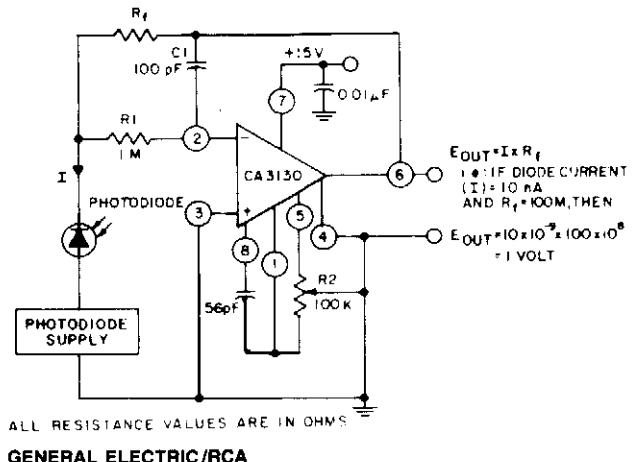


**Fig. 17-10**
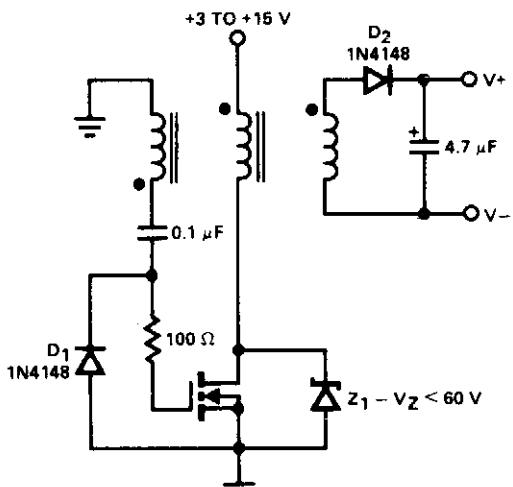
### Circuit Notes

The circuit uses three CA3130 BiMOS op amps in an application sensitive to sub-picoampere input currents. The circuit provides a ground-referenced output voltage proportional to input current flowing through the photodiode.

## SELF OSCILLATING FLYBACK CONVERTER




### Circuit Notes

Low-power converter uses the core characteristics to determine frequency. With the transformer shown, operating frequency is 250 kHz. Diode D1 prevents negative spikes from occurring at the MOSFET gate, the 100 ohm resistor is a parasitic suppressor, and Z1 serves as a dissipative voltage regulator for the output and also clips the drain voltage to a level below the rated power FET breakdown voltage.

SILICONIX, INC.

**Fig. 17-11**

## RMS-TO-DC CONVERTER

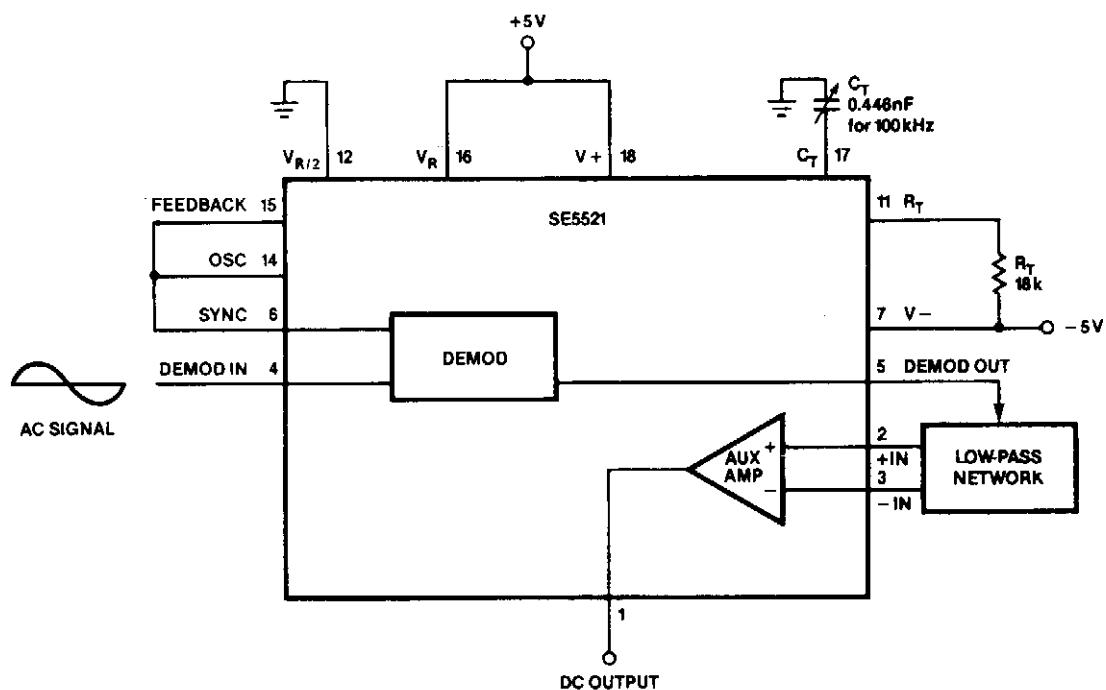

**NOTE:**

1. The DC output at Pin 1 varies linearly with the RMS input at Pin 4.
2. C<sub>T</sub> is tweaked until the sync signal is in phase with the AC signal.


**SIGNETICS**

**Fig. 17-12**

### Circuit Notes

An ac voltmeter may be easily constructed. Simplicity of the circuit and low component count make it particularly attractive. The demodulator output is a full-wave rectified signal from the ac input at Pin 4. The dc component on the rectified signal at Pin 5 varies linearity with the rms input at Pin 4 and thus provides an accurate rms-to-dc conversion at the output of the filter (Pin 1). C<sub>T</sub> is a variable capacitor that is tweaked until the oscillator signal to the sync input of the demodulator is in phase with the ac signal at Pin 4.

## 100 MHz CONVERTER

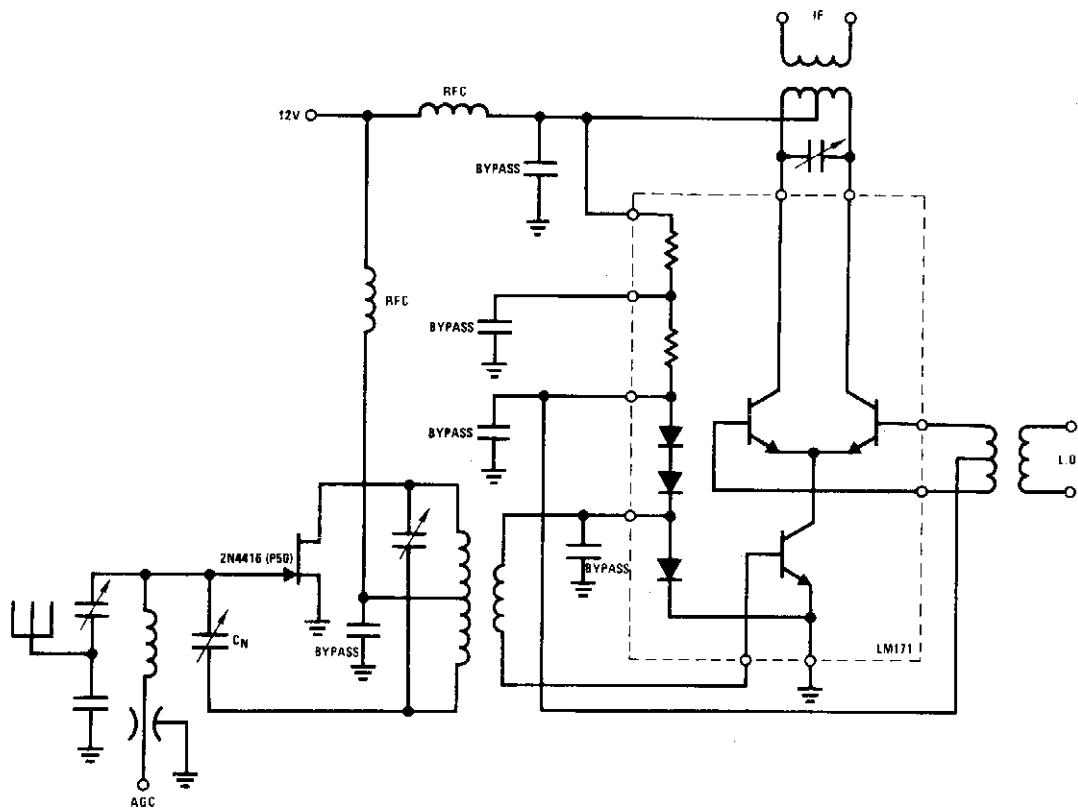


NATIONAL SEMICONDUCTOR CORP.

**Fig. 17-13**

### Circuit Notes

The 2N4416 JFET will provide noise figures of less than 3 dB and power gain of greater than 20 dB. The JFET's outstanding low crossmodulation and low intermodulation distortion provides an ideal characteristic for an input stage. The output feeds into an LM171 used as a balanced mixer. This configuration greatly reduces local oscillator radiation both into the antenna and into the *if* strip and also reduces *rf* signal feedthrough.
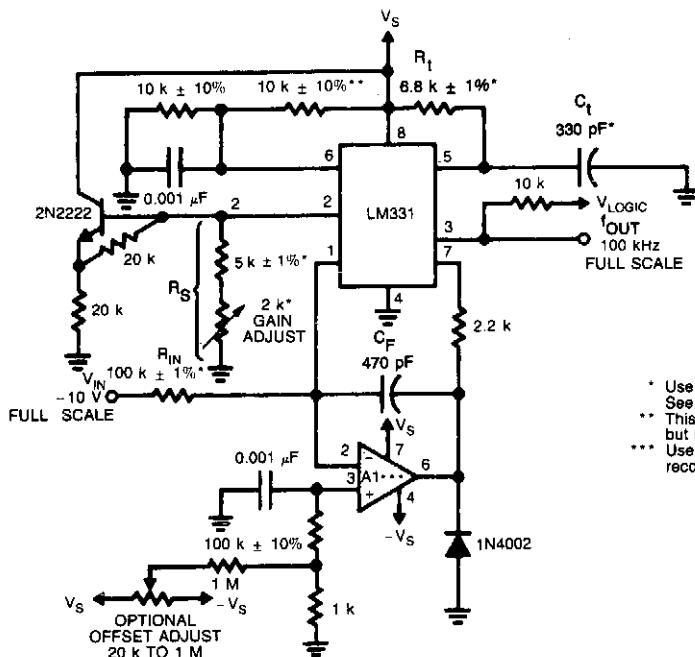
## PRECISION VOLTAGE-TO-FREQUENCY CONVERTER



\* Use stable components with low temperature coefficients.  
See Typical Applications section.

\*\* This resistor can be 5 kΩ or 10 kΩ for V<sub>S</sub> = 8 V to 22 V,  
but must be 10 kΩ = 4.5 V to 8 V.

\*\*\* Use low offset voltage and low offset current op amps for A1:  
recommended types LF411A or LF356.

NATIONAL SEMICONDUCTOR CORP.

**Fig. 17-14**

### Circuit Notes

In this circuit, integration is performed by using a conventional operational amplifier and feedback capacitor, C<sub>F</sub>. When the integrator's output crosses the nominal threshold level at pin 6 of the LM131, the timing cycle is initiated. The average current fed into the op amp's summing point (pin 2) is  $i \times (1.1 R_t C_t) \times f$  which is perfectly balanced with  $-V_{IN}/R_{IN}$ . In this circuit, the voltage offset of the LM131 input comparator does not affect the offset or accuracy of the V-to-F converter as it does in the stand-alone V-to-F converter, nor does the LM131 bias current or offset current. Instead, the offset voltage and offset current of the operational amplifier are the only limits on how small the signal can be accurately converted.

## BIPOLAR DC-DC CONVERTER REQUIRES NO INDUCTOR

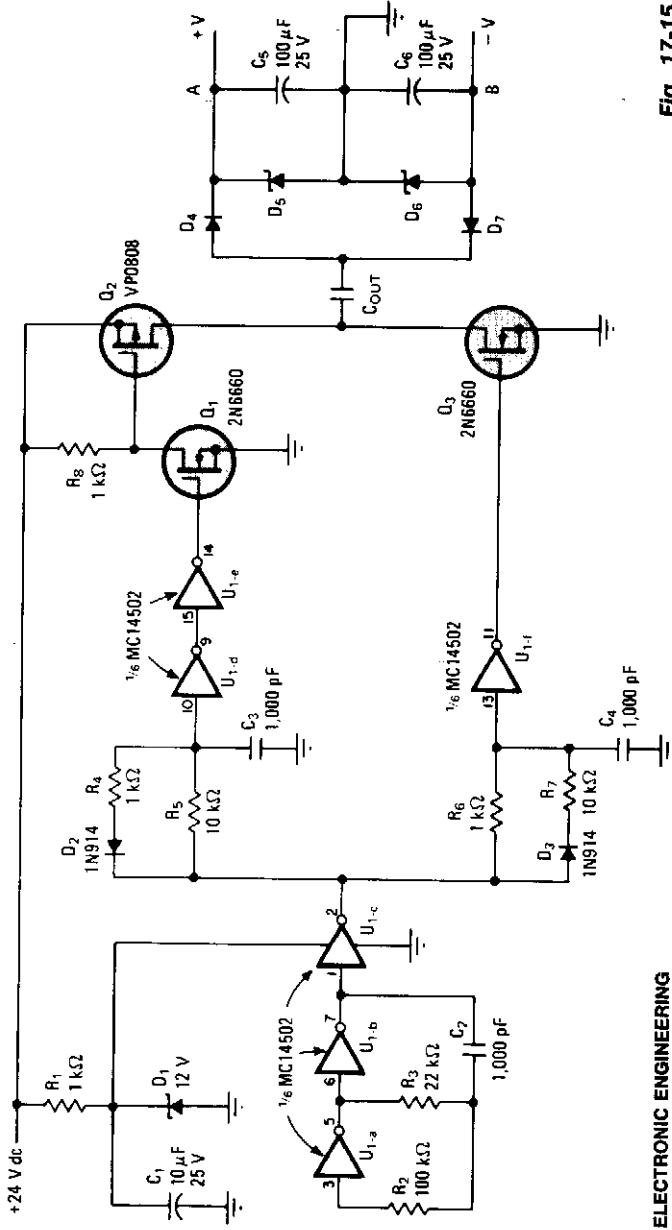


Fig. 17-15

Circuit Notes

Inverters U1a and U1b form a 20-kilohertz oscillator whose square wave output—further shaped by D2, R4, and R5 and by D3, R6, and R7—drives power field-effect transistors Q2 and Q3. The p-channel and n-channel FETs conduct alternately, in a push-pull configuration. When Q2 conducts, the positive charge on  $C_{out}$  forces diode D4 to conduct as well, which produces a positive voltage, determined by zener diode D5, at terminal A. Similarly, when Q3, in its turn conducts, the negative charge on  $C_{out}$  forces D7 to do so as well. A negative voltage, therefore, develops at terminal B, whose level is set by D6.

# **18**

## **Counters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- 8-Digit Up/Down Counter
- Ring Counter with Variable Timing
- 20 kHz Ring Counter
- Binary Counter
- 100 MHz Frequency, Period Counter
- Analog Counter Circuit
- Attendance Counter
- 10 MHz Universal Counter

## 8-DIGIT UP/DOWN COUNTER

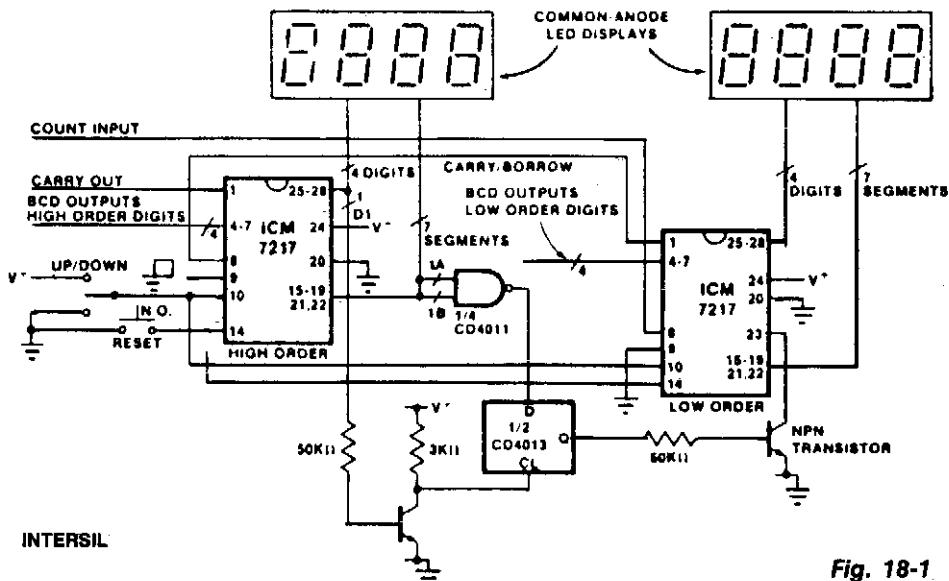


*Fig. 18-1*
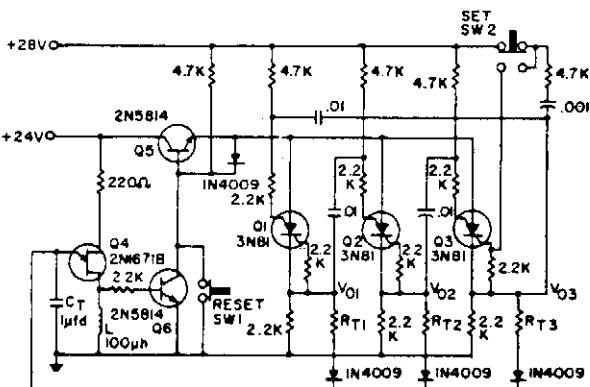
### Circuit Notes

This circuit shows how to cascade counters and retain correct leading zero blanking. The NAND gate detects whether a digit is active since one of the two segments a or b is active on any unblanked number. The flip flop is clocked by the least significant digit of the high order counter, and if this digit is not blanked, the Q output of the flip flop goes high and turns on the npn transistor, thereby inhibiting leading zero blanking on the low order counter.

## RING COUNTER WITH VARIABLE TIMING




### Circuit Notes

Shift pulses are generated by the unijunction transistors. The intervals between pulses are controlled by C<sub>T</sub> and R<sub>T</sub>. A different R<sub>T</sub> can be selected for each stage of the counter as shown.

*Fig. 18-2*


## 20 kHz RING COUNTER

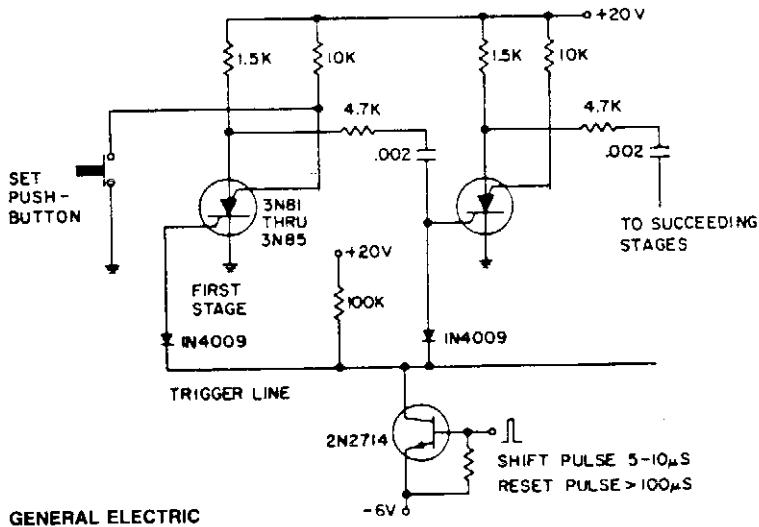

### Circuit Notes

The shift pulse turns off the conducting scs by reverse biasing the cathode gate. The charge stored on the coupling capacitor then triggers the next stage. An excessively long shift pulse charges up all the capacitors, turning off all stages. Grounding an anode gate will "set" that stage.


## BINARY COUNTER

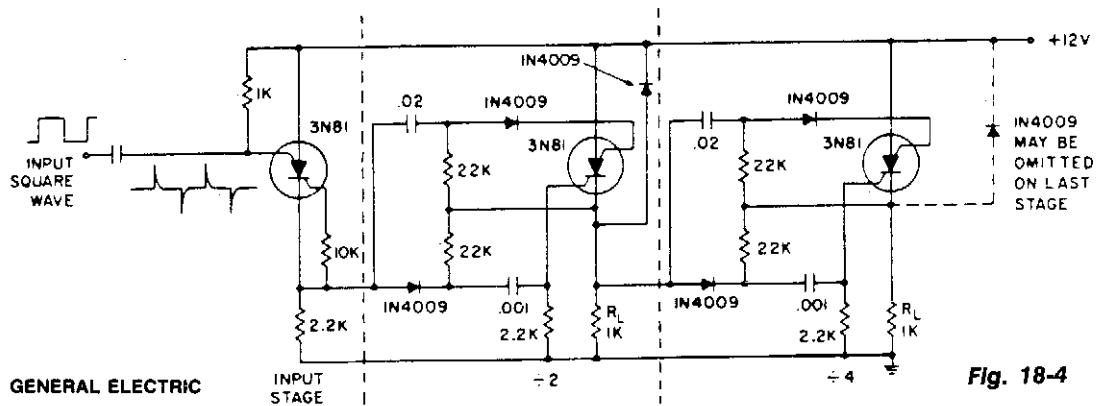

### Circuit Notes

Stages are triggered by the positive going edge. The scs is turned on at the cathode gate; turned off at the anode gate. The anode-to-cathode IN4009 suppresses positive transients while the scs is recovering. The input stage generates fast positive edges to trigger the counter.

## 100 MHz FREQUENCY, PERIOD COUNTER

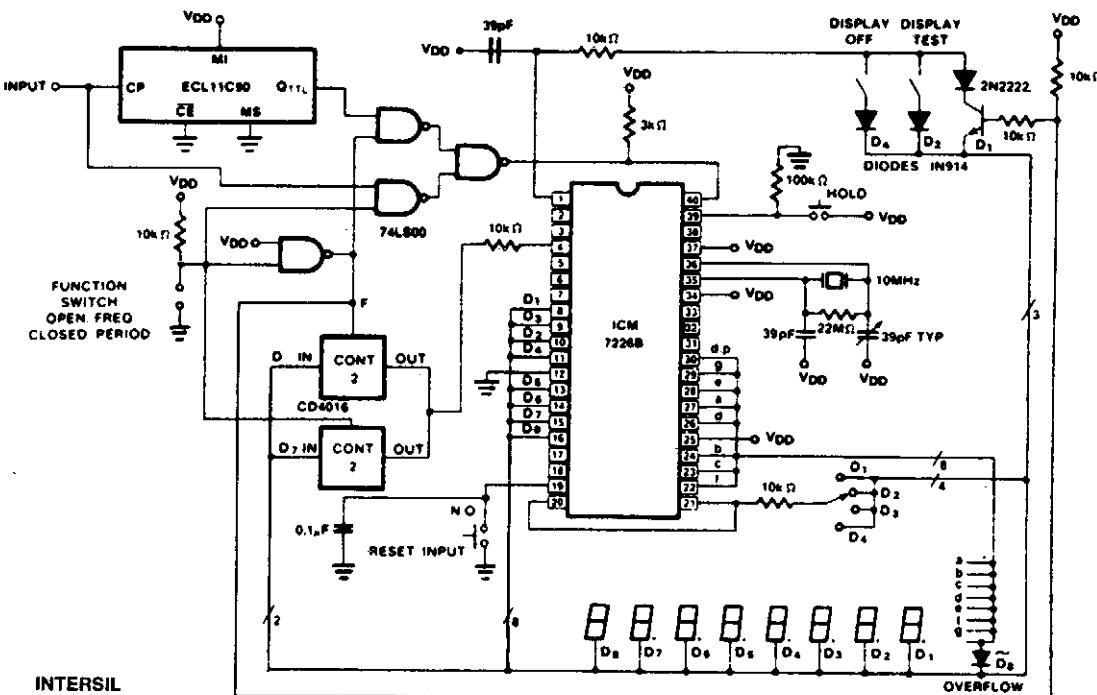


*Fig. 18-5*

### Circuit Notes

The figure shows the use of a CD4016 analog multiplex to multiplex the digital outputs back to the FUNCTION input. Since the CD4016 is a digitally controlled analog transmission gate, no level shifting of the digit output is required. The CD4051's or CD4052's could also be used to select the proper inputs for the multiplexed input on the ICM7226 from 2 or 3 bit digital inputs. These analog multiplexers may also be used in systems in which the mode of operation is controlled by a microprocessor rather than directly from front panel switches. TTL multiplexers such as the 74LS153 or 74LS251 may also be used, but some additional circuitry will be required to convert the digit output to TTL compatible logic levels.

## ANALOG COUNTER CIRCUIT

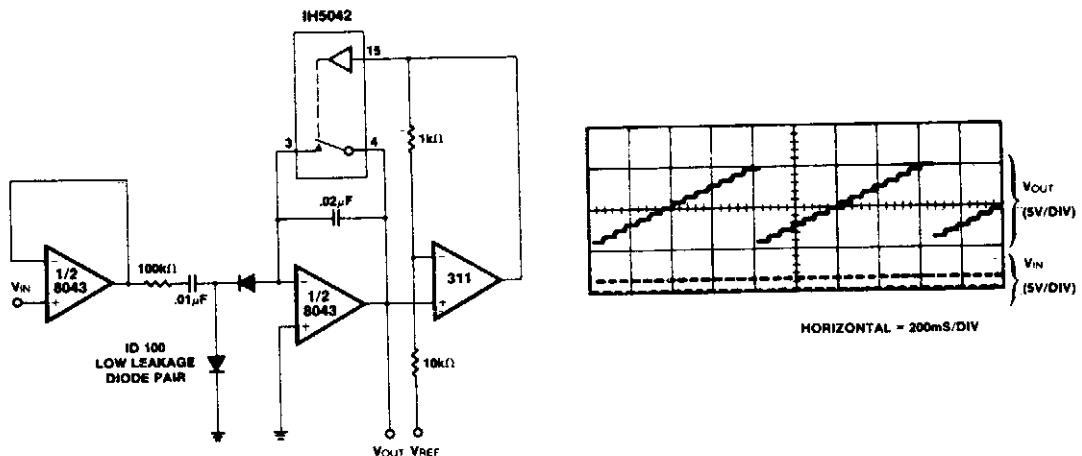


*Fig. 18-6*

INTERSIL

### Circuit Notes

A straightforward circuit using a LM311 for the level detector and a CMOS analog gate to discharge the capacitor is shown. An important property of this type of counter is the ease with which the count can be changed; it is only necessary to change the voltage at which the comparator trips. A low cost A-D converter can also be designed using the same principle since the digital count between reset periods is directly proportional to the analog voltage used as a reference for the comparator. A considerable amount of hysteresis is used in the comparator. This ensures that the capacitor is completely discharged during the reset period. In a more sophisticated circuit, a dual comparator "window detector" could be used, the lower trip point is set close to ground to ensure complete discharge. The upper trip point could then be adjusted independently to determine the pulse count.

## ATTENDANCE COUNTER

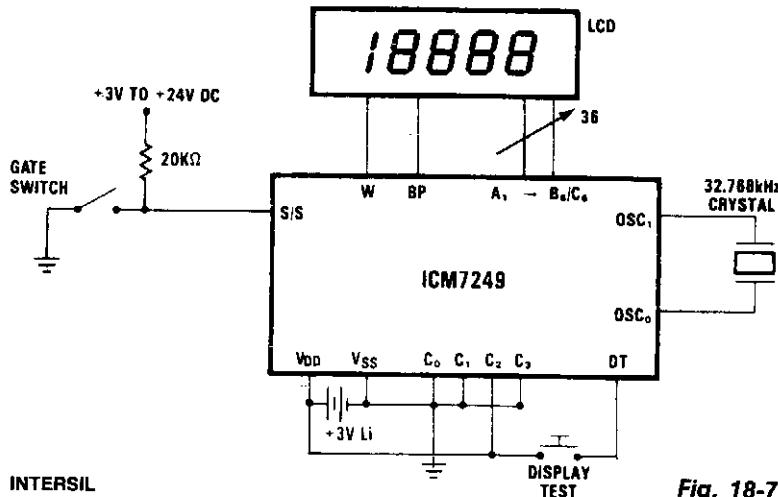


*Fig. 18-7*

### Circuit Notes

The display shows each increment. By using mode 2, external debouncing of the gate switch is unnecessary, provided the switch bounce is less than 35ms. The 3 V lithium battery can be replaced without disturbing operation if a suitable capacitor is connected in parallel with it. The display should be disconnected, if possible, during the procedure to minimize current drain. The capacitor should be large enough to store charge for the amount of time needed to physically replace the battery ( $t = VC/I$ ). A  $100 \mu\text{F}$  capacitor initially charged to 3 V will supply a current of  $1.0 \mu\text{A}$  for 50 seconds before its voltage drops to 2.5 V, which is the minimum operating voltage for the ICM7249.

Before the battery is removed, the capacitor should be placed in parallel, across the V<sub>DD</sub> and GND terminals. After the battery is replaced, the capacitor can be removed and the display reconnected.

## **10 MHz UNIVERSAL COUNTER**

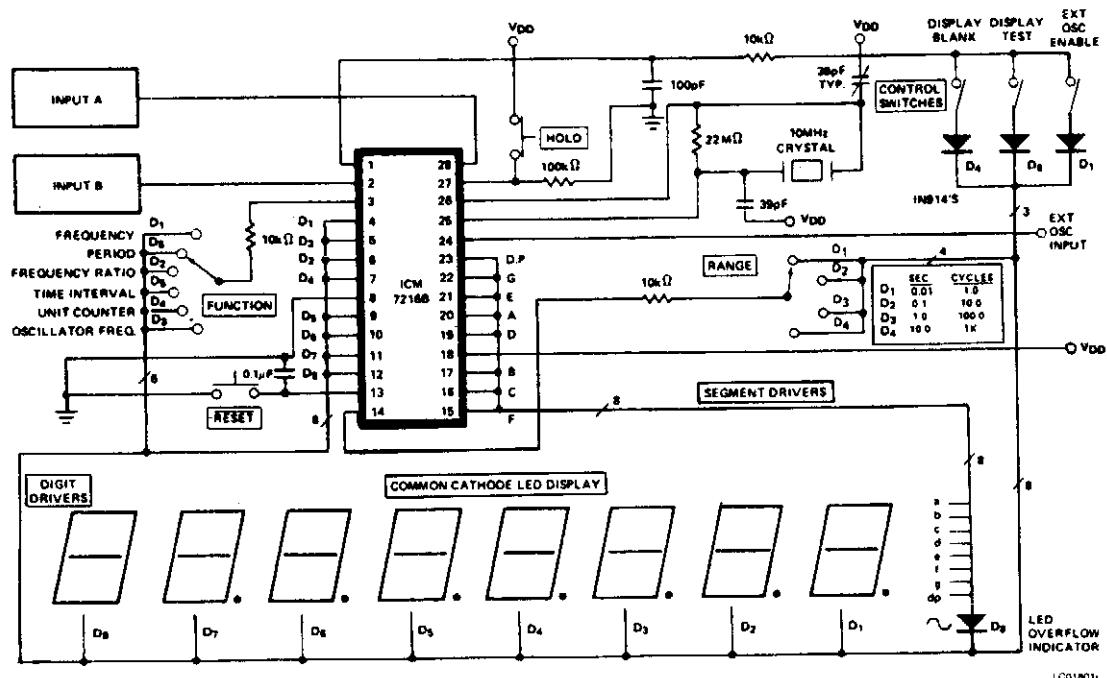

**Fig. 18-8**

**INTERSIL**

**Circuit Notes**

The ICM7216A or B can be used as a minimum component complete Universal Counter. This circuit can use input frequencies up to 10 MHz at INPUT A and 2 MHz at INPUT B. If the signal at INPUT A has a very low duty cycle it may be necessary to use a 74121 monostable multivibrator or similar circuit to stretch the input pulse width to be able to guarantee that it is at least 50 ns in duration.

# 19

## Crystal Oscillators

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Varactor-Tuned 10 MHz Ceramic Resonator  
Oscillator

10 MHz Crystal-Controlled Oscillator

Low Power, 5V Driven, Temperature Compensated  
Crystal Oscillator (TXCO)

Crystal-Controlled LO for SSB Transmitter  
Crystal Oscillator

Crystal Controlled Signal Source

1 MHz FET Crystal Oscillator

Pierce Crystal Oscillator

IC-Compatible Crystal Oscillator

Crystal Oscillator Provides Low Noise

Low-Frequency Crystal Oscillator-10 kHz-150 kHz

Overtone Crystal Oscillator

Colpitts Oscillator

Crystal-Controlled Oscillator

High-Frequency Crystal Oscillator


Crystal-Controlled Oscillator Operates from One  
Mercury Cell

High-Frequency Signal Generator

Crystal Tester

Crystal Stabilized IC Timer can Provide  
Subharmonic Frequencies

## VARACTOR-TUNED 10 MHz CERAMIC RESONATOR OSCILLATOR

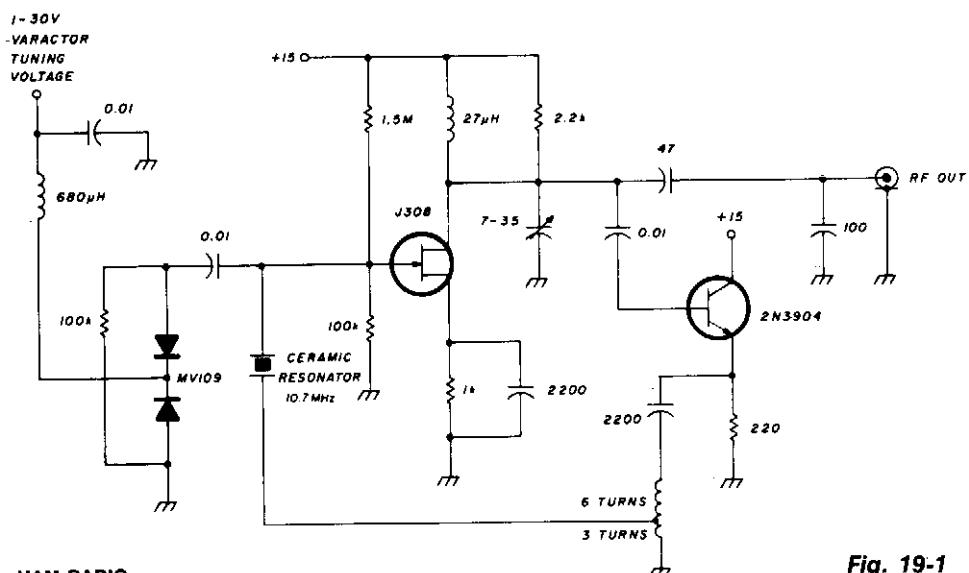

**Fig. 19-1**


### Circuit Notes

The FET input amplifier has fixed bias with source feedback. This provides a very high input impedance with very low capacitance. The FET amplifier drives an emitter follower which, in spite of the fact that it has a low output impedance, feeds a transformer with a 3:1 turns ratio for a nine-fold impedance reduction. The result is an impedance at the ceramic resonator of a few ohms maximum. The varactor-tuned ceramic resonator oscillator has a significant frequency-temperature coefficient. The tuning range of the VCO is approximately 232 kHz, with a temperature coefficient of -350 Hz per degree centigrade. When using this circuit as a VCO, the entire 232 kHz range cannot be used because some of the tuning range must be sacrificed for the temperature dependence. If the required tuning range were 200 kHz, leaving 32 kHz for temperature variation, the resulting temperature variation would be more than 90°C.

## 10 MHz CRYSTAL OSCILLATOR

### Circuit Notes

This xtal oscillator is a FET equivalent of a vacuum tube tuned to plate-tuned grid xtal oscillator. Feedback is via the drain to gate capacitance.

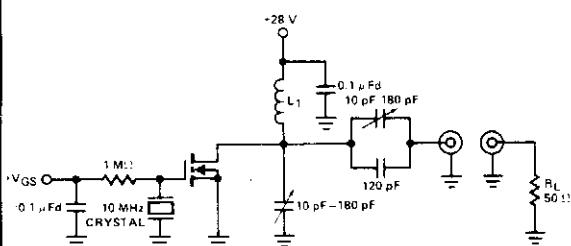

**Fig. 19-2**

**Parts List**

L<sub>1</sub> ~ 18 turns #22 enameled wire on micrometals  
T-50-6 torroid core.  $\approx 1.0 \mu\text{H}$ .

### LOW POWER, 5 V DRIVEN, TEMPERATURE COMPENSATED CRYSTAL OSCILLATOR (TXCO)

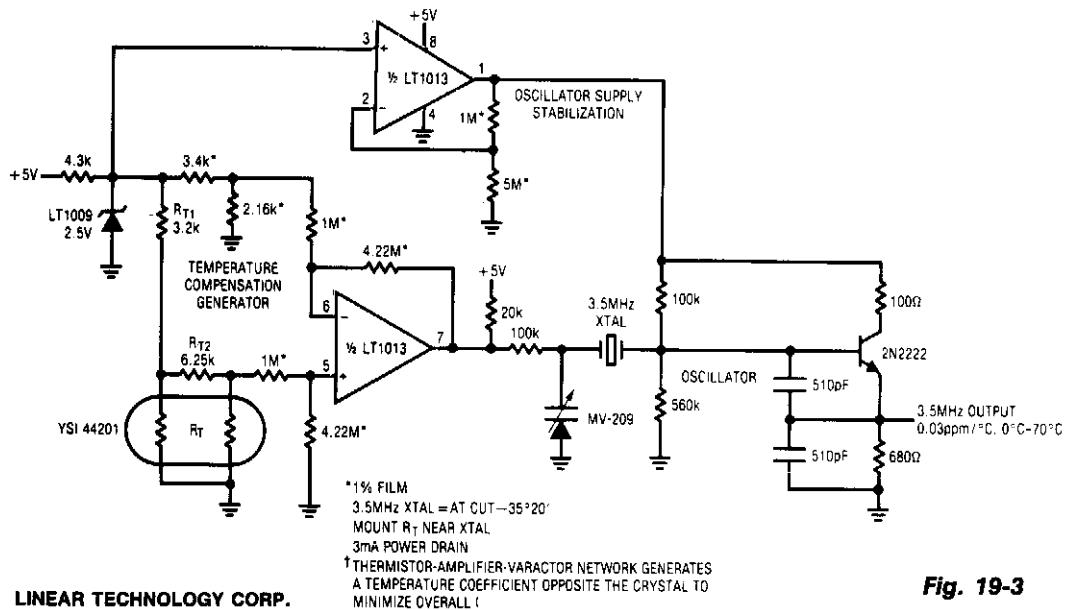


Fig. 19-3

### CRYSTAL-CONTROLLED LOCAL OSCILLATOR FOR SSB TRANSMITTER

OSC.


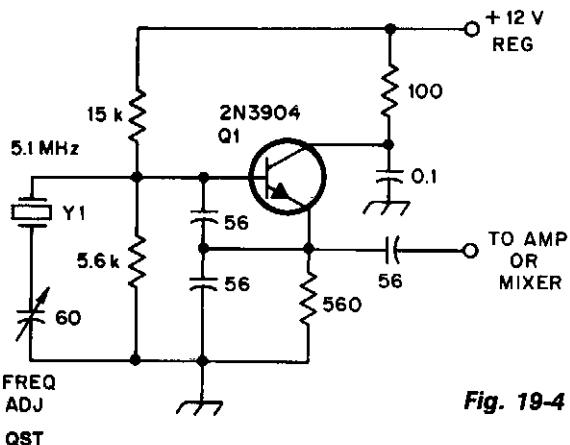


Fig. 19-4

#### Circuit Notes

This oscillator may contain several switched crystals to provide channelized operation. A buffer amplifier may be added, if desired.

## CRYSTAL OSCILLATOR

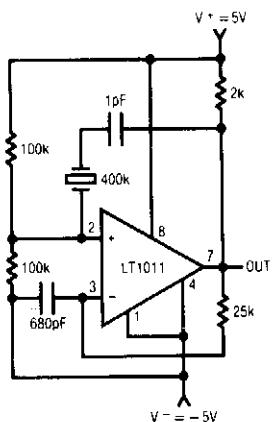


**Fig. 19-5**

### Circuit Notes

This circuit uses an LT1011 comparator biased in its linear mode and a crystal to establish its resonant frequency. This circuit can achieve a few hundred kHz, temperature independent clock frequency with nearly 50% duty cycle.

LINEAR TECHNOLOGY CORPORATION

## CRYSTAL-CONTROLLED SIGNAL SOURCE

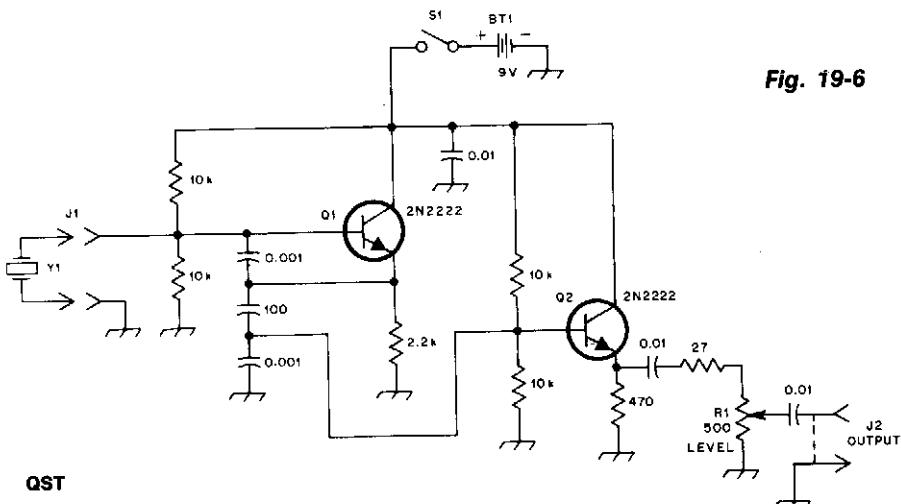


QST

**Fig. 19-6**

### Circuit Notes

This general purpose signal source serves very well in signal-tracing applications. The output level is variable to more than 1 Vrms into a  $50\ \Omega$  load. Almost any crystal in the 1 to 15 MHz range can be used. Q1 forms a Colpitts oscillator with the output taken from the emitter. A capacitive voltage divider (across the 2.2 K emitter resistor) reduces the voltage applied to the buffer amplifier, Q2. The buffer and emitter follower, provides the low input impedance necessary to drive  $50\ \Omega$  loads.

## 1 MHz FET CRYSTAL OSCILLATOR

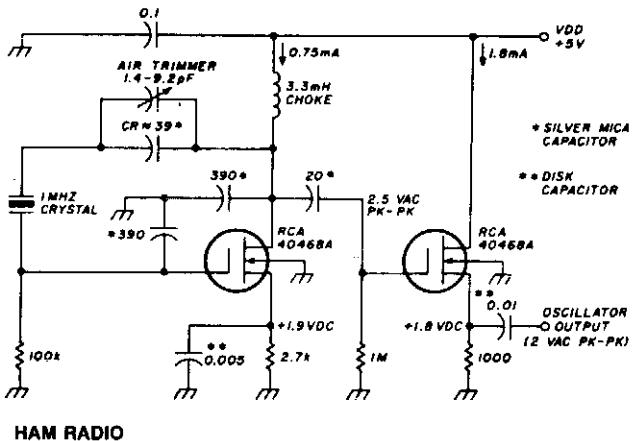


*Fig. 19-7*

### Circuit Notes

This stable oscillator circuit exhibits less than 1 Hz frequency change over a  $V_{DD}$  range of 3-9 volts. Stability is attributed to the use of MOSFET devices and the use of stable capacitors.

## PIERCE CRYSTAL OSCILLATOR

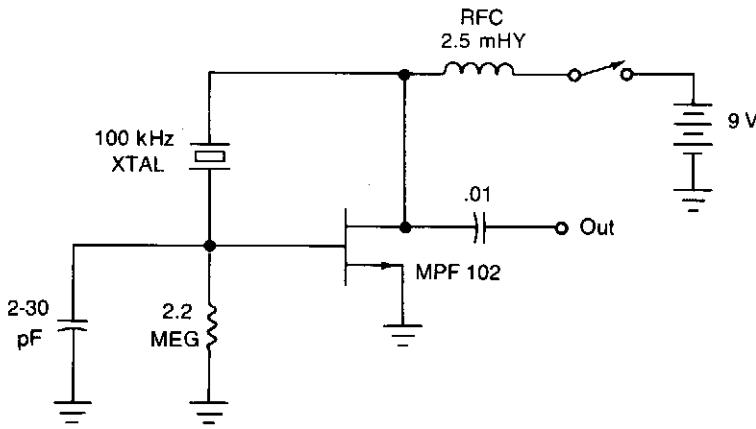


*Fig. 19-8*

### Circuit Notes

The JFET Pierce oscillator is stable and simple. It can be the clock of a microprocessor, a digital timepiece or a calculator. With a probe at the output, it can be used as a precise injection oscillator for troubleshooting. Attach a small length of wire at the output and this circuit becomes a micropower transmitter.

## IC-COMPATIBLE CRYSTAL OSCILLATOR

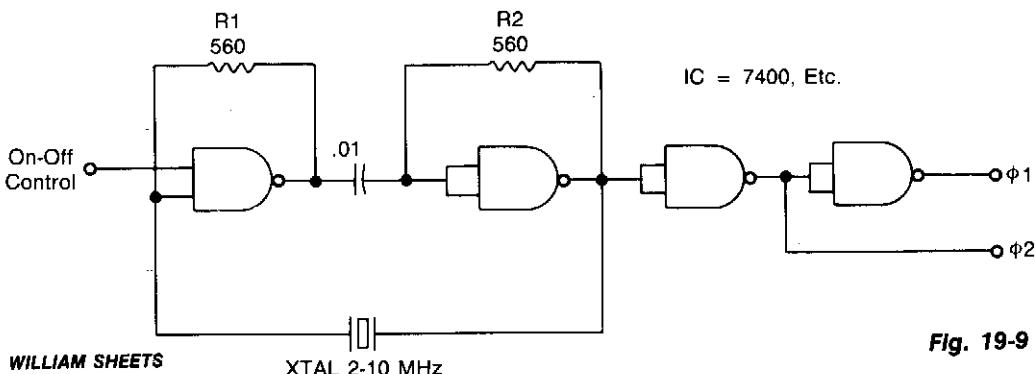


**Fig. 19-9**

### Circuit Notes

Resistors R1 and R2 temperature-stabilize the NAND gates; they also ensure that the gates are in a linear region for starting. Capacitor C1 is a dc block; it must have less than  $\frac{1}{10}$  ohm impedance at the operating frequency. The crystal runs in a series-resonant mode. Its series resistance must be low; AT-cut crystals for the 1- to 10-MHz range work well. The output waveshape has nearly a 50% duty cycle, with chip-limited rise times. The circuit starts well from  $0^\circ$  to  $70^\circ\text{C}$ .

## CRYSTAL OSCILLATOR PROVIDES LOW NOISE

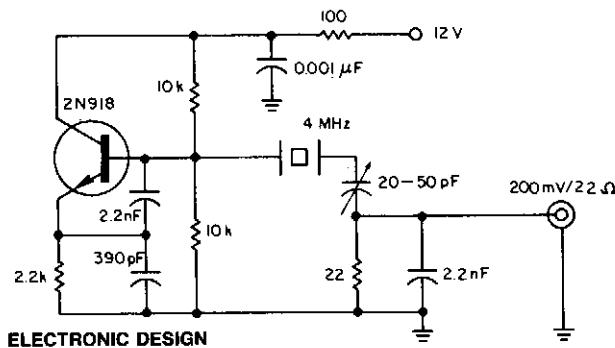

**Fig. 19-10**

### Circuit Notes

The oscillator delivers an output of high spectral purity without any substantial sacrifice of the usual stability of a crystal oscillator. The crystal in addition to determining the oscillator's frequency, is used also as a low-pass filter for the unwanted harmonics and as a bandpass filter for the sideband noise. The noise bandwidth is limited to less than 100 Hz. All higher harmonics are substantially suppressed—60 dB down for the third harmonic of the 4-MHz fundamental oscillator frequency.

## LOW-FREQUENCY CRYSTAL OSCILLATOR—10 kHz to 150 kHz


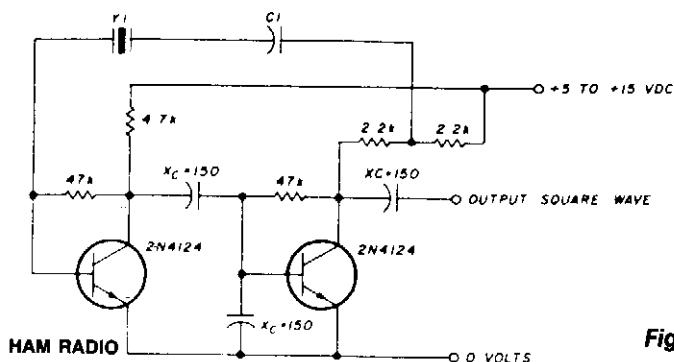


Fig. 19-11

### Circuit Notes

C1 in series with the crystal may be used to adjust the oscillator output frequency. Value may range between 20 pF and 0.01  $\mu$ F, or may be a trimmer capacitor and will approximately equal the crystal load capacitance. X values are approximate and can vary for most circuits and frequencies; this is also true for resistance values. Adequate power supply decoupling is required; local decoupling capacitors near the oscillator are recommended. All leads should be extremely short in high frequency circuits.

## OVERTONE CRYSTAL OSCILLATOR

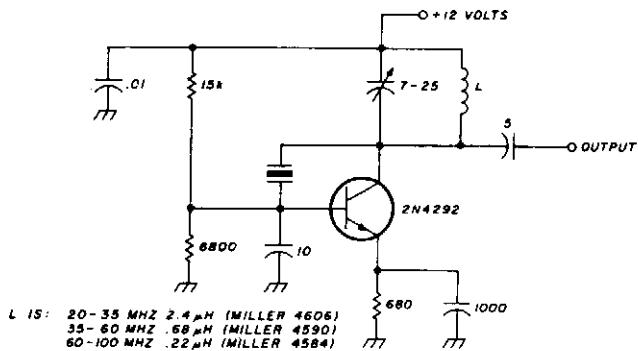


HAM RADIO

Fig. 19-12

### Circuit Notes

This oscillator is designed for overtone crystals in the 20-100 MHz range operating in the third and fifth mode. Operating frequency is determined by the tuned circuit.

## COLPITTS OSCILLATOR

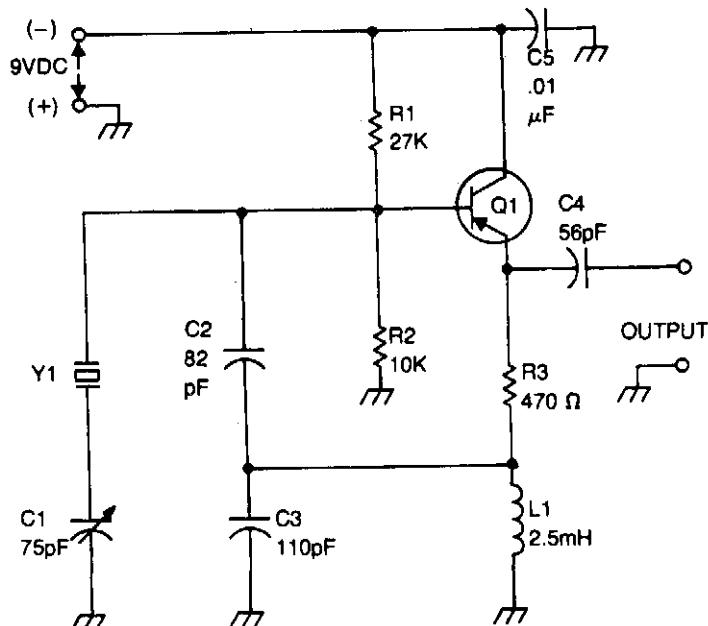


*Fig. 19-13*

TAB BOOKS, INC.

### Circuit Notes

Bias for the pnp bipolar transistor is provided by resistor voltage divider network R1/R2. The collector of the oscillator transistor is kept at ac ground by capacitor C5, placed close to the transistor. Feedback is provided by capacitor voltage divider C2/C3.


## CRYSTAL-CONTROLLED OSCILLATOR

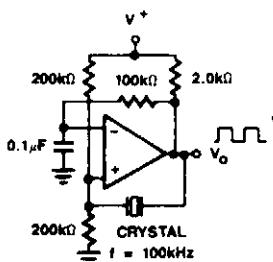


*Fig. 19-14*

SIGNETICS

## HIGH-FREQUENCY CRYSTAL OSCILLATOR

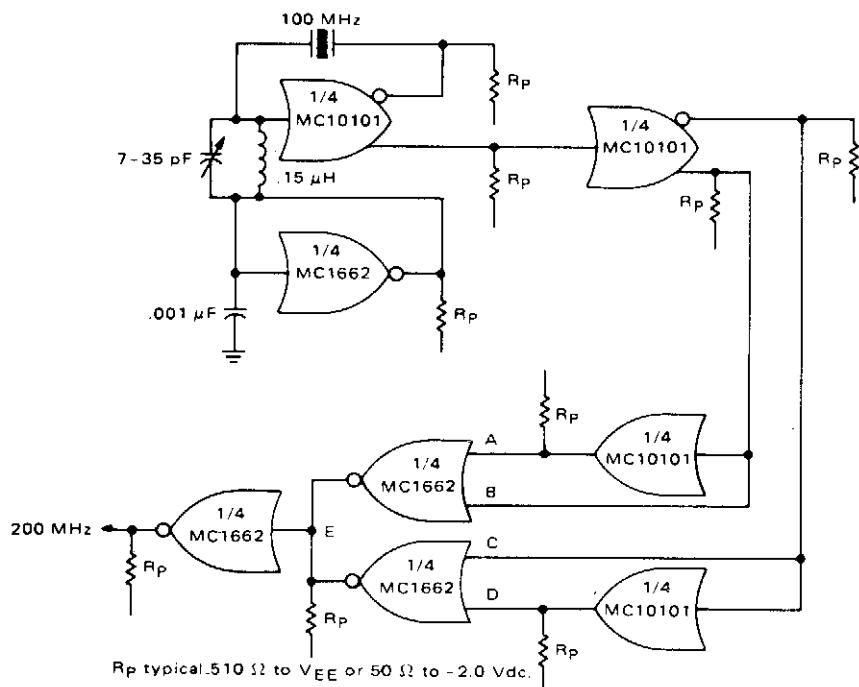

200 MHz Crystal Oscillator

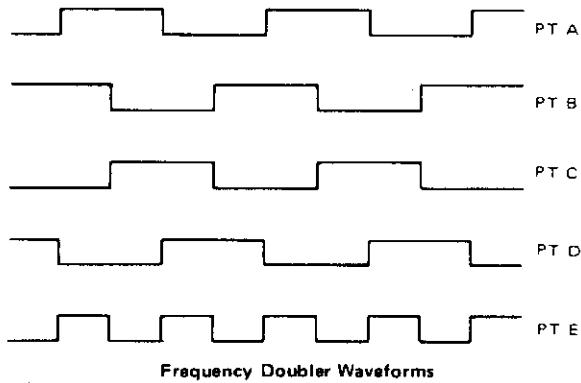

Frequency Doubler Waveforms

MOTOROLA, INC.

*Fig. 19-15*

## HIGH-FREQUENCY CRYSTAL OSCILLATOR, Continued.

### Circuit Notes

A high speed oscillator is possible by combining an MECL 10 K crystal oscillator with an MECL III frequency doubler as shown. One section of the MC10101 is connected as a 100 MHz crystal oscillator with the crystal in series with the feedback loop. The LC tank circuit tunes the 100 MHz harmonic of the crystal and may be used to calibrate the circuit to the exact frequency. A second section of the MC10101 buffers the crystal oscillator and gives complementary 100 MHz signals. The frequency doubler consists of two MC10101 gates as phase shifters and two MC1662 NOR gates. For a 50% duty cycle at the output, the delay to the true and complement 100 MHz signals should be 90°. This may be built precisely with 2.5 ns delay lines for the 200 MHz output or approximated by the two MC10101 gates. The gates are easier to incorporate and cause only a slight skew in output signal duty cycle. The MC1662 gates combine the 4 phase 100 MHz signals as shown in Figure B. The outputs of the MC1662's are wire-OR connected to give the 200 MHz signal. MECL III gates are used because of the bandwidth required for 200 MHz signals. One of the remaining MC1662 gates is used as a  $V_{BB}$  bias generator for the oscillator. By connecting the NOR output to the input, the circuit stays in the center of the logic swing or at  $V_{BB}$ . A 0.001  $\mu F$  capacitor ensures the  $V_{BB}$  circuit does not oscillate.

## CRYSTAL-CONTROLLED OSCILLATOR OPERATES FROM ONE MERCURY CELL

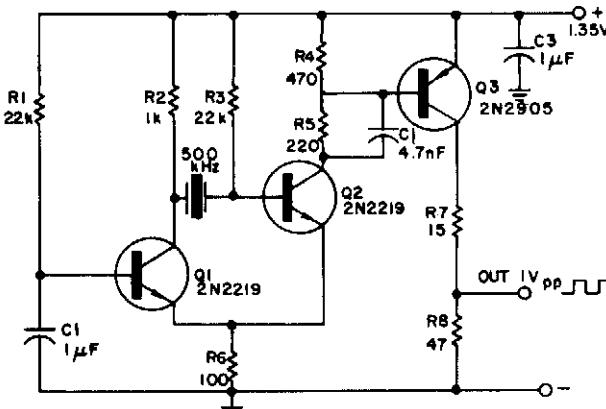


Fig. 19-16


ELECTRONIC DESIGN

Inexpensive crystal controlled oscillator operates from a 1.35-volt source.

### Circuit Notes

The circuit is powered by a single 1.35 V mercury cell and provides a 1 V square-wave output. As shown, the crystal is a tuned circuit between transistors Q1 and Q2, which are connected in the common-emitter configuration. Positive feedback provided by means of R permits oscillation. The signal at the collector of Q2 is squared by Q3, which switches between cutoff and saturation. R7 permits short-circuit-proof operation.

## HIGH FREQUENCY SIGNAL GENERATOR

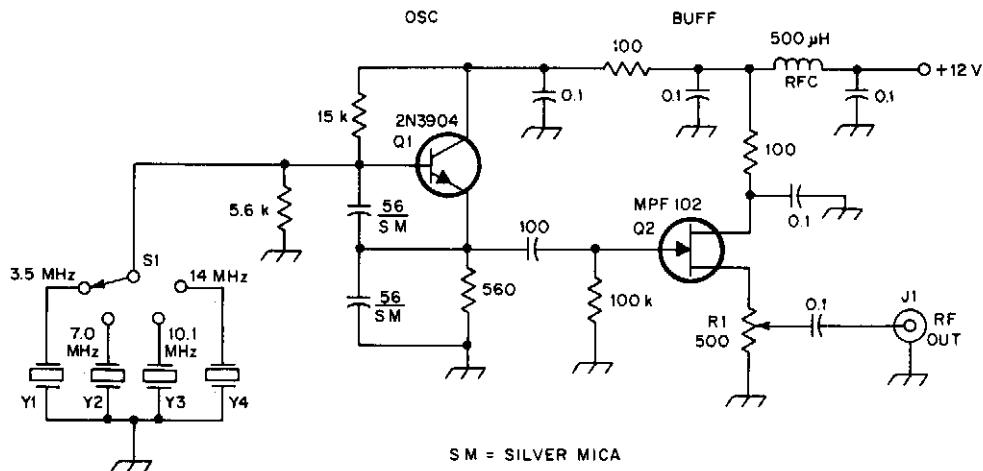


**QST**

**Fig. 19-17**

### Circuit Notes

A tapped-coil Colpitts oscillator is used at Q1 to provide four tuning ranges from 1.7 to 3.1 MHz, 3.0 to 5.6 MHz, 5.0 to 12 MHz and 11.5 to 31 MHz. A Zener diode (D2) is used at Q1 to lower the operating voltage of the oscillator. A small value capacitor is used at C5 to ensure light coupling to the tuned circuit. Q2 is a source-follower buffer stage. It helps to isolate the oscillator from the generator-output load. The source of Q2 is broadly tuned by means of RFC1. Energy from Q2 is routed to a feed-back, broadband class-A amplifier. A 2 dB attenuator is used at the output of T1 to provide a 50 ohm termination for Q3 and to set the generator-output impedance at 50 ohms. C16, C17 and RFC2 form a brute-force RF decoupling network to keep the generator energy from radiating outside the box on the 12 V supply.

## CRYSTAL TESTER

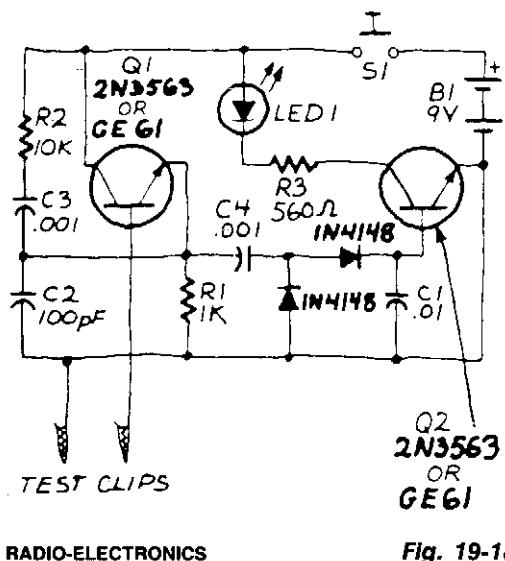


**Fig. 19-18**
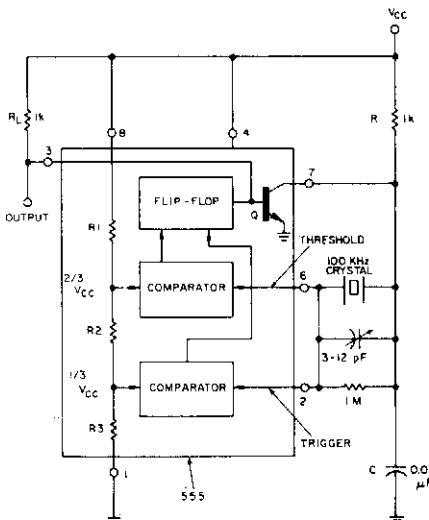
### Circuit Notes

Transistor Q1, a 2N3563, and its associated components form an oscillator circuit that will oscillate if, and only if, a good crystal is connected to the test clips. The output from the oscillator is then rectified by the two 1N4148 diodes and filtered by C1, a .01  $\mu$ F capacitor. The positive voltage developed across the capacitor is applied to the base of Q2, another 2N3563, causing it to conduct. When that happens, current flows through LED1, causing it to glow. Since only a good crystal will oscillate, a glowing LED indicates that the crystal is indeed OK. The circuit is powered by a standard nine-volt transistor-radio battery and the SPST pushbutton power-switch is included to prolong battery life.

## CRYSTAL-STABILIZED IC TIMER CAN PROVIDE SUBHARMONIC FREQUENCIES



**ELECTRONIC DESIGN**

The trimmer across the crystal can finely tune the circuit's oscillating frequency.

**Fig. 19-19**

# **20**

## **Current Meters**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Ammeter with Six Decade Range
- Current Sensing in Supply Rails
- Pico Ammeter
- Electrometer Amplifier with Overload Protection
- Guarded Input Picoammeter Circuit
- Ammeter with Six Decade Range
- Picoammeter Circuit

## AMMETER WITH SIX DECADE RANGE

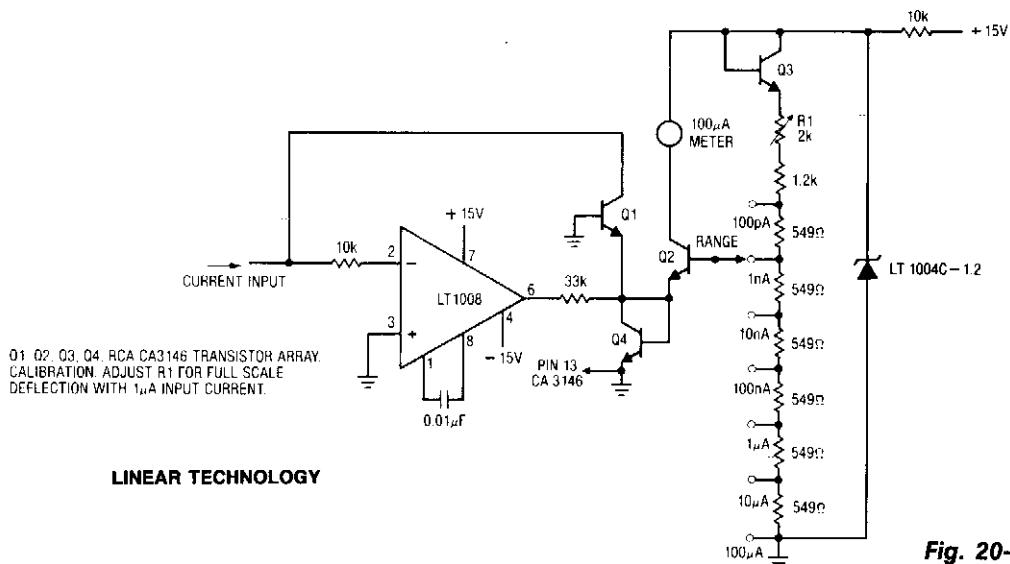


**Fig. 20-1**
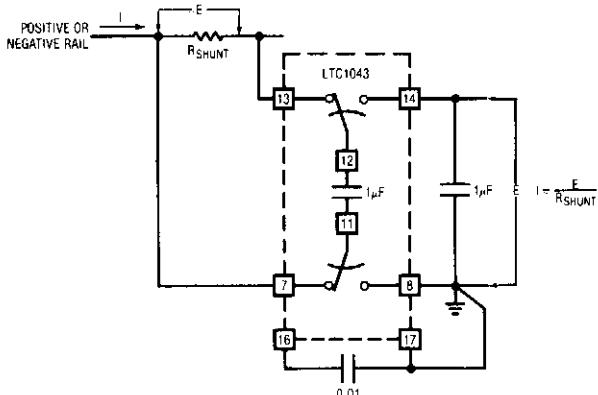
### Circuit Notes

The Ammeter measures currents from 100 pA to 100 μA without the use of expensive high value resistors. Accuracy at 100 μA is limited by the offset voltage between Q1 and Q2 and, at 100 pA, by the inverting bias current of the LT1008.

## CURRENT SENSING IN SUPPLY RAILS



### Circuit Notes

The LTC1043 can sense current through a shunt in either of its supply rails. This capability has wide application in battery and solar-powered systems. If the ground-referred voltage output is unloaded by an amplifier, the shunt can operate with very little voltage drop across it, minimizing losses.

## PICO AMMETER


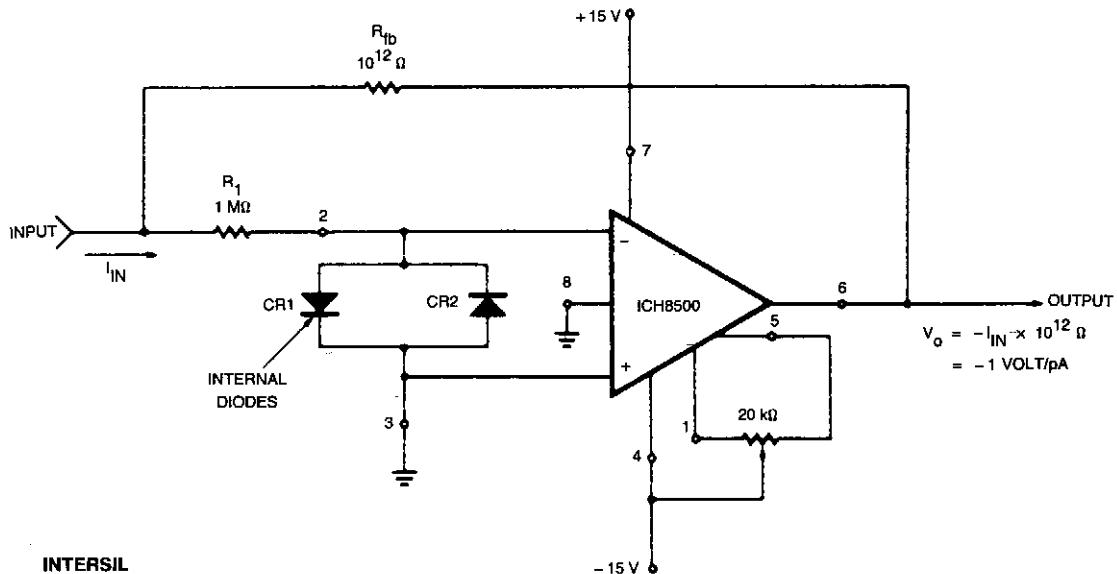


Fig. 20-3

### Circuit Notes

Care must be taken to eliminate any stray currents from flowing into the current summing node. This can be accomplished by forcing all points surrounding the input to the same potential as the input. In this case the potential of the input is at virtual ground, or OV. Therefore, the case of the device is grounded to intercept any stray leakage currents that may otherwise exist between the  $\pm 15$  V input terminals and the inverting input summing junctions. Feedback capacitance should be kept to a minimum in order to maximize the response time of the circuit to step function input currents. The time constant of the circuit is approximately the product of the feedback capacitance  $C_{fb}$  times the feedback resistor  $R_{fb}$ . For instance, the time constant of the circuit is 1 sec if  $C_{fb} = 1\text{pF}$ . Thus, it takes approximately 5 sec (5 time constants) for the circuit to stabilize to within 1% of its final output voltage after a step function of input current has been applied.  $C_{fb}$  of less than 0.2 to 0.3 pF can be achieved with proper circuit layout.
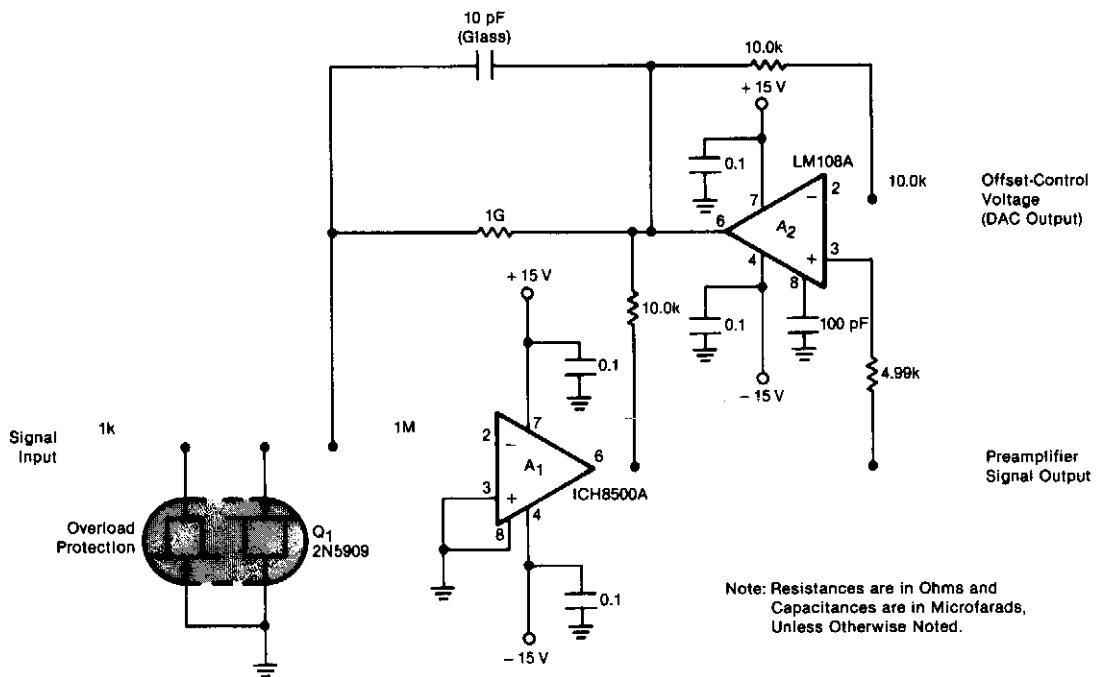
## ELECTROMETER AMPLIFIER WITH OVERLOAD PROTECTION




NASA TECH BRIEFS

Fig. 20-4

### Circuit Notes

The preamplifier is protected from excessive input signals of either polarity by the 2N5909 junction field-effect transistor. A nulling circuit makes it possible to set the preamplifier output voltage to zero at a fixed low level (up to  $\pm 10^{-8}$ A) of the input current. (This level is called the standing current and corresponds to the zero-signal level of the instrumentation.) The opposing (offset) current is generated in the  $10^9$  feedback resistor to buck the standing current. Different current ranges are reached by feeding the preamplifier output to low and high gain amplifier chains. To reduce noise, each chain includes a 1.5 Hz corner active filter.

## GUARDED INPUT PICOAMMETER CIRCUIT

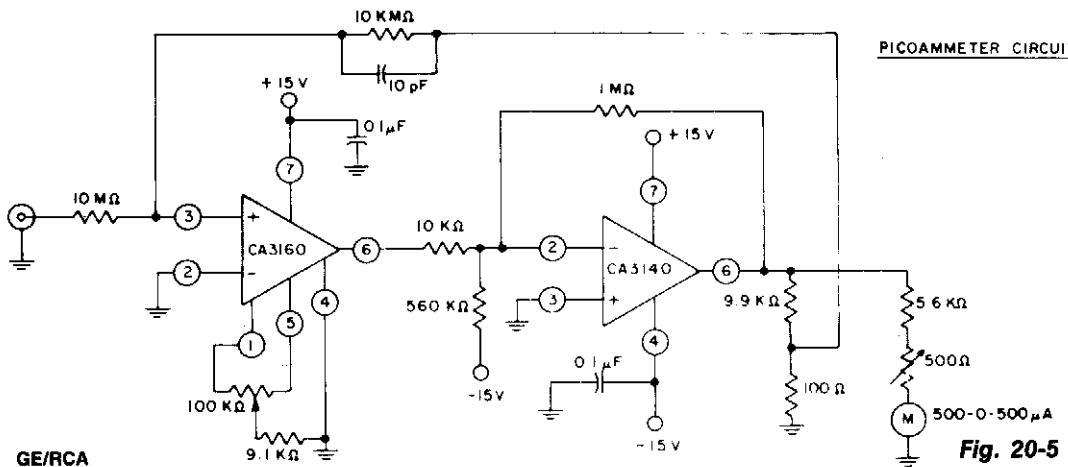

**Fig. 20-5**


### Circuit Notes

The circuit utilizes CA3160 and CA3140 BiMOS op amps to provide a full-scale meter deflection of  $\pm 3 \mu\text{A}$ . The CA3140 serves as an X100 gain stage to provide the required plus and minus output swing for the meter and feedback network. Terminals 2 and 4 of the CA3160 are at ground potential, thus its input is operated in the "guarded mode."

## AMMETER WITH SIX DECADE RANGE

LINEAR TECHNOLOGY CORP.

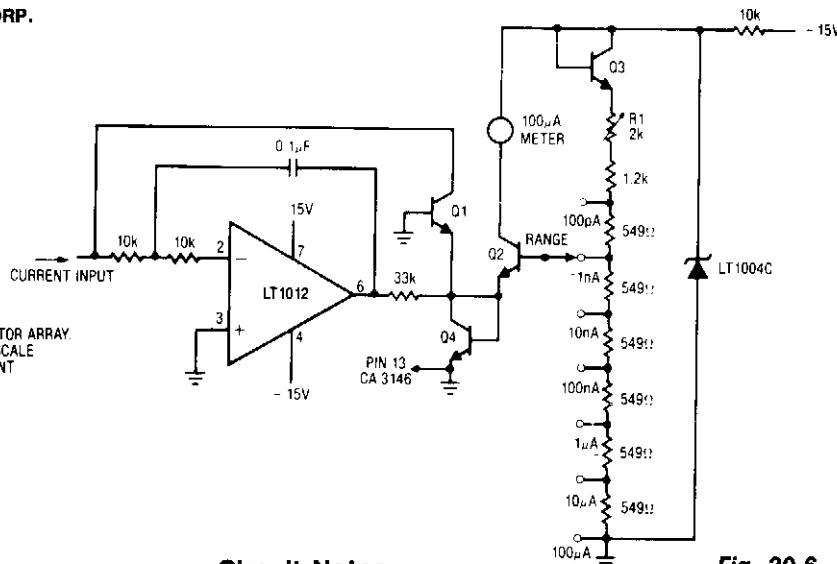Q1, Q2, Q3, Q4, RCA CA3146 TRANSISTOR ARRAY.  
CALIBRATION: ADJUST R1 FOR FULL SCALE  
DEFLECTION WITH  $1\mu\text{A}$  INPUT CURRENT




### Circuit Notes

The Ammeter measures currents from  $100 \text{ pA}$  to  $100 \mu\text{A}$  without the use of expensive high value resistors. Accuracy at  $100 \mu\text{A}$  is limited by the offset voltage between Q1 and Q2 and, at  $100 \text{ pA}$ , by the inverting bias current of the LT1008.

**Fig. 20-6**

## PICOAMMETER CIRCUIT

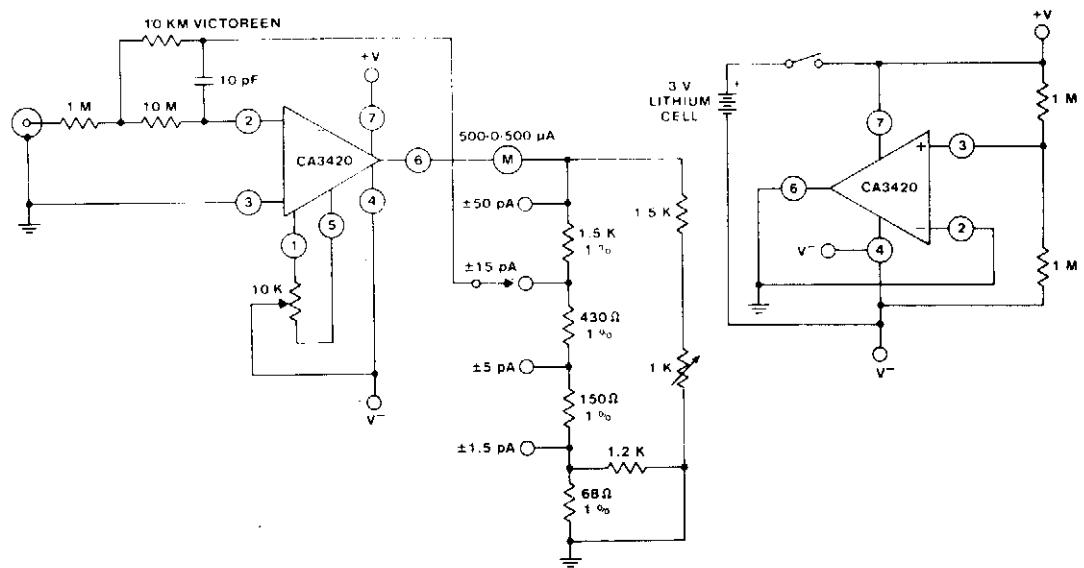

**GENERAL ELECTRIC /RCA**

**Fig. 20-7**

Circuit Notes

The circuit uses the exceptionally low input current (0.1pA) of the CA3420 BiMOS op amp. With only a single 10 megohm resistor, the circuit covers the range from  $\pm 50$  pA maximum to a full-scale sensitivity of  $\pm 1.5$  pA. Using an additional CA3420, a low-resistance center tap is obtained from a single 3-volt lithium battery.

# **21**

## **Demodulators**

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Narrow Band FM Demodulator with Carrier Detect  
Stereo Demodulator  
AM Demodulator  
FM Demodulator

## NARROW BAND FM DEMODULATOR WITH CARRIER DETECT


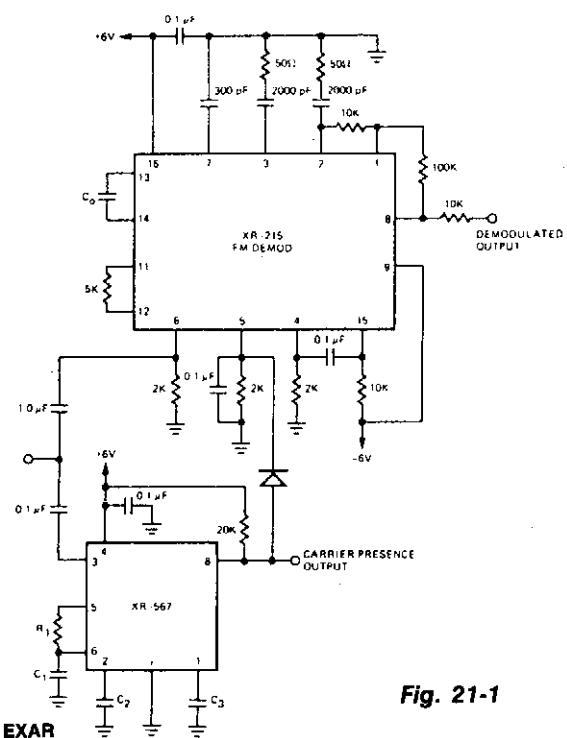


Fig. 21-1

## Circuit Notes

For FM demodulation applications where the bandwidth is less than 10% of the carrier frequency, an XR-567 can be used to detect the presence of the carrier signal. The output of the XR-567 is used to turn off the FM demodulator when no carrier is present, thus acting as a squelch. In the circuit shown, an XR-215 FM demodulator is used because of its wide dynamic range, high signal/noise ratio and low distortion. The XR-567 will detect the presence of a carrier at frequencies up to 500 kHz.

## STEREO DEMODULATOR

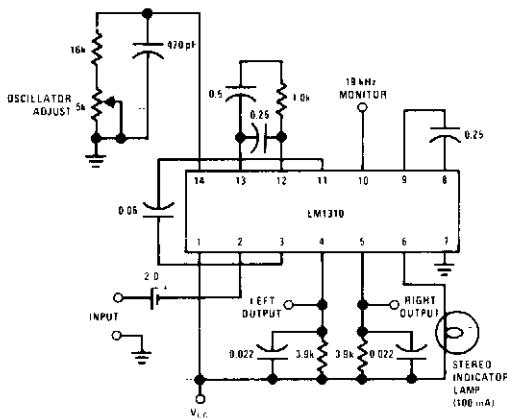


## Circuit Notes

This circuit uses a single IC LM1310 to provide left and right outputs from a composite MPX stereo signal. Oscillator adjust R1 is set for 76 kHz (19 kHz at pin 10). C1 should be a silver mica or NPO ceramic capacitor.

NATIONAL SEMICONDUCTOR CORP.

Fig. 21-2

## AM DEMODULATOR

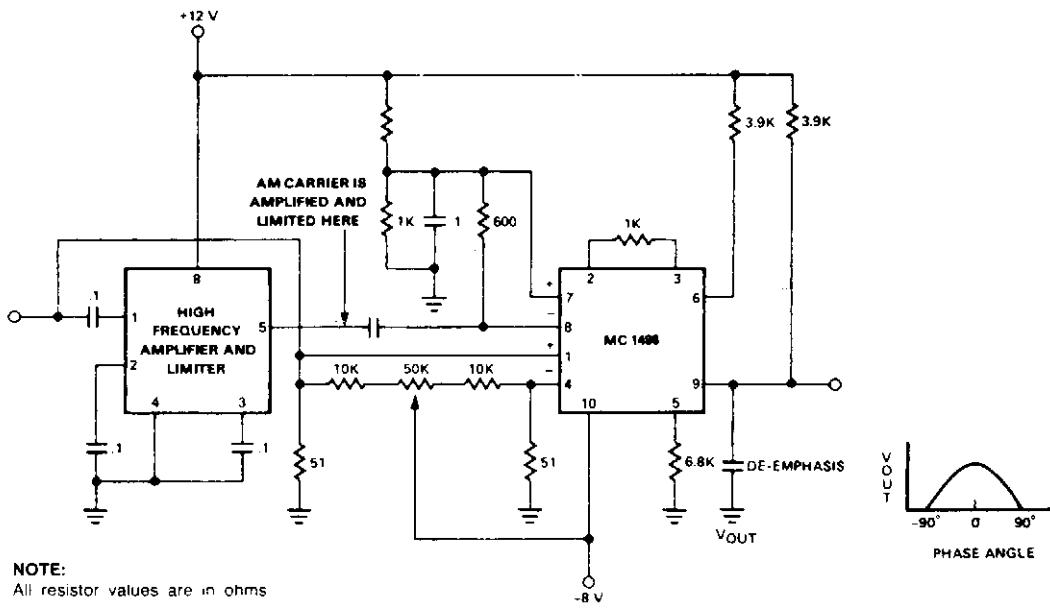

**Fig. 21-3**

**SIGNETICS**

### Circuit Notes

Amplifying and limiting of the AM carrier is accomplished by the if gain block providing 55 dB of gain or higher with a limiting of 40  $\mu$ V. The limited carrier is then applied to the detector at the carrier ports to provide the desired switching function. The signal is then demodulated by the synchronous AM demodulator (1496) where the carrier frequency is attenuated due to the balanced nature of the device. Care must be taken not to overdrive the signal input so that distortion does not appear in the recorded audio. Maximum conversion gain is reached when the carrier signals are in phase as indicated by the phase-gain relationship. Output filtering is also necessary to remove high frequency sum components of the carrier from the audio signal.

## FM DEMODULATOR

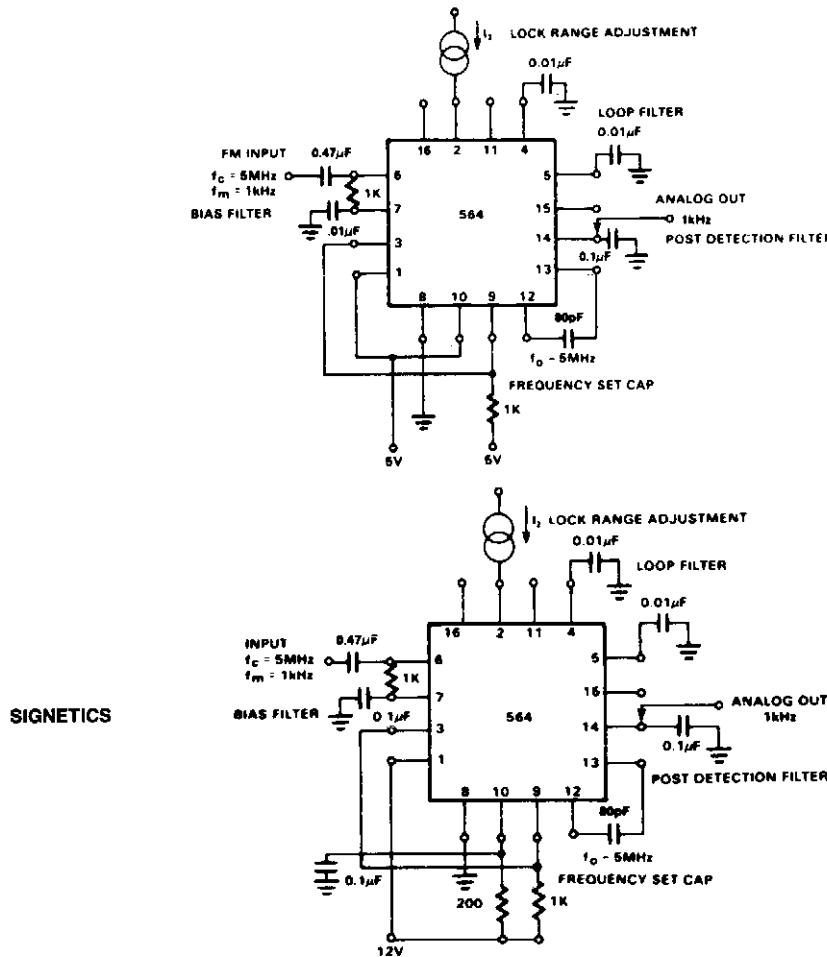


Fig. 21-4

### Circuit Notes

The NE564 is used as an FM demodulator. The connections for operation at 5 V and 12 V are shown in Figures 21-4A and 21-4B. The input signal is ac coupled with the output signal being extracted at Pin 14. Loop filtering is provided by the capacitors at Pins 4 and 5 with additional filtering being provided by the capacitor at Pin 14. Since the conversion gain of the VCO is not very high, to obtain sufficient demodulated output signal the frequency deviation in the input signal should be 1% or higher.

## **22**


# **Descramblers and Decoders**

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Sine Wave Descrambler
- Outband Descrambler
- Gated Pulse Descrambler
- SCA Decoder
- Dual Time Constant Tone-Decoder
- Stereo TV Decoder
- Time Division Multiplex (TDM) Stereo Decoder
- Frequency Division Multiplex (FDM) Stereo Decoder
- SCA (Background Music) Decoder

## SINE WAVE DESCRAMBLER

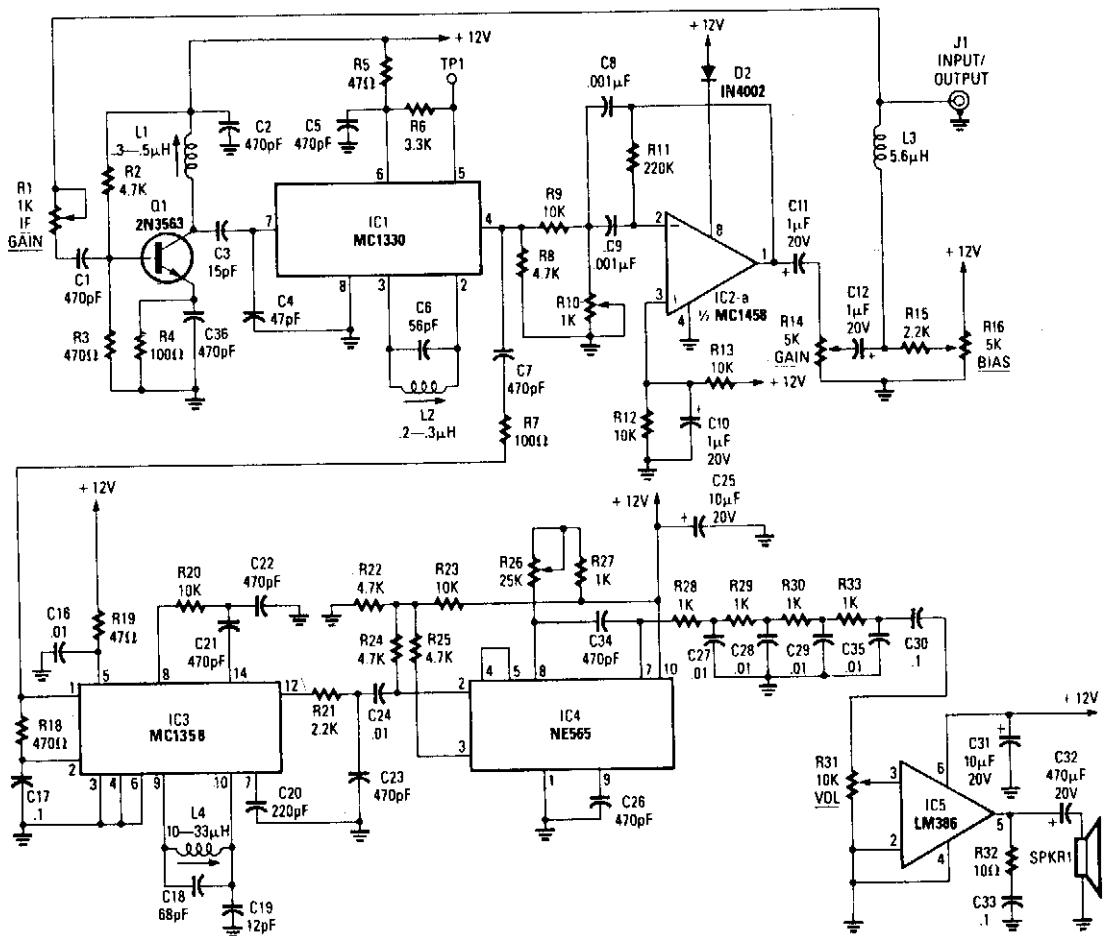

—A COMPLETE SINEWAVE DESCRAMBLER. Easy to build, and relatively easy to align, this circuit completely removes the 15.75-kHz scrambling sinewave.


RADIO-ELECTRONICS

Fig. 22-1

### Circuit Notes

This decoder features a sine wave recovery channel and uses a PIN diode attenuator driven by the sine wave recovery system to cancel out the sine wave sync suppression signal. Kit available from North Country Radio, P.O. Box 53, Wykagyl Station, New York 10804.

## OUTBAND DESCRAMBLER

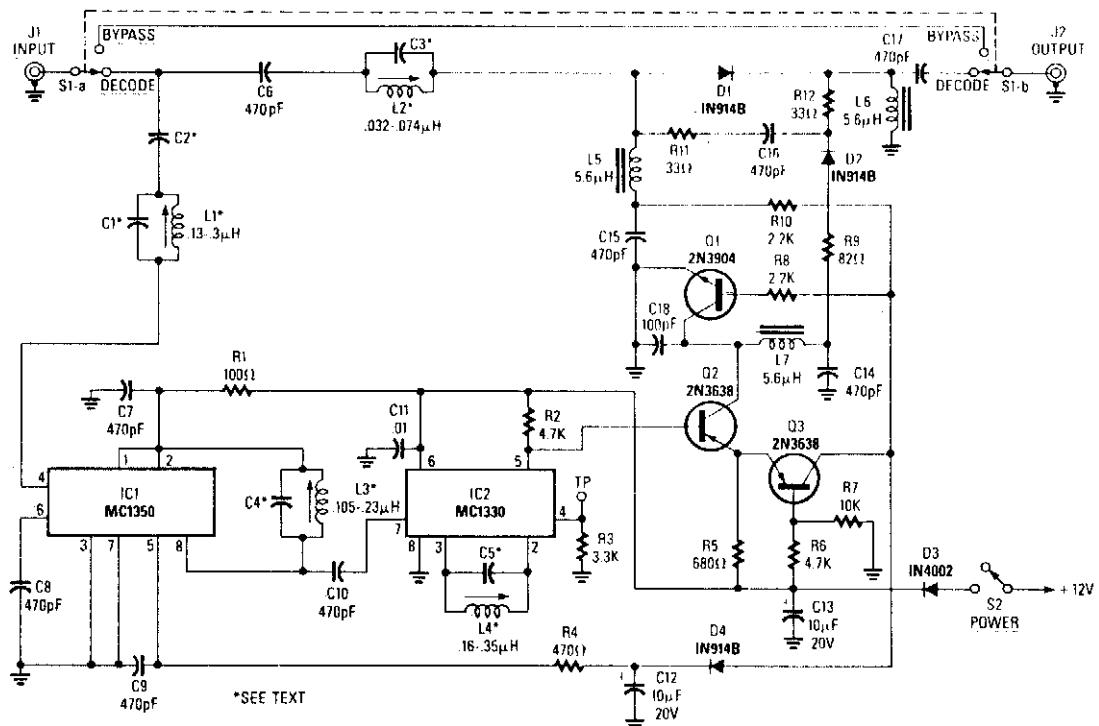

—FOR THE OUTBAND DECODER shown here to work, the cable company must provide at least a 1 millivolt signal. Values for C1-C5 and L1-L4 are found in Table 1.

**TABLE 1—CAPACITOR AND COIL VALUES**

	50 MHz	90–114 MHz
C1	5 pF	5 pF
C2	47 pF	12 pF
C3	200 pF	82 pF
C4	56 pF	12 pF
C5	56 pF	10 pF
L1	0.2 μH	0.2 μH
L2	0.05 μH	0.03 μH
L3	0.175 μH	0.2 μH
L4	0.175 μH	0.24 μH


**Fig. 22-2**

### RADIO-ELECTRONICS

### Circuit Notes

This circuit consists of an amplifier for the sync channel and a video detector which controls an attenuator so that the gain of the systems is increased during sync intervals. Kit available from North Country Radio, P.O. Box 53, Wykagyl Station, New York 10804.

## GATED PULSE DESCRAMBLER

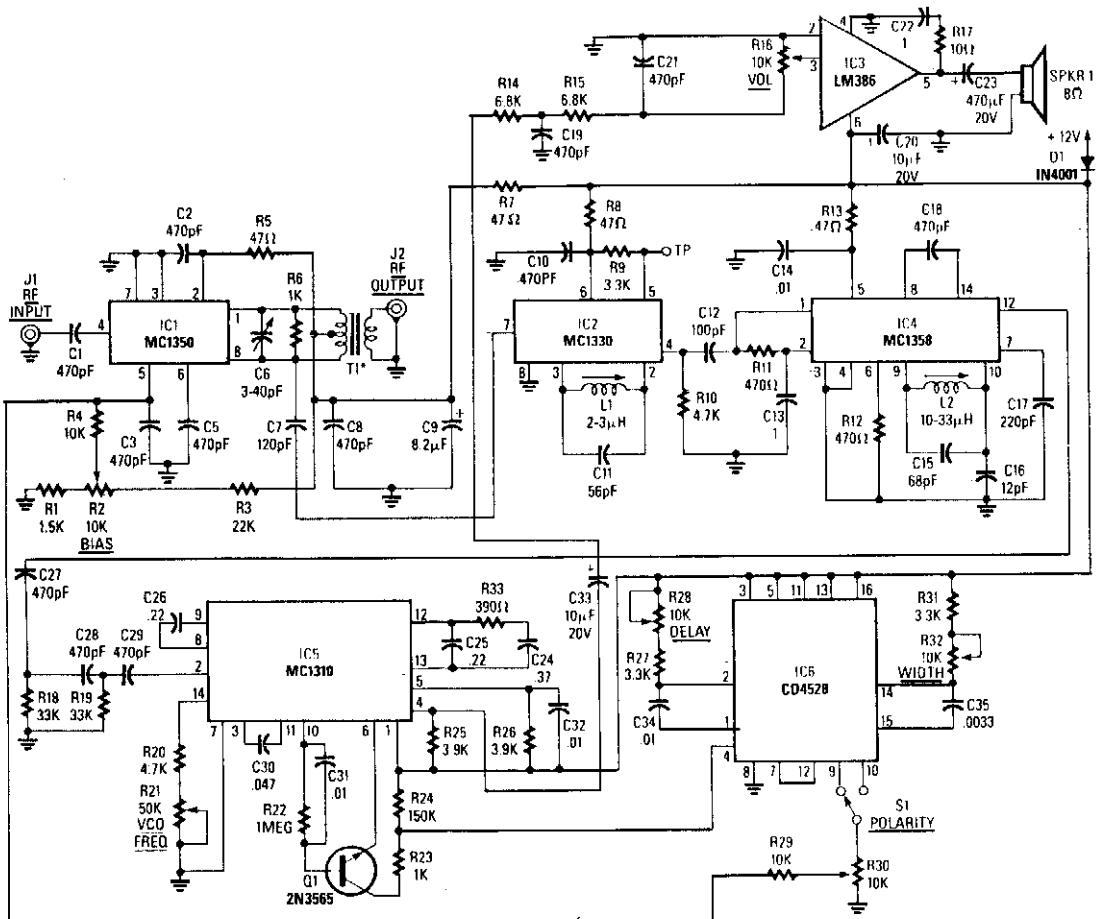

—DESCRAMBLE GATED-PULSE SIGNALS using this easy-to-build circuit. Information for winding transformer T1 and coil L1 can be found in the text.


RADIO-ELECTRONICS

Fig. 22-3

### Circuit Notes

This circuit consists of an amplifier and video detector with a second subcarrier detector for synch recovery purposes. A pulse-former circuit modulates the gain of the main channel increasing it during synch intervals. Provision for subcarrier audio descrambling is also provided. Kit available from North Country Radio, P.O. Box 53, Wykagyl Station, New York 10804.

## **SCA DECODER**

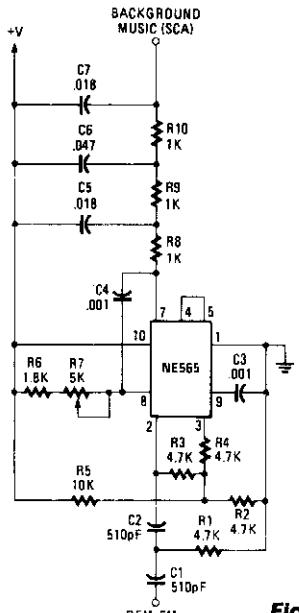


RADIO-ELECTRONICS

# DUAL TIME CONSTANT TONE DECODER


**Circuit Notes**

For some applications it is important to have a tone decoder with narrow bandwidth and fast response time. This can be accomplished by the dual time constant tone decoder circuit shown. The circuit has two low-pass loop filter capacitors,  $C_2$  and  $C'_2$ . With no input signal present, the output at pin 8 is high, transistor  $Q_1$  is off, and  $C'_2$  is switched out of the circuit. Thus, the loop low-pass filter is comprised of  $C_2$ , which can be kept as small as possible for minimum response time. When an in-band signal is detected, the output at pin 8 will go low,  $Q_1$  will turn on, and capacitor  $C'_2$  will be switched in parallel with capacitor  $C_2$ . The low-pass filter capacitance will then be  $C_2 + C'_2$ . The value of  $C'_2$  can be quite large in order to achieve narrow bandwidth. During the time that no input signal is being received, the bandwidth is determined by capacitor  $C_2$ .

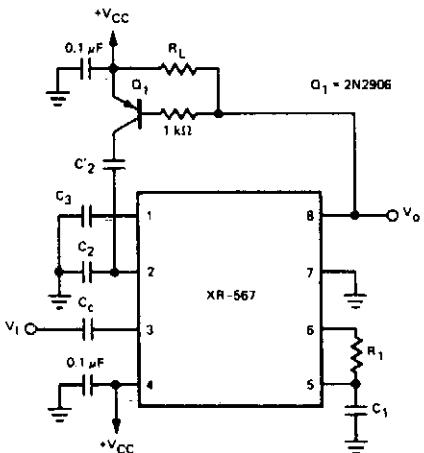

**Fig. 22-5**

## STEREO TV DECODER

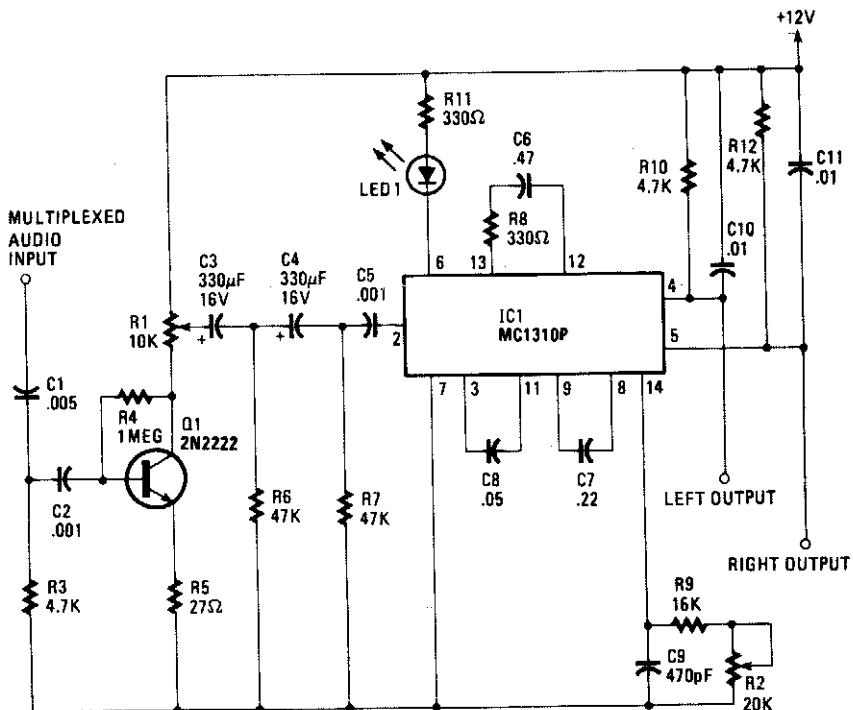


RADIO-ELECTRONICS

**Fig. 22-6**

### Circuit Notes

The composite input signal is preamplified by transistor Q1 and is then coupled to the high-pass filter composed of C3, C4, R6, and R7. The filtered audio is then passed to IC1, an MC1310P "Coilless Stereo Demodulator." That IC is normally used to demodulate broadcast-band FM signals, but by changing the frequency of its on-board VCO (Voltage Controlled Oscillator) slightly (from 19 kHz to 15.734 kHz), we can use that IC to detect stereo-TV signals. A block diagram of the MC1310P is shown in Fig. 22-5. Notice that the components connected to pin 14 control the VCO's frequency, hence the pilot-detect and carrier frequencies. For use in an FM receiver, the VCO would run at four times the 19 kHz pilot frequency (76 kHz), but for our application, it will run at four times the 15.734 kHz pilot frequency of stereo TV, or 62.936 kHz. The MC1310P divides the master VCO signal by two in order to supply the 31.468 kHz carrier that is used to detect the L - R audio signal. The L - R signal undergoes normal FM detection, and at that point we've got two audio signals: L + R and L - R. The decoder block in the IC performs the addition and subtraction to produce the separate left and right signals. R10 and C10 form a de-emphasis network that compensates for the 75  $\mu$ s pre-emphasis that the left channel underwent; R12 and C11 perform the same function for the right channel.
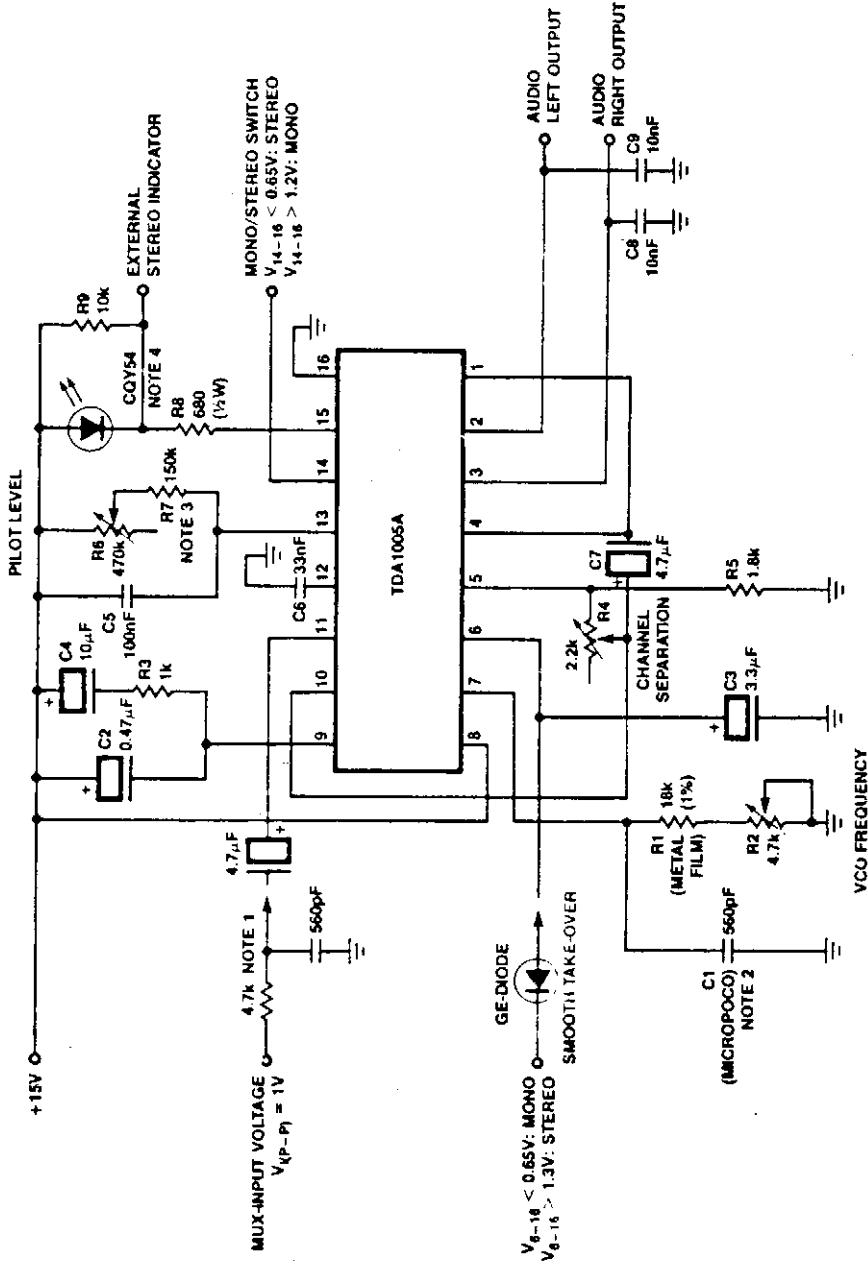
## TIME DIVISION MULTIPLEX (TDM) STEREO DECODER



00-1284


### NOTES:

1. For other input structures see Figures 7 to 11, shown here with RC-filter (Figure 8).
2. Micropoco capacitor has a temperature coefficient of  $125 \cdot 10^{-6} \cdot 10^{-6} \text{C}^{-1}$ .
3. In simplified circuits a fixed resistor (e.g. 620k) can be used for a guaranteed switching level of  $\leq 16\text{mV}$ .
4. Either the LED circuit or an external stereo indicator can be used.

### SIGNETICS

Fig. 22-7

## FREQUENCY DIVISION MULTIPLEX (FDM) STEREO DECODER

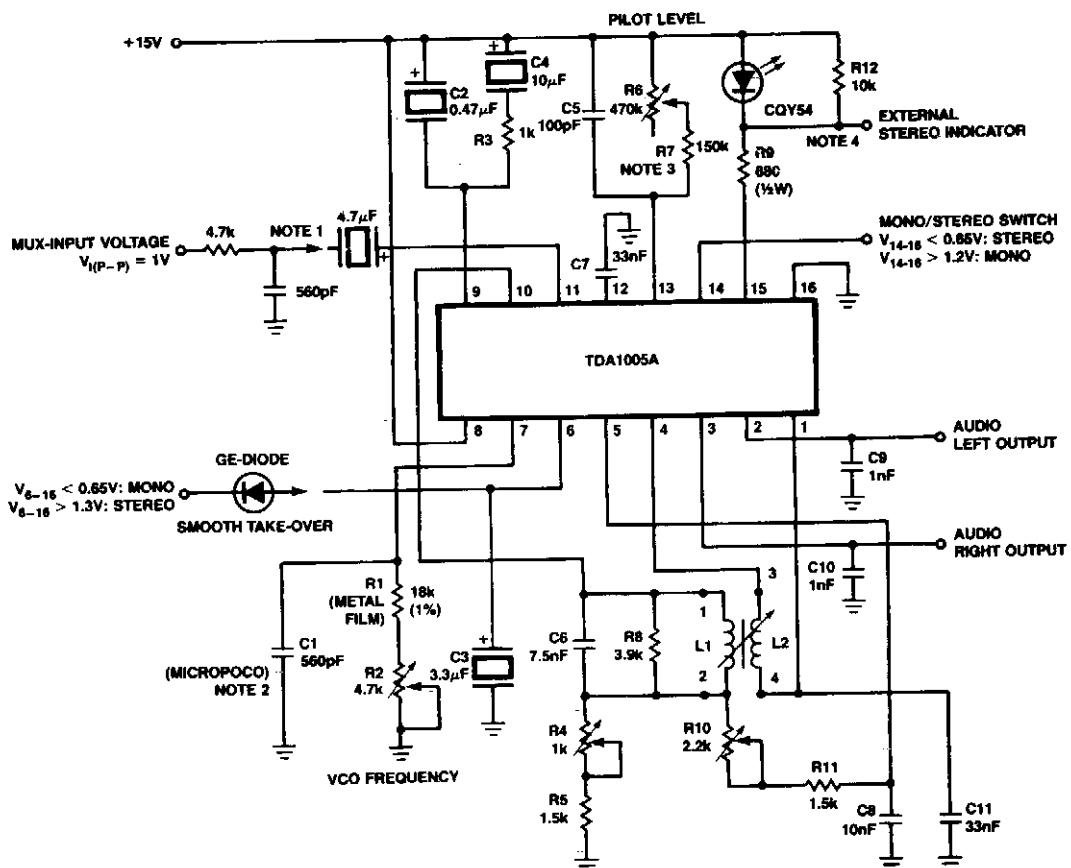

TC128105

### Coil data:

$$L_1, L_2 = 2.6mH$$

$$Q_{1,2} = 35; Q_{MIN} = 30$$

$$N_{1,2} = 357\frac{1}{2} \text{ turns}$$

$$N_{3,4} = 287\frac{1}{2} \text{ turns; scrambled wound with wire diameter } 0.09mm, \frac{E_{3,4}}{E_{1,2}} \times 100\% = 82\%$$


### NOTES:

- For other input structures see Figures 6 to 11; shown here with RC-filter (Figure 8).
- The micropoco capacitor has a temperature coefficient of  $125.10^{-6} \pm 60.10^{-6} \text{ K}^{-1}$ .
- In simplified circuits a fixed resistor (e.g. 620k) can be used for a guaranteed switching level of  $\leq 16mV$ .
- Either the LED circuit or an external stereo indicator can be used.

SIGNETICS

Fig. 22-8

## SCA (Background Music) DECODER

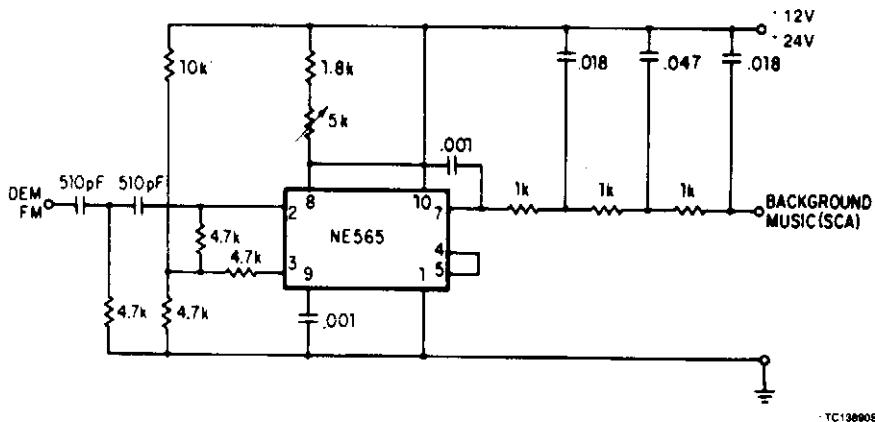

**SIGNETICS**

**Fig. 22-9**

### Circuit Notes

A resistive voltage divider is used to establish a bias voltage for the input (Pins 2 and 3). The demodulated (multiplex) FM signal is fed to the input through a two-stage high-pass filter, both to effect capacitive coupling and to attenuate the strong signal of the regular channel. A total signal amplitude, between 80 mV and 300 mV, is required at the input. Its source should have an impedance of less than 10,000 ohm. The Phase-Locked Loop is tuned to 67 kHz with a 5000 ohm potentiometer, only approximate tuning is required since the loop will seek the signal. The demodulated output (Pin 7) passes through a three-stage low-pass filter to provide de-emphasis and attenuate the high-frequency noise which often accompanies SCA transmission. Note that no capacitor is provided directly at Pin 7; thus, the circuit is operating as a first-order loop. The demodulated output signal is in the order of 50 mV and the frequency response extends to 7 kHz.

# **23**

## **Detectors**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Pulse Sequence Detector
- Voltage Level Detector
- Zero-Crossing Detector
- Peak Detector
- Level Detector
- High Frequency Peak Detector
- Tachometer, Single Pulse Generator, Power Loss  
Detector, Peak Detector
- Phase Detector with 10-Bit Accuracy
- Frequency Limit Detector
- Pulse Coincidence Detector

## PULSE SEQUENCE DETECTOR

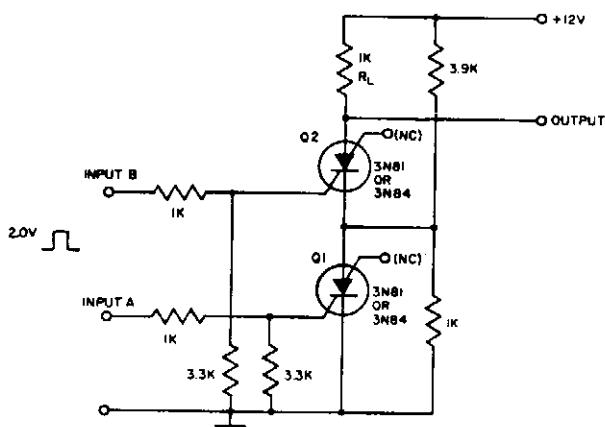


GENERAL ELECTRIC

*Fig. 23-1*

## Circuit Notes

The resistor divider connected between Q1 and Q2 supplies  $I_H$  to Q1 after input A triggers it. It also prevents input B from triggering Q2 until Q1 conducts. Consequently, the first B input pulse after input A is applied will supply current to  $R_L$ .


## VOLTAGE LEVEL DETECTOR

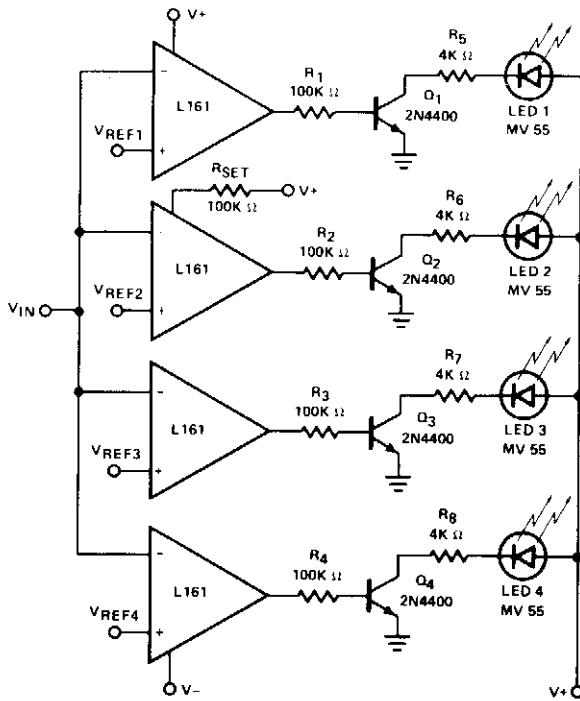

SILICONIX

*Fig. 23-2*

## ZERO-CROSSING DETECTOR

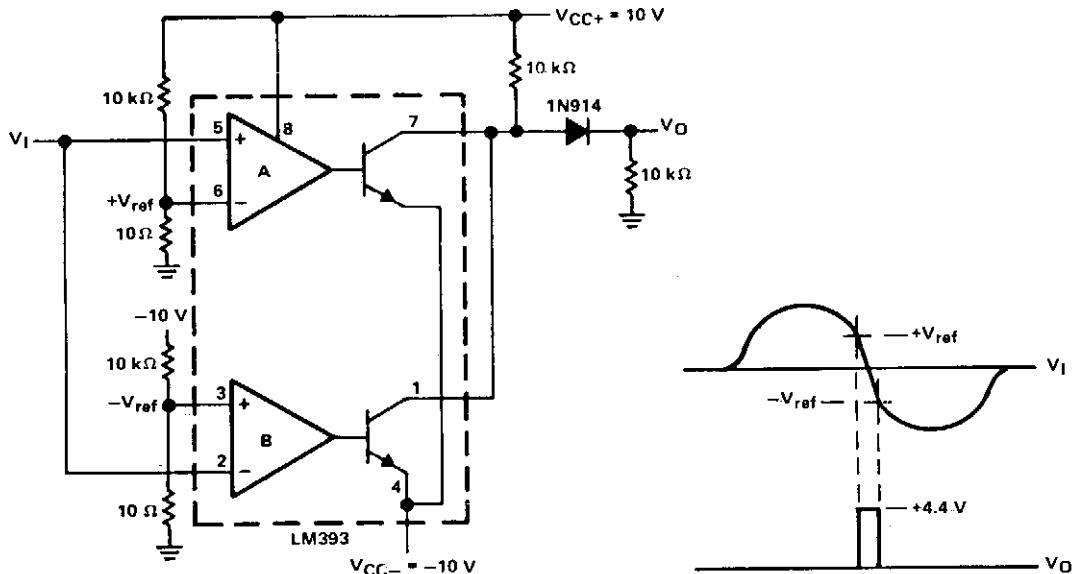

TEXAS INSTRUMENTS



**Fig. 23-3**

### Circuit Notes

This zero-crossing detector uses a dual LM393 comparator, and easily controls hysteresis by the reference levels which are set on the comparator inputs. The circuit illustrated is powered by  $\pm 10\text{-V}$  power supplies. The input signal can be an ac signal level up to  $+8\text{ V}$ . The output will be a positive going pulse of about  $4.4\text{ V}$  at the zero-crossover point. These parameters are compatible with TTL logic levels.

The input signal is simultaneously applied to the non-inverting input of comparator A and the inverting input of comparator B. The inverting input of comparator A has a  $+10\text{ mV}$  reference with respect to ground, while the non-inverting input of comparator B has a  $-10\text{ mV}$  reference with respect to ground. As the input signal swings positive (greater than  $+10\text{ mV}$ ), the output of comparator "A" will be low while comparator "B" will have a high output. When the input signal swings negative (less than  $-10\text{ mV}$ ), the reverse is true. The result of the combined outputs will be low in either case. On the other hand, when the input signal is between the threshold points ( $\pm 10\text{ mV}$  around zero crossover), the output of both comparators will be high. If more hysteresis is needed, the  $\pm 10\text{ mV}$  window may be made wider by increasing the reference voltages.

## PEAK DETECTOR

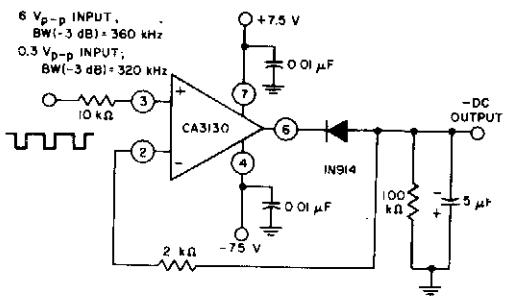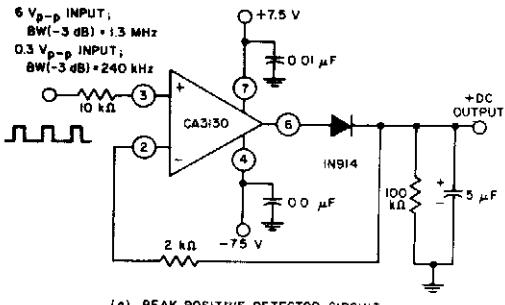


GENERAL ELECTRIC/RCA

Fig. 23-4

## Circuit Notes

Circuits are easily implemented using the CA3130 BiMOS op amp. For large-signal inputs the bandwidth of the peak-negative circuit is less than that of the peak-positive circuit. The second stage of the CA3130 limits bandwidth in this case.

## LEVEL DETECTOR

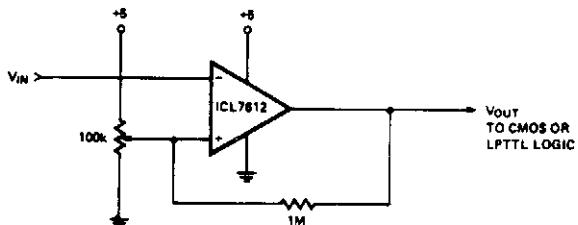

0307-31

INTERSIL

Fig. 23-5

## Circuit Notes

By using the ICL7612 in these applications, the circuits will follow rail to rail inputs.

## HIGH FREQUENCY PEAK DETECTOR


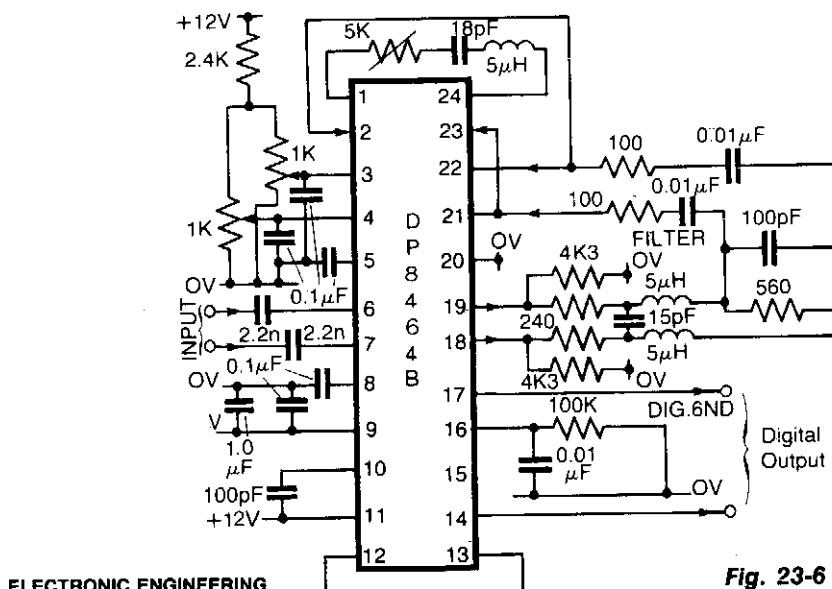


Fig. 23-6

### Circuit Notes

National Semiconductor's DP8464B is primarily intended for use in disk systems as a pulse detector. However it can be easily used as a general purpose peak detector for analogue signals up to 5 MHz. The chip can handle signals between 20 and 66 mV peak-to-peak. The circuit includes a filter with constant group delay characteristics to band limit the signal. Typically the  $-3$  dB point for this filter will be at about 1.5 times the highest frequency of interest. This differentiator network between pins 1 and 24 can be as simple as a capacitor, or can be more complex to band limit the differentiator response.

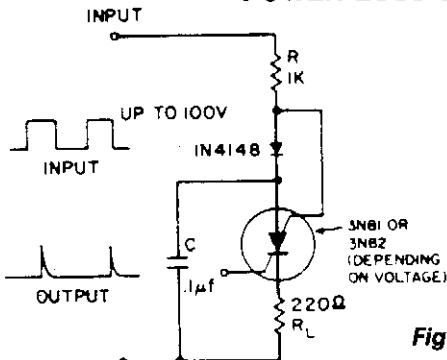
## TACHOMETER, SINGLE PULSE GENERATOR, POWER LOSS DETECTOR, PEAK DETECTOR




A positive going input charges C through the IN4148 and R. The diode keeps the scs off. A negative going input supplies anode-gate current triggering on the scs discharging C through  $R_L$ .

Fig. 23-7

## PHASE DETECTOR WITH 10-BIT ACCURACY

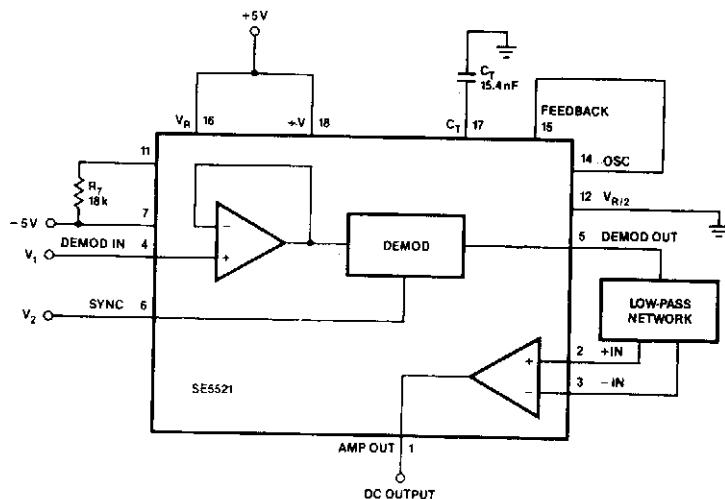


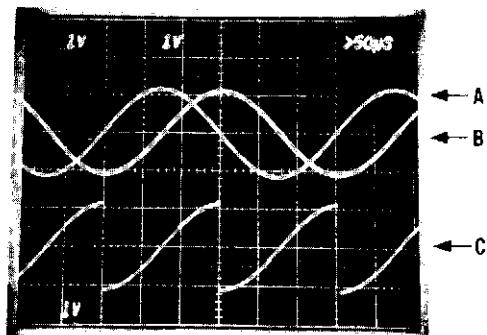a. Phase Detector Measures Phase Difference Between Signals  $V_1$  and  $V_2$  and Provides dc Output at Pin 1



b. When  $V_1$  and  $V_2$  in (a) are at Quadrature (Traces A and B), the DC Component of Demodulator Output (Trace C) is at 0V

SIGNETICS

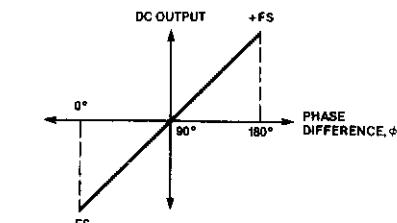



c. The dc Output and Phase Vary Linearly

**Fig. 23-8**

### Circuit Notes

Signals of identical frequency are applied to sync input (Pin 6) and to the demodulator input (Pin 4), respectively, the demodulator functions as a phase detector with output dc component being proportional to phase difference between the two inputs. The signals must be referenced to 0 V for dual supply operation or to  $V_R/2$  for single supply operation. At  $\pm 5\text{-V}$  supplies, the demodulator can easily handle 7-V peak-to-peak signals. The low-pass network configured with the uncommitted amplifier dc output at Pin 1 of the device. The dc output is maximum (+ full-scale) when  $V_1$  and  $V_2$  are  $180^\circ$  out of phase and minimum (- full-scale) when the signals are in phase.

## FREQUENCY LIMIT DETECTOR

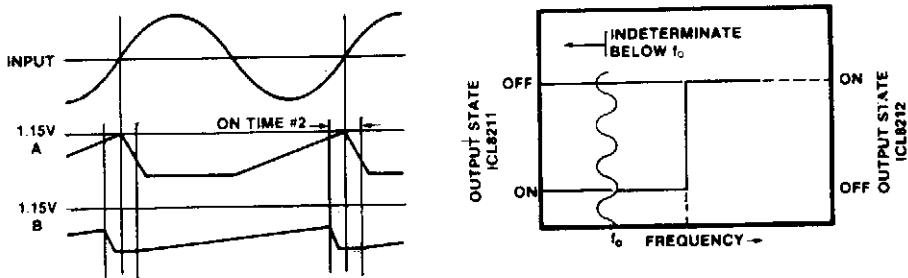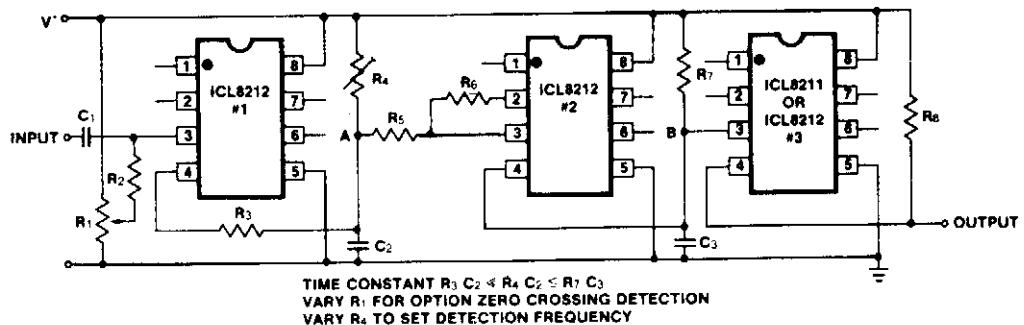

INTERSIL


Fig. 23-9

### Circuit Notes

Simple frequency limit detectors providing a GO/NO-GO output for use with varying amplitude input signals may be conveniently implemented with the ICL8211/8212. In the application shown, the first ICL8212 is used as a zero-crossing detector. The output circuit consisting of  $R_3$ ,  $R_4$  and  $C_2$  results in a slow output positive ramp. The negative range is much faster than the positive range.  $R_5$  and  $R_6$  provide hysteresis so that under all circumstances the second ICL8212 is turned on for sufficient time to discharge  $C_3$ . The time constant of  $R_7C_3$  is much greater than  $R_4C_2$ . Depending upon the desired output polarities for low and high input frequencies, either an ICL8211 or an ICL8212 may be used as the output driver.

The circuit is sensitive to supply voltage variations and should be used with a stabilized power supply. At very low frequencies the output will switch at the input frequency.

## PULSE COINCIDENCE DETECTOR

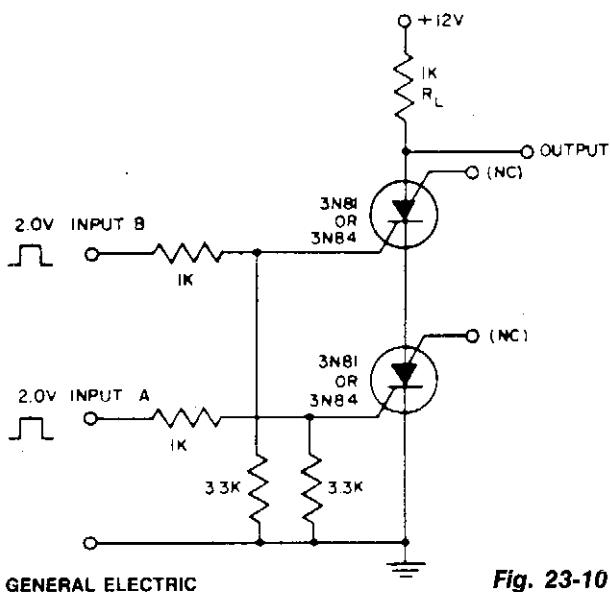

*Fig. 23-10*

### Circuit Notes

Unless inputs A and B (2- to 3-V amplitude) occur simultaneously no voltage exists across  $R_L$ . Less than 1 microsecond overlap is sufficient to trigger the scs. Coincidence of negative inputs is detected with gates  $G_A$  instead of  $G_C$  by using the scs in a complementary SCR configuration.

# **24**

## **Digital-to-Analog Converters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Two 8-Bit DACs Make a 12-Bit DAC  
12-Bit DAC with Variable Step Size

## TWO 8-BIT DACS MAKE A 12-BIT DAC

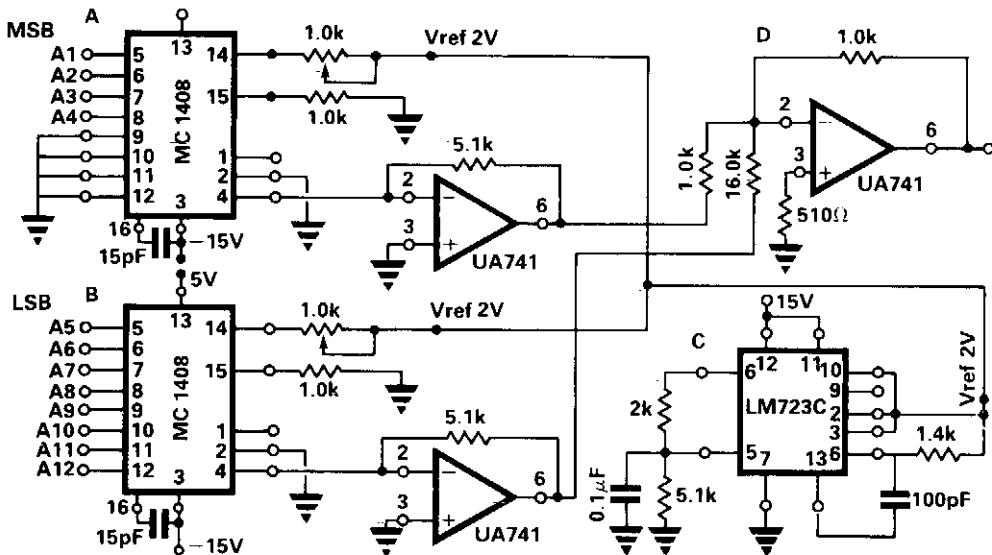

ELECTRONIC ENGINEERING

**Fig. 24-1**

### Circuit Notes

Two MC1408—8-bit D/A converters, A and B in the circuit diagram, are used. The four least-significant bits of A are tied to zero. The four most significant bits of the 12-bit data are connected to the remaining four input pins. The eight least significant bits of the 12-bit data are connected to the eight input pins of B. The four most significant bits of the 12-bit data together have a weight of 16 relative to the remaining eight bits. Hence, the output from B is reduced by a factor of 16 and summed with the output from A using the summing op-amp configuration D. Voltage regulator chip, LM7236, is used to provide an accurate reference voltage, 2 V, for the MC1408. The full-scale voltage of the converter is  $\frac{1}{16} \times 9.9609 + 1 \times (9.375)$  or 9.9976 V. The step size of the converter is 2.4 mV.

## 12-BIT DAC WITH VARIABLE STEP SIZE

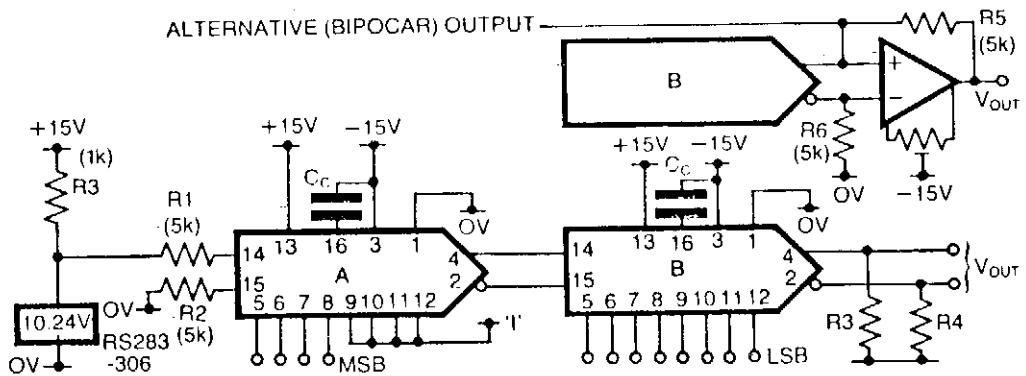


Fig. 24-2

ELECTRONIC ENGINEERING

### Circuit Notes

The step size of the converter is variable by selection of the high order data bits. The first DAC, A, has a stable reference current supplied via the 10.24 V reference IC and R1. R2 provides bias cancellation. As shown, only the first 4 MSB inputs are used, giving a step size of  $225/256 \times 2.048/16 = 0.127$  mA. This current supplies the reference for DAC B whose step size is then  $0.1275/256 = 0.498$   $\mu$ A. Complementary voltage outputs are available for unipolar output and using  $R3 = R4 = 10$  K,  $V_{out}$  is  $\pm 10.2$  V approximately, with a step size (1 LSB) of approximately 5 mV. If desired an op amp can be added to the output to provide a low impedance output with bipolar output symmetrical about ground, if  $R5 = R6$  within 0.05%. Note that offset null is required, and all resistors except R2 and R3 should be 1% high stability types.

By using lower order address lines than illustrated for DAC A, a smaller step size (and therefore full-scale output) can be obtained. Unused high order bits can be manipulated high or low to change the relative position of the full-scale output.

## **25**

# **Dip Meters**


---

---


The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Little Dipper

## LITTLE DIPPER

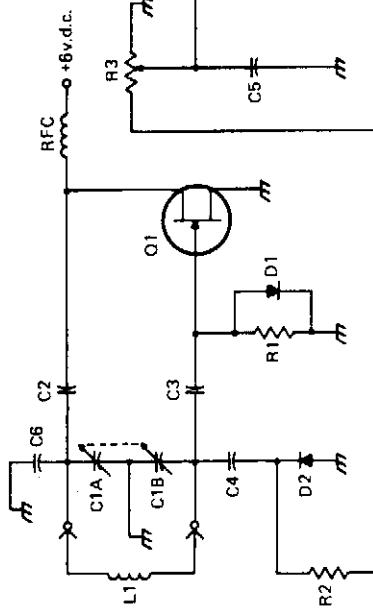

CQ

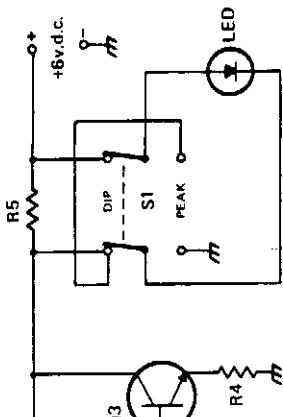

### Parts List

- L1—See coil data.
- C1A,B—Dual capacitor 100 pF per section (ETCO SV409 or similar)
- C2,C3—100 pF mica, mylar, etc., low voltage
- C4—10 pF mica, mylar, etc., low voltage
- C5—.01 UF ceramic, low voltage
- C6—5 pF mica, mylar, etc., low voltage
- D1,D2—1N914 silicon diode or similar
- R1—100 K ohms  $\frac{1}{4}$  watt
- R2—220 K ohms  $\frac{1}{4}$  watt
- R3—500 K ohms potentiometer
- R4—10 ohms  $\frac{1}{4}$  watt
- R5—270 ohms  $\frac{1}{4}$  watt
- Q1—MPF 102 FET
- Q2—Any general-purpose NPN transistor with a Beta (HFE) of 40 or so (2N3904 or similar)
- Q3—Any general-purpose NPN transistor capable of 20 mA collector current or more. Beta 40 or so (2N3904, 2N2222 or similar)
- RFC—1 mH miniature ferrite core choke (value not critical)
- LED—Panel mounting LED Radio Shack 276-068 or similar.
- SW1—Sub-miniature DPDT slide switch or similar
- Miscellaneous—6 volt AC adapter (Radio Shack 273-1454A)
- Coaxial DC power jack (RS 274-156S)
- Calibrated Dial knob (RS 274-413)
- Dual phono jack (RS 274-332)

**Fig. 25-1**

### Circuit Notes

The circuit consists of two basic circuits, the oscillator and the detector. The oscillator uses an FET in a Colpitts configuration. The energy circulating in the oscillator tank is coupled through C4 to the detector circuit, where a small diode (D2) rectifies it, feeding a dc voltage to the Darlington pair (Q2, A3) controlled by the sensitivity control (R3). Any small

variations in the bias of the amplifier will cause large variations of current through the LED indicator in the DIP mode; however, in the PEAK mode the current produces a corresponding voltage drop through R5 and the action of the LED is reversed. The circuit shown will work practically on any frequency from LF to VHF if the appropriate components are used.

# **26**


## **Display Circuits**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Vacuum Fluorescent Display  
Expanded Scale Meter, Dot or Bar  
Low-Cost Bar-Graph Indicator for ac Signals  
LED Bar-Graph Driver

## VACUUM FLUORESCENT DISPLAY

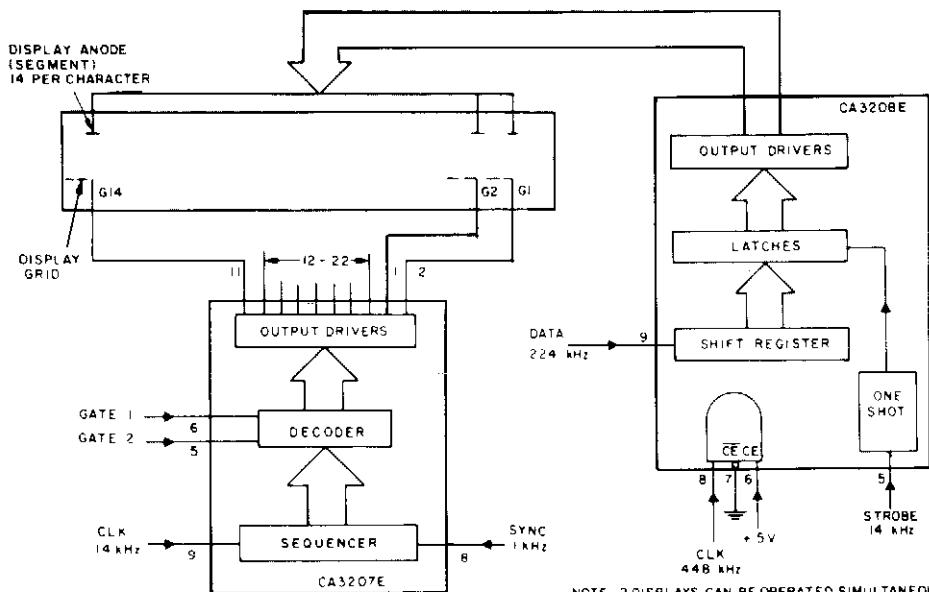


GENERAL ELECTRIC/RCA

Fig. 26-1

This circuit uses the CA3207 sequence driver and CA3208 segment latch-driver in combination to drive display devices of up to 14 segments with up to 14 characters of display. The CA3207 selects the digit or character to be displayed in sequence, CA3208 turns on the required alphanumeric segments.

## EXPANDED SCALE METER, DOT OR BAR

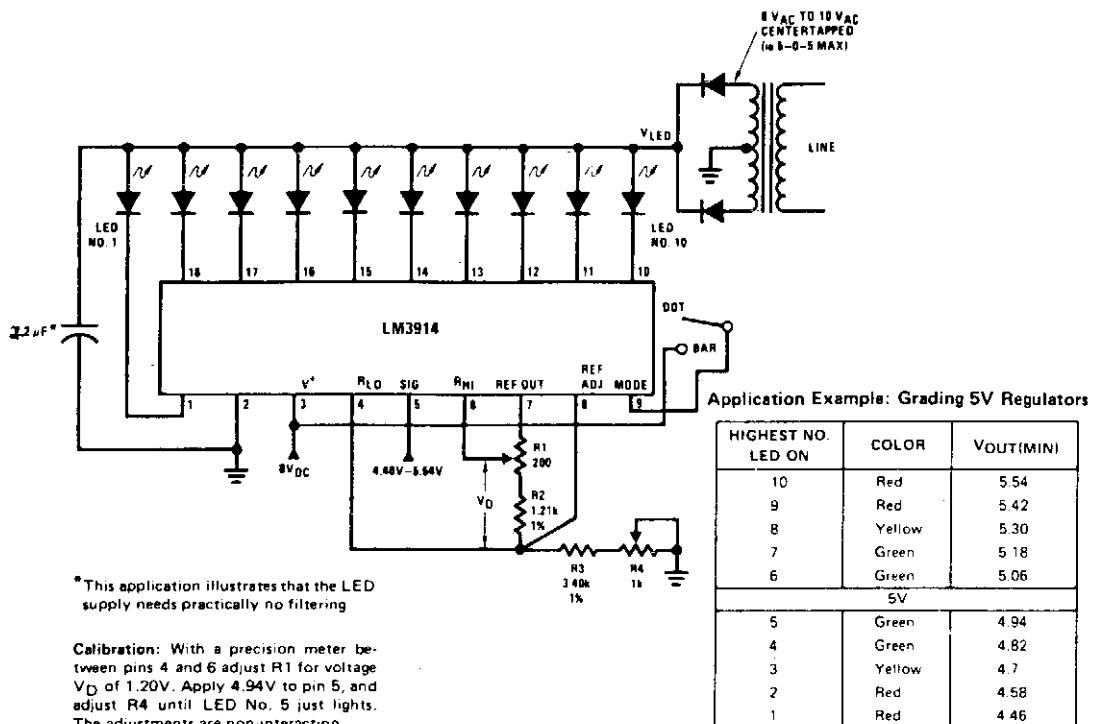


NATIONAL SEMICONDUCTOR CORP.

**Fig. 26-2**

### Circuit Notes

A bar graph driver IC LM314 drives an LED display. The LEDs may be separate or in a combined (integral) bar graph display.
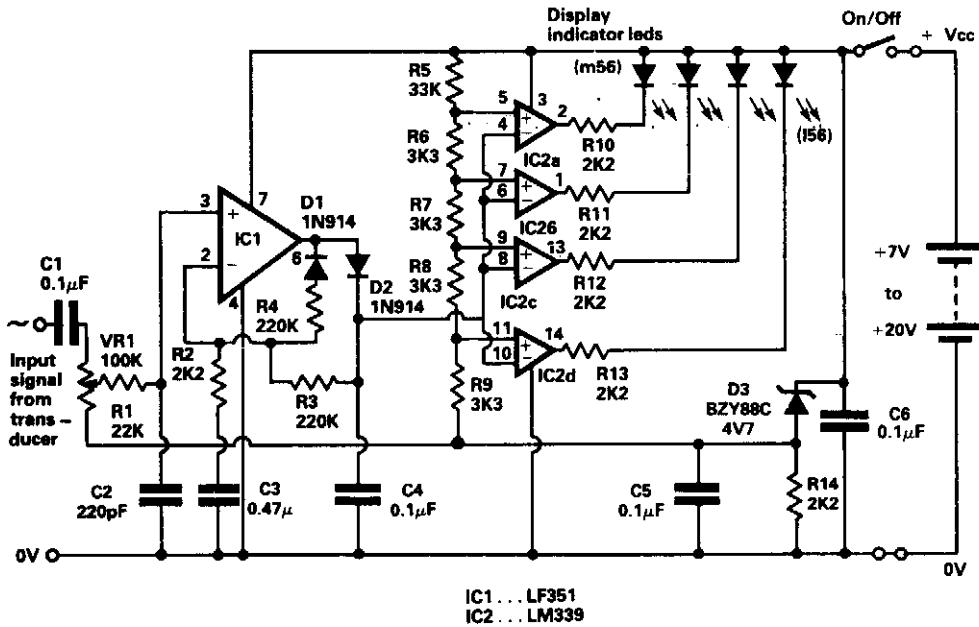
## LOW-COST BAR-GRAF INDICATOR FOR AC SIGNALS




ELECTRONIC ENGINEERING

Fig. 26-3

### Circuit Notes

Indicator was designed for displaying the peak level of small ac signals from a variety of transducers including microphones, strain gauges and photodiodes. The circuit responds to input signals contained within the audio frequency spectrum, i.e., 30 Hz to 20 kHz, although a reduced response extends up to 40 kHz. Maximum sensitivity for the component values shown, with VR1 fully clockwise, is 30 mV peak-to-peak. The indicator can be calibrated by setting VR1 when an appropriate input signal is applied.

## LED BAR-GRAPH DRIVER

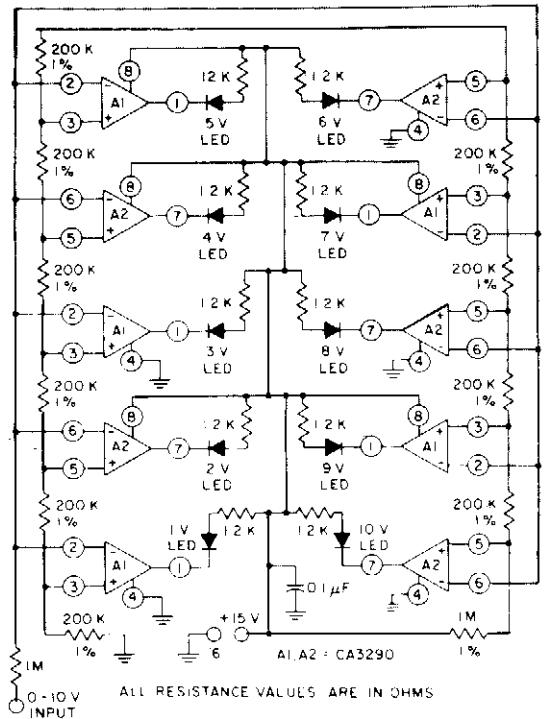

### Circuit Notes

The circuit uses CA3290 BiMOS dual voltage comparators. Non-inverting inputs of A1 and A2 are tied to voltage divider reference. The input signal is applied to the inverting inputs. LEDs are turned "on" when input voltage reaches the voltage on the reference divider.

GENERAL ELECTRIC/RCA

**Fig. 26-4**

# **27**

## **Drive Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source-entry in the Sources section.

- Line Driver Provides Full Rail Excursions
- Five Transistor Amplifier Boosts Fast Pulses into  
50-Ohm Coaxial Cable
- 50-Ohm Transmission Line Driver
- 600-Ohm Balanced Driver for Line Signals
- High Output 600-Ohm Line Driver
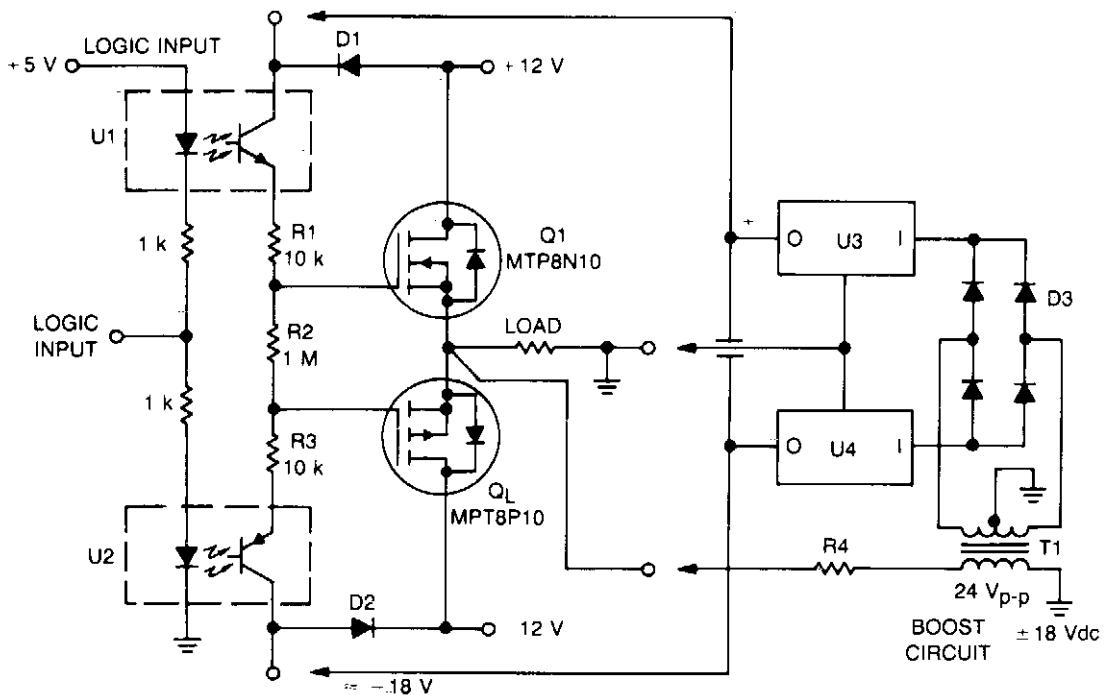
## LINE DRIVER PROVIDES FULL RAIL EXCURSIONS



MOTOROLA


Fig. 27-1

### Circuit Notes

The logic input is applied to opto-isolators U1 and U2 with, respectively, npn and pnp emitter follower outputs. Dc balance is adjusted by potentiometer R2. The emitter followers drive the gates of Q1 and Q2, the complementary TMOS pairs. With a ±12 V supply, the swing at the common source output point is about 12 V peak-to-peak.

By adding a ±18-V boost circuit, as shown, the output swing can approach the rail swing. This circuit applies the output to transformer T1, which is rectified by diode bridge D3, regulated by U3 and U4, and then applied to the collectors of U1 and U2. Diodes D1 and D2 are forward-biased when 12-V supplies are used, but they are back-biased when the 18-V boost is used.
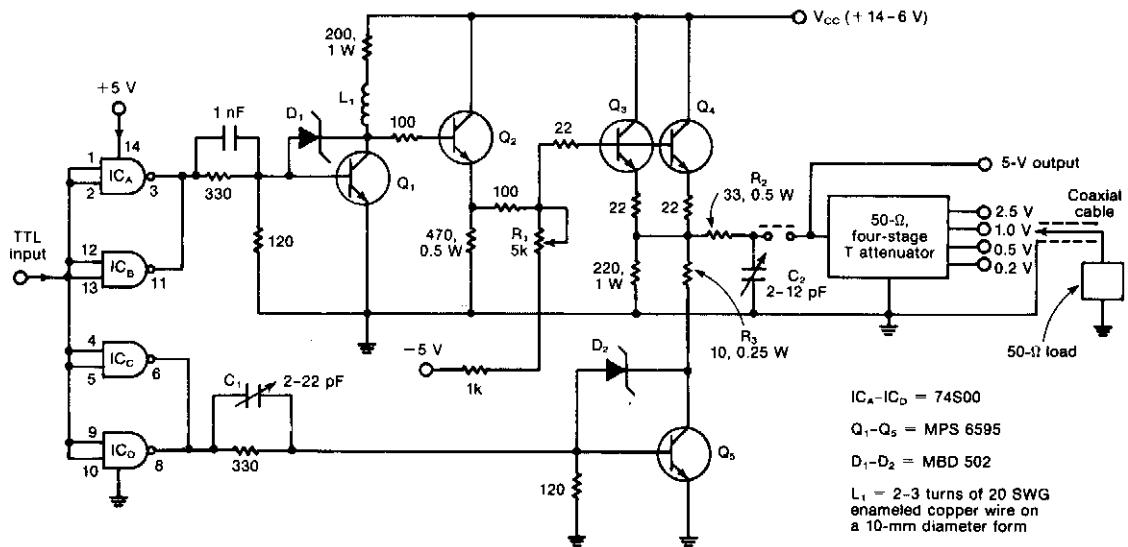
## FIVE-TRANSISTOR AMPLIFIER BOOSTS FAST PULSES INTO 50-OHM COAXIAL CABLE



ELECTRONIC DESIGN

**Fig. 27-2**

### Circuit Notes

The circuit works from dc to 50 MHz and will deliver pulses as short as 10 ns. It is driven by a TTL signal through a 740S00 quad Schottky NAND gate, IC<sub>A</sub> through IC<sub>D</sub>. Transistor Q<sub>1</sub>, wired as a common-emitter amplifier, drives transistor Q<sub>2</sub>, a simple emitter follower. Transistors Q<sub>3</sub> and Q<sub>4</sub>, wired in parallel, also form an emitter follower and drive the output. When Q<sub>3</sub> and Q<sub>4</sub> are both turned off, transistor Q<sub>5</sub> works as a low-impedance sink. Schottky diodes D<sub>1</sub> and D<sub>2</sub> prevent Q<sub>1</sub> and Q<sub>5</sub> from becoming saturated. To adjust the circuit, potentiometer R<sub>1</sub> is set to optimize the output pulse's fall time. Inductor L<sub>1</sub>, a peaking coil, should be adjusted to improve the rise time to within a permissible 5% overshoot. Likewise, capacitor C<sub>1</sub> can be varied to control preshoot. Further output pulse shaping is accomplished with the help of capacitor C<sub>2</sub>. Resistors R<sub>2</sub> and R<sub>3</sub> ensure a proper 50-ohm impedance at the amplifier's output when the pulse is on or off, respectively.

## 50-OHM TRANSMISSION LINE DRIVER


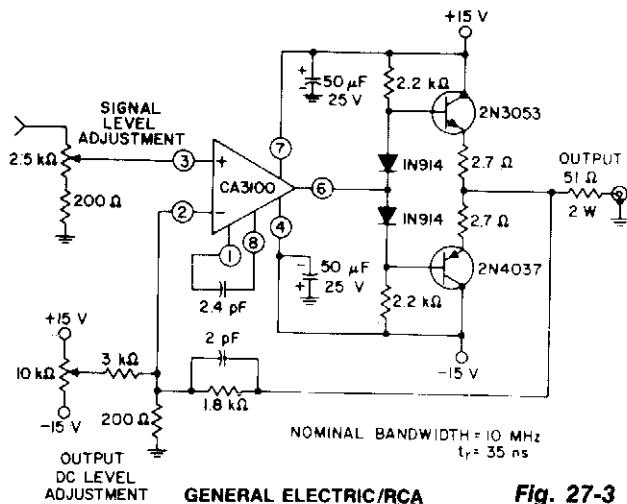


Fig. 27-3

### Circuit Notes

This circuit uses a wideband, high slew rate CA3100 BiMOS op amp. The slew rate for this amplifier is 28 V/μs. Output swing is 9 volts peak-to-peak into a terminated line, measured at the termination.
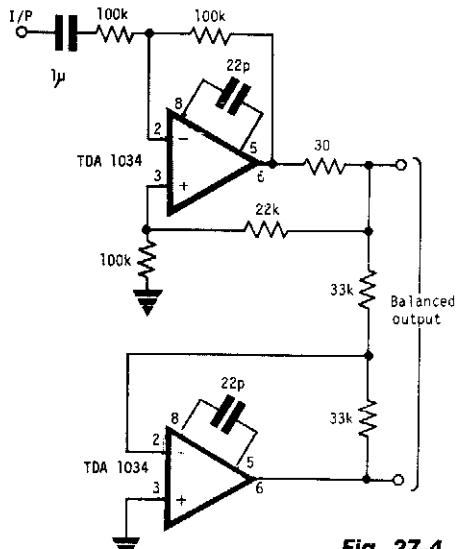
## 600-OHM BALANCED DRIVER FOR LINE SIGNALS




### Circuit Notes

This circuit uses current and voltage feedback. This circuit will handle +24 dBm with ±12 volts supply using TDA 1034s.

Fig. 27-4

ELECTRONIC ENGINEERING

## HIGH OUTPUT 600-OHM LINE DRIVER

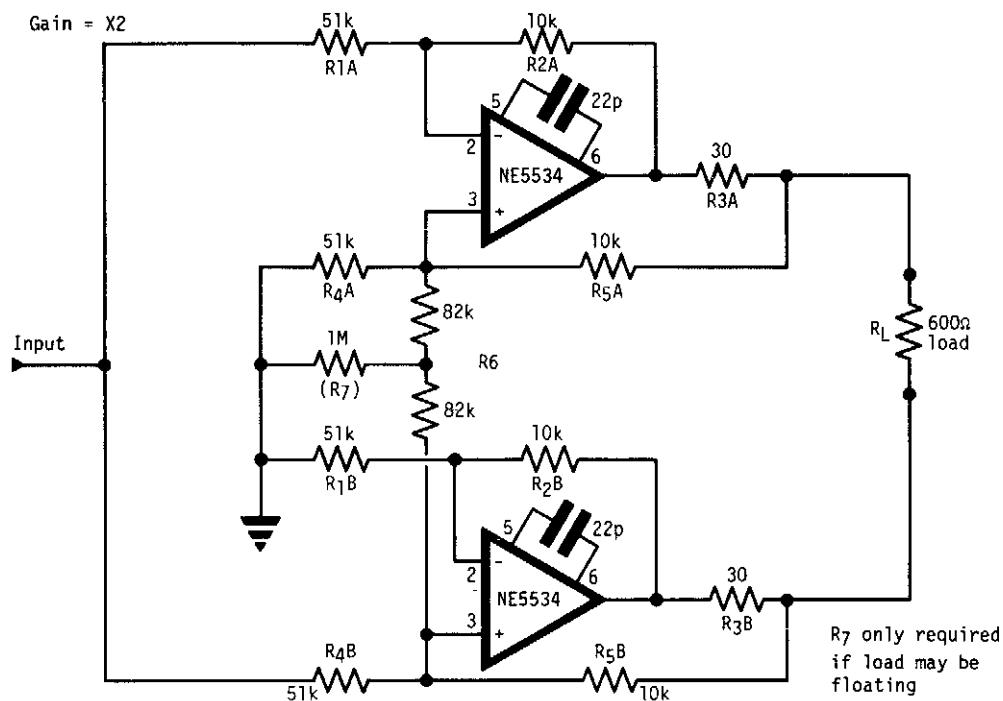

ELECTRONIC ENGINEERING

Fig. 27-5

### Circuit Notes

The circuit has a "floating" output, i.e., it behaves like an isolated transformer winding, with the output amplitude remaining unchanged whether the center or either end of the load is grounded. This is achieved by making Z-out, common mode, infinite. The circuit consists of two current-sources in push-pull. Since each has infinite output Z, the common mode output impedance is also infinite. Connecting a resistor between the non-inverting terminals of the op amps reduces the differential Z-out without affecting the Z-common-mode. Since the output is floating, if the load is also floating there is no output ground reference, which results in malfunction. This can be corrected by reducing the common-mode Z slightly.  $R_7$  fulfills this function. All resistors should be of close tolerance to give a good balance. The line driver provides +24 dB from  $\pm 12$  V or +16 dB from  $\pm 6$  V supplies.

# **28**

## **Electronic Locks**

---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Three-Dial Combination Lock  
Electronic Combination Lock

## THREE-DIAL COMBINATION LOCK

C1—500- $\mu$ F, 25-VDC electrolytic capacitor

D1, D2—1N4002 diode

K1—relay with 6-volt coil rated @ 250-ohms, with SPST contacts


Q1—2N5050 SCR

R1, R2—4,700-ohm, 1/2-watt resistor, 5%

S1, S2, S3—single pole, 10-position rotary or thumbwheel switches

S4—normally closed SPST pushbutton switch

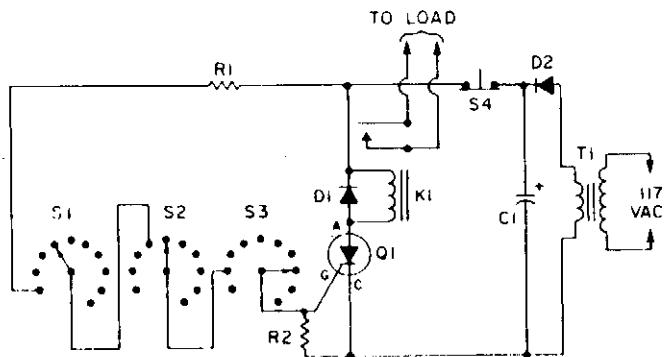T1—120-VAC to 6.3-VAC @ 300mA power transformer




TAB BOOKS, INC.

Fig. 28-1

### Circuit Notes

Here's an effective little combination lock that you can put together in one evening's time. To open the lock, simply dial in the correct combination on the three rotary or thumbwheel switches. With the correct combination entered, current flows through R1 into Q1's gate terminal, causing the SCR to latch in a conductive state. This sends a current through relay K1, which responds by closing its contacts and actuating whatever load is attached. After opening the lock, twirl the dials of S1 through S3 away from the correct combination so that nobody gets a look at it. The lock will remain open and your load will remain on because the SCR is latched on. To lock things up, it's only necessary to interrupt the flow of anode current through the SCR by pressing pushbutton S4.

## ELECTRONIC COMBINATION LOCK

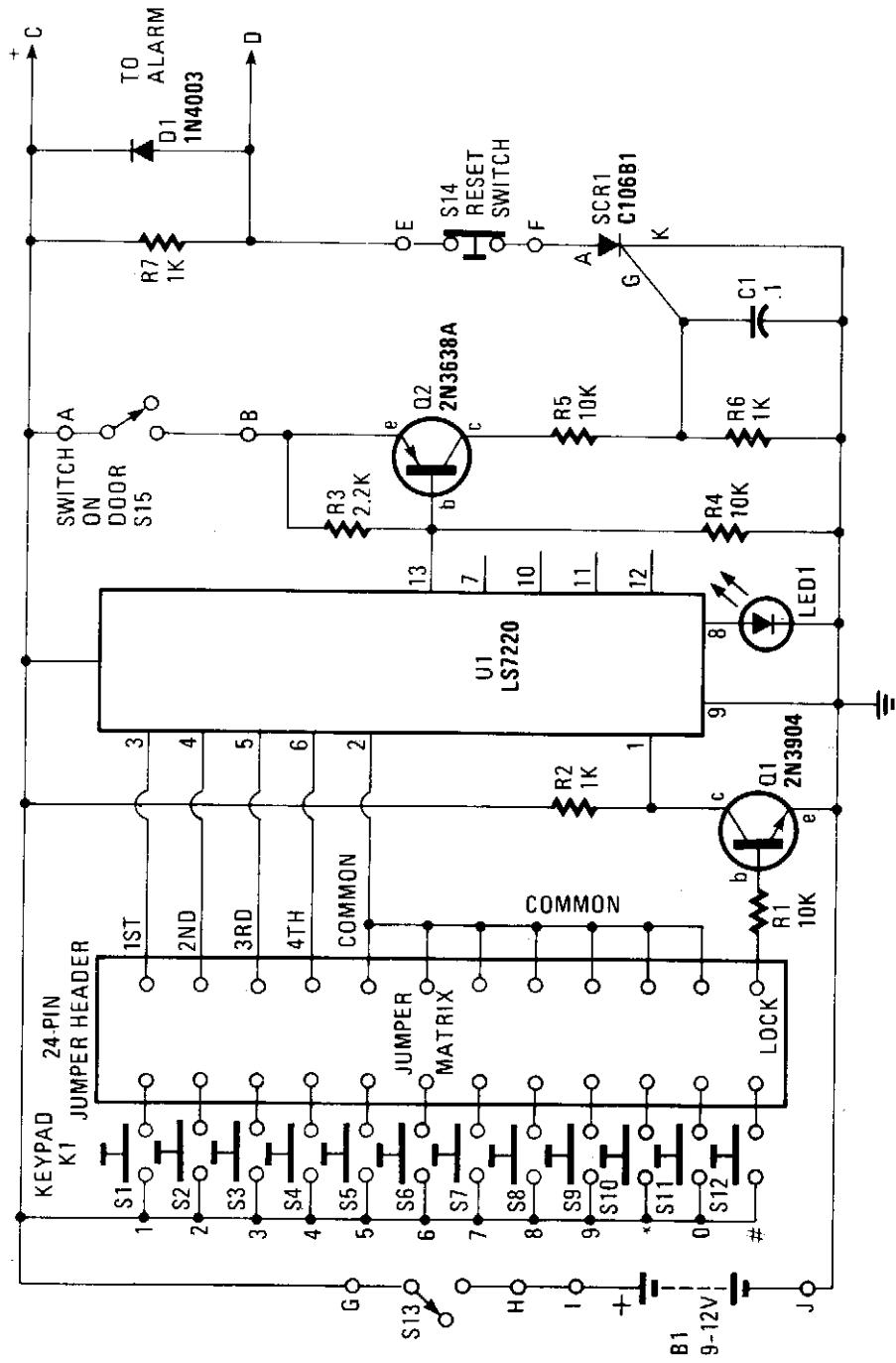

HANDS-ON ELECTRONICS

Fig. 28-2

### Circuit Notes

When button S12 (#) is pressed, a positive voltage fed through R1 appears at the base of transistor Q1, turning it on. When Q1 is conducting, pin 1 of U1 is brought to ground (low) or the battery's negative terminal. With pin 1 low, two things occur: Pin 8 of U1 goes high (+ 9 volts dc), turning on LED 1—indicating that the circuit has been armed—and pin 13 goes from high to low. Transistor Q2 requires a low signal or negative voltage on its base in order to conduct. It also needs a positive voltage on its emitter and a negative voltage on the collector. As long as the door switch (S15) remains open (with the door itself closed), Q2's emitter will not receive the necessary positive voltage. If, however, an unauthorized person opens the door, thus closing switch S15 and placing a positive voltage on the emitter of Q1, the following sequence occurs:

1. Transistor Q2 conducts, receiving the necessary biasing current through a current-divider network consisting of resistors R3 and R4.
2. As Q2 conducts, a voltage drop is developed across the voltage dividers made up of resistors R5 and R6. With R5 at 10,000 ohms and R6 at 1000 ohms, approximately one volt appears at the gate of SCR1. That's enough voltage to trigger the SCR's gate.

## **29**

# **Emulator Circuits**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Simulated Inductor  
Resistor Multiplier  
Capacitor Multiplier  
JFET ac Coupled Integrator

## SIMULATED INDUCTOR

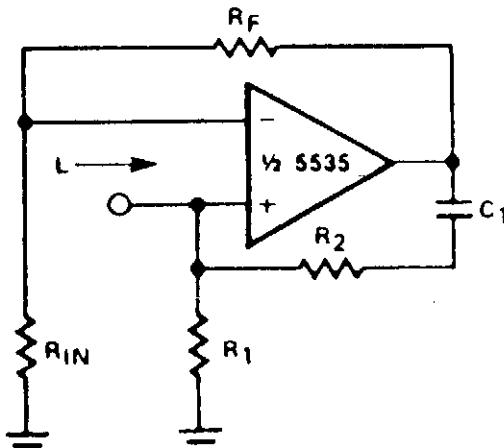


SIGNETICS

Fig. 29-1

## Circuit Notes

With a constant current excitation, the voltage dropped across an inductance increases with frequency. Thus, an active device whose output increases with frequency can be characterized as an inductance. The circuit yields such a response with the effective inductance being equal to:  $L = R_1 R_2 C$ . The Q of this inductance depends upon  $R_1$  being equal to  $R_2$ . At the same time, however, the positive and negative feedback paths of the amplifier are equal leading to the distinct possibility of instability at high frequencies.  $R_1$  should therefore always be slightly smaller than  $R_2$  to assure stable operation.


## RESISTOR MULTIPLIER

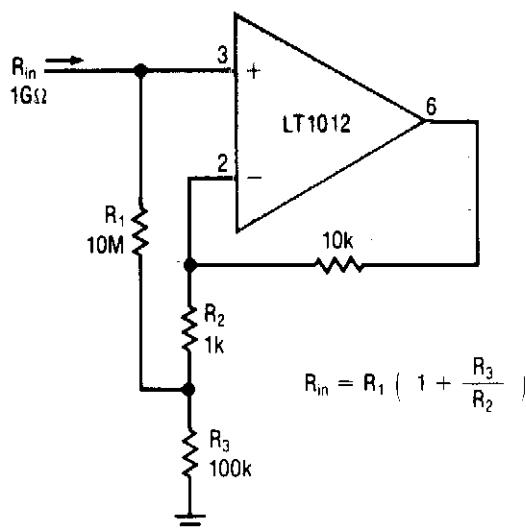

LINEAR TECHNOLOGY CORP.

Fig. 29-2

## CAPACITANCE MULTIPLIER

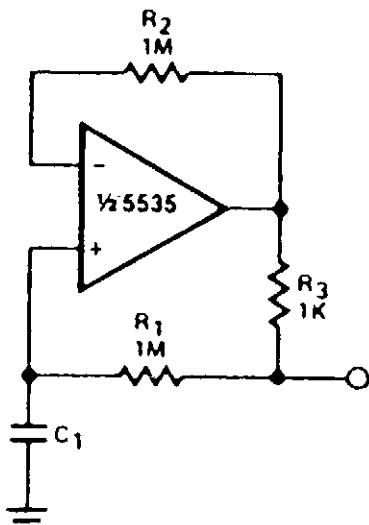

TC10620S

### NOTE:

All resistor values are in ohms.


SIGNETICS

Fig. 29-3

### Circuit Notes

The circuit can be used to simulate large capacitances using small value components. With the values shown and  $C = 10 \mu\text{F}$ , an effective capacitance of  $10,000 \mu\text{F}$  was obtained. The Q available is limited by the effective series resistance. So R1 should be as large as practical.

## JFET ac COUPLED INTEGRATOR

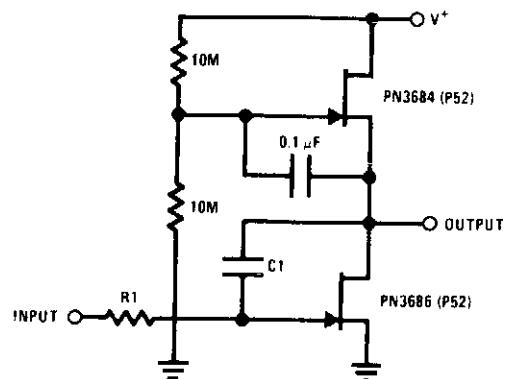

### Circuit Notes

This circuit utilizes the “ $\mu$ -amp” technique to achieve very high voltage gain. Using C1 in the circuit as a Miller integrator, or capacitance multiplier, allows this simple circuit to handle very long time constants.

NATIONAL SEMICONDUCTOR CORP.

Fig. 29-4

# **30**

## **Fence Chargers**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Battery-Powered Fence Charger  
Solid-State Electric Fence Charger  
Electric Fence Charger

## BATTERY-POWERED FENCE CHARGER

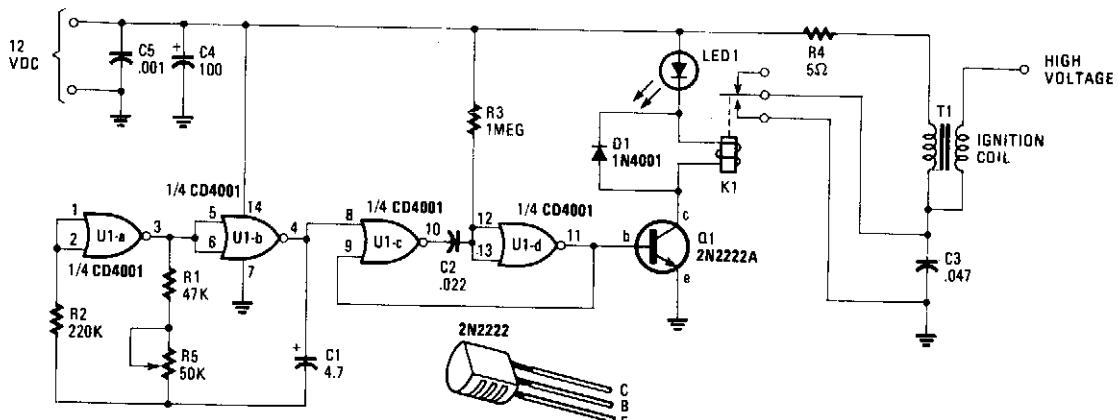


HANDS-ON ELECTRONICS

**Fig. 30-1**

### Circuit Notes

In essence, the circuit is nothing more than an auto ignition coil and a set of points which accomplishes the same thing. A pulsing circuit made from a single CMOS NOR integrated circuit (U1), opens and closes the relay contacts to simulate the action of the original breaker points. The relay pulser is divided into two clocking functions. The first circuit is a free-running squarewave generator that determines the rate or frequency of the pulses that activate the relay. It is essentially a pair of NOR gates connected as inverters and placed in a feedback loop, they are U1-b. The oscillating period of the feedback loop is determined by timing components C1, R1, and variable resistor R5.

## ELECTRIC FENCE CHARGER

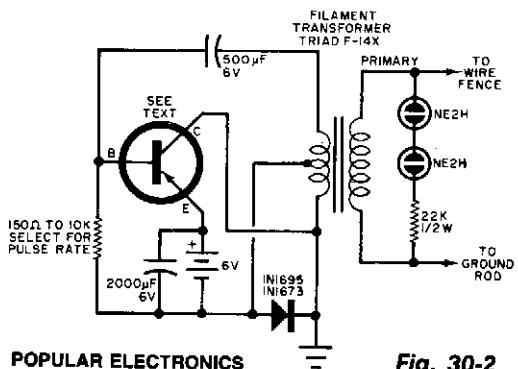


POPULAR ELECTRONICS

**Fig. 30-2**

### Circuit Notes

Any good power transistor can be used in this circuit. The base resistor should be adjusted to obtain a pulse rate of about 50 pulses per minute. The range of values shown can go from 10 pulses to 100 pulses per minute. The single fence wire must be insulated at each supporting pole and should be mounted low enough to prevent an animal from crawling under the wire. The two neon lamps indicate when the unit is operating.

## SOLID-STATE ELECTRIC FENCE CHARGER

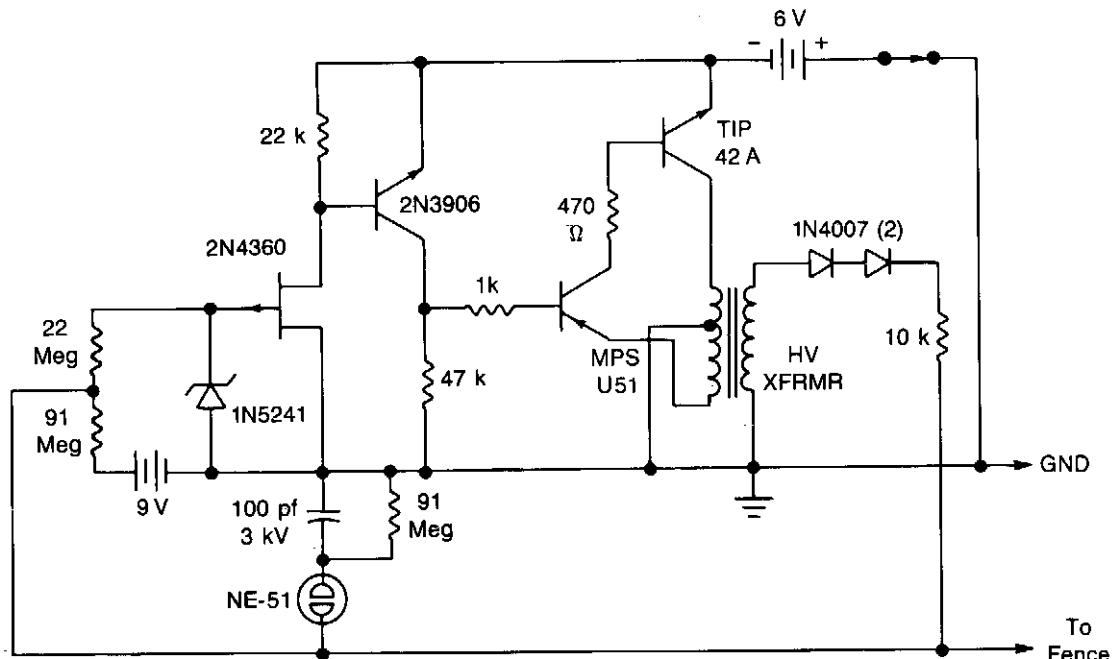

WILLIAM SHEETS

**Fig. 30-3**

### Circuit Notes

A touch-sensing circuit keeps the high-voltage generator cut off until something touches the fence wire. Contact with the fence sensing circuit wire starts the high-voltage generator which applies a series of 500 microsecond pulses at approximately 300 volts to the fence wire. Pulse repetition rate is determined by the intruder's resistance to earth ground. The lower the resistance, the higher the pulse rate. A ground rod is inserted several inches into the ground near the fence wire. In the sensing mode the neon lamp should not flicker or light. If it does, it indicates leakage between the fence wire and ground. If sensitivity is too great, it can be reduced by changing the 91 Meg resistor to 47 or 22 Meg as required.

# **31**

## **Fiberoptics Circuits**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Fiberoptic Interface  
10 MHz Fiberoptic Receiver  
DC Variable Speed Motor Control via Fiberoptics

## 10 MHz FIBEROPTIC RECEIVER

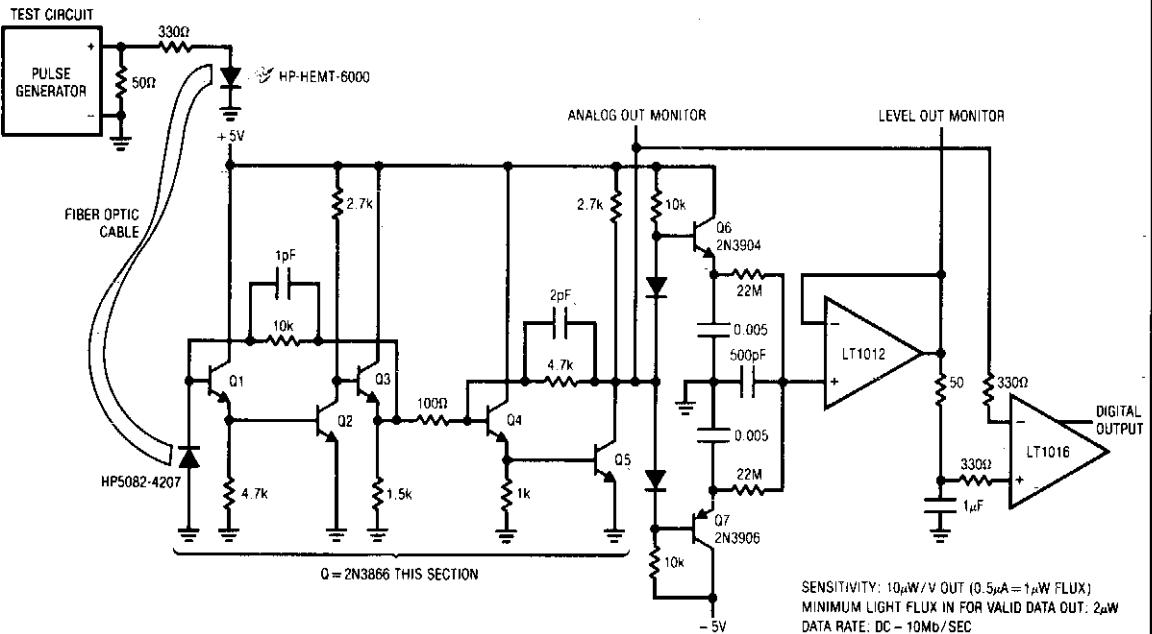


LINEAR TECHNOLOGY CORPORATION

Fig. 31-1

### Circuit Notes

The receiver will accurately condition a wide range of light inputs at up to 10 MHz data rates. The optical signal is detected by the PIN photodiode and amplified by a broadband feed-back stage, Q1-Q3. A second, similar, stage gives further amplification. The output of this stage (Q5's collector) biases a 2-way peak detector (Q6-Q7). The maximum peak is stored in Q6's emitter capacitor while the minimum excursion is retained in Q7's emitter capacitor. The dc value of Q5's output signal's mid-point appears at the junction of the  $0.005\ \mu\text{F}$  capacitor and the  $22\ \text{M}\ \Omega$  unit. This point will always sit midway between the signal's excursions, regardless of absolute amplitude. This signal-adaptive voltage is buffered by the low bias LT1012 to set the trigger voltage at the LT1016's positive input. The LT1016's negative input is biased directly from Q5's collector.
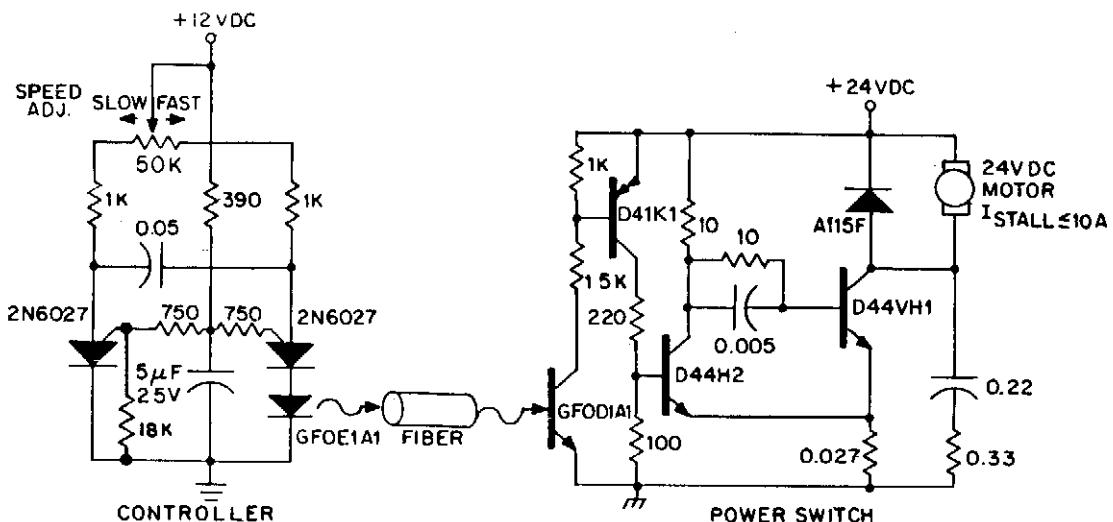
## DC VARIABLE SPEED MOTOR CONTROL VIA FIBEROPTICS




GENERAL ELECTRIC

Fig. 31-2

### Circuit Notes

Dc power can also be controlled via fiber optics. The circuit provides an insulated speed control path for a small dc actuator motor ( $\leq \frac{1}{12}$  hp). Control logic is a self-contained module requiring about 300 mW at 12 V, which can be battery powered. The control module furnishes infrared pulses, at a rate of 160 Hz, with a duty cycle determined by the position of the speed adjust potentiometer. The programmable unijunction multivibrator provides approximately 10 mA pulses to the GFOE1A1 at duty cycles adjustable over a range of 1% to 99%. The infrared pulses are detected by the GFOD1A1, amplified by the D39C1 pnp Darlington, and supplied to the power drive switch, which is connected in a Schmitt trigger configuration to supply the motor voltage pulses during the infrared pulses. Thus, the motor's average supply voltage is pulse width modulated to the desired speed, while its current is maintained between pulses by the A115F free-wheeling diode. The snubber network connected in parallel with the power switch minimizes peak power dissipation in the output transistor, and enhancing reliability. Larger hp motors can be driven by adding another stage of current gain, while longer fiber range lengths can be obtained with an amplifier transistor driving the GFOE1A1.

## FIBEROPTIC INTERFACE

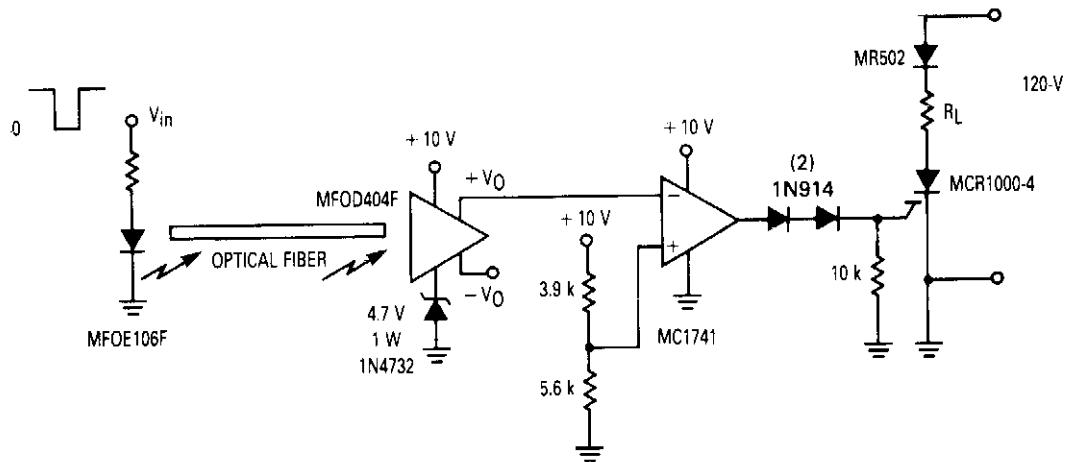

MOTOROLA

Fig. 31-3

### Circuit Notes

An op amp is used to interface between a fiberoptic system and the MOS SCR to multi-cycle, half-wave control of a load. This receiver has two complementary outputs, one at a quiescent level of about 0.6 V and the second at 3 V. By adding a 4.7 V zener in series with the return bus, the effective  $V_{CC}$  becomes 5.3 V and also the 0.6 V output level is translated up to about 5.3 V. This level is compatible with the reference input (5.9 V) of the single-ended powered op-amp acting as a comparator.

## **32**

# **Field Strength Meters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Field Strength Meter  
Field Strength Meter II  
RF Sniffer  
High Sensitivity Field Strength Meter  
Transmission Indicator  
LF or HF Field Strength Meter

## FIELD-STRENGTH METER

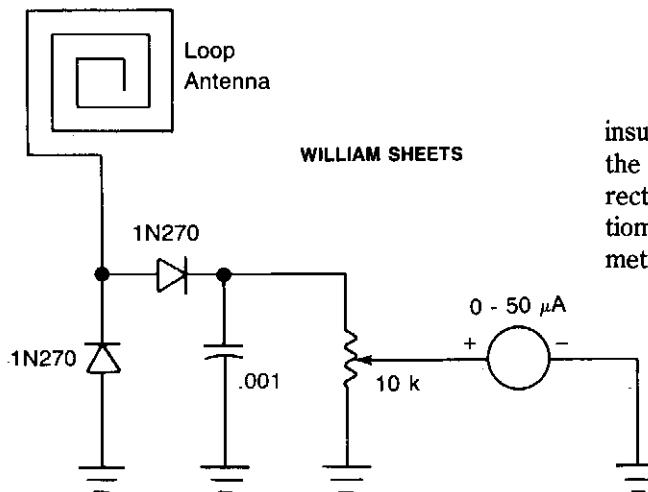


### Circuit Notes

The antenna consists of about 20 cm of insulated stranded wire glued or taped around the inside of a small plastic box. RF current is rectified by two diodes, and a 10 k potentiometer provides variable attenuation for the meter.

*Fig. 32-1*

## FIELD-STRENGTH METER II

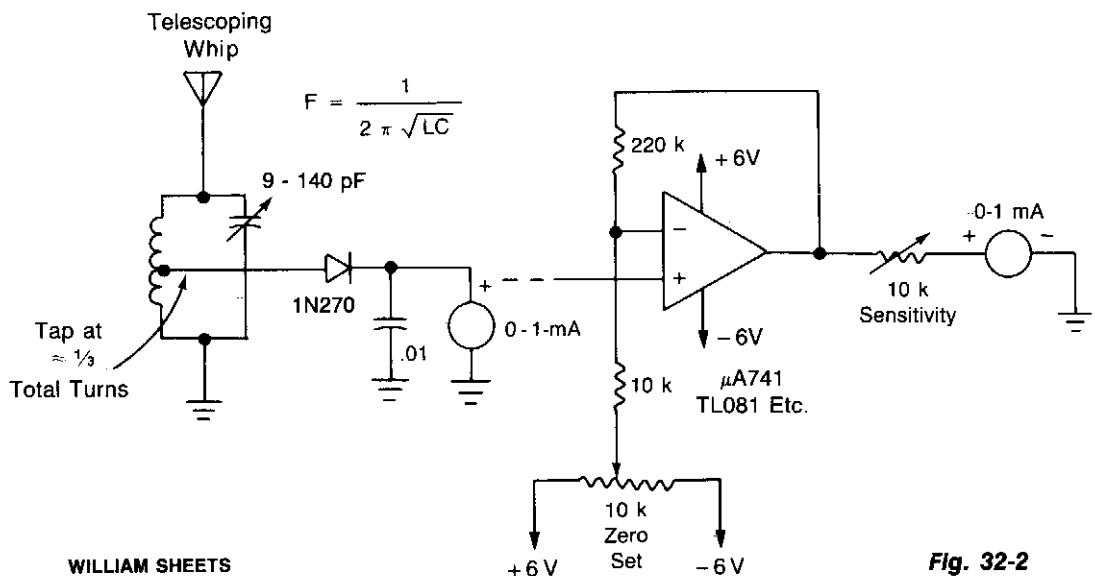


*Fig. 32-2*
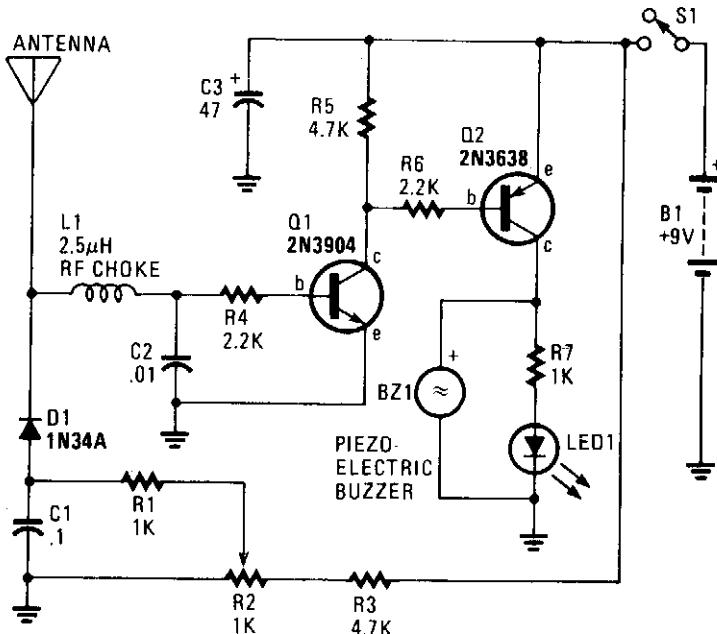
### Circuit Notes

"Minimum-parts" field-strength meter is shown here. For more distant testing, add the dc amplifier.

## RF SNIFFER



HANDS-ON ELECTRONICS

*Fig. 32-3*

### Circuit Notes

This circuit responds to RF signals from below the standard broadcast band to well over 500 MHz, and provides a visual and audible indication when a signal is received. The circuit is designed to receive low-powered signals as well as strong sources of energy by adjusting the bias on the pick-up diode, D1, with R2. A very sensitive setting can be obtained by carefully adjusting R2 until the LED just begins to light and a faint sound is produced by the Piezo sounder.

## HIGH-SENSITIVITY FIELD STRENGTH METER


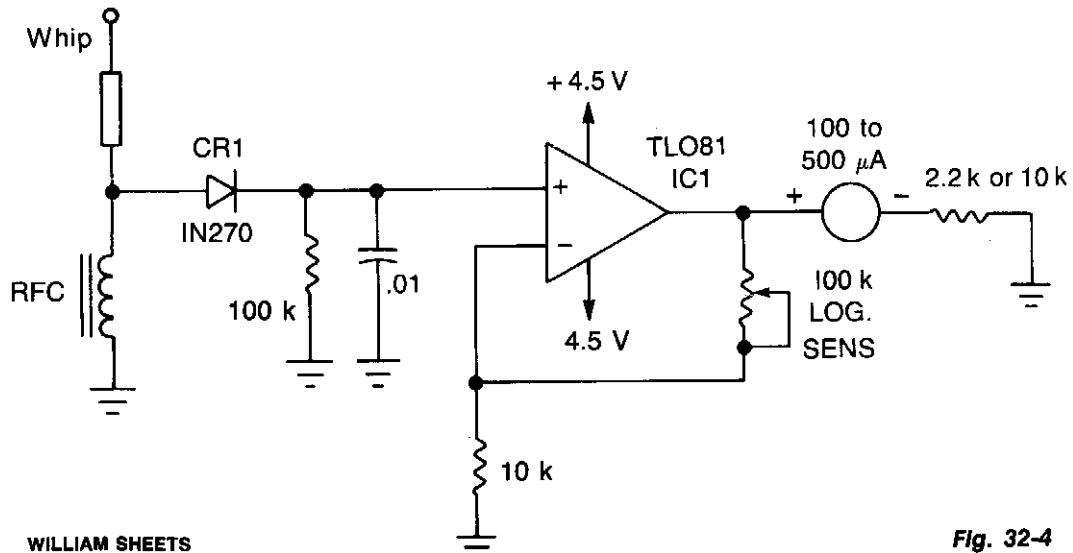


Fig. 32-4

### Circuit Notes

A TL081 (IC1 op amp is used to increase sensitivity. RF signal is detected by CR1 and is then amplified by IC1. Full-scale sensitivity is set with the 100 K potentiometer.

## TRANSMISSION INDICATOR

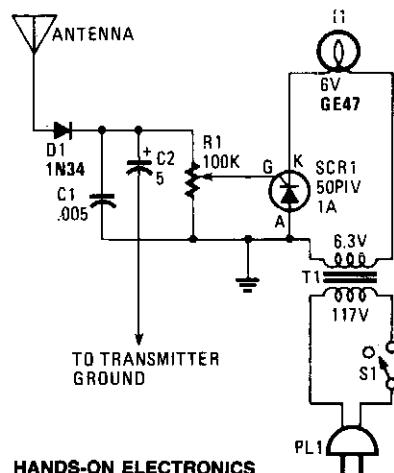

### Circuit Notes

Everytime the push-to-talk button is closed the light will go on. The antenna samples the output RF from the transmitter. That signal is then rectified (detected) by germanium diode D1, and used to charge capacitor C2. The dc output is used to trigger a small silicon-controlled rectifier (SCR1), which permits the current to flow through the small pilot lamp. For lower-power applications, such as CB radio, the antenna will have to be close-coupled to the antenna.

Fig. 32-5

## LF OR HF FIELD STRENGTH METER

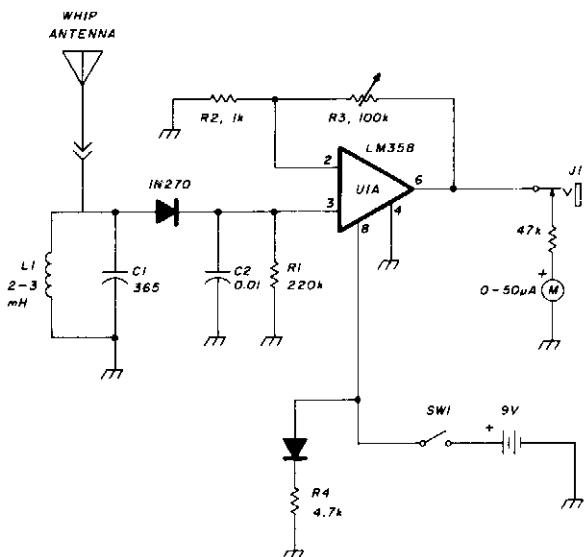


Table 1.

L1	C1 (variable)	Frequency Range	Ham Band
50 $\mu$ H	30-365 pF	1- 4 MHz	160, 80 meters
3 $\mu$ H	30-365 pF	5-16 MHz	40, 30, 20 meters
0.9 $\mu$ H	30-365 pF	9-30 MHz	30, 20, 15, 12, 10 meters
2.5 mH	—	Broadband at reduced gain	

### HAM RADIO

**Fig. 32-6**

### Circuit Notes

C1 and L1 resonate on the 1750 meter band, with coverage from 150 kHz to 500 kHz. L1 can be slug-tuned for 160-to-190 kHz coverage alone or a 2.5 mH choke can be used for L1, if desired, using C1 for tuning. A 1N270 germanium diode rectifies the RF signal and C2 is charged at the peak RF level. This dc level is amplified by an LM358. The gain is determined by R2 and R3, a 100-kilohm linear potentiometer that varies the dc gain from 1 to 100, driving the 50 microampere meter. This field strength meter need not be limited to LF use. The Table shows the L1 and C1 values for HF operation and broadband operation.

# **33**

## **Filter Circuits**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low Cost Universal Active Filter

State Variable Filter

Wideband Two-Pole High-Pass Filter

Active Low-Pass Filter with Digitally Selected Break Frequency

Digitally Tuned Low Power Active Filter

Razor Sharp CW Filter

Fifth Order Chebyshev Multiple Feedback Low-Pass Filter

Precision, Fast Settling Low-Pass Filter

Programmable Bandpass Using Twin-T Bridge

Active Bandpass Filter ( $f_0 = 1000$  Hz)


Bandpass Filter

Active Bandpass Filter

Bandpass and Notch Filter

Multiple-Feedback Bandpass Filter

## LOW COST UNIVERSAL ACTIVE FILTER

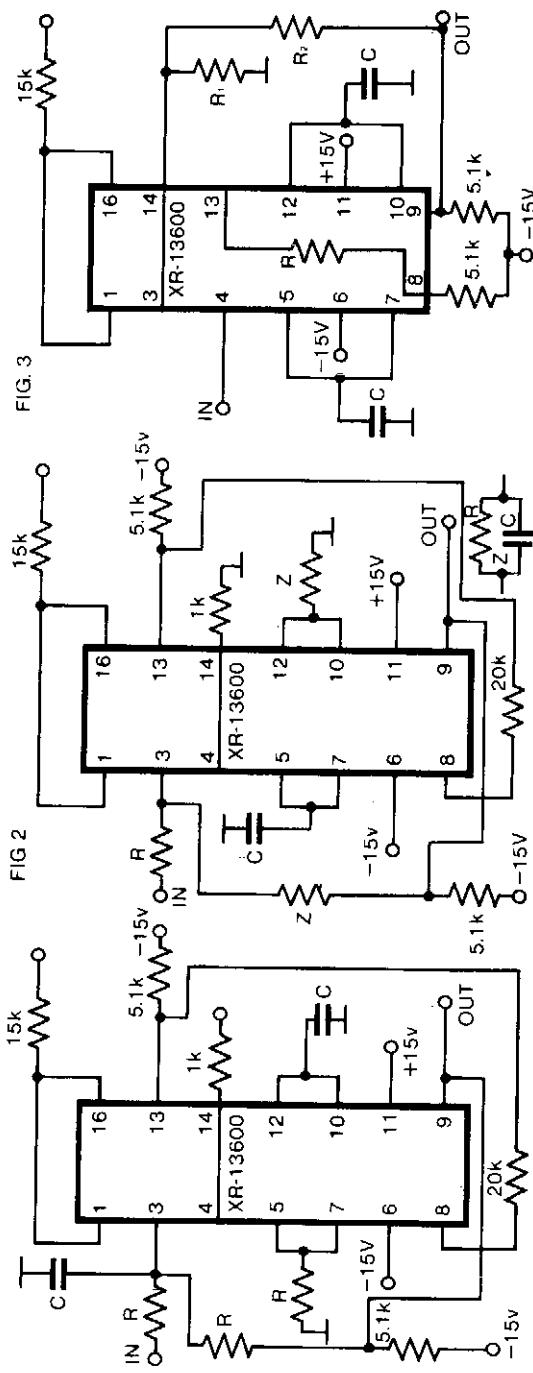

ELECTRONIC ENGINEERING

Fig. 33-1

### Circuit Notes

The circuit as shown in Fig. 1 gives the bandpass operation the transfer function calculated from

$$F_{BP}(s) = \frac{S/\omega_0}{K}$$

where  $K = 1 + s/Q\omega_0 + s^2/\omega_0^2$ . The cut-off frequency,  $\omega_0$ , and the Q-factor are given by

$$\omega_0 = g/C \text{ and } Q = gR/2$$


where  $g$  is the transconductance at room temperature.

Interchanging the capacitor C with the resistor R at the input of the circuit high-pass operation is obtained. A low-pass filter is obtained by applying two parallel connections of R and C as shown in Fig. 2.

The low-pass operation may be much improved with the circuit as given in Fig. 3. Here the gain and Q may be set up separately with respect to the cut-off frequency according to the equations

$$Q = 1/B = 1 + R_2/R_1, \\ A = Q^2 \text{ and } \omega_0 = gIB/C.$$

## STATE VARIABLE FILTER

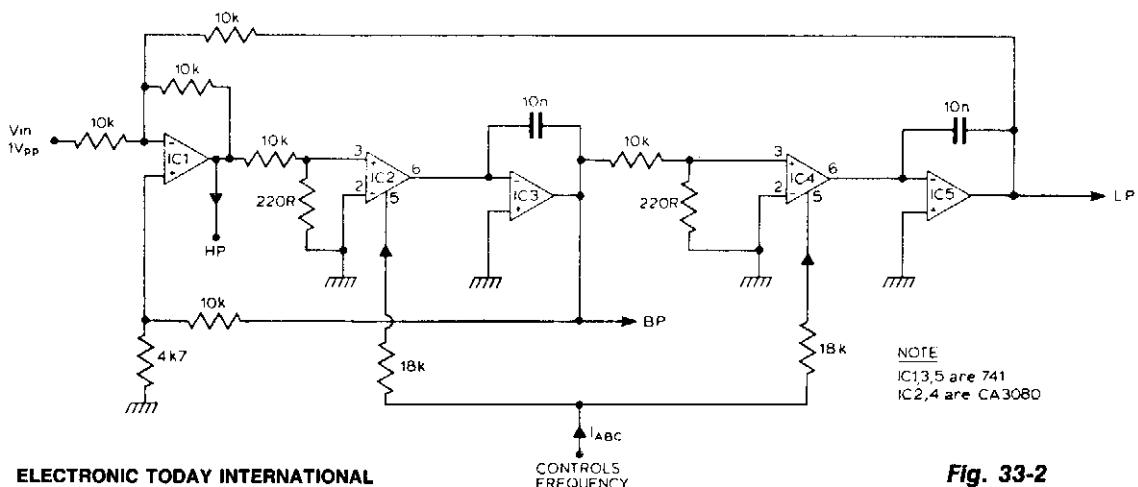


**Fig. 33-2**

### Circuit Notes

The filter produces three outputs: high-pass, bandpass, and low-pass. Frequency is linearly proportional to the gain of the two integrators. Two CA3080's, (IC2, 4) provide the variable gain, the resonant frequency being proportional to the current  $I_{ABC}$ . Using 741 op amps for IC3,a control range of 100 to 1, (resonant frequency) can be obtained. If CA3140's are used instead of 741's then this range can be extended to nearly 10,000 to 1.

## WIDEBAND TWO-POLE HIGH-PASS FILTER

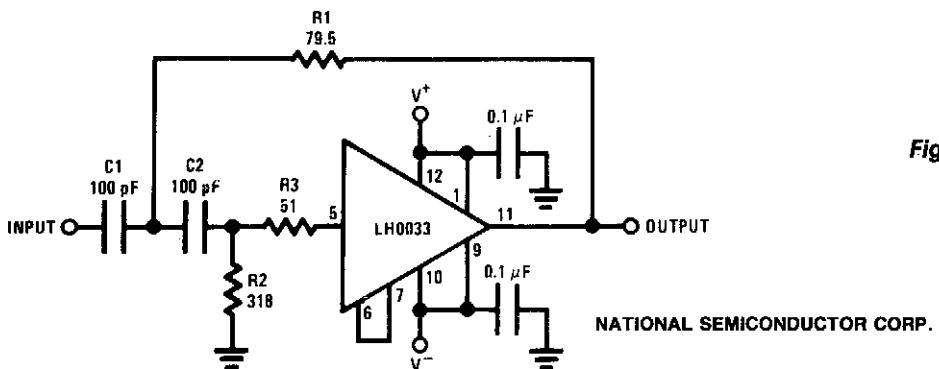

**Fig. 33-3**

### Circuit Notes

The circuit provides a 10MHz cutoff frequency. Resistor R3 ensures that the input capacitance of the amplifier does not interact with the filter response at the frequency of interest. An equivalent low pass filter is similarly obtained by capacitance and resistance transformation.

## ACTIVE LOW-PASS FILTER WITH DIGITALLY SELECTED BREAK FREQUENCY


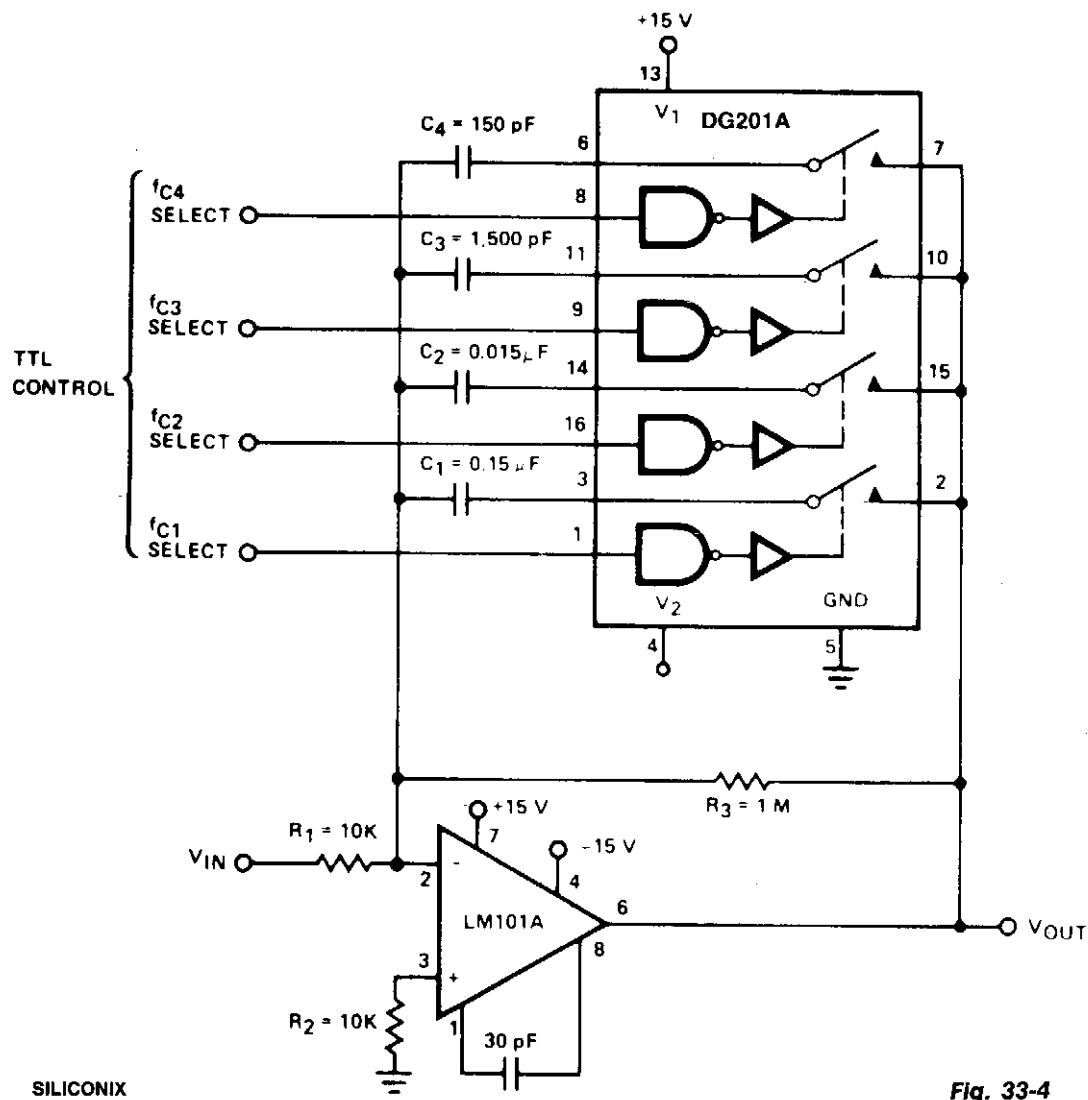


Fig. 33-4
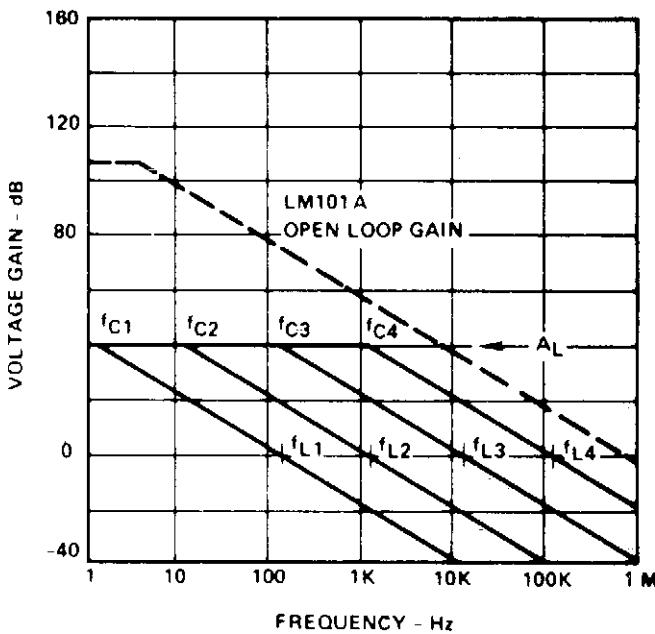
### Circuit Notes

Variable low-pass filter has break frequencies at 1, 10, 100 Hz and 1 kHz. The break frequency is

$$1. \quad f_c = \frac{1}{2 \pi R_3 C_X}$$



$A_L$  (VOLTAGE GAIN BELOW BREAK FREQUENCY)

$$= \frac{R_3}{R_1} = 100 \text{ (40 dB)}$$

$$f_c \text{ (BREAK FREQUENCY)} = \frac{1}{2\pi R_3 C_X}$$

$$f_L \text{ (UNITY GAIN FREQUENCY)} = \frac{1}{2\pi R_1 C_X}$$

$$\text{MAX ATTENUATION} = \frac{r_{DS(on)}}{10K} \approx -40 \text{ dB}$$

The low frequency gain is


$$2. \quad A_L = \frac{R_3}{R_1} = 100 \text{ (40 dB)}$$

A second break frequency (a zero) is introduced by  $r_{DS(on)}$  of the DG201A, causing the minimum gain to be

$$3. \quad A_{MIN} = \frac{r_{DS(on)}}{R_1} \approx \frac{100}{10K} = .01,$$

a maximum attenuation of 40 dB (80 dB relative to the low frequency gain).
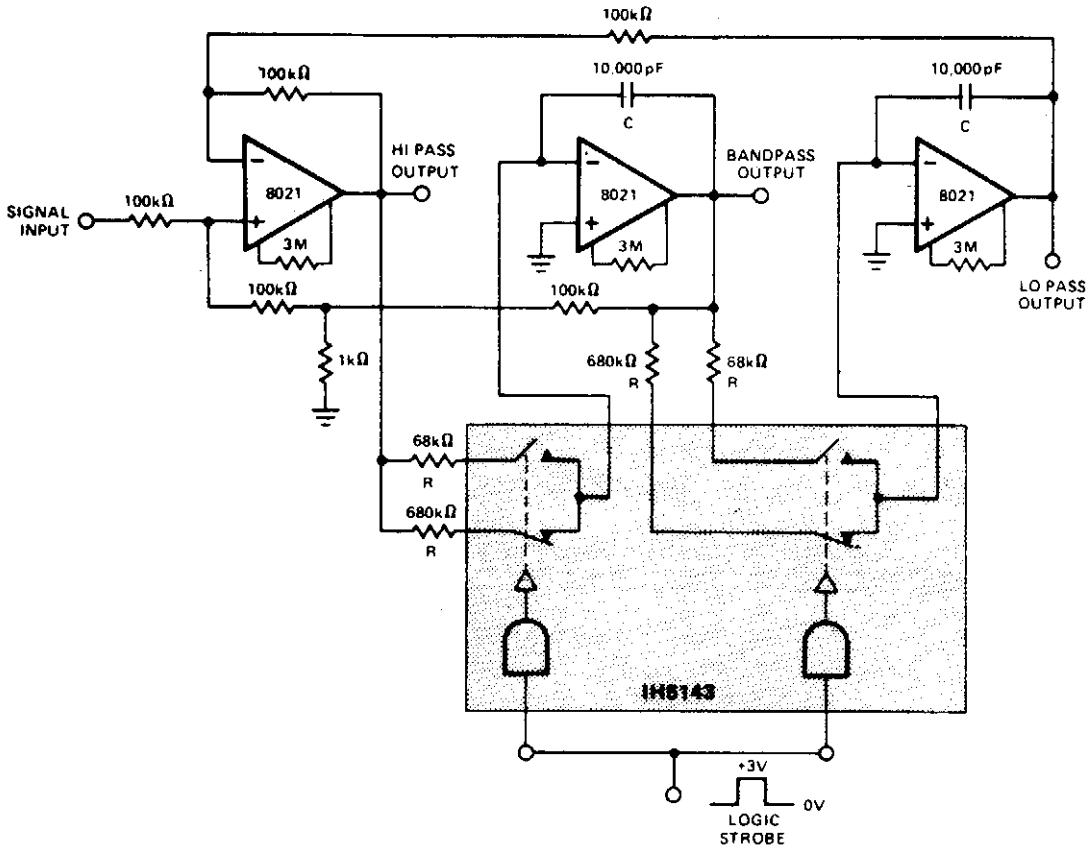
### DIGITALLY TUNED LOW POWER ACTIVE FILTER




INTERSIL

**Fig. 33-5**

#### Circuit Notes

This constant gain, constant Q, variable frequency filter provides simultaneous low-pass, bandpass, and high-pass outputs with the component values shown, the center frequency will be 235 Hz and 23.5 Hz for high and low logic inputs respectively,  $Q = 100$ , and gain = 100.

## RAZOR-SHARP CW FILTER

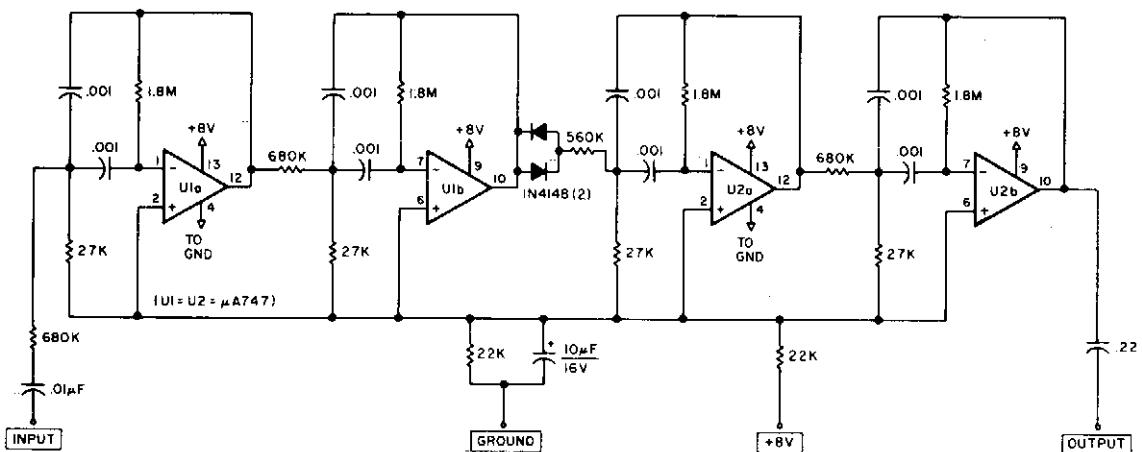


73 MAGAZINE

**Fig. 33-6**

### Circuit Notes

The circuit consists of four stages of active bandpass filtering provided by two type- $\mu$ A747 integrated-circuit dual op amps and includes a simple threshold detector (diodes D1 and D2) between stages 2 and 3 to reduce low-level background noise. Each of the four filter stages acts as a narrow bandpass filter with an audio bandpass centered at 750 Hz. The actual measured 3-dB bandwidth is only 80 Hz wide.
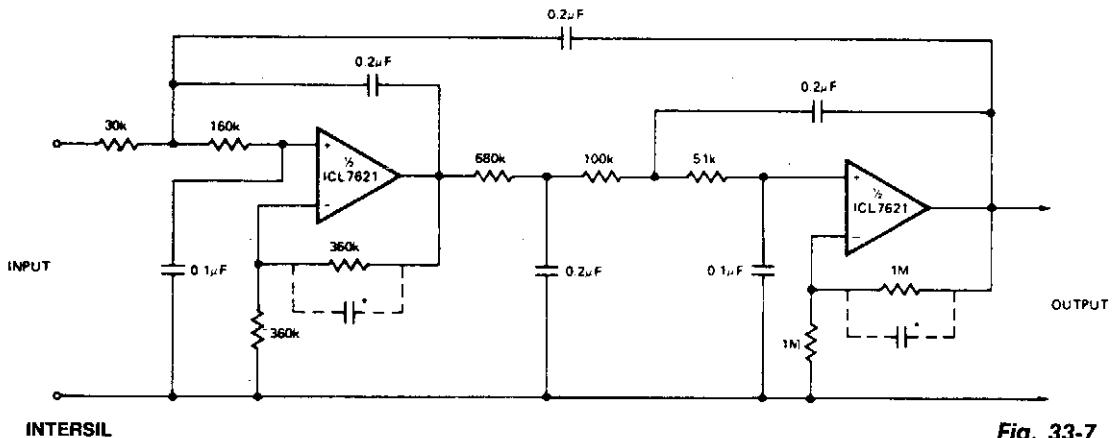
## FIFTH ORDER CHEBYSHEV MULTIPLE FEEDBACK LOW PASS FILTER




INTEGRISL

**Fig. 33-7**

### Circuit Notes

The low bias currents permit high resistance and low capacitance values to be used to achieve low frequency cutoff.  $f_c = 10$  Hz,  $A_{VCL} = 4$ , Passband ripple = 0.1 dB. Note that small capacitors (25-50 pF) may be needed for stability in some cases.
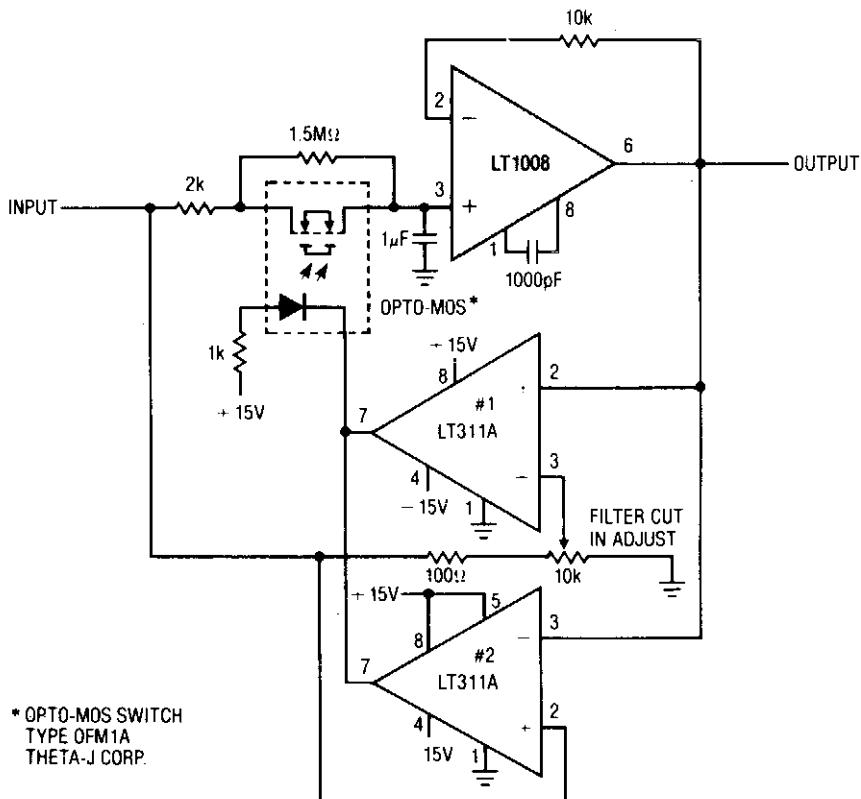
## PRECISION, FAST SETTLING, LOW-PASS FILTER




LINEAR TECHNOLOGY

*Fig. 33-8*

### Circuit Notes

This circuit is useful where fast signal acquisition and high precision are required, as in electronic scales. The filter's time constant is set by the 2 K ohm resistor and the 1  $\mu$ F capacitor until comparator No. 1 switches. The time constant is then set by the 1.5 M ohm resistor and the 1  $\mu$ F capacitor. Comparator No. 2 provides a quick reset. The circuit settles to a final value three times as fast as a simple 1.5 M ohm—1  $\mu$ F filter, with almost no dc error.
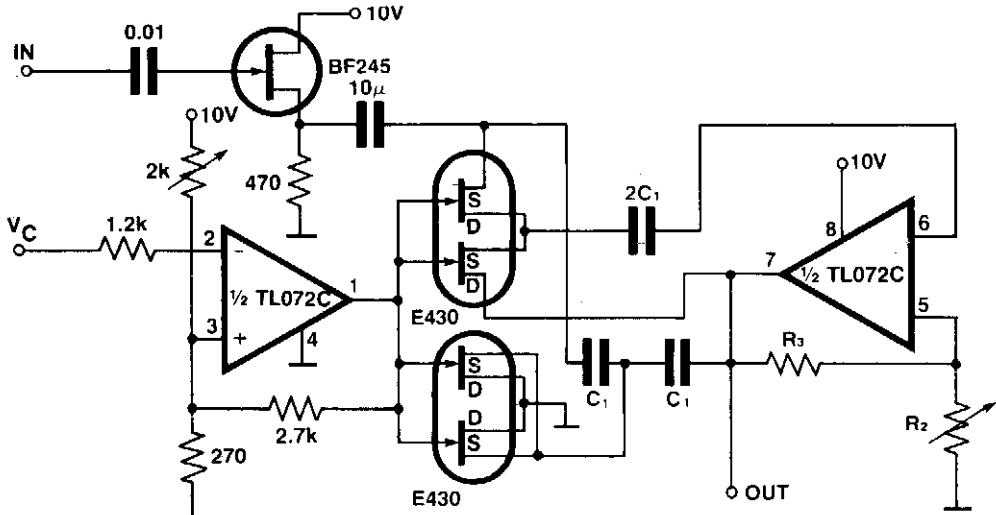
## **PROGRAMMABLE BANDPASS USING TWIN-T BRIDGE**




## ELECTRONIC ENGINEERING

**Fig. 33-9**

## Circuit Notes

The circuit gives a programmable bandpass where both the cut-over frequency and the gain, A, are controlled independently. In the twin-T bridge the resistors R and R/2 are replaced by two double FETs, E 430, the channel resistance of the first one in the series, the channel resistances of the second one are in parallel as to stimulate the resistance R/2. Both these resistors are controlled by  $V_c$  which ranges from 0 V to about 1 V. The gain of the circuit is set by means of the resistors R2 and R3.
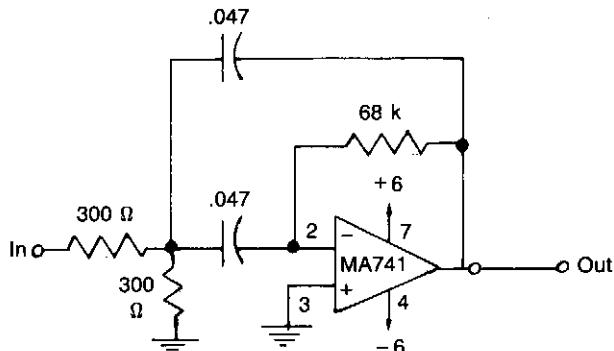
## ACTIVE BANDPASS FILTER ( $f_0 = 1000$ Hz)



## **WILLIAM SHEETS**


**Fig. 33-10**

**Circuit Notes**


This filter has a bandpass centered around 1kHz, for applications such as bridge amplifiers, null detectors, etc.

The circuit uses a μA741 IC and standard 5% tolerance components.

## BANDPASS FILTER

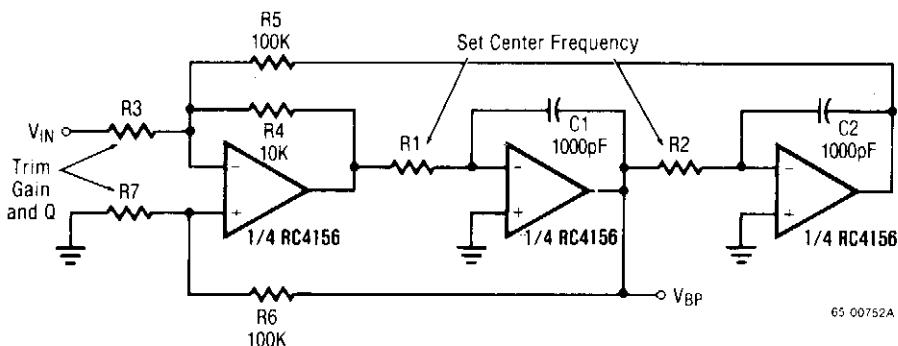

65-00752A

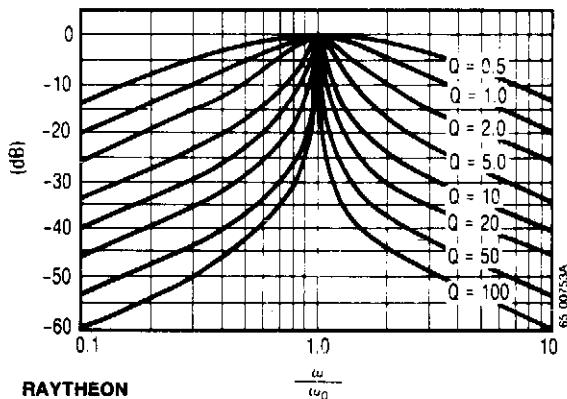

RAYTHEON

$$\frac{V_{BP}}{V_{IN}} = \sqrt{\frac{\frac{\omega}{\omega_0} - \frac{1}{Q}}{\left[1 - \left(\frac{\omega}{\omega_0}\right)^2\right]^2 + \left(\frac{1}{Q} - \frac{\omega}{\omega_0}\right)^2}}$$

Fig. 33-11

### Circuit Notes

The input signal is applied through R3 to the inverting input of the summing amplifier and the output is taken from the first integrator. The summing amplifier will maintain equal voltage at the inverting and non-inverting inputs. Defining  $1/R_1C_1$  as  $\omega_1$  and  $1/R_2C_2$  as  $\omega_2$ , this is now a convenient form to look at the center-frequency  $\omega_0$  and filter Q.

$$\omega_0 = \sqrt{0.1 \omega_1 \omega_2}$$


$$\text{and } Q =$$

$$= 10^{-9} \sqrt{0.1 R_1 R_2}$$

$$\left[ \frac{1 + \frac{10^5}{R_7}}{1.1 + \frac{10^4}{R_3}} \right] \omega_0$$

The frequency response for various values of Q is shown.

## ACTIVE BANDPASS FILTER

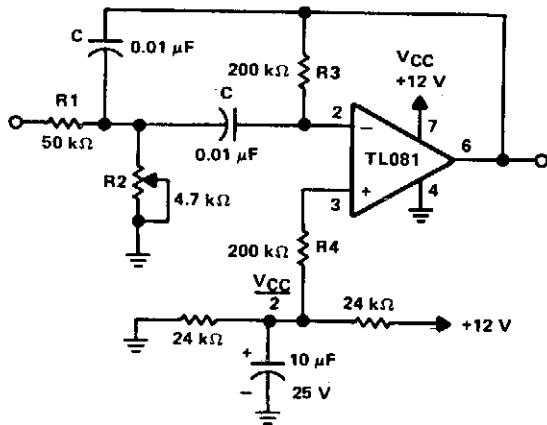

TEXAS INSTRUMENTS

*Fig. 33-12*

### Circuit Notes

The circuit is a two-pole active filter using a TL081 op amp. This type of circuit is usable only for Qs less than 10. The component values for this filter are calculated from the following equations.


$$R_1 = \frac{Q}{2 f G C}$$

$$R_3 = \frac{2Q}{2fC}$$

$$R_2 = \frac{Q}{(2Q^2 - G)2fC} \quad R_4 = R_3$$

The values shown are for a center frequency of 800 Hz.

## BANDPASS AND NOTCH FILTER

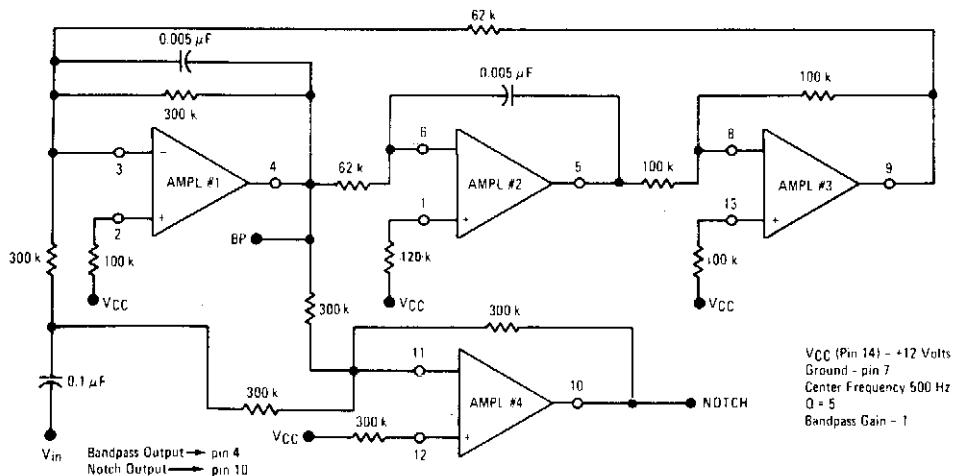

MOTOROLA

*Fig. 33-13*

### Circuit Notes

The Quad op amp MC4301 is used to configure a filter that will notch out a given frequency and produce that notched-out frequency at the BP terminal, useful in communications or measurement setups. By proper component selection any frequency filter up to a few tens of kilohertz can be obtained.

## MULTIPLE-FEEDBACK BANDPASS FILTER

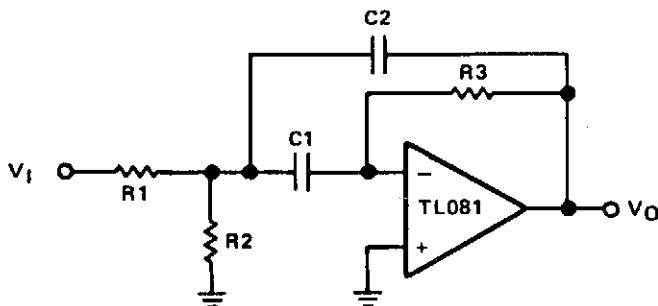


Fig. 33-14

TEXAS INSTRUMENTS

### Circuit Notes

The op amp is connected in the inverting mode. Resistor R3 from the output to the inverting input sets the gain and current through the frequency-determining capacitor, C1. Capacitor C2 provides feedback from the output to the junction of R1 and R2. C1 and C2 are always equal in value. Resistor R2 may be made adjustable in order to adjust the center frequency which is determined from:

$$f_0 = \frac{1}{2\pi C} \times \frac{1}{R3} \times \frac{R1 + R2^{1/2}}{R1R2}$$

When designing a filter of this type it is best to select a value for C1 and C2, keeping them equal. Typical audio filters have capacitor values from  $0.01 \mu\text{F}$  to  $0.1 \mu\text{F}$  which will result in reasonable values for the resistors.

## **34**

# **Flashers and Blinkers**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- |  |   |
|--|---|
| Low Voltage Lamp Flasher                                 | 2 kW Flasher with Photoelectric Control |
| Miniature Transistorized Light Flasher                   | Sequential Flasher                      |
| Alternating Flasher                                      | 1 kW Flip-Flop Flasher Circuit          |
| Electronic Light Flasher                                 | Low Frequency Oscillator Flasher        |
| High-Power Battery-Operated Flasher                      | High Drive Oscillator/Flasher           |
| Series SCR Lamp Flasher Handles a Wide Range<br>of Loads | Transistorized Flashers                 |
| SCR Relaxation Flasher                                   | Sequential ac Flasher                   |
| Low Current Consumption Lamp Flasher                     | Astable Flip-Flop with Starter          |
| LED Flasher Uses PUT                                     | LED Flasher Uses UJT                    |

## LOW VOLTAGE LAMP FLASHER

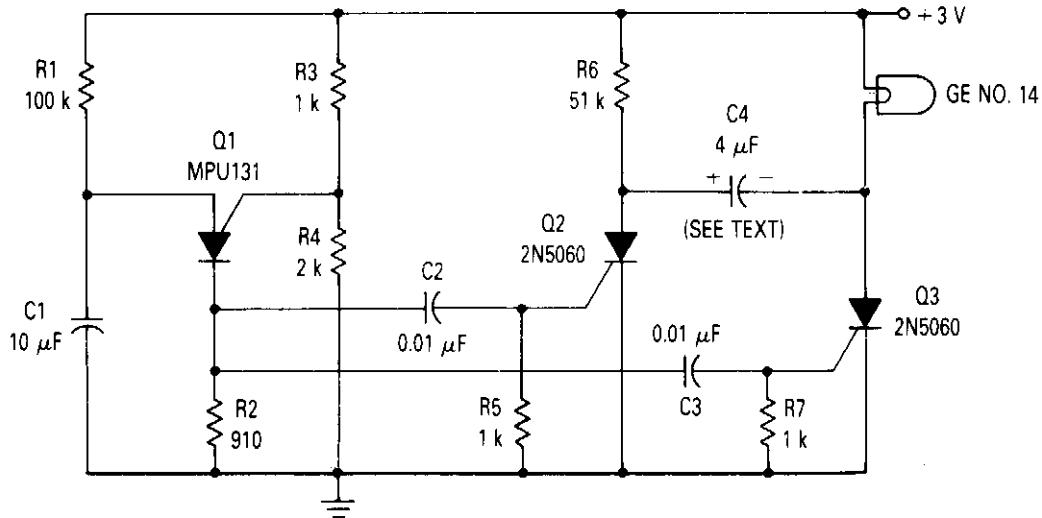


MOTOROLA

**Fig. 34-1**

### Circuit Notes

The circuit is composed of a relaxation oscillator formed by Q1 and an SCR flip-flop formed by Q2 and Q3. With the supply voltage applied to the circuit, the timing capacitor C1 charges to the firing point of the PUT, 2 volts plus a diode drop. The output of the PUT is coupled through two  $0.02 \mu\text{F}$  capacitors to the gate of Q2 and Q3. To clarify operation, assume that Q3 is on and capacitor C4 is charged plus to minus as shown in the figure. The next pulse from the PUT oscillator turns Q2 on. This places the voltage on C4 across Q3 which momentarily reverse biases Q3. This reverse voltage turns Q3 off. After discharging, C4 then charges with its polarity reversed to that shown. The next pulse from Q1 turns Q3 on and Q2 off. Note that C4 is a non-polarized capacitor. For the component values shown, the lamp is on for about  $\frac{1}{2}$  second and off the same amount of time.
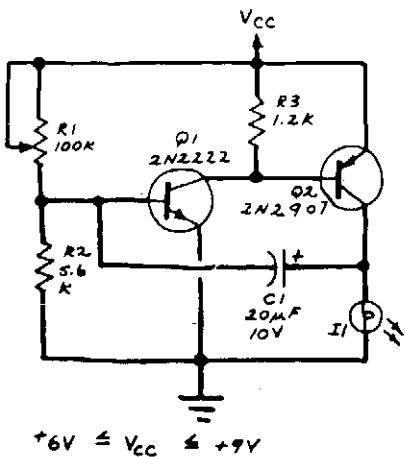
## MINIATURE TRANSISTORIZED LIGHT FLASHER




POPULAR ELECTRONICS

**Fig. 34-2**

## Circuit Notes

R1 adjusts the flash rate. The lamp should be a No. 122, No. 222 or other similar, miniature incandescent lamp.

## ALTERNATING FLASHER

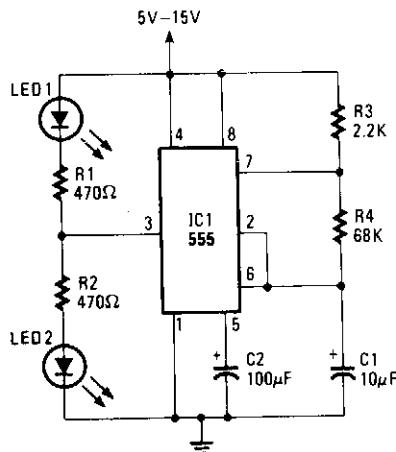


HANDS-ON ELECTRONICS

**Fig. 34-3**

## Circuit Notes

The LED's flash alternately. The flash rate is determined by C1 and R4.

## ELECTRONIC LIGHT FLASHER

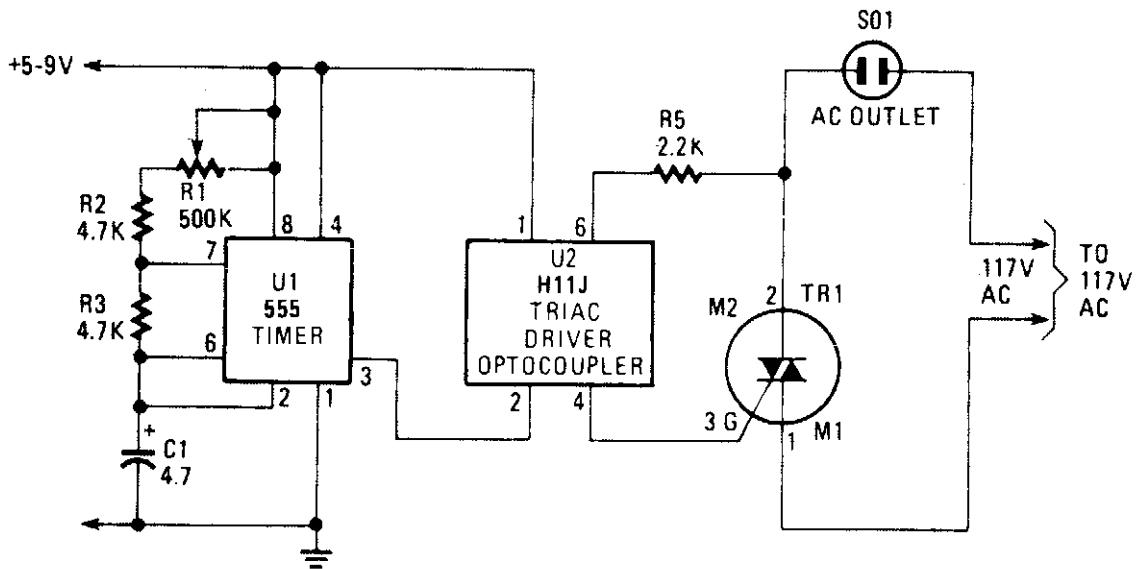

HANDS-ON ELECTRONICS

Fig. 34-4

### Circuit Notes

The blinking or flashing rate is determined by U1, a 555 timer integrated circuit. Its output, at pin 3, feeds U2, a H11J triac driver. That driver consists of an infrared LED that is coupled internally to a light-activated silicon bilateral switch (DIAC). When the LED internal to U2 is turned on by the timer, U1, its light triggers the DIAC; effectively closing the circuit between pins 4 and 6, and fires the Triac, TR1 through its gate circuit. When the Triac is firing, it acts as a closed circuit that turns on the light (or other device it may be controlling via S01). When the timer turns off, the LED, the DIAC and Triac stop conducting and the light turns off. The sequence then repeats. The flashing rate can be varied by means of R1, a 500,000 ohm potentiometer.

## HIGH-POWER BATTERY-OPERATED FLASHER

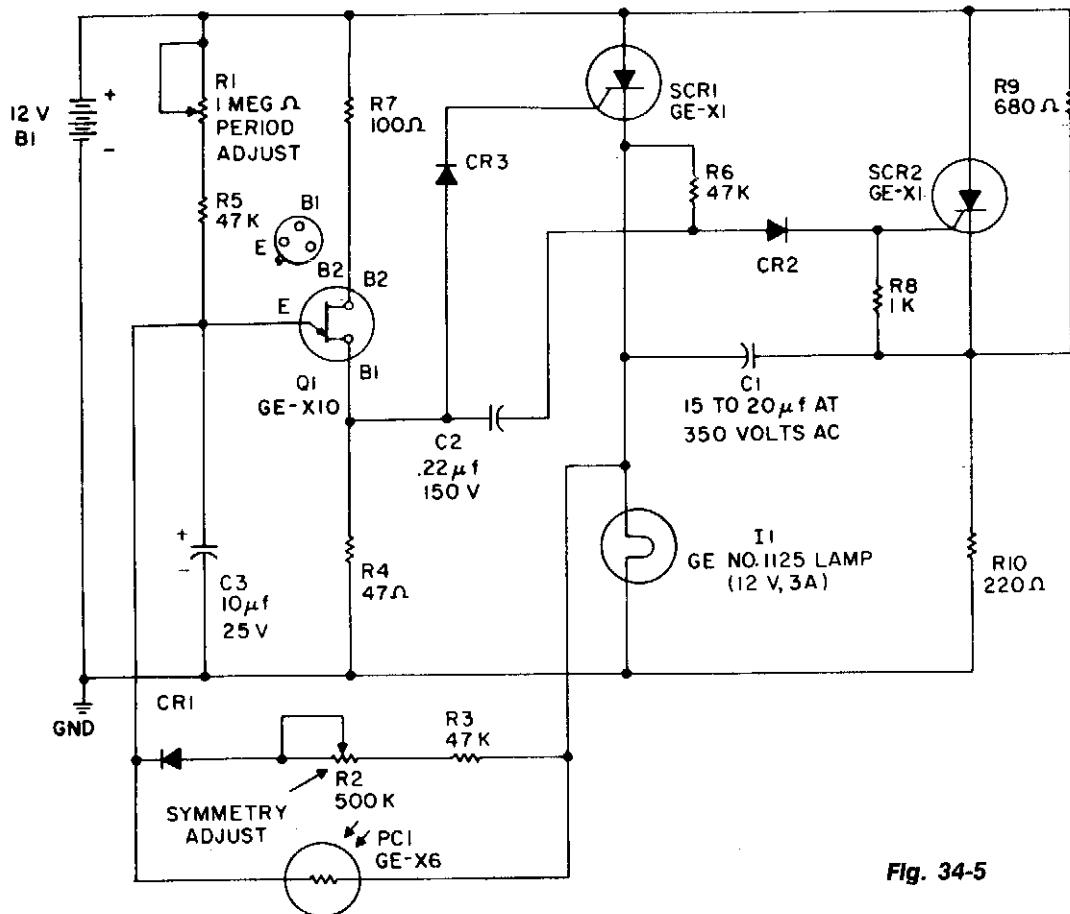


Fig. 34-5

GENERAL ELECTRIC

### Circuit Notes

This flasher operates from a 12-volt car or boat battery. It offers 36 to 40-watts output, variable flash rate (up to 60 flashes per minute), independent control of both on and off cycles and photoelectric night and day control that turns the flasher on at night and shuts it off during the day for automatic operation. SCR1 and SCR2 form a basic dc flip-flop. The lamp load is the cathode leg of one SCR so that the other side of the load may be at ground (negative) potential (required in some applications). The flip-flop timing is controlled by a conventional UJT oscillator arrangement (Q1, R1, C3, etc.). Potentiometer R2 and diode CR1 provide on/off timing independence. Photoconductor PC1 locks out the UJT firing circuit during the daylight hours.

## SERIES SCR LAMP FLASHER HANDLES A WIDE RANGE OF LOADS

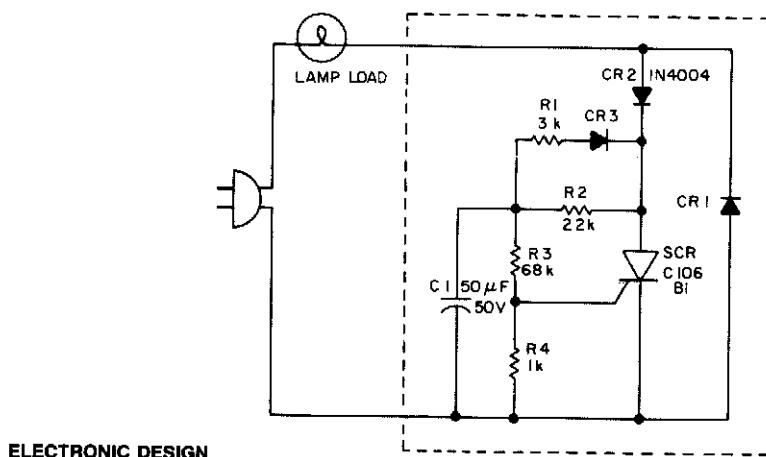


Fig. 34-6

### Circuit Notes

Brief full-power flashes are obtained when the SCR conducts during positive half cycles of the line voltage. The SCR fires when the voltage at the divider, R3 and R4, reaches the gate-firing level. Diode D1 conducts during the reverse cycle of the SCR and provides preheating current to the lamp filaments.

## SCR RELAXATION FLASHER

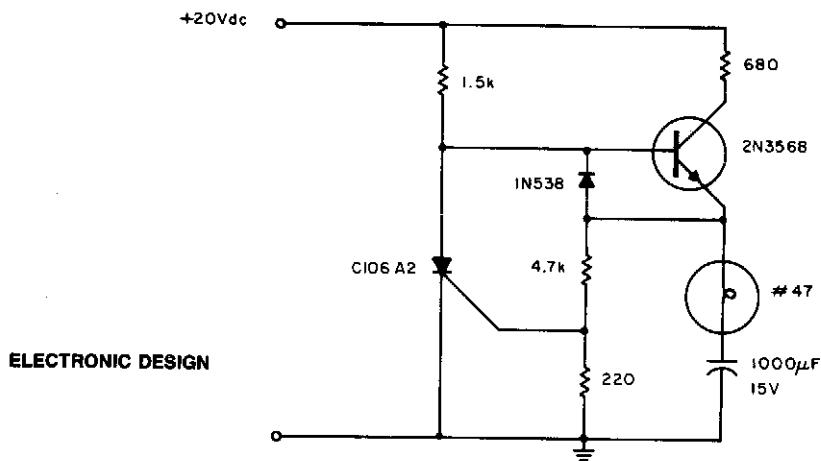


Fig. 34-7

### Circuit Notes

Flashing occurs each time the capacitor discharges through the turned-on SCR. When the discharge current falls below the SCR holding current, the SCR turns off, and the capacitor begins charging for another cycle. The circuit will maintain a slower but good flashing capability even after considerable battery degradation.

## LOW CURRENT CONSUMPTION LAMP FLASHER

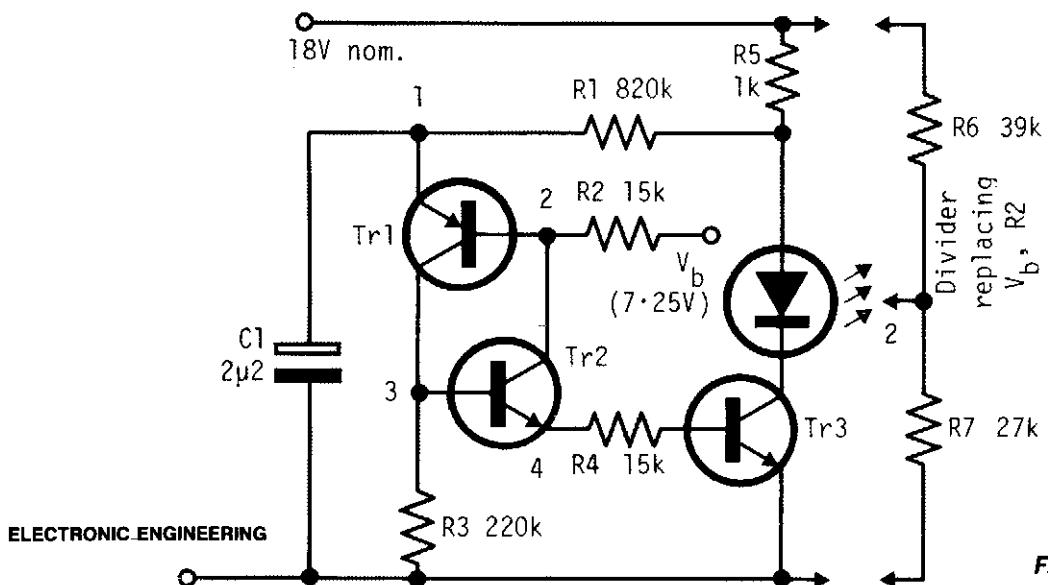


Fig. 34-8

### Circuit Notes

The circuit is economical in components, and will work with virtually any transistors and is reliably self-starting. The voltage  $V_b$  can be taken from a divider, as shown at the right. If taken from a fixed source, flashing becomes slower as battery voltage falls. The lowest drive current into the base of Tr3 is about  $(V_b - 0.6\text{ V})/(R_2 + R_4)$ . Resistor R4 limits the initial current from C1 and, as shown, R2 and R4 can be roughly equal when a divider is used for  $V_b$ . Resistor R2 equals  $R_6 R_7 / (R_6 + R_7)$ . With the voltages shown, and with  $R_2 = R_4$ , the on-time is about  $1.1 C_1 R_2$  and the off-time about  $0.28 C_1 R_1$ . Using the component values shown the period is about 0.55 sec. with a duty cycle of about 7% and a mean battery current including the  $V_b$  divider, about 1.5 mA.

## LED FLASHER USES UJT


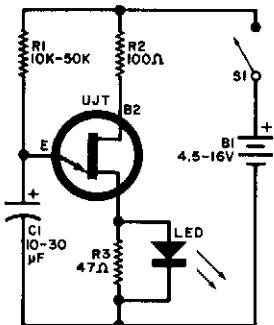


Fig. 34-9

### Circuit Notes

A relaxation oscillator is used to flash an LED in the base circuit. C1 is charged slowly through R1 by the power source, then discharged periodically through R3 and the LED by the UJT. Flashing rate is determined by the supply voltage and by R1-C1's time constant. UJT = 2N4871
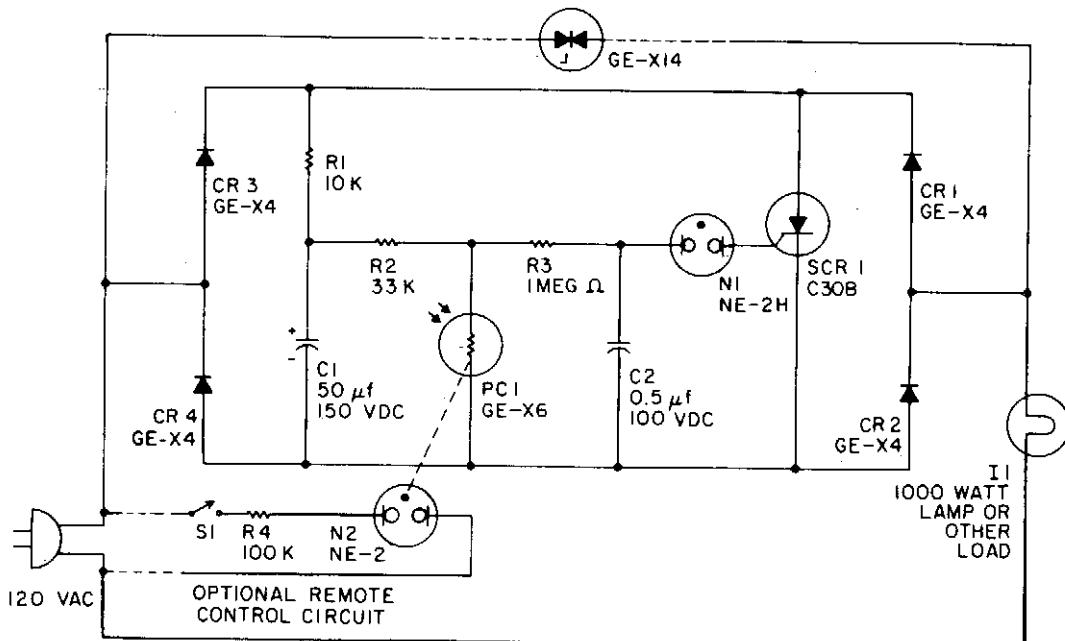
## 2 KW FLASHER WITH PHOTOELECTRIC CONTROL




GENERAL ELECTRIC

**Fig. 34-10**

### Circuit Notes

CR1, CR2, CR3, and CR4 form a bridge circuit with the SCR across the dc legs. With light on the photoconductor PC1, C1 charges through R1 to about 150 Vdc. The resistance of PC1 is low when illuminated, so very little voltage appears across it or C2. At about 90 volts C1 starts discharging through R1 and the SCR, but the SCR cannot turn off until C1 is almost completely discharged. When the SCR turns off during the interval line voltage is near zero, the full supply voltage again appears across the bridge, and C1 charges again to a high voltage. The voltage on C2 also starts rising until the neon lamp fires and the cycle repeats. An alternative remote control can be made by adding a second neon lamp, N2, and masking the photocell so it sees only N2. A very sensitive remote control is thus obtained that is completely isolated from the load circuit. For low-voltage remote control a flashlight lamp may be used instead of N2 and operated at about  $\frac{1}{2}$  its normal voltage thus giving exceptionally long life. Performance of the photoelectric control may be inverted (flash when the photoconductor is illuminated) by interchanging PC1, and R2. Sensitivity in either the normal or inverted modes can be decreased by partially masking PC1, and can be increased by increasing resistor R2 to about 470 K. To increase on time, increase C1; to increase off time, increase R3.

## SEQUENTIAL FLASHER

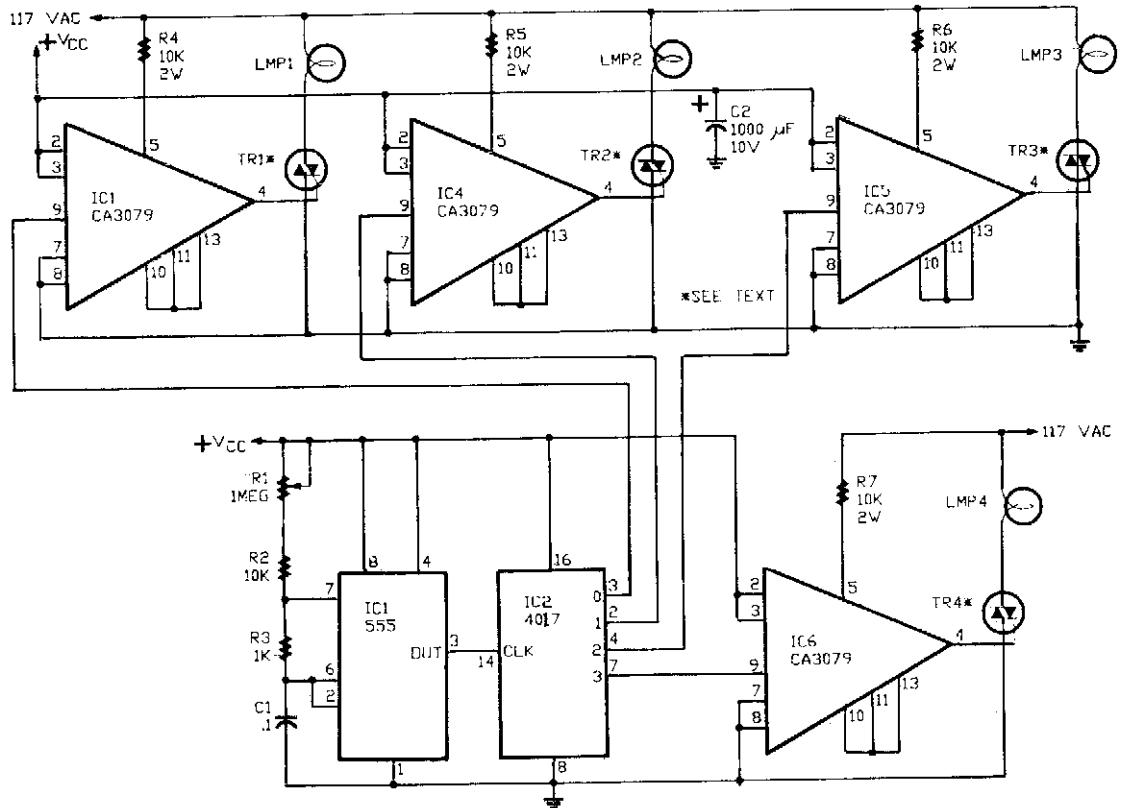

RADIO-ELECTRONICS


**Fig. 34-11**

### Circuit Notes

A 555 timer, IC1, drives a 4017 CMOS decade counter. Each of the 4017's first four outputs drives a CA3079 zero-voltage switch. Pin 9 of the CA3079 is used to inhibit output from pin 4, thereby disabling the string of pulses that IC normally delivers. Those pulses occur every 8.3 ms, i.e., at a rate of 120 Hz. Each pulse has a width of 120  $\mu$ s. Due to the action of the CA3079, the lamps connected to the TRI-AC's turn on and off near the zero crossing of the ac waveform. Switching at that point increases lamp life by reducing the inrush of current that would happen if the lamp were turned on near the high point of the ac waveform. In addition, switching at the zero crossing reduces Radio-Frequency Interference (RFI) considerably.

**CAUTION:** The CA3079's are driven directly from the 117-volt ac power line, so use care.

### 1 kW FLIP-FLOP FLASHER CIRCUIT

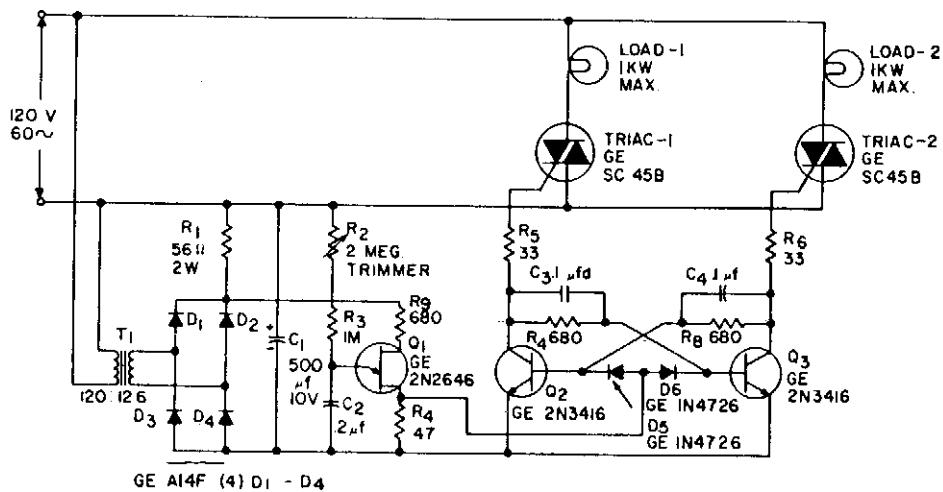

GENERAL ELECTRIC

Fig. 34-12

### Circuit Notes

This is an application of the static switch circuit where the control logic is a flip-flop which is controlled by the unijunction transistor. The flashing rate can be adjusted from about 0.1 second to a 10 second cycle time.

### LOW FREQUENCY OSCILLATOR-FLASHER


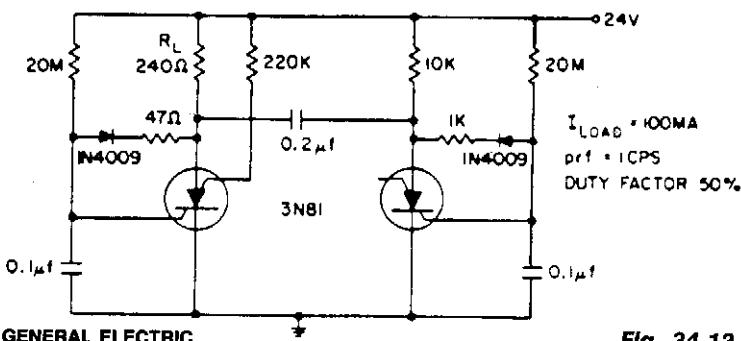


Fig. 34-13

### Circuit Notes

Electrolytic capacitors are unnecessary to generate a 1 cps frequency. As an scs triggers on, the 0.2  $\mu$ F commutating capacitor turns off the other one and charges its gate capacitor to a negative potential. The gate capacitor charges towards 24 volts through 20 M retriggering its scs. Battery power is delivered to the load with 88% efficiency. The 20 M resistors can be varied to change prf or duty factor.

## HIGH DRIVE OSCILLATOR/FLASHER

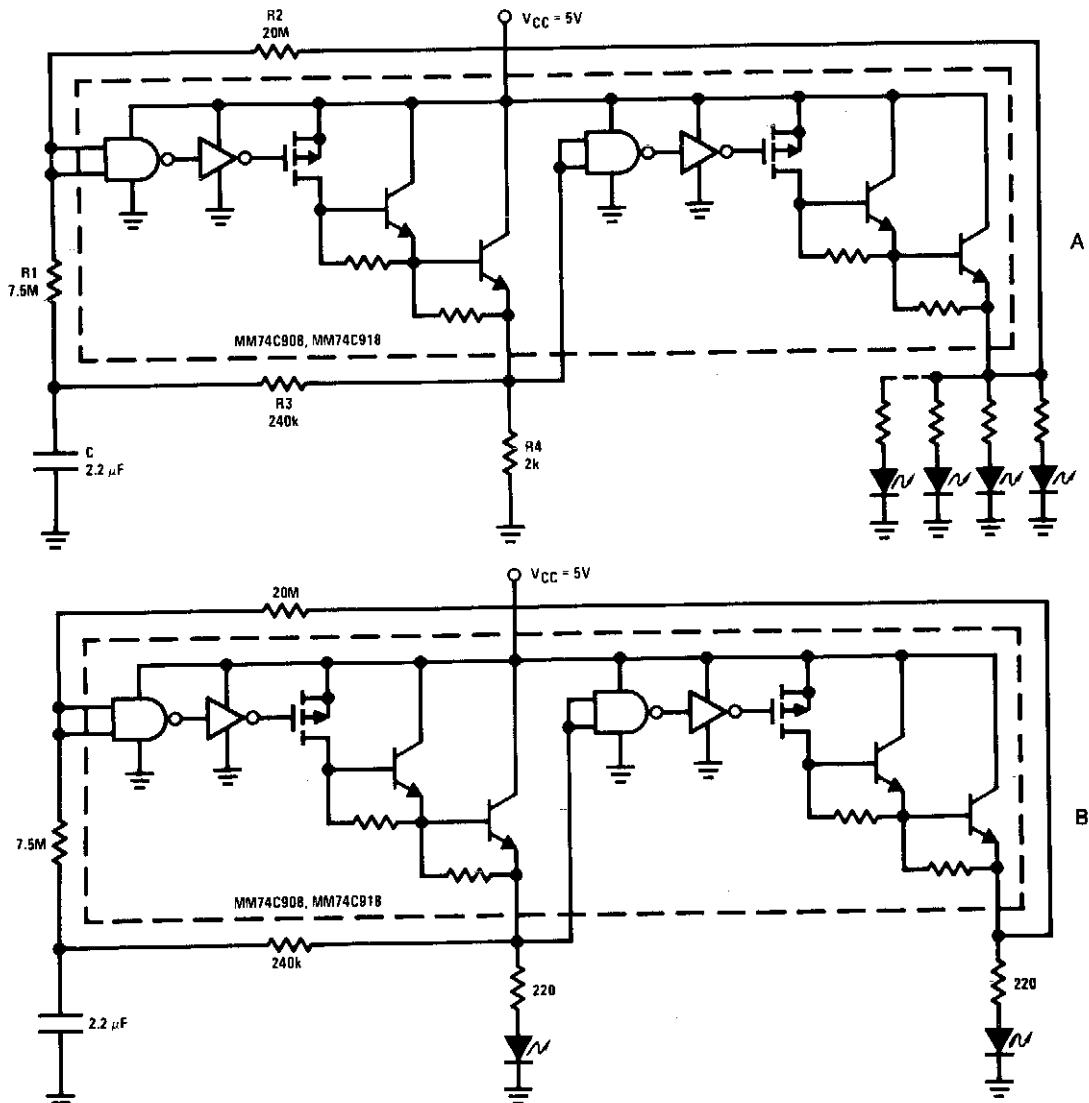

NATIONAL SEMICONDUCTOR CORP.

Fig. 34-14

### Circuit Notes

The driver in the package is connected as a Schmitt trigger oscillator (A) where R1 and R2 are used to generate hysteresis. R3 and C are the inverting feedback timing elements and R4 is the pull-down load for the first driver. Because of its current capability, the circuit can be used to drive an array of LEDs or lamps. If resistor R4 is replaced by an LED (plus a current limiting resistor), the circuit becomes a double flasher with the 2 LEDs flashing out of phase (B).

## TRANSISTORIZED FLASHERS

Flasher circuit performance as a function of temperature using 11limit sample transistors.

		AMBIENT TEMPERATURE		
		-40°F	77°F	212°F
CIRCUIT #1	Flashes per Minute	min. max.	58.0 56.7	60.0 59.6
	Flash Duration in %	min. max.	14.5 15.1	14.6 14.9
CIRCUIT #2	Flashes per Minute	min. max.	58.6 55.6	60.0 58.1
	Flash Duration in %	min. max.	26.3 28.8	27.5 29.1
CIRCUIT #3	Flashes per Minute	min. max.	59.0 55.4	60.0 57.7
	Flash Duration in %	min. max.	45.2 45.6	46.0 46.2

### Circuit Notes

Transistors Q1 and Q2 are connected as a free running multivibrator. The output, at the emitter of Q2, drives the base of the common emitter amplifier Q3, which controls the lamp. This circuit configuration permits the flash duration, the interval between flashes, and the lamp type to be varied independently. Flash duration is proportional to the product of R2C2 while the off interval is proportional to the product of R3C1. Consequently, when the flash timing must be accurately maintained, these component tolerances will have to be held to similar limits.

All three circuits described are designed for barricade warning flasher lights such as used in highway construction. They differ only in flash duration which normally is 15%, 25%, or 50% of the flash rate. Performance has been checked at ambient temperatures of -40°F, 77°F, and 212°F. A GE 5 volt, 90 millampere type No. 1850 lamp is used.

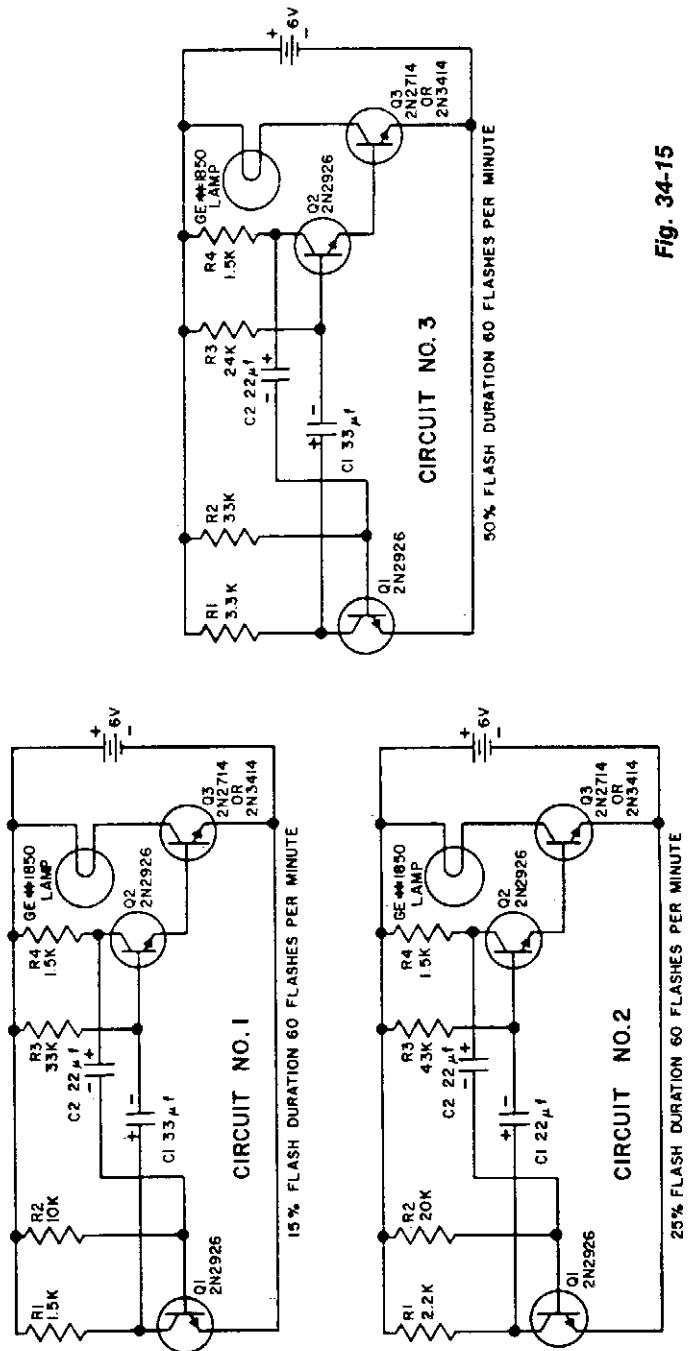
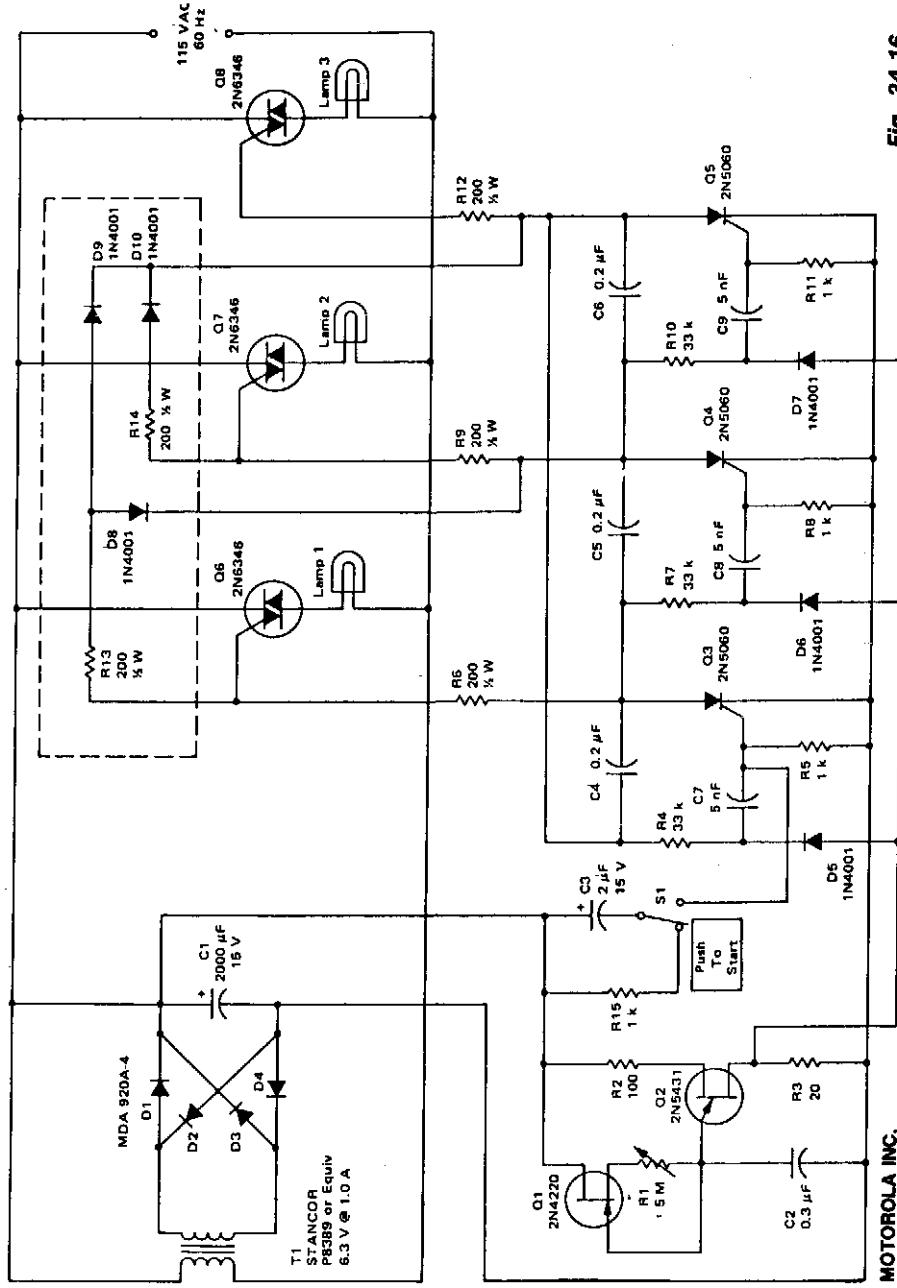


Fig. 34-15

## SEQUENTIAL AC FLASHER

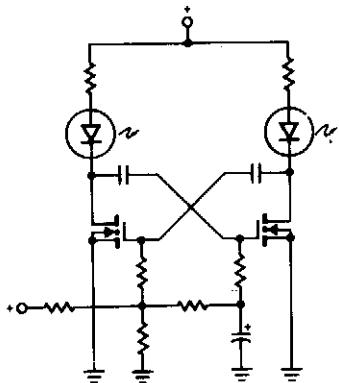


**Fig. 34-16**

### Circuit Notes

This circuit uses a ring counter made up of Q3, Q4 and Q5. Q2 acts as an oscillator which triggers the SCRs Q3, Q4 and Q5 in sequence. When an SCR fires, a 0.2 $\mu$ F capacitor provides commutation, shutting off the previous stage. Triacs Q6, Q7 and Q8 control lamps 1, 2 and 3 respectively.

## ASTABLE FLIP-FLOP WITH STARTER




SILICONIX, INC.

Fig. 34-17

### Circuit Notes

A pair of non-zenered MOSPOWER transistors, a pair of LEDs and a simple RC circuit make an easy sequential flasher with almost unlimited sequencing time—from momentary to several seconds. The infinite input resistance of the MOSFET gate allows for very long sequencing times that are impossible when using bipolars. One precaution, though, don't wire your circuit using phenolic or printed circuit boards when looking for slow sequencing (they exhibit too much leakage!).

## LED FLASHER USES PUT

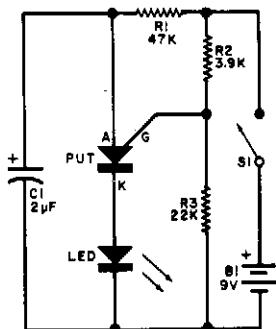

POPULAR ELECTRONICS

Fig. 34-18

### Circuit Notes

This flasher circuit operates as a relaxation oscillator with C1 discharged periodically through the LED as the PUT switches on. The flashing rate is about 100/min with the component values listed.

# **35**

## **Flow Detectors**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Thermally Based Anemometer (Air Flowmeter)  
Air Flow Detector

## **THERMALLY BASED ANEMOMETER (AIR FLOWMETER)**

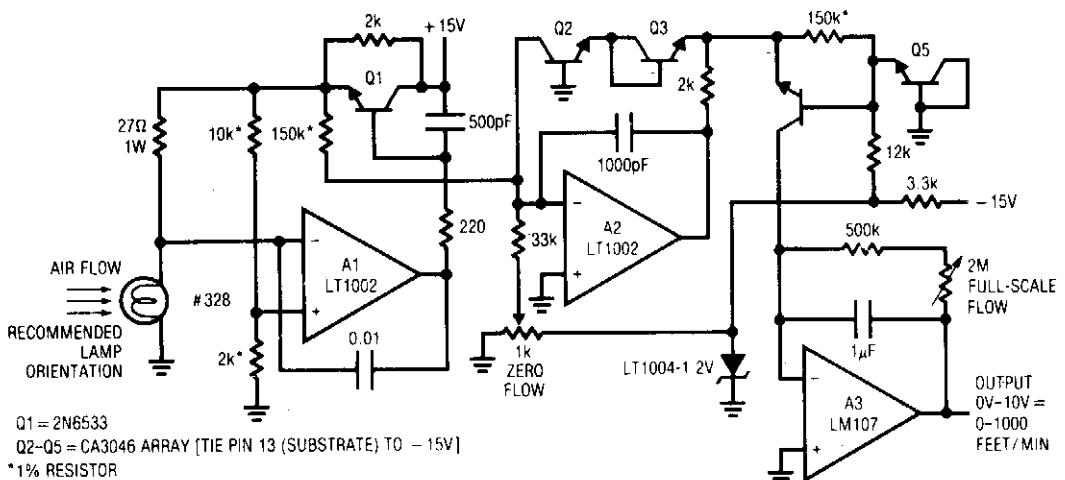

*Fig. 35-1*

**LINEAR TECHNOLOGY CORPORATION**

## Circuit Notes

This design used to measure air or gas flow works by measuring the energy required to maintain a heated resistance wire at constant temperature. The positive temperature coefficient of a small lamp, in combination with its ready availability, makes it a good sensor. A type 328 lamp is modified for this circuit by removing its glass envelope. The lamp is placed in a bridge which is monitored by A1. A1's output is current amplified by Q1 and fed back to drive the bridge. When power is applied, the lamp is at a low resistance and Q1's emitter tries to come full on. As current flows through the lamp, its temperature quickly rises, forcing its resistance to increase. This action increases A1's negative input potential. Q1's emitter voltage decreases and the circuit finds a stable operating point. To keep the bridge balanced, A1 acts to force the lamp's resistance, hence its temperature, constant. The 20 k - 2 k bridge values have been chosen so that the lamp operates just below the incandescence point.

To use this circuit, place the lamp in the air flow so that its filament is at a 90° angle to the flow. Next, either shut off the air flow or shield the lamp from it and adjust the zero flow potentiometer for a circuit output of 0 V. Then, expose the lamp to air flow of 1000 feet/minute and trim the full flow potentiometer for 10 V output. Repeat these adjustments until both points are fixed. With this procedure completed, the air flowmeter is accurate within 3% over the entire 0-1000 foot/minute range.

## AIR FLOW DETECTOR

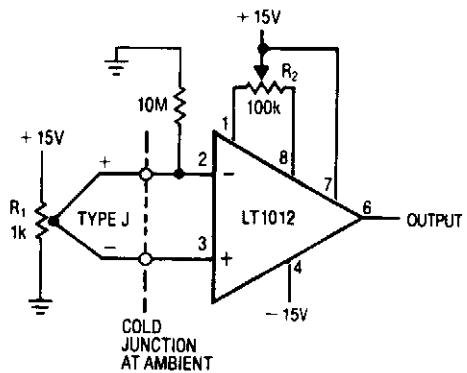


Fig. 35-2

Mount R<sub>1</sub> in airflow.  
Adjust R<sub>2</sub> so output goes high when airflow stops.

LINEAR TECHNOLOGY CORP.

# 36

## Fluid and Moisture Detectors

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Rain Warning Beeper
- Water-Level Indicator
- Acid Rain Monitor
- Plant-Water Monitor
- Water-Level Sensing and Control
- Single Chip Pump Controller
- Plant-Water Gauge
- Liquid Flowmeter

### RAIN WARNING BLEEPER

Rain  
sensing  
grid

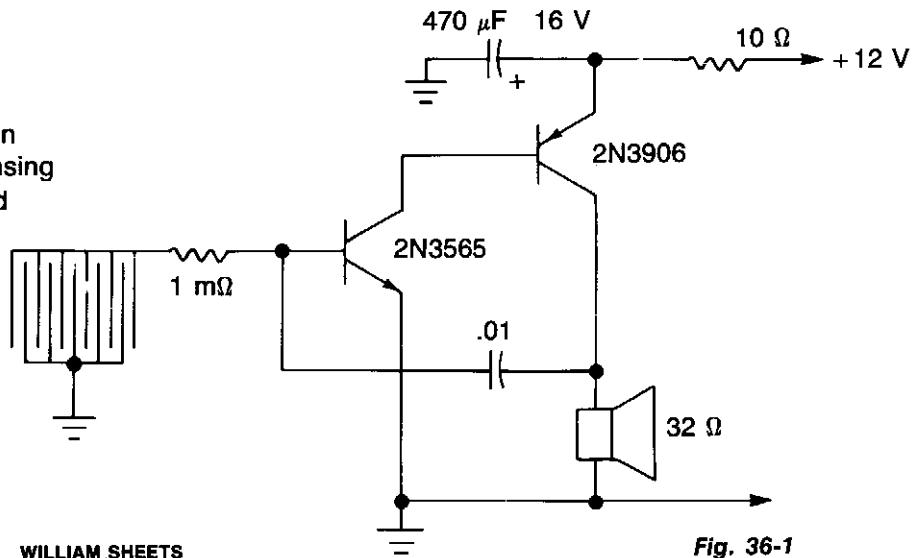


WILLIAM SHEETS

Fig. 36-1

### Circuit Notes

One small spot of rain on the sense pad of this beeper will start this audio warning. It can also be operated by rising water. The circuit has two transistors, with feedback via capacitor C1, but Tr1 cannot operate as long as the moisture sense pad is dry. When the pad conducts, Tr1 and Tr2 form an audio oscillatory circuit, the pitch depends somewhat on the resistance.

### WATER-LEVEL INDICATOR

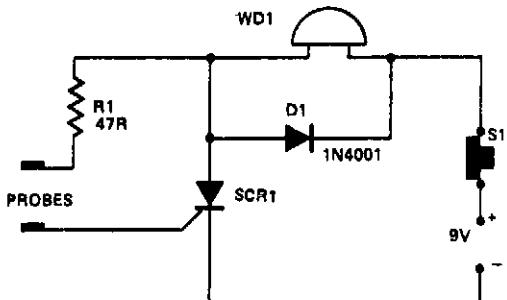


### Circuit Notes

In this a warning device WD1 is in series with SCR1. When the liquid level causes a conductive path between the probes, the SCR conducts sounding WD1. The warning device may be a Sonalert (TM), a lamp or a buzzer. D1 acts as a transient suppressor. Press S1 to reset the circuit.

ELECTRONICS TODAY INTERNATIONAL

Fig. 36-2

## ACID RAIN MONITOR

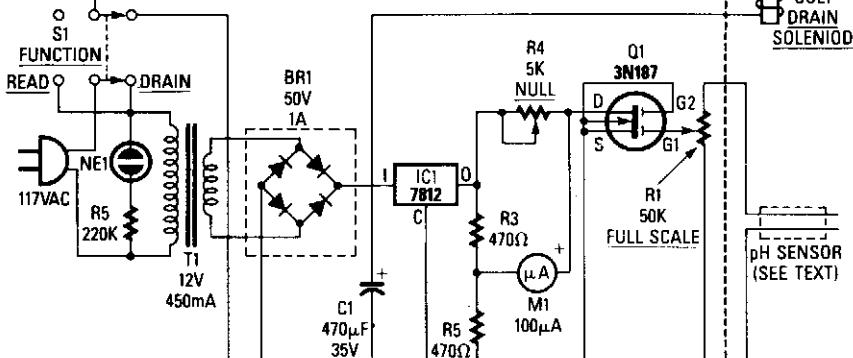


RADIO-ELECTRONICS

Fig. 36-3

### Circuit Notes

A bridge rectifier and 12-volt regulator powers the MOSFET sensing circuit. The unregulated output of the bridge rectifier operates the drain solenoid via switch S1. The sensor itself is built from two electrodes, one made of copper, the other of lead. In combination with the liquid trapped by the sensor, they form a miniature lead-acid cell whose output is amplified by MOSFET Q1. The maximum output produced by our prototype cell was about 50  $\mu$ A. MOSFET Q1 serves as the fourth leg of a Wheatstone bridge. When acidity causes the sensor to generate a voltage, Q1 turns on slightly, so its drain-to-source resistance decreases. That resistance variation causes an imbalance in the bridge, and that imbalance is indicated by meter M1.

## PLANT-WATER MONITOR

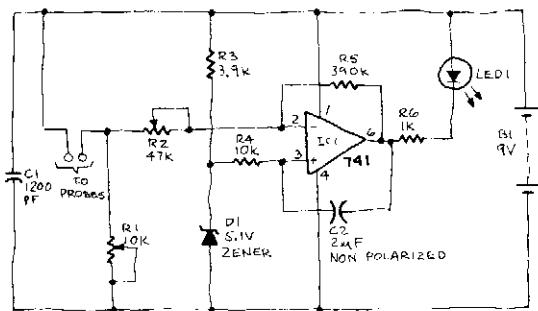


RADIO-ELECTRONICS

Fig. 36-4

### Circuit Notes

When the soil is moist, the LED glows. If the moisture falls below a certain predetermined level, the LED begins to flash. If there is still less moisture, the LED turns off. To calibrate, connect the battery and insert the probe into a container of dry soil. Set R1 to its maximum value then reduce that resistance until the LED begins to flash. The range over which the LED flashes before going out is adjusted using R2.

## WATER-LEVEL SENSING AND CONTROL

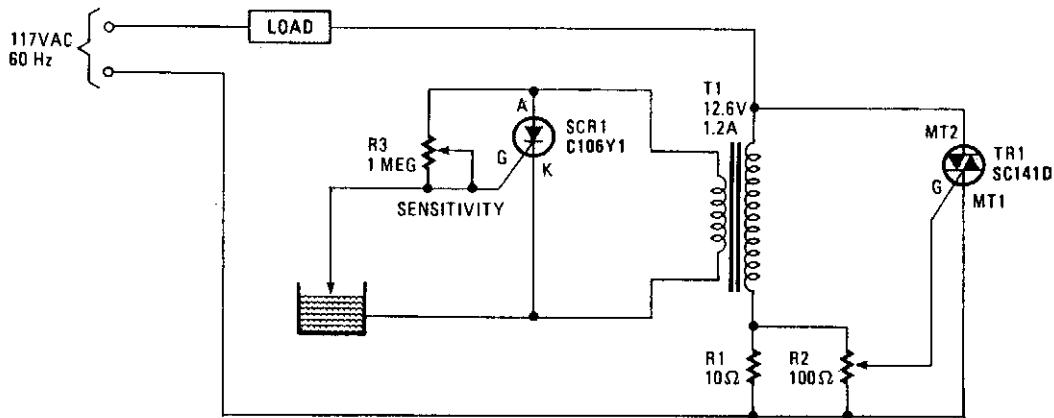


HANDS-ON ELECTRONICS

**Fig. 36-5**

### Circuit Notes

The operation of the circuit is based on the difference in the primary impedance of a transformer when its secondary is loaded and when it is open-circuit. The impedance of the primary of T1 and resistor R1 are in series with the load. The triac's gate-control voltage is developed across parallel resistors R1 and R2. When the water level is low, the probe is out of the water and SCR1 is triggered on. It conducts and imposes a heavy load on transformer T1's secondary winding. That load is reflected back into the primary, gating triac TR1 on, which energizes the load. If the load is an electric value in the water-supply line, it will open and remain open until the water rises and touches the probe, which shorts SCR1's gate and cathode, thereby turning off the SCR1, which effectively open-circuits the secondary. The open-circuit condition—when reflected back to the primary winding—removes the triac's trigger signal, thereby turning the water off. The load may range from a water valve, a relay controlling a pump supplying water for irrigation, or a solenoid valve controlling the water level in a garden lily pond.

## SINGLE CHIP PUMP CONTROLLER

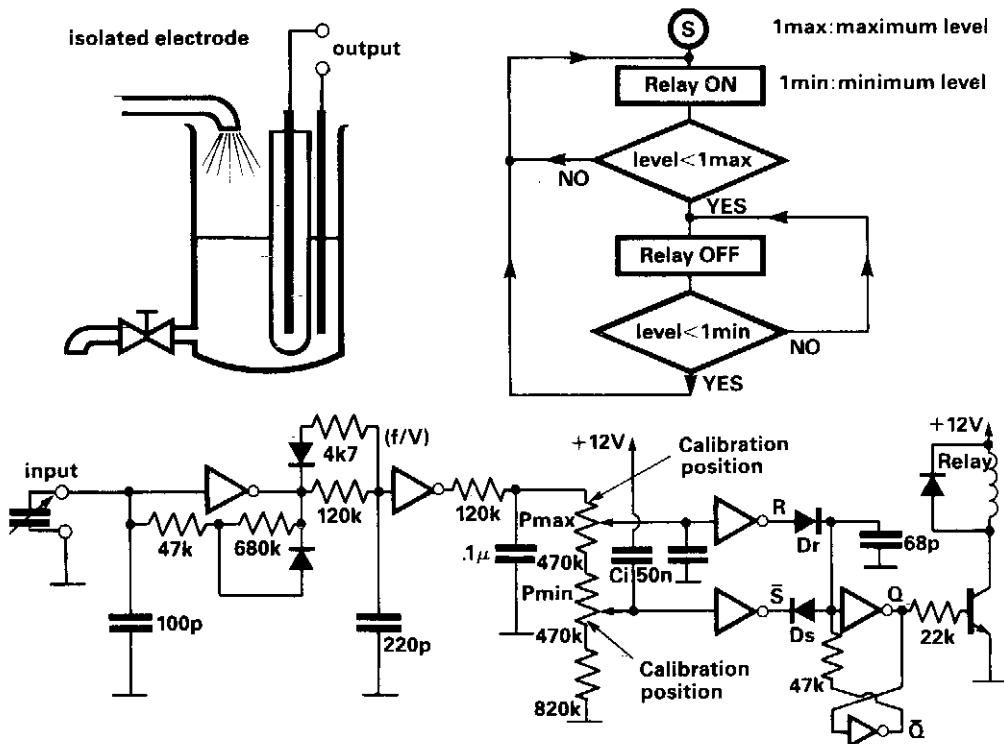


ELECTRONIC ENGINEERING

Fig. 36-6

### Circuit Notes

This circuit controls the level of a tank using a bang-bang controlled electrical pump. The actual level of liquid is measured by a capacitive level-meter. The first inverter performs as a capacitance to frequency converter. It is a Schmitt oscillator and its frequency output decreases as the capacitance increases. The second inverter is a monostable which performs as a frequency to voltage converter ( $f/V$ ). Its output is applied to the maximum and minimum level comparators inputs. Maximum and minimum liquid levels may be set by the potentiometers. The maximum level (1 max) may be preset between the limits: 65 pF less than C (1 max) less than 120 pF. The minimum level is presetable and the limits are: 0 less than C (1 min) less than 25 pF.

## PLANT WATER GAUGE

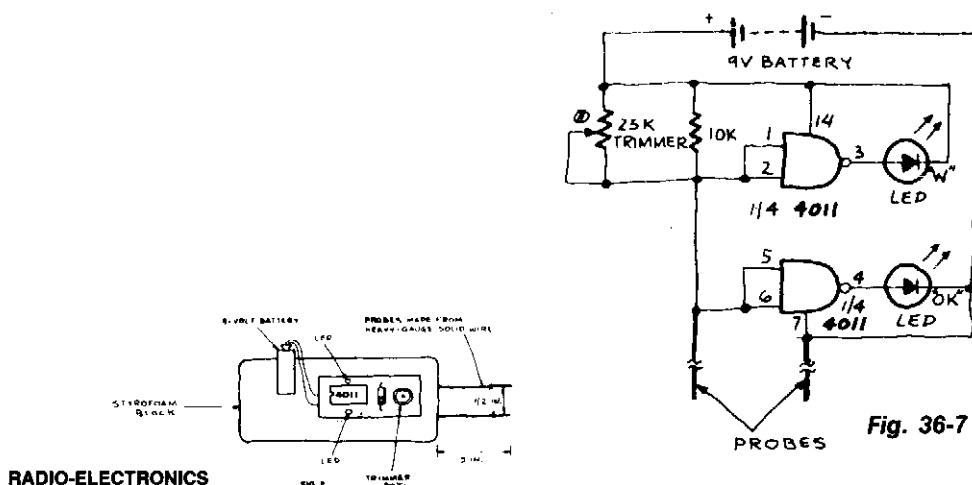

**Fig. 36-7**


RADIO-ELECTRONICS

FIG. 2

### Circuit Notes

To calibrate the gauge, connect the battery and press the probes gently into a pot containing a plant that is just on the verge of needing water (stick it in so that only an inch of the probe is left visible at the top). Turn the potentiometer until the "OK" LED lights and then turn it back to the point where that LED goes out and the "W", or "Water", LED just comes on. The device should now be properly adjusted.

## LIQUID FLOWMETER

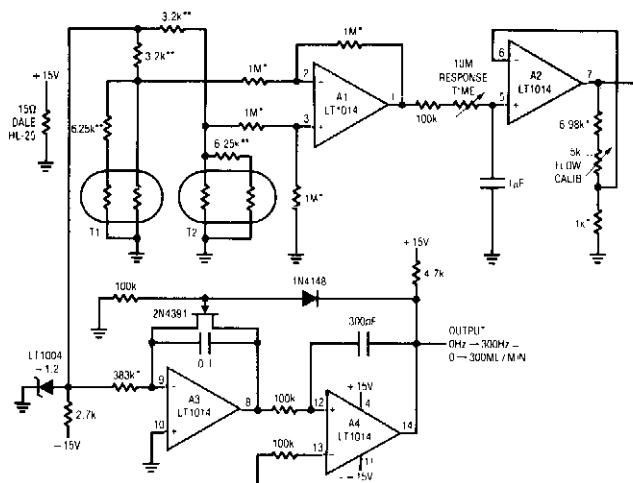

**Fig. 36-8**

LINEAR TECHNOLOGY CORP.

\* 1% FILM RESISTOR  
\*\* SUPPLIED WITH YSI THERMISTOR NETWORK  
T1, T2 YSI THERMISTOR NETWORK = #44201  
FLOW IN PIPE IS INVERSELY PROPORTIONAL TO  
RESISTANCE OF T1-T2 TEMPERATURE DIFFERENCE.  
A1-A2 PROVIDE GAIN A3 A4 PROVIDE LINEARIZED  
FREQUENCY OUTPUT.

# **37**

## **Frequency Meters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Power Frequency Meter  
Low Cost Frequency Indicator

## POWER-FREQUENCY METER

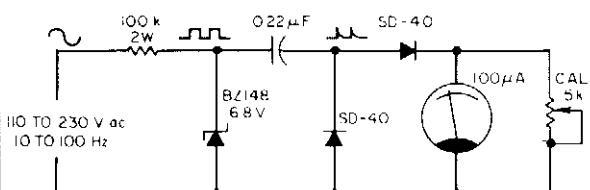


ELECTRONIC DESIGN

**Fig. 37-1**

### Circuit Notes

The meter uses a zener diode to form square waves from input sine waves. After calibration with the 5 k ohm potentiometer, the 100  $\mu$ A meter reads directly in hertz.

## LOW COST FREQUENCY INDICATOR

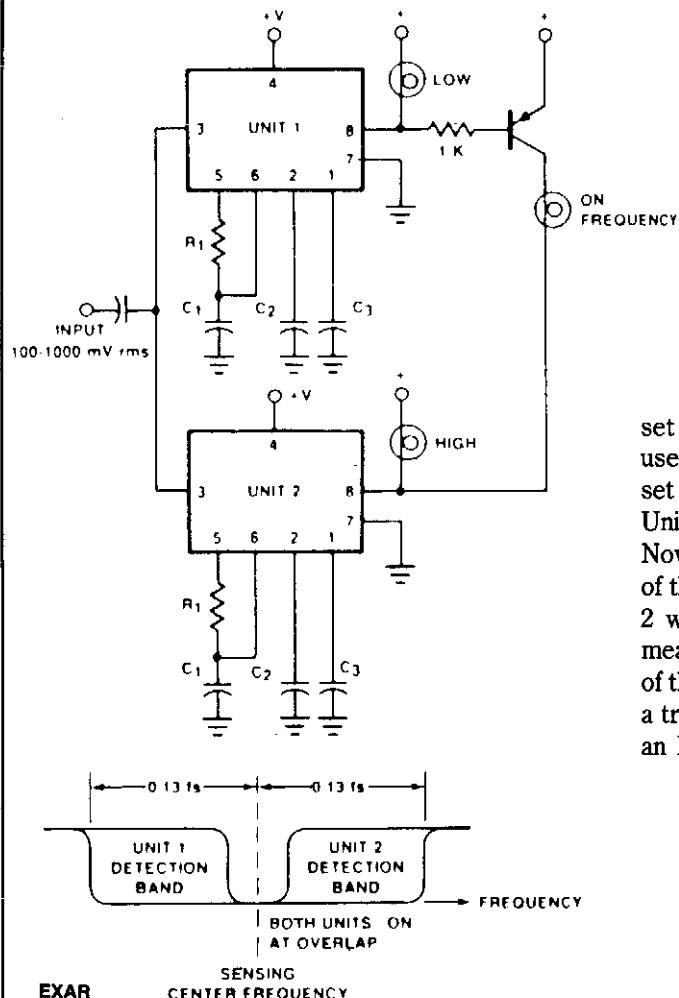

### Circuit Notes

The circuit shows how two tone decoders set up with overlapping detection bands can be used for a go/no go frequency meter. Unit 1 is set 6% above the desired sensing frequency and Unit 2 is set 6% below the desired frequency. Now, if the incoming frequency is within 13% of the desired frequency, either Unit 1 or Unit 2 will give an output. If both units are on, it means that the incoming frequency is within 1% of the desired frequency. Three light bulbs and a transistor allow low cost read-out. The IC is an EXAR 567.

**Fig. 37-2**

# **38**

## **Frequency Multiplier and Divider Circuits**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Nonselective Frequency Tripler Uses Transistor Saturation Characteristics
- Frequency Doubler Works to 1 MHz
- Low Frequency Divider
- Frequency Divider
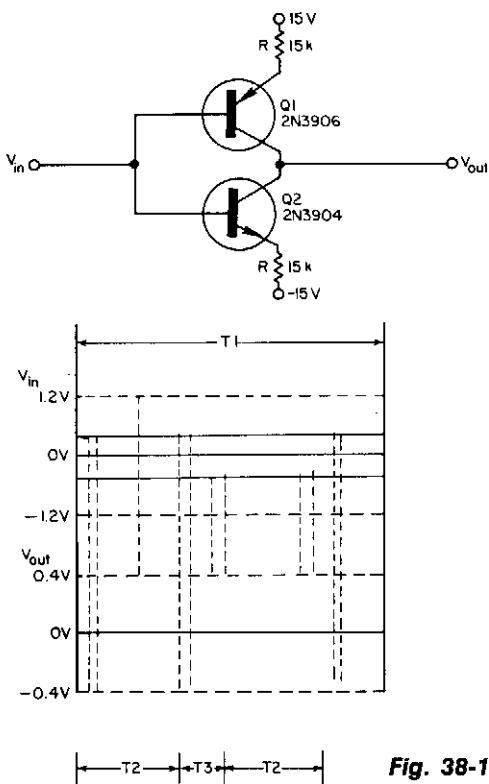
## NONSELECTIVE FREQUENCY TRIPLER USES TRANSISTOR SATURATION CHARACTERISTICS




### Circuit Notes

The turn-on and turn-off characteristics of two complementary transistors can be combined to attain nonselective frequency tripling. The resulting circuit handles any periodic waveform with nonvertical sides. Each input signal peak produces three output signal peaks. The additional peaks occur where the input signal causes saturation of one of the two transistors. The circuit operates over a frequency range from dc to the upper limits of the complementary transistor pair. About the only disadvantage of the circuit is the lack of symmetry of the output signal peaks.

ELECTRONIC DESIGN

**Fig. 38-1**

## FREQUENCY DOUBLER WORKS TO 1 MHz

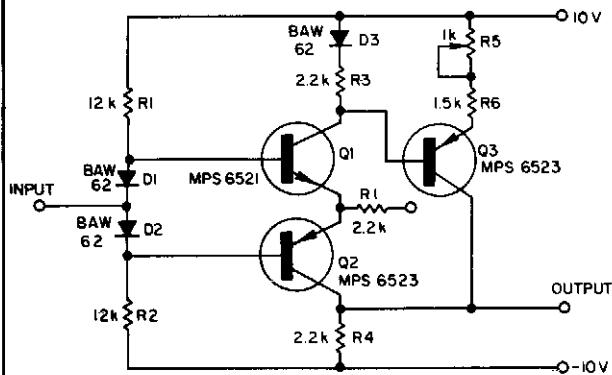


### Circuit Notes

Adding components Q3, D3, and resistors R3 through R6 to a conventional complementary symmetry class AB buffer can double the frequency of an input sine wave.

ELECTRONIC DESIGN

**Fig. 38-2**

## LOW FREQUENCY DIVIDER

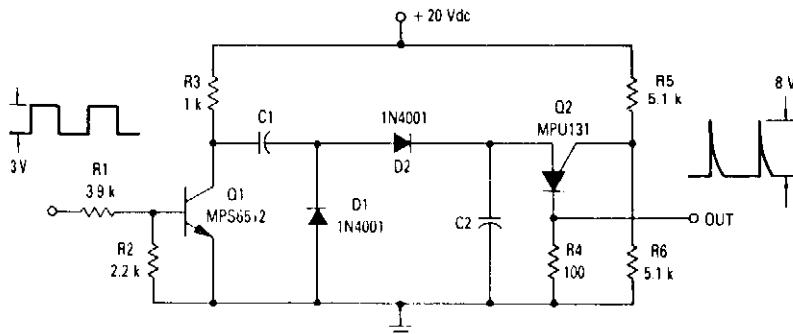

TABLE

<b>C<sub>1</sub></b>	<b>C<sub>2</sub></b>	<b>Division</b>
0.01 $\mu$ F	0.01 $\mu$ F	2
0.01 $\mu$ F	0.02 $\mu$ F	3
0.01 $\mu$ F	0.03 $\mu$ F	4
0.01 $\mu$ F	0.04 $\mu$ F	5
0.01 $\mu$ F	0.05 $\mu$ F	6
0.01 $\mu$ F	0.06 $\mu$ F	7
0.01 $\mu$ F	0.07 $\mu$ F	8
0.01 $\mu$ F	0.08 $\mu$ F	9
0.01 $\mu$ F	0.09 $\mu$ F	10
0.01 $\mu$ F	0.1 $\mu$ F	11

MOTOROLA

*Fig. 38-3*


### Circuit Notes

The ratio of capacitors C1 and C2 determines division. With a positive pulse applied to the base of Q1, assume that C1 = C2 and that C1 and C2 are discharged. When Q1 turns off, both C1 and C2 charge to 10 volts each through R3. On the next pulse to the base of Q1, C1 is again discharged but C2 remains charged to 10 volts. As Q1 turns off this time, C1 and C2 again charge. This time C2 charges to the peak point firing voltage of the PUT causing it to fire. This discharges capacitor C2 and allows capacitor C1 to charge to the line voltage. As soon as C2 discharges and C1 charges, the PUT turns off. The next cycle begins with another positive pulse on the base of Q1 which again discharges C1. The input and output frequency can be approximated by the equation


$$f_{in} = \frac{(C_1 + C_2)}{C_1} f_{out}$$

For a 10 kHz input frequency with an amplitude of 3 volts, the table shows the values for C1 and C2 needed to divide by 2 to 11.

## FREQUENCY DIVIDER

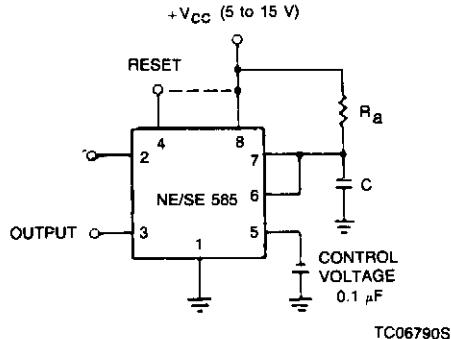

Schematic Diagram

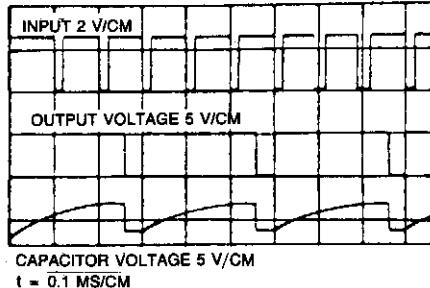

WF14990S  
Expected Waveforms

**SIGNETICS**

**Fig. 38-4**

### Circuit Notes

If the input frequency is known, the timer can easily be used as a frequency divider by adjusting the length of the timing cycle. Figure shows the waveforms of the timer when used as a divide-by-three circuit. This application makes use of the fact that this circuit cannot be retriggered during the timing cycle.

# 39

## Frequency-to-Voltage Converters


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

### Frequency-to-Voltage Converters

## FREQUENCY-TO-VOLTAGE CONVERTERS

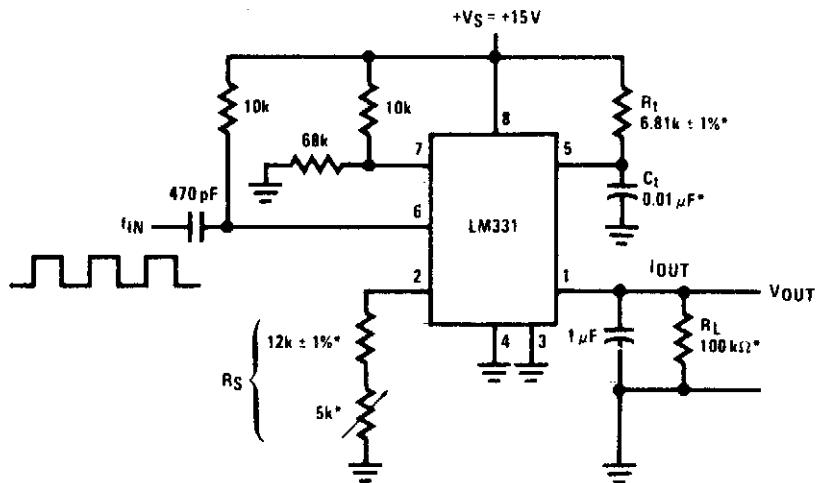

TL/H/5680-7

$$V_{OUT} = f_{IN} \times 2.09V \times \frac{R_L}{R_S} \times (R_1 C_1)$$

\*Use stable components with low temperature coefficients.


### Simple Frequency-to-Voltage Converter, 10 kHz Full-Scale, ± 0.06% Non-Linearity

NATIONAL SEMICONDUCTOR CORP.

Fig. 39-1
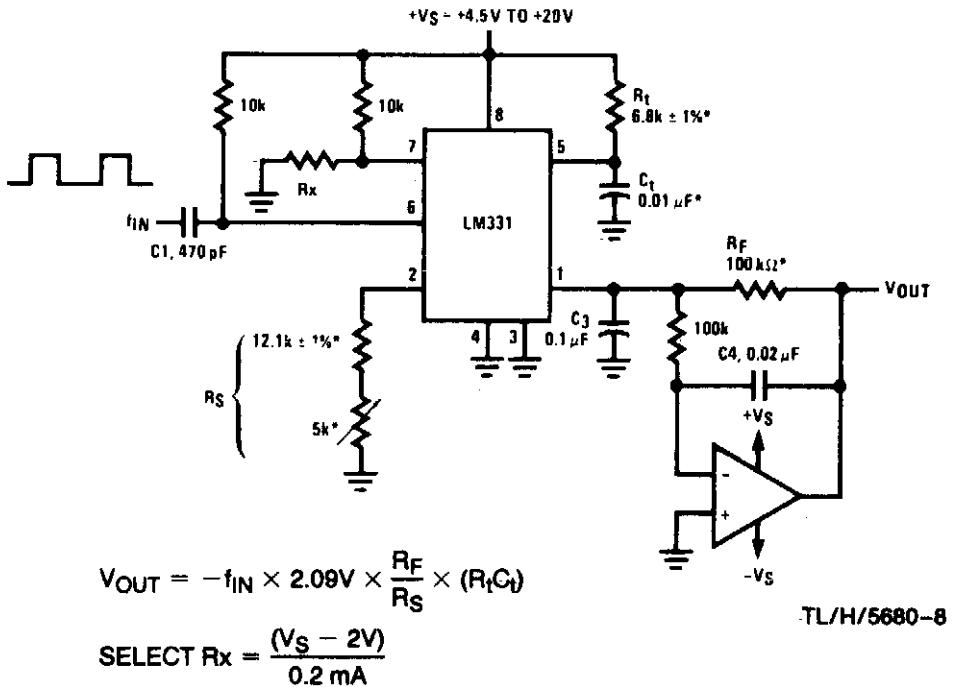
#### Circuit Notes

In these applications, a pulse input at  $f_{IN}$  is differentiated by a C-R network and the negative-going edge at pin 6 causes the input comparator to trigger the timer circuit. Just as with a V-to-F converter, the average current flowing out of pin 1 is  $I_{AVERAGE} = i \times (1.1 R_1 C_1) \times f$ . In this simple circuit, this current is filtered in the network  $R_L = 100 \text{ k ohm}$  and  $1 \mu\text{F}$ . The ripple will be less than 10 mV peak, but the response will be slow, with a 0.1 second time constant, and settling of 0.7 second to 0.1%



\*Use stable components with low temperature coefficients.

### Precision Frequency-to-Voltage Converter, 10 kHz Full-Scale with 2-Pole Filter, $\pm 0.01\%$ Non-Linearity Maximum

accuracy. In the precision circuit, an operational amplifier provides a buffered output and also acts as a 2-pole filter. The ripple will be less than 5 mV peak for all frequencies above 1 kHz, and the response time will be much quicker than in Part 1. However, for input frequencies below 200 Hz, this circuit will have worse ripple than the figure. The engineering of the filter time-constants to get adequate response and small enough ripple simply requires a study of the compromises to be made. Inherently, V-to-F converter response can be fast, but F-to-V response cannot.

# **40**

## **Function Generator Circuits**

---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Quad Op Amp Generates Four Different  
Synchronized Waveforms Simultaneously  
A Sine/Cosine Generator for 0.1-10 kHz  
Oscillator or Amplifier with Wide Frequency Range  
Linear Triangle/Square Wave VCO  
Circuit for Multiplying Pulse Widths  
Programmable Voltage Controlled Frequency  
Synthesizer  
Emitter-Coupled RC Oscillator  
Voltage Controlled High Speed One Shot  
Ramp Generator with Variable Reset Level

555 Astable with Low Duty Cycle  
Monostable Using Video Amplifier and Comparator  
UJT Monostable Circuit Insensitive to Change in  
Bias Voltage  
Astable Multivibrator  
Waveform Generator  
Linear Ramp Generator  
Function Generator  
Waveform Generator  
Single Supply Function Generator  
Precise Wave Generator

## QUAD OP AMP GENERATES FOUR DIFFERENT SYNCHRONIZED WAVEFORMS SIMULTANEOUSLY

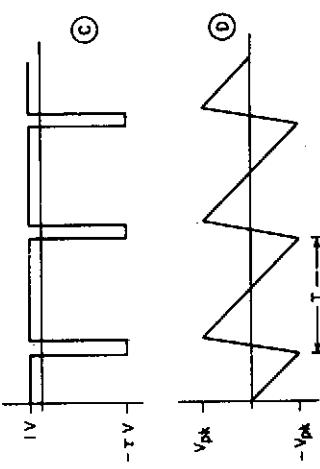
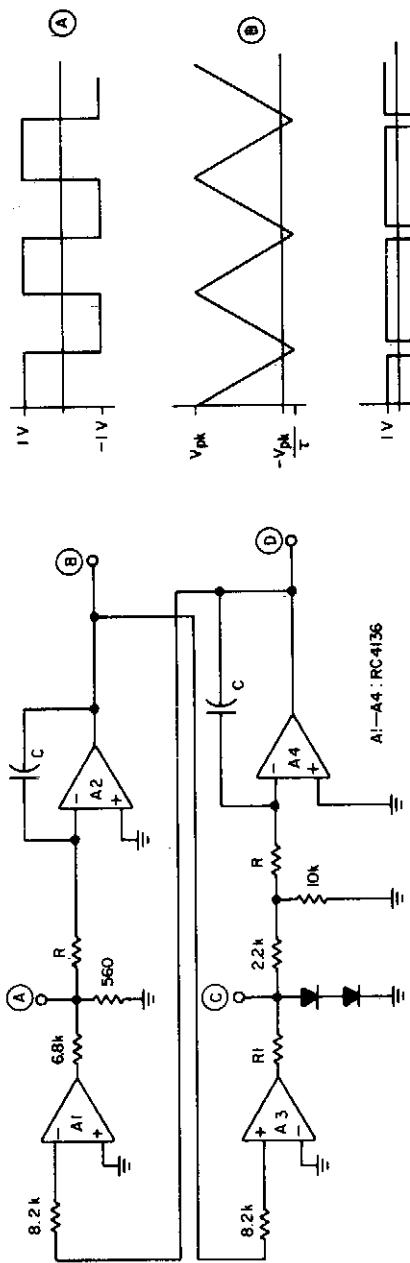


Fig. 40-1


ELECTRONIC DESIGN

$R_1(k\Omega)$	$T$	Duty cycle (%)
0.3	10.4	8.8
0.5	10.2	8.9
1	9.85	9.2
4	8.0	11.1
10	5.86	14.6
20	4.04	19.84
50	2.09	32.4
100	1.16	46.30
117.8	1	50


### Circuit Notes

A quad op amp can simultaneously generate four synchronized waveforms. The two comparators (A1 and A3) produce square and pulse waves, while the two integrators (A2 and A4) give triangular and sawtooth waves. Resistor R1 sets the duty cycle and the frequency, along with resistors R and capacitors C.
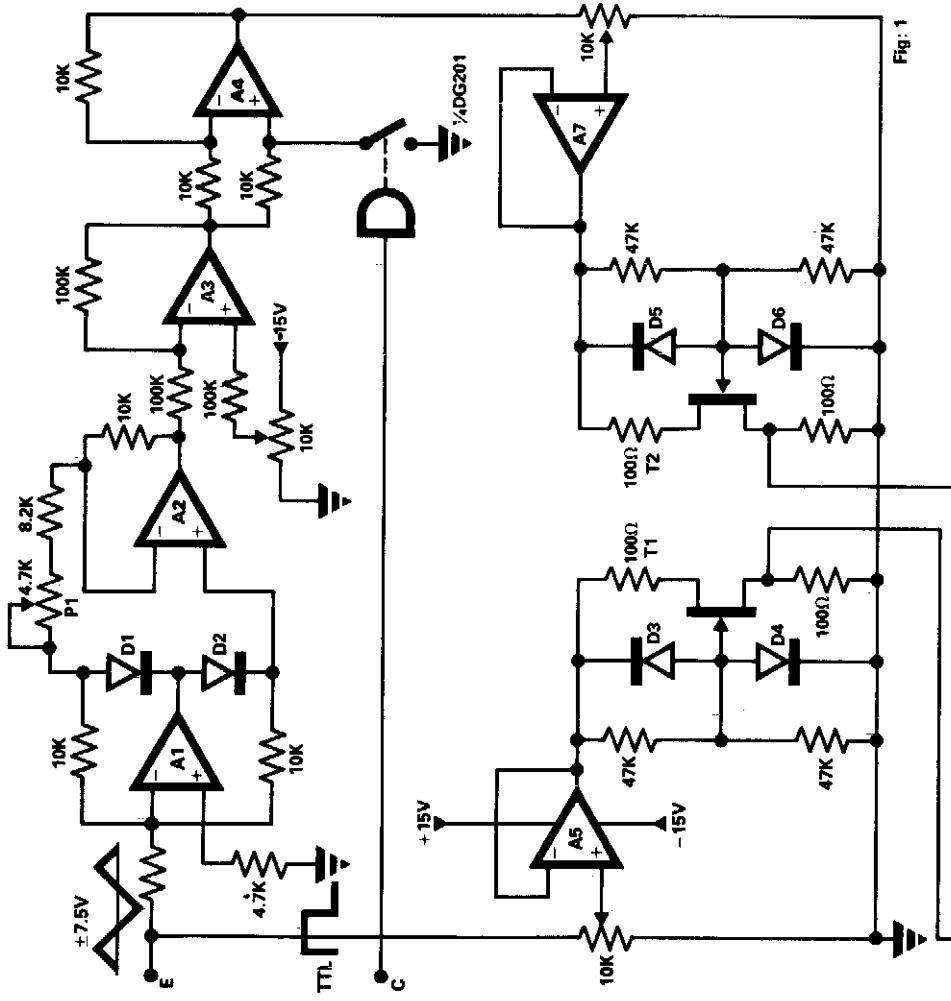
## A SINE/COSINE GENERATOR FOR 0.1 - 10 kHz



四

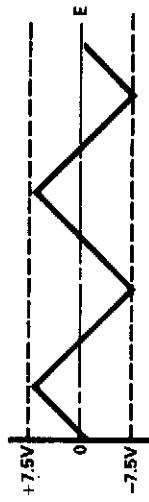

**Fig. 40-2**

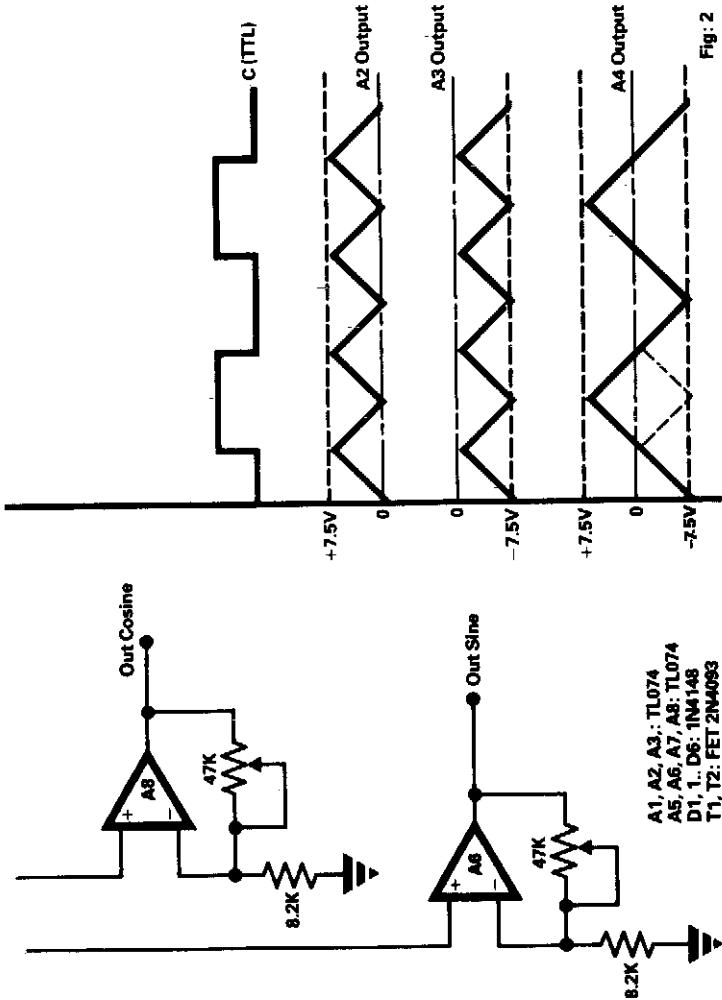


Fig. 2


### Circuit Notes

The scheme presented delivers waveforms from any function generator producing a triangular output and a synchronized TTL square wave. A1 and A2 act as a two-phase current rectifier by inverting the negative voltage appearing at the input of A1.

Positive input: Both A1 and A2 work as unity gain followers, D1 and D2 being in the off-state.

Negative input: A1 has a  $-1/3$  gain (D1 off and D2 on), A2 has a  $+1/3$  gain and the total voltage transfer is  $-1$  between output and input. P1 allows a fine trimming of the  $-1$  gain for the negative input signals. A3 adds a continuous voltage to the rectified positive signal in order to attack A4 which acts as a  $\pm$  multiplier commanded by the TTL input through the analog switch. The signal polarity is reconstructed and the output of A4 delivers a triangular waveform shifted by  $90^\circ$  with respect to the input signal, Fig. 2. The original and the shifted voltages are fed into the triangle to sine converters through A5 and A7 working as impedance converters. Over the frequency dynamic ranges from 0.1 Hz to 10 kHz, the phase shift is constant and the distortion on the sine voltage is less than 1%.
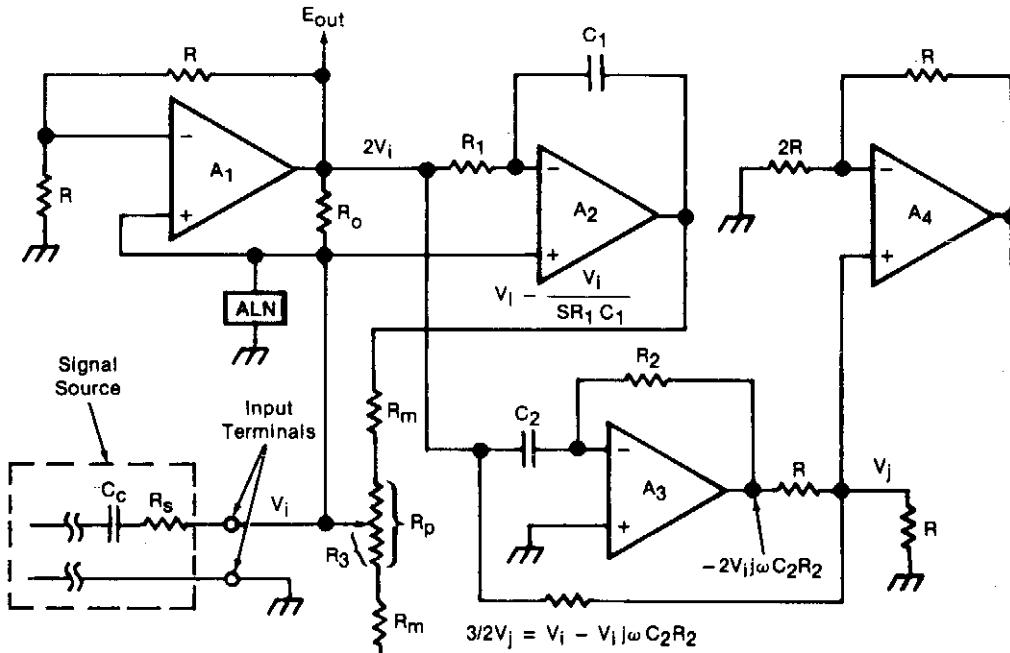
## OSCILLATOR OR AMPLIFIER WITH WIDE FREQUENCY RANGE



NASA


NOTES: 1. A<sub>1</sub>, A<sub>2</sub>, A<sub>3</sub>, and A<sub>4</sub> are operational amplifiers  
 2. ALN = Amplitude-Limiting Network

*Fig. 40-3*

### Circuit Notes

An oscillator/amplifier is resistively tunable over a wide frequency range. Feedback circuits containing operational amplifiers, resistors, and capacitors synthesize the electrical effects of an inductance and capacitance in parallel between the input terminals. The synthetic inductance and capacitance, and, therefore, the resonant frequency of the input admittance, are adjusted by changing a potentiometer setting. The input signal is introduced in parallel to the noninverting input terminals of operational amplifiers A<sub>1</sub> and A<sub>2</sub> and to the potentiometer cursor. The voltages produced by the feedback circuits in response to input voltage V<sub>i</sub> are indicated at the various circuit nodes.

### LINEAR TRIANGLE/SQUARE WAVE VCO

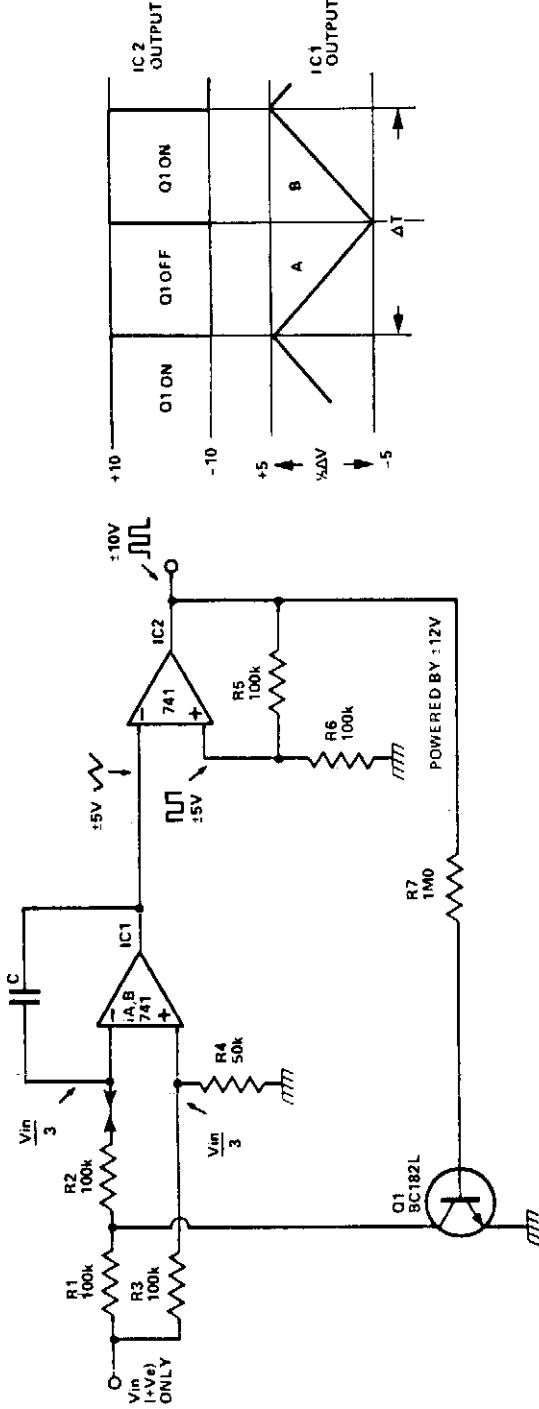



ELECTRONICS TODAY INTERNATIONAL

*Fig. 40-4*

### Circuit Notes

The VCO has two buffered outputs; a triangle wave and a square wave. Frequency is dependent on the output voltage swing of the Schmitt trigger, IC2. Superior performance can be obtained by replacing Q1 with a switching FET. Fast FET op amps will improve high frequency performance.

### CIRCUIT FOR MULTIPLYING PULSE WIDTHS

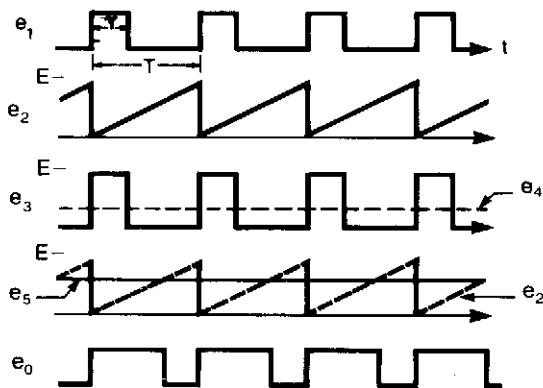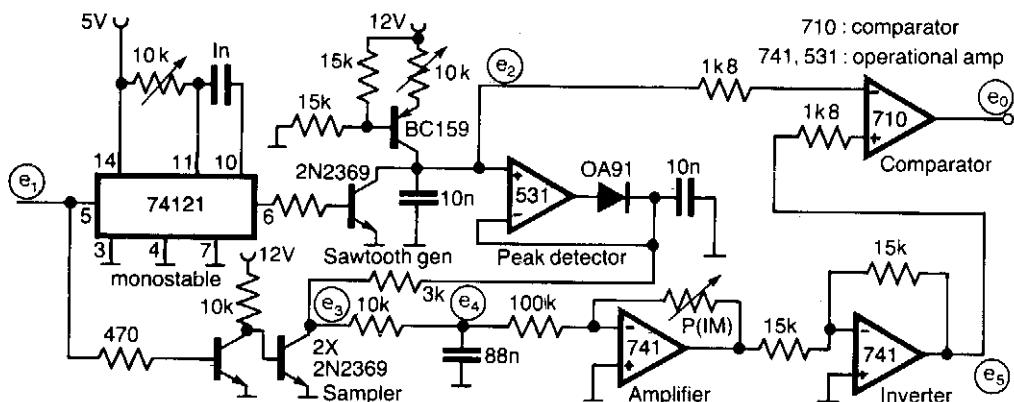


ELECTRONIC ENGINEERING

Fig. 40-5

#### Circuit Notes

A circuit for multiplying the width of incoming pulses by a factor greater or less than unity is simple to build and has the feature that the multiplying factor can be selected by adjusting one potentiometer only. The multiplying factor is determined by setting the potentiometer  $P$  in the feedback of a 741 amplifier. The input pulses  $e_1$  of width  $\tau$  and repetition period  $T$  is used to trigger a sawtooth generator at its rising edges to produce the waveform  $e_2$  having a peak value of  $(E)$  volt. This peak value is then sampled by the input pulses to generate the pulse train  $e_3$  having an average value of  $e_4 (= E \tau/T)$  which is proportional to  $\tau$  and independent on  $T$ . The dc voltage  $e_4$  is amplified by a factor  $k$  and compared with sawtooth waveform  $e_2$  giving output pulses of duration  $k\tau$ . The circuit is capable of operating over the frequency range 10 kHz - 100 kHz.
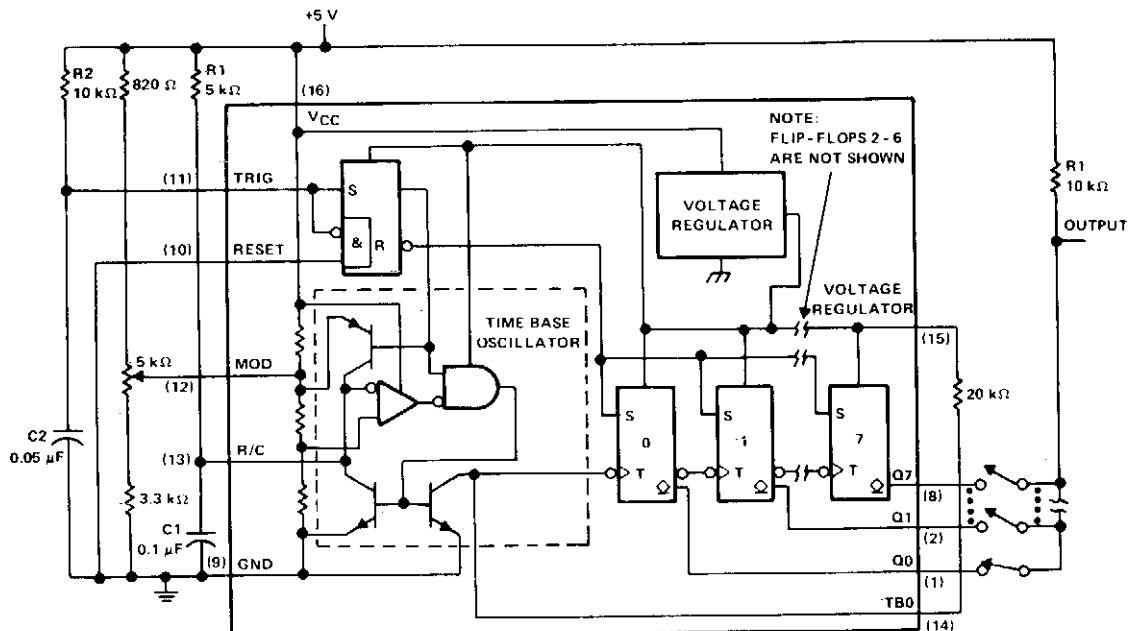
## PROGRAMMABLE VOLTAGE CONTROLLED FREQUENCY SYNTHESIZER




TEXAS INSTRUMENTS

**Fig. 40-6**

### Circuit Notes

The  $\mu$ A2240 consists of four basic circuit elements: (1) a time-base oscillator, (2) an eight-bit counter, (3) a control flip-flop, and (4) a voltage regulator. The basic frequency of the time-base oscillator (TBO) is set by the external time constant determined by the values of R1 and C1 ( $1?R1C1 = 2 \text{ kHz}$ ). The open-collector output of the TBO is connected to the regulator output via a  $20 \text{ k}\Omega$  pull-up resistor, and drives the input to the eight-bit counter. At power-up, a positive trigger pulse is detected across C2 which starts the TBO and sets all counter outputs to a low state. Once the  $\mu$ A2240 is initially triggered, any further trigger inputs are ignored until it is reset. In this astable operation, the  $\mu$ A2240 will free-run from the time it is triggered until it receives an external reset signal. Up to 255 discrete frequencies can be synthesized by connecting different counter outputs.


### EMITTER-COUPLED RC OSCILLATOR

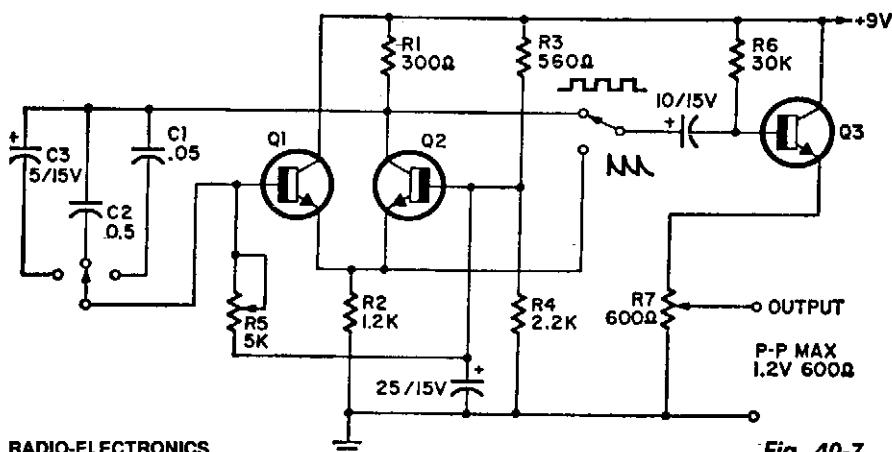

### Circuit Notes

The circuit covers 15 Hz-30 kHz and is useful as a function generator. The 2N2926 or equivalent transistors can be used.
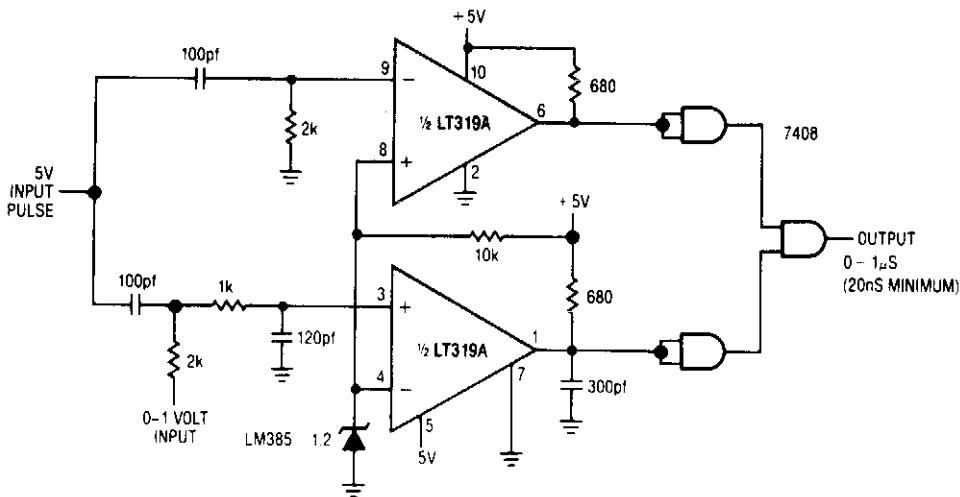
### VOLTAGE CONTROLLED HIGH SPEED ONE SHOT



LINEAR TECHNOLOGY CORP.

*Fig. 40-8*

## RAMP GENERATOR WITH VARIABLE RESET LEVEL

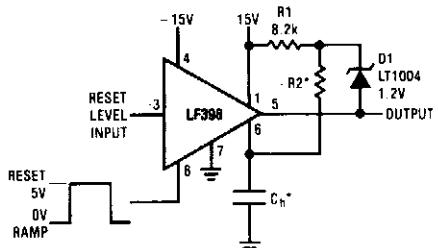


Fig. 40-9

\*SELECT FOR RAMP RATE  $\Delta V = 1.2V$   
 $R \geq 10k$

LINEAR TECHNOLOGY CORP.

## 555 ASTABLE WITH LOW DUTY CYCLE

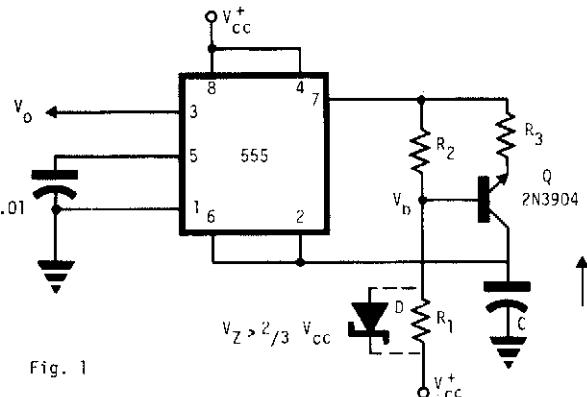


Fig. 1

ELECTRONIC ENGINEERING

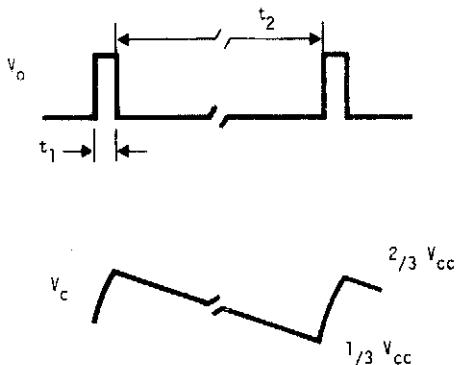


Fig. 40-10

### Circuit Notes

This free-running multivibrator uses an external current sink to discharge the timing capacitor, C. Therefore, interval t<sub>2</sub> may easily be  $1000 \times$  the pulse duration, t<sub>1</sub>, which defines a positive output. Capacitor voltage, V<sub>C</sub>, is a negative going ramp with exponential rise during the pulse output periods.

### MONOSTABLE USING VIDEO AMPLIFIER AND COMPARATOR

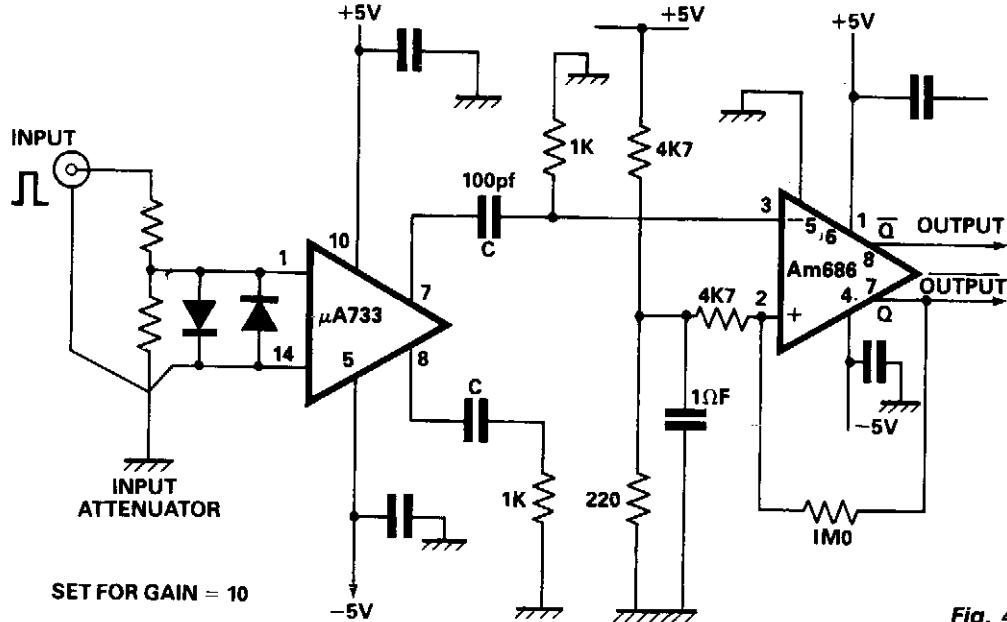


Fig. 40-11

ELECTRONIC ENGINEERING

#### Circuit Notes

The output of a video amplifier is differentiated before being fed to a Schottky comparator. The propagation delay is reduced to typically 10ns. The output pulse width is set by the value of C, 100pf giving a pulse of about 90ns duration.

### UJT MONOSTABLE CIRCUIT INSENSITIVE TO CHANGE IN BIAS VOLTAGE

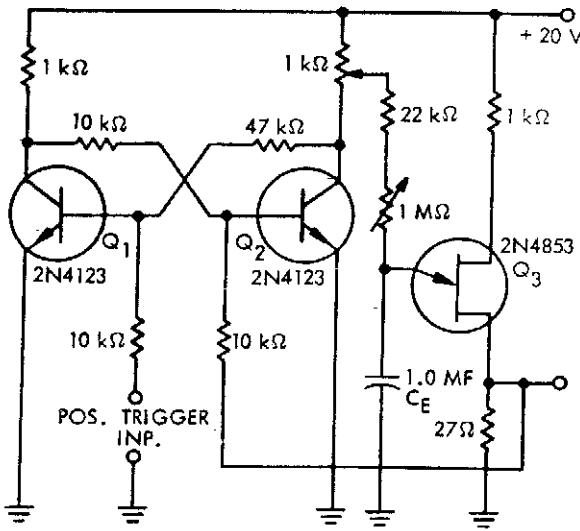
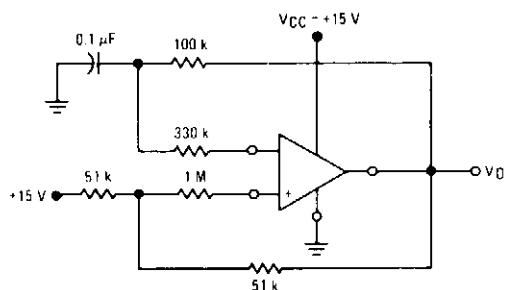


Fig. 40-12

## ASTABLE MULTIVIBRATOR

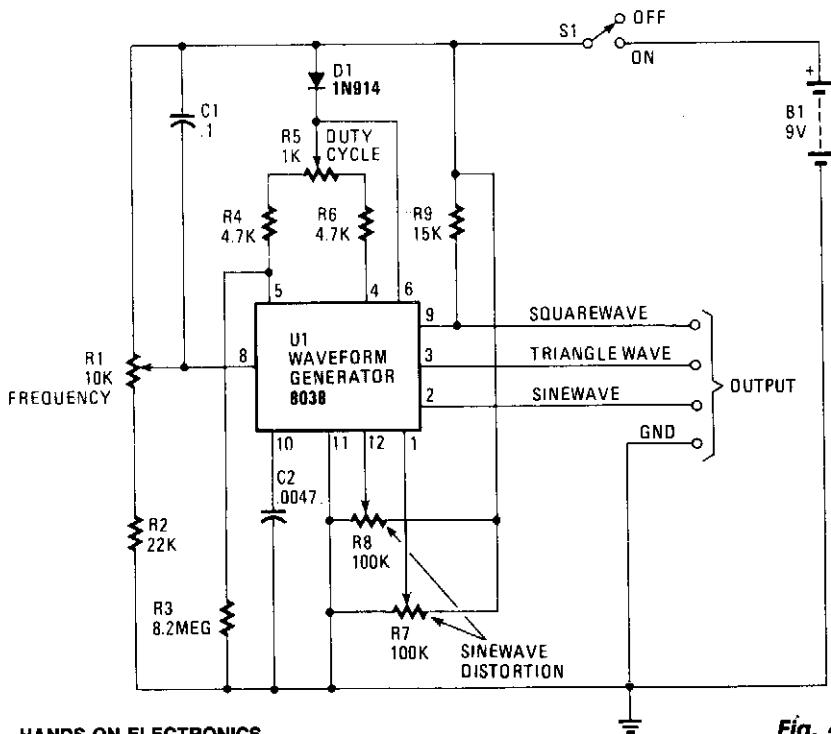


**Fig. 40-13**

IC = MC3301

MOTOROLA INC.

## WAVEFORM GENERATOR




**Fig. 40-14**

HANDS-ON ELECTRONICS

### Circuit Notes

The circuit is designed around the Intersil 8038CC. Frequency range is approximately 20 Hz to 20 kHz—a tuning range of 1000:1 with a single control. The output frequency depends on the value of C2 and on the setting of potentiometer R1. Other values of C2 change the frequency range. Increase the value of C2 to lower the frequency. The lowest possible frequency is around .001 Hz and the highest is around 300 kHz.

### LINEAR RAMP GENERATOR

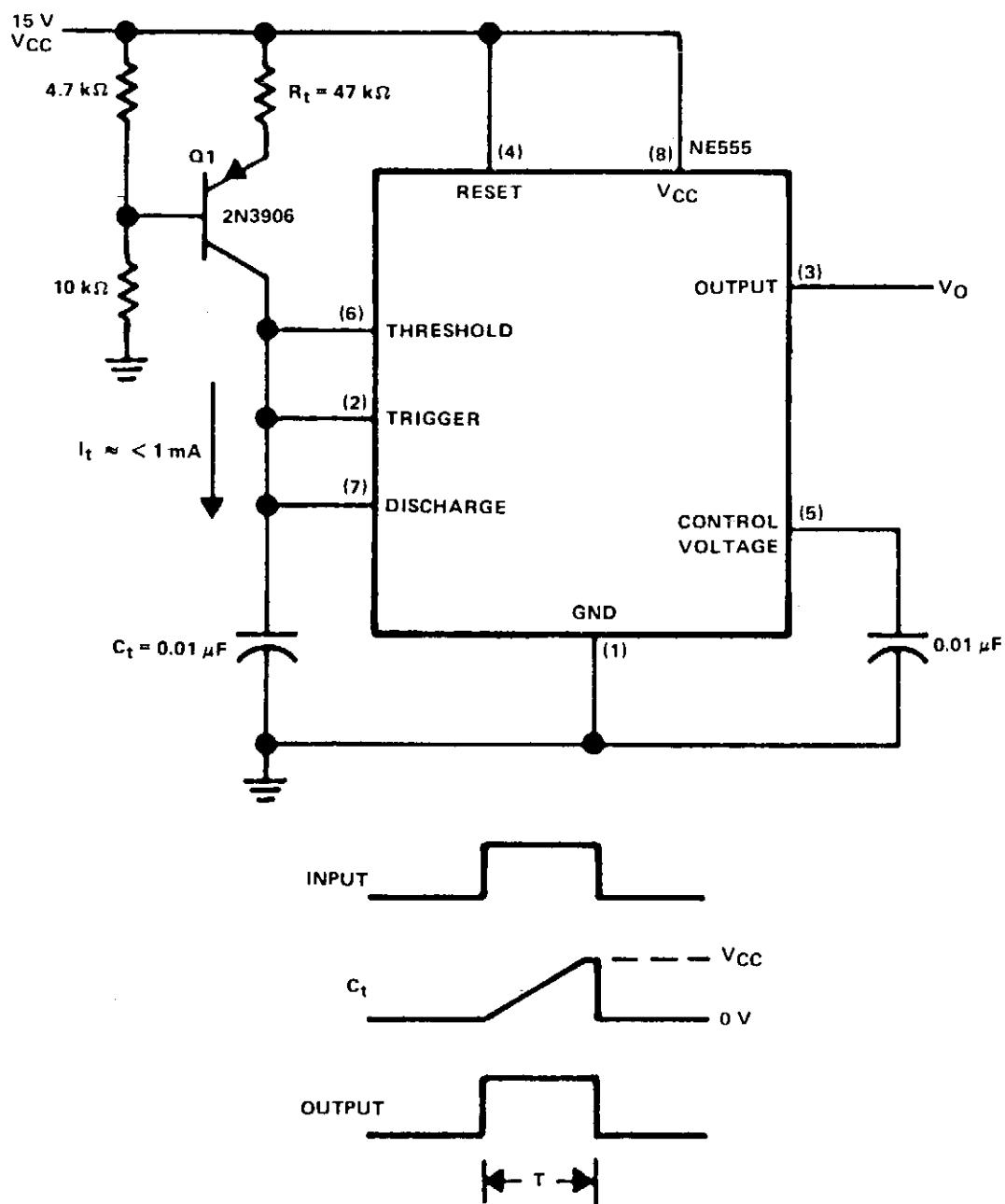

TEXAS INSTRUMENTS

*Fig. 40-15*


## LINEAR RAMP GENERATOR, Continued.

### Circuit Notes

The linear charging ramp is most useful where linear control of voltage is required. Some possible applications are a long period voltage controlled timer, a voltage to pulse width converter, or a linear pulse width modulator. Q1 is the current source transistor, supplying constant current to the timing capacitor  $C_t$ . When the timer is triggered, the clamp on  $C_t$  is removed and  $C_t$  charges linearly toward  $V_{CC}$  by virtue of the constant current supplied by Q1. The threshold at pin 6 is  $\frac{1}{3} V_{CC}$ ; here, it is termed  $V_C$ . When the voltage across  $C_t$  reaches  $V_C$  volts, the timing cycle ends. The timing expression for output pulse with T is:

In general,  $I_t$  should be 1 mA value compatible with the NE555.


## FUNCTION GENERATOR

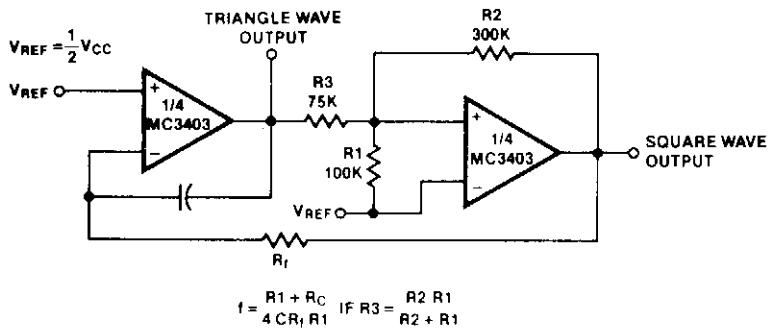

SIGNETICS

*Fig. 40-16*

## WAVEFORM GENERATOR

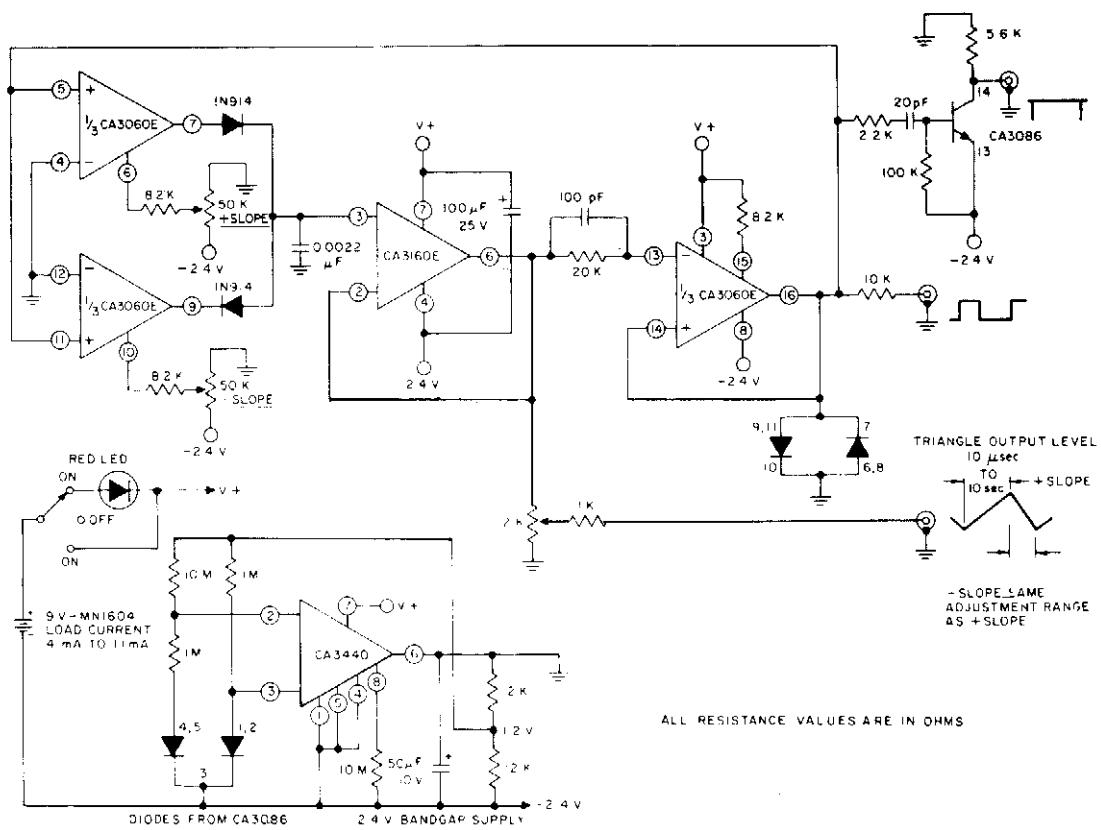


GENERAL ELECTRIC/RCA

Fig. 40-17

### Circuit Notes

The circuit uses a CA3060 triple OTA (two units serve as switched current generators controlled by a third amplifier). A CA3160 BiMOS op amp serves as a voltage follower to buffer the  $0.0022 \mu\text{F}$  integrating capacitor. The circuit has an adjustment range of 1,000,000:1 and a timing range of  $20 \mu\text{s}$  to  $20 \text{ sec}$ . The "ON-OFF" switch actuates an LED that serves as both a pilot light and a low-battery indicator. The LED extends battery life, since it drops battery voltage to the circuit by approximately 1.2 volts, thus reducing supply current.

## SINGLE SUPPLY FUNCTION GENERATOR

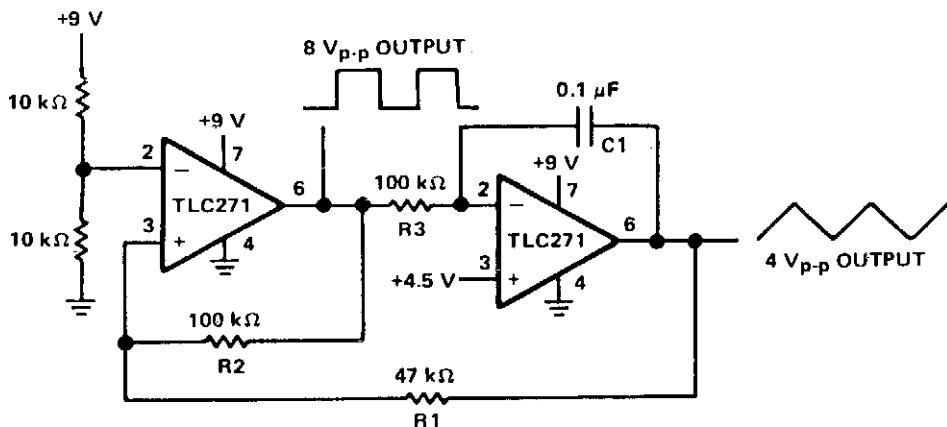

TEXAS INSTRUMENTS

Fig. 40-18


### Circuit Notes

The circuit has both square-wave and triangle-wave output. The left section is similar in function to a comparator circuit that uses positive feedback for hysteresis. The inverting input is biased at one-half the  $V_{CC}$  voltage by resistors R4 and R5. The output is fed back to the non-inverting input of the first stage to control the frequency. The amplitude of the square wave is the output swing of the first stage, which is 8 V peak-to-peak. The second stage is basically an op amp integrator. The resistor R3 is the input element and capacitor C1 is the feedback element. The ratio R1/R2 sets the amplitude of the triangle wave, as referenced to the square-wave output. For both waveforms, the frequency of oscillation can be determined by the equation:

$$f_0 = \frac{1}{4R_3C_1} \frac{R_2}{R_1}$$

The output frequency is approximately 50 Hz with the given components.

## PRECISE WAVE GENERATOR

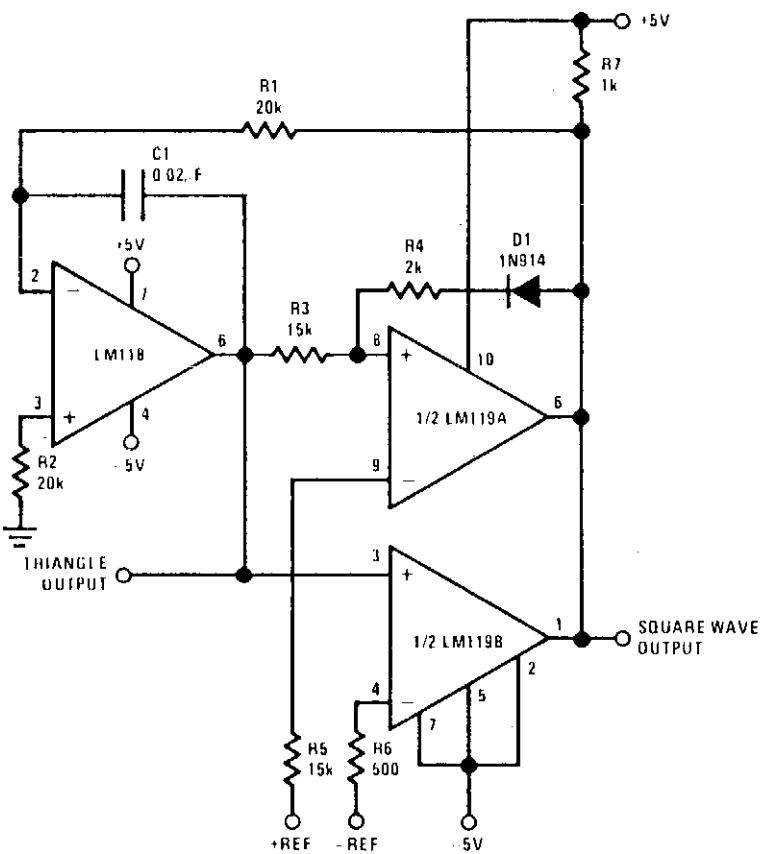

NATIONAL SEMICONDUCTOR

*Fig. 40-19*

### Circuit Notes

The positive and negative peak amplitude is controllable to an accuracy of about  $\pm 0.01$  V by a dc input. Also, the output frequency and symmetry are easily adjustable. The oscillator consists of an integrator and two comparators—one comparator sets the positive peak and the other the negative peak of the triangle wave. If R1 is replaced by a potentiometer, the frequency can be varied over at least a 10 to 1 range without affecting amplitude. Symmetry is also adjustable by connecting a 50 kΩ resistor from the inverting input of the LM118 to the arm of the 1 kΩ potentiometer. The ends of the potentiometer are connected across the supplies. Current for the resistor either adds or subtracts from the current through R1, changing the ramp time.

# **41**

## **Games**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Electronic Roulette  
Lie Detector

## ELECTRONIC ROULETTE

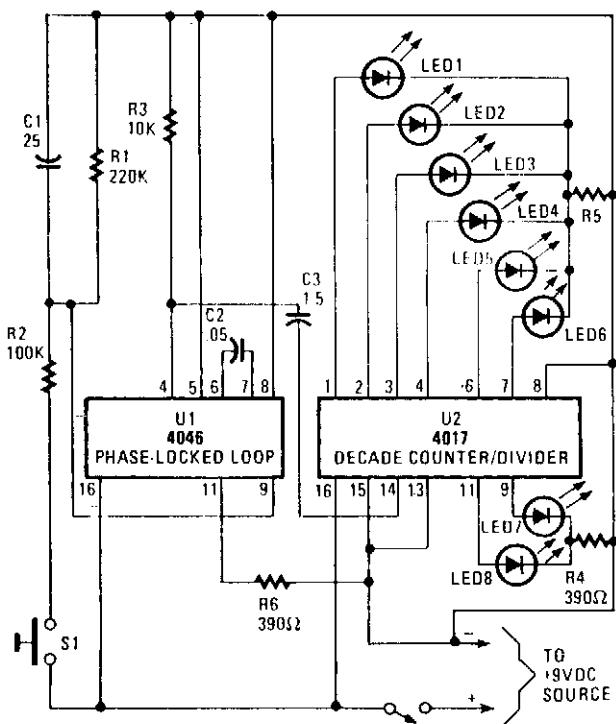

**Fig. 41-1**

### Circuit Notes

U1 (a 4046 PLL containing a voltage controlled oscillator or VCO, two phase comparators, a source follower, and a Zener diode) is used to produce a low-frequency, pulsed output of about 40 Hz. The VCO's frequency range is determined by R6 and C2, which can be altered by varying the voltage at pin 9. The rising voltage causes the frequency to rise from zero to threshold and remain at that frequency as long as S1 is closed. When S1 is opened, C1 discharges slowly through R1 to ground and the voltage falls toward zero. That produces a decreasing pulse rate. The output of U1 at pin 4 is connected to the clock input of U2 (a 4017 decade decoder/driver) at pin 14 via C3. U2 sequentially advances through each of its ten outputs (0 to 9)—pins 1 to 7, and 9 to 11—with each input pulse. As each output goes high, its associated LED is lighted, and extinguished when it returns to the low state. Only eight outputs are used in the circuit, giving two numbers to the spinner of the house. The circuit can be set up so that the LED's lights sequence or you can use some staggered combination; the LEDs grouped in a straight line or a circle.

## LIE DETECTOR

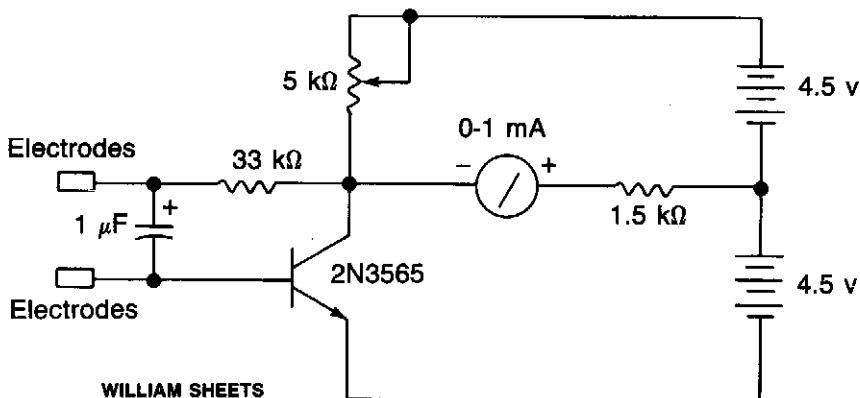


Fig. 41-2

### Circuit Notes

The two probes shown are held in the hands and the skin resistance applies bias to the transistor. The  $5\text{ k}\Omega$  pot is set for zero deflection on the meter. When the "subject" is embarrassed or lies, sweating on the hands takes place, increasing the bias to the transistor and upsetting the bridge balance.

# **42**


## **Gas and Smoke Detectors**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Gas and Vapor Detector  
Toxic Gas Detector  
Gas Analyzer

## GAS AND VAPOR DETECTOR

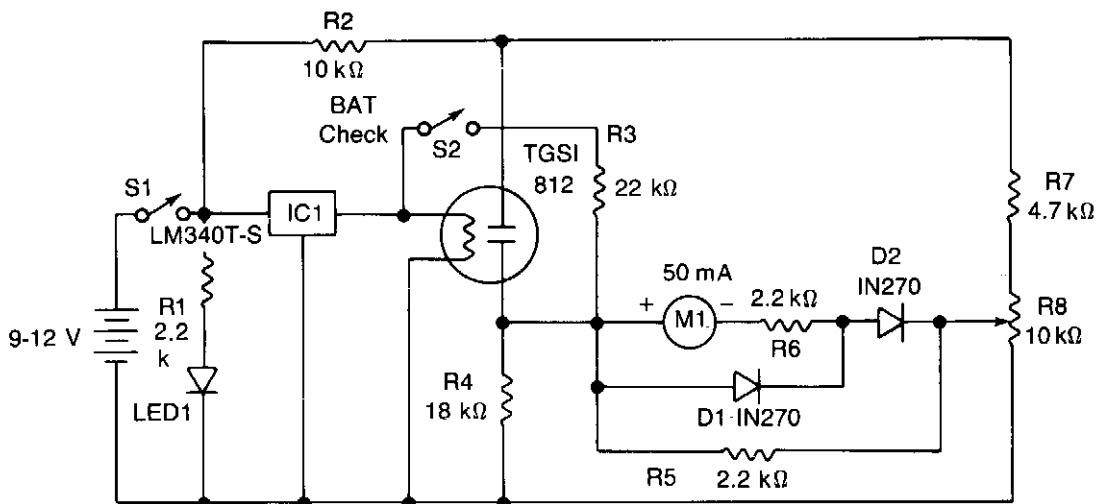


WILLIAM SHEETS

*Fig. 42-1*

### Circuit Notes

The power drain is approximately 150 mA. IC1 provides a regulated 5-volt supply for the filament heater of the sensor. The gas sensitive element is connected as one arm of a resistance bridge consisting of R4, R7, R8 and the meter M1 with its associated resistors R5 and R6. The bridge can be balanced by adjusting R8 so that no current flows through the meter. A change in the sensor's resistance, caused by detection of noxious gases, will unbalance the circuit and deflect the meter. Diodes D1, D2 and resistor R5 protect the meter from overload while R6 determines overall sensitivity. R2 limits the current through the sensor; R1 and LED1 indicate that the circuit is working, so that you do not drain the battery leaving the unit on inadvertently; R3 and S2 give a battery level check.

## TOXIC GAS DETECTOR

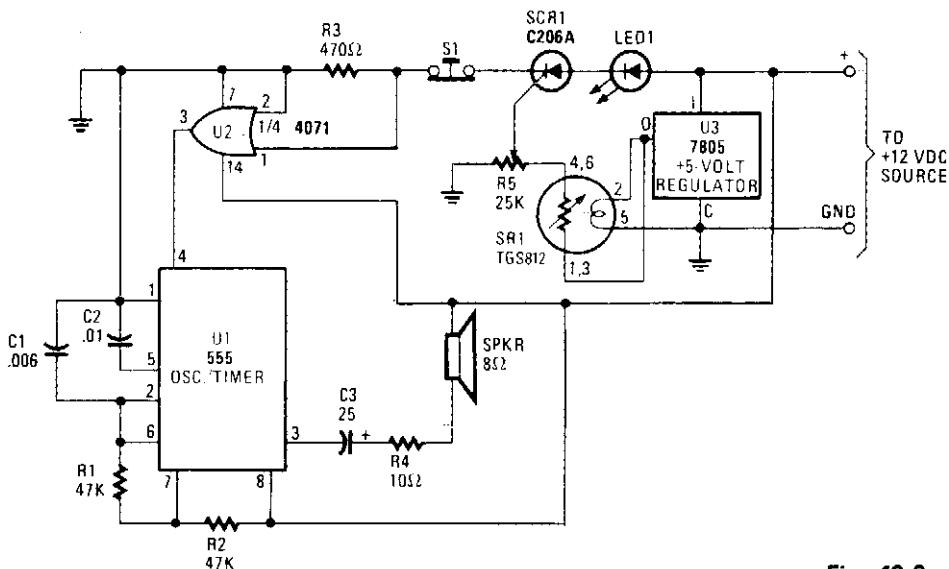

**Fig. 42-2**

**HANDS-ON ELECTRONICS**

### Circuit Notes

The major device in the circuit is SR1 (a TGS812 toxic-gas sensor manufactured by Figaro Engineering Inc.) The gas-sensitive semiconductor (acting like a variable resistor in the presence of toxic gas) decreases in electrical resistance when gaseous toxins are absorbed from the sensor surface. A 25,000 ohm potentiometer (R5) connected to the sensor serves as a load, voltage-dividing network, and sensitivity control and has its center tap connected to the gate of SCR1. When toxic fumes come in contact with the sensor, decreasing its electrical resistance, current flows through the load (potentiometer R5). The voltage developed across the wiper of R5, which is connected to the gate of SCR1, triggers the SCR into conduction. With SCR1 now conducting, pin 1-volt supply for the semiconductor elements of the TGS812 in spite of the suggested 10 volts, thus reducing the standby current. A 7805 regulator is used to meet the 5-volt requirement for the heater and semiconductor elements.

## GAS ANALYZER

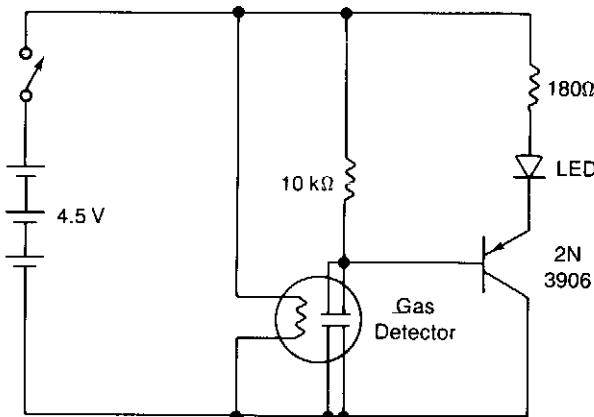


Fig. 42-3

WILLIAM SHEETS

### Circuit Notes

The circuit shows a simple yes/no gas detector. Three 1.5-V D cells are used as a power supply, with S1 acting as an on/off switch. The heater is energized directly from the battery, while the electrodes are in series with a 10 k resistor. The voltage across this resistor is monitored by a pnp transistor. When the sensor is in clean air, the resistance between the electrodes is about 40 k, so that only about 0.9 V is dropped across the 10 k resistor. This is insufficient to turn on the transistor, because of the extra 1.6 V required to forward bias the light emitting diode (LED) in series with the emitter. When the sensor comes in contact with contaminated air, the resistance starts to fall, increasing the voltage dropped across the 10 k resistor. When the sensor resistance falls to about 10 k or less, the transistor starts to turn on, current passes through the LED, causing it to emit. The 180 ohm resistor limits the current through the LED to a safe value.

## **43**

# **Hall Effect Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Angle of Rotation Detector  
Door Open Alarm
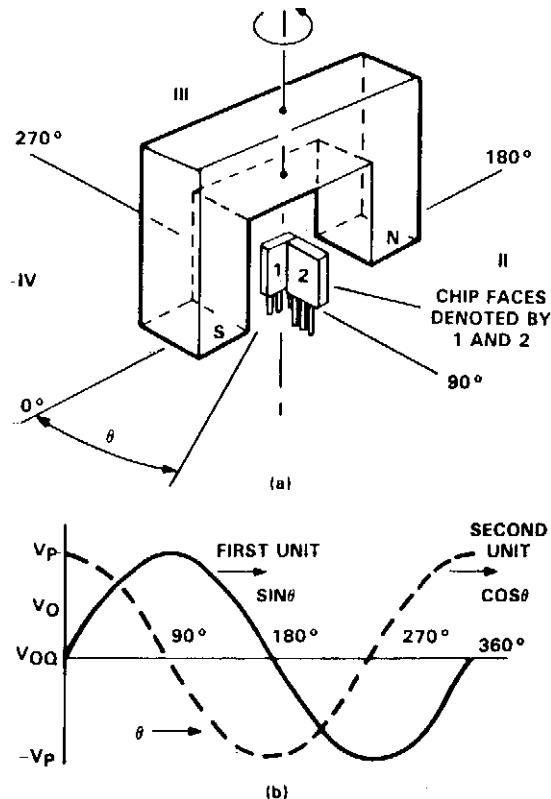
### ANGLE OF ROTATION DETECTOR


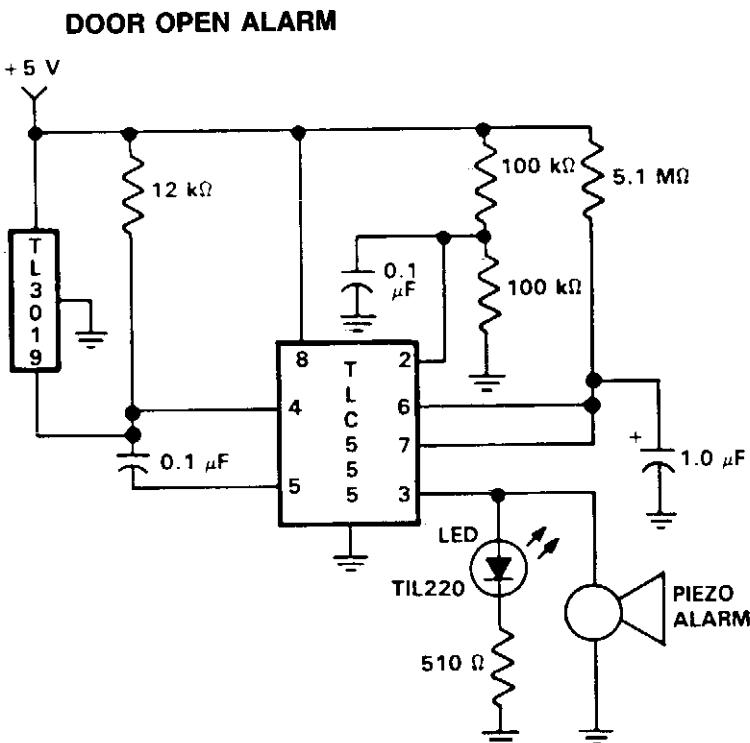


**Fig. 43-1**

TEXAS INSTRUMENTS
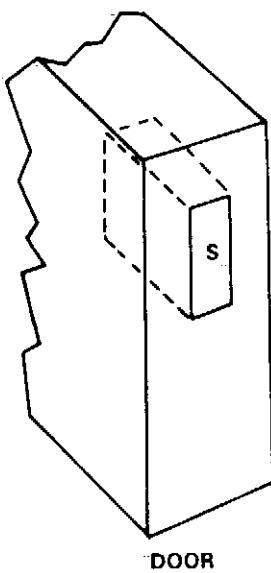
#### Circuit Notes

The figure shows two TL3103 linear Hall-effect devices used for detecting the angle of rotation. The TL3103s are centered in the gap of a U-shaped permanent magnet. The angle that the south pole makes with the chip face of unit #1 is defined as angle 0. Angle 0 is set to 0° when the chip face of unit #1 is perpendicular to the south pole of the magnet. As the south pole of the magnet sweeps through a 0° to 90° angle, the output of the sensor increases from 0°. Sensor unit #2 decreases from its peak value of +  $V_p$  at 0° to a value  $V_{QQ}$  at 90°. So, the output of sensor unit #1 is a sine function of 0 and the output of unit #2 is a cosine function of 0 as shown. Thus, the first sensor yields the angle of rotation and the second sensor indicates the quadrant location.



TEXAS INSTRUMENTS

*Fig. 43-2*

#### Circuit Notes

Door open alarms are used chiefly in automotive, industrial, and appliance applications. This type of circuit can sense the opening of a refrigerator door. When the door opens, a triac could be activated to control the inside light. The figure shows a door position alarm. When the door is opened, an LED turns on and the piezo alarm sounds for approximately 5 seconds. This circuit uses a TL3019 Hall-effect device for the door sensor. This normally open switch is located in the door frame. The magnet is mounted in the door. When the door is in the closed position, the TL3019 output goes to logic low, and remains low until the door is opened. This design consists of a TLC555 monostable timer circuit. The  $1 \mu\text{F}$  capacitor and  $5.1 \text{ M ohm}$  resistor on pins 6 and 7 set the monostable RC time constant. These values allow the LED and piezo alarm to remain on about 5 seconds when triggered. One unusual aspect of this circuit is the method of triggering. Usually a 555 timer circuit is triggered by taking the trigger, pin 2, low which produces a high at the output, pin 3. In this configuration with the door in the closed position, the TL3019 output is held low. The trigger, pin 2, is connected to  $\frac{1}{2}$  the supply voltage  $V_{CC}$ . When the door opens, a positive high pulse is applied to control pin 5 through a  $0.1 \mu\text{F}$  capacitor and also to reset pin 4. This starts the timing cycle. Both the piezo alarm and the LED visual indicator are activated.

# **44**

## **Humidity Sensors**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Relative Humidity Sensor Signal Conditioner
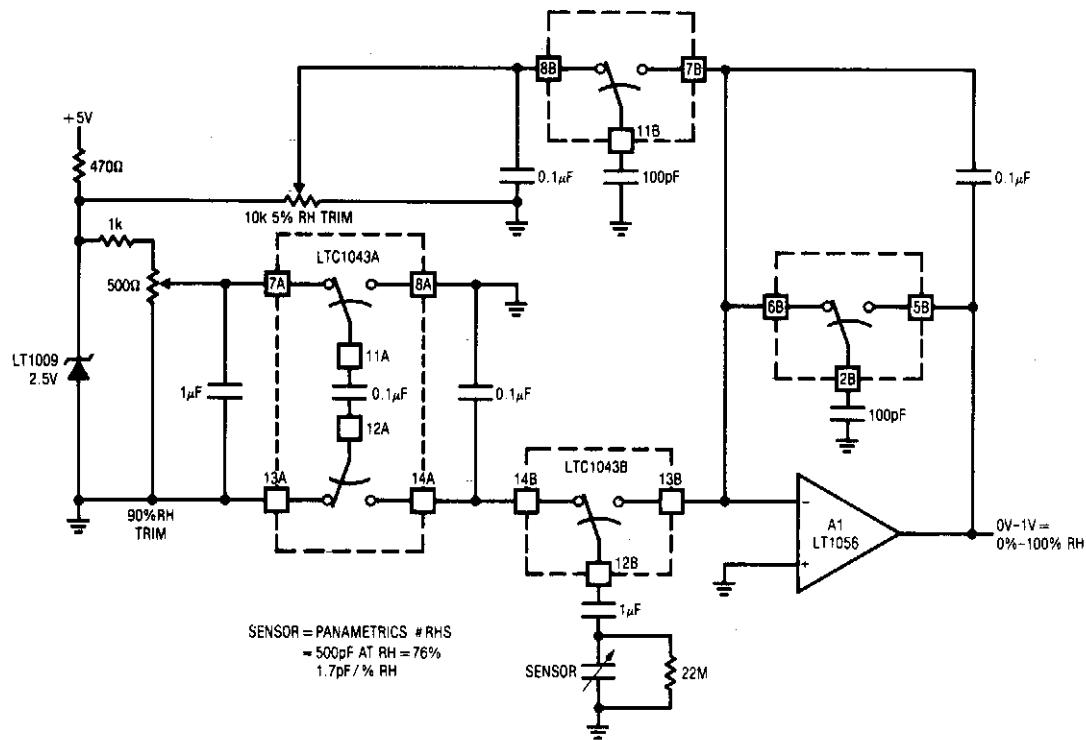
## RELATIVE HUMIDITY SENSOR SIGNAL CONDITIONER




LINEAR TECHNOLOGY CORPORATION

**Fig. 44-1**
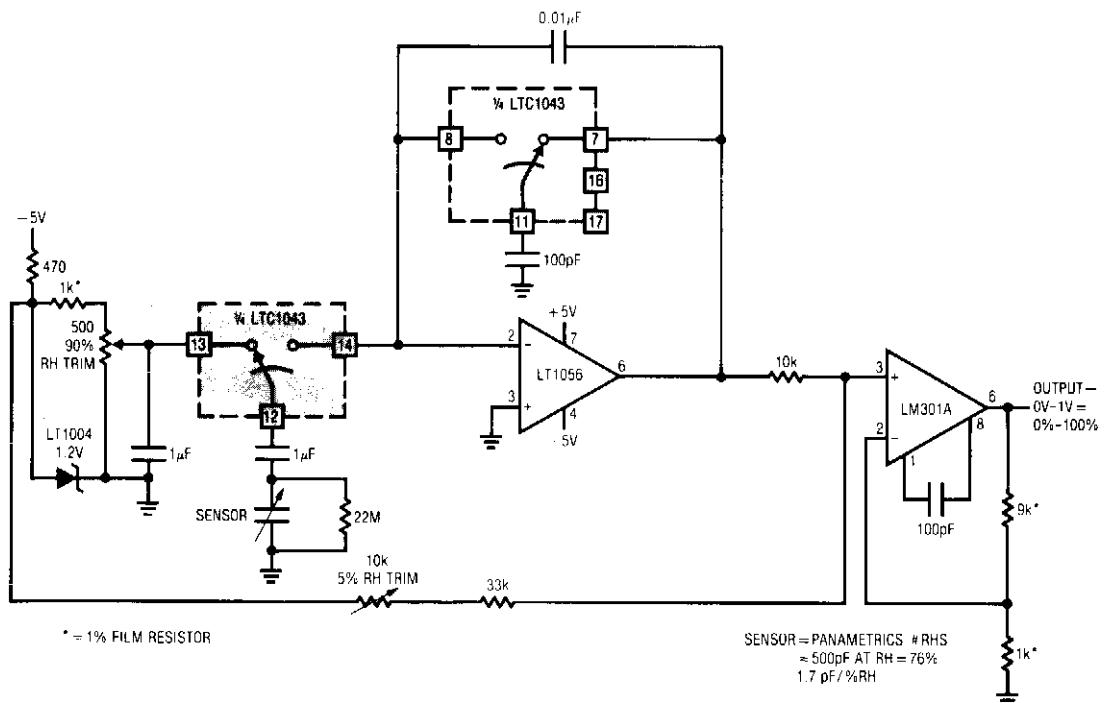
### Circuit Notes

This circuit combines two LTC1043s with a based humidity transducer in a simple charge-pump based circuit. The sensor specified has a nominal 400 pF capacitance at RH = 76%, with a slope of 1.7 pF/% RH. The average voltage across this device must be zero. This provision prevents deleterious electrochemical migration in the sensor. The LTC1043A inverts a resistively scaled portion of the LT1009 reference, generating a negative potential at pin 14A. The LTC1043B alternately charges and discharges the humidity sensor via pins 12B, 13B, and 14B. With 14B and 12B connected, the sensor charges via the 1  $\mu$ F unit to the negative potential at pin 14A. When the 14B-12B pair



opens, 12B is connected to A1's summing point via 13B. The sensor now discharges into the summing point through the 1 μF capacitor. Since the charge voltage is fixed, the average current into the summing point is determined by the sensor's humidity related value. The 1 μF value ac couples the sensor to the charge-discharge path, maintaining the required zero average voltage across the device. The 22M resistor prevents accumulation of charge, which would stop current flow. The average current into A1's summing point is balanced by packets of charge delivered by the switched-capacitor gives A1 an integrator-like response, and its output is dc.

# **45**

## **Infrared Circuits**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Low Noise Infrared Detector
- Infrared Transmitter
- Infrared Transmitter
- Invisible Infrared Pulsed Laser Rifle
- Infrared Receiver
- Pulsed Infrared Diode Emitter Drive


## LOW NOISE INFRARED DETECTOR

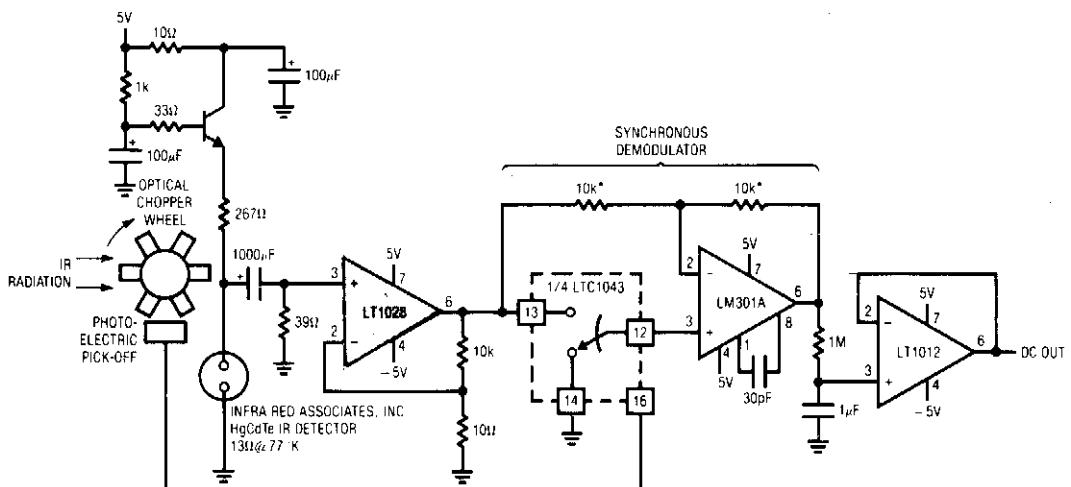

LINEAR TECHNOLOGY CORP.

**Fig. 45-1**

## **INFRARED TRANSMITTER**

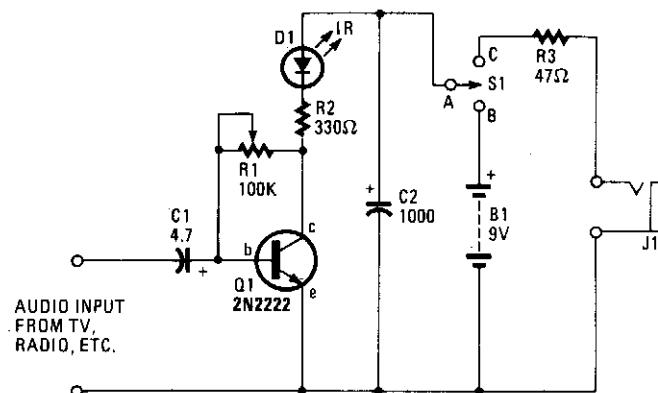


HANDS-ON ELECTRONICS

**Fig. 45-2**

**Circuit Notes**

The ultra-simple one-transistor, IR transmitter shown is designed to transmit the sound from any 8 or 16 ohm audio source, such as a TV, radio, or tape recorder on an infrared beam of light.

## INFRARED TRANSMITTER

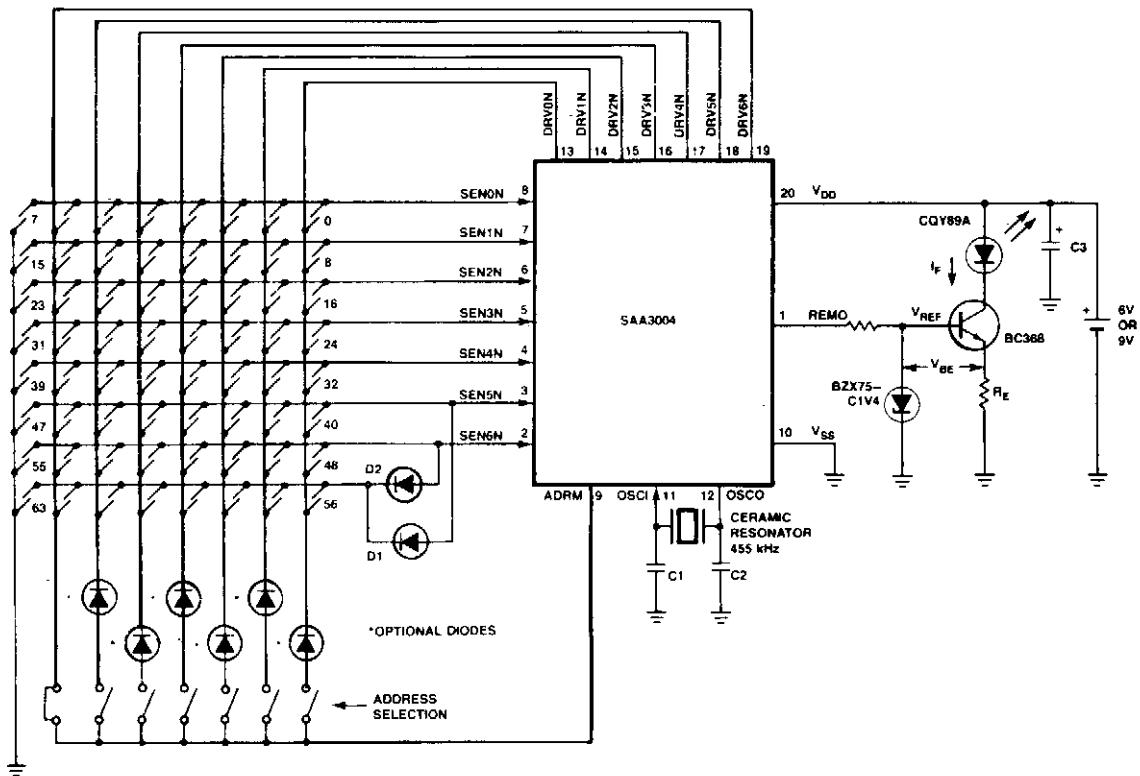


**SIGNETICS**

**Fig. 45-3**

### Circuit Notes

The transmitter keyboard is arranged as a scanned matrix. The matrix consists of 7 driver outputs and 7 sense inputs. The driver outputs DRVON to DRV6N are open-drain n-channel transistors and they are conductive in the stand-by mode. The 7 sense inputs (SEN0N to SEN6N) enable the generation of 56 command codes. With 2 external diodes all 64 commands are addressable. The sense inputs have p-channel pull-up transistors, so that they are HIGH until they are pulled LOW by connecting them to an output via a key depression to initiate a code transmission.

## INVISIBLE INFRARED PULSED LASER RIFLE

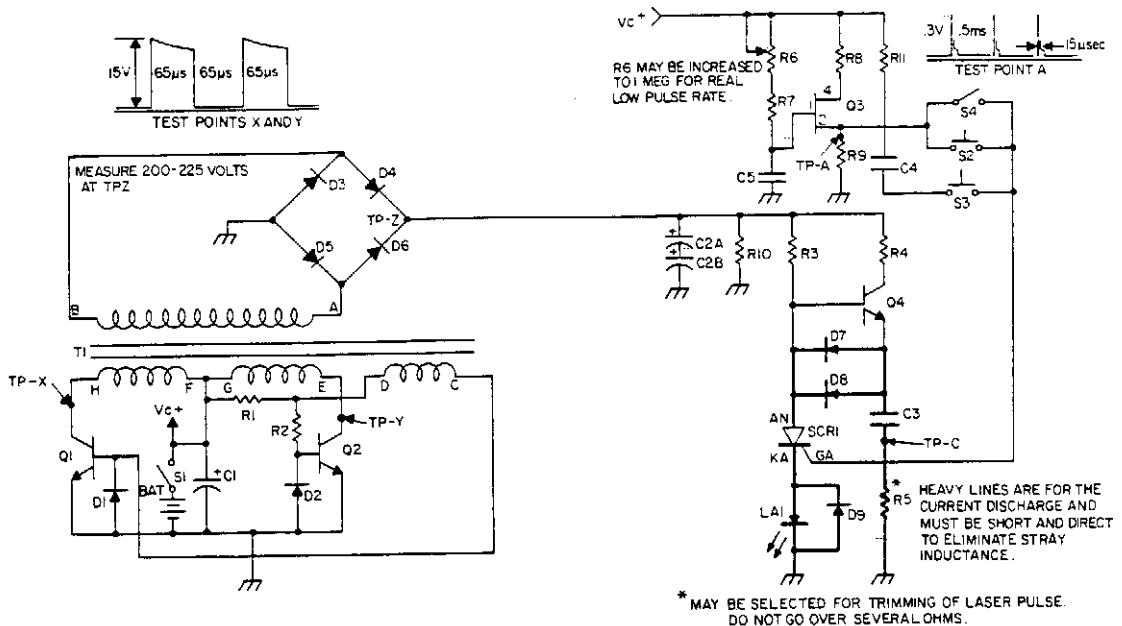

**Fig. 45-4**


**TAB BOOKS INC.**

### Circuit Notes

The device generates an adjustable frequency of low to medium powered IR pulses of invisible energy and must be treated with care.

The portable battery pack is stepped up to 200 to 300 volts by the inverter circuit consisting of Q1, Q2, and T1. Q1 conducts until saturated, at which time, the base no longer can sustain it in an "on" state and Q1 turns "off," causing the magnetic field in its collector winding to collapse thus producing a voltage or proper phase in the base drive winding that turns on Q2 until saturated, repeating the above sequence of events in an "on/off" action. The diodes connected at the bases provide a return path for the base drive current. The stepped up squarewave voltage on the secondary of T1 is rectified and integrated on C2.


## INFRARED RECEIVER

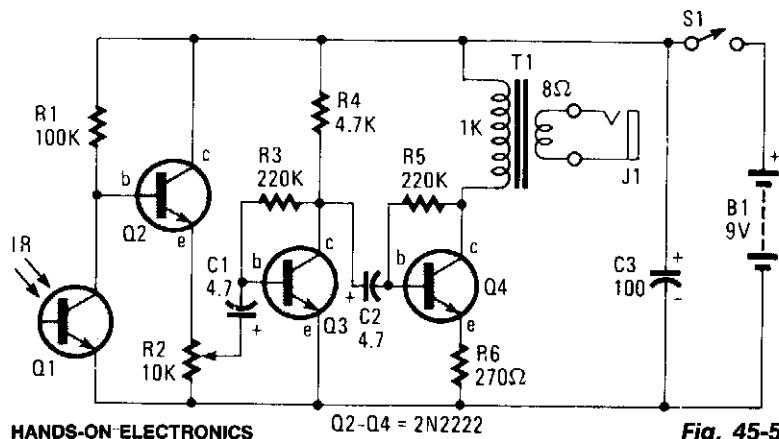

### Circuit Notes

The circuit consists of Q1—a phototransistor that responds to an intensity of amplitude-modulated IR light source—and a three-stage, high-gain audio amplifier. Transformer T1 is used to match the output impedance of the receiver to today's popular low-impedance (low-Z) headphones; but if a set of 1000-2000 ohm, magnetic (not crystal), high-impedance (high-Z) phones are to be used, remove T1 and connect the high-Z phones in place of T1's primary winding—the 1000-ohm winding.

## PULSED INFRARED DIODE EMITTER DRIVE

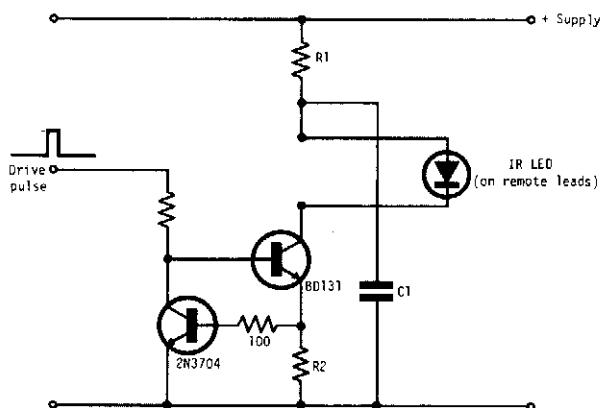

### Circuit Notes

Q1 and Q2 form a constant current drive defined by R2. ( $I$  approximates to the reciprocal of  $R2$  in the circuit shown for values of  $I$  greater than 1 amp). The pulse current is drawn from C1 which is recharged during the time between pulses via R1. The value of C1 is determined from the duration and magnitude of the peak current required, and the time constant  $R1 C1$  is determined from the duration between pulses.

# **46**

## **Instrumentation Amplifiers**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Instrument Preamp
- Instrumentation Amplifier with  $\pm 100$  Volt Common  
Mode Range
- Current-Collector Head-Amplifier
- Instrumentation Meter Driver
- Saturated Standard Cell Amplifier

## INSTRUMENT PREAMP

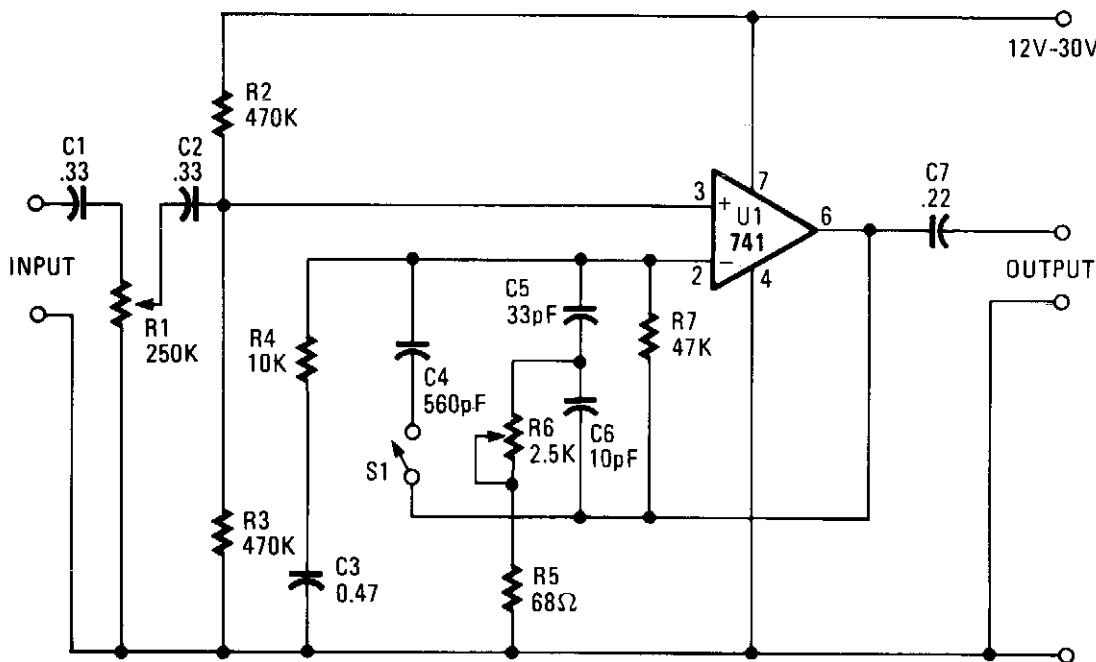


HANDS-ON ELECTRONICS

**Fig. 46-1**

### Circuit Notes

The input impedance is the value of potentiometer R1. If your instrument has extra-deep bass, change capacitor C1 to 0.5 μF. What appears to be an extra part in the feedback loop is a brightening tone control. The basic feedback from the op amp's output (pin 6) to the inverting input (pin 2) consists of resistor R7, and the series connection of resistor R4 and capacitor C3, which produce a voltage gain of almost 5 (almost 14 dB). That should be more extra oomph than usually needed. If the circuit is somewhat short on bass response, increase the value of capacitor C3 to 1 to 10 μF. Start with 1 μF and increase the value until you get the bass effect you want.


## INSTRUMENTATION AMPLIFIER WITH $\pm 100$ VOLT COMMON MODE RANGE

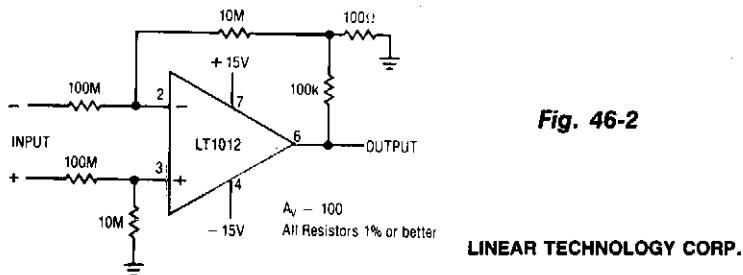

**Fig. 46-2**

LINEAR TECHNOLOGY CORP.

## CURRENT-COLLECTOR HEAD-AMPLIFIER

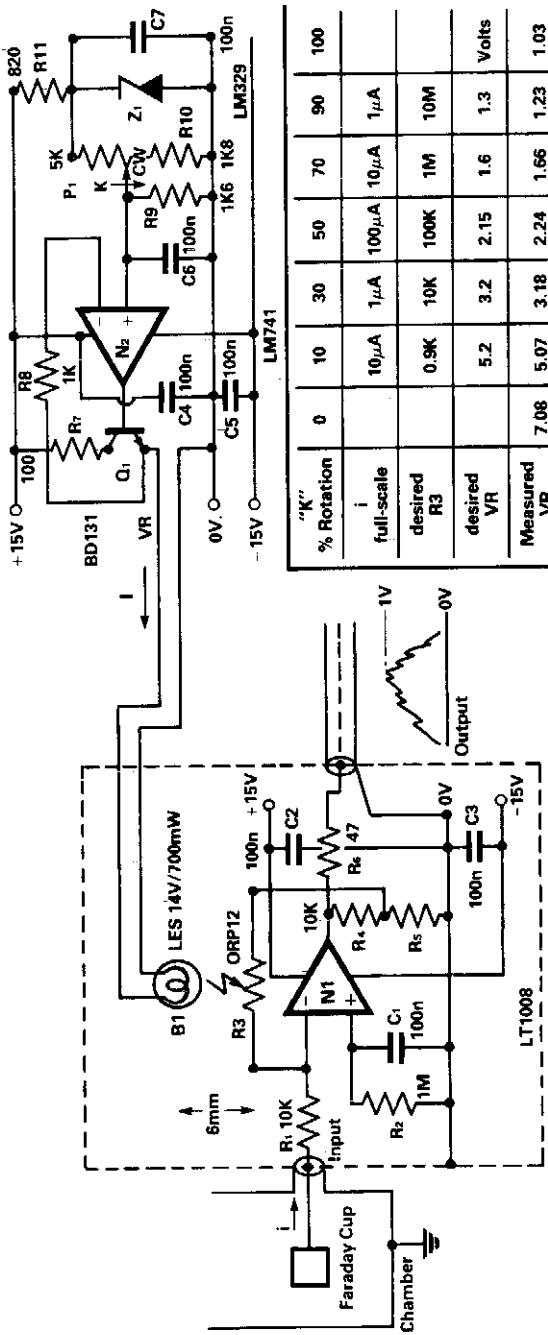

ELECTRONIC ENGINEERING


Fig. 46-3

### Circuit Notes

To amplify small current signals such as from an electron-collector inside a vacuum chamber, it is convenient for reasons of noise and bandwidth to have a "head-amplifier" attached to the chamber. The op amp N1 is a precision bipolar device with extremely low bias current and offset voltage ( $I_{OS}$ ) as well as low noise, which allows the 100:1 feedback attenuator R4:R5. The resistance of R3 can be varied from above 10M to below 1R, and so the nominal 0 to 1 V-peak output signal corresponds to input current ranges of 1 nA to 10  $\mu\text{A}$ ; this current  $i$  enters via the protective resistor R1. Light from the bulb B1 shines on R3, and the filament current  $I$  is controlled by the op amp N2.

The reference voltage VR is "shaped" by the resistors R9R10 so as to tailor the bulb and LDR characteristics to the desired current ranges. Thus, rotation of the calibrated knob K gives the appropriate resistance to R3 for the peak-current scale shown.


## INSTRUMENTATION METER DRIVER

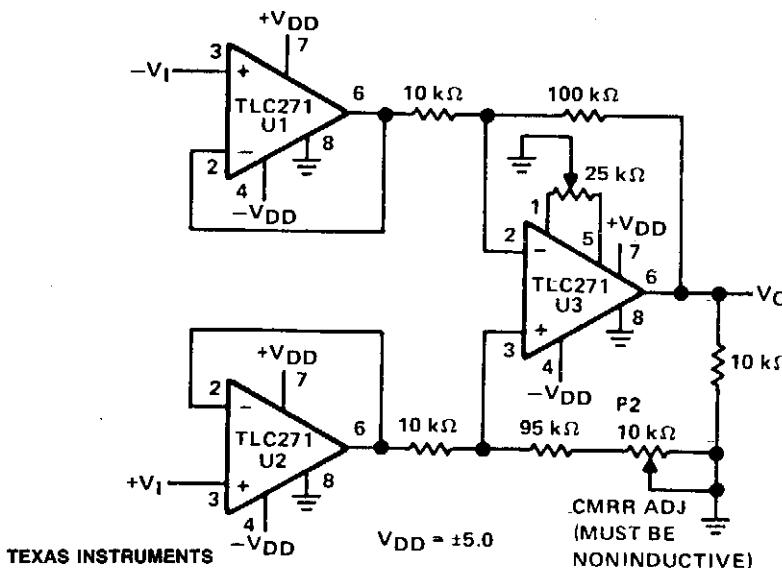

### Circuit Notes

Three op amps U1, U2, and U3 are connected in the basic instrumentation amplifier configuration. Operating from  $\pm 5\text{ V}$ , pin 8 of each op amp is connected directly to ground and provides the ac performance desired in this application (high bias mode). P1 is for offset error correction and P2 allows adjustment of the input common mode rejection ratio. The high input impedance allows megohms without loading. The resulting circuit frequency response is 200 kHz at  $-3\text{ dB}$  and has a slew rate of  $4.5\text{ V}/\mu\text{s}$ .

## SATURATED STANDARD CELL AMPLIFIER

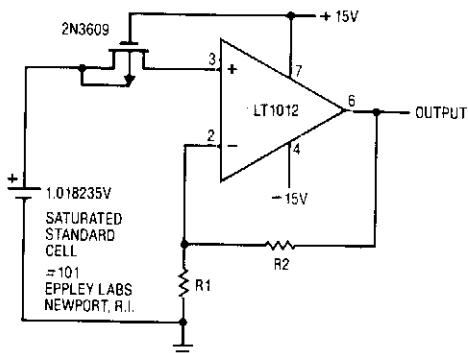

**Fig. 46-5**

The typical 30pA bias current of the LT1012 will degrade the standard cell by only 1 ppm/year. Noise is a fraction of a ppm. Unprotected gate MOSFET isolates standard cell on power down.

LINEAR TECHNOLOGY CORP.

# 47

## Integrator Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Improved Non-Inverting Integrator  
Active Integrator with Inverting Buffer  
Long Time Integrator

## IMPROVED NON-INVERTING INTEGRATOR

Fig. 1

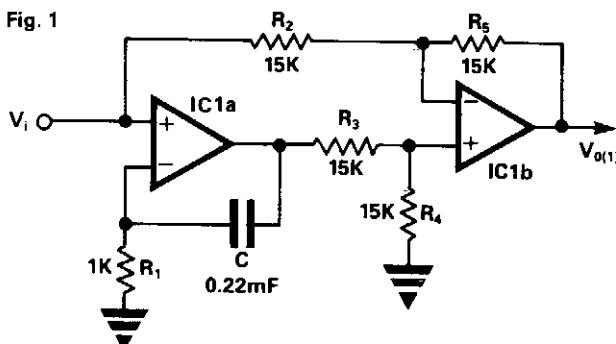


Fig. 2


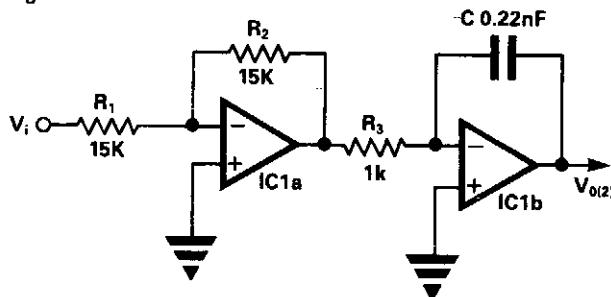


Fig. 3

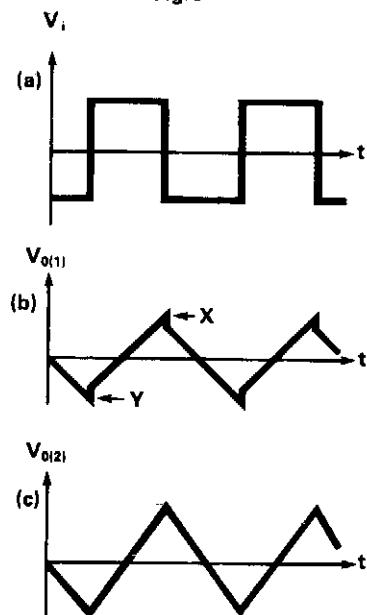

ELECTRONIC ENGINEERING


Fig. 47-1

### Circuit Notes


In the circuit in Fig. 1, IC1a produces the integral term required but also has the side effect of producing a proportional term not required, so this term is subtracted by IC1b leaving a pure integral. If the ratio  $R_2/R_5$  does not exactly match the ratio of  $R_3/R_4$ , the subtraction will not be complete and a small amount of the proportional term will reach the output. The result of this with a squarewave input is shown in Fig. 3a as small steps in the output waveform at points X and Y.

This effect can be completely removed by using the simplified circuit shown in Fig. 2. Here the signal is pre-inverted by IC1a, then fed to a standard inverting integrator IC1b. The result is a non-inverting integrator with the advantage that the unwanted proportional term is never produced, so it does not need to be subtracted.
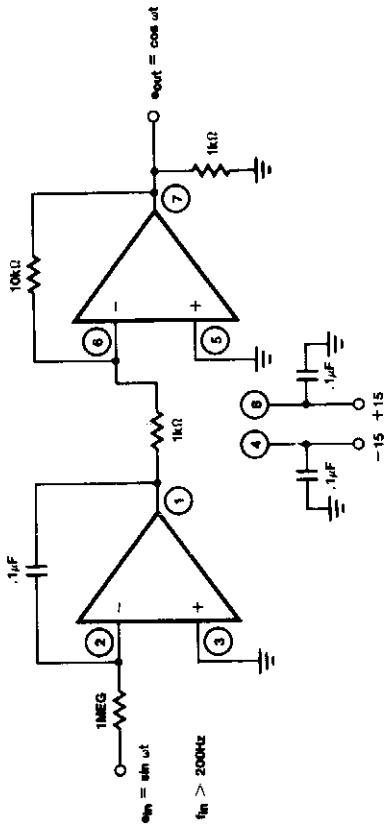
### ACTIVE INTEGRATOR WITH INVERTING BUFFER




### INTEGRATOR WAVEFORMS

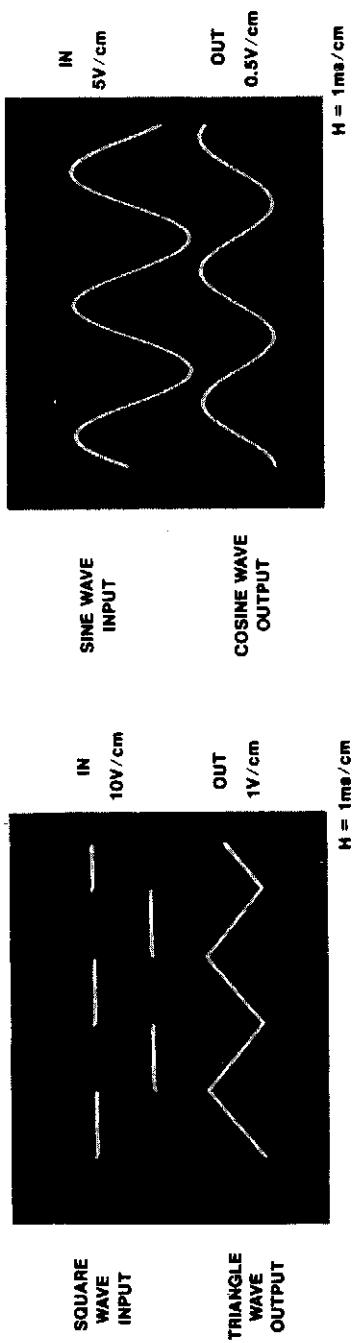

IC = NE/SE5512  
SIGNETICS

Fig. 47-2

## LONG TIME INTEGRATOR

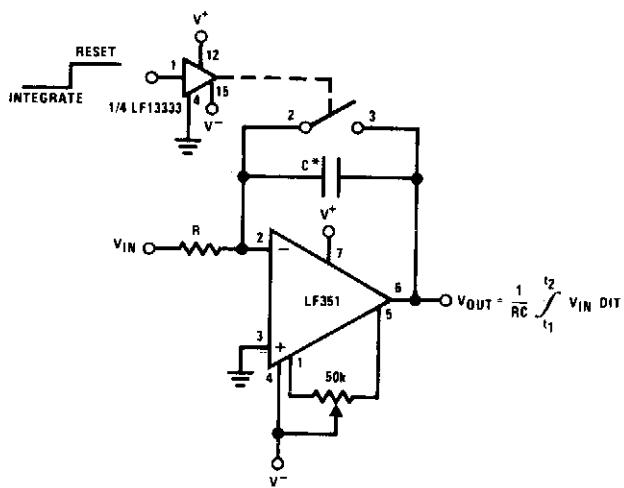

*Fig. 47-3*

- \* Low leakage capacitor
- 50k pot used for less sensitive  $V_{DS}$  adjust

NATIONAL SEMICONDUCTOR CORP.

# **48**

## **Intercom Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Intercom  
Party-Line Intercom

## INTERCOM

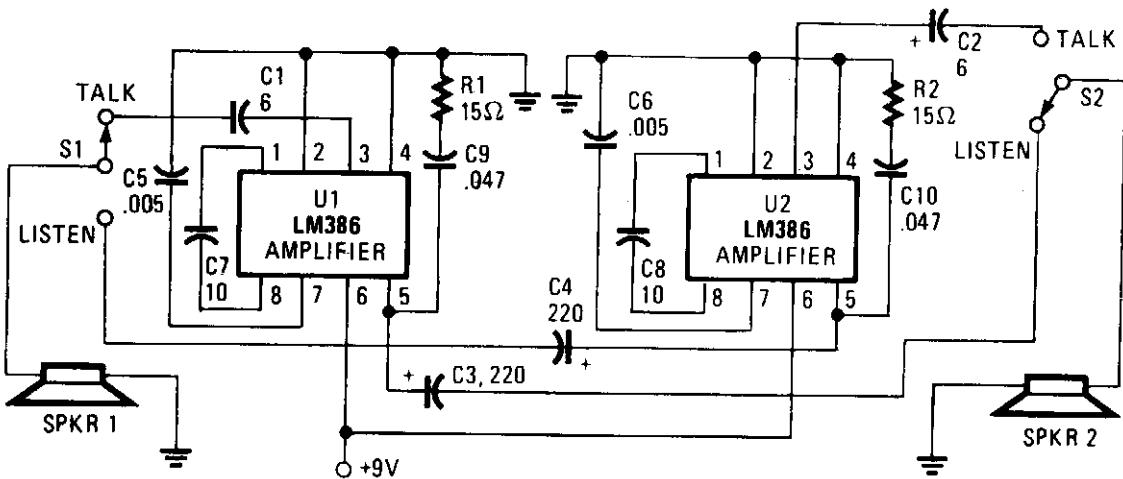


HANDS-ON ELECTRONICS

**Fig. 48-1**

### Circuit Notes

The circuit consists of separate amplifiers—one for each station—rather than a single amplifier and a time sharing arrangement. U1 and U2 are low-voltage audio amplifiers, each of which operates as separate entities with switches at either station controlling which will transmit or receive. With capacitors C7 and C8 included in the circuit, the amplifiers have a gain of 200. Omitting those two components drops the gain to about 20. Other gain levels are available with the addition of a series-connected R/C combination connected between pin 1 and pin 8—for example, a 1000 ohm resistor and 10 μF capacitor for a gain of about 150.

## PARTY-LINE INTERCOM

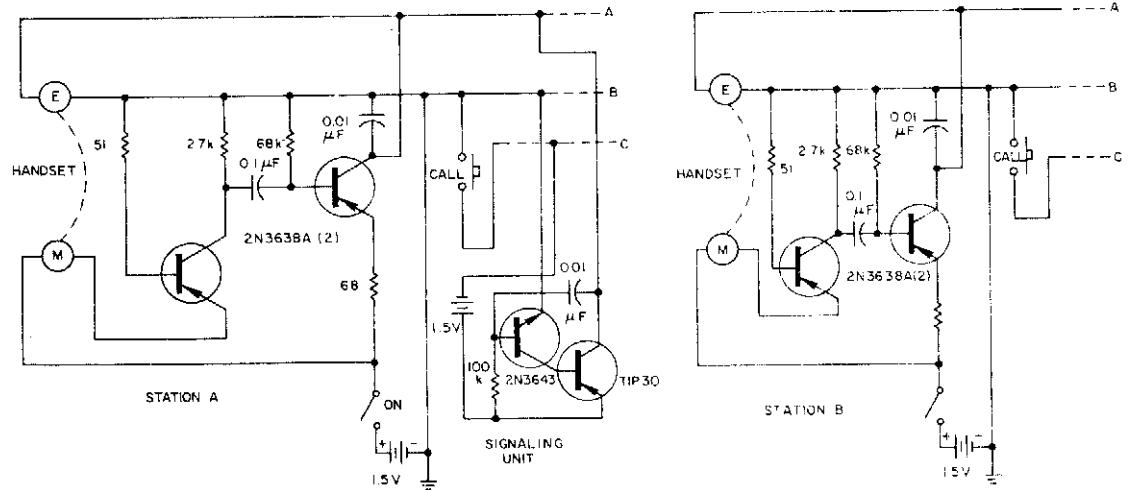

ELECTRONIC DESIGN

Fig. 48-2

### Circuit Notes

A large number of intercom stations can be tied together. All units are connected in parallel, and the entire system is buzzed by only one signaling circuit. Each unit is powered individually from 1.5-V cells for redundancy. For greater signal volume, 3-V sources can be used for the supplies without changing any other parts of the system. The carbon microphone of a standard telephone handset at each station feeds into a common-base amplifier, and a tandem high-gain common-emitter stage drives the intercom line. All phone earpieces are in parallel across the line. The signaling circuit, also connected across the line, is a simple oscillator that drives all the earpieces.

# **49**

## **Lamp-Control Circuits**

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Voltage Regulator for a Projection Lamp  
Machine Vision Illumination Stabilizer  
dc Lamp Dimmer  
Automatic Light Controller for Carport  
800 W Light-Dimmer

Lamp Dimmer  
Rugged Lamp Driver is Short-Circuit Proof  
TRIAC Lamp Dimmer  
TRIAC Zero-Point Switch  
Tandem Dimmer (Cross-Fader)

## VOLTAGE REGULATOR FOR A PROJECTION LAMP

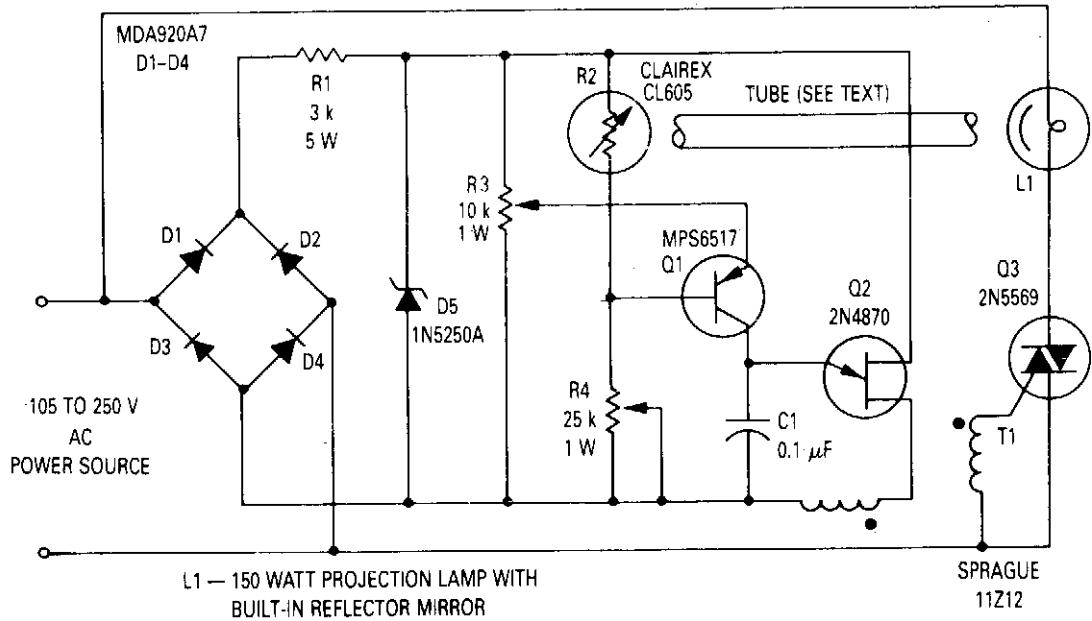

**Fig. 49-1**

### Circuit Notes

The circuit will regulate the rms output voltage across the load (a projection lamp) to 100 volts  $\pm 2\%$  for an input voltage between 105 and 250 volts ac. This is accomplished by indirectly sensing the light output of lamp L1 and applying this feedback signal to the firing circuit (Q1 and Q2) which controls the conduction angle of TRIAC Q3. The lamp voltage is provided by TRIAC Q3, whose conduction angle is set by the firing circuit for unijunction transistor Q2. The circuit is synchronized with the line through the full-wave bridge rectifier. The voltage to the firing circuit is limited by zener diode D5. Phase control of the supply voltage is set by the charging rate of capacitor C1. Q2 will fire when the voltage on C1 reaches approximately 0.65 times the zener voltage. The charging rate of C1 is set by the conduction of Q1, which is controlled by the resistance of photocell R2. Potentiometers R3 and R4 are used to set the lamp voltage to 100 volts when the line voltage is 105 volts and 250 volts, respectively.

## MACHINE VISION ILLUMINATION STABILIZER


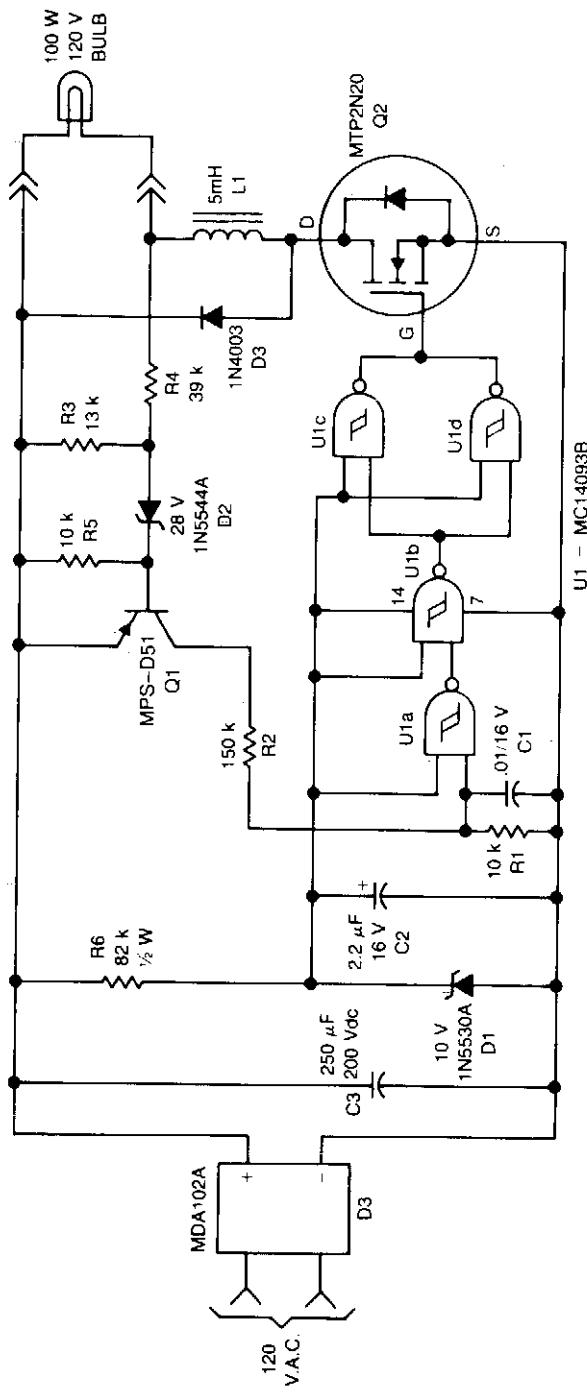


Fig. 49-2

### Circuit Notes

The combination of Q1, Q2 and U1 form a hysteresis oscillator to stabilize lamp illumination. In operation, full wave bridge D3 operates directly from the ac line to supply unregulated dc to the lamp and also to the 10 V zener that provides power to the quad CMOS Schmitt trigger, U1. When the lamp supply exceeds 115 V, Q1 is turned ON, charging C1 through R2 to raise the input to U1 past the positive-going logic threshold. This drops the output voltage at U1c and U1d, which drives the gate of Q2, turning it OFF. Current then decays through the lamp, L1 and D3 until the lamp voltage falls below 115 V, at which time Q1 turns OFF and the cycle repeats.

## DC LAMP DIMMER

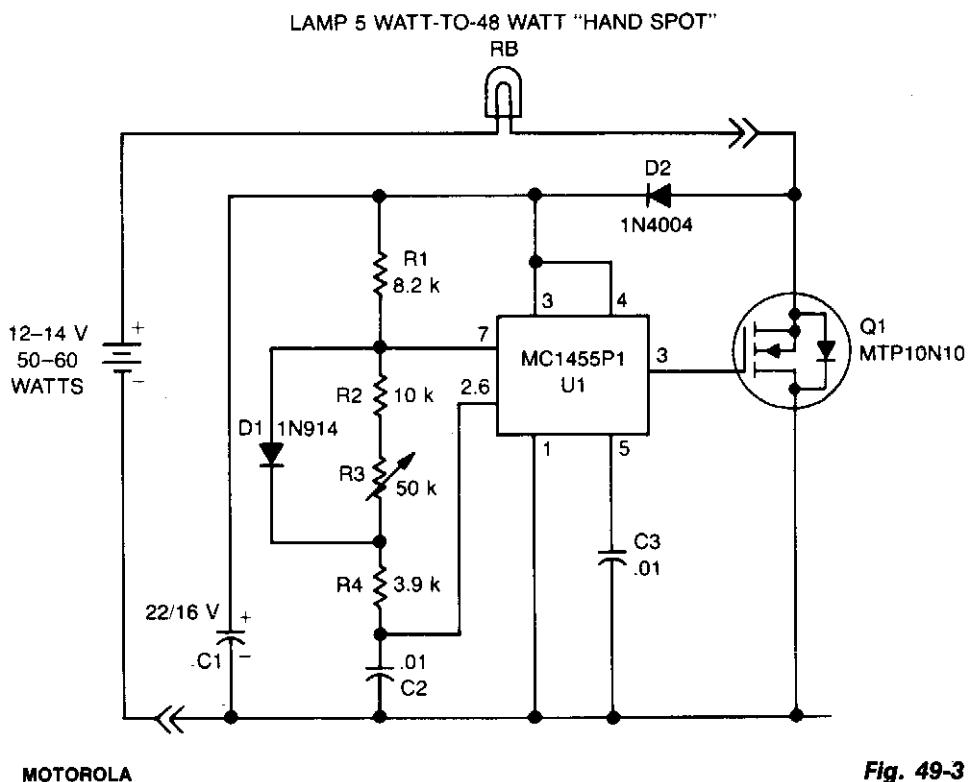


### Circuit Notes

A low power, low cost dc lamp dimmer for a two-wire portable "flashlight" can be realized with little or no heatsinking. In addition, a single potentiometer, R3 adjusts lamp brightness.

Battery power is stored in C1 for U1, which is a free-running multivibrator whose frequency is determined by R1, R2, R3, R4, and C2. U1 drives the gate of Q1, turning it and the lamp ON and OFF at a rate proportional to the multivibrator duty cycle.
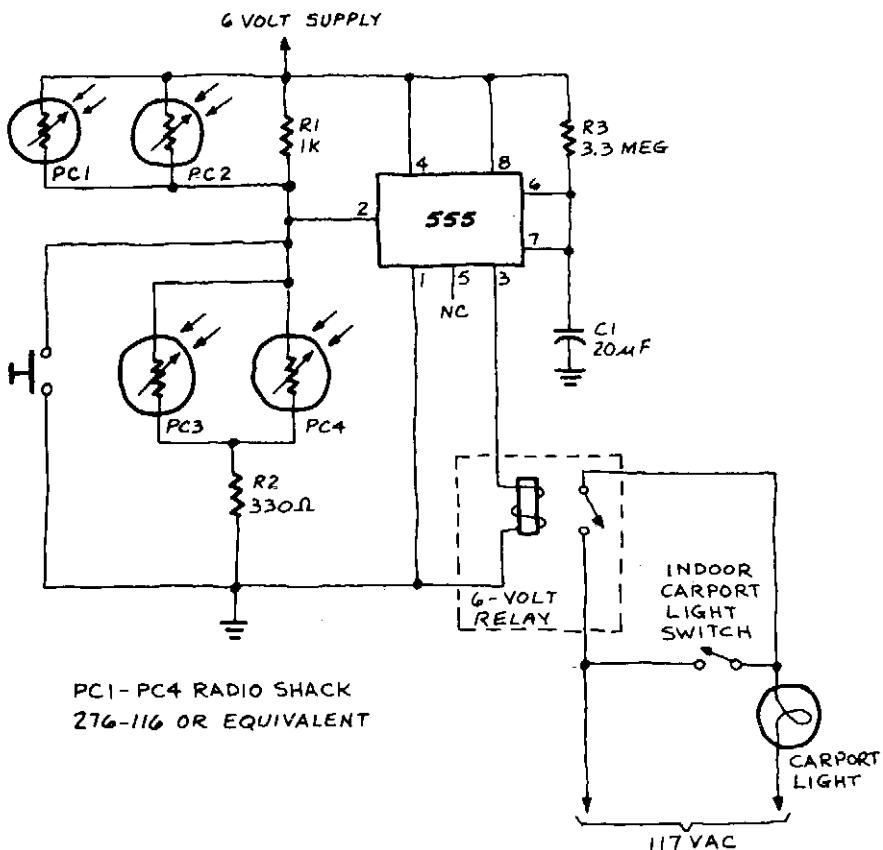
## AUTOMATIC LIGHT CONTROLLER FOR CARPORT




RADIO-ELECTRONICS

Fig. 49-4

### Circuit Notes

A 555 timer IC, operating in the one-shot mode, is triggered by light striking photoresistors. These normally have a resistance of several megohms but, in the presence of light, that resistance drops to several hundred ohms, permitting current from the six-volt source to flow in the circuit. The R-C combination shown gives an on-time of about two minutes. Photoresistors PC3 and PC4 are mounted at headlight-height. When headlights illuminate the photoresistor, the timer starts. That actuates a relay, RY1, and the lights are turned on. The lights are automatically turned off when the timer's two minutes are up.

## 800 W LIGHT-DIMMER

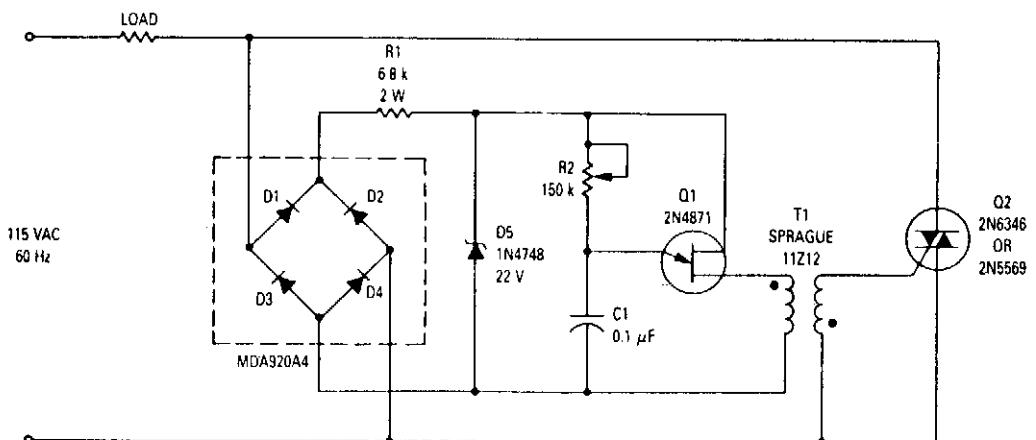

MOTOROLA

**Fig. 49-5**


### Circuit Notes

This wide-range light dimmer circuit uses a unijunction transistor and a pulse transformer to provide phase control for the TRIAC. The circuit operates from a 115 volt, 60 Hz source and can control up to 800 watts of power to incandescent lights. The power to the lights is controlled by varying the conduction angle of the TRIAC from 0° to about 170°. The power available at 170° conduction is better than 97% of that at the full 180°.

## LAMP DIMMER
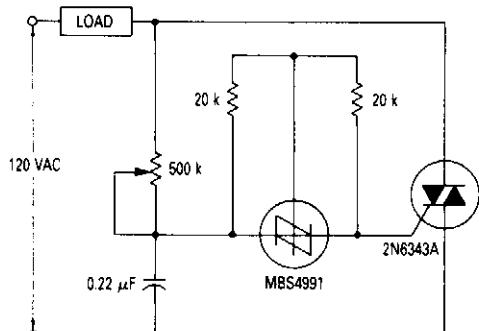
### Circuit Notes


A full range power controller suitable for lamp dimming and similar applications operate from a 120 volt, 60 Hz ac source, and can control up to 1000 watts of power to incandescent bulbs. The power to the bulbs is varied by controlling the conduction angle of TRIAC Q1. At the end of each positive half-cycle when the applied voltage drops below that of the capacitor, gate current flows out of the SBS and it switches on, discharging the capacitor to near zero volts. The RC network shown across the TRIAC represents a typical snubber circuit that is normally adequate to prevent line transients from accidentally firing the TRIAC.



MOTOROLA

**Fig. 49-6**
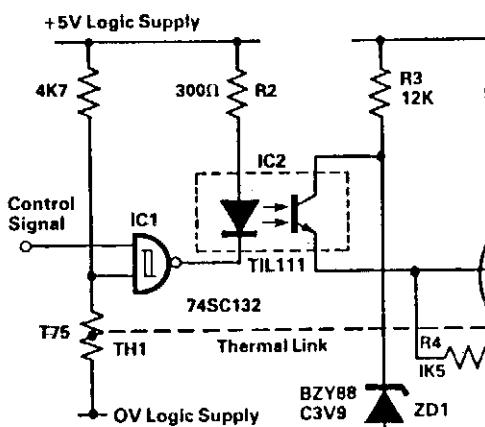
## RUGGED LAMP DRIVER IS SHORT-CIRCUIT PROOF



ELECTRONIC ENGINEERING

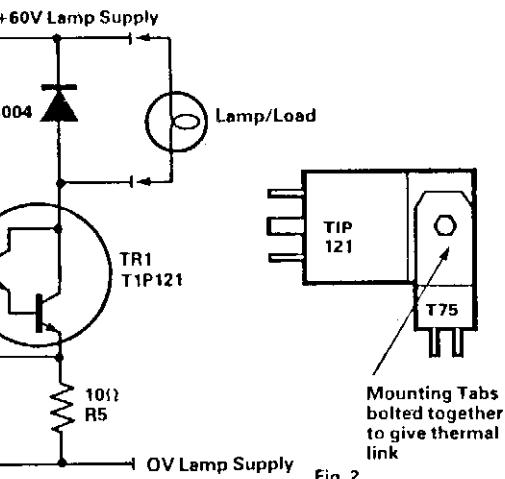



Fig. 49-7

### Circuit Notes

This circuit is capable of driving filament lamps of nominal rating 200 mA at 60 V dc from a CMOS logic signal.

The lamp or load is connected in series with the Darlington transistor TR1 and emitter resistor R5. The Zener diode ZD1 establishes a soft reference voltage on the collector of the optical coupler IC2. When the logic control signal from the processor switches the optocoupler on via IC1, base drive is applied to TR1 and the lamp is switched on.

## TRIAC LAMP DIMMER

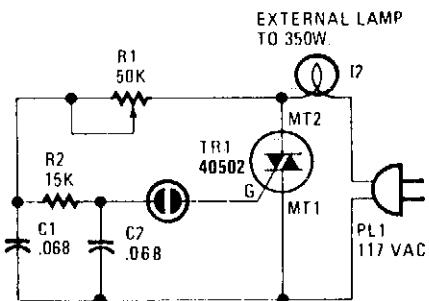


TAB BOOKS, INC.

Fig. 49-8

### Circuit Notes

Using a heatsink, the TRIAC (TR1) can handle up to 350 watts. The neon lamp, I1, won't trip the gate until after it conducts and using R1, set the lighting wherever you want it.

### TRIAC ZERO-POINT SWITCH

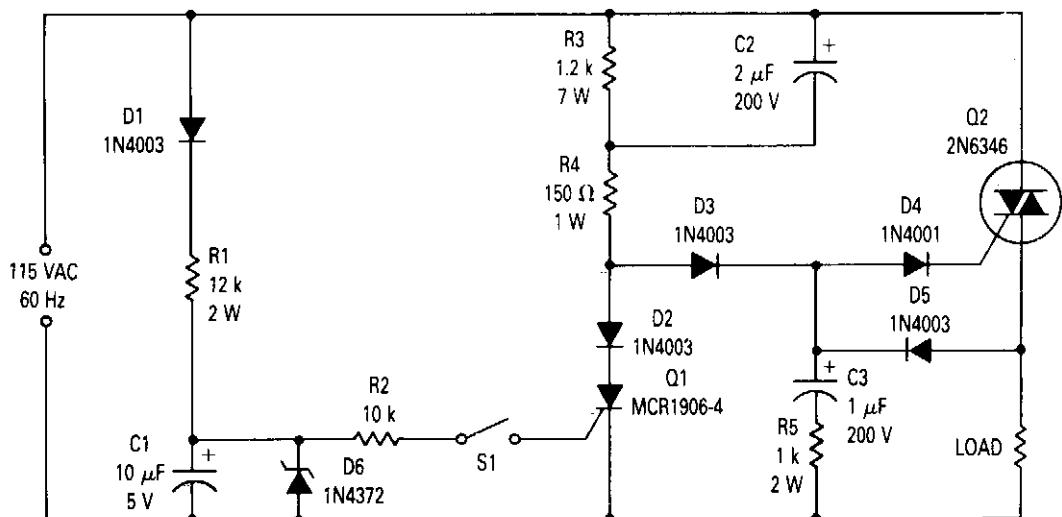


MOTOROLA

Fig. 49-9

#### Circuit Notes

On the initial part of the positive half cycle, the voltage is changing rapidly from zero causing a large current to flow into capacitor C2. The current through C2 flows through R4, D3, and D4 into the gate of the TRIAC Q2 causing it to turn on very close to zero voltage. Once Q2 turns on, capacitor C3 charges to the peak of the line voltage through D5. When the line voltage passes through the peak, D5 becomes reverse-biased and C3 begins to discharge through D4 and the gate of Q2. At this time the voltage on C3 lags the line voltage. When the line voltage goes through zero there is still some charge on C3 so that when the line voltage starts negative C3 is still discharging into the gate of Q2. Thus Q2 is also turned on near zero on the negative half cycle. This operation continues for each cycle until switch S1 is closed, at which time SCR Q1 is turned on. Q1 shunts the gate-current away from Q2 during each positive half cycle keeping Q2 from turning on. Q2 cannot turn on during the negative cycle because C3 cannot charge unless Q2 is on during the positive half cycle.

### TANDEM DIMMER (CROSS-FADER)

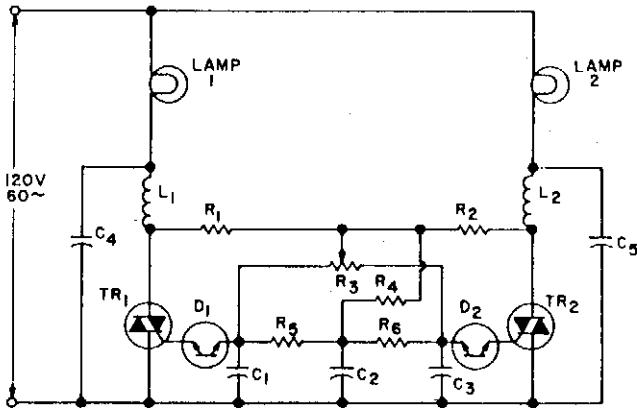

$R_1 = R_2 = 6800\Omega$ , 1 WATT  
 $R_3 = 150K \Omega$  LINEAR POT. 1W  
 $R_5 = R_6 = 22K\Omega$ , 1/2W.  
 $R_4 = 15K\Omega$ , 1/2W.  
 $TR_1 = TR_2 =$  TRIAC  
 $D_1 = D_2 =$  GE ST-2 DIAC

$L_1 = L_2 = 60\mu\text{H}$  (FERRITE CORE)  
 $C_1 = C_2 = C_3 = 0.1\mu\text{F}$  50V  
 $C_4 = C_5 = 0.1\mu\text{F}$  200 VOLTS  
 NOTE: TOTAL LIGHT LEVEL (SUM OF LAMPS 1+2) CONSTANT WITHIN 15%.

GENERAL ELECTRIC

*Fig. 49-10*

### Circuit Notes

This cross fader circuit can be used for fading between two slide projectors. As  $R_3$  is moved to either side of center, one triac is fired earlier in each half cycle, and the other later. The total light output of both lamps stays about the same for any control position.

# **50**

## **Laser Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Laser Light Detector  
Stabilizing a Laser Discharge Current

## LASER LIGHT DETECTOR

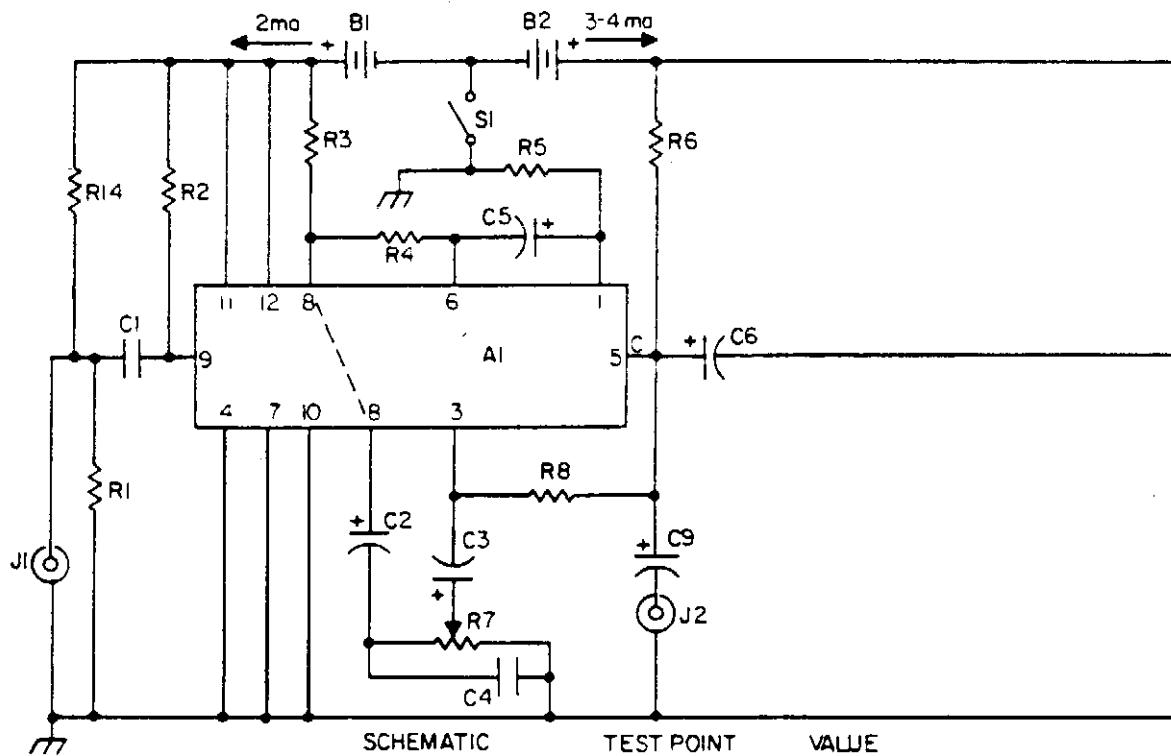

TEST POINT      VALUE

A	6-8V
B	4-5V
C	3-4V
D	0(3)V
E	9(4.5)V
F	0(3)V
G	0(1)V
H	9(.2)V


VALUE IN PARENTHESIS ARE IN THE  
"ACTUATED" STATE AND ARE WITH A  
REALISTIC #CTR-43 RECORDER.



TAB BOOKS INC.

*Fig. 50-1*

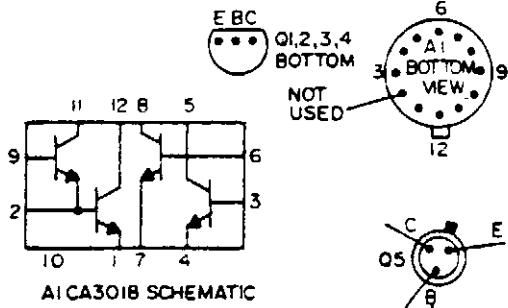
### Circuit Notes

The laser light detector utilizes a sensitive photo transistor (Q5) placed at the focal point of a lens (LE2). The output of Q5 is fed to a sensitive amplifier consisting of array (A1) and is biased via the voltage divider consisting of R14 and R1. The base is not used. Q5 is capacitively coupled to a Darlington pair for impedance transforming and is further fed to a capacitively coupled cascaded pair of common-emitter amplifiers for further signal



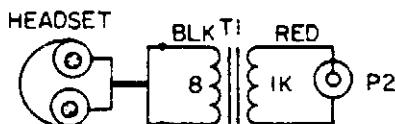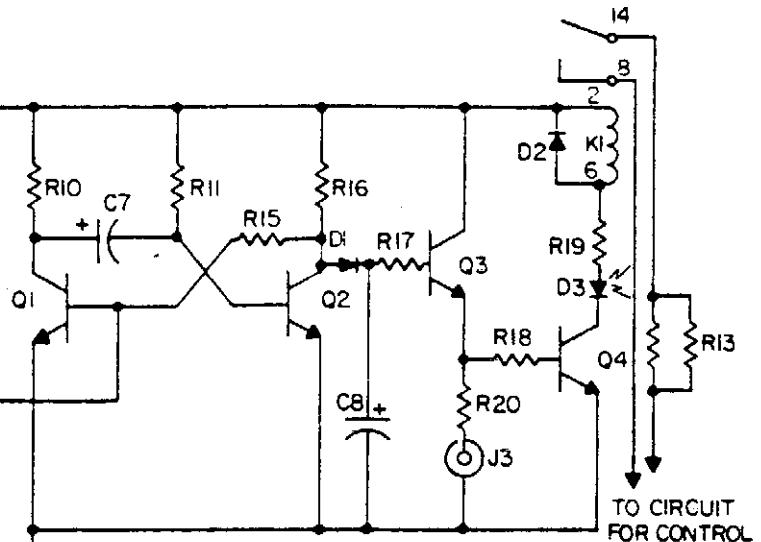

SPLICE T1 INTO HEADSET PLUG LEAD

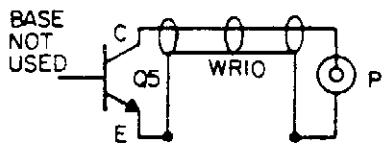

RECEIVER PHOTOTRANSISTOR  
AND CABLE

amplification. Sensitivity control (R7) controls base drive to the final transistor of the array and hence controls overall system sensitivity. Output of the amplifier array is capacitively coupled to a one-shot consisting of Q1 and Q2 in turn integrating the output pulses of Q2 onto capacitor C8 through D1. This dc level now drives relay drivers Q3 and Q4 activating K1 along with energizing indicator D3, consequently controlling the desired external circuitry. The contacts of K1 are in series with low ohm resistor R13 to prevent failure when switching capacitive loads. J2 allows "listening" to the intercepted light beam via headsets. This is especially useful when working with pulsed light sources such as GaAs lasers or any other varying periodic light source.

## STABILIZING A LASER DISCHARGE CURRENT

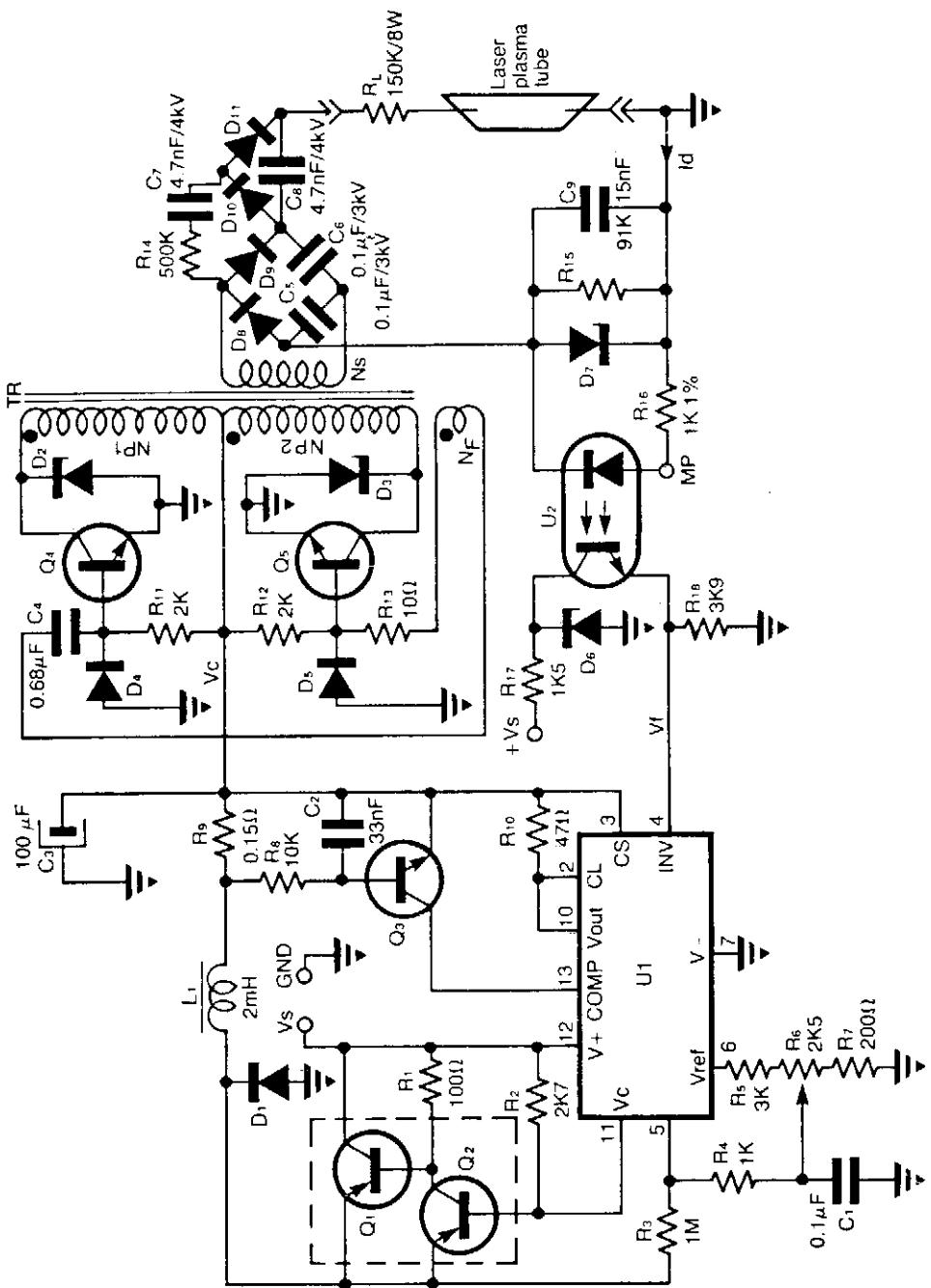


Fig. 50-2

			D <sub>1</sub>	BA159
			D <sub>2</sub> , D <sub>3</sub>	PL33Z
		Q <sub>1</sub>	KD167	1N4148
		Q <sub>2</sub>	BD140	D <sub>6</sub>
		Q <sub>3</sub>	BC173C	D <sub>7</sub>
		Q <sub>4</sub> , Q <sub>5</sub>	2N5496	D <sub>8</sub> ...D <sub>11</sub>
				LA40
N <sub>p1</sub> =N <sub>p2</sub>	8 turns			
U <sub>1</sub>	LM723	N <sub>s</sub>	1100 turns	
U <sub>2</sub>	MB101	N <sub>f</sub>	5 turns	

### Circuit Notes

The circuit uses a free-running push-pull dc to dc high voltage converter to get the necessary voltage for the laser plasma tube supply. The supply voltage  $V_C$  of this converter, is adjusted by a switch-mode power supply in order to keep the load current constant, at set value. The linear opto-electronic isolator U2, connected in series with the laser plasma tube, gives a voltage  $V_F$  proportional to the discharge current  $I_D$  across R18, having the correct polarity to drive directly the inverting input of U1, D<sub>7</sub>, R15 protects the optoisolator diode against damage produced by the high voltage ignition pulse.

Due to the high operating frequency of the high voltage converter (25 kHz) the ripple of the laser output power is less than  $2 \cdot 10^{-4}$ . The stability of  $I_D$  is better than  $10^{-2}$ , for variations of supply voltage  $V_s$  is the range of  $\pm 10\%$ , and depends on the optoisolator sensitivity.

# 51

## Light-Controlled Circuits


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- |  |  |
|--|--|
| Photo Alarm                                      | Synchronous Photoelectric Switch                                 |
| Warning Light Operates from Battery Power Supply | Photocurrent Integrator  |
| Light Operated Switch                            | Robot Eyes   |
| Photoelectric Switch                             | Modulated Light-Beam Circuit Cancels Ambient<br>Light Effects    |
| Back-Biased GaAsP LED Operates as Light Sensor   | Monostable Photocell Circuit has Self-Adjusting<br>Trigger Level |
| Twilight-Triggered Circuit                       | Thermally Stabilized PIN Photodiode Signal<br>Conditioner        |
| Automatic Mooring Light                          |  |
| Electronic Wake-Up Call                          |  |
| Photodiode Sensor Amplifier                      |  |
| Light Seeking Robot                              |  |

## PHOTO ALARM

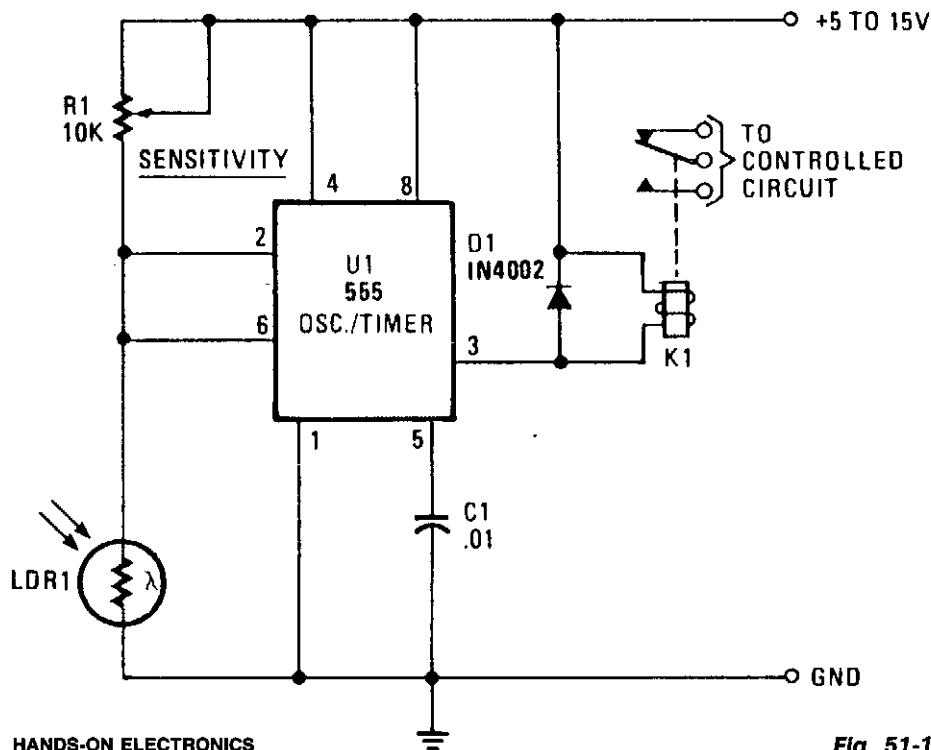


**Fig. 51-1**

### Circuit Notes

LDR1, a cadmium sulphide (CDS) photoresistive cell is used as the lower leg of a voltage divider between  $V_{CC}$  and ground. The timer terminals 2 and 6 are connected to the junction of the photocell and SENSITIVITY control R1. The resistance of the photoresistive cell varies inversely as the light intensity; resistance is high when the illumination level is low; low in bright light. (The Radio Shack CDS cell 276-116 has a typically wide resistance range—about 3 megohms in darkness and 100 ohms in bright light.) When the light is interrupted or falls below a level set by SENSITIVITY control R1, the rise in LDR1's resistance causes the voltage on pins 2 and 6 to rise. If the control is set so the voltage rises above  $\frac{1}{3} V_{CC}$ , the relay pulls in. The relay drops out when the light level increases and the drop across the photocell falls below  $\frac{1}{3} V_{CC}$ . (The circuit can be modified by placing relay K1 and diode D1 between pin 3 and ground. In this case, the relay drops out when the voltage on pins 2 and 6 rises above  $\frac{1}{3} V_{CC}$ , and pulls in when it falls below  $\frac{1}{3} V_{CC}$ . This modification is valuable when the relay has single-throw contacts.) Opening and closing of the relay contacts occurs at different illumination levels. This  $\frac{1}{3} V_{CC}$  hysteresis is an advantage that prevents the circuit from hunting and the relay from chattering when there are very small changes in illumination.

## WARNING LIGHT OPERATES FROM BATTERY POWER SUPPLY

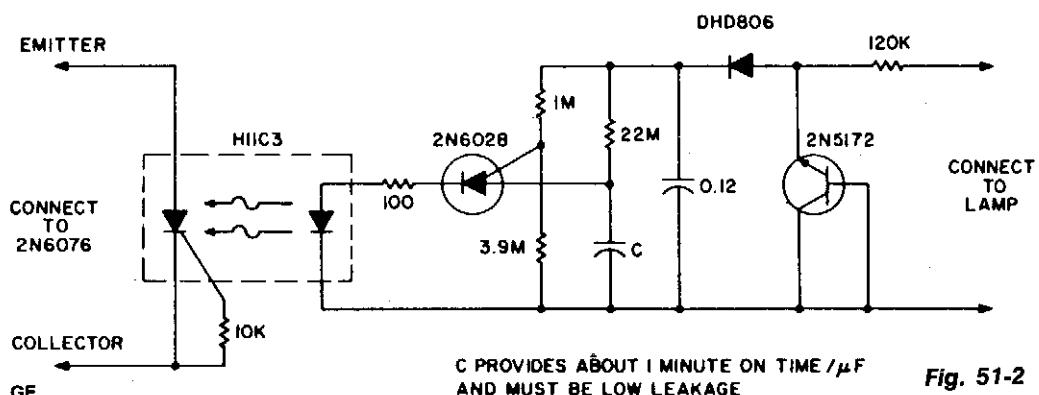


**Fig. 51-2**
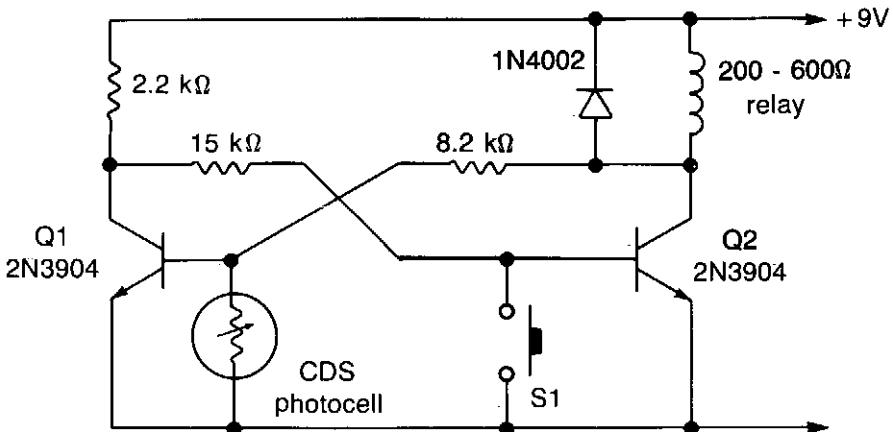
### Circuit Notes

The circuit provides illumination when darkness comes. By using the gain available in darlington transistors, this circuit is simplified to use just a photodarlington sensor, a darlington amplifier, and three resistors. The illumination level will be slightly lower than normal, and longer bulb life can be expected, since the D40K saturation voltage lowers the lamp operating voltage slightly.

## LIGHT-OPERATED SWITCH



WILLIAM SHEETS

**Fig. 51-3**

### Circuit Notes

This circuit uses a flip-flop arrangement of Q1 and Q2. Normally Q1 is conducting heavily. Light on CDS photocell causes Q1 bias to decrease, cutting it off, turning on Q2, removing the remaining bias from Q1. Reset is accomplished by depressing S1.

### PHOTOELECTRIC SWITCH

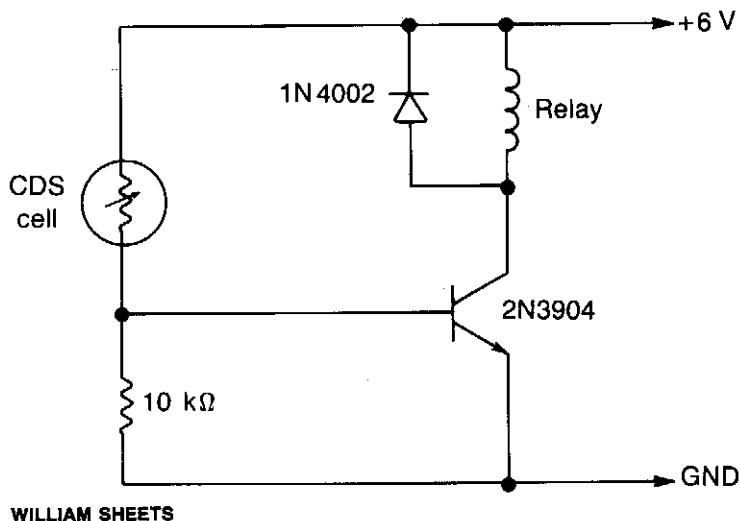



Fig. 51-4

WILLIAM SHEETS

### Circuit Notes

The CDS cell resistance decreases in the presence of light, turning on the 2N3904 relay driver.
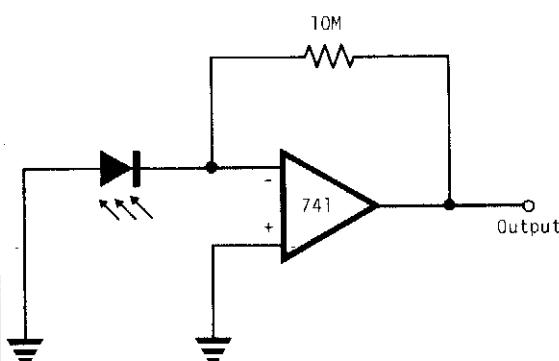
### BACK-BIASED GaAsP LED OPERATES AS LIGHT SENSOR




### Circuit Notes

Using a simple 741 amplifier connected as a current-to-voltage converter with the LED as the current source, the voltage at the output is proportional to incident light. The junction is biased only by the difference between the summing node junction potential and ground, preventing the possibility of reverse breakdown. The photon-generated current equals the short-circuit current of the junction, which is linearly related to incident light. The sensor requires a level of incident illumination that depends on the degree of opacity of the LED package.

ELECTRONIC ENGINEERING

Fig. 51-5

## TWILIGHT-TRIGGERED CIRCUIT

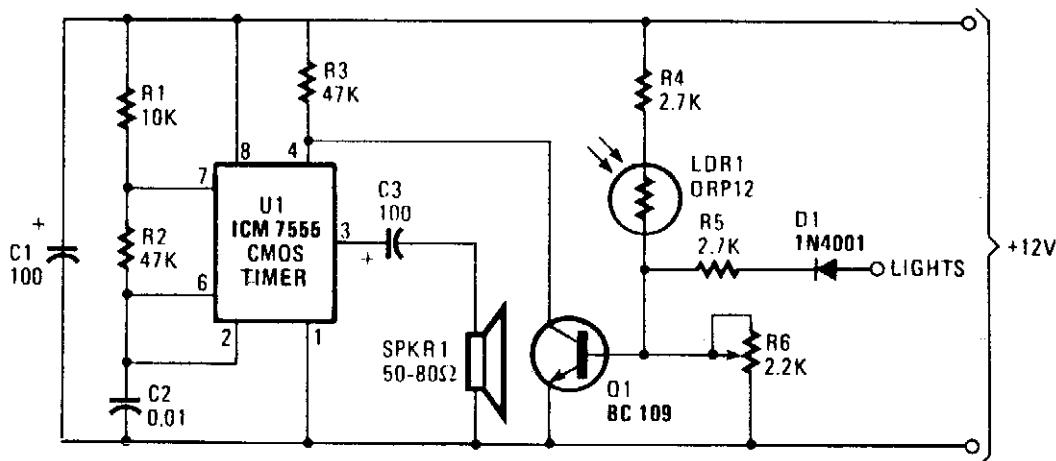


HANDS-ON ELECTRONICS

**Fig. 51-6**

### Circuit Notes

As dusk begins to fall, the sensor (a cadmium-sulfide light-dependent resistor or LDR) operates a small horn to provide an audible reminder that it's time to turn on your lights. To turn the circuit off—simply turn your headlights on and the noise stops. The base of Q1 is fed through a voltage divider formed by R4, LDR1—a light-dependent resistor with an internal resistor of about 100 ohms under bright-light conditions and about 10 megohms in total darkness—potentiometer R6. Q1's base voltage depends on the light level received by LDR1 and the setting of R6. If LDR1 detects a high light level, its resistance decreases, thereby providing a greater base current for Q1, causing it to conduct. When Q1 conducts, pin 4 of U1 is pulled to near ground potential, muting the oscillator. If, on the other hand, LDR1 detects a low light level, its resistance increases (reducing base current to Q1), cutting off the transistor and enabling the oscillator. In actual practice, you set R6 so that at a suitable light level (dusk), the oscillator will sound. The anode of diode D1 connects to the light switch, where it connects to the vehicle's parking lights. With the lights switched off, that point is connected to the negative chassis by way of the parking lamp. That has no effect on the circuit, as D1 blocks any current flow to ground from Q1's base via R6 and the sidelight lamps. When the lights are switched on, the anode of D1 is connected to the positive supply via the parking lamp switch, thereby applying a voltage to the base of Q1, biasing it into conduction. With Q1 conducting, pin 4 of U1 is pulled virtually to ground, disabling the oscillator even though LDR1's resistance is not enough to do so.

## AUTOMATIC MOORING LIGHT

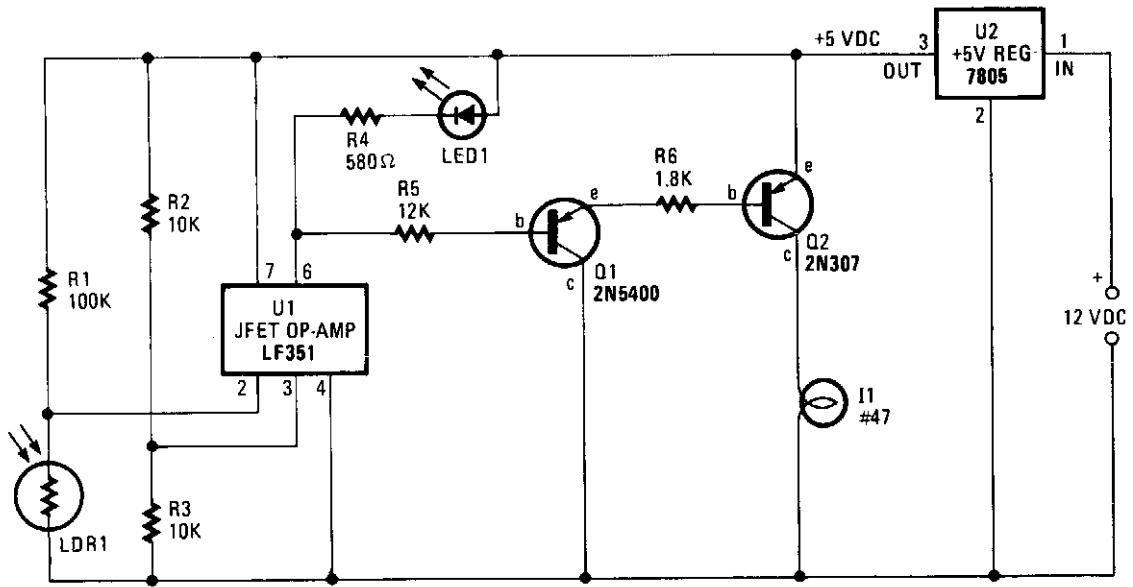

HANDS-ON ELECTRONICS

**Fig. 51-7**

### Circuit Notes

Integrated-circuit U1—an LF351 or 741 op amp—is used as a comparator to control the light. Resistors R2 and R3 provide a reference voltage of about 2.5 volts at pin 3 of U1. When daylight falls on light-dependent resistor LDR1, its resistance is low: about 1000 ohms. In darkness, the LDR's resistance rises to about 1 megohm. Since R1 is 100,000 ohms, and the LDR in daylight is 1000 ohms, the voltage ratio is 100 to 1; the voltage drop across the LDR is less than the 2.5 volt reference voltage and pin 2 of U1 is held at that voltage. In that state, the output at pin 6 of U1 is positive at about 4.5 volts, a value that reverse-biases Q1 to cutoff, which in turn holds Q2 in cutoff, thereby keeping lamp I1 off. When darkness falls, the LDR's resistance rises above R1's value and the voltage at pin 2 of U1 rises above the reference voltage of 2.5 volts. U1's output terminal (pin 6) falls to less than a volt and Q1 is biased on. The base-to-emitter current flow turns Q2 on, which causes current to flow through the lamp. When daylight arrives, the LDR's resistance falls sharply, which causes the lamp to be turned off, ready to repeat the next night/day cycle.

## ELECTRONIC WAKE-UP CALL


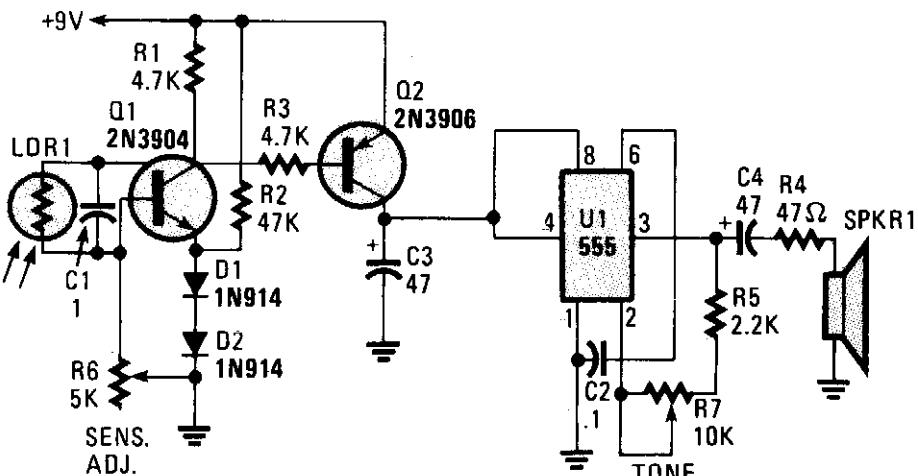


Fig. 51-8

### Circuit Notes

A cadmium sulfide photocell (LDR1, which is a light-dependent resistor) is connected to the base and collector of an npn transistor, Q1. When light hits LDR1, the internal resistance goes from a very high (dark) value to a low (light) value, supplying base current to Q1, turning it on. The voltage across R1 produces a bias that turns Q2 on, which in turn, supplies the positive voltage to U1 at pin 8 (the positive-supply input) and pin 4 (the reset input), to operate the 555 audio oscillator circuit. The circuit's sensitivity to light can be set via R6 (a 50,000 ohm potentiometer). R7 sets the audio tone to the most desirable sound. The squarewave audio tone is fed from U1 pin 3 to a small speaker through coupling-capacitor C4 and current limiting resistor R4.


## PHOTODIODE SENSOR AMPLIFIER

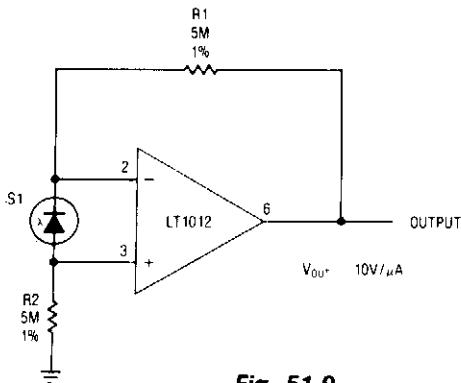

LINEAR TECHNOLOGY CORP.

Fig. 51-9

## LIGHT-SEEKING ROBOT

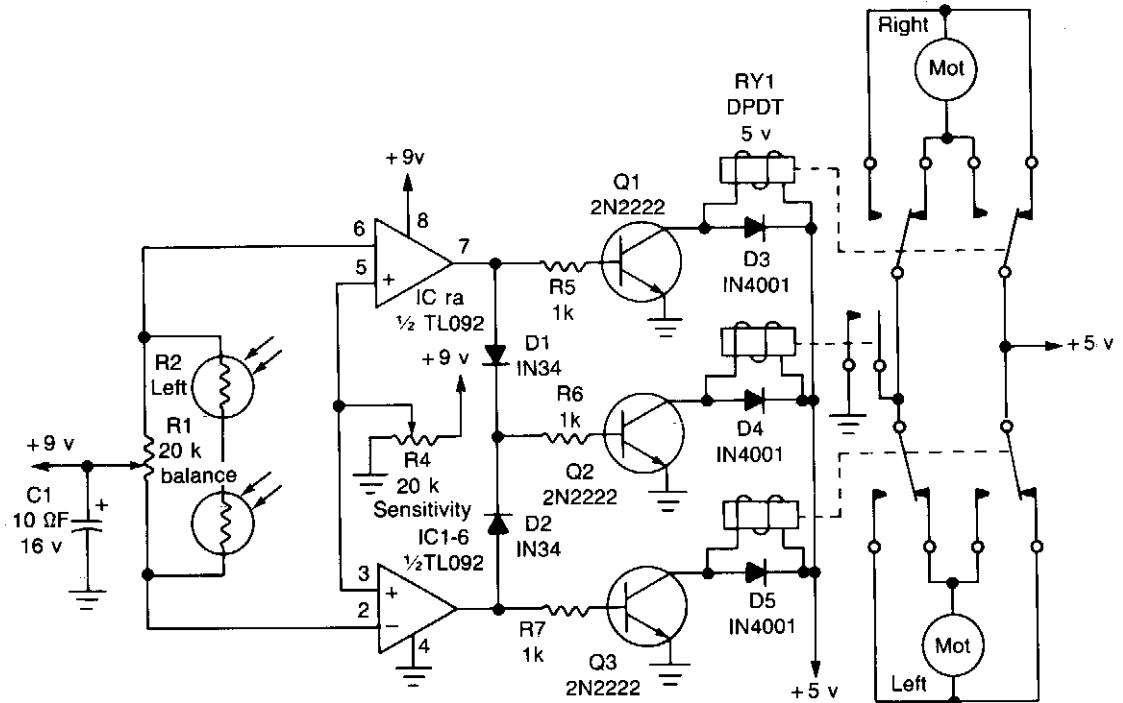

*Fig. 51-10*

## Circuit Notes

The circuit is light seeking; it will follow a flashlight around a darkened room. A pair of photocells determine the direction in which the robot will move. Each photocell is connected to an op amp configured as a comparator. When sufficient light falls on photocell R2, the voltage at the inverting input (pin 6) of IC1-a will fall below the voltage at the non-inverting input (pin 5), so the output of the comparator will go high, and transistors Q1 and Q2 will turn on. That will enable relays RY1 and RY2, and thereby provide power for the right motor. The robot will then turn left. Likewise, when light falling on R3 lowers its resistance, Q2 and Q3 will turn on, the left motor will energize, and the robot will turn right.

## SYNCHRONOUS PHOTOELECTRIC SWITCH


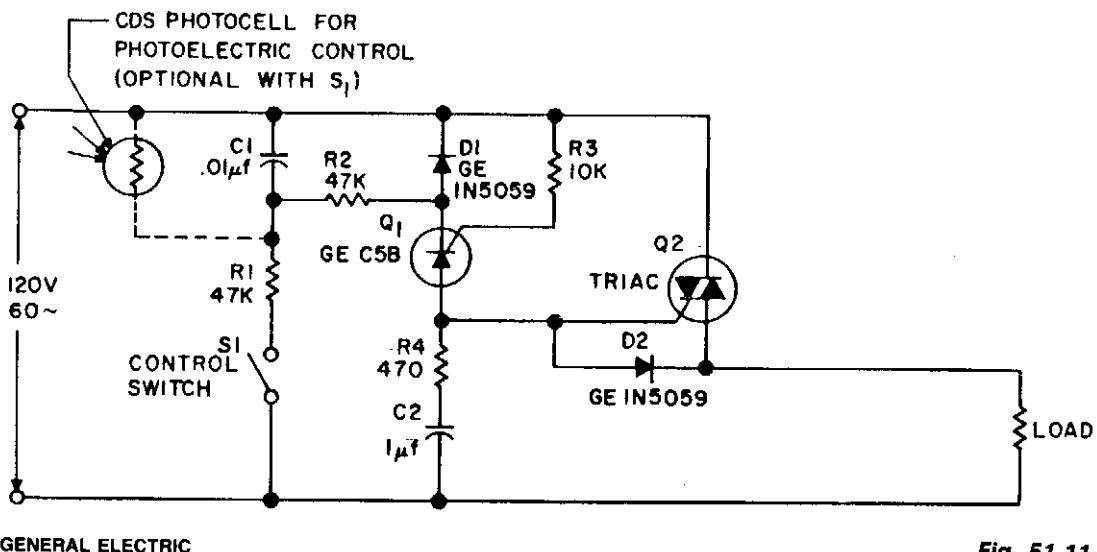


Fig. 51-11

### Circuit Notes

Synchronous switching is turning on only at the instant the ac supply voltage passes through zero, and turning off only when current passes through zero. This circuit provides this function in response to either a mechanical switch or a variable resistance such as a cadmium-sulfide photocell. This circuit produces the minimum disturbance to the power supply when switching, and always conducts an integral number of whole cycles. It is ideal for use wherever RFI and audio filtering is undesirable, where magnetizing inrush current of transformers causes nuisance fuse-blowing, and where sensitive equipment must operate in the vicinity of power switches.

## PHOTOCURRENT INTEGRATOR

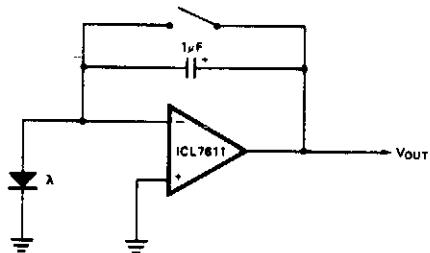

### Circuit Notes


Low leakage currents allow integration times up to several hours.

0307-32

INTERSIL

Fig. 51-12

## ROBOT EYES

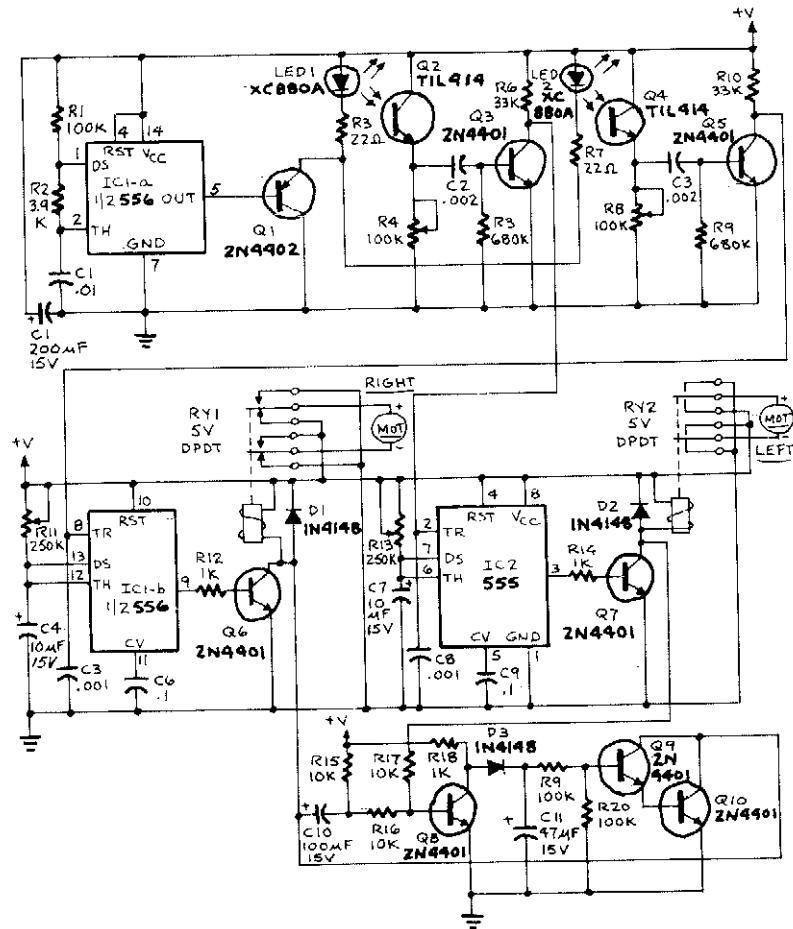


**Fig. 51-13**

**RADIO ELECTRONICS**

### Circuit Notes

An infrared LED and a phototransistor are used for each eye. Half of a 556 timer IC (IC1-a) functions as an astable multivibrator oscillating at a frequency of about 1 kHz. That IC drives transistor Q1 which in turn drives the two infrared LED's, LED1 and LED2. The right eye is composed of LED1 and Q2. If an obstacle appears in front of the right eye, pulses from LED1 are reflected by the obstacle and detected by Q2. The signal from Q2 is amplified by Q3, which triggers IC2, a 555. That IC operates in the monostable mode, and it provides a pulse output with a width of as much as 2.75 seconds, depending on the setting of R11. That pulse output energizes relay RY1, and that reverses the polarity of the voltage applied to the motor. Corresponding portions of the circuit of the left eye operate in the same fashion, using the unused half of the 556 (IC1-b). That action causes the robot to turn away from an obstacle.

## MODULATED LIGHT-BEAM CIRCUIT CANCELS AMBIENT LIGHT EFFECTS

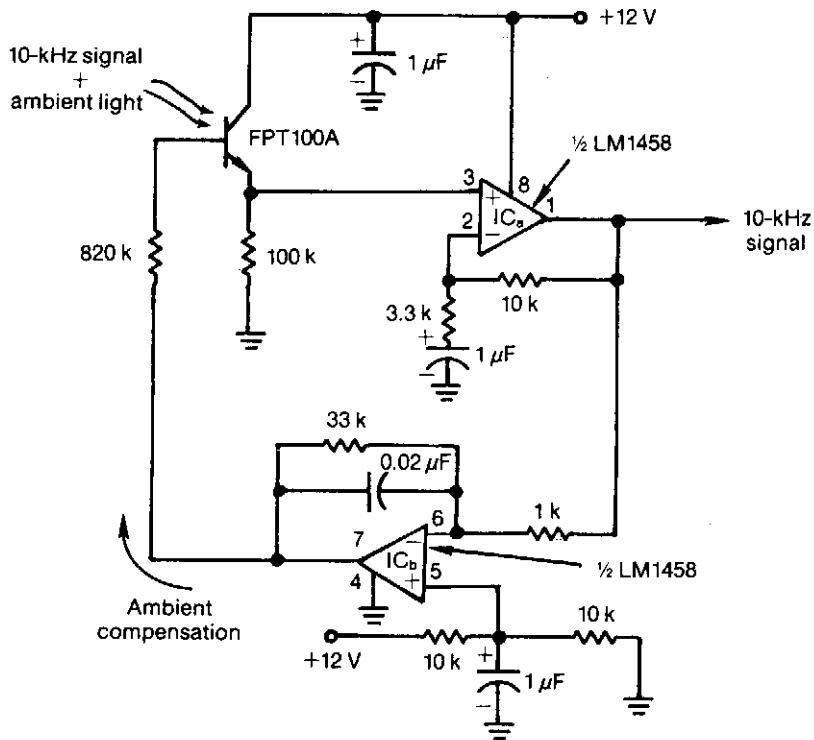


**Fig. 51-14**

ELECTRONIC DESIGN

### Circuit Notes

Feedback control of the phototransistor in this optical detector helps negate the effects of varying ambient light sources. The output of a modulated visible-light LED is detected, amplified, buffered, and fed through a low-pass filter. Ambient light signals below the LED's 10-kHz modulating rate reach the detector's base out of phase with incoming ambient light and cancel the undesired effects.
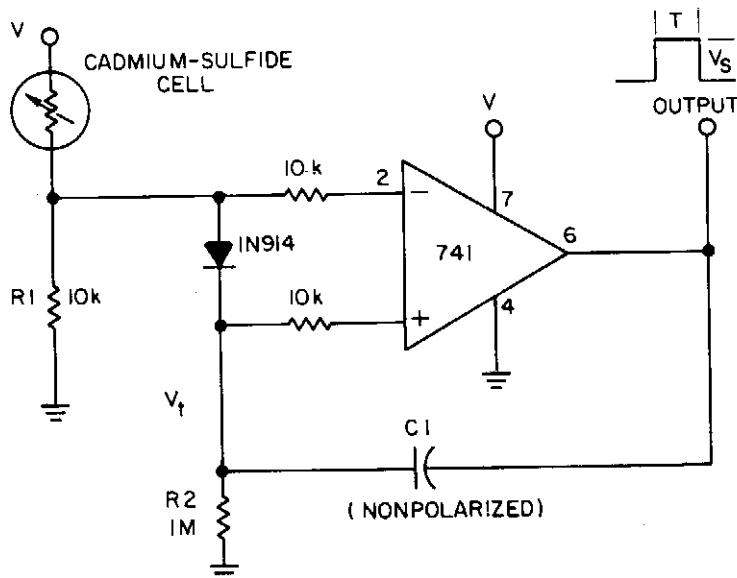
## MONOSTABLE PHOTOCELL CIRCUIT HAS SELF-ADJUSTING TRIGGER LEVEL




ELECTRONIC DESIGN

*Fig. 51-15*

### Circuit Notes

A photocell circuit provides automatic threshold adjustment. Monostable action prevents undesired retrigging of the output. With only one op amp IC, the circuit offers: Automatic adjustment of its trigger level to accommodate various light sources, changes in ambient light and misalignments; A built-in monostable action to provide only a single output pulse during a preset time; Feedback action to raise the threshold level after triggering and to speed switching. The feedback also eliminates the circuit's tendency to oscillate during switching.
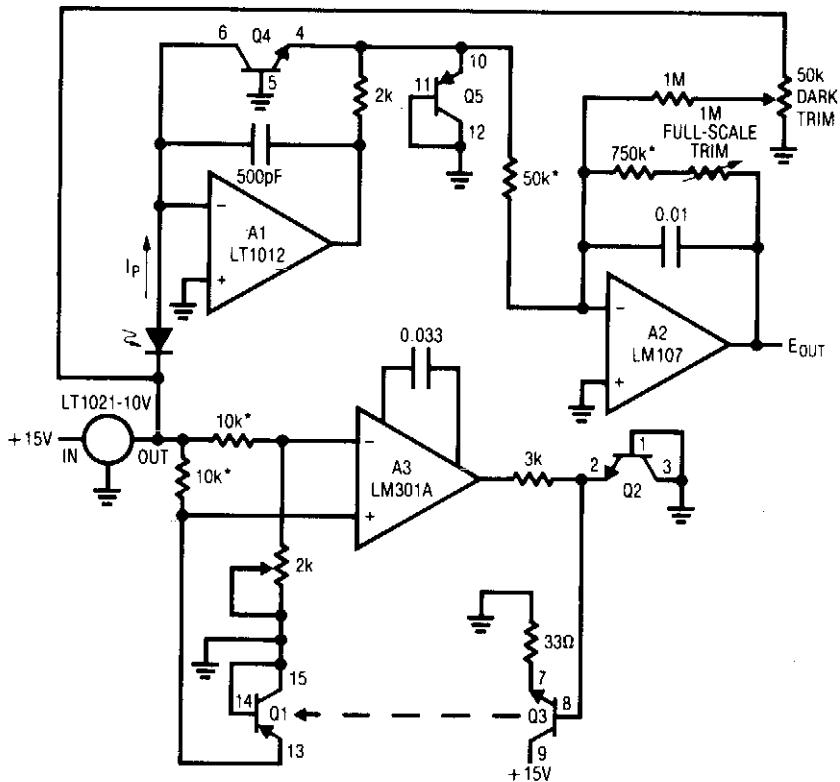
## THERMALLY STABILIZED PIN PHOTODIODE SIGNAL CONDITIONER



LINEAR TECHNOLOGY CORPORATION

**Fig. 51-16**

### Circuit Notes

The photodiode specified responds linearly to light intensity over a 100 dB range. Digitizing the diodes linearly amplified output would require an A-D converter with 17 bits of range. This requirement can be eliminated by logarithmically compressing the diode's output in the signal conditioning circuitry. A1 and Q4 convert the diode's photocurrent to voltage output with a logarithmic transfer function. A2 provides offsetting and additional gain. A3 and its associated components form a temperature control loop

RESPONSE DATA		
LIGHT (900 $\mu$ M)	DIODE CURRENT	CIRCUIT OUTPUT
1mW	350 $\mu$ A	10.0V
100 $\mu$ W	35 $\mu$ A	7.85V
10 $\mu$ W	3.5 $\mu$ A	5.70V
1 $\mu$ W	350nA	3.55V
100nW	35nA	1.40V
10nW	3.5nA	-0.75V

 = HP-5082-4204 PIN PHOTODIODE.

Q1-Q5 = CA3096.  
CONNECT SUBSTRATE OF CA3096  
ARRAY TO Q4'S EMITTER.  
\*1% RESISTOR

which maintains Q4 at constant temperature (all transistors in this circuit are part of a CA3096 monolithic array). The 0.033  $\mu$ F value at A3's compensation pins gives good loop damping if the circuit is built using the array's transistors in the location shown. Because of the array die's small size, response is quick and clean. A full-scale step requires only 250 ms to settle to final value. To use this circuit, first set the thermal control loop. To do this, ground Q3's base and set the 2 k pot so A3's negative input voltage is 55 mV above its positive input. This places the servo's setpoint at about 50°C (25°C ambient +  $(2.2 \text{ mV}/\text{ }^{\circ}\text{C}) \times 25^{\circ}\text{C}$  rise = 55 mV = 50°C). Unground Q3's base and the array will come to temperature. Next, place the photodiode in a completely dark environment and adjust the "dark trim" so A2's output is 0 V. Finally, apply or electrically simulate 1 mW of light and set the "full-scale" trim for 10 V out. Once adjusted, this circuit responds logarithmically to light inputs from 10nW to 1mW with an accuracy limited by the diode's 1% error.

# **52**

## **Logic Amplifiers**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.


- Low Power Inverting Amplifier with Digitally Selectable Gain
- Low Power Binary to  $10^N$  Gain Low Frequency Amplifier
- Low Power Non-Inverting Amplifier with Digitally Selectable Inputs and Gain
- Programmable Amplifier
- A Precision Amplifier with Digitally Programmable Inputs and Gains

## LOW POWER INVERTING AMPLIFIER WITH DIGITALLY SELECTABLE GAIN

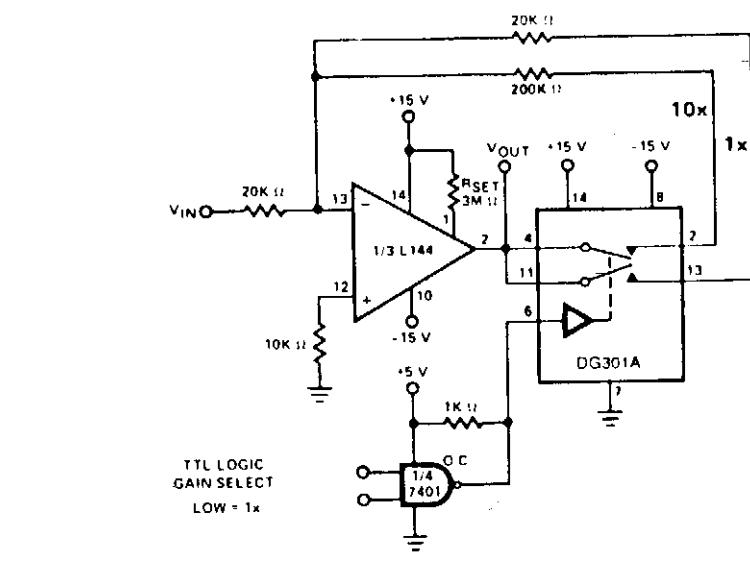

**Fig. 52-1**

## LOW POWER BINARY TO $10^n$ GAIN LOW FREQUENCY AMPLIFIER

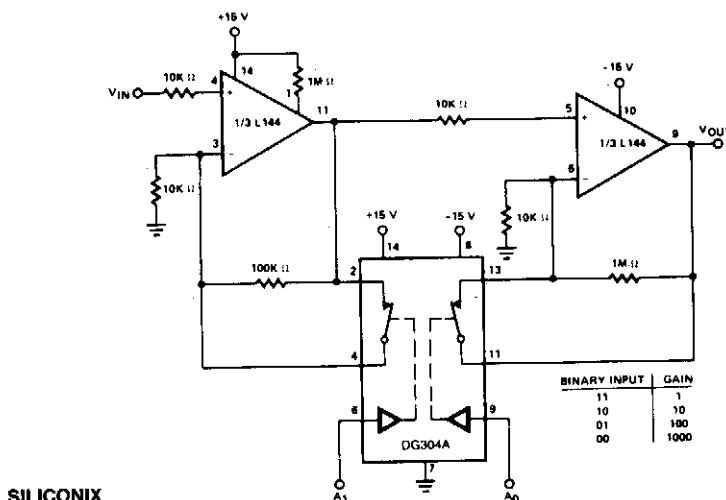


**Fig. 52-2**

### Circuit Notes


Gain increases by decades as the binary input decreases from 1,1 to 0,0. Minimum gain is 1 and maximum gain is 1000. Since the switch is static in this type of amplifier the power dissipation of the switch will be less than a tenth of a milliwatt.

## LOW POWER NON-INVERTING AMPLIFIER WITH DIGITALLY SELECTABLE INPUTS AND GAIN

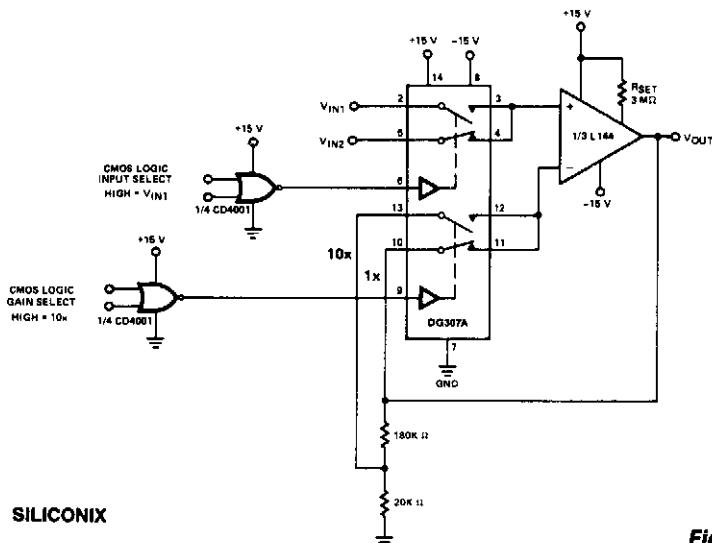

*Fig. 52-3*

## PROGRAMMABLE AMPLIFIER

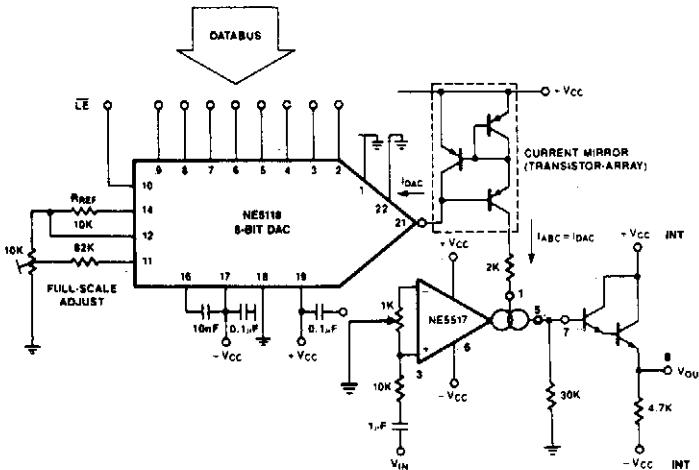


SIGNETICS

*Fig. 52-4*

### Circuit Notes

The intention of the following application shows how the NE5517 works in connection with a DAC. In the application, the NE5118 is used—an 8-bit DAC with current output—its input register making this device fully  $\mu\text{P}$ -compatible. The circuit consists of three functional blocks; the NE5118 which generates a control current equivalent to the applied data byte, a current mirror, and the NE5517.

# A PRECISION AMPLIFIER WITH DIGITALLY PROGRAMMABLE INPUTS AND GAIN

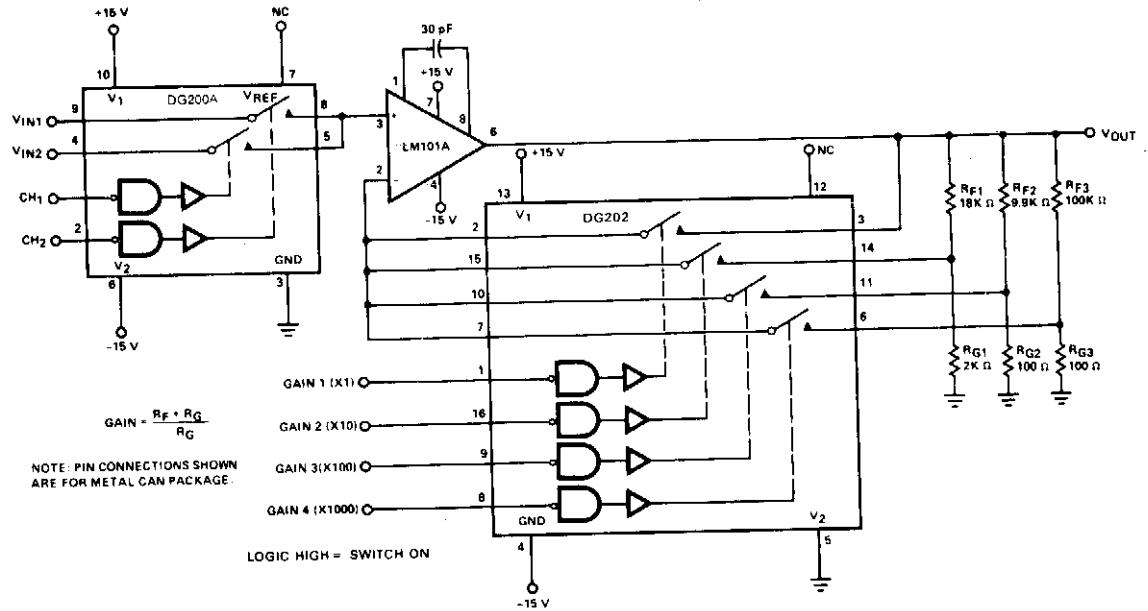

**Fig. 52-5**

SILICONIX

# **53**

## **LVDT Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

LVDT Driver Demodulator  
Linear Variable Differential Transformer Signal  
Conditioner

## LVDT DRIVER DEMODULATOR


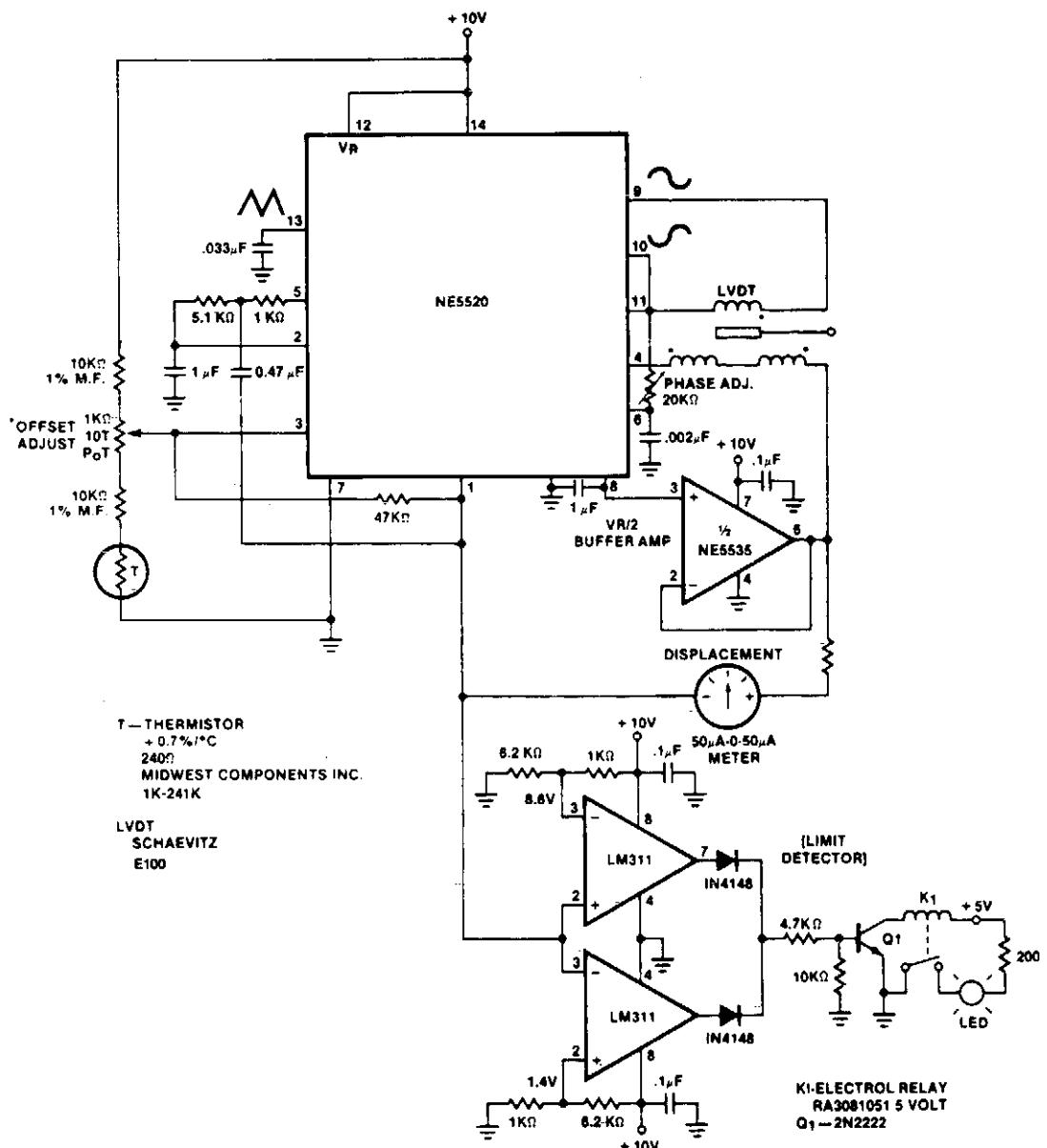


Fig. 53-1
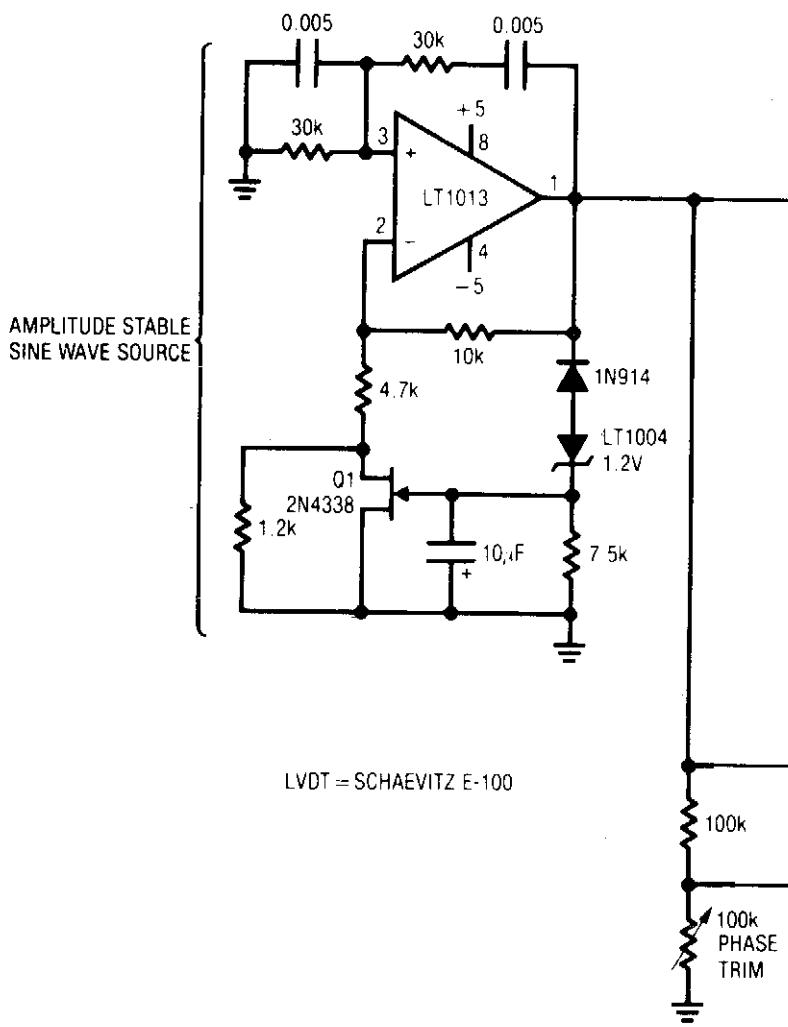
## LINEAR VARIABLE DIFFERENTIAL TRANSFORMER SIGNAL CONDITIONER




LINEAR TECHNOLOGY CORPORATION

*Fig. 53-2*
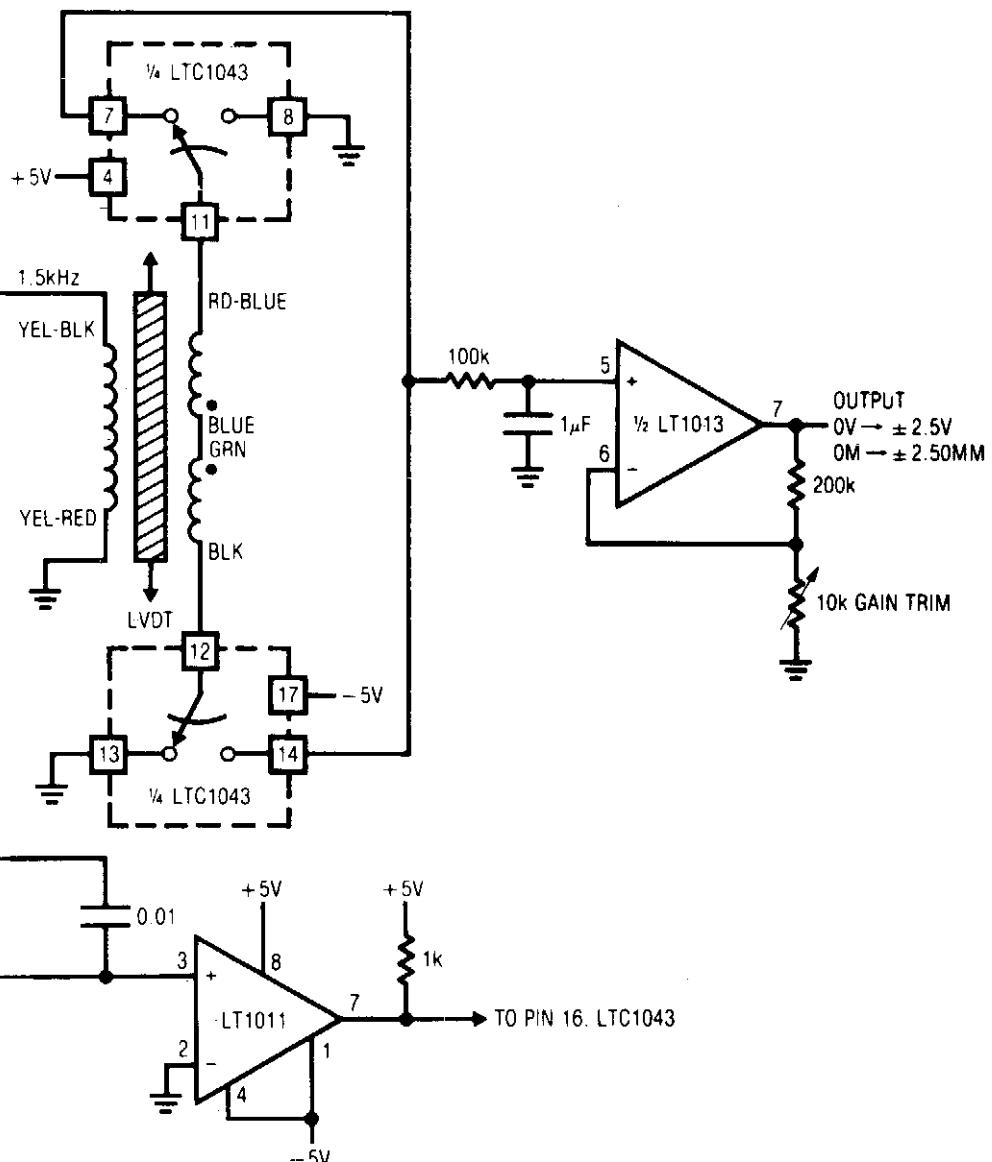
### Circuit Notes

A1 and its associated components furnish an amplitude stable sine wave source. A1's positive feedback path is a Wein bridge, tuned for 1.5 kHz, Q1, the LT1004 reference, and additional components in A1's negative loop unity-gain stabilize the amplifier. A1's output an amplitude stable sine wave, drives the LVDT. C1 detects zero crossings and feeds the LTC1043 clock pin. A speed-up network at C1's input compensates LVDT phase shift, synchronizing the LTC1043's clock to the transformer's output zero



crossings. The LTC1043 alternately connects each end of the transformer to ground, resulting in positive half-wave rectification at pins 7 and 14. These points are summed at a low-pass filter which feeds A2. A2 furnishes gain scaling and the circuit's output. The LTC1043's synchronized clocking means the information presented to the low-pass filter is amplitude and phase sensitive. The circuit output indicates how far the core is from center and on which side. To calibrate this circuit, center the LVDT core in the transformer and adjust the phase trim for 0 V output. Next, move the core to either extreme position and set the gain trim for 2.50 V output.

# **54**

## **Measuring and Test Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Magnetometer
- Resistance-Ratio Detector
- Continuity Tester for PCB's
- Wire Tracer
- Diode Testing
- Measuring Phase Difference from  $0^\circ$  to  $\pm 180^\circ$
- Ground Tester
- Making Slow Logic Pulses Audible
- Unidirectional Motion Sensor

## MAGNETOMETER

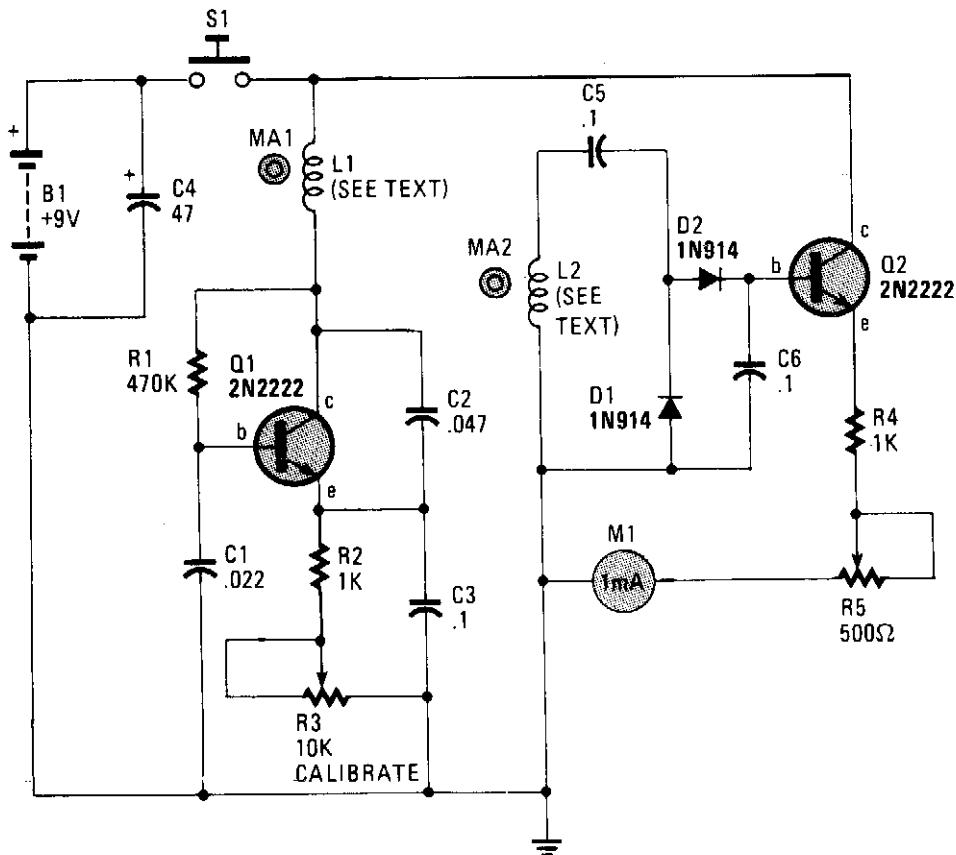


HANDS-ON ELECTRONICS

Fig. 54-1

### Circuit Notes

The circuit uses two general-purpose npn transistors, Q1 and Q2, and a special hand-wound, dual-coil probe ferrets out the magnetism. Q1 and its associated components form a simple VLF oscillator circuit, with L1, C2, and C3 setting the frequency. The VLF signal received by the pickup coil, L2, is passed through C5 and rectified by diodes D1 and D2. The small dc signal output from the rectifier is fed to the base of Q2 (configured as an emitter follower), which is then fed to a 0-1 mA meter, M1.

## RESISTANCE-RATIO DETECTOR

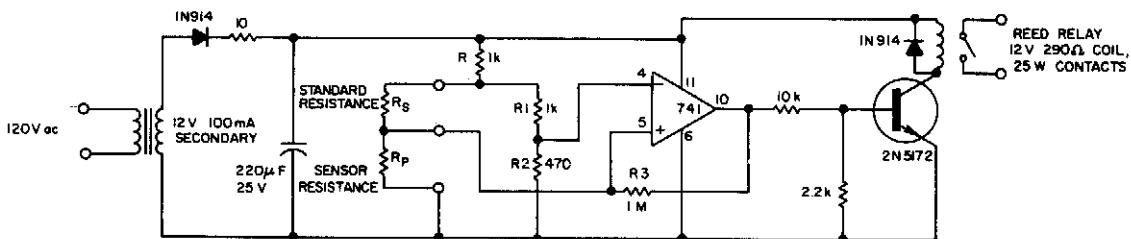

ELECTRONIC DESIGN

**Fig. 54-2**


### Circuit Notes

Applications such as photoelectric control, temperature detection and moisture sensing require a circuit that can accurately detect a given resistance ratio. A simple technique that uses an op amp as a sensing element can provide 0.5% accuracy with low parts cost. The reed-relay contacts close when the resistance of the sensor  $R_p$  equals 47% of the standard  $R_s$ . Adjusting either  $R_1$  or  $R_2$  provides a variable threshold; the threshold is controlled by varying  $R_3$ . For the most part, the type of resistors used for  $R_1$  and  $R_2$  determines the accuracy and stability of the circuit. With metal-film resistors, less than 0.5% change in ratio sensing occurs over the commercial temperature range (0 to 70°C) with ac input variations from 105 to 135 V.

## CONTINUITY TESTER FOR PCB'S
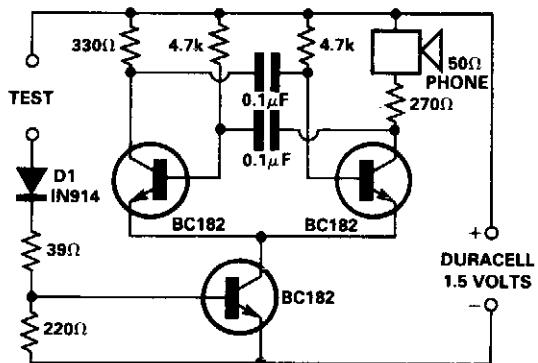
### Circuit Notes


The continuity tester is for tracing wiring on printed circuit boards. It only consumes any appreciable power when the test leads are shorted, so no On/Off switch is used or required. The applied voltage at the test terminals is insufficient to turn on diodes or other semiconductors. Resistors below 50 ohms act as short circuit; above 100 ohms as open circuit. The circuit is a simple multivibrator—T1 and T2, which are switched on by transistor T3. The components in the base of T3 are D1, R1, R2, and the test resistance. With a 1.5 volt supply, there is insufficient voltage to turn on a semiconductor connected to the test terminals. The phone is a telephone earpiece but a 30 ohm speaker would work equally as well.



ELECTRONIC ENGINEERING

**Fig. 54-3**

## WIRE TRACER

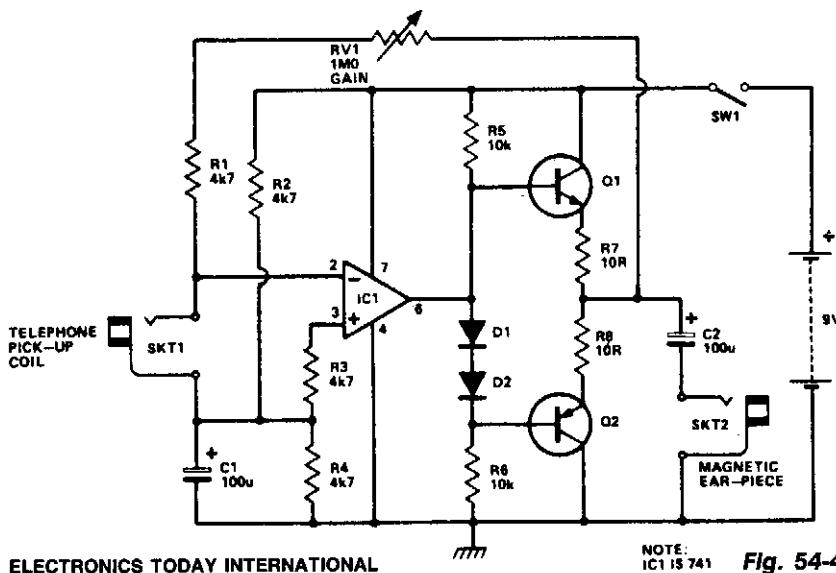


**Fig. 54-4**

### Circuit Notes


The tracer detects the weak magnetic field of any current-carrying house wiring and amplifies this signal to a level that is adequate for driving a magnetic earpiece. The unit uses a telephone pick-up coil to detect the magnetic field.

## DIODE TESTING

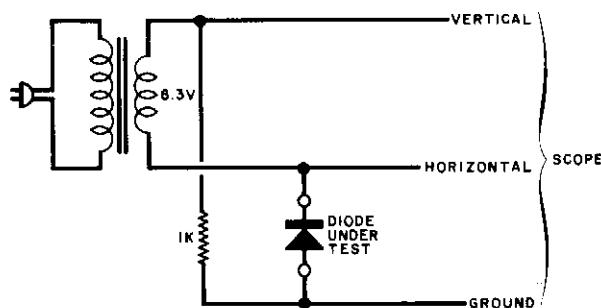

**Fig. 54-5**





POPULAR ELECTRONICS CAL

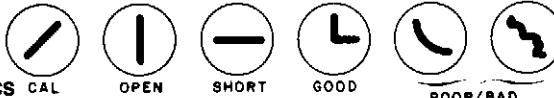

### Circuit Notes

The circuit will display curves on a scope, contingent on the state of the diode. To "calibrate," substitute a 1000-ohm resistor for the diode and adjust the scope gains for a 45-degree line. The drawings show some expected results.
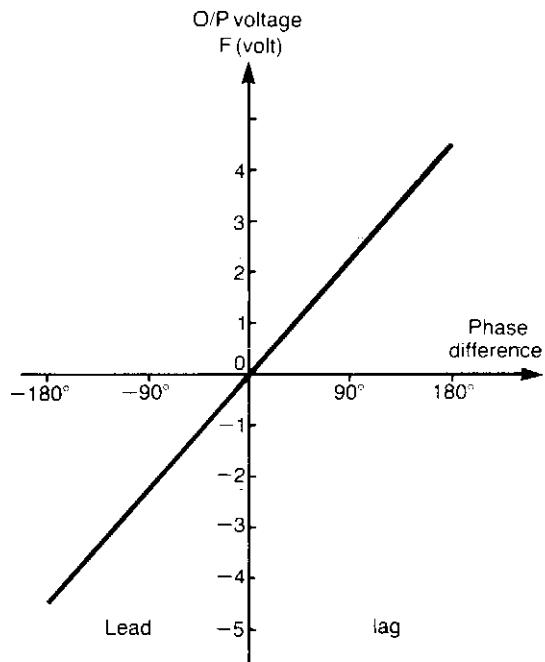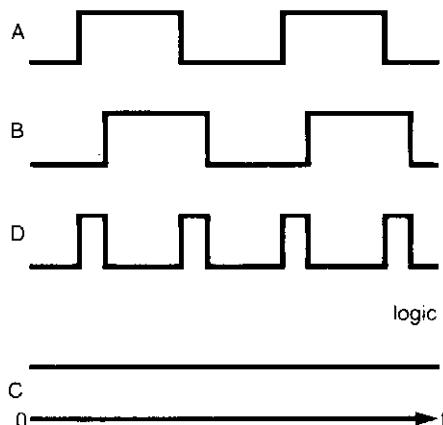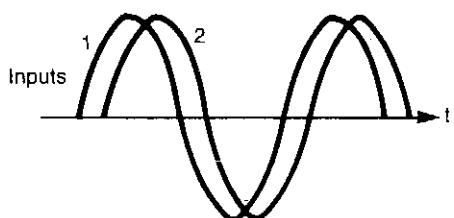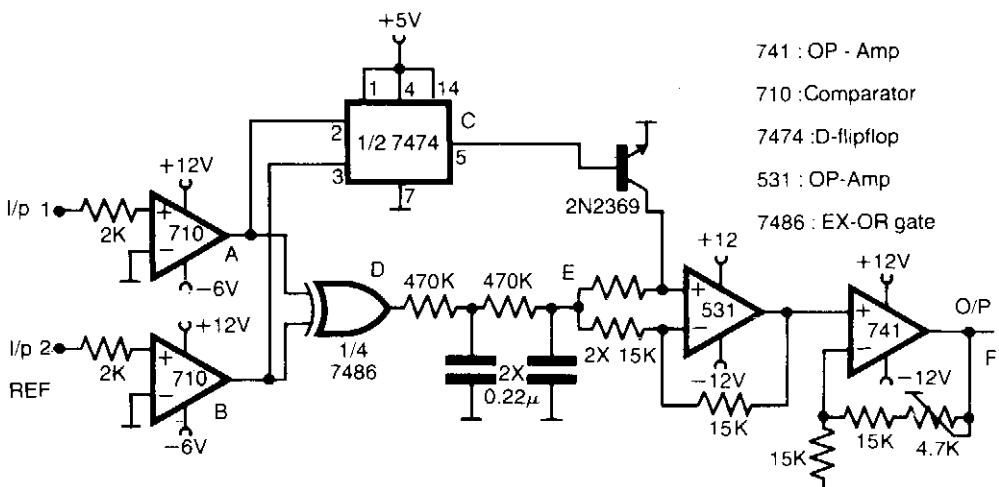
### MEASURING PHASE DIFFERENCE FROM $0^\circ$ to $\pm 180^\circ$




## MEASURING PHASE DIFFERENCE FROM $0^\circ$ to $\pm 180^\circ$ , Continued.

### Circuit Notes

This method is capable of measuring phase between 0 to  $\pm 180^\circ$ . The generated square waves A and B are fed to a D flip-flop which gives an output C equal to logic 1 when input 1 leads input 2 and equal to logic 0 in case of lagging. When C = logic 0, the output of the amplifier F will be positive proportional to the average value E of the output of the EX-OR. When C = logic 1, F will be negative and also proportional to E by the same factor. Hence, the output of the meter is positive in case of lagging and negative for leading. The circuit is tested for sinusoidal inputs and indicates a linearity within 1%. Measurements are unaffected by the frequency of the inputs up to 75 kHz.

## GROUND TESTER

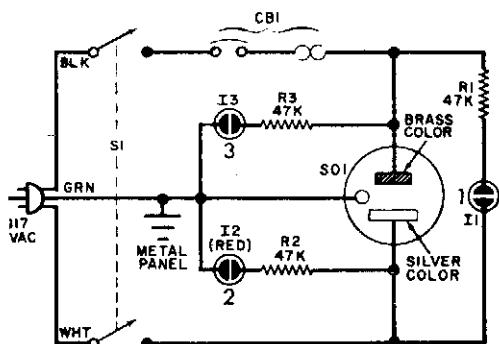


POPULAR ELECTRONICS

Fig. 54-7

### Circuit Notes

The circuit is simple and foolproof if wired correctly. Under normal conditions, only lamps 1 and 3 should be lit. If lamp 2 comes on, the cold lead is 117 volts above ground.

## MAKING SLOW LOGIC PULSES AUDIBLE

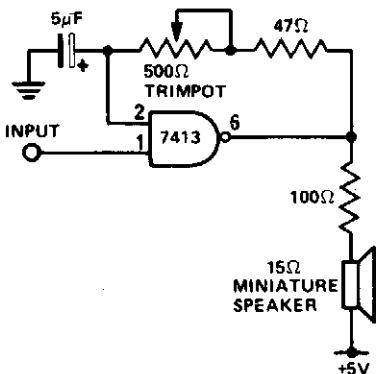


ELECTRONICS TODAY INTERNATIONAL

Fig. 54-8

### Circuit Notes

This circuit is useful for monitoring slow logic pulses as a keying monitor or digital clock alarm. The Schmitt trigger is connected as an oscillator. The trimpot controls the pitch of the output. When the input goes high, the circuit will oscillate.

### UNIDIRECTIONAL MOTION SENSOR

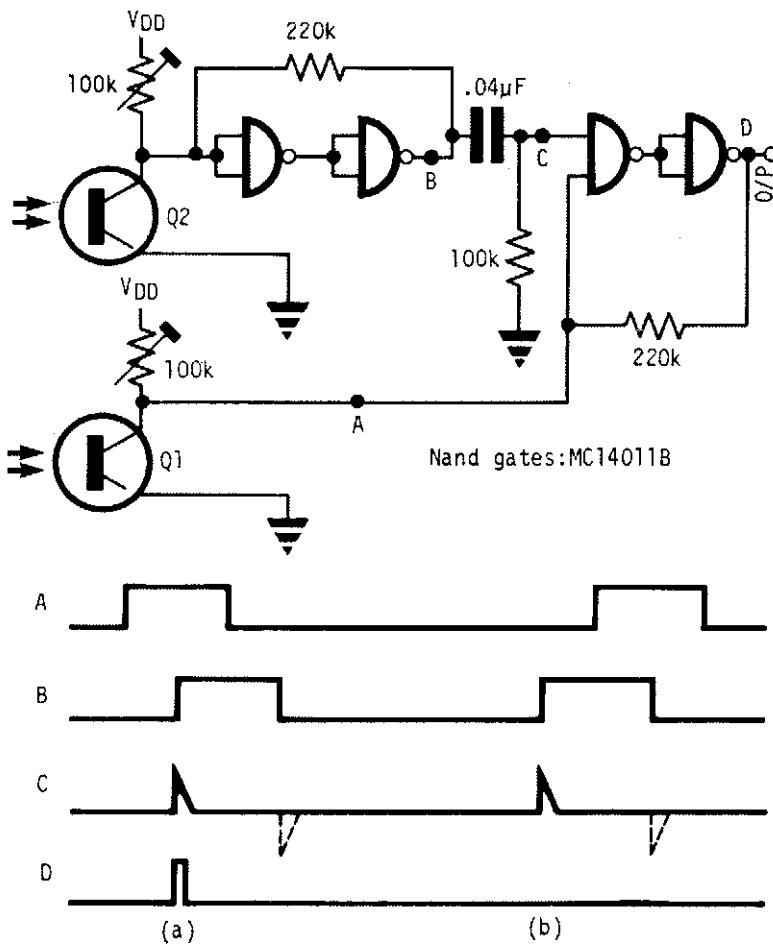

ELECTRONIC ENGINEERING

*Fig. 54-9*

#### Circuit Notes

This circuit detects an object passing in one direction but ignores it going the opposite way. Two sensors define the sense of direction. The object blocks the light to phototransistor Q1 or Q2 first dependent on the direction of approach. When the object passes Q1 then Q2, an output pulse is generated at D; while no pulse is seen at D as the object passes Q2 then Q1. Object length (measured along the direction of the two sensors) should be greater than the separation of the two sensors Q1 and Q2.

# **55**

## **Medical Electronics Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Heart Rate Monitor  
Medical Instrument Preamplifier

## HEART RATE MONITOR

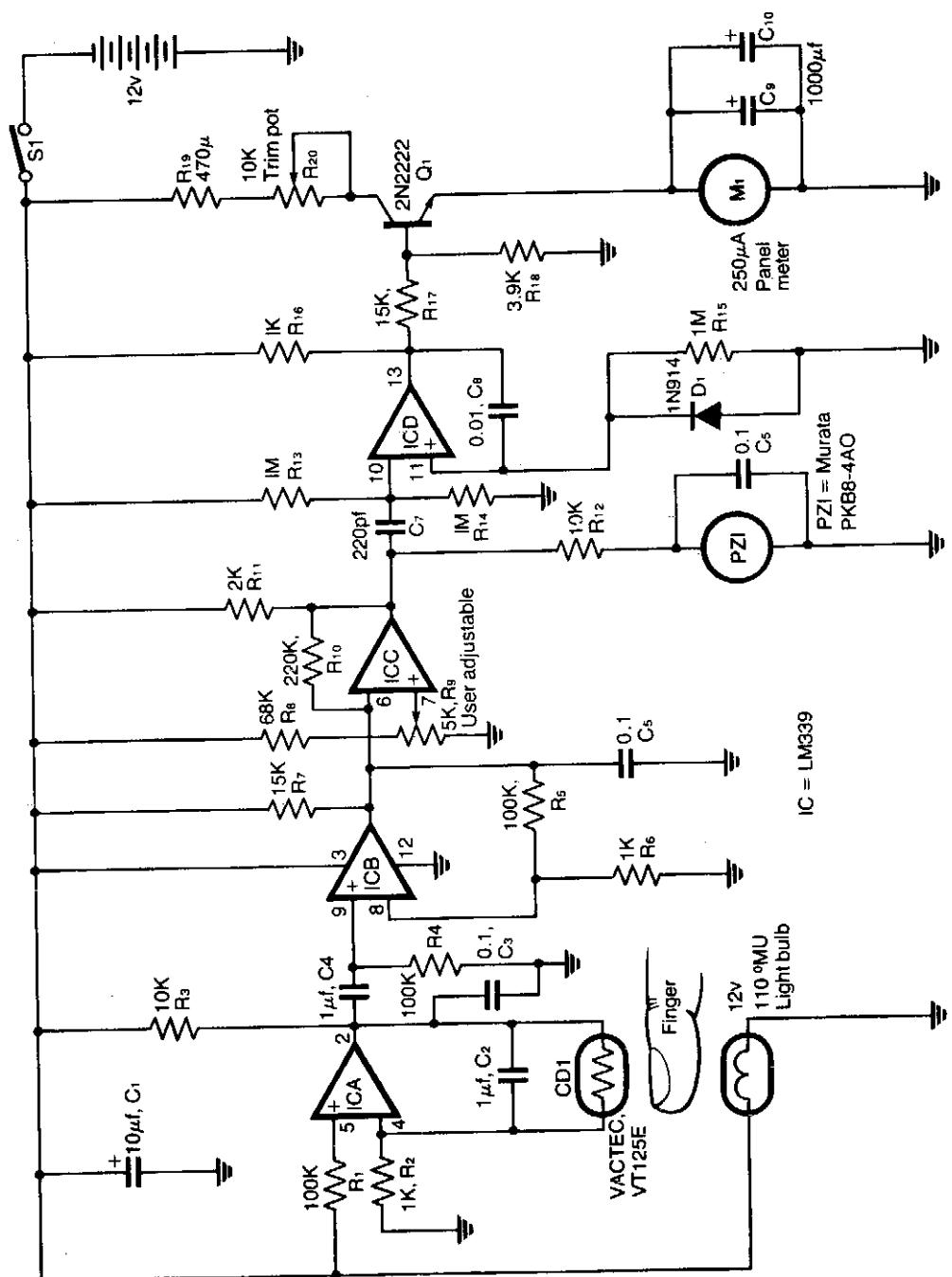


Fig. 55-1


ELECTRONIC ENGINEERING

## HEART RATE MONITOR, Continued.

### Circuit Notes

Light filtering through the finger tip is detected by the cadmium sulphide photoresistor CD1 which forms the feedback network for transducer amplifier section ICA producing a weak signal which is further amplified by ICB. This signal is now compared against a user adjusted threshold, comparator ICD triggers gating on the piezoelectric buzzer PZ1. On each falling edge of the comparator's output signal one-shot multivibrator ICD produces a  $2\ \mu\text{s}$  pulse which is inverted by Q1 and averaged by the RC network consisting of M1, C6 and C7. The 10 K trimpot R20 in Q1's collector circuit sets the scale factor for M<sub>1</sub> where full scale is 150 beats per minute.

## MEDICAL INSTRUMENT PREAMPLIFIER

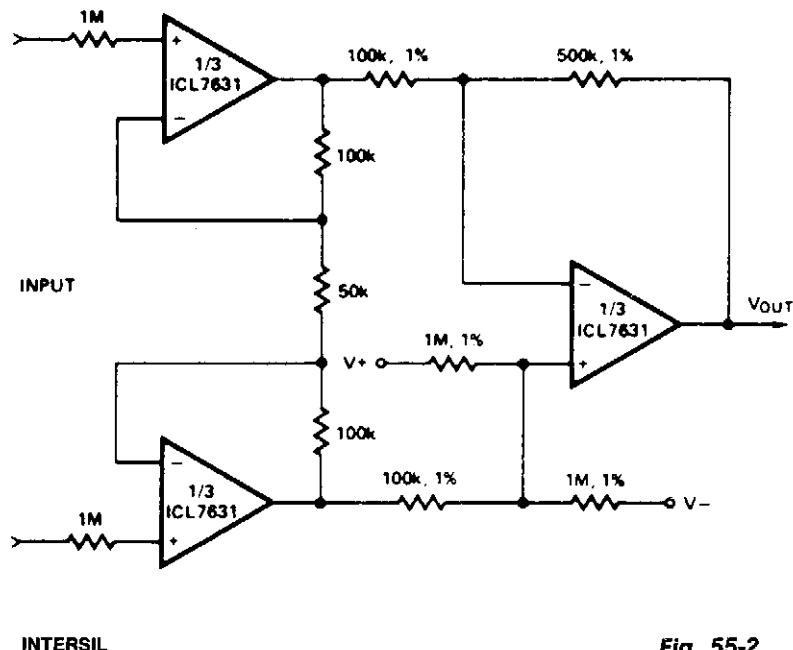

INTERSIL

Fig. 55-2

### Circuit Notes

Note that  $A_{VOL} = 25$ ; single Ni-cad battery operation. Input current (from sensors connected to the patient) is limited to less than  $5\ \mu\text{A}$  under fault conditions.

# **56**

## **Metal Detectors**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Metal Locator II  
Metal Locator

## METAL LOCATOR II

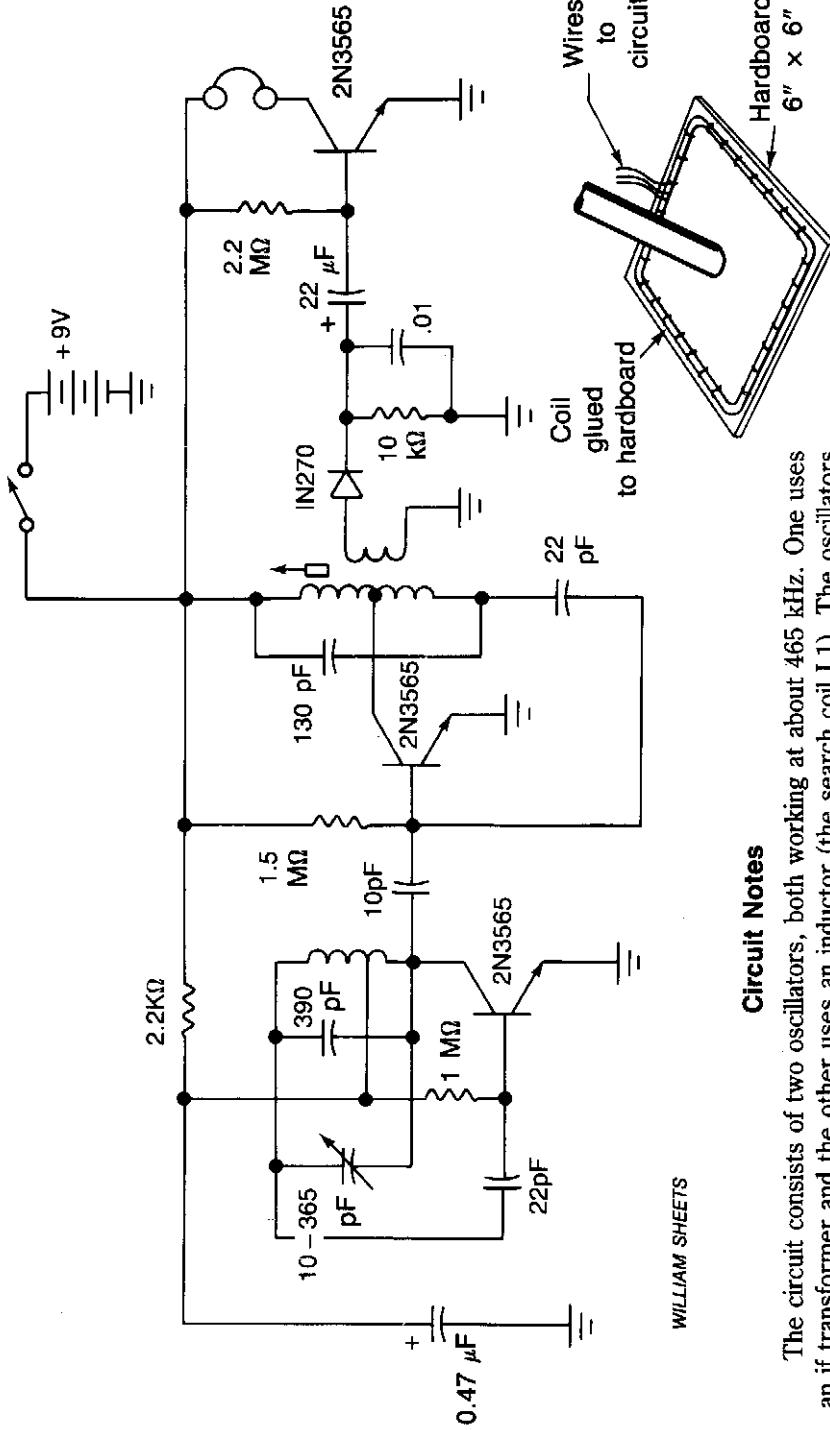


### Circuit Notes

The circuit consists of two oscillators, both working at about 465 kHz. One uses an if transformer and the other uses an inductor (the search coil L1). The oscillators are coupled by a capacitor (10 pF). A beat note (produced if the two oscillators are working closely together) is detected by the diode and fed to the headphone amplifier and the 22 μF capacitor. The search coil oscillator is tuned by a 10-365 pF variable capacitor. The search coil comprises 22 turns of wire (any gauge between 24 swg and 36 swg enameled) center tapped. The wire should be wound on a temporary form then taped and glued to a piece of hardboard. The coil size should be about 6" x 6". Headphones should be high impedance.

Fig. 56-1

## METAL LOCATOR

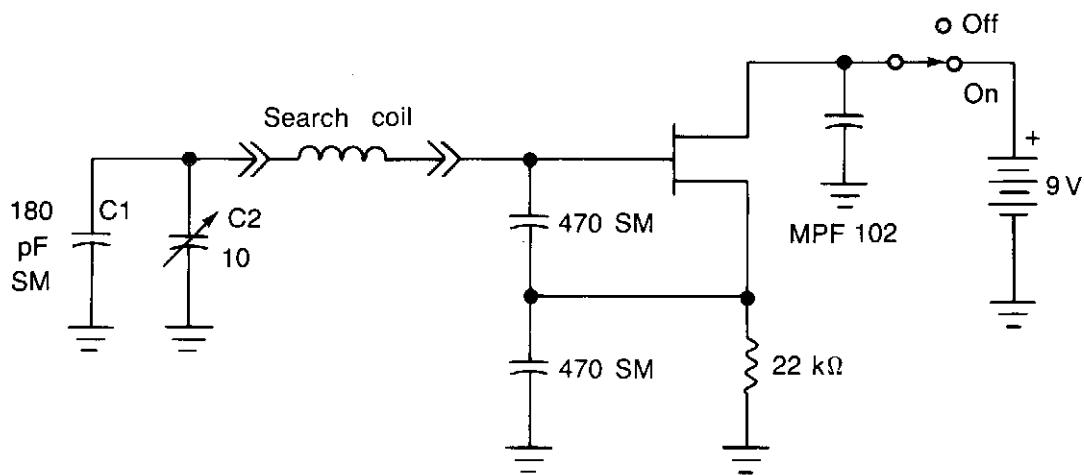

WILLIAM SHEETS

**Fig. 56-2**

### Circuit Notes

The search coil, C1 and C2 form a tuned circuit for the oscillator which is tuned near the center of the broadcast band. Tune a portable radio to a station near the middle of the band, then tune C2 until a squeal is heard as the two signals mix to produce a beat (heterodyne) note. Metal near the search coil will detune the circuit slightly, changing the pitch of the squeal. The search coil is 20 turns of number 30 enameled wire, wound on a 6" x 8" wood or plastic form. It is affixed at the end of a 30" to 40" wooden or plastic pole, and connected to the remainder of the metal detector circuit through a coaxial cable.

# **57**

## **Metronomes**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Simple Metronome  
Metronome I  
Ac-Line Operated Unijunction Metronome  
Metronome II

## SIMPLE METRONOME

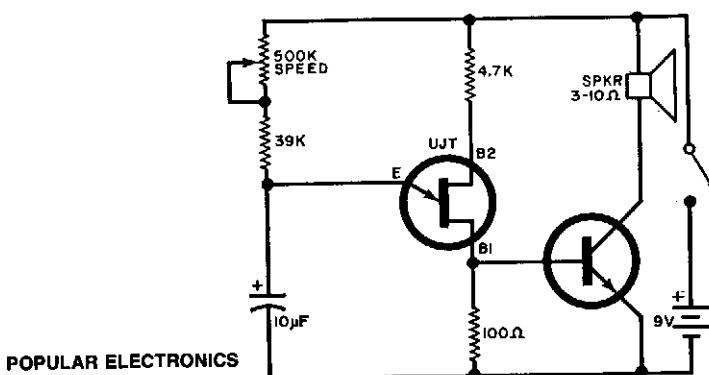

POPULAR ELECTRONICS


**Fig. 57-1**

### Circuit Notes

Adjustable from 15 to 240 beats per minute. The UJT oscillator output is applied to a general purpose npn transistor which drives the speaker.

UJT = 2N4871  
NPNxistor = TIP31

## METRONOME I

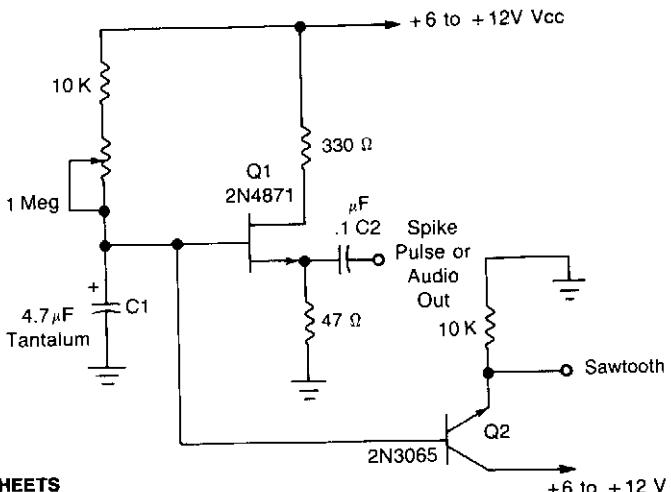


WILLIAM SHEETS

**Fig. 57-2**

### Circuit Notes

This simple oscillator uses a 2N4871 UJT to give pulses from 0.2 to about 20 Hz. A spike is available at C2, a sawtooth at the emitter of Q2 of about 2-3 V p-p, depending on  $V_{CC}$ .

### AC-LINE OPERATED UNIJUNCTION METRONOME

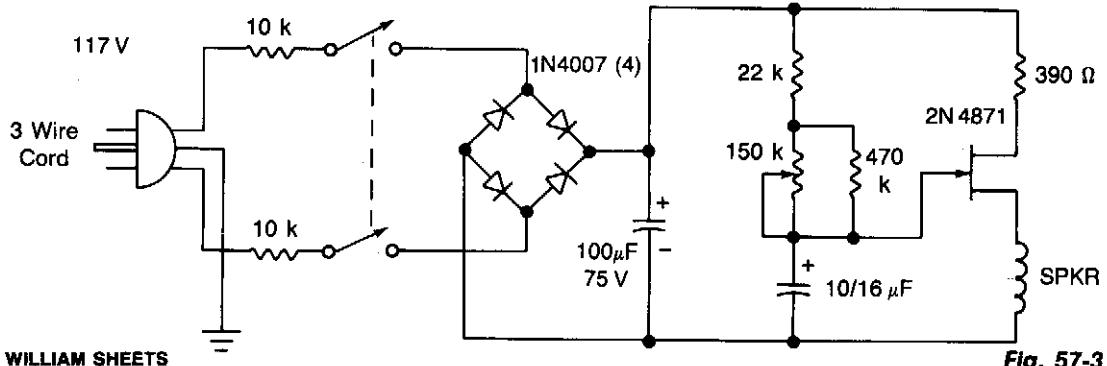


**Fig. 57-3**

#### Circuit Notes

The UJT-oscillator frequency is determined by the  $100\ \mu\text{F}$  capacitor and the effective resistance of the  $22\ \text{k}$  and  $470\ \text{k}$  resistors and the potentiometer. Rate can be varied from 42 to 208 beats/minute. The circuit should be housed in an insulated box for safety, or use ground (3-wire cord).

### METRONOME II

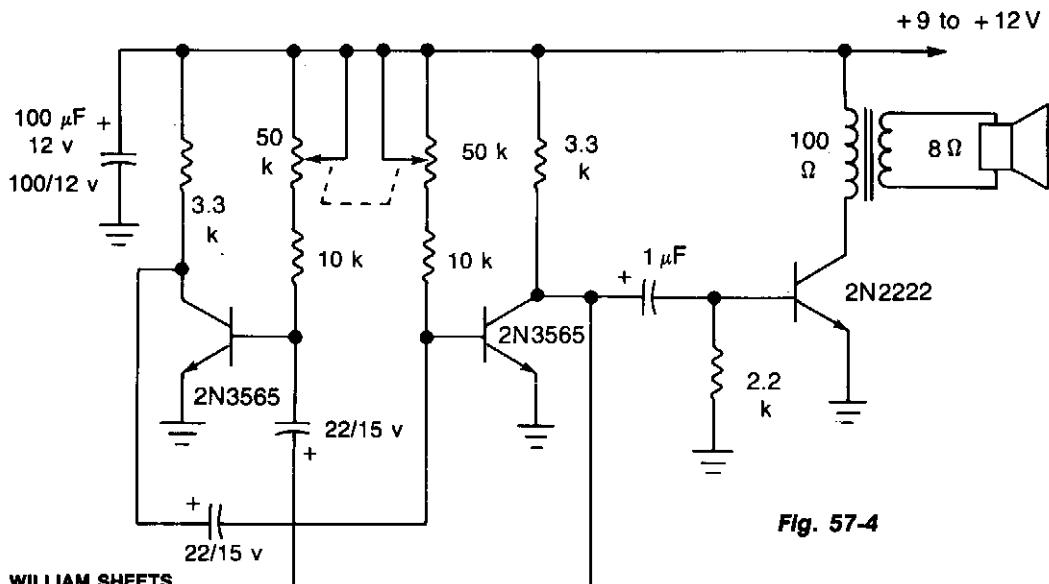

**Fig. 57-4**

#### Circuit Notes

This simple circuit uses a multivibrator to generate the beats and a subsequent audio amplifier stage to increase the output level. Range of adjustment is approximately from 40 to 200 beats per minute set by the gauged potentiometer.

# 58

## Miscellaneous Treasures

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Squib-Firing Circuit (I)

Squib-Firing Circuit (II)

Model Rocket Launcher

Push-On/Push Off Electronic Switch

Game Feeder Controller

Single LED Can Indicate Four Logic States

Inexpensive Radio-Control Uses Only SCR

Guitar and Bass Tuner

4-Channel Commutator

Two-Wire Tone Encoder

Differential Hold

5 MHz Phase-Encoded Data Read Circuitry

Shift Register

Power-On Reset


Noise Immune 60 Hz Line Sync

DC Static Switch (SCR Flip-Flop)

## SQUIB-FIRING CIRCUIT (I)
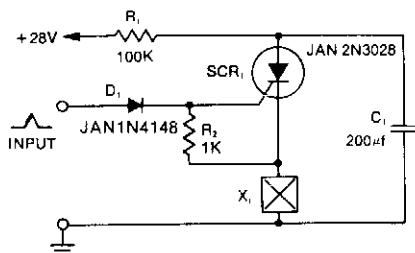
### Circuit Notes


Capacitor C1 is charged to +28 V through R1 and stores energy for firing the squib. A positive pulse of 1 mA applied to the gate of SCR1 will cause it to conduct, discharging C1 into the squib load X1. With the load in the cathode circuit, the cathode rises immediately to +28 V as soon as the SCR is triggered on. Diode D1 decouples the gate from the gate trigger source, allowing the gate to rise in potential along with the cathode so that the negative gate-to-cathode voltage rating is not exceeded. This circuit will reset itself after test firing, since the available current through R1 is less than the holding current of the SCR. After C1 has been discharged, the SCR automatically turns off—allowing C1 to recharge.



UNITRODE CORP.

**Fig. 58-1**

## SQUIB-FIRING CIRCUIT (II)

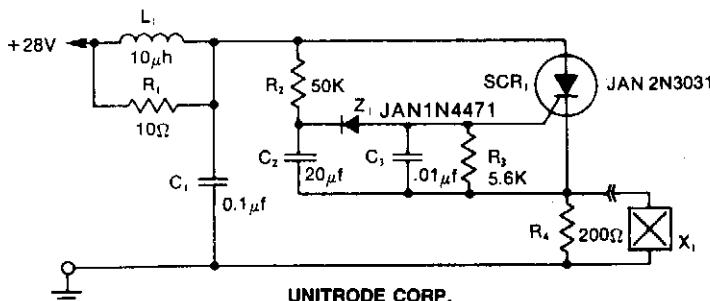


UNITRODE CORP.

**Fig. 58-2**

### Circuit Notes

The LRC input network limits the anode dv/dt to a safe value—below 30 V/μs. R1 provides critical damping to prevent voltage overshoot. While a simple RC filter section could be used, the high current required by the squib would dictate a small value of resistance and a much larger capacitor. Resistor R3 provides dc bias stabilization, while C3 provides stiff gate bias during the transient interval when anode voltage is applied. The SCR is fired one second after arming by means of the simple R2C2Z1 time delay network. R4 provides a load for the SCR for testing the circuit with the squib disconnected—limiting the current to a level well within the continuous rating of the SCR. The circuit can be reset by opening the +28 V supply and then re-arming.

## MODEL ROCKET LAUNCHER

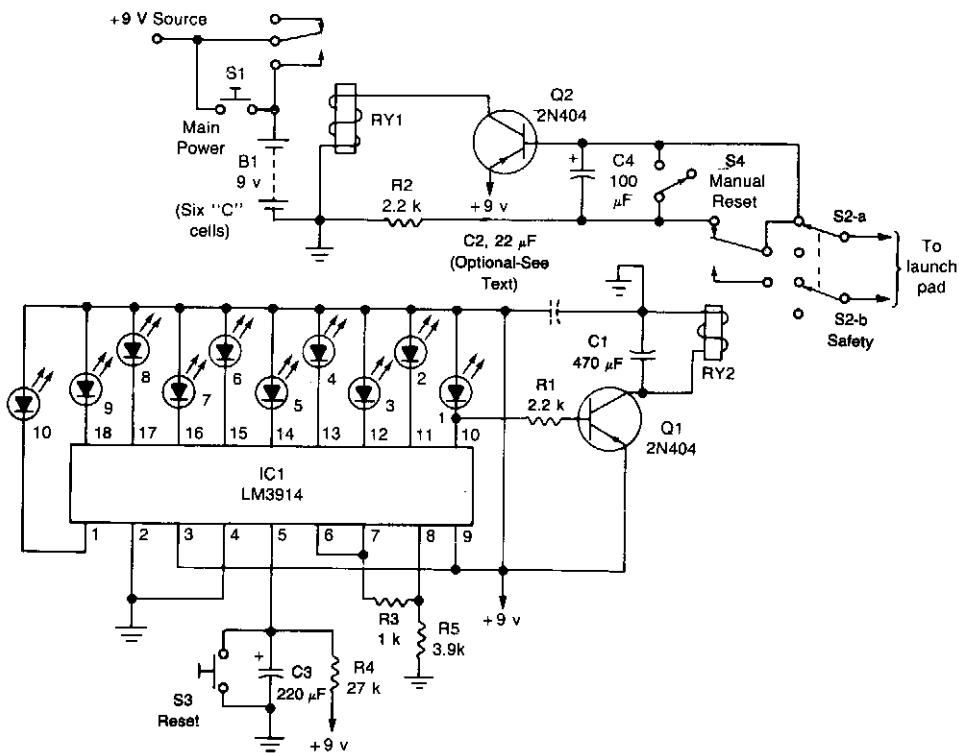


RADIO ELECTRONICS

**Fig. 58-3**

### Circuit Notes

The circuit consists of the launch timer itself and an automatic-off timer. When power is applied to that IC, the countdown LED's sequence is on until they are all lit. When the last one LED1, is fully lit, transistor Q1 saturates, energizing RY2. When that happens, a circuit between the lantern battery at the launch pad and the nickel-chromium wire is completed; the wire heats up as before, and the rocket is launched. Resistor R4 and capacitor C3 determine the countdown timing; with the values shown it should be approximately 10 seconds. Resistors R3 and R5 set the LED brightness. Safety is of the utmost importance. That's the purpose of the second half of the circuit. When RY2 opens, the current flow to Q2 is disrupted. But, because of the presence of R2 and C4, the transistor remains saturated for about 3 seconds. After that, however, the transistor stops conducting and RY1 is de-energized. That cuts off the power to the rest of the circuit, and RY2 de-energizes again, breaking the circuit to the launch pad. Switch S3 is used to reset the countdown. Once that is done, pressing S1 starts the launch sequence; the rest is automatic. Switch S4 is used to latch RY1 manually if needed.

## PUSH-ON/PUSH-OFF ELECTRONIC SWITCH

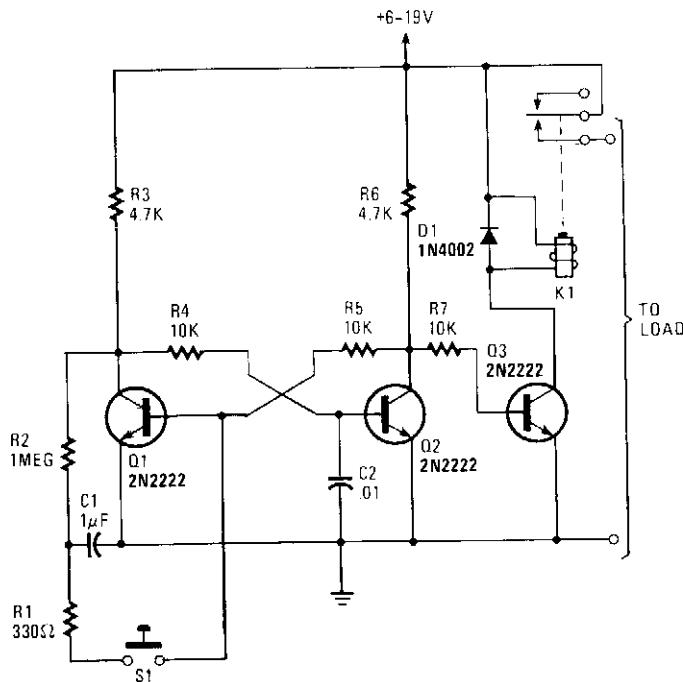


HANDS-ON ELECTRONICS

*Fig. 58-4*

### Circuit Notes

Transistors Q1 and Q2 make up the flip-flop while Q3 drives a reed relay. When power is first applied to the circuit, Q1 and Q3 are conducting and Q2 is cut off. Momentarily closing S1 causes the flip-flop to switch states—Q1 cuts off and Q2 conducts. When Q2 is conducting, its collector drops to around 0.6 volt. That prevents base current from flowing into Q3 so it is cut off, de-energizing relay K1. The flip-flop changes state every time S1 is pressed. Capacitors C1 and C2 ensure that Q1 is always the transistor that turns on when power is first applied to the circuit. When power is first applied to the basic flip-flop, the initial status is random—Q1 and Q2 both try to conduct and, usually, the transistor with the higher gain will take control, reaching full conduction and cutting off the other one. However, differences in the values of the collector and coupling resistors will also influence the initial state at power-on. With C2 in the circuit, it and R4 form an R-C network that slightly delays the rise in Q2's base voltage. That gives Q1 sufficient time to reach saturation and thus take control.

## GAME FEEDER CONTROLLER

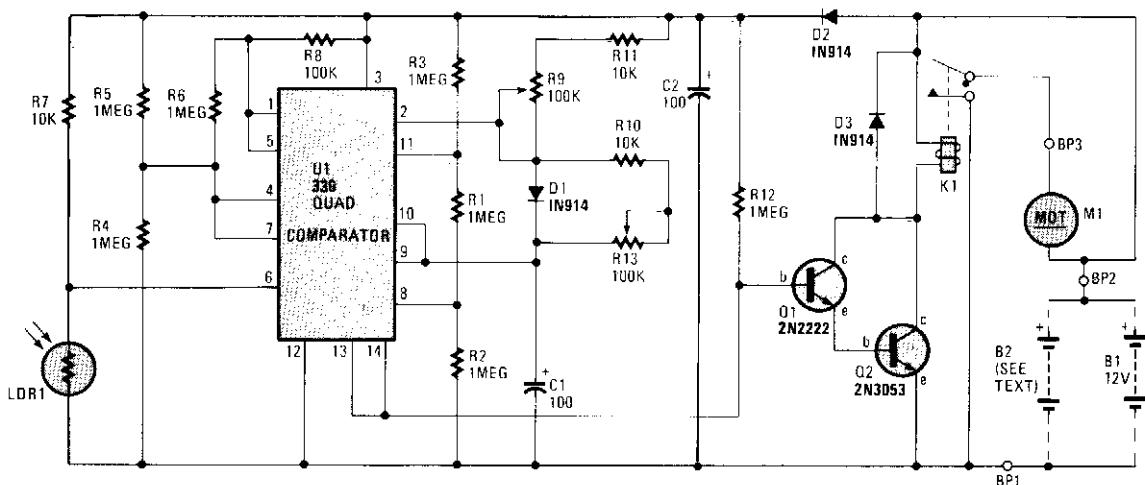


## HANDS-ON ELECTRONICS

*Fig. 58-5*

## Circuit Notes

The circuit is built around an LM339 quad comparator, U1, which forms the basis of a Schmitt trigger, timer circuit, and a window comparator. One comparator within the LM339 (pins 1, 7, 6), plus LDR1, R4, R5, R6 and R8, is used as a Schmitt trigger. The timer circuit (which receives its input from the Schmitt trigger) consists of R9, R10, R11, R13. The last two-fourth's of U1 (pins 8, 9, 10, 11, 13 and 14) are wired as a window comparator. The two inputs to the window comparator are derived from the charge on capacitor C1—which is fed to pins 9 and 10 of U1. The other inputs are picked from two points along a voltage-divider network, consisting of R1, R2, and R3. Diode D1 is used as a blocking diode, forcing capacitor C1 to discharge through R10 and R13. The window comparator looks for any voltage falling between one-third and two-thirds of the supply voltage. When the voltage falls between those two points, the output of the window comparator (pins 13/14) goes high. Transistors Q1, and Q2 are turned on, when the pins 13/14 junction goes high, energizing the relay, K1. The energized relay provides a dc path to ground, activating the motor, M1, which reloads the feeder. The timer circuit also provides immunity from triggering, due to lightning. The on-time of relay K1 is determined by the charge cycle of C1, R11, and R9 or the discharge cycle of C1, R10, and R13. Changing the value of either a resistor or the capacitor, changes the timing cycle.
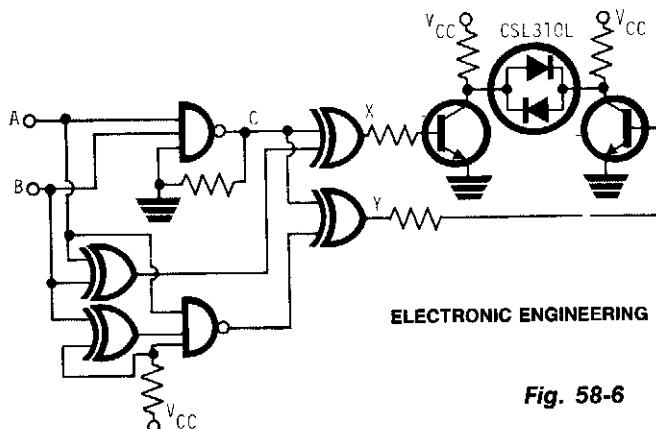
## SINGLE LED CAN INDICATE FOUR LOGIC STATES



ELECTRONIC ENGINEERING

Fig. 58-6

### Circuit Notes

The LED is the CSL310L which contains a red LED and a green LED connected back to back and mounted close together in a single moulding. The LED can emit red or green light by controlling the polarity of the applied voltage and if the polarity is switched at a rate of several hundred Hertz the emitted light appears yellow. The four combinations of inputs A and B can therefore be converted to four LED states—red, green, yellow and off. The truth table shows the LED colors corresponding to the combinations of A and B levels.

### Truth Table

A	B	X	Y	LED color
0	0	1	0	red
0	1	0	0	off
1	0	0	1	green
1	1	C	C	yellow

## INEXPENSIVE RADIO-CONTROL USES ONLY ONE SCR


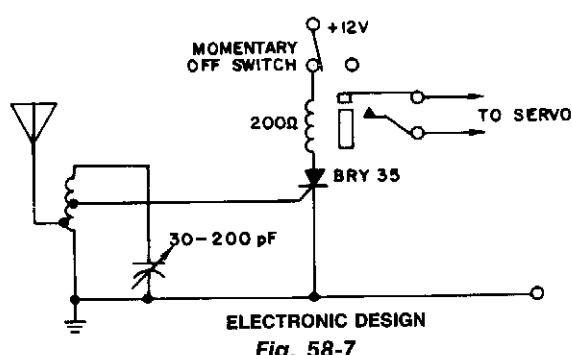


Fig. 58-7

### Circuit Notes

A simple and effective receiver for actuating garage doors, alarms, warning systems, etc. The SCR, which has a very low trigger current 30  $\mu$ A is typical—it requires an input power of only 30  $\mu$ W to activate the relay. A high Q tuned antenna circuit assures rejection of spurious signals. A whip or wire antenna is adequate up to 100 feet from a low power transistor transmitter. A momentary-off switch resets the circuit.

## GUITAR AND BASS TUNER

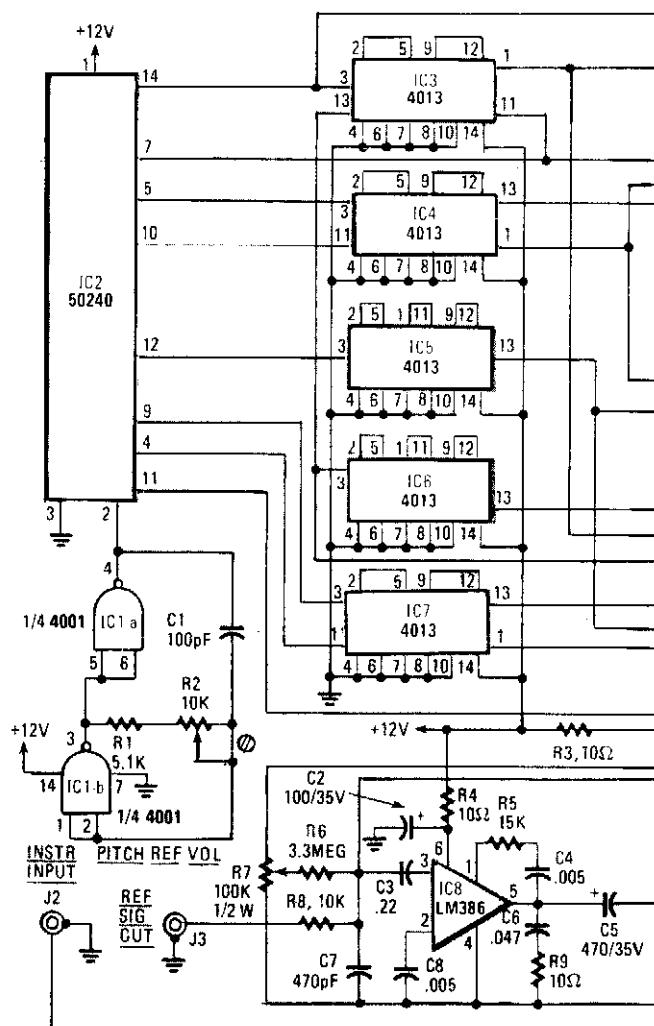


RADIO-ELECTRONICS

**Fig. 58-8**

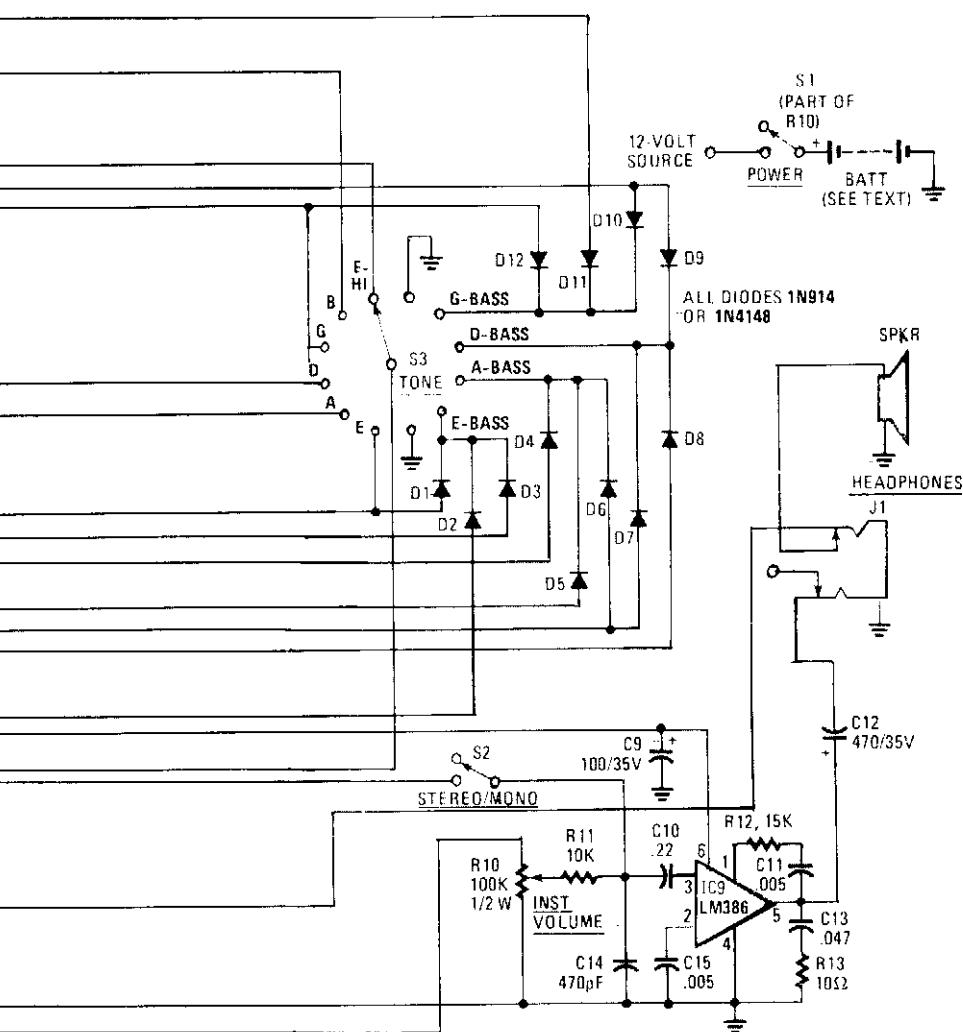
### Circuit Notes

The heart of the circuit is IC2, a 50240 top-octave generator. That device uses a single input-frequency to generate all twelve notes of the musical scale. The input signal is provided by IC1, a 4001 quad 2-input NOR gate. Two sections of that IC are used to form an oscillator that runs at approximately 2 MHz. The frequency can be adjusted by trimmer potentiometer R2. Dual D flip-flops, IC3-IC7, are used as frequency dividers. They divide down the upper-octave frequencies from IC2, thus generating the lower-frequency notes required for the pitch references. The chords for the bass pitch-references are composed of three notes each. Those notes are taken from various outputs



of IC2-IC7 through isolation diodes D1-D12. All signals are routed to the TONE switch, S3. The wiper arm of that switch is connected through R7 to the input of audio power-amplifier IC8, an LM386. The resistor acts as a volume control for the pitch reference. Another LM386, IC9, serves as an amplifier for the instrument being tuned, with R10 acting as its volume control. The outputs of IC8 and IC9 are coupled, through C5 and C12 respectively, to the headphone jack, J1. Switch S2 STEREO/MONO is used to mix the reference and instrument signals at IC9 for mono operation. Power is supplied by eight "AA" cells connected in series.

## 4-CHANNEL COMMUTATOR

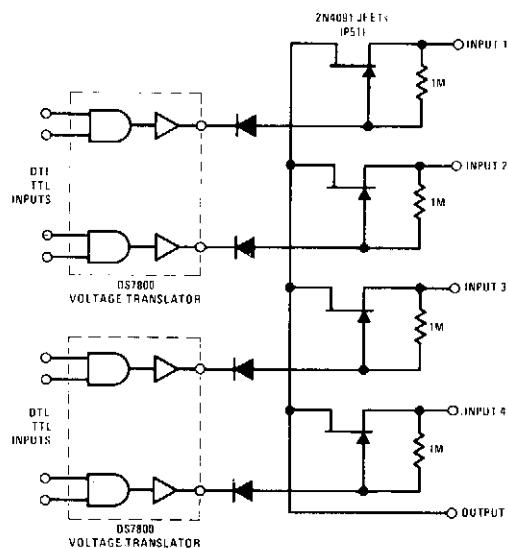


### Circuit Notes

This 4-channel commutator used the 2N4091 to achieve low channel on resistance (< 30 ohm) and low off current leakage. The DS7800 voltage translator is a monolithic device that provides from 10 V to -20 V gate drive to the JFETs while at the same time providing DTL/TTL logic compatibility.

*Fig. 58-9*

NATIONAL SEMICONDUCTOR CORP.


## TWO-WIRE TONE ENCODER

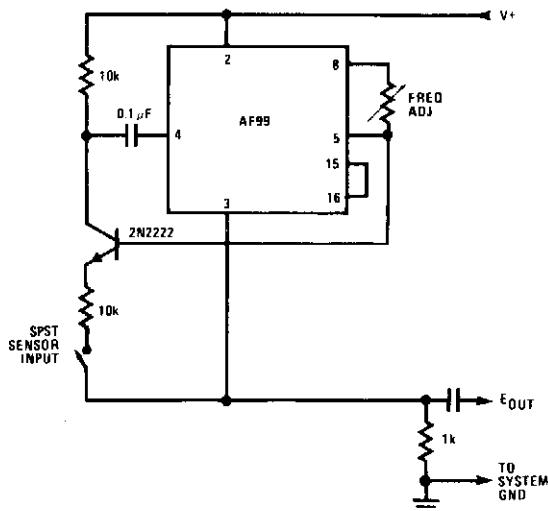

*Fig. 58-10*

NATIONAL SEMICONDUCTOR CORP.


## DIFFERENTIAL HOLD

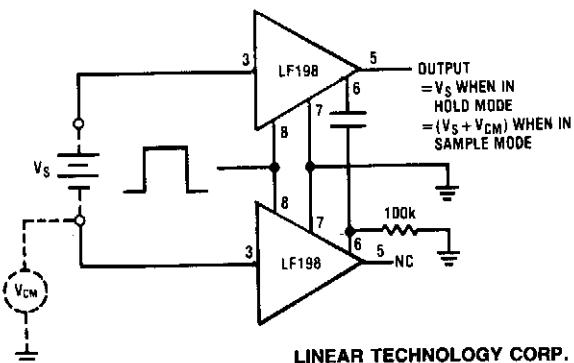

*Fig. 58-11*

LINEAR TECHNOLOGY CORP.

## 5 MHz PHASE-ENCODED DATA READ CIRCUITRY

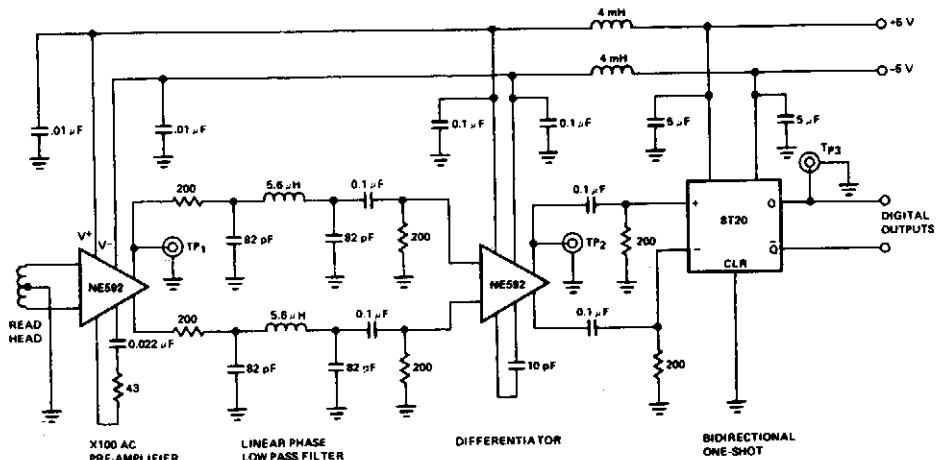

TC100805

**NOTE:**  
All resistor values are in ohms


**SIGNETICS**

*Fig. 58-12*

### Circuit Notes

Readback data is applied directly to the input of the first NE592. This amplifier functions as a wide-band ac coupled amplifier with a gain of 100. By direct coupling of the readback head to the amplifier, no matched terminating resistors are required and the excellent common-mode rejection ratio of the amplifier is preserved. The dc components are also rejected because the NE592 has no gain at dc due to the capacitance across the gain select terminals. The output of the first stage amplifier is routed to a linear phase shift low-pass filter, with a characteristic impedance of 200 ohms. The second NE592 is utilized as a low noise differentiator/amplifier stage. The output of the differentiator/amplifier is connected to the 8T20 bidirectional monostable unit to provide the proper pulses at the zero-crossing points of the differentiator.


## SHIFT REGISTER

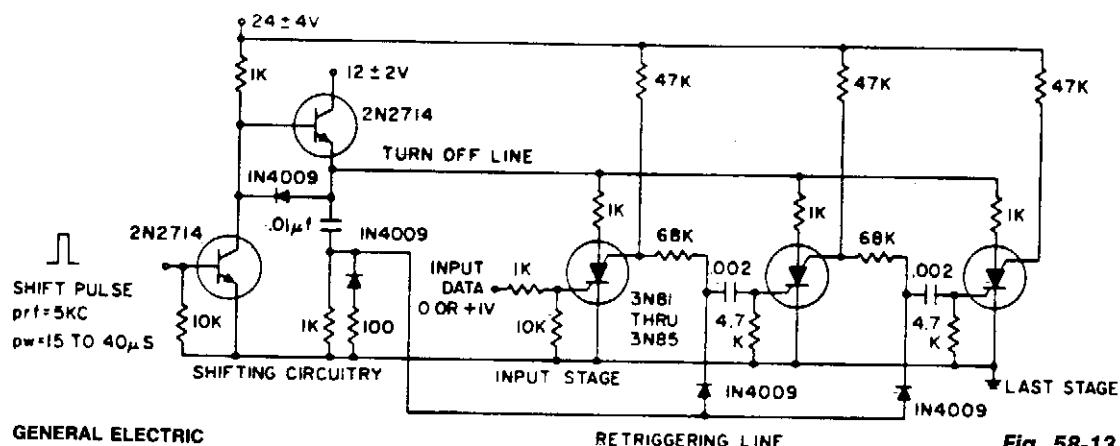

### Circuit Notes

The shift pulse amplitude is less than 15 volts. If a stage is off, the shift pulse will not be coupled to the next stage. If it is on, the diode will conduct triggering the next stage. Just prior to the shift pulse the anode supply is interrupted to turn off all stages. The stored capacitor charge determines which stages will be retriggered.

## POWER-ON RESET

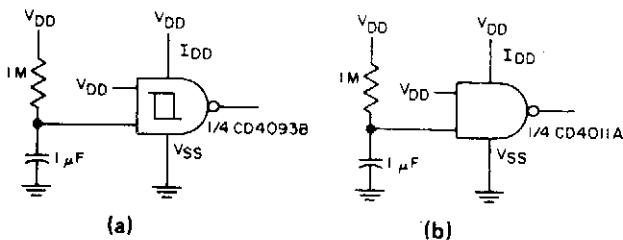


RCA

**Fig. 58-14**

### Circuit Notes

A reset pulse is often required at power-on in a digital system. This type of reset pulse is ideally provided by this circuit. Because of the high input impedance of the Schmitt trigger, long reset pulse times may be achieved without the excess dissipation that results when both output devices are on simultaneously, as in an ordinary gate device (B).

### NOISE IMMUNE 60 Hz LINE SYNC

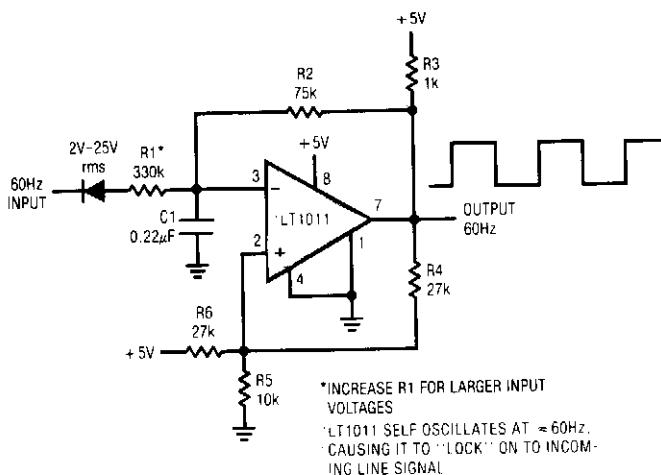

LINEAR TECHNOLOGY CORP.

Fig. 58-15

### DC STATIC SWITCH (SCR FLIP-FLOP)

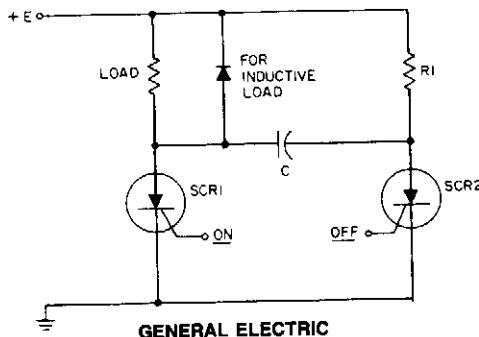


Fig. 58-16

### Circuit Notes

This circuit is a static SCR switch for use in a dc circuit. When a low power signal is applied to the gate of SCR1, this SCR is triggered and voltage is applied to the load. The right hand plate of C charges positively with respect to the left hand plate through R1. When SCR2 is triggered on, capacitor C is connected across SCR1, so that this SCR is momentarily reverse biased between anode and cathode. This reverse voltage turns SCR1 off provided the gate signal is not applied simultaneously to both gates. The current through the load will decrease to zero in an exponential fashion as C becomes charged.

# **59**

## **Modulator Circuits**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Double Sideband, Suppressed Carrier RF Modulator
- Low-Distortion Low Level Amplitude Modulator
- Video Modulator Circuit
- Video Modulator
- TTL Oscillator Interfaces Data for Display by a Television Set

## DOUBLE SIDEBAND, SUPPRESSED CARRIER RF MODULATOR

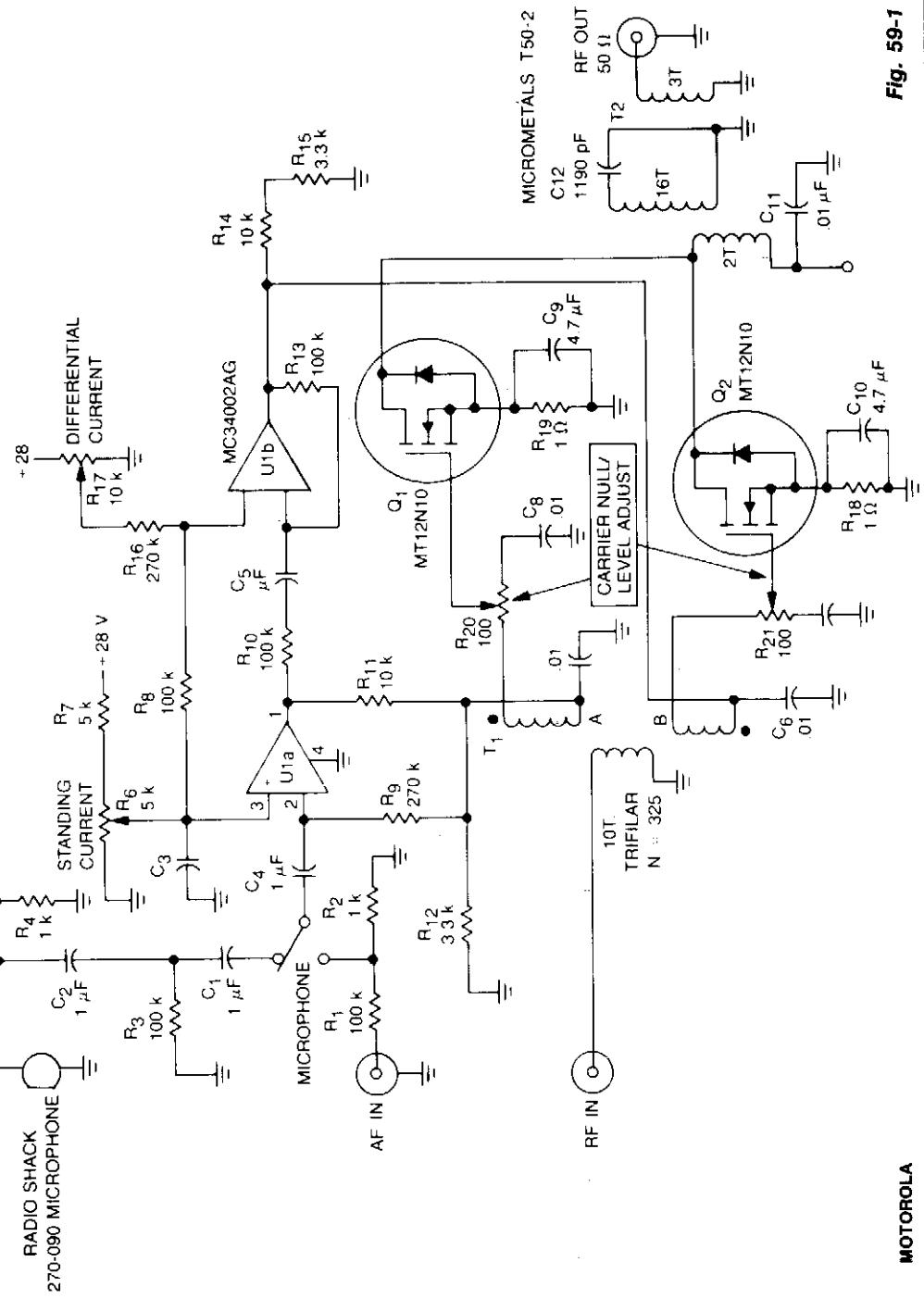


Fig. 59-1

MOTOROLA

## DOUBLE SIDEBAND, SUPPRESSED CARRIER RF MODULATOR , Continued.


### Circuit Notes

An RF input is applied to the primary of T1, which applies equal amplitude, opposite phase RF drive for output FETs Q1 and Q2. With no AF modulation at points A and B, the opposite phase RF signals cancel each other and no output appears at the 50 V output connector.

When AF modulation is applied to points A and B, a modulated RF output is obtained. The dc stability and low frequency gain are improved by source resistors R18 and R19.

A phase inverter consisting of a dual op amp (U1a and U1b) produces the out-of-phase, equal amplitude AF modulation signals.
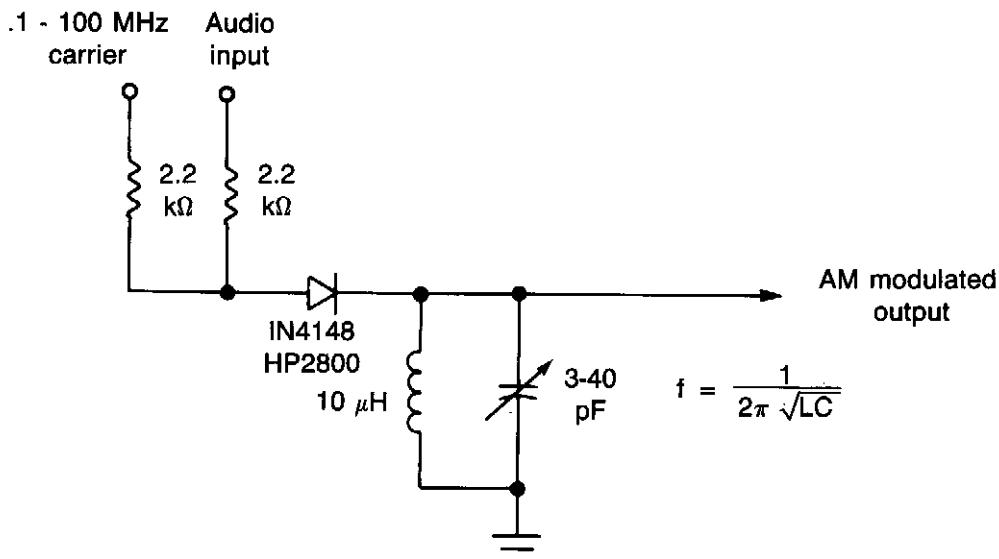
## LOW-DISTORTION LOW-LEVEL AMPLITUDE MODULATOR



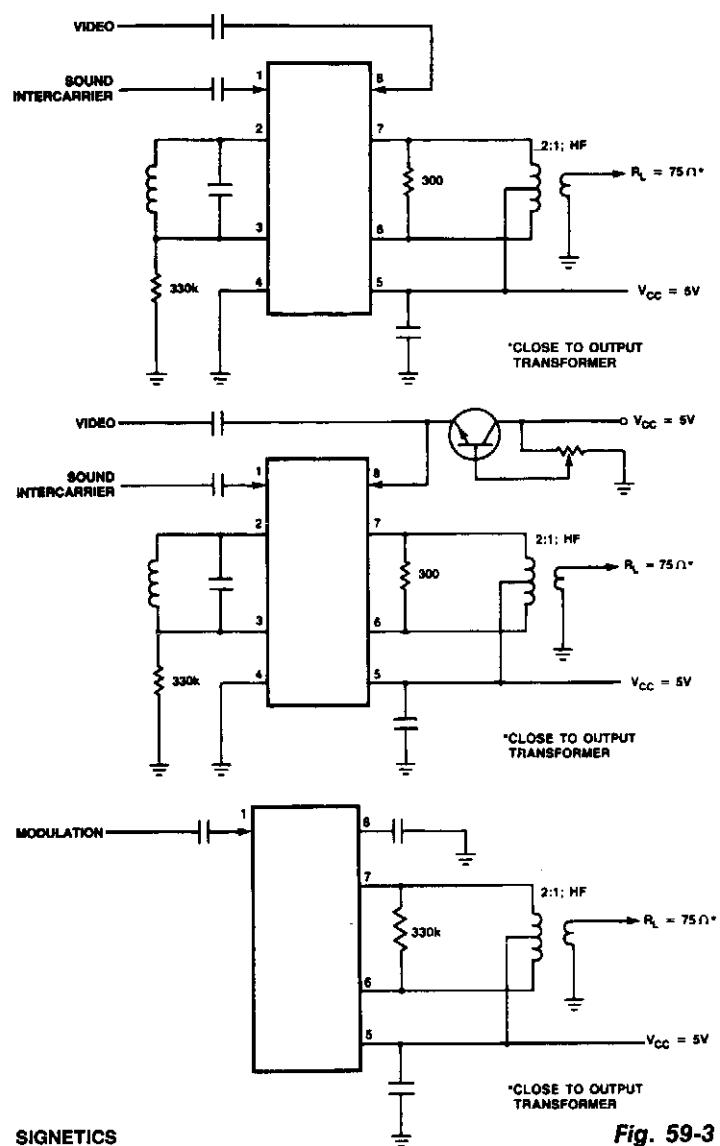
WILLIAM SHEETS

Fig. 59-2

### Circuit Notes

This simple diode modulator delivers excellent results when used for high percentage modulation at low signal levels. Constants are shown for a carrier frequency of about 10 MHz, but, with a suitable tank, the circuit will give good results at any frequency at which the diode approximates a good switch. To extend frequency above that for which the IN4148 is suited, a hot-carrier diode (HP2800, etc.) can be substituted. A shunt resistor across the tank circuit can be used to reduce the circuit Q so as to permit high percentage modulation without appreciable distortion.

## VIDEO MODULATOR CIRCUIT

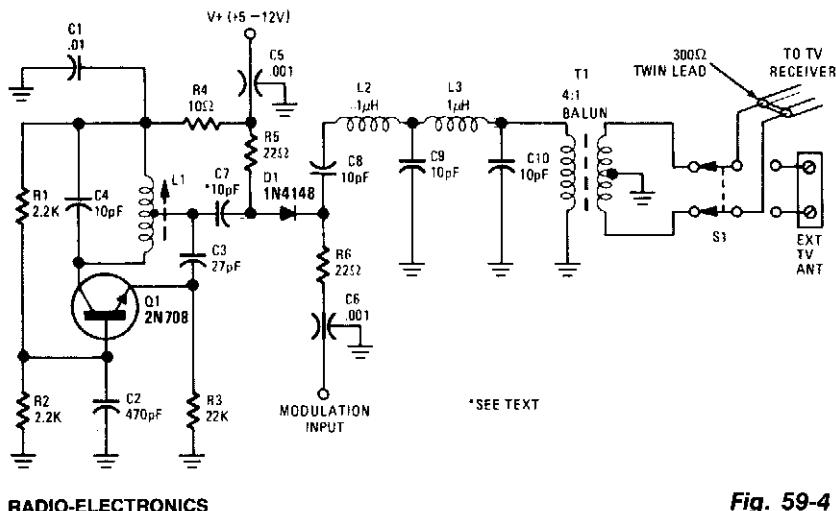


*Fig. 59-3*

### Circuit Notes

These are modulator circuits for modulation of video signals on a VHF/UHF carrier. The circuits require a 5 V power supply and few external components for the negative modulation mode. For positive modulation an external clamp circuit is required. The circuits can be used as general-purpose modulators without additional external components. The IC is TDA6800.

## VIDEO MODULATOR

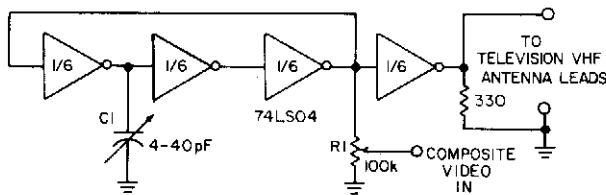


**Fig. 59-4**

### Circuit Notes

This circuit permits direct connection of composite video signals from video games and microcomputers to the antenna terminals of TV sets. The output signal level is controlled by the modulation input.

## TTL OSCILLATOR INTERFACES DATA FOR DISPLAY BY A TELEVISION SET



**Fig. 59-5**

### Circuit Notes

Three gates of a 74LS04 form the oscillator circuit. Capacitor C1 allows fine-frequency adjustment to a specific television channel and helps stabilize the circuit. Potentiometer R1 acts as the mixing input and provides adjustment of the contrast ratio for the best viewing. A fourth gate buffers and helps stabilize the oscillator.

# 60

## Motor Control Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Bi-Directional Proportional Motor Control

AC Motor Control

PWM Motor Speed Control

Stepping Motor Driver

Low-Cost Speed Regulator For DC Motors

Motor Speed Control Circuit

Constant Speed Motor Control Using Tachometer

Feedback

Back EMF PM Motor Speed Control

DC Motor Speed Control

Reversing Motor Drive, DC Control Signal

N-Phase Motor Drivers

Servo Motor Drive Amplifier

DC Servo Drive Employs Bipolar Control Input


400 Hz Servo Amplifier

Three-Phase Power-Factor Controller

Motor/Tachometer Speed Control

Closed Loop, Tachometer Feedback Control
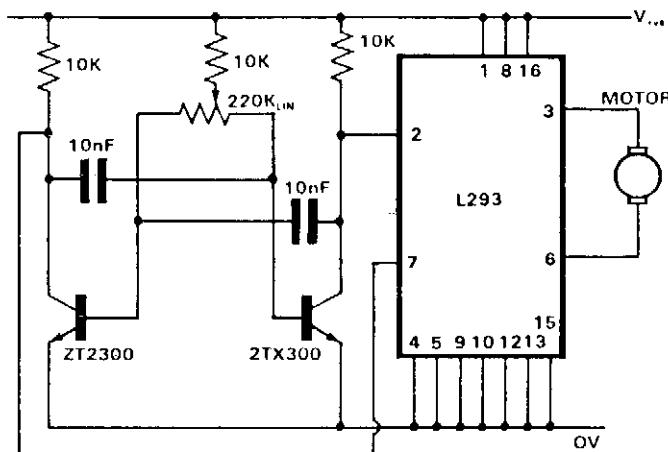
## BI-DIRECTIONAL PROPORTIONAL MOTOR CONTROL



ELECTRONIC ENGINEERING

*Fig. 60-1*


### Circuit Notes

The control of both direction and of proportional motor speed is achieved by rotation of a single potentiometer. The motor driver is an SGS integrated circuit L293 which will drive up to 1 amp in either direction, depending on the logic state of input 1 and input 2 as per table.

I/P 1	I/P 2	Function
High	Low	Motor turns one way
Low	High	Motor reverses

By applying a variable M/S ratio flip-flop to these inputs, both speed and direction will be controlled. With RV1 in its center position the M/S will be 1:1 whereby the motor will remain stationary due to its inability to track at the flip-flop frequency. Movement of RV1 in either direction will gradually alter the M/S ratio and provide an average voltage bias in one direction proportional to the M/S ratio.

## AC MOTOR CONTROL

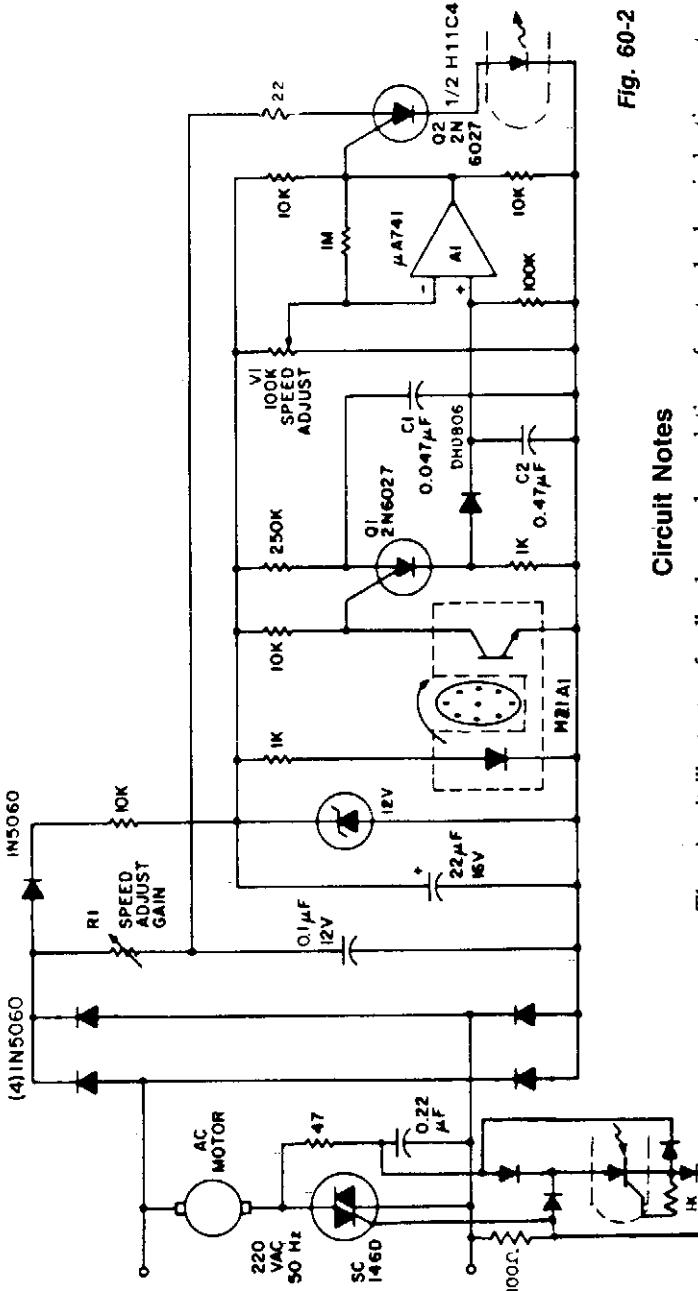

**Fig. 60-2**

### Circuit Notes

The circuit illustrates feedback speed regulation of a standard ac induction motor, a function difficult to accomplish other than with a costly, generator type, precision tachometer. When the apertured disc attached to the motor shaft allows the light beam to cross the interrupter module, the programmable unijunction transistor, Q1, discharges capacitor, C1, into the much larger storage capacitor, C2. The voltage on C2 is a direct function of the rotational speed of the motor. Subsequently, this speed-related potential is compared against an adjustable reference voltage, V1, through the monolithic operational amplifier, A1, whose output, in turn, establishes a dc control input to the second P.U.T. (Q2). This latter device is synchronized to the ac supply frequency and furnishes trigger pulses in the conventional manner to the triac at a phase angle determined by the speed control, R1, and by the actual speed of the motor.

1/2 H11C4 (4) 1N5060  
GENERAL ELECTRIC

## PWM MOTOR SPEED CONTROL

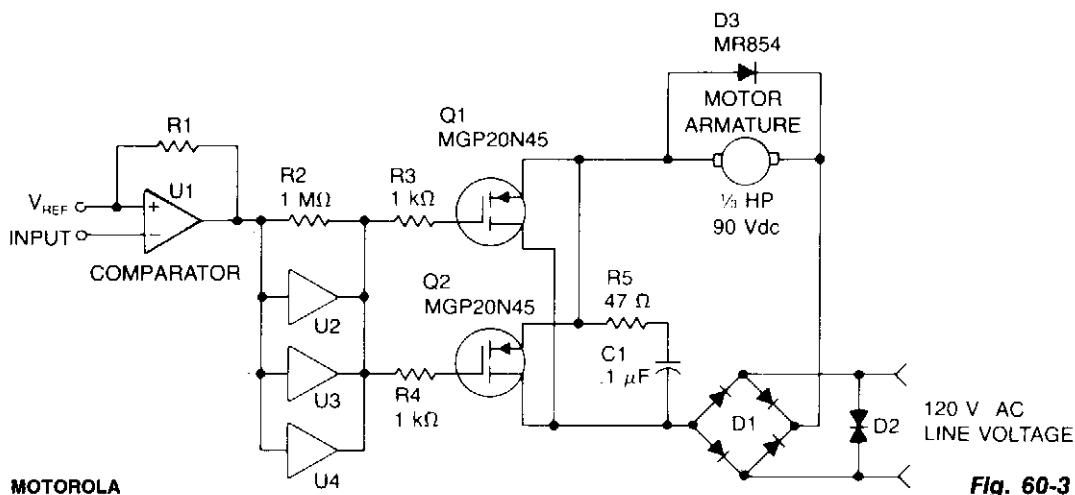



Fig. 60-3

### Circuit Notes

Speed control is accomplished by pulse width modulating the gates of two MGP20N45 TMOS devices. Therefore, motor speed is proportional to the pulse width of the incoming digital signal, which can be generated by a microprocessor or digital logic.

The incoming signal is applied to comparator U1, then to paralleled inverters U2, U3, and U4 that drive the two TMOS devices, which, in turn, control power applied to the motor armature. Bridge rectifier D1 supplies fullwave power that is filtered by R5 and C1. Free-wheeling diode D3 (MR854) prevents high voltage across Q1 and Q2. A back-to-back zener diode, D2, protects against transients and high voltage surges.

## STEPPING MOTOR DRIVER

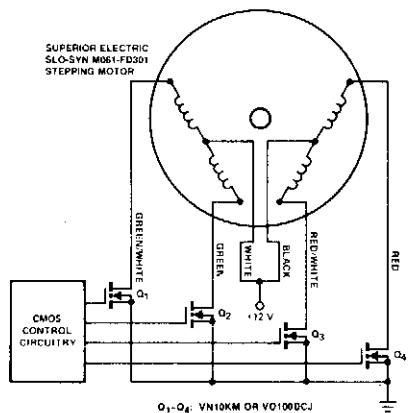

SILICONIX, INC.


Fig. 60-4

### Circuit Notes

Stepping motors find wide use in disk drives and machine control. MOSPOWER transistors are ideal motor drivers because of their freedom from second breakdown. Note that snubbing networks are not used because load line shaping is not necessary with MOSPOWER and the inductance of the motor is fairly low so that the inductive spike is small. The MOSFET gates are tied directly to the outputs of the CMOS control circuitry. The logic is arranged to sequence the motor in accordance with the needs of the application.

## LOW-COST SPEED REGULATOR FOR DC MOTORS

FIG.1

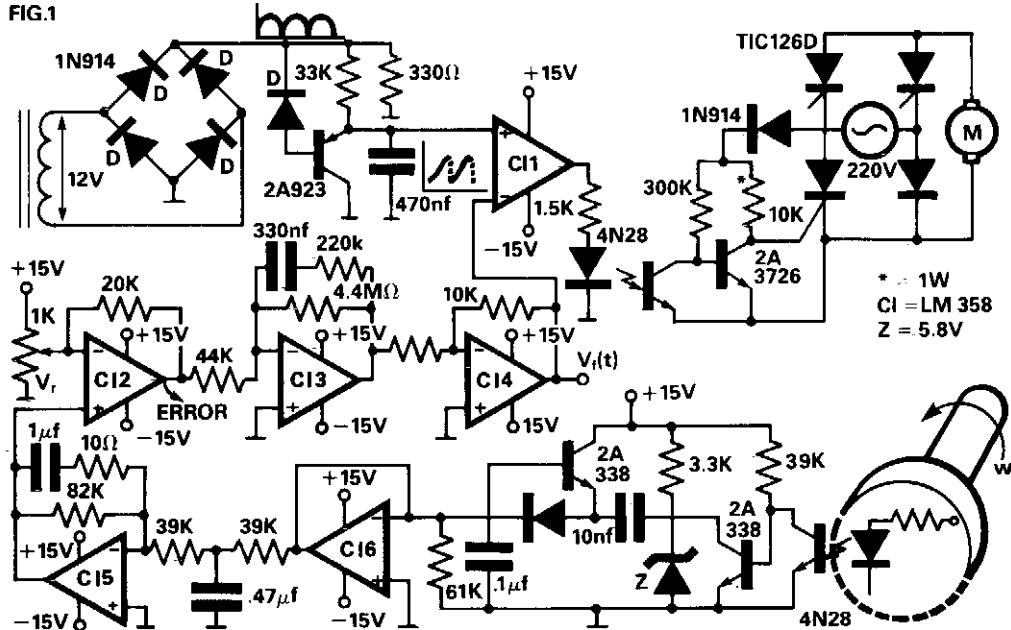

ELECTRONIC ENGINEERING

*Fig. 60-5*

### Circuit Notes

A four thyristor controlled bridge is used for operation in two quadrants of the torque-speed characteristics. In the trigger circuits the usual pulse transformers were replaced by self-biased circuits which minimize gate power consumption and increase noise immunity. Electrical isolation is guaranteed by the use of optocouplers. The trigger pulses are generated by the comparison between an error signal, previously processed and amplified, and a line synchronism signal. The converter's output is a dc voltage proportional to the speed, which after being compared with a reference signal, becomes the error signal.

### MOTOR SPEED CONTROL CIRCUIT

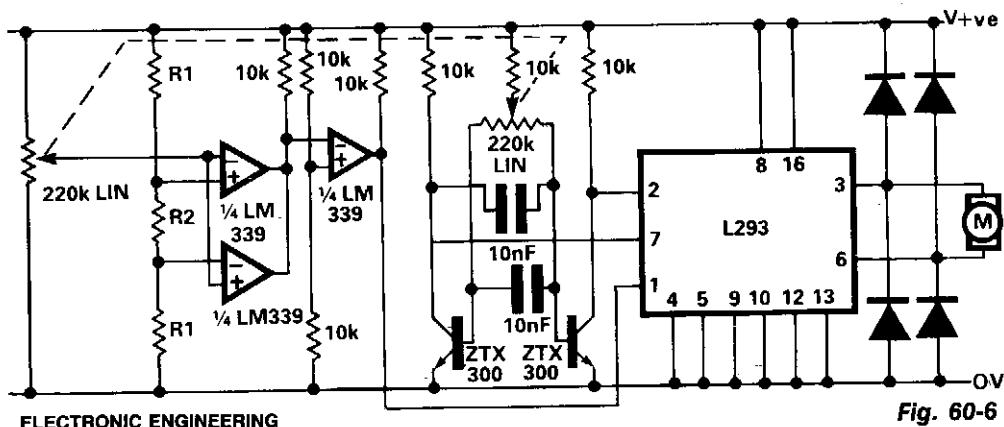


Fig. 60-6

#### Circuit Notes

A shortcoming of the above bi-directional proportional motor control circuit is that with the potentiometer in its center position the motor does not stop, but creeps due to the difficulty in setting the potentiometer for an exact 1:1 mark-space ratio from the flip-flop. This modified circuit uses a second potentiometer, ganged with the first used to inhibit drive to the motor near the center position. This potentiometer is connected between the supply lines and feeds a window comparator which in turn drives the inhibit input of the L293.

### CONSTANT SPEED MOTOR CONTROL USING TACHOMETER FEEDBACK

#### Circuit Notes

The generator output is rectified then filtered and applied between the positive supply voltage and the base of the detector transistor. This provides a negative voltage which reduces the base-voltage when the speed increases. In normal operation, if the tachometer voltage is less than desired, the detector transistor is turned on, then turns on Q2 which causes the timing capacitor for the unijunction transistor to charge quickly. As the tachometer output approaches the voltage desired, the base-emitter voltage is reduced to the point at which Q1 is almost cut off. Thereby, the collector current which charges the unijunction timing capacitor is reduced, causing that capacitor to charge slowly and trigger the thyristor later in the half cycle. In this manner, the average power to the motor is reduced until just enough power to maintain the desired motor speed is allowed to flow.


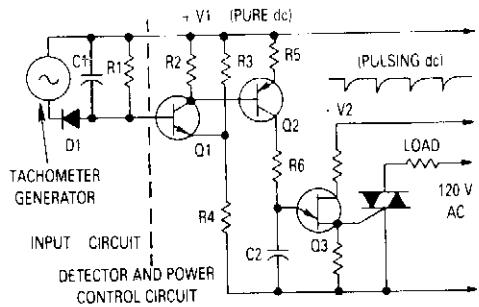


Fig. 60-7

## BACK EMF PM MOTOR SPEED CONTROL

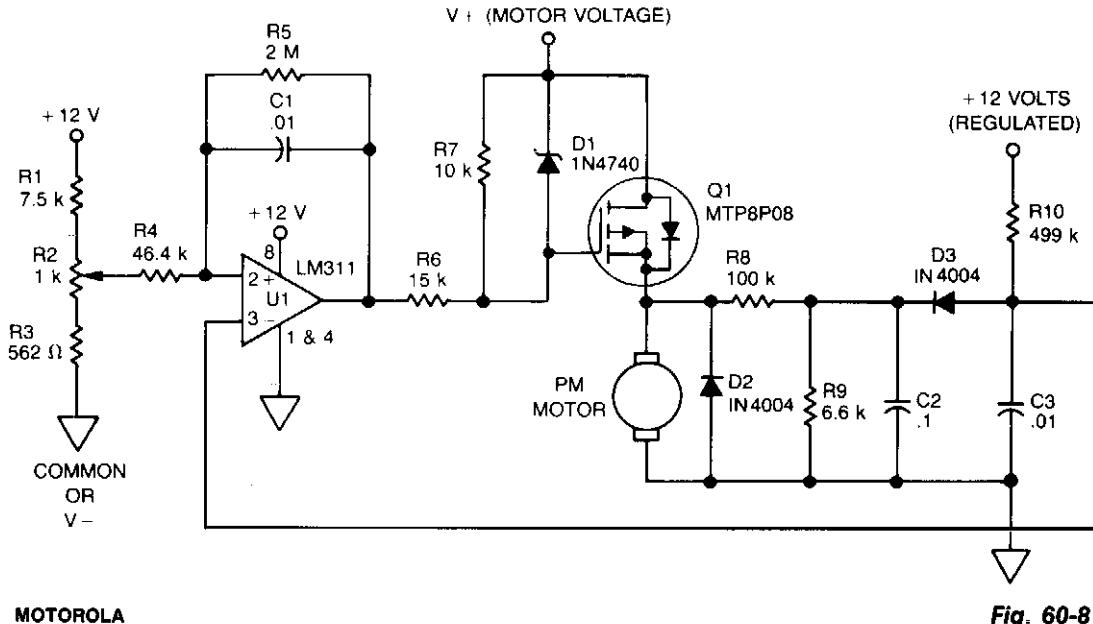

MOTOROLA

**Fig. 60-8**

### Circuit Notes


The use of power MOSFETs allows a direct interface between logic and motor power, which permits circuit simplicity as well as high efficiency. This speed control circuit can be packaged on a 22-pin, double-sided, 3.5 × 4-in. pc board.

A 12 V control supply and a TRW BL11, 30 V motor are used; with minor changes other motor and control voltages can be accommodated. For example, a single 24 V rail could supply both control and motor voltages. Motor and control voltages are kept separate here because CMOS logic is used to start, stop, reverse and oscillate the motor with a variable delay between motor reversals.

Motor speed is established by potentiometer R2, which applies a corresponding dc voltage to the + input of comparator U1, whose output is then applied to TMOS device MTP8P08 (Q1). Zener diode D1 limits the drive to Q1. The output of Q1 drives the permanent magnet motor.

Back emf is obtained from the motor via the network consisting of R8, R9, R10, C2, C3 and D3; it is applied to—input of comparator U1.

## DC MOTOR SPEED CONTROL

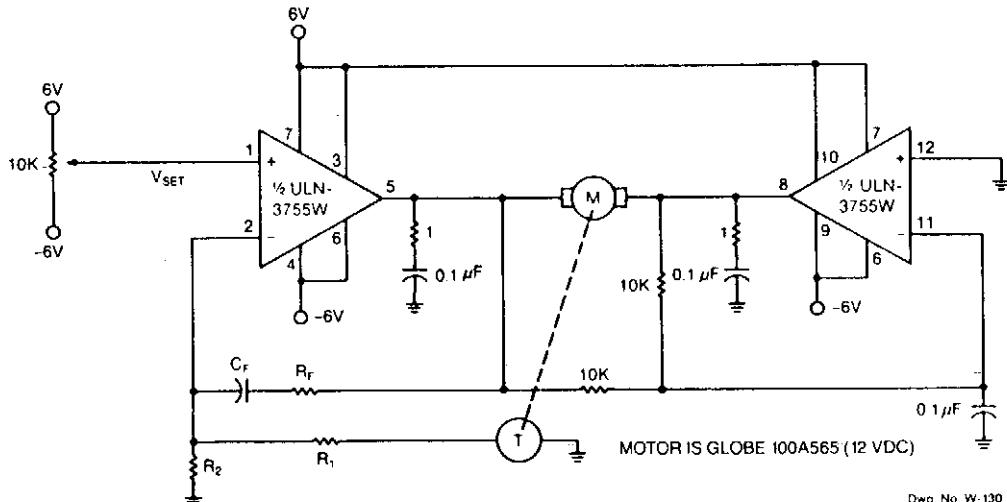


SPRAGUE ELECTRIC CO.

**Fig. 60-9**

### Circuit Notes

Power op amps provide accurate speed control for dc motors. The circuit provides bidirectional speed control. The amplifiers' push-pull configuration ensures a full rail-to-rail voltage swing (minus the output stages' saturation drops) across the motor in either direction. The circuit uses a mechanically-coupled tachometer to provide speed-stabilizing feedback to the first amplifier section. The motor's speed and direction of rotation is set by adjusting the 10 k ohm potentiometer at the amplifier's noninverting input. The RFCF feedback network prevents oscillation by compensating for the inherent dynamic mechanical lag of the motor. Select the RFCF time constant to match the particular motor's characteristics.
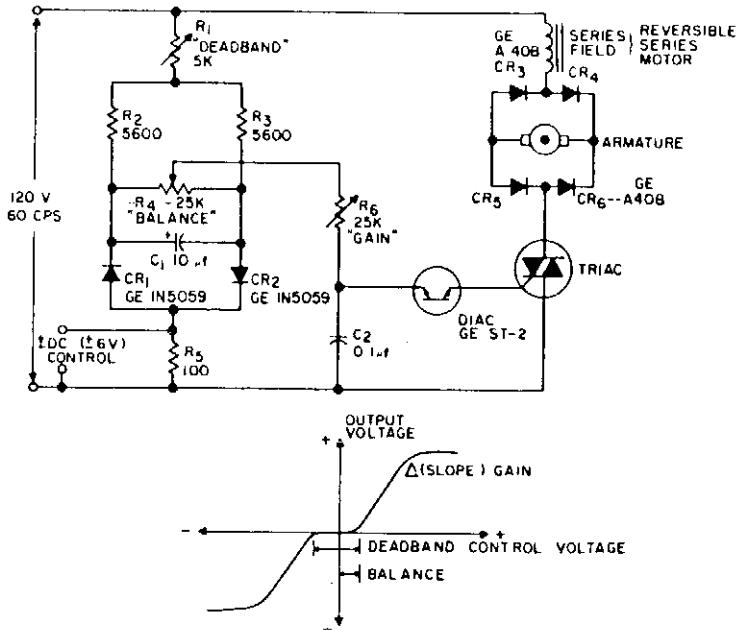
## REVERSING MOTOR DRIVE, DC CONTROL SIGNAL



GENERAL ELECTRIC


**Fig. 60-10**

### Circuit Notes

This is a positioning servo drive featuring adjustment of balance, gain, and deadband. In addition to control from a dc signal, mechanical input can be fed into the balance control, or that control could be replaced by a pair of resistance transducers for control by light or by temperature.


## N-PHASE MOTOR DRIVERS

### SINGLE-PHASE AC MOTOR DRIVER

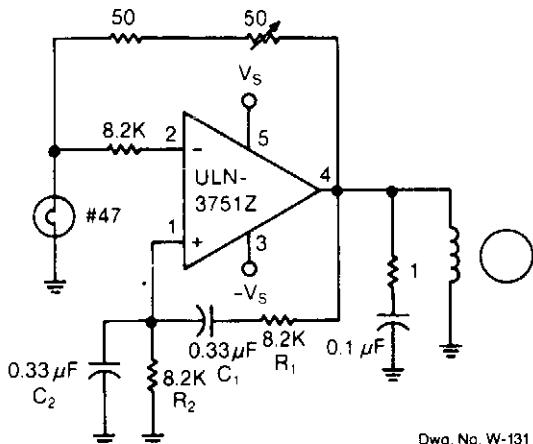

Dwg. No. W-131

### TWO-PHASE AC MOTOR DRIVER

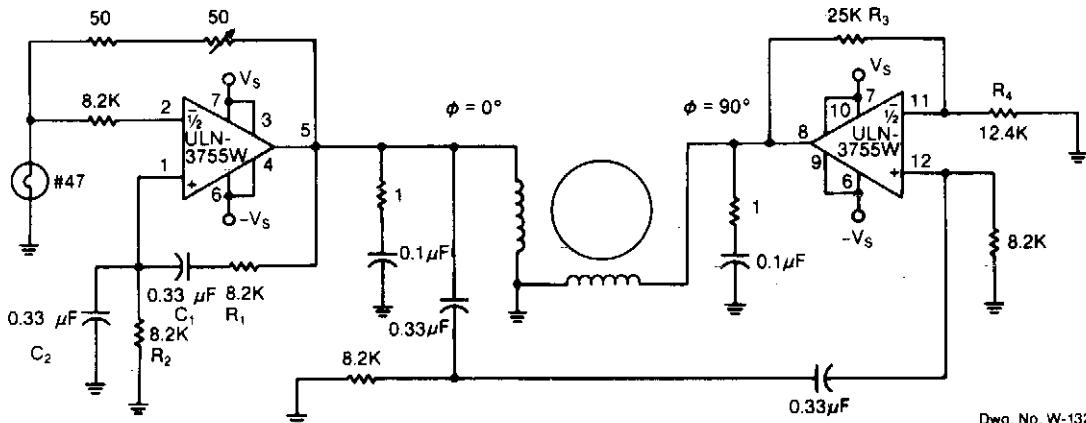

Dwg. No. W-132


SPRAGUE ELECTRIC CO.

**Fig. 60-11**

### Circuit Notes

Because of its high amplification factor and built-in power-output stage, an integrated power operational amplifier makes a convenient driver for ac motors. One op amp can be configured as an oscillator to generate the required ac signal. The power-output stage, of course, supplies the high-current drive to the motor. The controlling op amp is

### THREE-PHASE AC MOTOR DRIVER

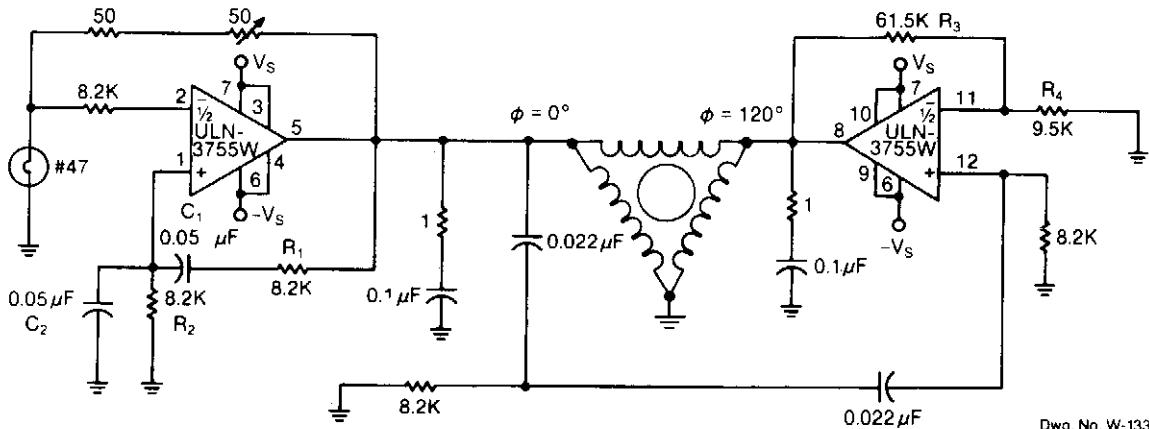


configured as a Wein bridge oscillator. The  $R_1C_1$ ,  $R_2C_2$  feedback networks determine the oscillation frequency, according to the following expression:

$$f_o = \frac{1}{(2 \pi \sqrt{R_1 R_2 C_1 C_2})}$$

By varying either  $R_1$  or  $R_2$ , the oscillator frequency can be adjusted over a narrow range. The  $R_3/R_4$  ratio sets the second amplifier's gain to compensate for signal attenuation occurring in the phase shifters. The circuits can be driven from an external source, such as a pulse or square wave, setting the gain of the left-hand amplifier to a level less than that required for oscillation. The RC feedback networks then function as an active filter causing the outputs to be sinusoidal.

## SERVO MOTOR DRIVE AMPLIFIER

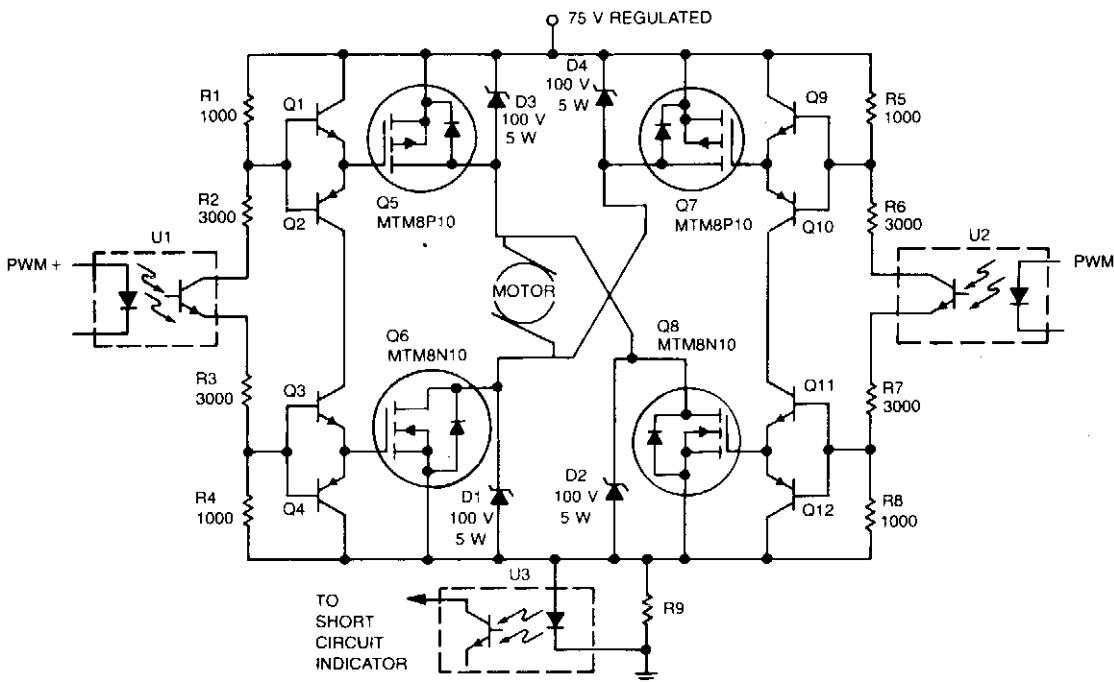

MOTOROLA

**Fig. 60-12**

### Circuit Notes

Digital ICs and opto-isolators provide the drive for this TMOS servo amplifier, resulting in fewer analog circuits and less drift. Fast and consistent turn-on and turn-off characteristics also enable accurate analog output results directly from the digital signal without the need for analog feedback.

An "H" bridge configuration is employed for the servo amplifier, which obtains complementary PWM inputs from digital control circuits. The PWM inputs are applied via opto-isolators, which keep the digital control logic isolated from the 75 V supply used for the amplifier. A short circuit indicator is provided by opto-isolator U3; if there is a short, the drop across R9 increases to a value sufficient to activate the isolator and send a short indication to the digital control logic.

## DC SERVO DRIVE EMPLOYS BIPOLAR CONTROL INPUT

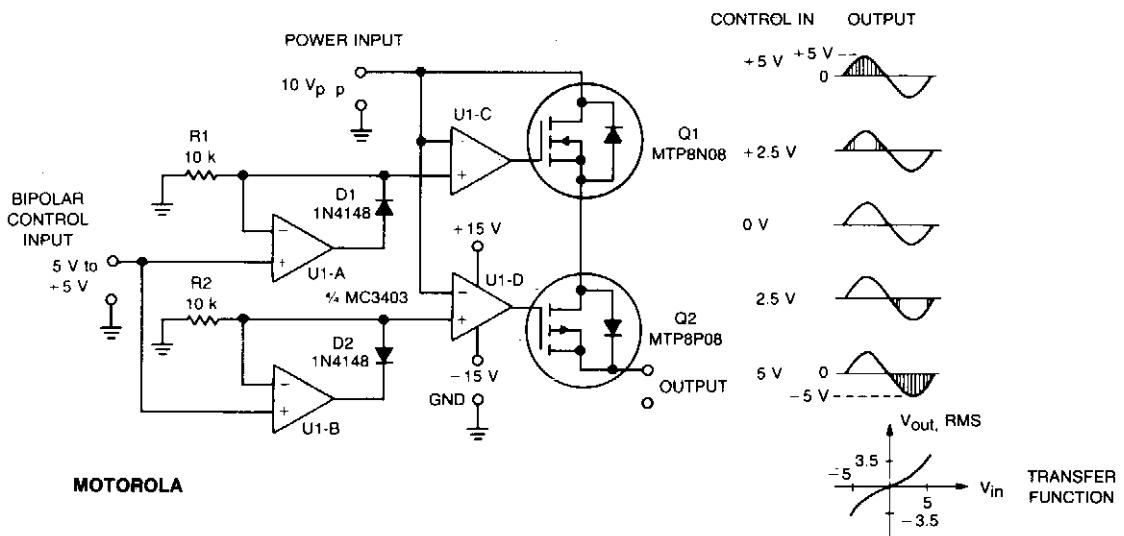


Fig. 60-13


### Circuit Notes

This circuit accepts bipolar control inputs of  $\pm 5\text{ V}$  and provides a phase-chopped output to a dc load (such as a servo motor) of the same polarity as the input. The rms voltage of the output is closely proportional to the control input voltage.

N-channel and p-channel TMOS devices, Q1 and Q2, are connected in anti-series to form a bidirectional switch through which current can flow in either the forward or reverse direction. Control circuits turn Q1 and Q2 on when they are reverse biased, bypassing their reverse rectifier and increasing circuit efficiency. Each device is allowed to turn off only when forward biased.

The Q1-Q2 switch connects the ac power source to the load when its instantaneous voltage is the same polarity and less than the control voltage. U1a is configured as an ideal positive rectifier whose output follows the control voltage when it is positive, and is zero otherwise. Similarly, U1b is a negative rectifier. U1c turns Q1 on whenever the ac input voltage is lower than the positive rectifier output. For negative control voltages, Q1 is turned on only during the negative half-cycle. For positive control voltages, Q1 is turned on during the end portions of the positive half-cycle. Similarly, U1d turns Q2 on whenever the ac input voltage is higher than the output of the negative rectifier.


## 400 Hz SERVO AMPLIFIER

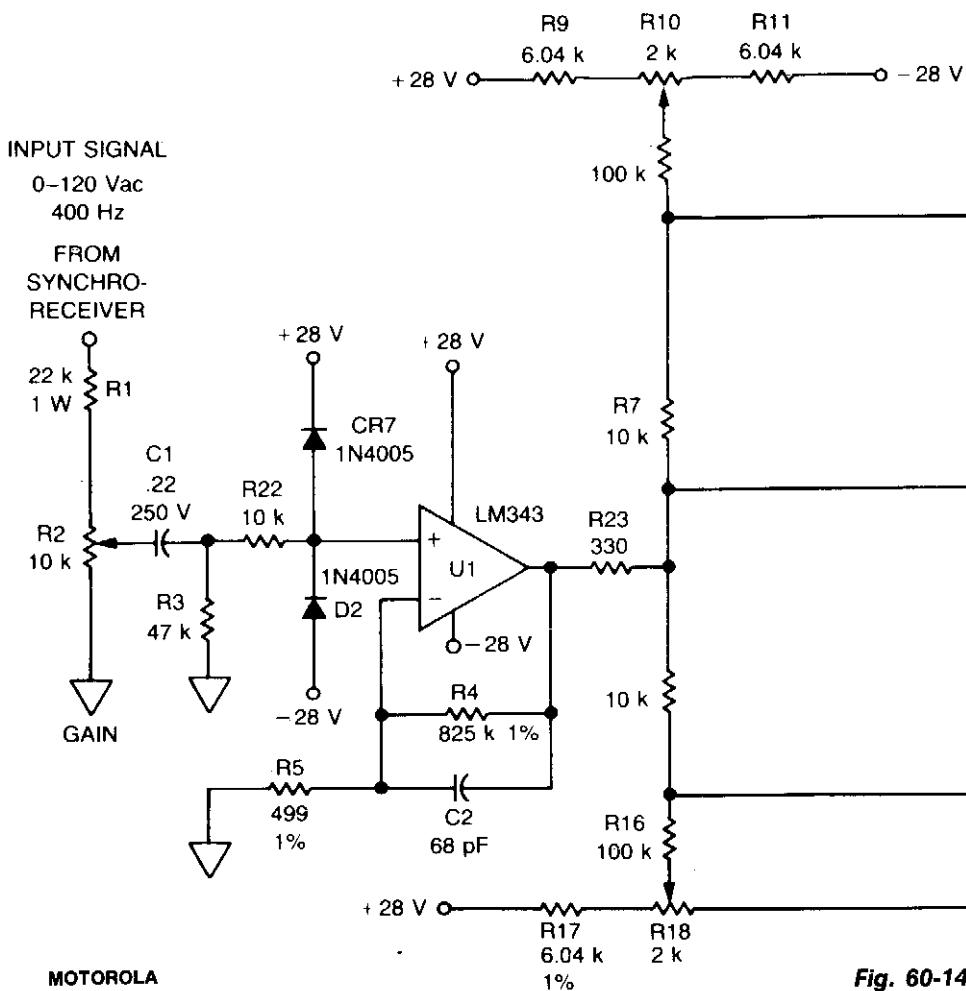


**Fig. 60-14**
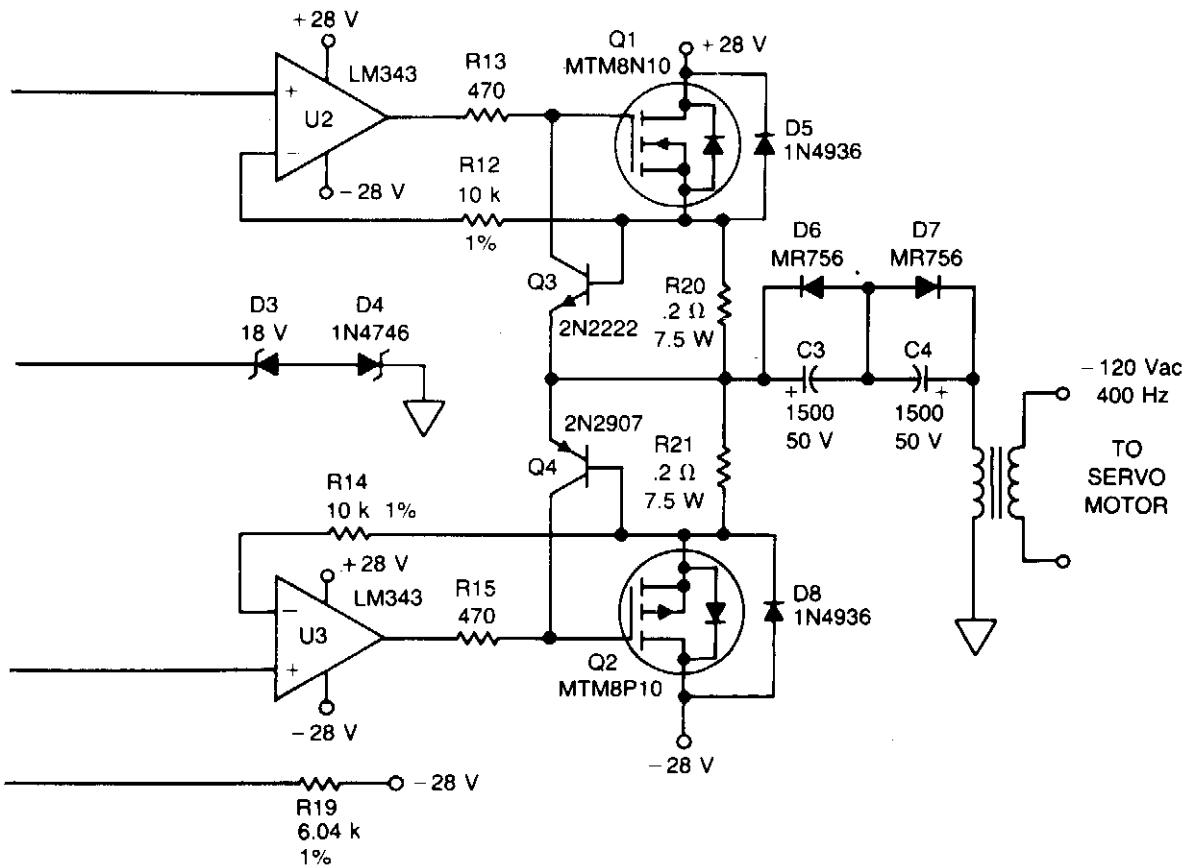
### Circuit Notes

The signal from a synchro receiver or a variable resistive cam follower (potentiometer) is boosted by operational amplifier U1, whose output swing is limited by back-to-back zeners D3 and D4. The signal is then applied to operational amplifiers U2 and U3, which drive the gates of Q1 and Q2 respectively. The npn transistor (Q3) is a fast current limiter for the n-channel MTM8N10; a pnp transistor (Q4) performs the same function for the p-channel MTM8P10. Capacitors C3 and C4 eliminate the need for accurate dc offset zeroing. T1 steps up the output voltage to 120 V for the 400 Hz servo motor.



## THREE-PHASE POWER-FACTOR CONTROLLER

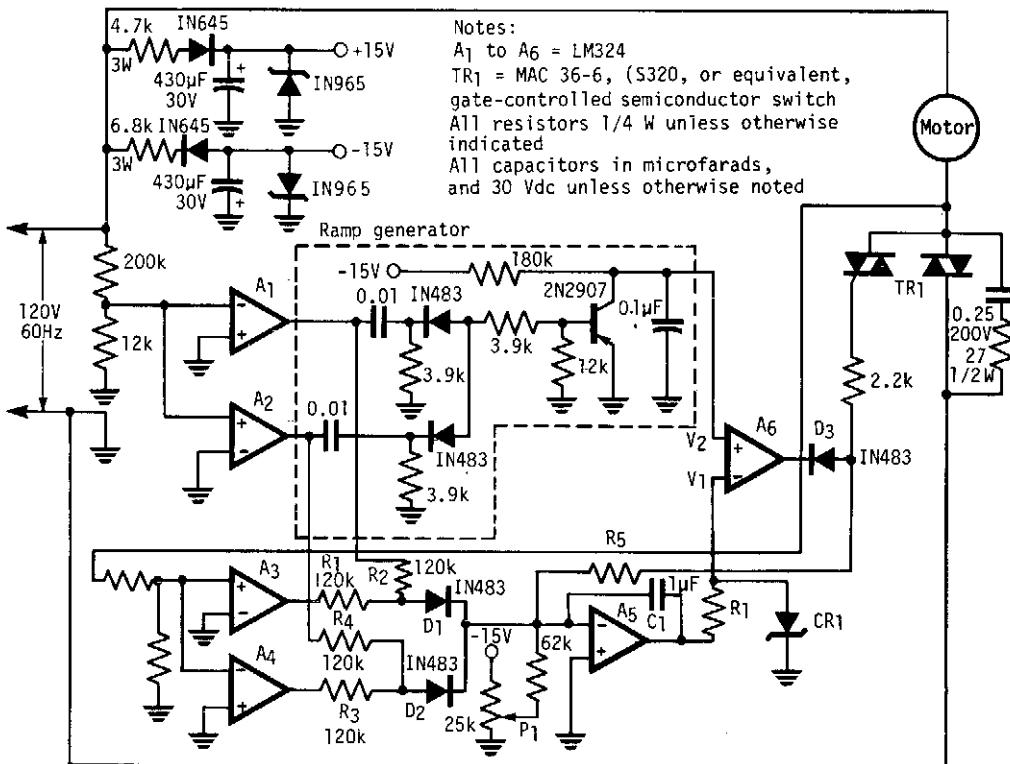


ELECTRONIC ENGINEERING

Fig. 60-15

### Circuit Notes

The modified power-factor controller, developed at the Marshall Space Flight Center, employs a phase detector for each of the three phase-windings of a delta-connected induction motor. The phase-difference sum is the basis for control. Instabilities of earlier systems are overcome with improved feedback control incorporating a 20Hz bandwidth signal.

## MOTOR/TACHOMETER SPEED CONTROL

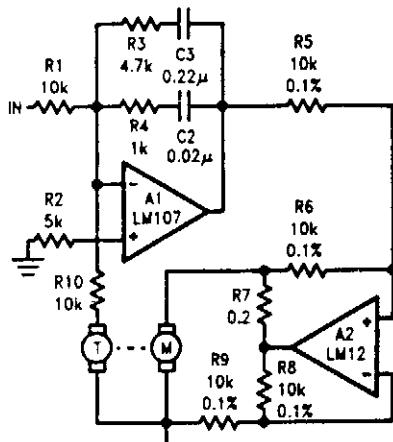


NATIONAL SEMICONDUCTOR CORP.

*Fig. 60-16*

### Circuit Notes

The tachometer, on the same shaft as the dc motor, is simply a generator. It gives a dc output voltage proportional to the speed of the motor. A summing amplifier, A1, controls its output so that the tachometer voltage equals the input voltage, but of opposite sign. With current drive to the motor, phase lag to the tachometer is  $90^\circ$ , before the second order effects come in. Compensation on A1 is designed to give less than  $90^\circ$  phase shift over the range of frequencies where the servo loop goes through unity gain. Should response time be of less concern, a power op amp could be substituted for A1 to drive the motor directly. Lowering break frequencies of the compensation would, of course, be necessary. The circuit could also be used as a position servo. All that is needed is a voltage indicating the sense and magnitude of the motor shaft displacement from a desired position. This error signal is connected to the input, and the servo works to make it zero. The tachometer is still required to develop a phase-correcting rate signal because the error signal lags the motor drive by  $180^\circ$ .
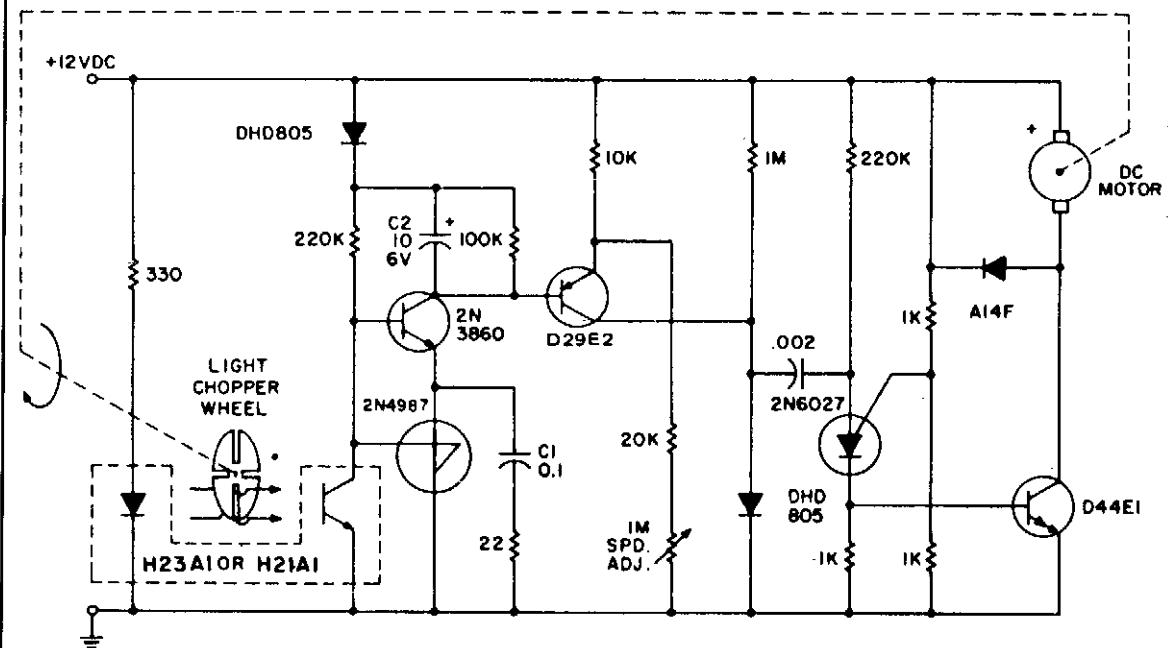
#### **CLOSED LOOP, TACHOMETER FEEDBACK CONTROL**



**GENERAL ELECTRIC**

*Fig. 60-17*

**Circuit Notes**

The system utilizes the H21A1 and a chopper disc to provide superior speed regulation when the dynamic characteristics of the motor system and the feedback system are matched to provide stability. The tachometer feedback system illustrated was designed around specific motor/load combinations and may require modification to prevent hunting or oscillation with other combinations. This dc motor control utilizes the optotachometer circuit previously shown to control a P.U.T. pulse generator that drives the D44E1 darlington transistor which powers the motor.

# **61**

## **Multiplier Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Analog Multiplier  
0.01% Analog Multiplier

## ANALOG MULTIPLIER


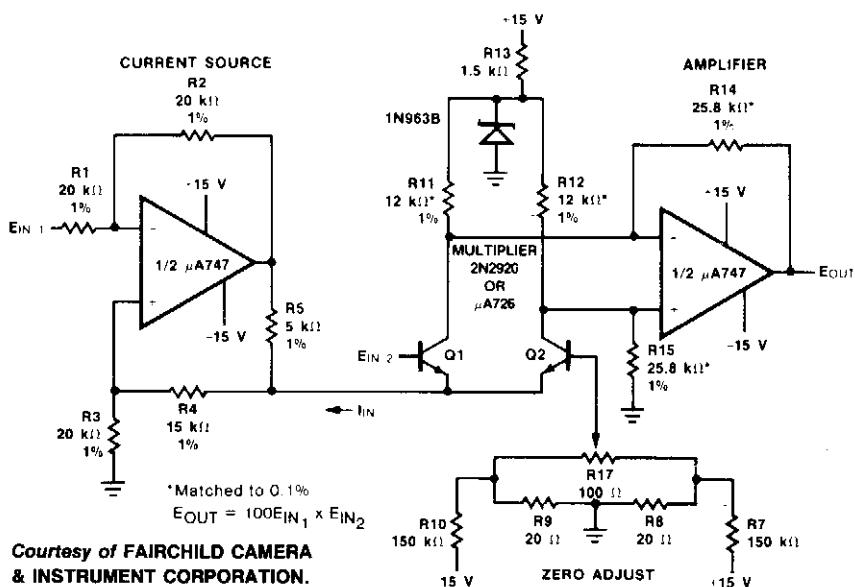


Fig. 61-1

## 0.01% ANALOG MULTIPLIER

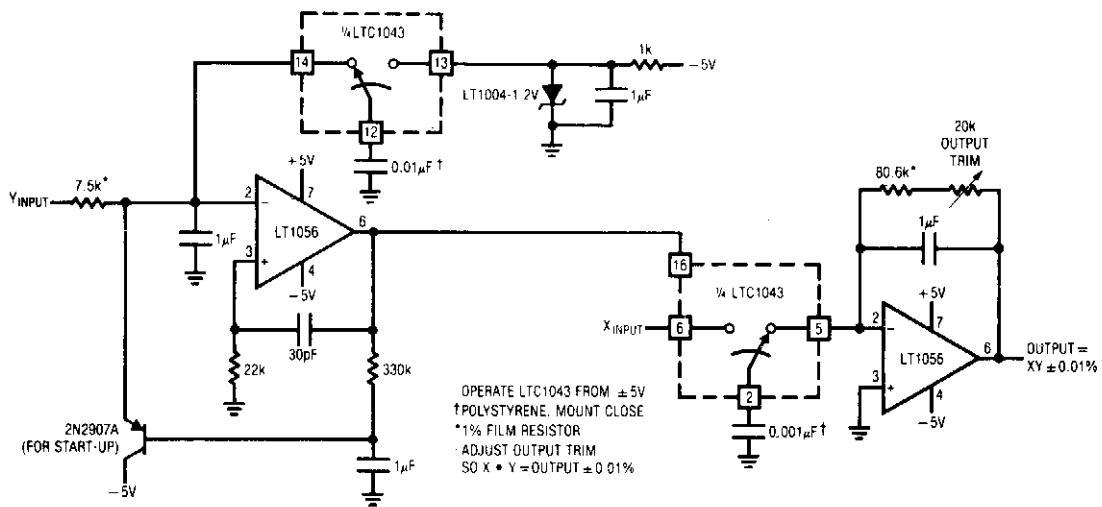

LINEAR TECHNOLOGY CORPORATION

Fig. 61-2

### Circuit Notes

The F → V input frequency is locked to the V → F output because the LTC1043's clock is common to both sections. The F → V's reference is used as one input of the multiplier, while the V → F furnishes the other. To calibrate, short the X and Y inputs to 1.7320 V and trim for a 3-V output.

# 62

## Noise Reduction Circuits

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Audio Squelch Circuit
- Precise Audio Clipper
- Balance Amplifier with Loudness Control
- Noise Limiter
- Audio-Powered Noise Clipper
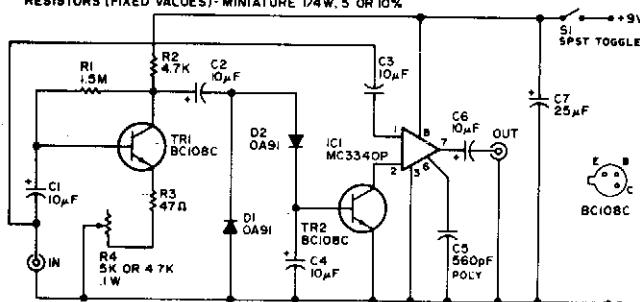
## AUDIO SQUELCH CIRCUIT

C1,C2,C3,C4,C6 AND C7-ELECTROLYTIC, 16V WKG  
RESISTORS (FIXED VALUES)-MINIATURE 1/4W, 5 OR 10%




73 MAGAZINE

Fig. 62-1

### Circuit Notes

This simple audio squelch unit suppresses all input signals below a preset threshold.

## PRECISE AUDIO CLIPPER

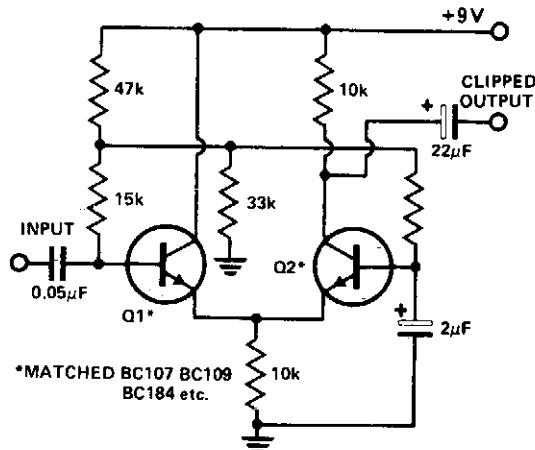

ELECTRONICS INTERNATIONAL TODAY

Fig. 62-2

### Circuit Notes

A differential amplifier makes an excellent audio clipper and can provide precise, symmetrical clipping. The circuit shown commences clipping at an input of 100 mV. The output commences clipping at  $\pm 3$  V. Matching Q7 and Q2 is necessary for good symmetrical clipping. (If some asymmetry can be tolerated, this need not be done.)

## BALANCE AMPLIFIER WITH LOUDNESS CONTROL

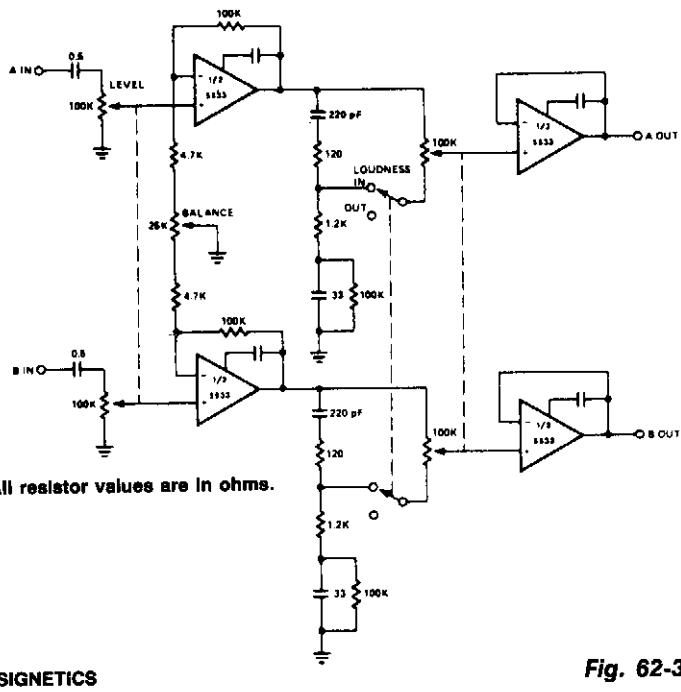


Fig. 62-3

## NOISE LIMITER

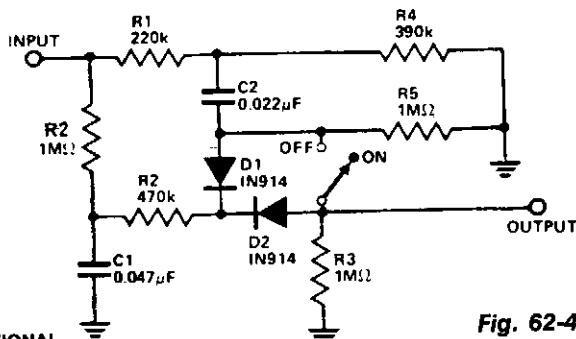


Fig. 62-4

ELECTRONICS TODAY INTERNATIONAL

### Circuit Notes

This limiter improves signal-to-noise ratio. It is connected between the detector output and the audio input (if high impedance) or at some relatively high-impedance section between two audio stages—preferably the low level stages. D1 and D2 can be any diode having relatively low forward resistance and very high back resistance. The circuit is excellent for receivers having bandwidths down to 2 or 3 kHz. Increase the value of C1 for receivers having narrower bandwidths.

## AUDIO-POWERED NOISE CLIPPER

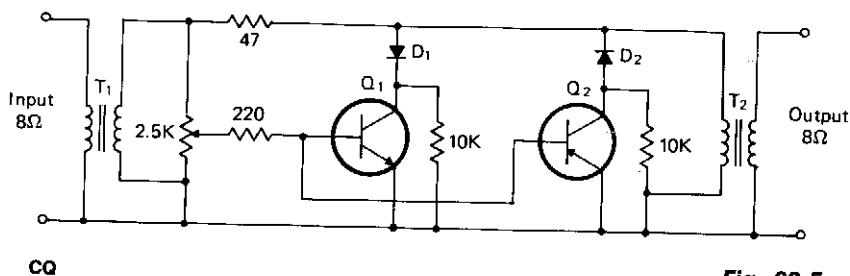


Fig. 62-5

### Circuit Notes

T<sub>1</sub> and T<sub>2</sub> are 600 to 8 ohm transformers (any transistor radio output transformers with 500 to 4 ohm impedance may be used). Q<sub>1</sub> is a 2N2222 npn transistor, and Q<sub>2</sub> is a 2N2907 pnp transistor. D<sub>1</sub> and D<sub>2</sub> 1N270 signal diodes (HEP 134 or 135). Two transistors, powered by the audio power contained within the signal, will clip signal peaks which exceed the threshold established by the 2.5 K potentiometer. The diodes isolate the positive and negative clipping circuits represented by the npn and pnp transistors, respectively. A desired audio operating level can be established and the potentiometer needs little or no further adjustment.

# **63**

## **Notch Filters**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Adjustable Q Notch Filter

1800 Hz Notch Filter

550 Hz Notch Filter

Tunable Audio Notch Filter Circuit

Audio Notch Filter

Tunable Notch Filter Uses an Operational Amplifier


Active Band-Reject Filter

Wien Bridge Notch Filter

Tunable Audio Filter

Passive Bridged, Differentiator Tunable Notch Filter

## ADJUSTABLE Q NOTCH FILTER

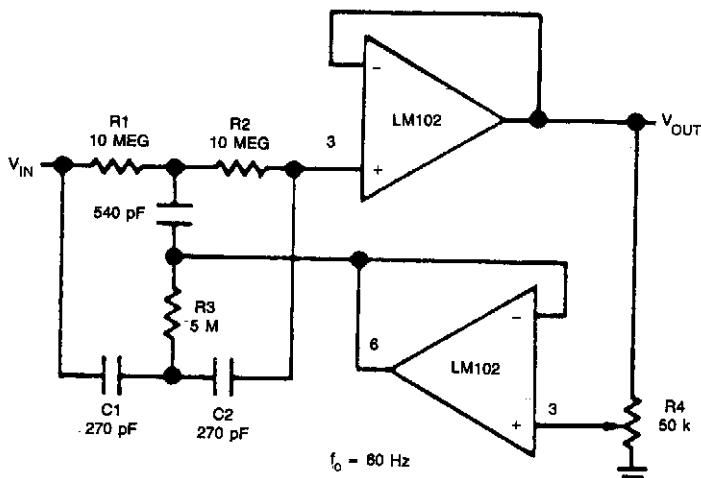


NATIONAL SEMICONDUCTOR CORP.

**Fig. 63-1**

### Circuit Notes

In applications where the rejected signal might deviate slightly from the null on the notch network, it is advantageous to lower the Q of the network. This insures some rejection over a wider range of input frequencies. The figure shows a circuit where the Q may be varied from 0.3 to 50. A fraction of the output is fed back to  $R_3$  and  $C_3$  by a second voltage follower, and the notch Q is dependent on the amount of signal fed back. A second follower is necessary to drive the twin "T" from a low-resistance source so that the notch frequency and depth will not change with the potentiometer setting.

## 1800 Hz NOTCH FILTER

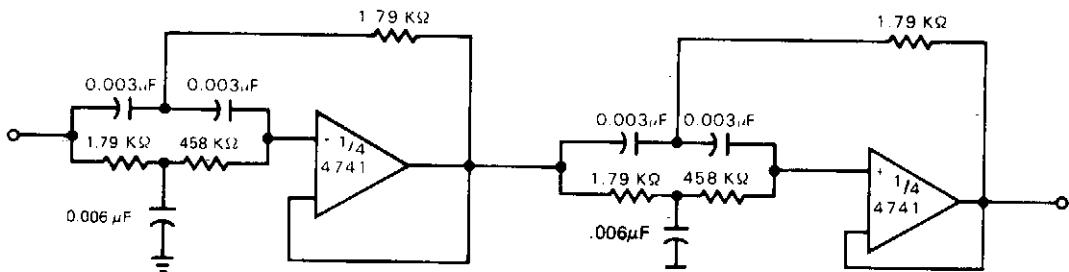


EXAR

**Fig. 63-2**

### Circuit Notes

The circuit produces at least 60 dB of attenuation of the notch frequency.

### 550 Hz NOTCH FILTER

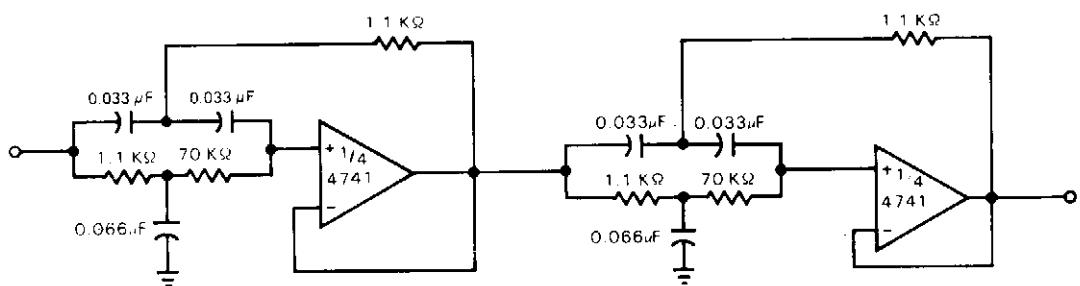


EXAR

Fig. 63-3

### Circuit Notes

The circuit produces at least 60 dB of attenuation of the notch frequency.

### TUNABLE AUDIO NOTCH FILTER CIRCUIT

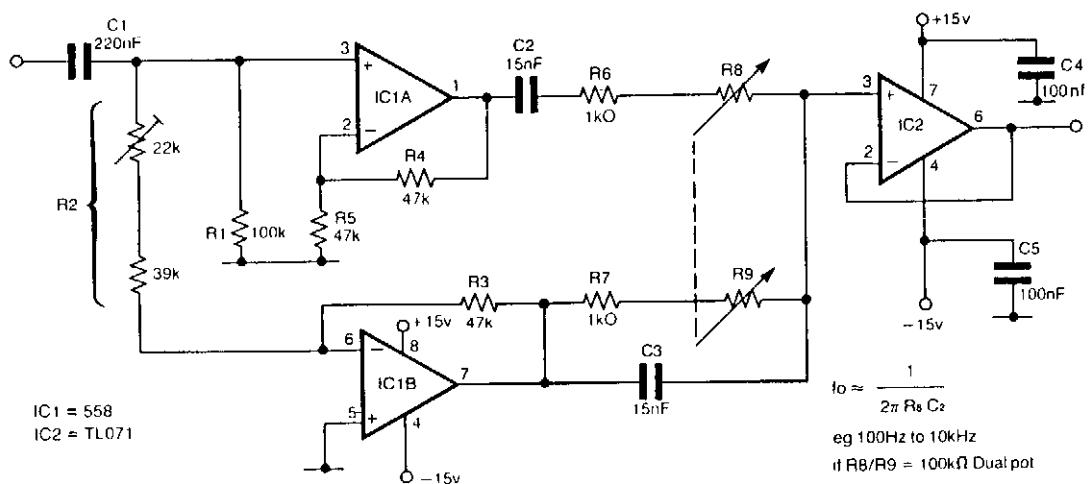


ELECTRONIC ENGINEERING

Fig. 63-4

### Circuit Notes

The circuit requires only one dual-ganged potentiometer to tune over a wide range; if necessary over the entire audio range in one sweep. The principle used is that of the Wien bridge, fed from anti-phase inputs. The output should be buffered as shown with a FET input op amp, particularly if a high value pot is used. An op amp with differential outputs (e.g., MC1445) may be used in place of the driver ICS; R2 may be made trimmable to optimize the notch.

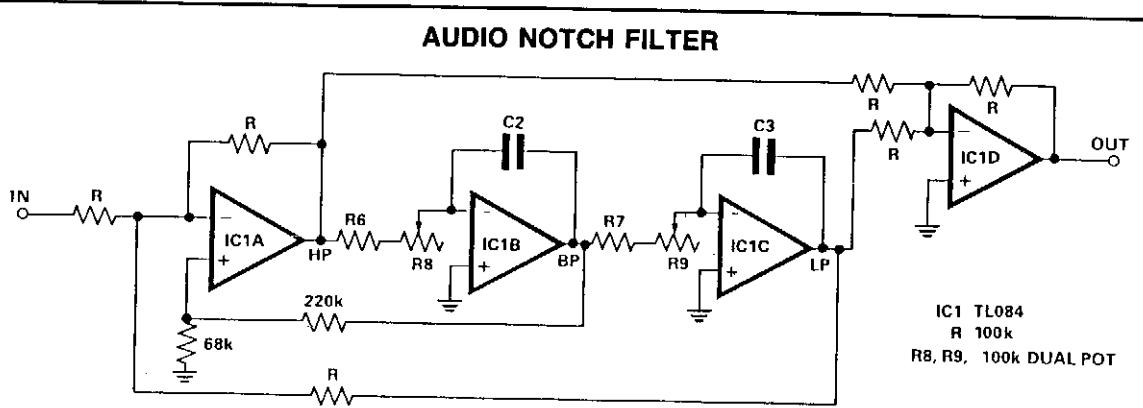


**Fig. 63-5**
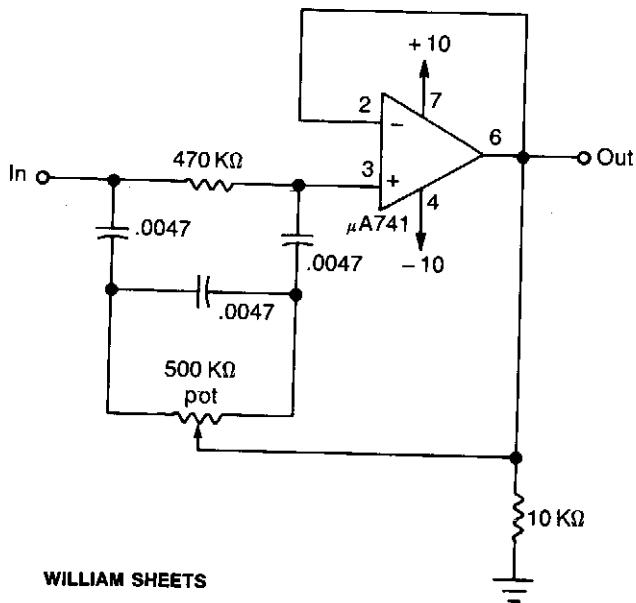
#### Circuit Notes

With the circuit shown here the response at one octave off tune is within 10% of the far out response: notch sharpness may be increased or reduced by reducing or increasing respectively the 68 K ohm resistor. Linearity tracking of R8 and R9 has no effect on notch depth. The signals at HP and LP are always in antiphase, notch will always be very deep at the tuned frequency, despite tolerance variations in R6-9 and C2, C3.

#### TUNABLE NOTCH FILTER USES AN OPERATIONAL AMPLIFIER





WILLIAM SHEETS

**Fig. 63-6**

#### Circuit Notes

This notch filter is useful for tunable band-reject applications in the audio range. The values shown will give a tuning range of about 300-1500 Hz.

### ACTIVE BAND-REJECT FILTER

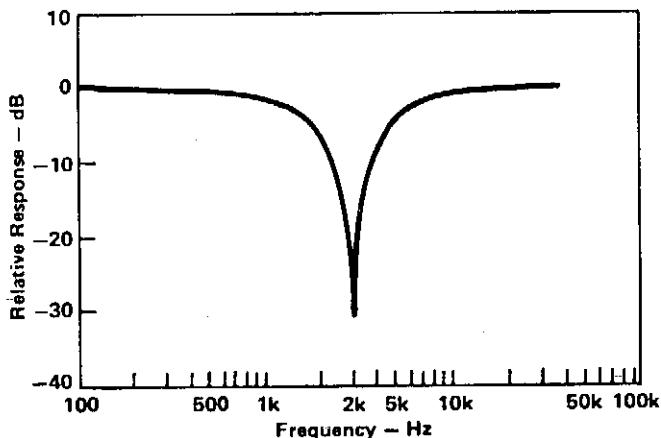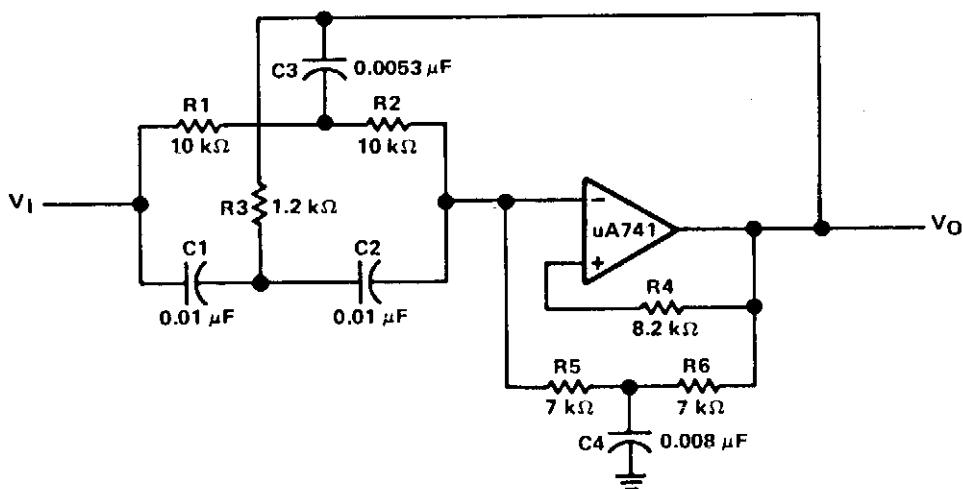

TEXAS INSTRUMENTS

Fig. 63-7

#### Circuit Notes

A filter with a band-reject characteristic is frequently referred to as a notch filter. A typical circuit using a  $\mu$ A 741 is the unity-gain configuration for this type of active filter shown. The filter response curve shown is a second-order band-reject filter with a notch frequency of 3 kHz. The resulting Q of this filter is about 23, with a notch depth of -31 dB. Although three passive T networks are used in this application, the operational amplifier has become a sharply tuned low-frequency filter without the use of inductors or large-value capacitors.

### WIEN BRIDGE NOTCH FILTER

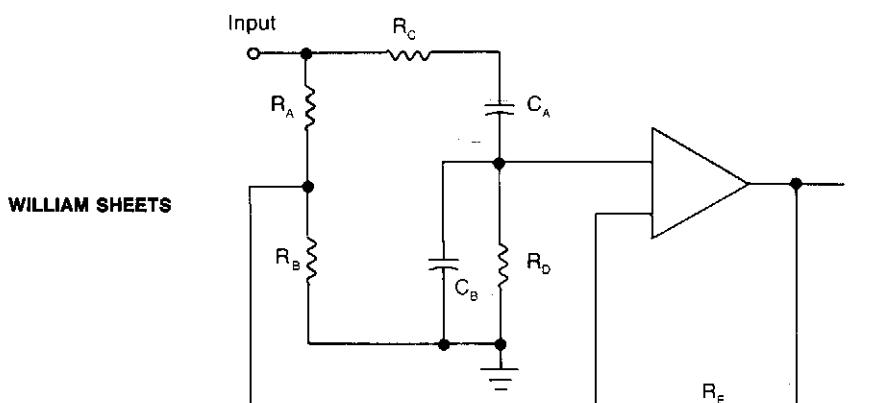


Fig. 63-8

if  $R_A = R_B = R_C = R_D = R_E = R$  and  $C_A = C_B = C$

$$f_{\text{null}} = \frac{1}{6.28 RC} \quad \begin{array}{l} R \text{ megohm} \\ C \text{ microfarad} \\ f \text{ Hertz} \end{array}$$

### TUNABLE AUDIO FILTER

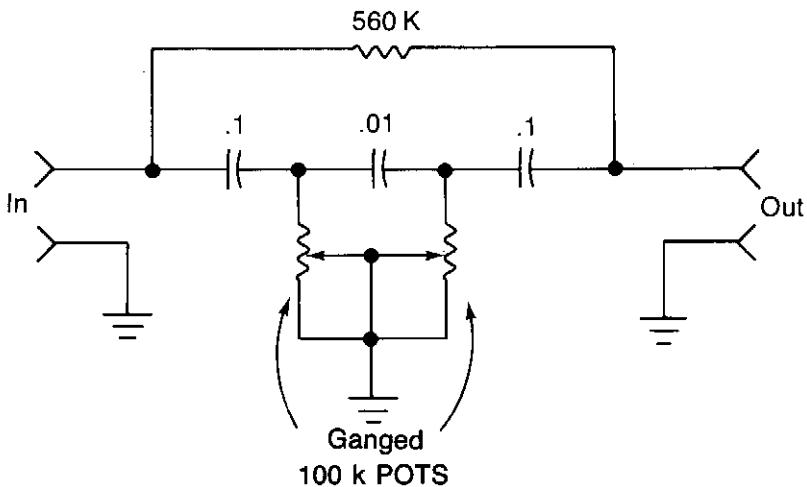



Fig. 63-9

WILLIAM SHEETS.

### Circuit Notes

This filter covers the upper part of the audio passband and can be used to eliminate unwanted high frequencies from audio signals.

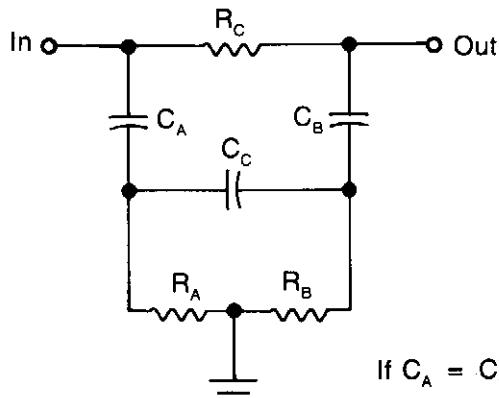
## PASSIVE BRIDGED, DIFFERENTIATOR TUNABLE NOTCH FILTER



If  $C_A = C_B = C_C = C$   
And if  $R_3 = 6(R_A + R_B)$

$$\text{Then } \left\{ \begin{array}{l} \text{Notch} \\ \text{freq} \end{array} \right\} = \frac{1}{6.28 C \sqrt{3R_A R_B}}$$

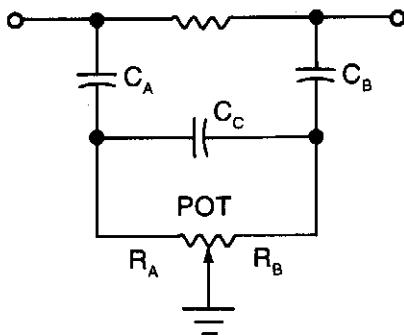If  $R_A$  and  $R_B$  is made a potentiometer  
then the filter can be variable.



WILLIAM SHEETS

Fig. 63-10

$R_A$  and  $R_B$  are sections of potentiometer.

# 64

## Operational Amplifier Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Variable Gain and Sign Op Amp Circuit  
Single Potentiometer Adjusts Op Amp's Gain Over  
Bipolar Range

## VARIABLE GAIN AND SIGN OP AMP CIRCUIT

Fig.1


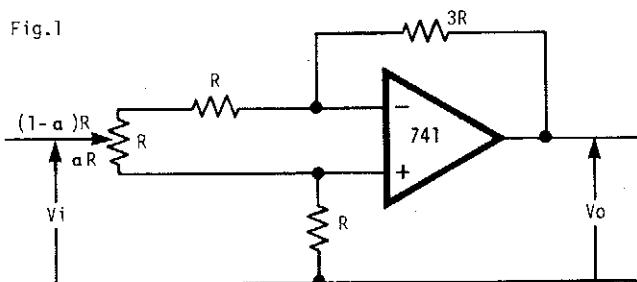


Fig.2

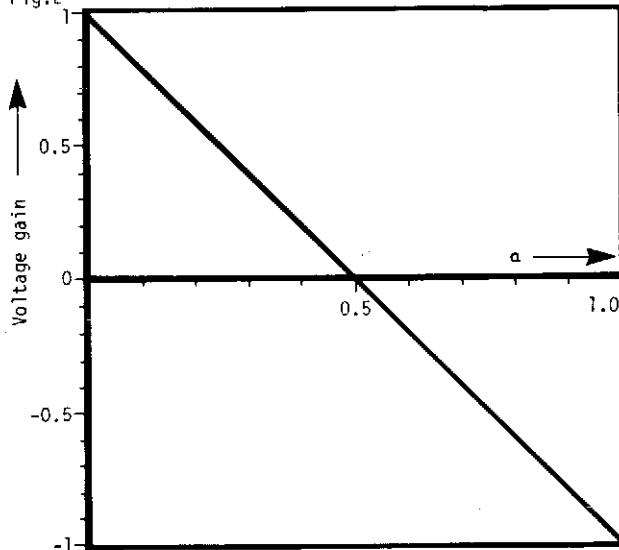

ELECTRONIC ENGINEERING

**Fig. 64-1**


### Circuit Notes

The gain of the amplifier is smoothly-controllable between the limits of +1 to -1. It is adjustable over this range using a single potentiometer. The voltage gain of the arrangement is given by:

$$\frac{V_o}{V_i} = \frac{2(1-2\alpha)}{(1+\alpha)(2-\alpha)}$$

Where  $\alpha$  represents the fractional rotation of the potentiometer, R.

## SINGLE POTENTIOMETER ADJUSTS OP AMP'S GAIN OVER BIPOLAR RANGE

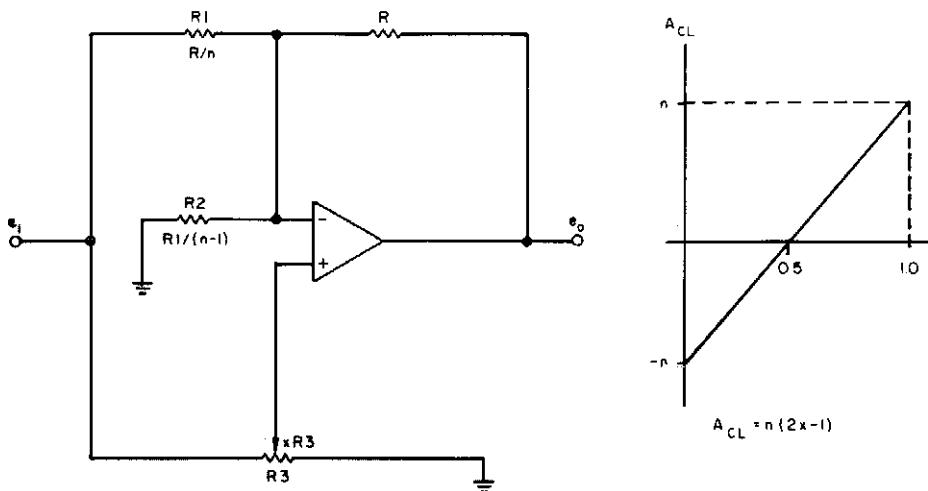

**Fig. 64-2**

### ELECTRONIC DESIGN

#### Circuit Notes

An op amp's gain level can be adjusted over its full inverting and noninverting gain range.  $R_3$  varies the signal applied to both the inverting and noninverting amplifier inputs. When the wiper position (denoted by  $x$ ) equals zero, the noninverting amplifier input is grounded. This also holds the voltage across  $R_2$  at zero, so  $R_2$  has no effect on operation. Now only  $R_1$  and  $R$  carry feedback current, and the amplifier operates at a gain of  $-n$ . At the other pot extreme, where  $x = 1$ , the input signal is connected directly to the noninverting input. Since feedback maintains a near-zero voltage between the amplifier inputs, the amplifier's inverting input will also be near the input signal level, thus little voltage is across  $R_1$ , also now the gain is  $+n$ . The amplifier should be driven from a low impedance source to minimize source loading error, low offset op amps should be used.

# 65

## Optically-Coupled Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Three-Phase Switch for Inductive Load

Integrated Solid State Relay

Stable Optocoupler

Microprocessor Triac Array Driver

DC Linear Coupler

Linear AC Analog Coupler

Simple AC Relay Using Two Photon Couplers

Linear Analog Coupler

High Sensitivity, Normally Open, Two Terminal,

Zero Voltage Switching Half-Wave Contact Circuit

High Speed Paper Tape Reader

Digital Transmission Isolator

Isolation and Zero Voltage Switching Logic

Optical Communication System

Linear Optocoupler Circuit for Instrumentation

50 kHz Center Frequency FM Optical Transmitter Receiver for 50 kHz FM Optical Transmitter

### THREE-PHASE SWITCH FOR INDUCTIVE LOAD

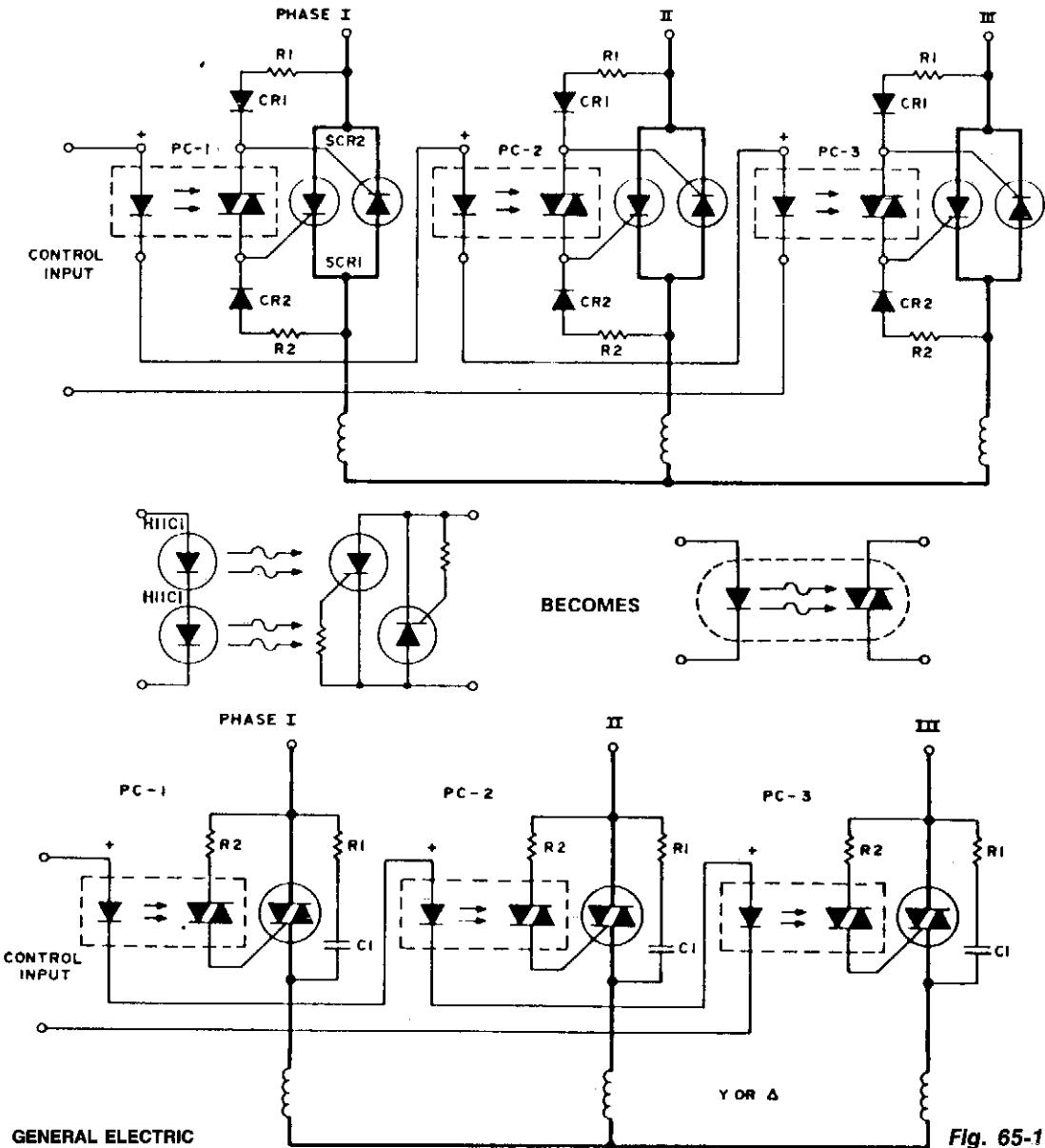
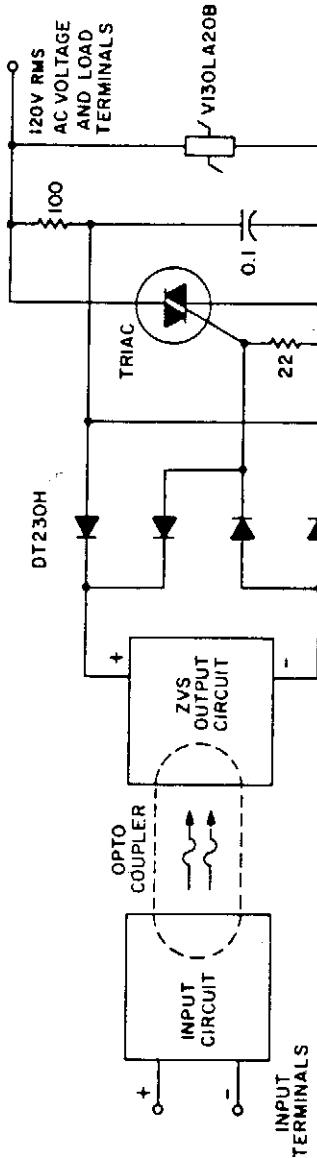


Fig. 65-1

#### Circuit Notes

The following are three-phase switches for low voltage. Higher currents can be obtained by using inverse parallel SCRs which would be triggered as shown. To simplify the following schematics and facilitate easy understanding of the principles involved, the following schematic substitution is used (Note the triac driver is of limited use at  $3\phi$  voltage levels).

## INTEGRATED SOLID STATE RELAY

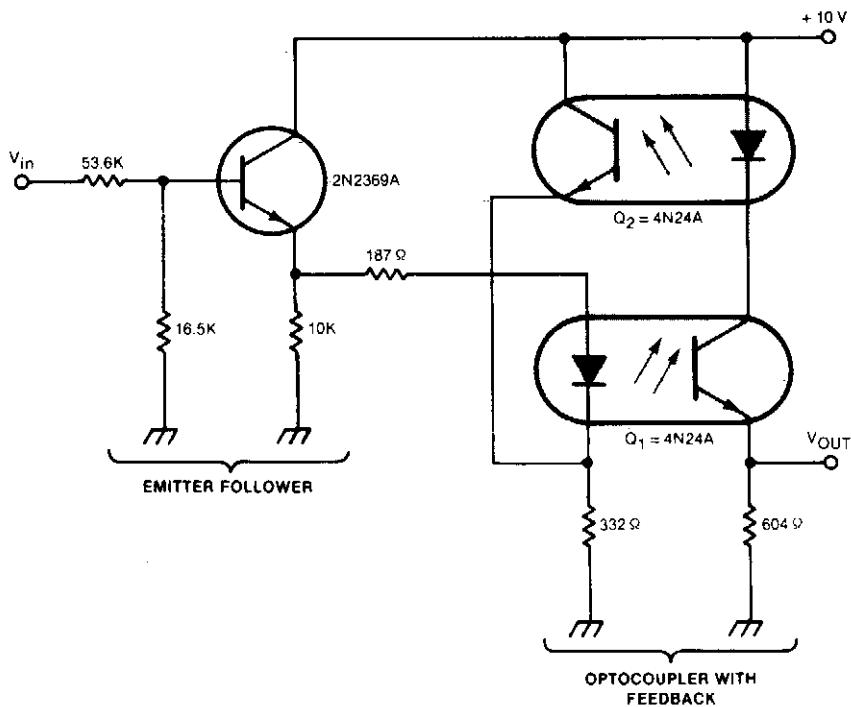


**Fig. 65-2**

### Circuit Notes

A complete zero-voltage switch solid-state relay contains an input circuit, an output circuit, and the power thyristor. The circuit illustrates a triac power thyristor with snubber circuit and GE-MOV R II Varistor transient over-voltage protection. The 22 ohm resistor shunts di/dt currents, passing through the bridge diode capacitances, from the triac gate, while the 100 ohm resistor limits surge and gate currents to safe levels. Although the circuits illustrated are for 120-V rms operation, relays that operate on 220 V require higher voltage ratings on the MOV, rectifier diodes, triac, and pilot SCR. The voltage divider that senses zero crossing must also be selected to minimize power dissipation in the transistor isolator circuit for 220-V operation.

## STABLE OPTOCOUPLED




NASA

*Fig. 65-3*

### Circuit Notes

A circuit stabilizes the current-transfer ratio (CTR) of an optically coupled isolator used as a linear transducer. The optocoupler produces a voltage output that is proportional to—but electrically isolated from—the voltage input. However, the output voltage is directly affected by changes in the CTR, and the CTR can change substantially with temperature and current. To a lesser extent the CTR changes with time over the life of the optocoupler. The circuit employs a feedback circuit containing a second optocoupler. The feedback signal tends to oppose changes in the overall CTR.

## MICROPROCESSOR TRIAC ARRAY DRIVER

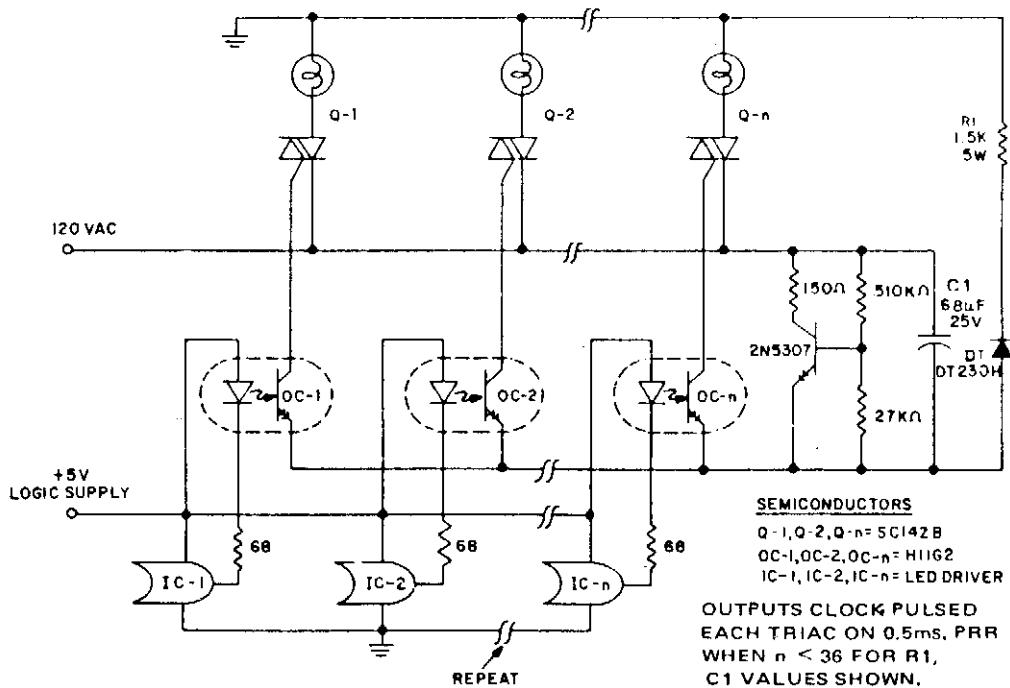


GENERAL ELECTRIC

Fig. 65-4

### Circuit Notes

In microprocessor control of multiple loads, the minimum cost per load is critical. A typical application example is a large display involving driving arrays of incandescent lamps. This circuit provides minimal component cost per stage and optocoupler triggering of triac power switches from logic outputs. The minimal component cost is attained by using more complex software in the logic. A darlington output optocoupler provides gate current pulses to the triac, with cost advantages gained from eliminating the current limiting resistor and from the low cost coupler. The trigger current source is a dipped tantalum capacitor, charged from the line via a series resistor with coarse voltage regulation being provided by the darlington signal transistor. The resistor and capacitor are shared by all the darlington-triac pairs and are small in size and cost due to the low duty cycle of pulsing. Coupler IRED current pulses are supplied for the duration of one logic clock pulse (2-10  $\mu$ sec), at 0.4 to 1 msec intervals, from a LED driver I.C. The pulse timing is derived from the clock waveform when the logic system requires triac conduction. A current limiting resistor is not used, which prevents Miller effect slowdown of the H11G2 switching speed to the extent the triac is supplied insufficient current to trigger. Optodarlington power dissipation is controlled by the low duty cycle and the capacitor supply characteristics.

## DC LINEAR COUPLER

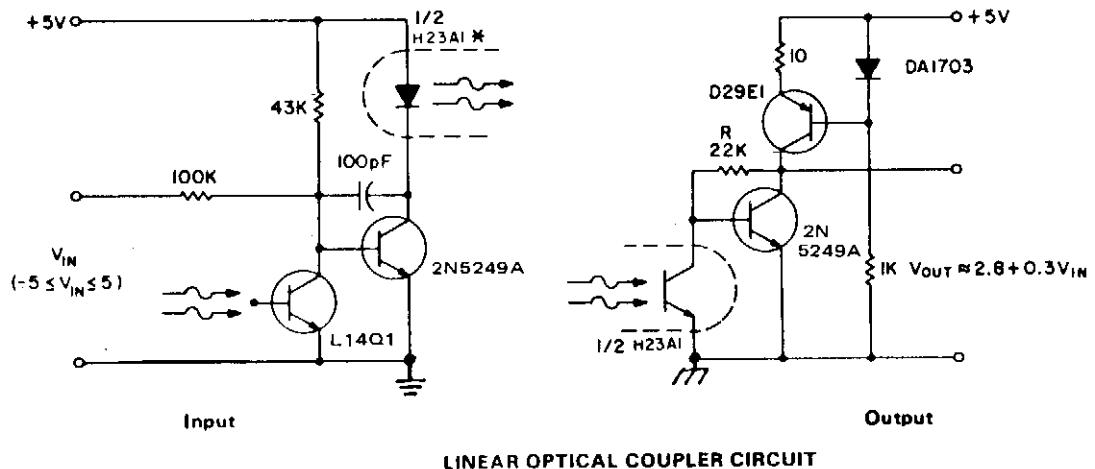

\*Closely positioned to illuminate L14Q1 and H23A1 Detector, such that  $V_{OUT} \cong 2.8V$  at  $V_{IN} = 0$ .

GENERAL ELECTRIC

**Fig. 65-5**

### Circuit Notes

The accuracy of direct linear coupling of analog current signals via an optocoupler is determined by the coupler linearity and its temperature coefficient. Use of an additional coupler for feedback can provide linearity only if the two couplers are perfectly matched and identically biased. These are not practical constraints in most equipment designs and indicate the need for a different design approach. One of the most successful solutions to this problem can be illustrated by using a H23 emitter-detector pair and a L14H4. The H23 detector and L14H4 are placed so both are illuminated by the H23 IRED emitter. Ideally, the circuit is mechanically designed such that the H23 emitter may be positioned to provide  $V_{OUT} = 2.8V$  when  $V_{IN} = 0$ , thereby insuring collector current matching in the detectors. Then all three devices are locked in position relative to each other. Otherwise, R may be adjusted to provide the proper null level, although temperature tracking should prove worse when R is adjusted. Note that the input bias is dependent on power supply voltage, although the output is relatively independent of supply variations. Testing indicated linearity was better than could be resolved, due to alignment motion caused by using plastic tape to lock positions. The concept of feedback control of IRED power output is useful for both information transmission and sensing circuitry.

### LINEAR AC ANALOG COUPLER

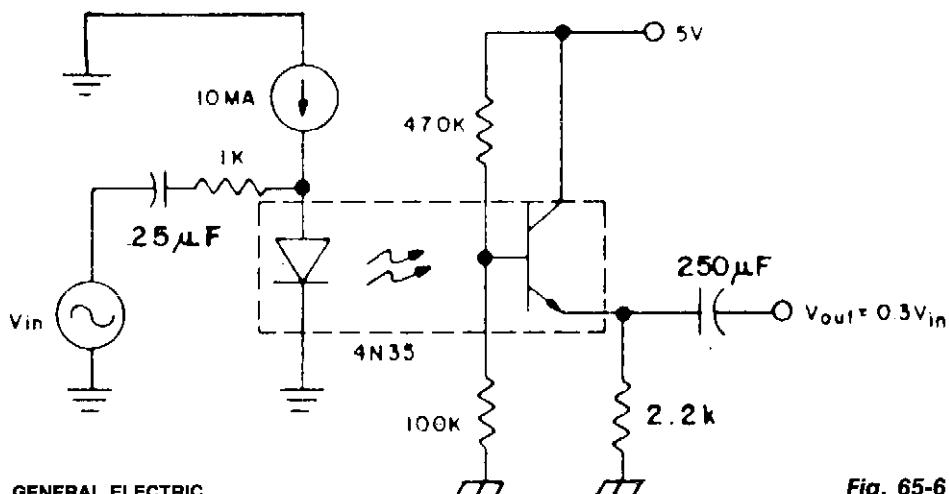


Fig. 65-6

### Circuit Notes

With the coupler biased in the linear region by the 10 mA dc bias on the IRED and the voltage divider on the phototransistor base, photodiode current flows out of the base into the voltage divider, producing an ac voltage proportional to the ac current in the IRED. The transistor is biased as an emitter follower and requires less than 10% of the photodiode current to produce the low impedance ac output across the emitter resistor. Note that the H11AV1 may be substituted for the 4N35 to provide VDE line voltage rated isolation of less than 0.5 pF.

### SIMPLE AC RELAY USING TWO PHOTON COUPLERS


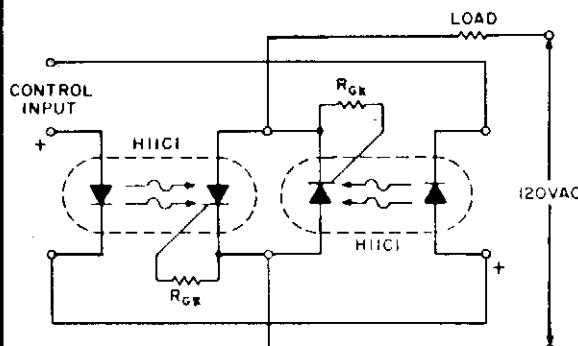


Fig. 65-7

### Circuit Notes

If load current requirements are relatively low (i.e. maximum forward rms current 500 mA), an ac solid state relay can be constructed quite simply by the connection of two H11C optically coupled SCRs in a back-to-back configuration as illustrated.

## LINEAR ANALOG COUPLER

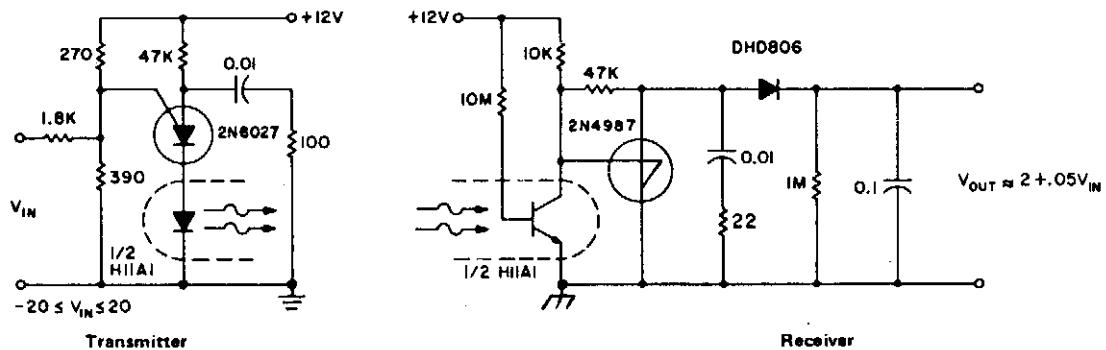

GENERAL ELECTRIC

Fig. 65-8

### Circuit Notes

The minimum parts count version of this system provides isolated, linear signal transfer useful at shorter distances or with an optocoupler for linear information transfer. Although the output is low level and cannot be loaded significantly without harming accuracy, a single I.C. operational or instrumentation amplifier can supply both the linear gain and buffering for use with a variety of loads.

## HIGH SENSITIVITY, NORMALLY OPEN, TWO TERMINAL, ZERO VOLTAGE SWITCHING, HALF-WAVE CONTACT CIRCUIT

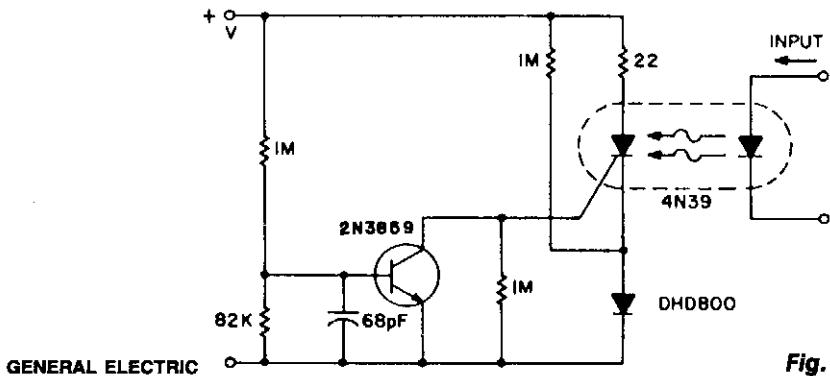


Fig. 65-9

### Circuit Notes

The SCR coupler circuit provides higher sensitivity to input signals as illustrated. This allows the lower cost 4N39 (H11C3) to be used with the  $> 7$  mA drive currents supplied by the input circuit.

## HIGH SPEED PAPER TAPE READER


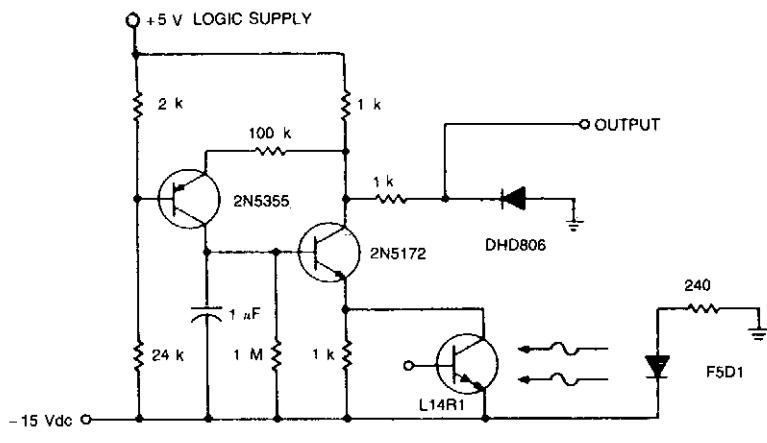


Fig. 65-10

### Circuit Notes

When computer peripheral equipment is interfaced, it is convenient to work with logic signal levels. With a nominal 4 V at the output dropping to -0.6 V on illumination, this circuit reflects the requirements of a high-speed, paper tape optical reader system. The circuit operates at rates of up to 1000 bits per second. It will also operate at tape translucency such that 50% of the incident light is transmitted to the sensor, and provide a fixed threshold signal to the logic circuit, all at low cost. Several circuit tricks are required. Photodarlington speed is enhanced by cascode constant voltage biasing. The output threshold and tape translucency requirements are provided for by sensing the output voltage and operating to 2000 bits per second at ambient light levels equal to signal levels.

## DIGITAL TRANSMISSION ISOLATOR

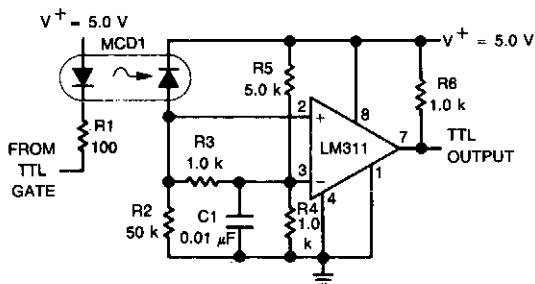


### Circuit Notes

An optoelectronics device is used to couple a digital (TTL) signal to another system. The photodiode in the optocoupler drives an LM311 set up to produce a TTL compatible output. It is useful where grounds are not able to be connected for any reason.

Fig. 65-11
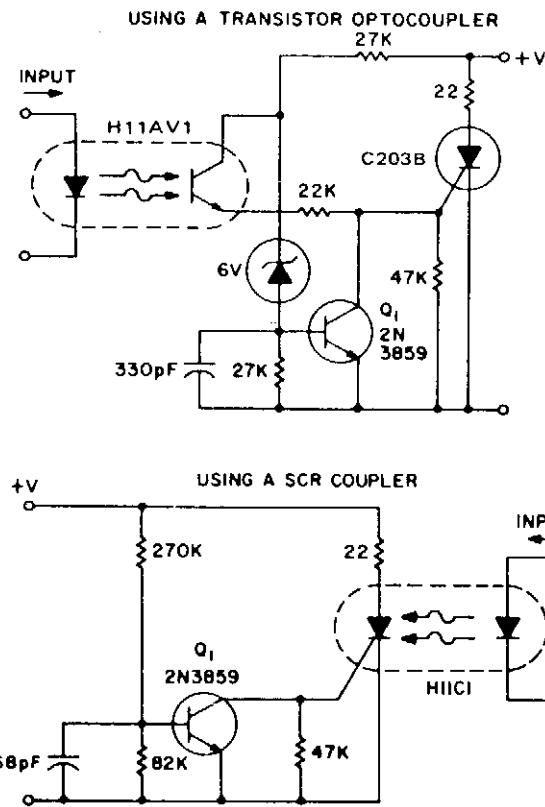
## ISOLATION AND ZERO VOLTAGE SWITCHING LOGIC



NORMALLY OPEN, TWO TERMINAL, ZERO VOLTAGE SWITCHING HALF WAVE CONTACT CIRCUITS


GENERAL ELECTRIC

*Fig. 65-12*

### Circuit Notes

These two simple circuits provide zero voltage switching. They can be used with full wave bridges or in antiparallel to provide full wave control and are normally used to trigger power thyristors. If an input signal is present during the time the ac voltage is between 0 to 7 V, the SCR will turn on. But, if the ac voltage has risen above this range and the input signal is then applied, the transistor, Q1, will be biased to the "on" state and will hold the SCR and, consequently, the relay "off" until the next zero crossing.

## OPTICAL COMMUNICATION SYSTEM

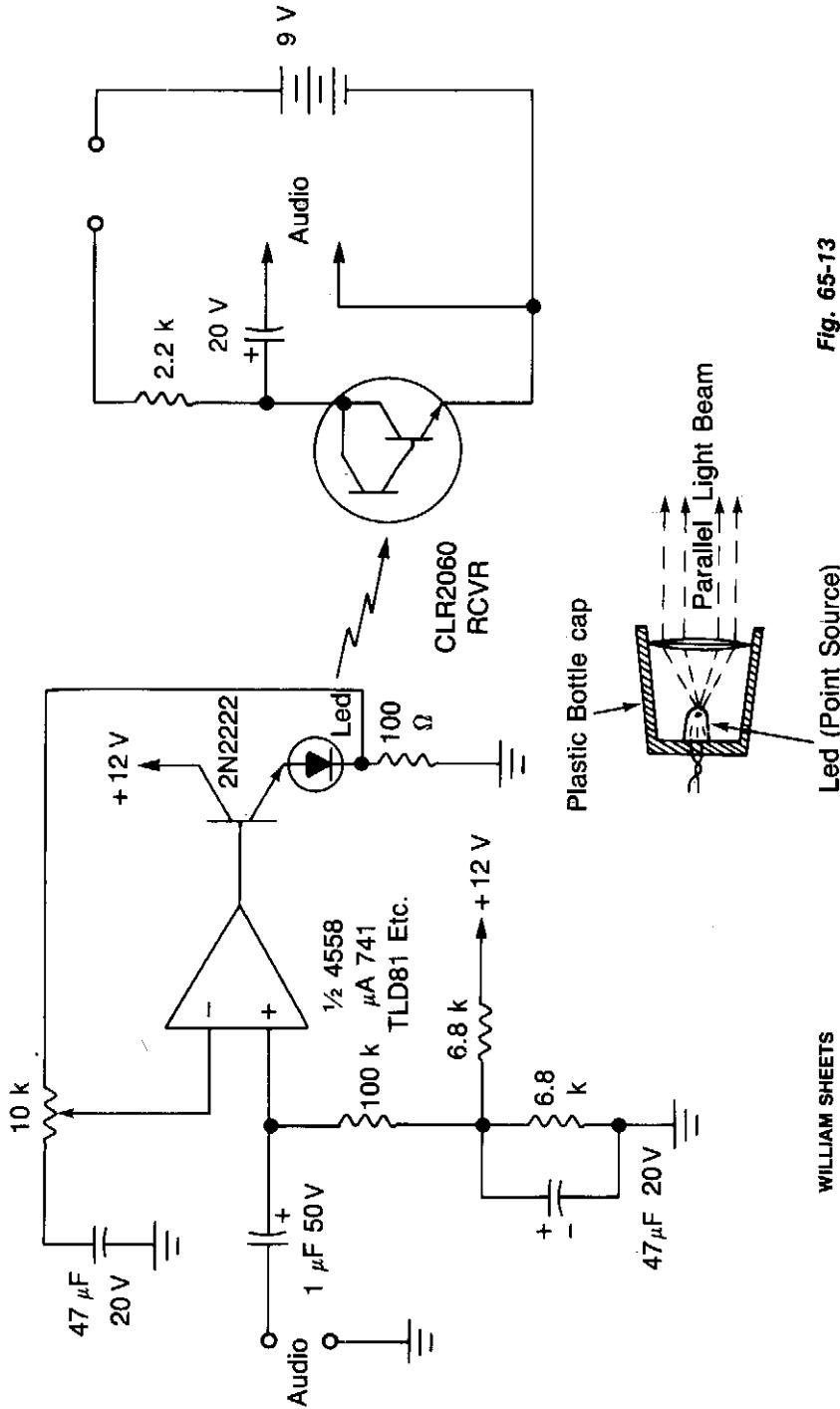


**Fig. 65-13**

Led (Point Source)

### Circuit Notes

The circuit will modulate the light from the LED using a crystal microphone or a loudspeaker output. To obtain the maximum range, the optical system must be efficient (see example). Either a convex lens or a concave mirror can be used to convert the LED output into a parallel beam. The received light is concentrated onto a sensitive photodarlington transistor. At short range the signal across the load resistor is adequate to drive a crystal earpiece, for longer range an amplifier and a loudspeaker are needed.

## 50 kHz CENTER FREQUENCY FM OPTICAL TRANSMITTER

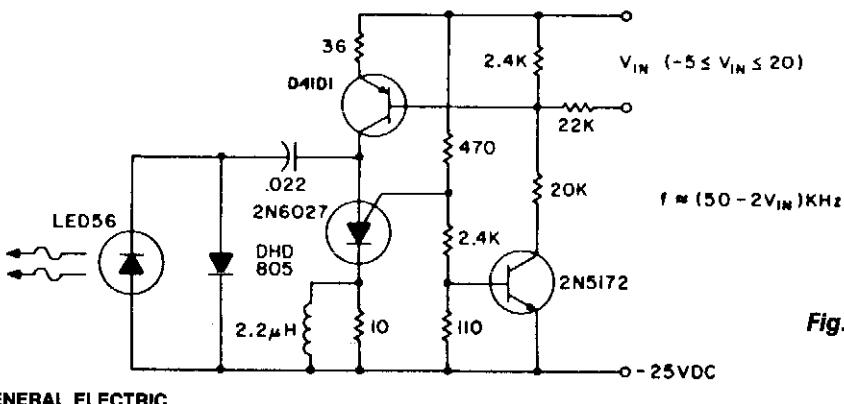


**Fig. 65-14**
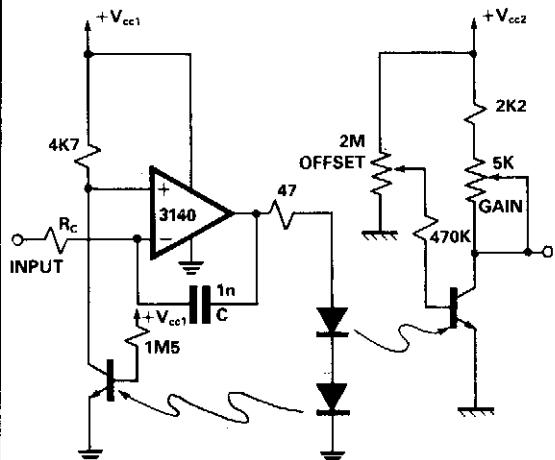
### Circuit Notes

The pulse repetition rate is relatively insensitive to temperature, and power supply voltage and is a linear function of  $V_{IN}$ , the modulating voltage. Useful information transfer was obtained in free air ranges of 12 feet ( $\approx 4\text{m}$ ). Lenses or reflectors at the light emitter and detector increases range and minimizes stray light noise effects. Greater range can also be obtained by using a higher power output IRED such as the F5D1 in combination with the L14P2 phototransistor. Average power consumption of the transmitter circuit is less than 3 watts.

## LINEAR OPTOCOUPLER CIRCUIT FOR INSTRUMENTATION




### Circuit Notes

A dual optocoupler is used in a configuration which has the same current throughout as the LEDs. Assuming similar optocoupler features the output voltage must be equal to the non-inverting input voltage. Since the op amp is within a closed loop the output voltage becomes equal to the input voltage.  $R_c$  and  $C$  perform as a compensation network to prevent oscillations.

**Fig. 65-15**
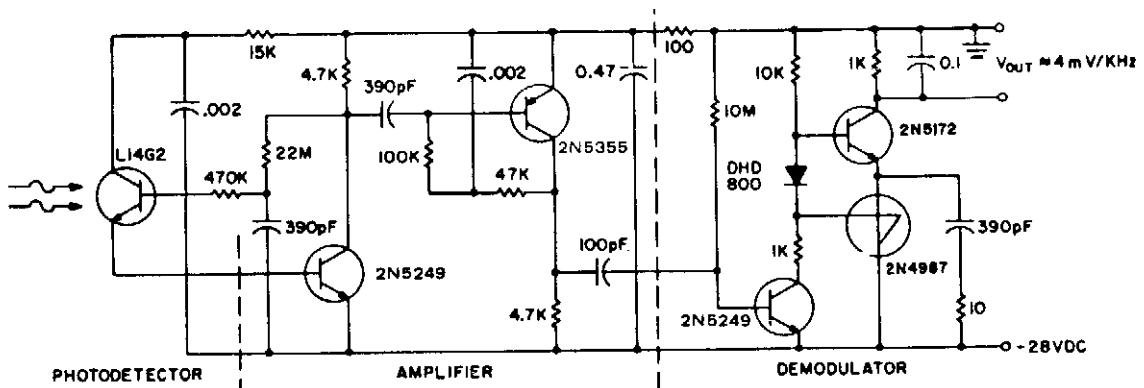
## RECEIVER FOR 50 kHz FM OPTICAL TRANSMITTER



GENERAL ELECTRIC

*Fig. 65-16*

### Circuit Notes

For maximum range, the receiver must be designed in the same manner as a radio receiver front end, since the received signals will be similar in both frequency component and in amplitude of the photodiode current. The major constraint on the receiver performance is signal to noise ratio, followed by e.m. shielding, stability, bias points, parts layout, etc. These become significant details in the final design. This receiver circuit consists of a L14G2 detector, two stages of gain, and a FM demodulator which is the tachometer circuit, modified to operate up to 100 kHz. Better sensitivity can be obtained using more stages of stabilized gain with AGC, lower cost and sensitivity may be obtained by using an H23A1 emitter-detector pair and/or by eliminating amplifier stages. For some applications, additional filtering of the output voltage may be desired.

# **66**

## **Oscillators**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

RF-Genie	Resistance Controlled Digital Oscillator
Emitter-Coupled Big Loop Oscillator	Cassette Bias Oscillator
Simple Triangle Square Wave Oscillator	1 kHz Oscillator
Oscillator Adjustable over 10:1 Range	Inexpensive Oscillator is Temperature Stable
One Second, 1 kHz Oscillator	Code Practice Oscillator
Single Control Four-Decade Variable Oscillator	Wide Range Variable Oscillator
Tunable Frequency Oscillators	

## RF-GENIE

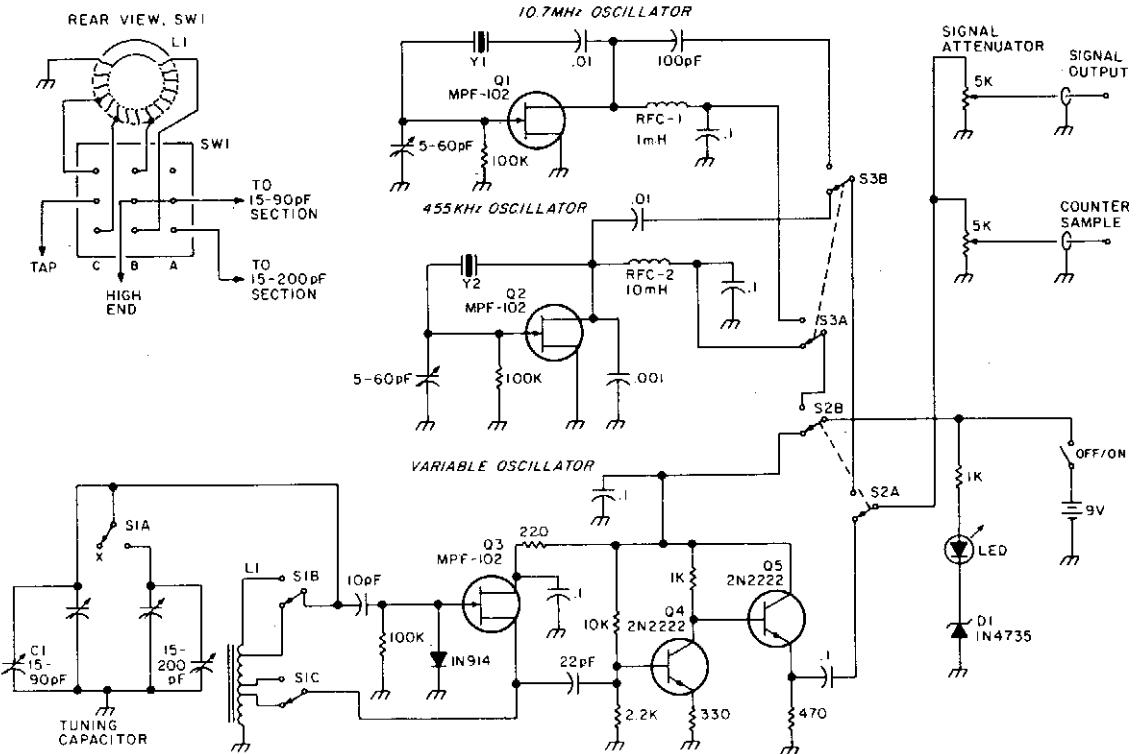


73 MAGAZINE

Fig. 66-1

### Circuit Notes

A variable oscillator covers 3.2 to 22 MHz in two bands—providing coverage of 80 through 15 meters plus most crystal-filter frequencies. Optional 455 kHz and 10.7 MHz crystal oscillators can be switched on-line for precise *if* alignment. Generator output is on the order of 4 volts p-p into a 500 ohm load. A simple voltage-divider attenuator controls the generator's output level, and a second output provides sufficient drive for an external frequency counter.

## EMITTER-COUPLED BIG LOOP OSCILLATOR

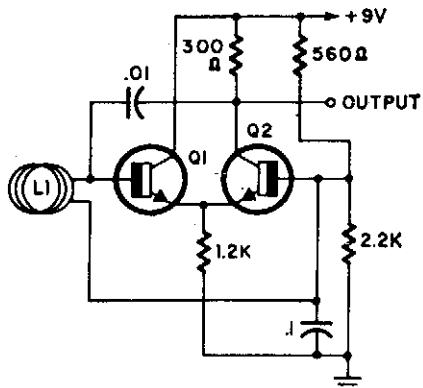


RADIO-ELECTRONICS

Fig. 66-2

### Circuit Notes

L1 is a loop of 10 to 20 turns of insulated wire with a diameter anywhere between 4" to 4'. Oscillator frequency (7 to 30 MHz) shifts substantially when a person comes near or into the loop. This oscillator together with a resonant detector might make a very good anti-personnel alarm. Transistors are 2N2926 or equivalent.
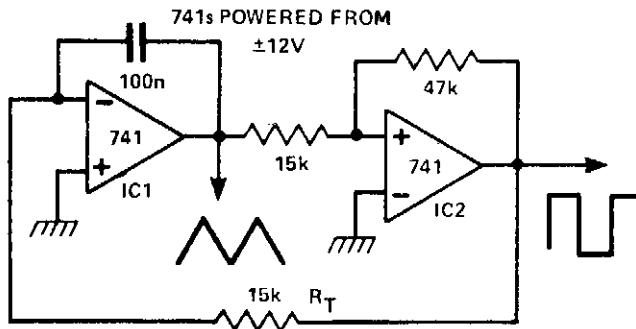
## SIMPLE TRIANGLE SQUARE WAVE OSCILLATOR




ELECTRONICS TODAY INTERNATIONAL

Fig. 66-3

### Circuit Notes

This circuit generates simultaneously, a triangle and a square waveform. It is self starting and has no latch up problems. IC1 is an integrator with a slew rate determined by CT and RT and IC2 is a Schmitt trigger. The output of IC1 ramps up and down between the hysteresis levels of the Schmitt, the output of which drives the integrator. By making RT variable, it is possible to alter the operating frequency over a 100 to 1 range. Three resistors, one capacitor, and a dual op amp is all that is needed to make a versatile triangle and square wave oscillator with a possible frequency range of 0.1 Hz to 100 kHz.

## OSCILLATOR ADJUSTABLE OVER 10:1 RANGE

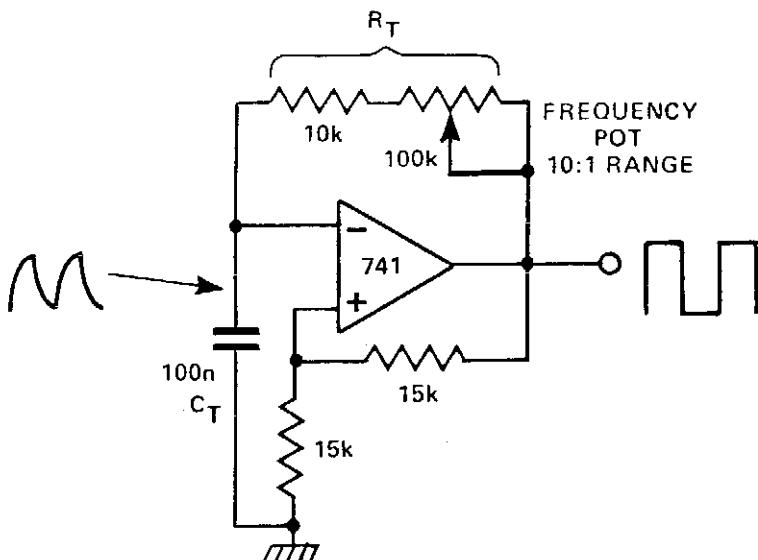


ELECTRONICS TODAY INTERNATIONAL

**Fig. 66-4**

### Circuit Notes

In this circuit, there are two feedback paths around an op amp. One is positive dc feedback which forms a Schmitt trigger. The other is a CR timing network. Imagine that the output voltage is +10 V. The voltage at the noninverting terminal is +15 V. The voltage at the inverting terminal is a rising voltage with a time constant of  $C_T R_T$ . When this voltage exceeds +5 V, the op amp's output will go low and the Schmitt trigger action will make it snap into its negative state. Now the output is -10 V and the voltage at the inverting terminal falls with the time constant as before. By changing this time constant with a variable resistor, a variable frequency oscillation may be produced.

## ONE SECOND, 1 kHz OSCILLATOR

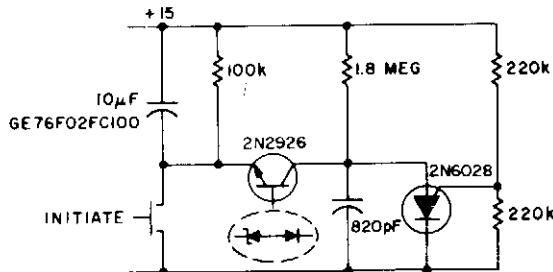


GENERAL ELECTRIC

**Fig. 66-5**

### Circuit Notes

This circuit operates as an oscillator and a timer. The 2N6028 is normally on due to excess holding current through the 100 k resistor. When the switch is momentarily closed, the 10  $\mu$ F capacitor is charged to a full 15 volts and 2N2926 starts oscillating (1.8 M and 820 pF). The circuit latches when 2N2926 zener breaks down again.
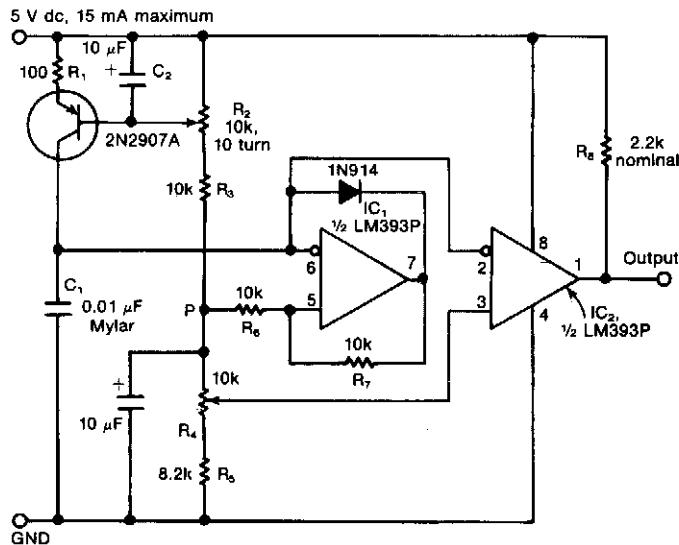
## SINGLE CONTROL FOUR-DECADE VARIABLE OSCILLATOR



ELECTRONIC DESIGN

*Fig. 66-6*

### Circuit Notes

The circuit consists of a variable current source that charges a capacitor, which is rapidly discharged by a Schmitt-trigger comparator. The sawtooth waveform thus produced is fed to another comparator, one with a variable switching level. The output from the second comparator is a pulse train with an independently adjustable frequency and duty cycle. The variable-frequency ramp generator consists of capacitor C1, which is charged by a variable and nonlinear current source. The latter comprises a 2N2907A pnp transistor, plus resistor R1 and the potentiometer R2. Capacitor C2 eliminates any ripple or noise at the base of the transistor that might cause frequency jitter at the output.

## TUNABLE FREQUENCY OSCILLATORS

**FREQUENCY RANGE**  
40 Hz to 65 kHz

**OUTPUT PULSE**

Rise time ~ 200 nsec.  
Pulse width ~ 10  $\mu$ sec.  
Recovery time < 200 nsec.

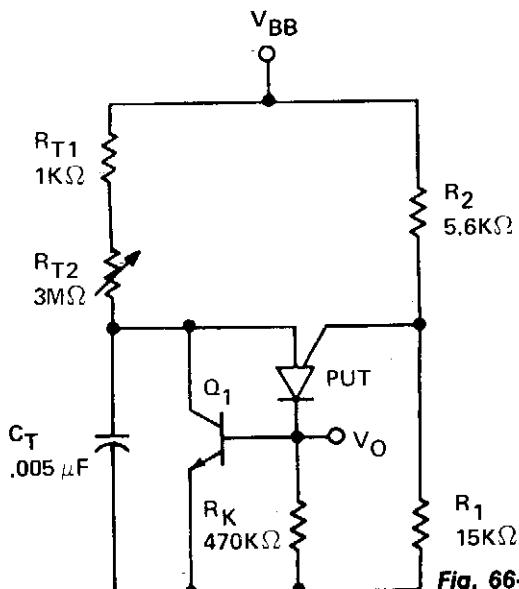


Fig. 66-7A

**FREQUENCY RANGE**  
40 Hz to 40 kHz

**OUTPUT PULSE**  
Width ~ 5  $\mu$ sec.

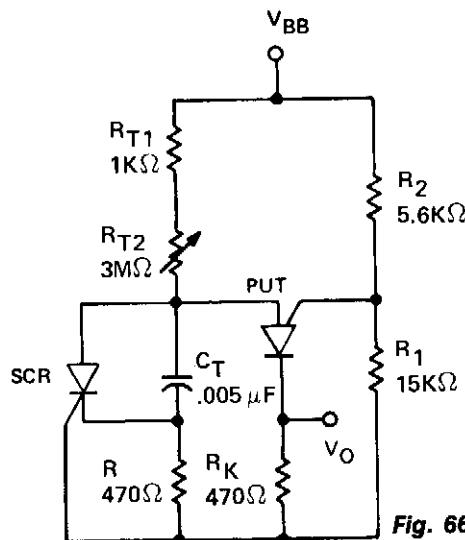



Fig. 66-7B

UNITRODE CORPORATION

### Circuit Notes

The variable oscillator circuit includes active elements for discharging the timing capacitor  $C_T$  shown in Fig. 66-7A. A second method is given as in Fig. 66-7B.
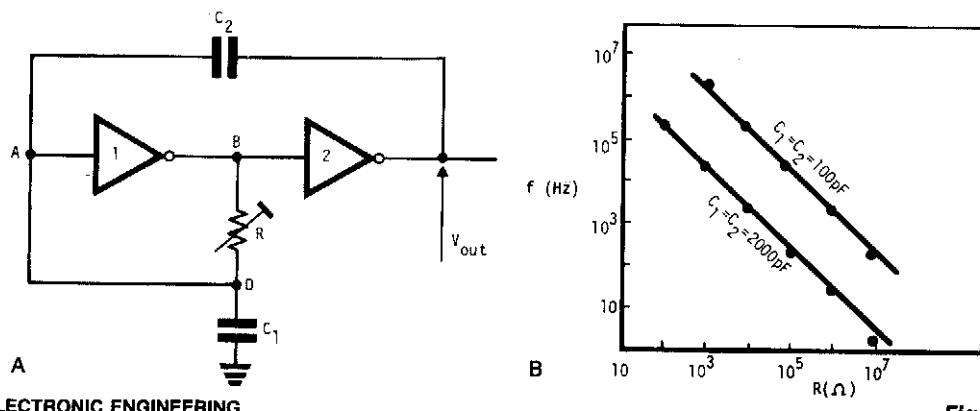
## RESISTANCE CONTROLLED DIGITAL OSCILLATOR



ELECTRONIC ENGINEERING

**Fig. 66-8**


### Circuit Notes

This very simple, low cost oscillator, is built with two CMOS buffer inverters, two capacitors and a variable resistance. The circuit can work with voltages ranging from 4 V up to 18 V. If C<sub>1</sub> = C<sub>2</sub>, the frequency of oscillation, (ignoring the output and input impedance) is given by:

$$f = \frac{1}{4\pi\sqrt{2RC}}$$

The graph in Fig. B shows how the output frequency varies with resistance when C<sub>1</sub> = C<sub>2</sub> = 100 pF and C<sub>1</sub> = C<sub>2</sub> = 2000 pF.


## CASSETTE BIAS OSCILLATOR

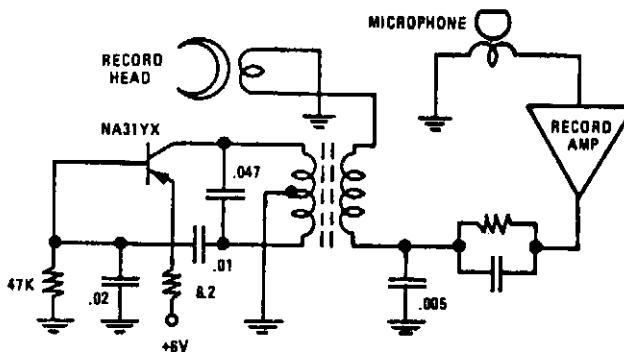

**Fig. 66-9**

NATIONAL SEMICONDUCTOR

## 1 kHz OSCILLATOR

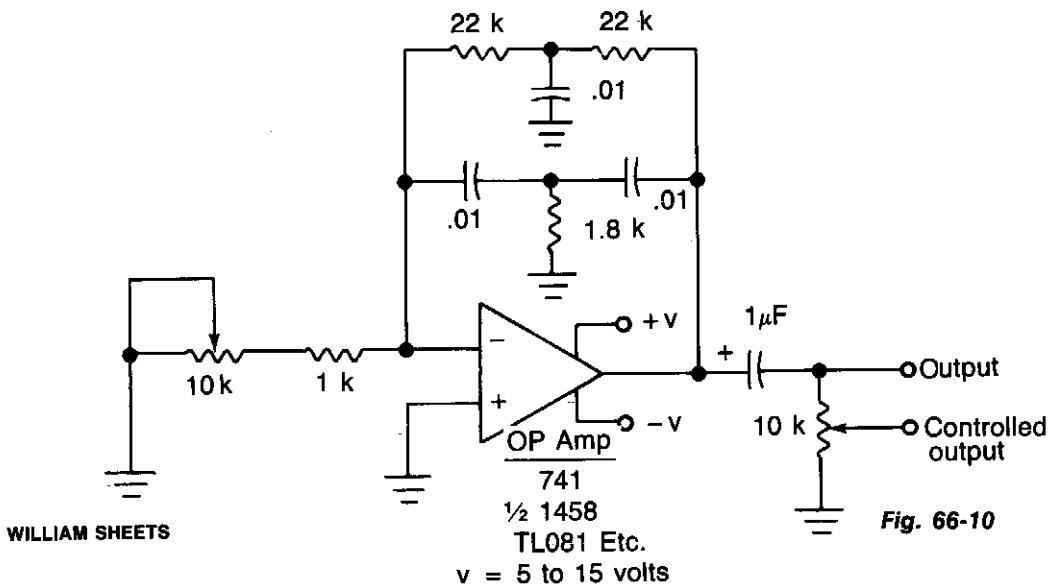

### Circuit Notes


If fine output control is desired, add the 10 K potentiometer. When the oscillator is connected to a dc circuit then connect a dc blocking capacitor in series with the potentiometer's wiper arm.

## INEXPENSIVE OSCILLATOR IS TEMPERATURE STABLE
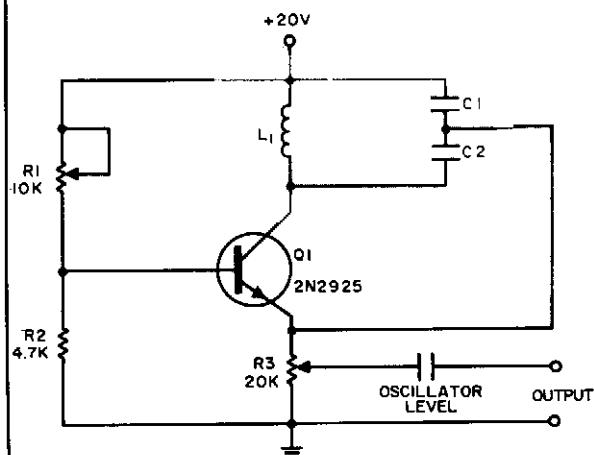
### Circuit Notes

The Colpitts sinusoidal oscillator provides stable output amplitude and frequency from 0°F to +150°F. In addition, output amplitude is large and harmonic distortion is low. Oscillation is sustained by feedback from the collector tank circuit to the emitter. The oscillator's frequency is determined by:

$$f = \frac{1}{2\pi \sqrt{\frac{L_1 C_1 C_2}{C_1 + C_2}}}$$



Potentiometer R3 is an output level control. Control R1 may be used to adjust base bias for maximum-amplitude output. The circuit was operated at 50 kHz with  $L_1 = 10\text{mH}$ ,  $C_1 = 3500 \text{ pF}$ , and  $C_2 = 1500 \text{ pF}$ .

## CODE PRACTICE OSCILLATOR


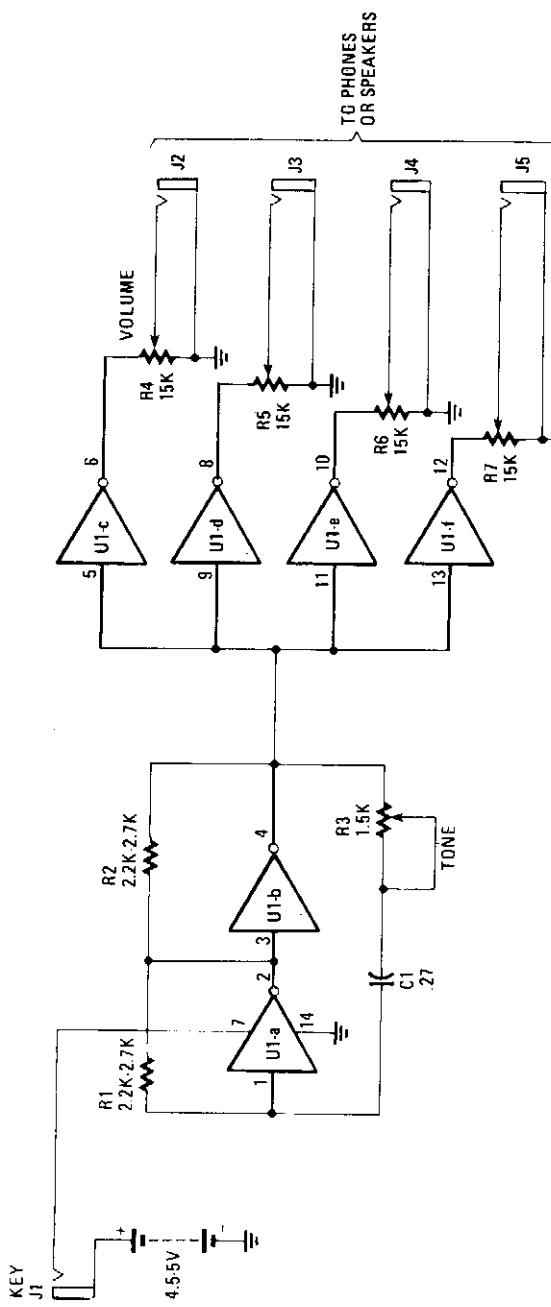


Fig. 66-12

### Circuit Notes

The inexpensive 7404 hex-inverter has enough amplification to handle a wide range of transducers. Closing the key completes the battery circuit and applies four to five volts to the 7404. Bias for the first two inverter amps (U1a and U1b) comes from the two resistors, R1 and R2, connected between their inputs and outputs. The capacitor and rheostat (R3/C1) close the feedback loop from the input to the properly-phased output. The signal leaving U1b drives the remaining four inverter amplifiers, U1c through U1f; they, in turn, drive the phones or speakers. The volume control potentiometers, R4-R7, may have any value from 1500 ohms to 10,000 ohms. The smaller values work best when speakers, or low impedance phones, are used.

## WIDE RANGE VARIABLE OSCILLATOR

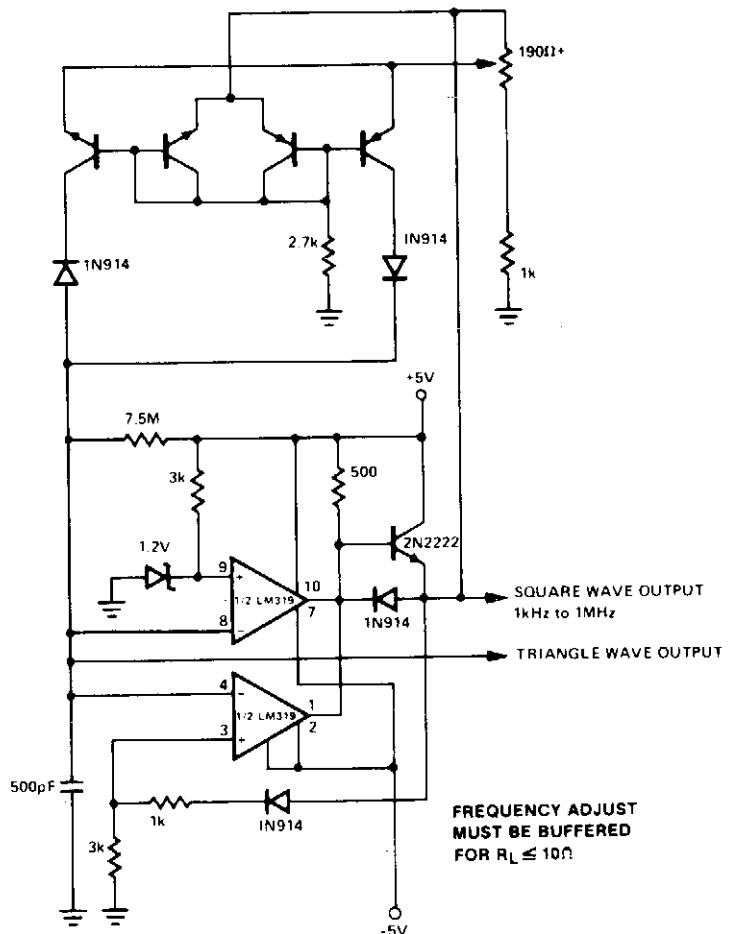

SIGNETICS

*Fig. 66-13*

# **67**

## **Oscilloscope Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Analog Multiplexer Converts Single-Trace Scope to  
Four-Trace  
FET Dual-Trace Scope Switch  
Scope Calibrator

## ANALOG MULTIPLEXER CONVERTS SINGLE-TRACE SCOPE TO FOUR-TRACE

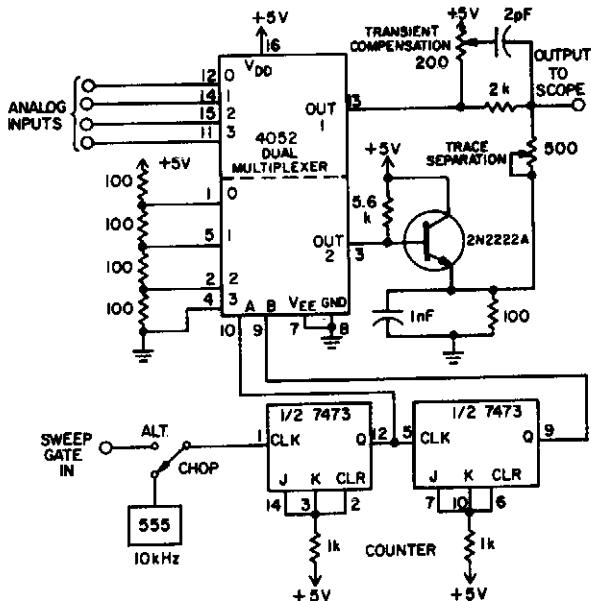


**Fig. 67-1**

ELECTRONIC DESIGN

### Circuit Notes

This adapter circuit, based on a dual four-channel analog multiplexer handles digital signals to at least 1 MHz, and analog signals at least through the audio range. The dual multiplexer's upper half selects one input for display. The lower half generates a staircase to offset the baselines of each channel, keeping them separate on the screen. The emitter-follower buffers the staircase, which is then summed with the selected signal. A two-bit binary counter addresses the CMOS 4052 multiplexer.

### FET DUAL-TRACE SCOPE SWITCH

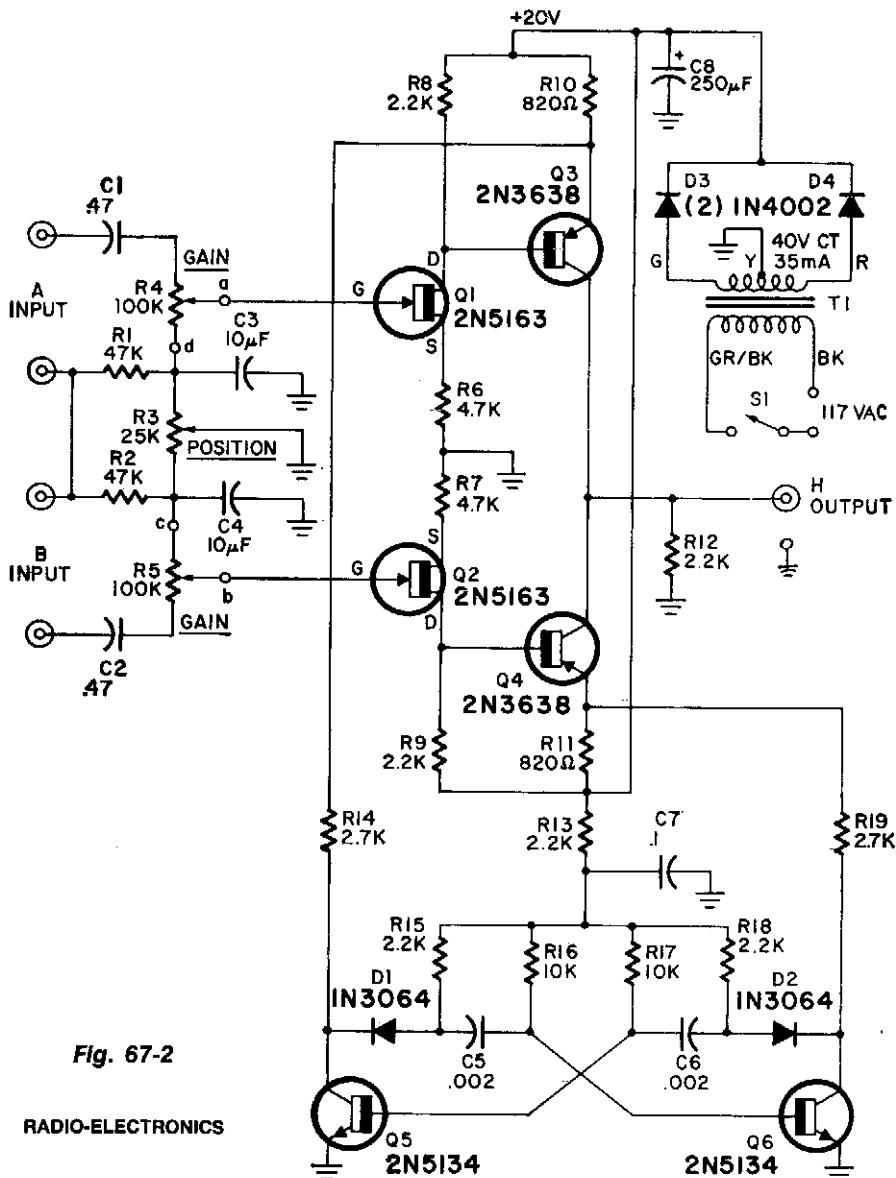


**Fig. 67-2**

RADIO-ELECTRONICS

#### Circuit Notes

The switcher output goes to the single vertical input of the scope, and a sync line from one of the inputs is taken to the scope's external-sync input. Frequency response of the input amplifiers is 300 kHz over the range of the gain controls. With the gain controls wide open so no attenuation of the signal takes place, the frequency response is up to 1 MHz.

## SCOPE CALIBRATOR

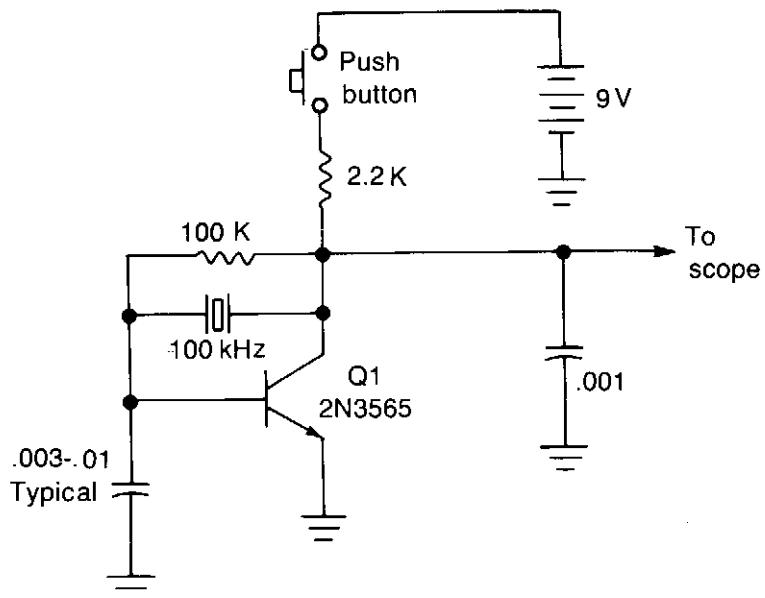

WILLIAM SHEETS

Fig. 67-3

### Circuit Notes

The calibrator operates on exactly 100 kHz providing a reference for calibrating the variable time base oscillator of general purpose scopes. For example, if the scope is set so that one cycle of the signal fills exactly 10 graticule divisions then each division represents 1 MHz, or 1 microsecond. If the scope is adjusted for 10 cycles on 10 graticule divisions. (1 cycle per division) then each division represents 100 kHz or 10 microseconds.

# **68**

## **Peak Detector Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Positive Peak Detector  
Peak Detector

## POSITIVE PEAK DETECTOR

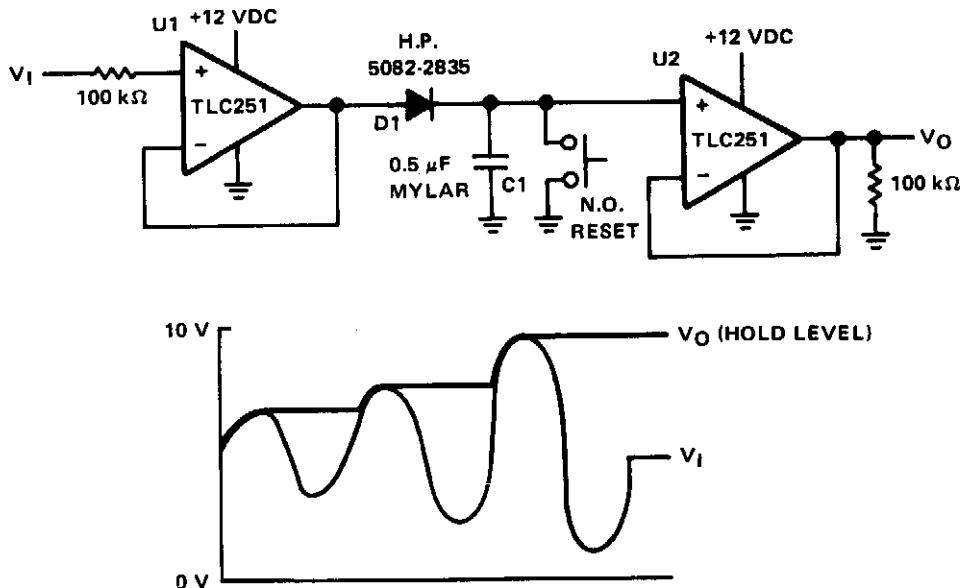


TEXAS INSTRUMENTS

**Fig. 68-1**

### Circuit Notes

The purpose of the circuit is to hold the peak of the input voltage on capacitor C1, and read the value,  $V_O$ , at the output of U2. Op amps U1 and U2 are connected as voltage followers. When a signal is applied to  $V_I$ , C1 will charge to this same voltage through diode D1. This positive peak voltage on C1 will maintain  $V_O$  at this level until the capacitor is reset (shorted). Of course, higher positive peaks will raise this level while lower power peaks will be ignored. C1 can be reset manually with a switch, or electronically with an FET that is normally off. The capacitor specified for C1 should have low leakage and low dielectric absorption. Diode D1 should also have low leakage. Peak values of negative polarity signals may be detected by reversing D1.

## PEAK DETECTOR

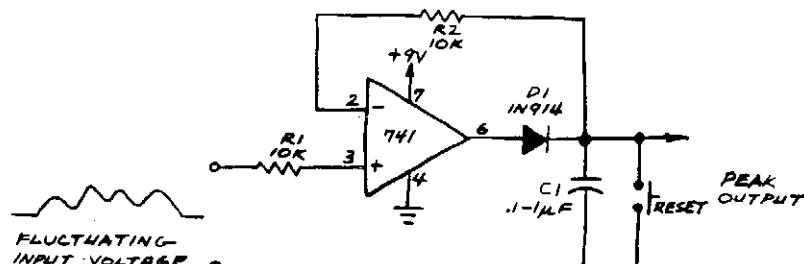

POPULAR ELECTRONICS

Fig. 68-2

### Circuit Notes

The comparator will charge C1 until the voltage across the capacitor equals the input voltage. If subsequent input voltage exceeds that stored in C1, the comparator voltage will go high and charge C1 to new higher peak voltage.

# **69**


## **Phase Sequence Circuits**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- RC Circuit Detects Phase Sequence Reversal
- Phase Indicator
- Phase Sequence Detector
- Three Phase Tester
- Phase Sequence Detector II
- Simple Phase Detector Circuit
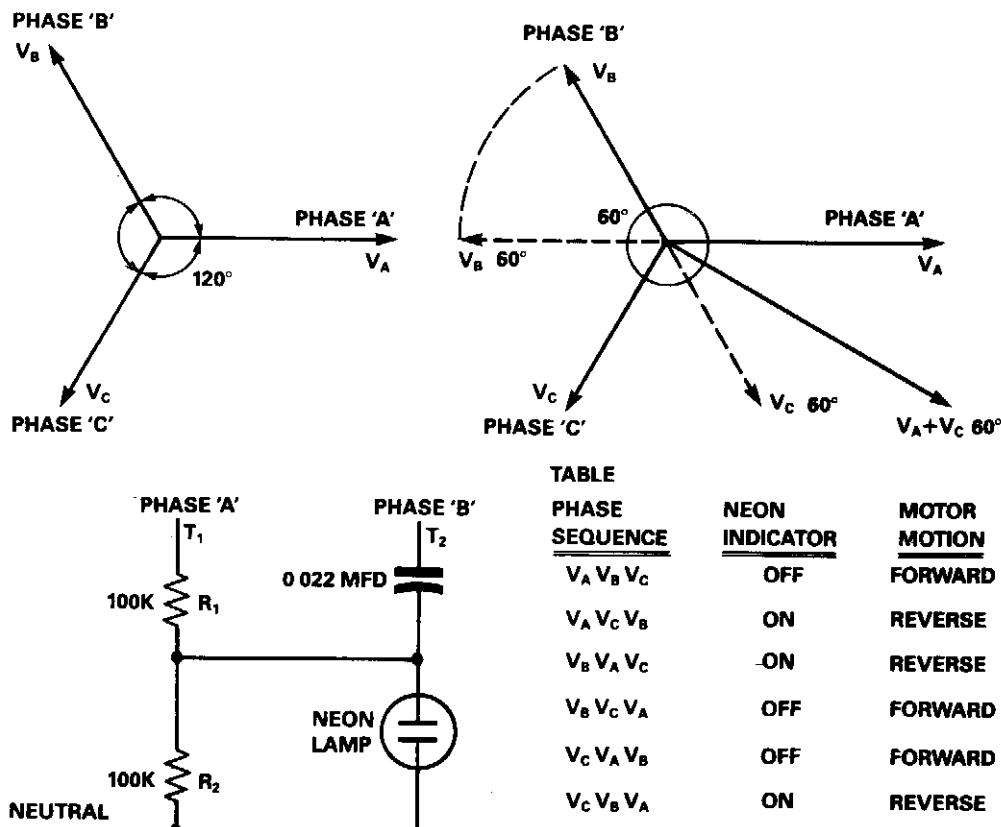
## RC CIRCUIT DETECTS PHASE SEQUENCE REVERSAL



ELECTRONIC ENGINEERING


Fig. 69-1

### Circuit Notes

Assume the correct phase sequence to be  $V_A - V_B - V_C$ . The circuit terminals are connected such that  $T_1$  gets connected to phase  $A$  and  $T_2$  to phase  $B$ . The capacitor advances the voltage developed across  $R_2$  due to phase " $B$ " by  $\sim 60^\circ$ , while the voltages developed across it by phase " $A$ " is in phase with  $V_A$  as shown in Fig. 69-1. The net voltage developed across  $R_2 \sim$  zero, the neon lamp is not energized, thereby signaling correct phase sequence. If terminal  $T_2$  gets connected to phase  $C$ , a large voltage,  $K(V_A + V_C \sim 60^\circ)$ , gets developed across  $R_2$ , energizing the neon indicator to signal reverse phase sequence.


The motor terminals can be connected to the three phases in six different combinations. A three-phase motor will run in the forward direction for three such combinations, while for the other three it will operate in the reverse direction. As shown in the table, the circuit detects all three reverse combinations. This circuit can be wired into any existing motor starter where the operator can see whether the phase sequence has been altered, before starting the machine.

## PHASE INDICATOR

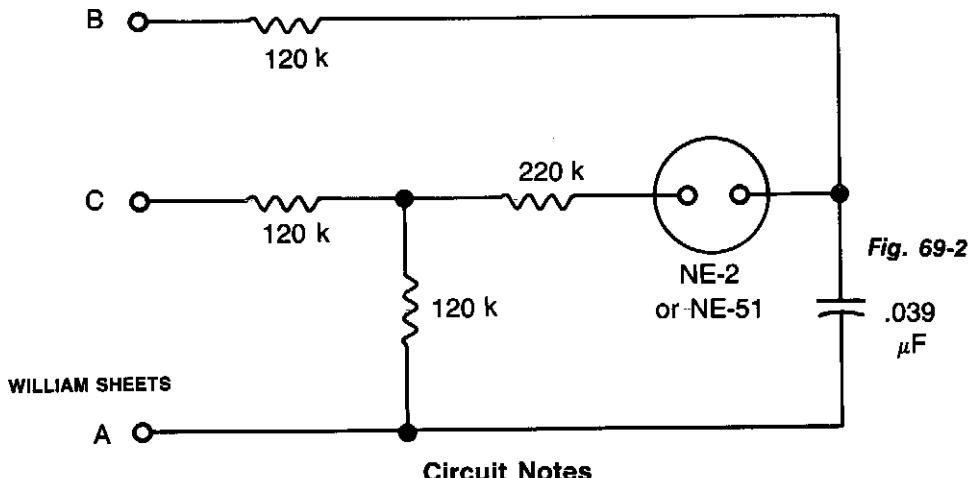

The circuit provides a simple means of determining the succession of phases of a 3-phase 120 V source used in synchro work. Terminals A, B, and C are connected to the three terminals of the source to be checked. If the neon bulb lights, interchange any two leads; the light then extinguishes and A, B, and C indicate the correct sequence. If power on any one line is lost, the neon bulb will light. This feature may be useful for monitoring purposes.




## PHASE SEQUENCE DETECTOR

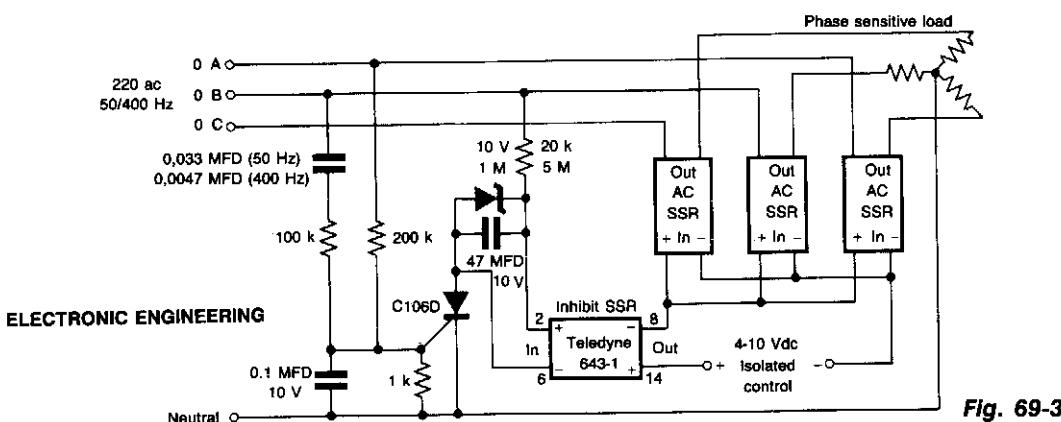

## Circuit Notes

This circuit prevents damage to the load due to incorrect phasing. The three power SSR's are only permitted to turn-on for a phase sequence of phase A leading phase B. If phase A lags phase B the input currents will cancel, causing the SCR and the inhibit SSR to remain off until the sequence is reversed. The inhibit SSR is included to maintain isolation at the input.

### THREE PHASE TESTER

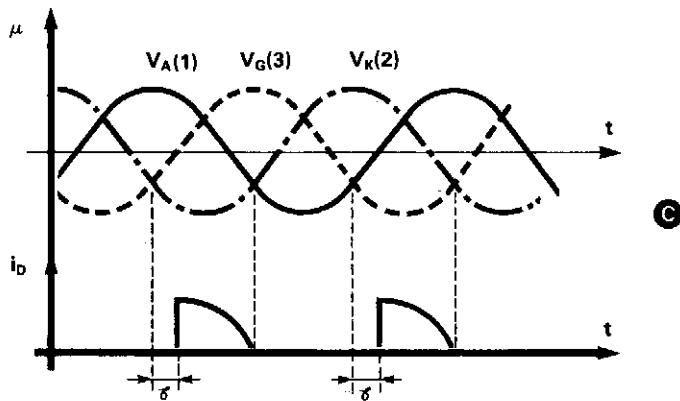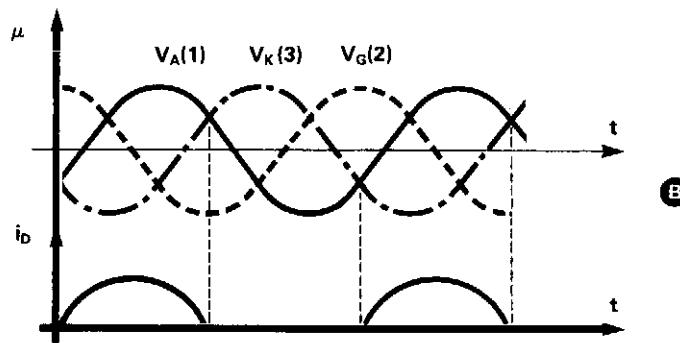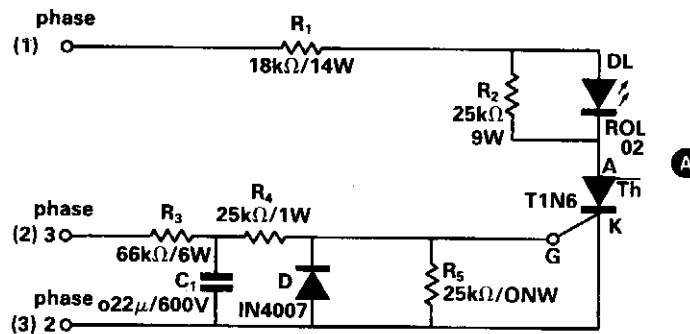

## THREE PHASE TESTER, Continued.

### Circuit Notes

This simple three-phase tester, uses only a small current thyristor as a main element for testing the right or wrong succession of the three phases, and there is no need for a supplementary power supply.


The basic circuit is shown in Fig. 69-4A. When connecting to the thyristor anode, grid, and cathode the three phases of the supply network in the sequence phase 1, phase 3, phase 2, are considered as correct, the mean value of the current through the thyristor is relatively high (since it is turned on during an entire half-period of one phase). The result is that the LED will emit a normal light.

The wave shapes for the three voltages and the current through the LED for this situation are shown in Fig. 69-4B.

If the three phases are not correctly connected—phase 1 to the anode, phase 2 to the grid, and phase 3 to the cathode, for instance—the thyristor will be turned on for a very short time and the LED will produce a very poor light. The wave shapes for this case are shown in Fig. 69-4C. The delay time is given by the R3-R1-R4 group.

When any of the three phases is missing, there is no current through the thyristor and the LED will emit no light.

## PHASE-SEQUENCE DETECTOR II

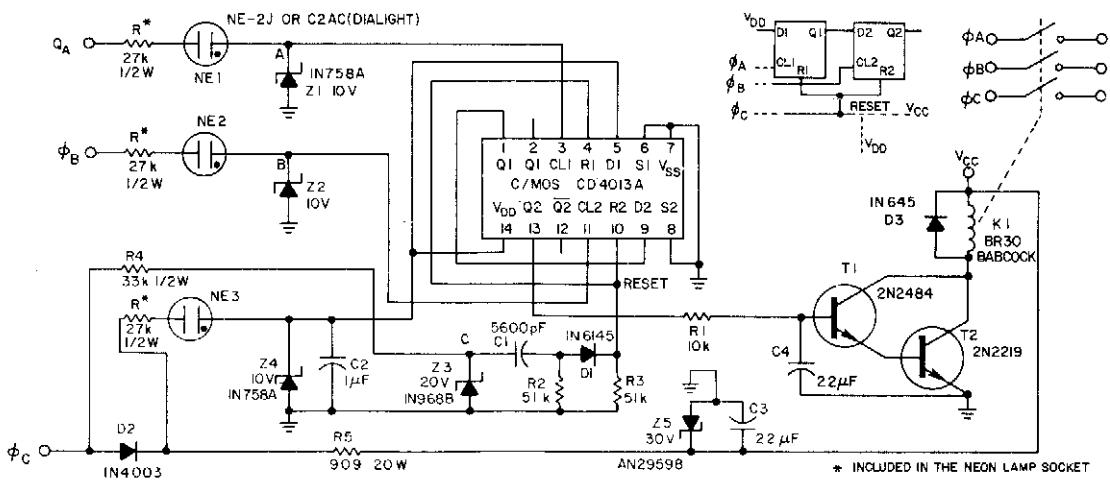

**Fig. 69-5**

### Circuit Notes

This circuit derives its supply voltage,  $V_{cc}$  and  $V_{dd}$  from  $\phi_c$ . This factor, together with the neon lamps and zener diodes in the phase inputs, establishes 50% threshold that detects low voltage or absence of one or more phases. Relay K1 energizes for correct phase volts.

### SIMPLE PHASE DETECTOR CIRCUIT

Fig. 1



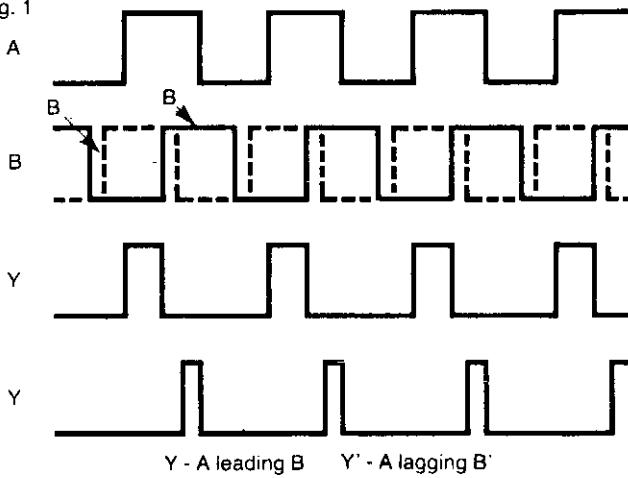


Fig. 2

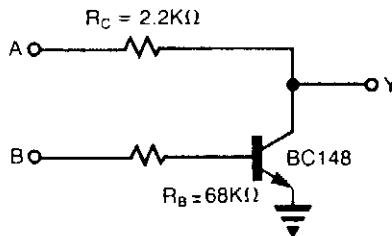

**Fig. 69-6**

Fig. 3

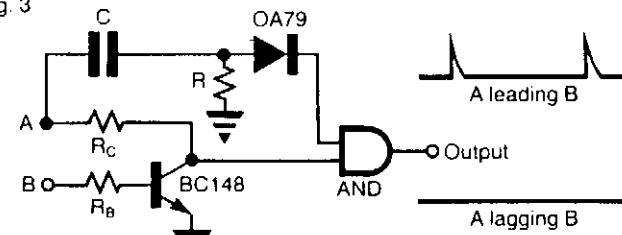

ELECTRONIC ENGINEERING

#### Circuit Notes

The operation of the circuit is like an enabled inverter, that is, the output  $Y=B$  provided  $A$  is high. If  $A$  is low, output is low (independent of the state of  $B$ ). When the signals  $A$  and  $B$  or  $B_1$  are connected to the inputs  $A$  and  $B$  of this gate the output  $Y$  is a pulse train signal (shown a  $Y$  or  $Y_1$ ) which has a pulse duration equal to the phase difference between the two signals. The circuit is directly suitable for phase difference measurement from zero to  $180^\circ$ . This performance is similar to the circuits like the Exclusive OR gate used for this purpose. With this method leading and lagging positions of the signals can also be found using an AND gate. Phase difference measured along with the leading and lagging information gives complete information about the phases of the two signals between zero and  $360^\circ$ .

# 70

## Photography-Related Circuits


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Auto-Advance Projector
- Shutter-Speed Tester
- Enlarger Timer
- Contrast Meter
- Electronic Flash Trigger
- Sound Trigger for Flash Unit

## AUTO-ADVANCE PROJECTOR

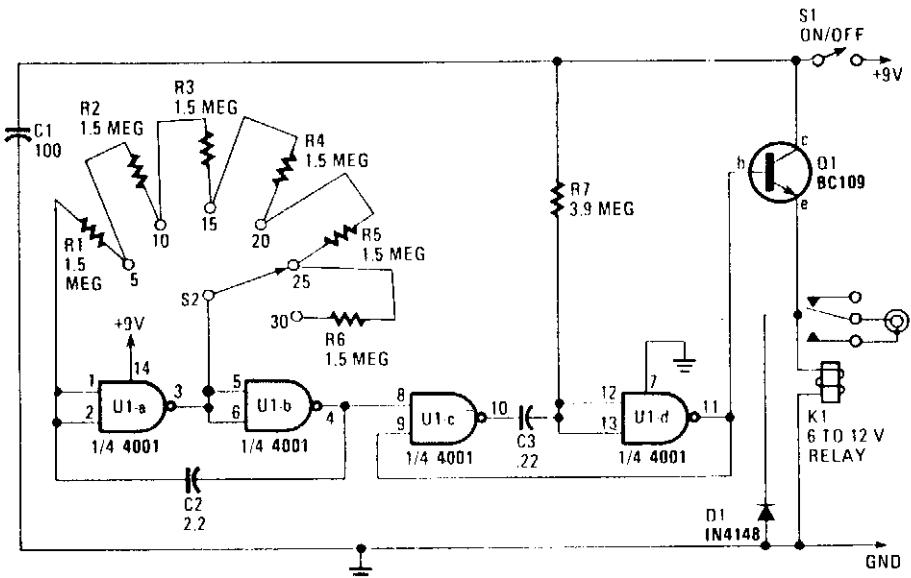


HANDS-ON ELECTRONICS

**Fig. 70-1**

### Circuit Notes

The circuit is built around a 4001 quad two-input NOR gate, it provides switch selectable auto-advance times of 5, 10, 15, 20, 25 or 30 seconds through the remote-control socket of your projector. U1a and U1b form an astable multivibrator, with its operating frequency dependent on the number of timing resistors switched into the circuit via S2. The frequency is about one cycle for every five seconds with a single timing resistor, one every ten seconds with two resistors, etc., providing six switched time intervals. The output of the astable at pin 4 of U1b is fed to the input of a monostable multivibrator, consisting of the second pair of gates, U1c and U1d. R7 and C3 are the timing components; they set the length of the (positive) output pulse of the monostable at a little more than half a second. The monostable is triggered by each positive-going input it receives from the astable. The output from the monostable therefore, consists of a series of short pulses, the interval between the pulses being controlled using S2. The output of the monostable (at pin 11) controls a relay by way of Q1, which is configured as an emitter-follower buffer stage. The projector is controlled via the normally-open contacts of relay K1. When the output of the monostable goes positive, the relay contacts close, triggering the slide-change mechanism of the projector. The monostable assures that the power to the relay is applied only briefly by the timer, so that multiple operation of the projector is avoided.

## SHUTTER-SPEED TESTER

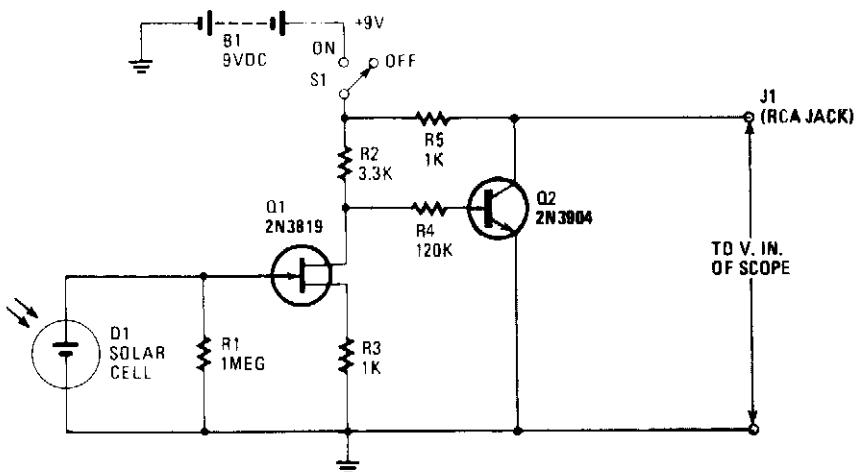


HANDS-ON ELECTRONICS

*Fig. 70-2*

### Circuit Notes

The solar cell is connected across the input of the FET (field-effect transistor), Q1, so that it will produce positive dc voltage to the gate when activated by light shining through the open shutter, decreasing the negative gate-source bias already established by the source resistor, and causes an increase in drain current. The drain voltage goes more negative which causes a decrease in Q2's base current. Q2's collector current decreases, and its collector voltage becomes more positive. There is an amplified positive-going voltage output at the collector, and it's applied directly to the oscilloscope's vertical input, producing a waveform that is displaced vertically whenever light strikes the cell.

## **ENLARGER TIMER**

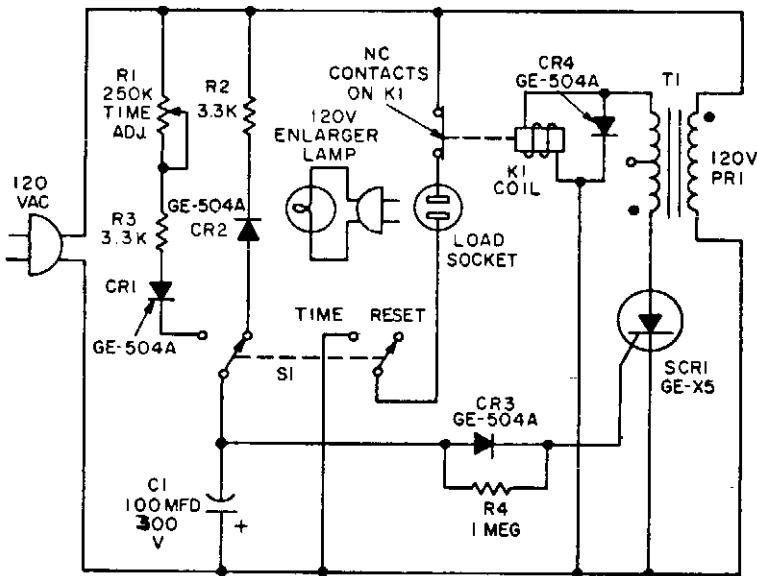

## Parts List

*C1 - 100-mfd, 300-volt electrolytic capacitor*

*CR1 thru CR4 - GE-504A  
rectifier diode*

K1—12-volt a-c relay (Potter & Brumfield No. MR5A, or equivalent)

*R1 = 250K-ohm, 2-watt  
potentiometer*

*R2, R3 - 3.3K-ohm, 1/2-watt  
resistor*

*R4 — 1-megohm, 1/2-watt resistor*

*S1 - DPDT toggle switch  
SCR1 - GE-X5 silicon controlled rectifier*

**T1 — Filament transformer:**  
primary, 120-volts a-c;  
secondary, 12.6-volts cen-  
tapped (Triad F25X, or  
equivalent)

*Line cord, vectorboard, minibox  
etc.*


**GENERAL ELECTRIC**

**Fig. 70-3**

**Circuit Notes**

This precision, solid state, time delay circuit has delayed *off* and delayed *on* switching functions that are interchangeably available by simply interchanging the relay contacts.

## CONTRAST METER

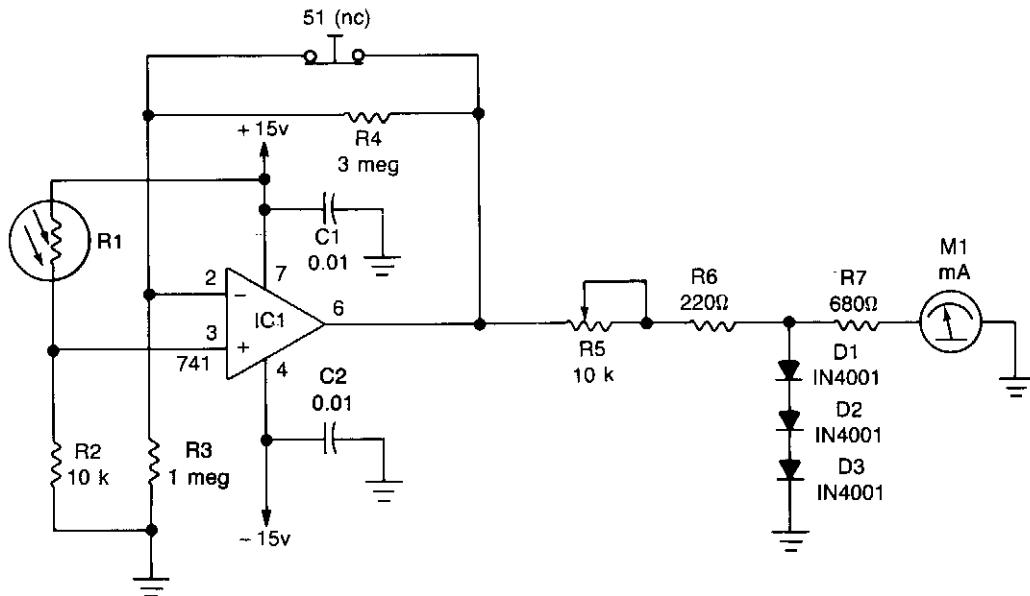


RADIO ELECTRONICS

**Fig. 70-4**

### Circuit Notes


One leg of the photocell (R1) is tied to the +15 volt supply and the other end is connected to ground through resistor R2, forming a voltage-divider network. The non-inverting input of the 741 op amp, IC1, is tied to the junction formed by R1 and R2, while its inverting input is grounded through resistor R3. When switch S1 is pressed, another divider network is formed, reducing the voltage applied to the inverting input of the op amp. When light hits the photocell its resistance begins to decrease causing a greater voltage drop across R2 and a higher voltage to be presented to the non-inverting input of IC1. This causes IC1 to output a voltage proportional to the two inputs. The circuit gives a meter reading that depends on the intensity of light hitting photocell R1; therefore, R1 should be mounted in a bottle cap so that the light must pass through a 3/16 inch hole. Potentiometer R5 is used to adjust the circuit for the negative you're working with.

### ELECTRONIC FLASH TRIGGER

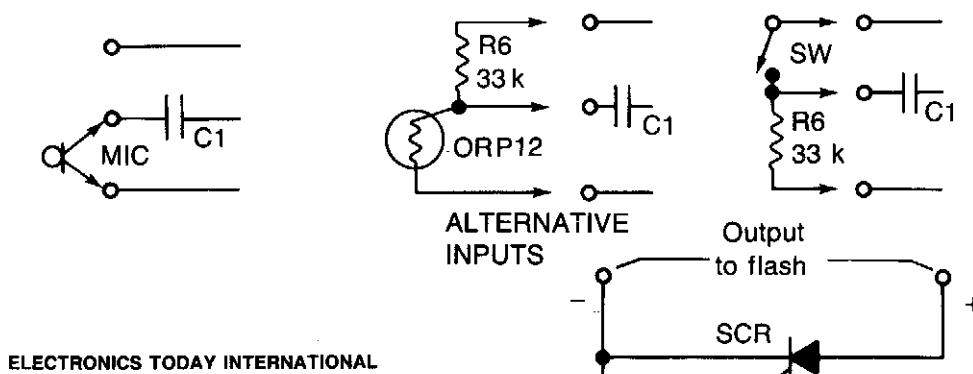

ELECTRONICS TODAY INTERNATIONAL


Fig. 70-5

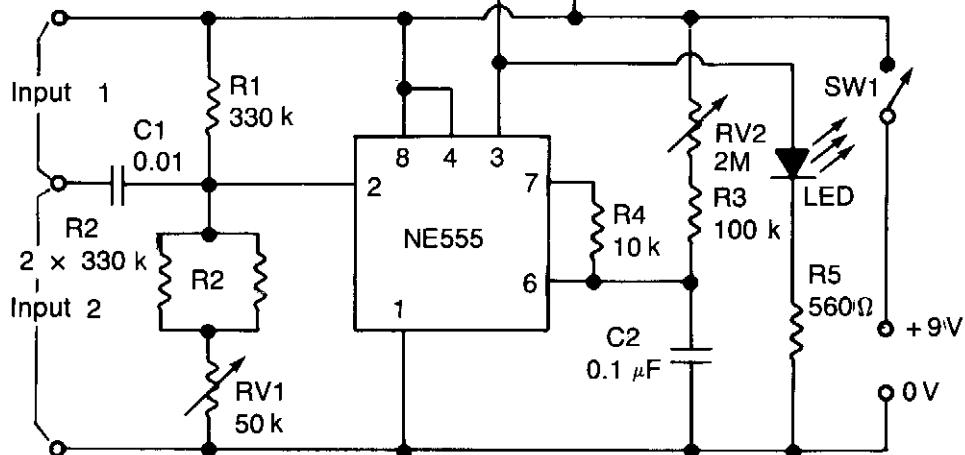

#### Circuit Notes

A negative pulse at the input is fed via capacitor C1 to the input pin (2) of the IC. Pin 2 is held slightly above its triggering voltage of  $1/3 V_{cc}$  by the voltage divider comprising R1, R2 and RV1. The negative pulse triggers the IC and the output (pin 3) goes high for a time period controlled by RV2, R3 and C2. When the output goes low again at the end of the time interval, capacitor C3 charges through the gate cathode circuit of the SCR switching it on and firing the flash. Capacitor C1 isolates the input from the voltage divider so that the unit isn't sensitive to the dc level at the input. RV1 acts as a sensitivity control by allowing the voltage to be adjusted to a suitable level so that the input signal will trigger the IC. Resistor R4 limits the discharge current from C2 at the end of the timing cycle protecting the IC. The LED and its protective resistor R5 act as an indicator to show that the unit has triggered, simplifying the setting up process and minimizing the number of times the strobe has to be fired. This means that the strobe needn't be fired until a photo is to be taken.

## SOUND TRIGGER FOR FLASH UNIT

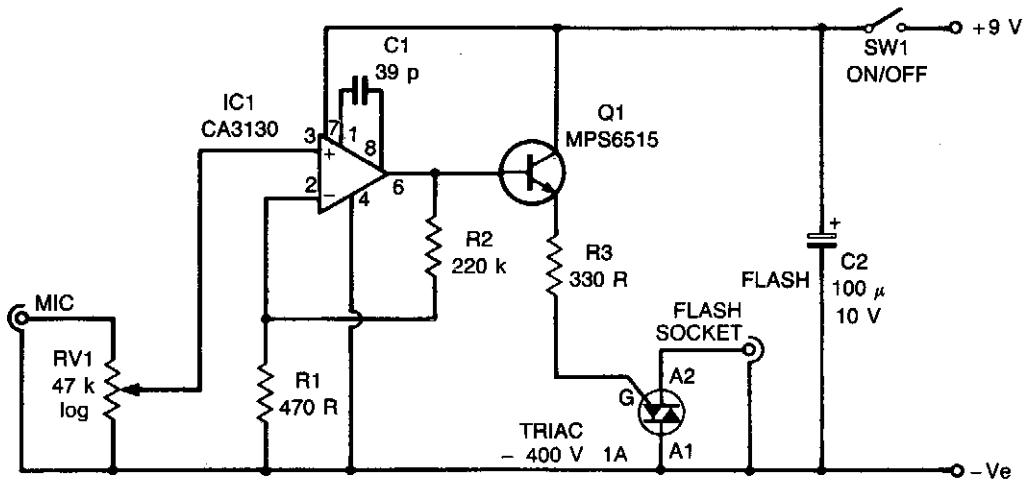

ELECTRONICS TODAY INTERNATIONAL

**Fig. 70-6**

### Circuit Notes

The circuit is based on operational amplifier IC1 used in the noninverting amplifier mode. R1 and 2 set the gain at about 500. RV1 (sensitivity) biases the noninverting input to the negative supply. Q1 provides the relatively high trigger current required by the triac. When a signal is received by the microphone, the signals are amplified (by IC1). The triac is triggered and a low resistance appears across its A1 and A2 terminals which are connected via the flashlead to the strobe. The circuit operates almost instantly, giving very little delay between the commencement of the sound and the flashgun being triggered.

# 71

## Power Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

2 To 6 W Audio Amplifier with Preamplifier

Audio Power Amplifier

25 Watt Amplifier

Bull Horn

Low Power Audio Amplifier

Audio Booster


Walkman Amplifier

Rear Speaker Ambience (4-Channel) Amplifier

90 W Audio Power Amplifier with Safe Area Protection


Power Amplifier
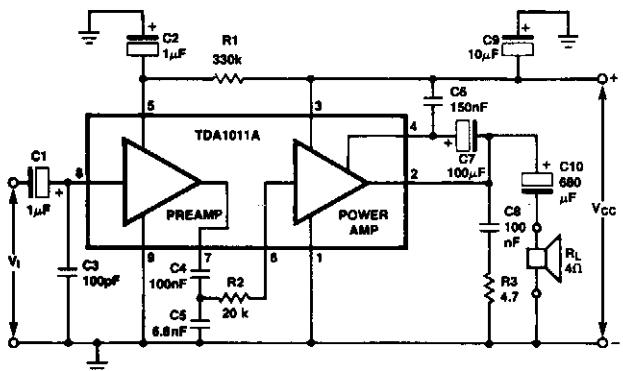
## 2 TO 6 W AUDIO AMPLIFIER WITH PREAMPLIFIER



SIGNETICS

Fig. 71-1

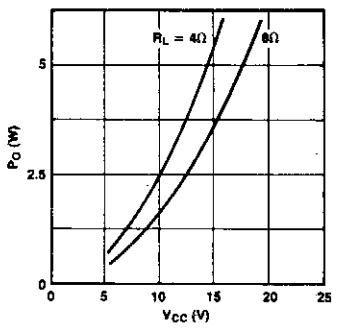


NOTES:  
 $d_{TOT} = 10\%$ ; typical values. The available output power is 5% higher when measured at Pin 2 (due to series resistance of C1). \*

Output Power Across  $R_L$   
as a Function of Supply  
Voltage with Bootstrap

### Circuit Notes

The monolithic integrated audio amplifier circuit is especially designed for portable radio and recorder applications and delivers up to 4 W in a 4 ohm load impedance.

## AUDIO POWER AMPLIFIER

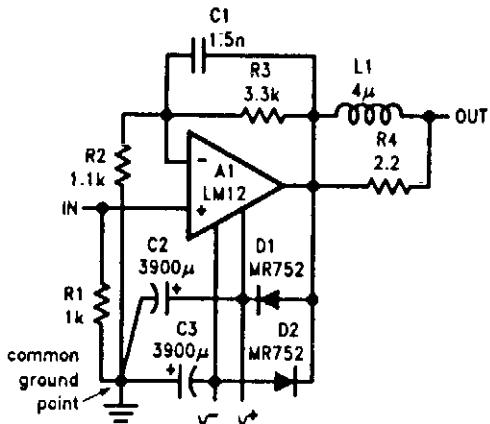


NATIONAL SEMICONDUCTOR CORP.

Fig. 71-2

### Circuit Notes

Output-clamp diodes are mandatory because loudspeakers are inductive loads. Output LR isolation is also used because audio amplifiers are usually expected to handle up to 2  $\mu$ F load capacitance. Large, supply-bypass capacitors located close to the IC are used so that the rectified load current in the supply leads does not get back into the amplifier, increasing high-frequency distortion. Single-point grounding for all internal leads plus the signal source and load is recommended to avoid ground loops that can increase distortion.

## 25 WATT AMPLIFIER

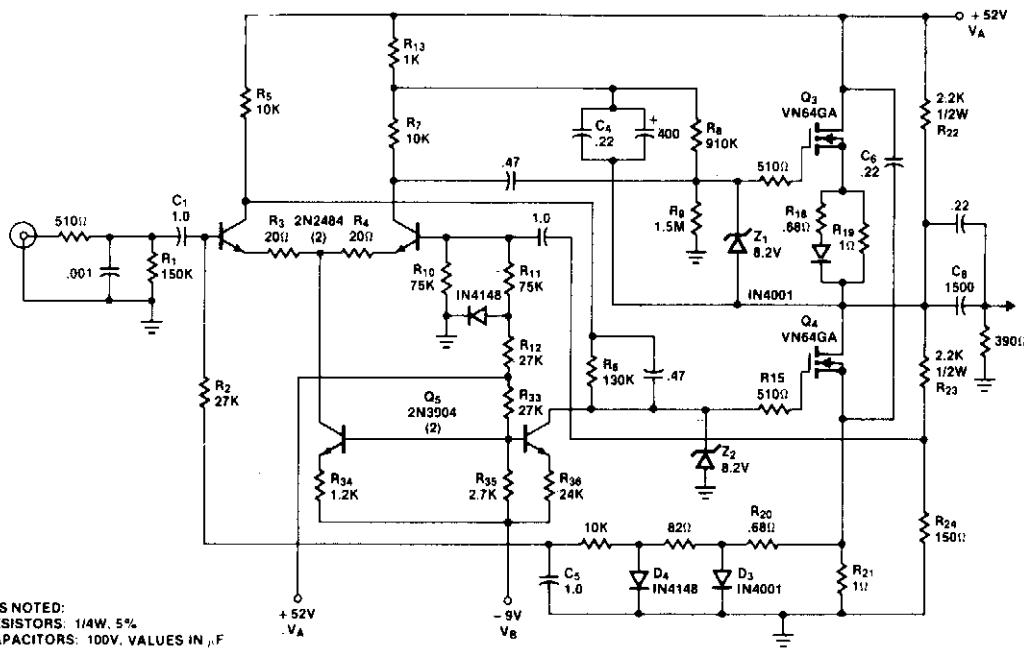


SILICONIX, INC.

**Fig. 71-3**

### Circuit Notes

Transistors are used for current sources. Base drive for these transistors is derived from the main power supply  $V_A$ , so that their collector current is proportional to the rail voltage. This feature holds the voltage on the diff-amp collectors close to  $V_A/2$ . The sensitivity of  $I_Q$  to  $V_A$  is about 3.4 mA/volt when  $V_B$  is held constant; the sensitivity of  $I_Q$  to  $V_B$  is  $-15$  mA/volt when  $V_A$  is held constant. In a practical amplifier with a non-regulated supply, variations in power output will cause fluctuations in  $V_A$ , but will not affect  $V_B$ ; therefore, having  $I_Q$  increase slightly with power output will tend to compensate for the 3.4 mA/volt  $I_Q V_A$  sensitivity. In the case of line voltage variations, since  $V_A$  is about five times  $V_B$ , the sensitivities tend to cancel, leaving a net sensitivity of about 2 mA/volt.

## BULL HORN

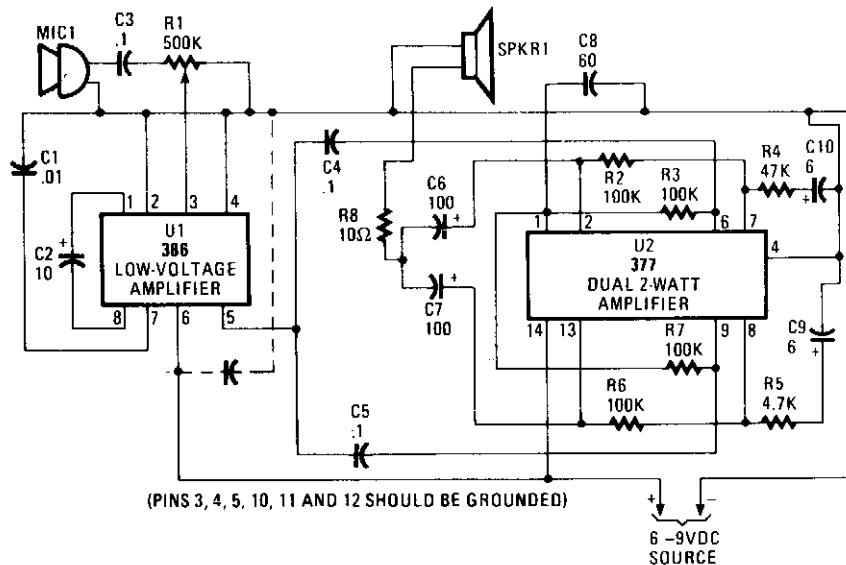


HANDS-ON ELECTRONICS

**Fig. 71-4**

### Circuit Notes

The input audio signal is fed to pin 3 of U1, an LM386 low-voltage amplifier, via C3 and R1. Potentiometer R1 sets the drive or volume level. U1, which serves as a driver stage, can be set for a gain of from 20 to 200. The output of U1 at pin 5 is fed to U2—a 377 dual two-watt amplifier connected in parallel to produce about four watts of output power—at pins 6 and 9 via C4 and C5. Frequency stability is determined by R2, R4, and C10 on one side, and the corresponding components R6, R5, and C9 on the other side. The outputs of the two amplifiers (at pins 2 and 13) are capacitively coupled to SPKR1 through C6 and C7.

## LOW POWER AUDIO AMPLIFIER

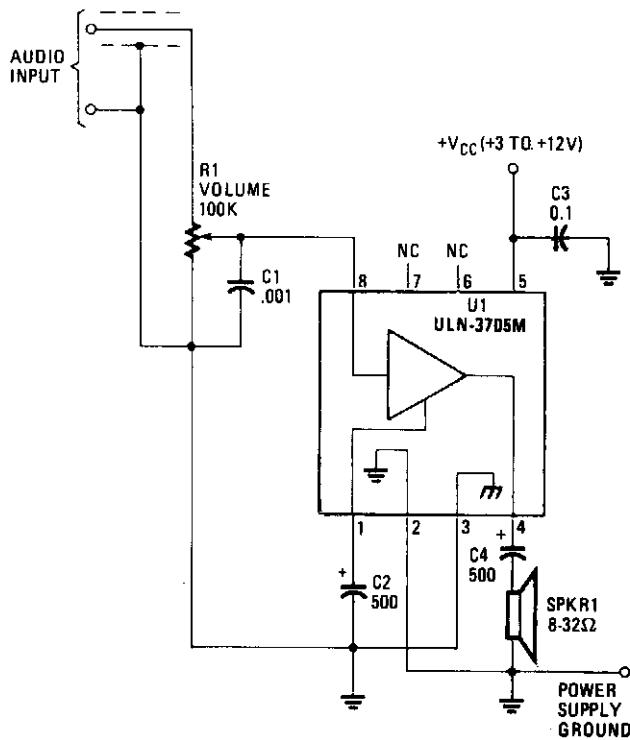


HANDS-ON ELECTRONICS

*Fig. 71-5*

### Circuit Notes

The amplifier operates from supplies ranging up to 12 volts, and operates (with reduced volume) from supply voltages as low as 1.8 volts without having distortion rise to unacceptable levels. (Its power requirements make it suitable for solar-cell application.) Components external to the integrated circuit, U1, consist of four capacitors and a potentiometer for volume control. Capacitor C3 is for decoupling, low-frequency roll-off, and power-supply ripple rejection. Capacitor C4 is an electrolytic type that couples the audio output to an 8 to 32 ohm speaker that is efficient.

## AUDIO BOOSTER

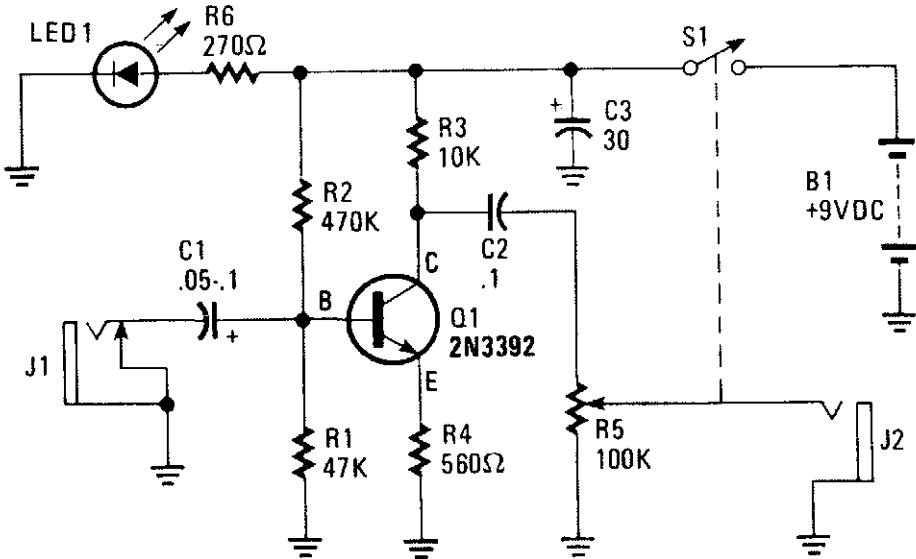


HANDS-ON ELECTRONICS

Fig. 71-6

### Circuit Notes

The amplifier's gain is nominally 20 dB. Its frequency response is determined primarily by the value of just a few components—primarily C1 and R1. The values of the schematic diagram provide a response of  $\pm 3.0$  dB from about 120 Hz to better than 20,000 Hz. Actually, the frequency response is ruler flat from about 170 Hz to well over 20,000 Hz; it's the low end that deviates from a flat frequency response. The low end's roll-off is primarily a function of capacitor C1 (since R1's resistive value is fixed). If C1's value is changed to  $0.1 \mu\text{F}$ , the low end's corner frequency—the frequency at which the low-end roll-off starts—is reduced to about 70 Hz. If you need an even deeper low-end roll-off, change C1 to a  $1.0 \mu\text{F}$  capacitor; if it's an electrolytic type, make certain that it's installed into the circuit with the correct polarity, with the positive terminal connected to Q1's base terminal.

## WALKMAN AMPLIFIER

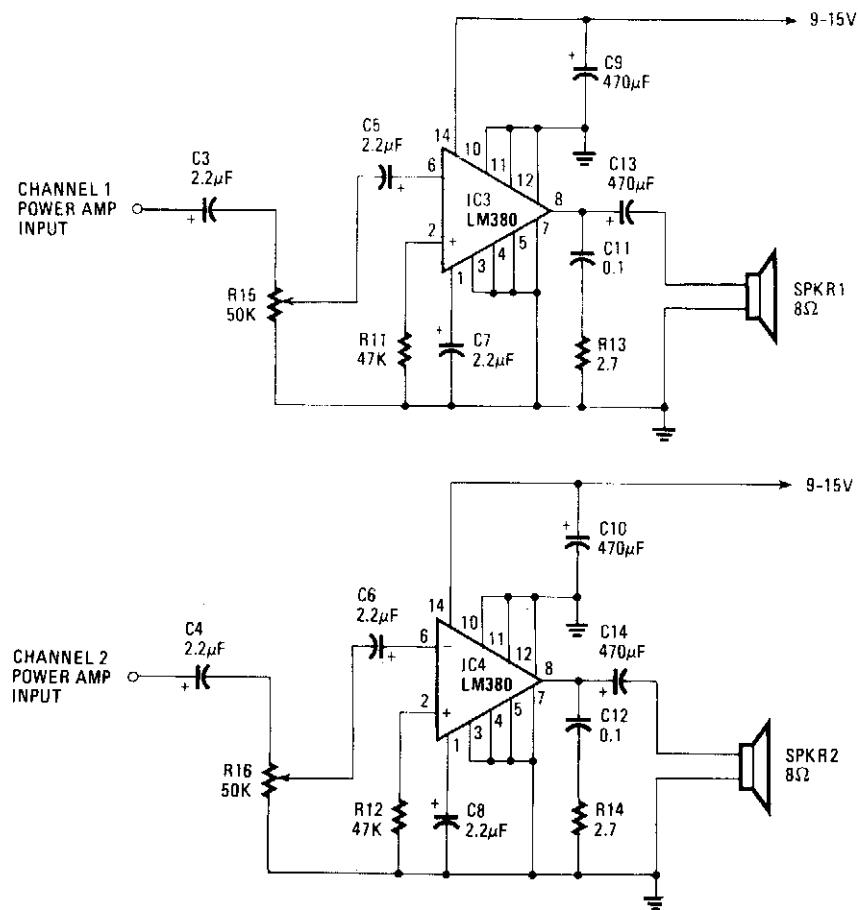


RADIO-ELECTRONICS

**Fig. 71-7**

### Circuit Notes

The gain of the low-cost IC is internally fixed so that it is not less than 34 dB (50 times). A unique input stage allows input signals to be referenced to ground. The output is automatically self centering to one half the supply voltage. The output is also short-circuit proof with internal thermal limiting. With a maximum supply of 15 volts and an 8 ohm load, the output is around 1.5 watts per channel. The input stage is usable with signals from 50 mV to 500 mV rms. If the amplifier is to be used with a source other


## WALKMAN AMPLIFIER, Continued.

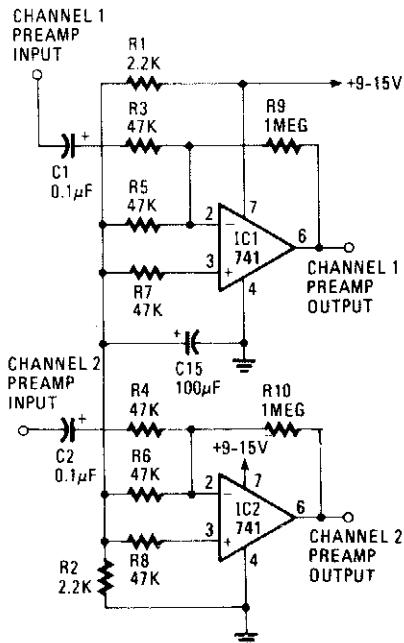

**-THE PREAMP.** If you wish to amplify low-level signals, such as the output of a turntable, the signal will first have to be fed to the preamp shown here.

than a personal stereo, such as a phonograph or an electric guitar, some type of preamplifier is required. A suitable circuit is shown. In that circuit, two 741 op amps have been configured as input amplifiers. Their input stages referenced to a common point—half the supply voltage. That voltage is derived from a voltage divider made up of R1 and R2, two 2.2 k resistors. The gain of each of the 741's has been fixed at 21 by the input resistors (R9, R10). Input capacitors, C1 and C2, are used to filter out any dc component from the input signal.
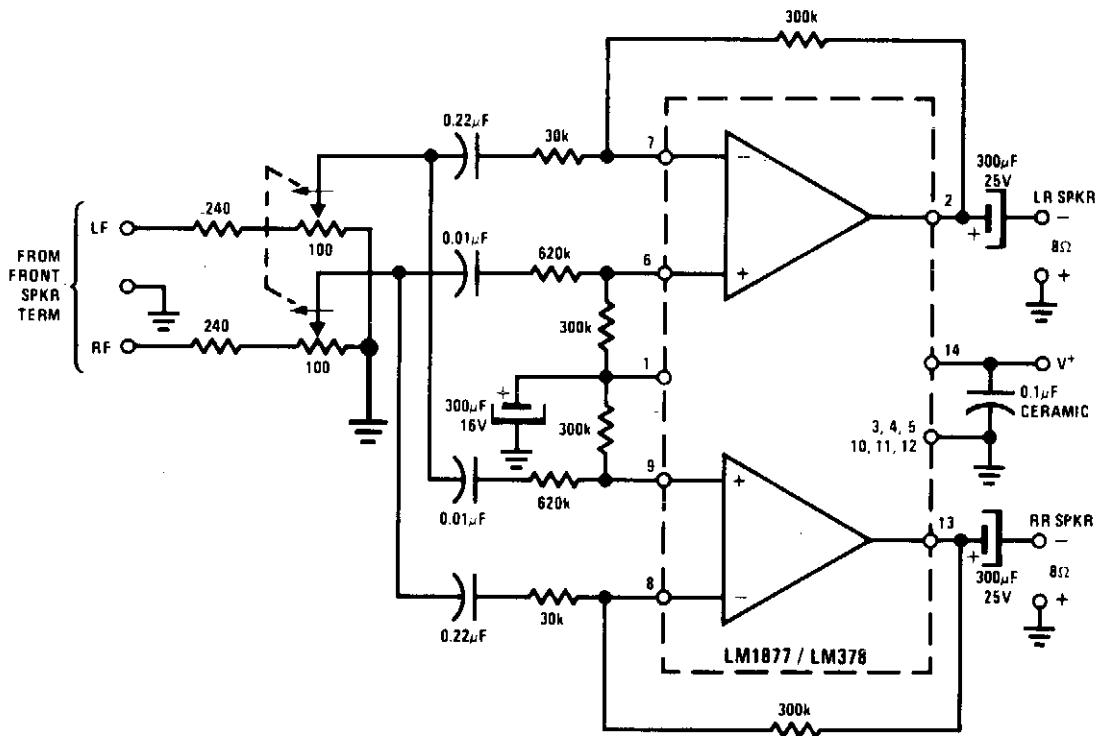
## REAR SPEAKER AMBIENCE (4-CHANNEL) AMPLIFIER




NATIONAL SEMICONDUCTOR CORP.

**Fig. 71-8**

### Circuit Notes

Rear channel "ambience" can be added to an existing stereo system to extract a difference signal ( $R - L$  or  $L - R$ ) which, when combined with some direct signal ( $R$  or  $L$ ), adds fullness, or "concert hall realism" to the reproduction of recorded music. Very little power is required at the rear channels, hence an LM1877 suffices for most "ambience" applications. The inputs are merely connected to the existing speaker output terminals of a stereo set, and two more speakers are connected to the ambience circuit outputs. The rear speakers should be connected in the opposite phase to those of the front speakers, as indicated by the  $+/-$  signs.

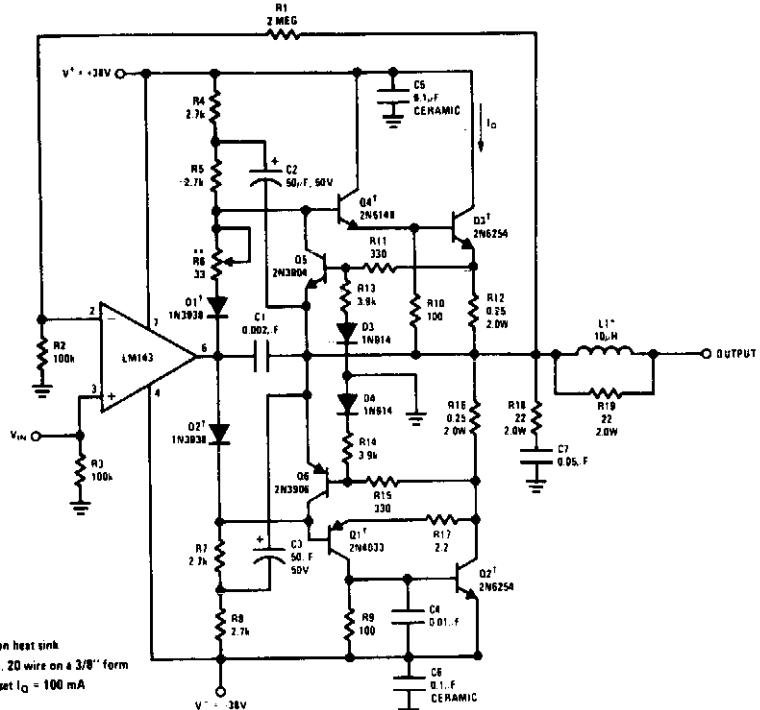
## 90 W AUDIO POWER AMPLIFIER WITH SAFE AREA PROTECTION



NATIONAL SEMICONDUCTOR

**Fig. 71-9**

## POWER AMPLIFIER

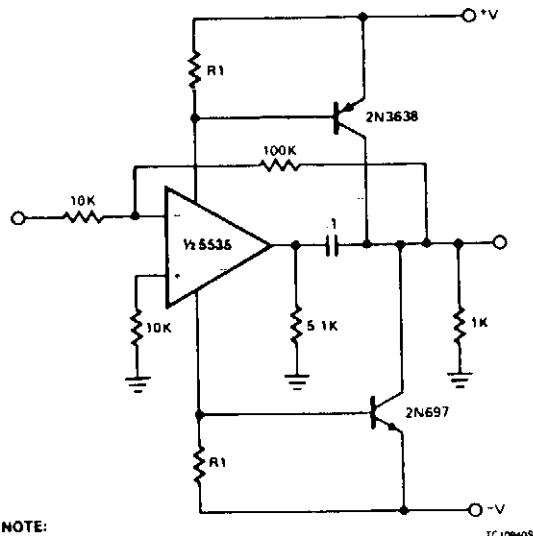

SIGNETICS

**Fig. 71-10**

### Circuit Notes

For most applications, the available power from op amps is sufficient. There are times when more power handling capability is necessary. A simple power booster capable of driving moderate loads uses an NE5535 device. Other amplifiers may be substituted only if  $R_1$  values are changed because of the  $I_{CC}$  current required by the amplifier.  $R_1$  should be calculated from the expression

$$R_1 = \frac{600 \text{ mV}}{I_{CC}}$$

# 72

## Power Supply Circuits

---


The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- 8 Amp Regulated Power Supply for Operating Mobile Equipment
- Uninterruptible Power Supply for Personal Computers
- 5 V Supply Including Stabilized Momentary Backup Power-Switching Circuit
- Radiation-Hardened, 125 A Linear Regulator Switch Mode Power Supply
- Micropower Bandgap Reference Supply
- Variable Current Source, 100 mA to 2 Amp
- Basic Single-Supply Voltage Regulator
- Bench Top Power Supply
- 400-Volt, 60-Watt Push-Pull Power Supply
- 500 kHz Switching Inverter for 12 V Systems
- 10-Amp Regulator with Current and Thermal

### Protection

- Bipolar Power Supply for Battery Instruments
- Power Supply for 25-Watt Arc Lamp
- Stand-by Power for Non-Volatile CMOS RAMs
- HV Regulator with Foldback Current Limiting
- 90 V rms Voltage Regulator Using a PUT
- 12-14 V Regulated 3 A Power Supply
- DC-to-DC SMPS Variable 18 V to 30 V out at 0.2 A
- Off-Line Flyback Regulator
- SCR Preregulator Fits Any Power Supply
- Voltage Regulator
- Zener Diode Increase Fixed PNP Regulator's Output Voltage Ratings
- Increasing the Power Rating of Zener Diodes
- Memory Save on Power-Down
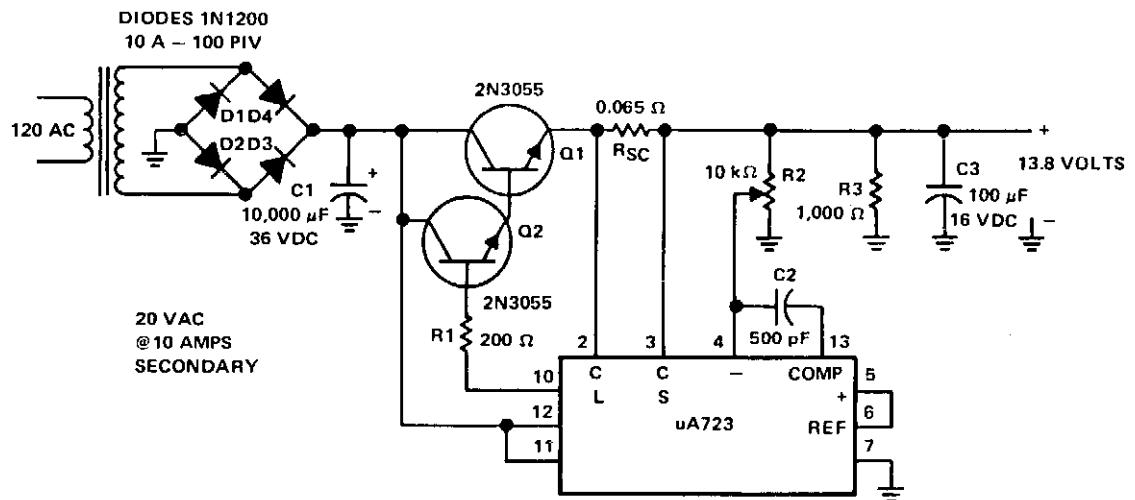
## 8-AMP REGULATED POWER SUPPLY FOR OPERATING MOBILE EQUIPMENT



TEXAS INSTRUMENTS


Fig. 72-1

### Circuit Notes

This supply is powered by a transformer operating from 120 Vac on the primary and providing approximately 20 Vac on the primary, and providing approximately 20 Vac on the secondary. Four 10-A diodes with a 100 PIV rating are used in a full-wave bridge rectifier. A 10,000  $\mu$ F/36 Vdc capacitor completes the filtering, providing 28 Vdc. The dc voltage is fed to the collectors of the Darlington connected 2N3055's. Base drive for the pass transistors is from pin 10 of the  $\mu$ A723 through a 200 ohm current limiting resistor, R1. The reference terminal (pin 6) is tied directly to the non-inverting input of the error amplifier (pin 5), providing 7.15 V for comparison.

The inverting input to the error amplifier (pin 4) is fed from the center arm of a 10 k ohm potentiometer connected across the output of the supply. This control is set for the desired output voltage of 13.8 V. Compensation of the error amplifier is accomplished with a 500 pF capacitor connected from pin 13 to pin 4. If the power supply should exceed 8 A or develop a short circuit, the  $\mu$ A723 regulator will bias the transistors to cutoff and the output voltage will drop to near zero until the short circuit condition is corrected.
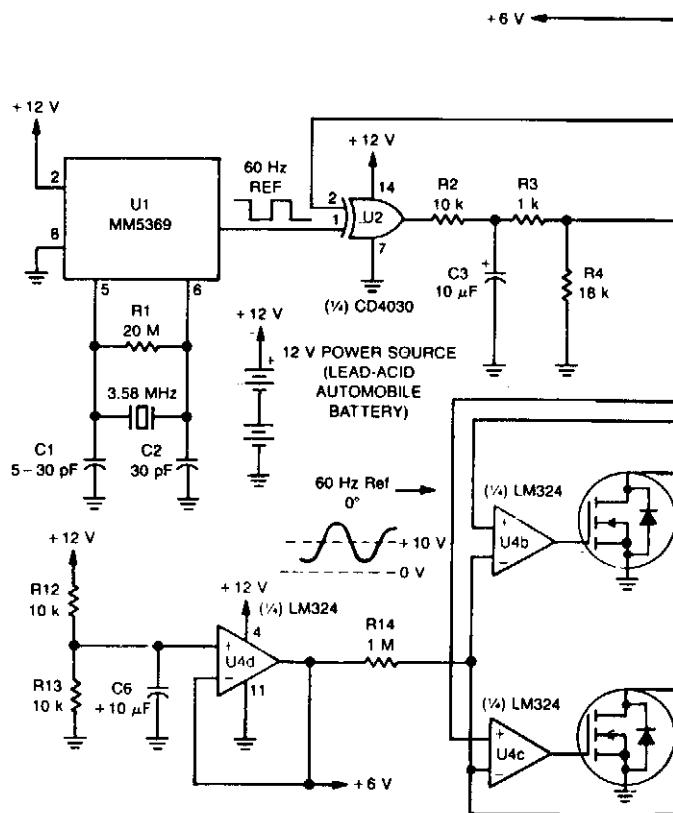
## UNINTERRUPTIBLE POWER SUPPLY FOR PERSONAL COMPUTERS





MOTOROLA

**Fig. 72-2**
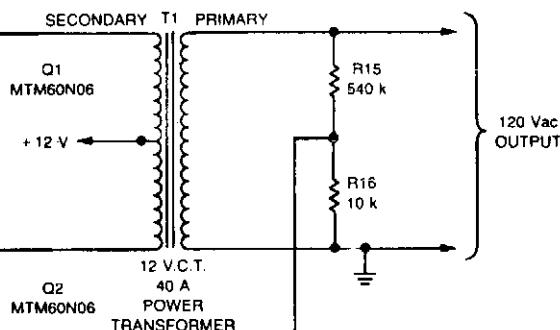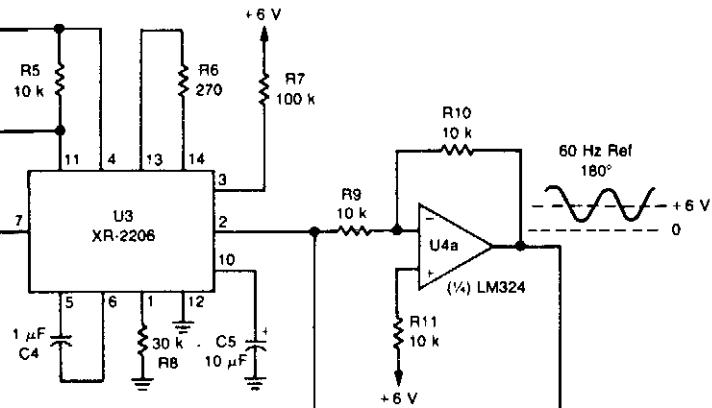
### Circuit Notes



The UPS is basically an ac inverter that is powered by a 12-V, lead-acid automobile battery. During power outages, it can supply several minutes of power for an average personal computer. It incorporates a crystal-controlled 60 Hz time base, so that a computer with a real time clock can maintain its accuracy. It isolates the ac line from the computer, so it can be used to operate sensitive electronic equipment on noisy power sources.

Two MTM60N06 Power FETs (Q1 and Q2) alternately switch current through a center-tapped 120-V to 12-V filament transformer (T1) with its primary and secondary reversed. The 120-V output is compared with a 60 Hz reference in a closed-loop configuration that maintains a constant output at optimum efficiency.



A 60 Hz reference frequency is derived from a crystal oscillator and divider circuit, U1. An inexpensive 3.58 MHz color burst crystal provides the time base that can be accurately adjusted by C1. The 60 Hz output from U1 is applied to the exclusive-OR gate, U2, and then to the XR-2206 function generator (U3) that converts the square wave into a sine wave. U2 and U3 form a phase-locked loop that synchronizes the sine wave output of U3 with the 60 Hz square wave reference of U1. The sine wave is then inverted by op amp U4a, so that two signals 180° out of phase can be applied to U4b and U4c that drive Q1 and Q2. Due to the closed-loop configuration of the drive circuits, Q1 and Q2 conduct only during the upper half of the sine wave. Therefore, one TMOS device conducts during the first half of the sine wave and the other conducts during the second half.
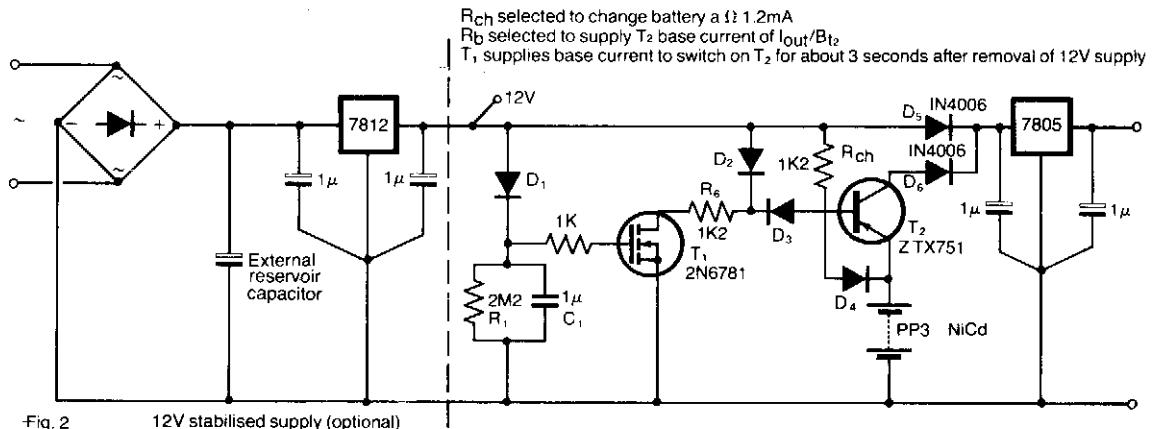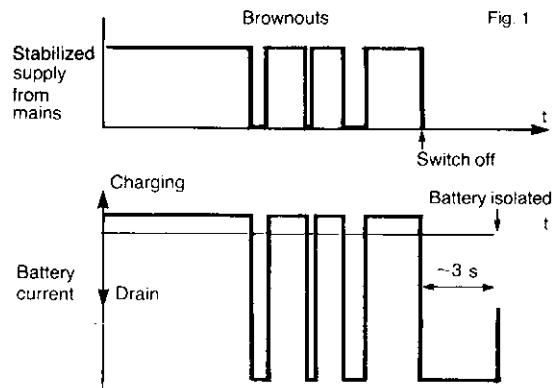
## 5 V SUPPLY INCLUDING STABILIZED MOMENTARY BACKUP



ELECTRONIC ENGINEERING

Fig. 72-3


## **5 V SUPPLY INCLUDING STABILIZED MOMENTARY BACKUP , Continued.**

### **Circuit Notes**

This circuit protects microprocessor systems from "brownouts" without the expense of an uninterruptible power supply. Designed around a small 9-V nickel cadmium battery the circuit continues to provide a constant 5-V output during brownouts of up to a few seconds. Load currents of up to 500 mA may be drawn using the components shown. With this mains-derived supply present, D5 is forward biased so that the stabilized supply powers the 5-V regulator and hence the circuitry to be protected. FET T<sub>1</sub> is held on by D1, its drain current being provided from the dc supply via R<sub>b</sub> and D2. Diode D3 is reverse-biased so that T2 is off, and the battery is isolated from D6. R<sub>CH</sub> and D4 serve to trickle charge the battery with approximately 1.2 mA.

When the 12-V supply is removed, R1 and C1 initially keep T1 switched on. D3 is now forward biased, so that T1 drain current is drawn via R<sub>b</sub>, D3 and T2 from the battery. This switches T2 on, allowing the load circuitry to draw current from the battery via D6 and the 5-V regulator. After a few seconds C1 has discharged (via R1) such that V<sub>gs</sub> falls below the threshold value for the FET, and T1 switches off. There is then no path for T2 base current, so that it also switches off, isolating the battery.

## POWER-SWITCHING CIRCUIT

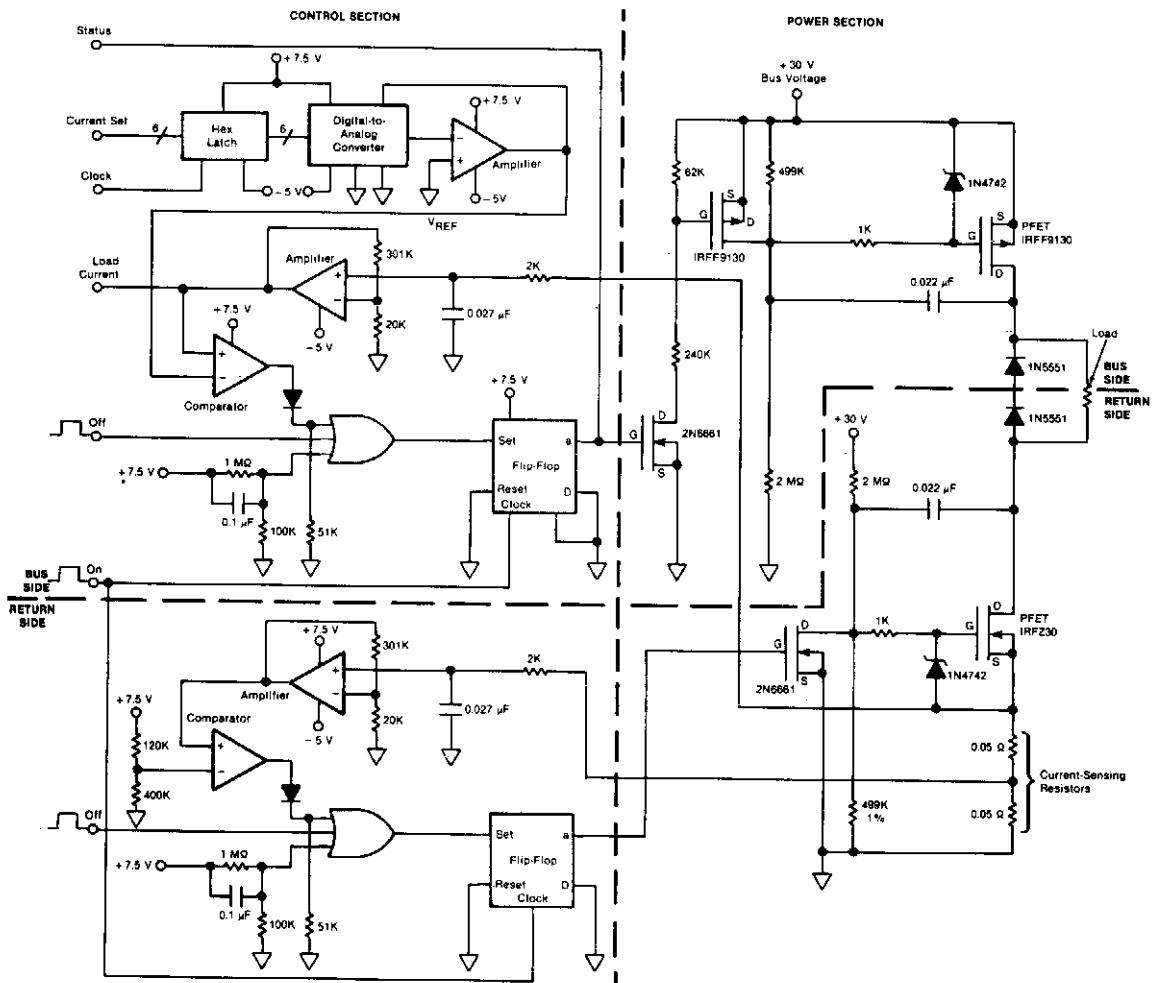

NASA


Fig. 72-4

## **POWER-SWITCHING CIRCUIT, Continued.**

### **Circuit Notes**

This circuit provides on/off switching, soft starting, current monitoring, current tripping, and protection against overcurrent for a 30 Vdc power supply at normal load currents up to 2 A. The switch is turned on by an "on" command pulse; it is turned off by an "off" command pulse. An overcurrent trip can also be set on the bus side by a 6-digit binary signal, which is converted to an analog voltage and compared with the amplified voltage developed across a load-current-sensing resistor. Resistor/capacitor combinations ( $0.027 \mu\text{F}$ ,  $2 \text{k}\Omega$ ) at the inputs of the current-sensing amplifiers act as low-pass filters: this introduces a few hundred  $\mu\text{s}$  of delay in the response to overcurrent, thereby providing some immunity to noise. The  $0.022 \mu\text{F}$  capacitors connected to the drain terminals of the PFETs provide a Miller effect, which reduces the rate of change of the drain voltage and therefore the rate of rise of current at turn-on. The soft-turn-on time depends upon the load impedance and is typically 100 to 200 ms.

## RADIATION-HARDENED, 125 A LINEAR REGULATOR

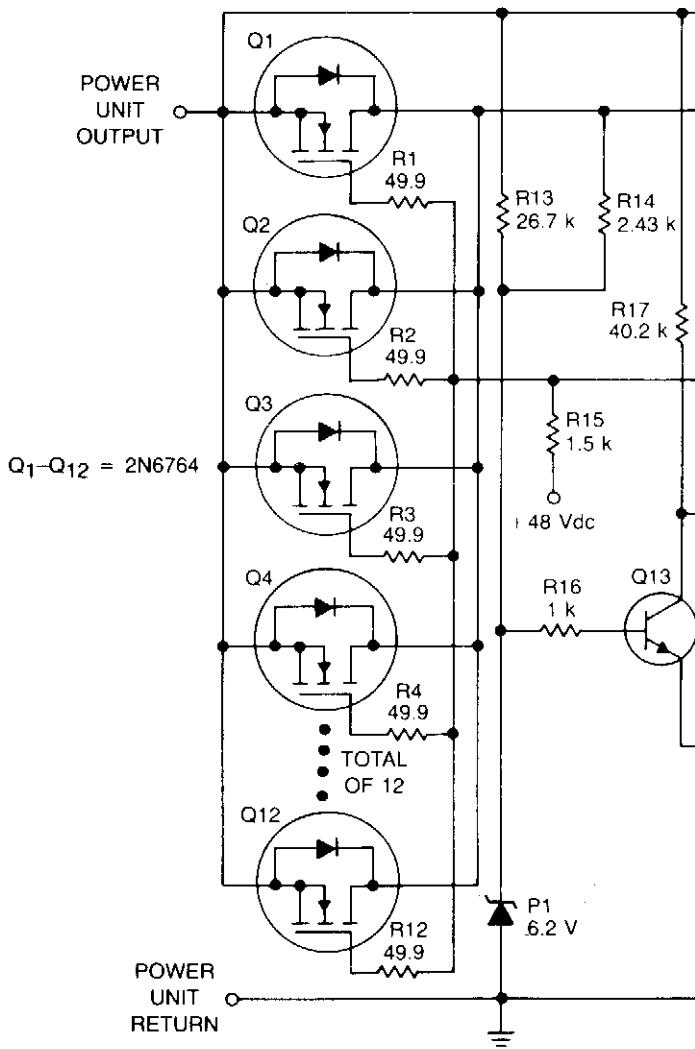


**Fig. 72-5**

MOTOROLA
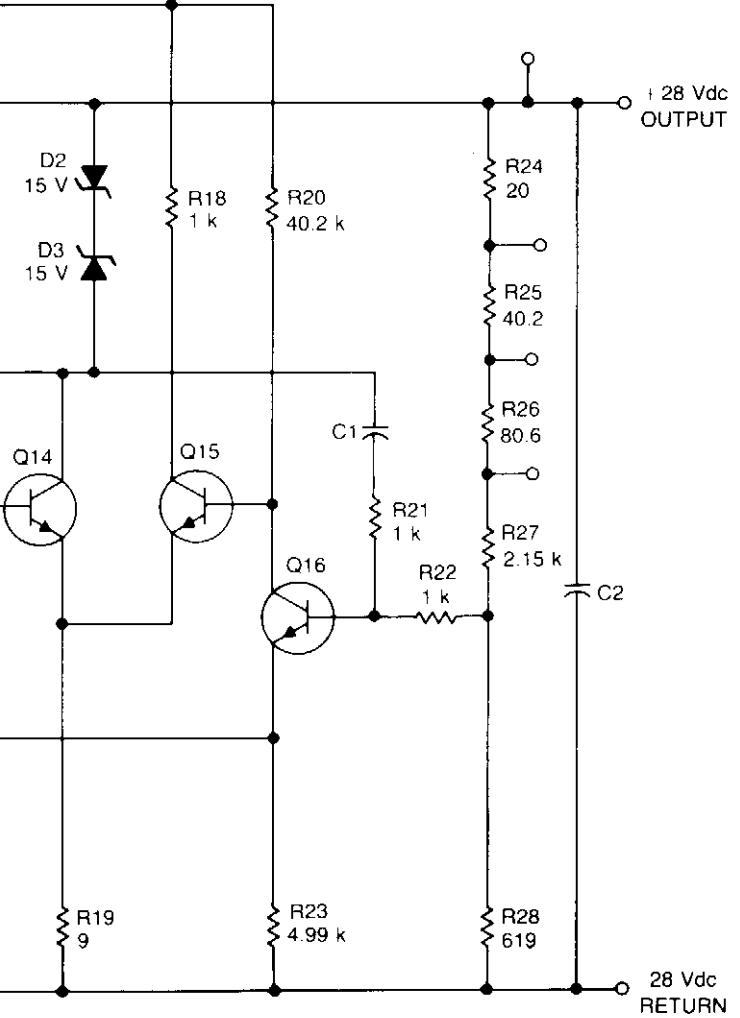
### Circuit Notes


Intended for extreme temperature, radiation-hardened environments, this linear supply is capable of supplying 28 Vdc at 125 A from an ac-driven power unit.

In operation, power supply output voltage is sensed by the voltage divider consisting of R24 to R28 and fed to one input of a discrete differential amplifier composed of Q13



through Q16. The other input of the amplifier is connected to a radiation-hardened zener diode, D1. Local feedback using R21 and C1 produces gain to phase shift that are independent of individual component parameters, which provides stable operation into the required loads.

## SWITCH MODE POWER SUPPLY

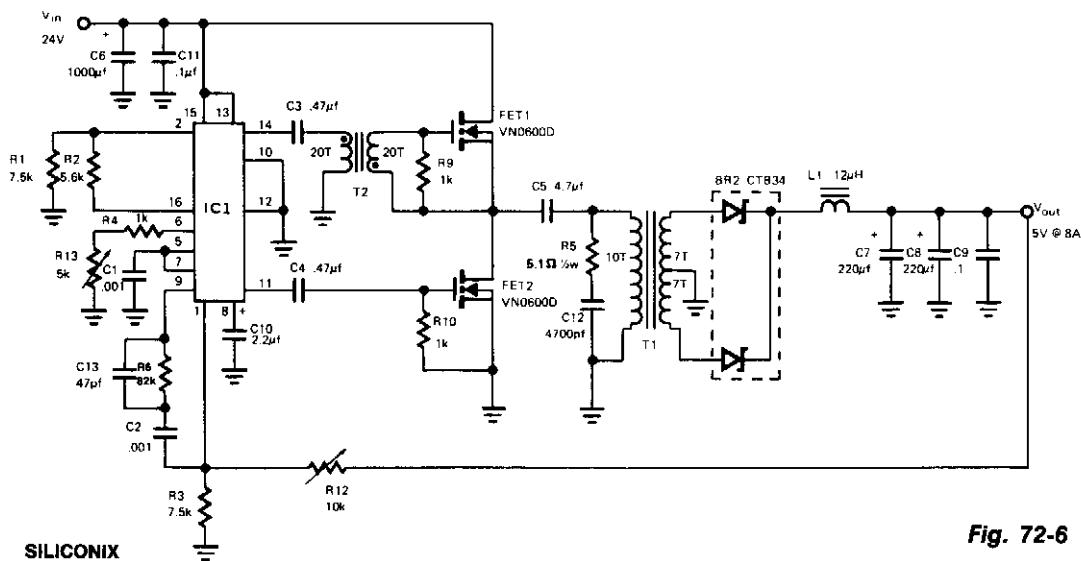


**Fig. 72-6**
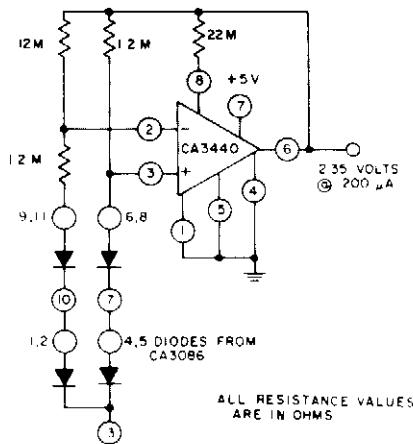
### Circuit Notes

This buck-derived circuit provides up to 8 A at 5 Vdc operating off 24 to 32 Vdc. The two power MOSFETs in the circuit conduct alternately for equal periods. Switching frequency is 150 kHz, set by the PWM125 controller. Output of the two MOSFETs is transformed to a low-voltage level, then rectified. Efficiency of the circuit is 75% when operated in a 22 to 32 V range. Efficiency approaches 90% with higher voltage inputs.

## MICROPOWER BANDGAP REFERENCE SUPPLY




### Circuit Notes

The circuit uses a CA3440 BiMOS op amp and CA3086 transistor array. The no-load current from 5-volt supply is 1.5  $\mu$ A. Load current can go as high as 200  $\mu$ A and still maintain output voltage regulation within 0.05%.

**Fig. 72-7**

GENERAL ELECTRIC/RCA
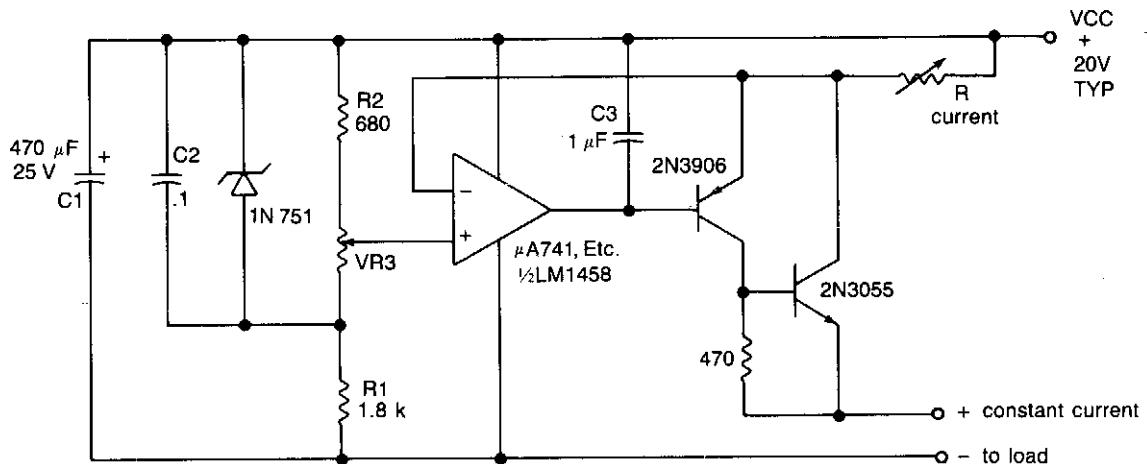
## VARIABLE CURRENT SOURCE, 100 mA TO 2 AMP




WILLIAM SHEETS

Fig. 72-8

### Circuit Notes

The output current is set by the resistor R in the collector of Tr2, which may be varied to offer a range of output currents from 100 mA to 2 A with fine control by means of VR3 which varies the reference voltage to the non-inverting input of the op amp. The feedback path from the output to the inverting input of the op amp maintains a constant voltage across R, equal to  $(V_{CC} - V_{IN})$  and hence a constant current to the load given by  $(V_{CC} - V_{IN})/R$ .

## BASIC SINGLE-SUPPLY VOLTAGE REGULATOR

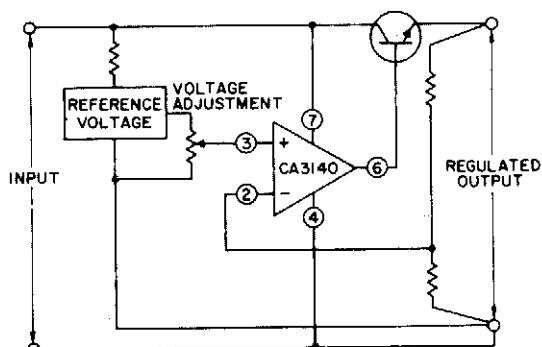


GENERAL ELECTRIC/RCA

Fig. 72-9

### Circuit Notes

The circuit uses a CA3140 BiMOS op amp capable of supplying a regulated output that can be adjusted from essentially 0 to 24 volts.

## BENCH TOP POWER SUPPLY

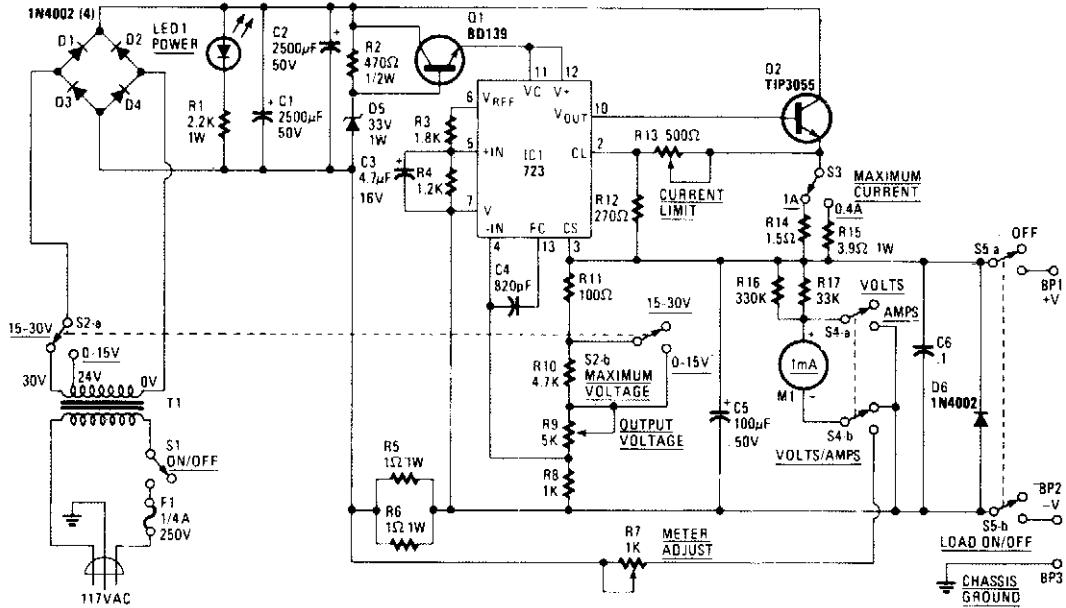


# RADIO-ELECTRONICS

*Fig. 72-10*

Circuit Notes

A tapped transformer drives a diode bridge (D1-D4) and two 2500  $\mu$ F filter capacitors (C1 and C2), that provide a no-load voltage of 37 or 47 volts, depending upon the position of switch S2a. The unregulated dc is then fed to a pre-regulator stage composed of Q1 and D5. Those components protect IC1 (the 723) from an over-voltage condition; the 723 can't handle more than 40 volts. The LED (LED1) and its 2.2 k current-limiting resistor (R1) provide on/off indication. The current through the LED varies slightly according to the transformer tap selected, but that's of no real consequence. The series-pass transistor in IC1 drives voltage-follower Q2, providing current amplification. The transistor can handle lots of power. It has a maximum collector current of 15 amps and a maximum  $V_{CE}$  of 70 V, both of which are more than adequate for our supply.
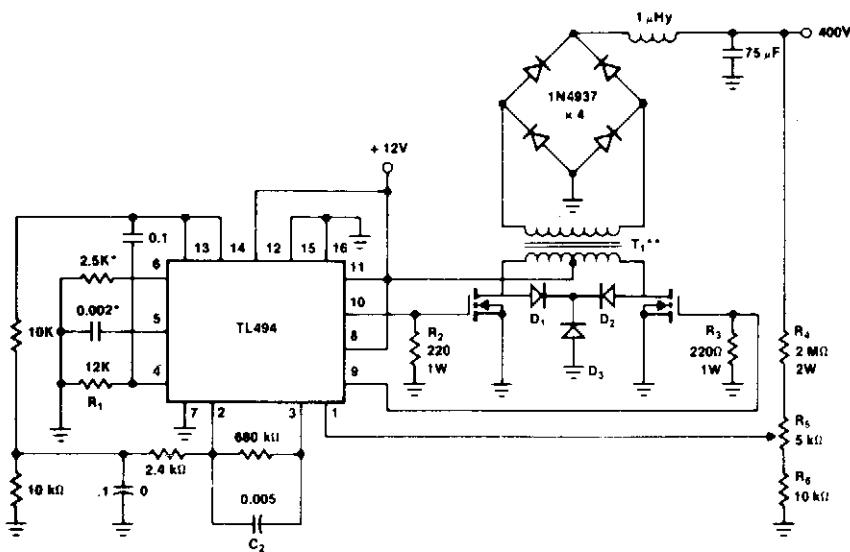
## 400-VOLT, 60-WATT PUSH-PULL POWER SUPPLY



**NOTES**

UNLESS OTHERWISE NOTED.

ALL RESISTORS 5%,  $\frac{1}{4}$  W

ALL CAPACITOR VALUES IN MICROFARADS, 25V

Q<sub>1</sub> & Q<sub>2</sub>: VN64GA ON HEAT SINK

D<sub>1</sub> & D<sub>2</sub>: 1N4934

D<sub>3</sub>: 33V, 3W ZENER

T<sub>1</sub>: PRI: 12T, CT, NO 18 AWG

SEC: 275T, NO 24 AWG

CORE: IND GEN 8231-1

SILICONIX, INC.

**Fig. 72-11**

### Circuit Notes

The design delivers a regulated 400-V, 60-W output. The TL494 switching regulator governs the operating frequency and regulates output voltage. R1 and C1 determine switching frequency, which is approximately  $0.5RC = 100$  kHz for the values shown. The TL494 directly drives the FET's gates with a voltage-controlled, pulse-width-modulated signal. After full-wave rectification, the output waveform is filtered by a choke-input arrangement. The  $1 \mu\text{H}$ ,  $75 \mu\text{F}$  filter accomplishes the job nicely at 100 kHz. A feedback scheme using R4, R5 and R6 provides for output-voltage regulation adjustment, with loop compensation handled by C2. Diodes D1 and D2 provide isolation and steering for the 33-V zener transient clamp, D3. Output regulation is typically 1.25% from no-load to the full 60-W design rating. Regulation is essentially determined by the TL494. Output noise and ripple consists mainly of positive and negative 0.8-V spikes occurring when the output stage switches.

## 500 kHz SWITCHING INVERTER FOR 12 V SYSTEMS

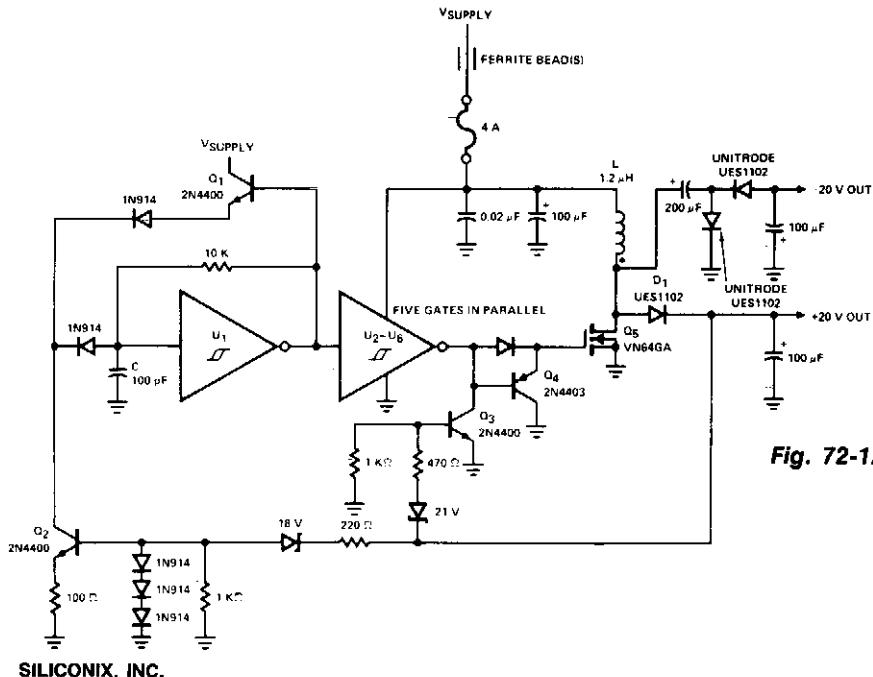


Fig. 72-12

SILICONIX, INC.

### Circuit Notes

This PWM control circuit provides the control pulse to the DMOS Power Switch in the flyback circuit. The output of the PWM is a pulse whose width is proportional to the input control voltage and whose repetition rate is determined by an external clock signal. To provide the control input to the PWM and to prevent the output voltage from soaring or sagging as the load changes the error amplifier and reference voltage complete the design. They act as the feedback loop in this control circuit much like that of a servo control system.

## 10 AMP-REGULATOR WITH CURRENT AND THERMAL PROTECTION

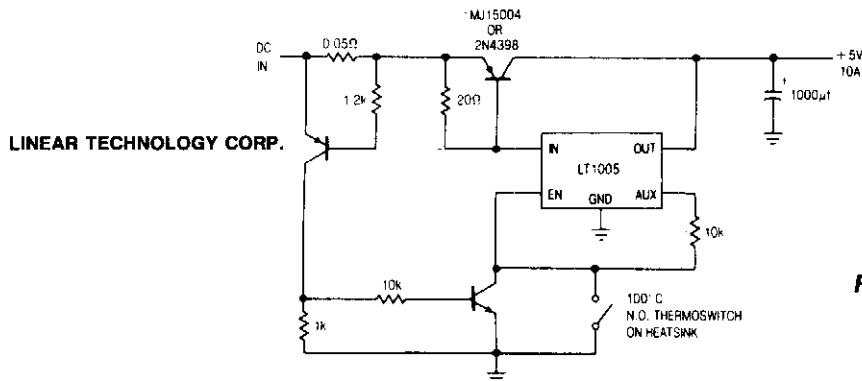


Fig. 72-13

## BIPOLAR POWER SUPPLY FOR BATTERY INSTRUMENTS

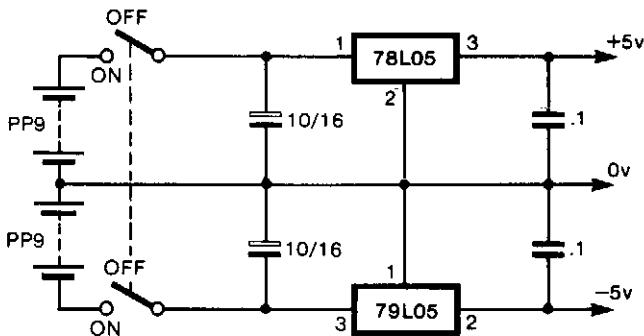


Fig. 1

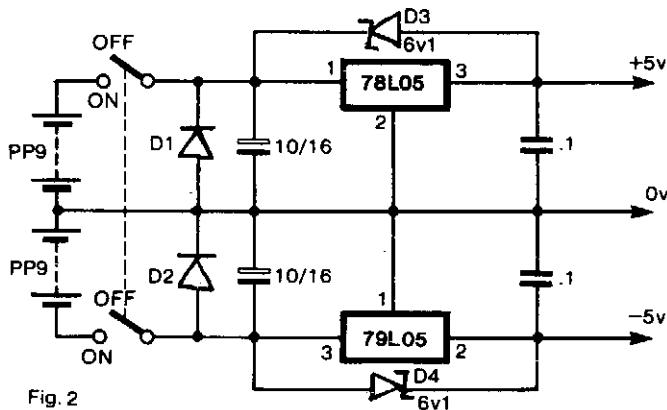


Fig. 2

ELECTRONIC ENGINEERING


**Fig. 72-14**

### Circuit Notes

To generate regulated  $\pm 5$ -V supplies from a pair of dry batteries, the circuit of Fig. 1 is commonly used. In order to give protection from inadvertent reverse connection of a battery, a diode in series with each battery would produce an unacceptable voltage drop. The more effective approach is to fit diodes D1 and D2 as shown in Fig. 2, in parallel with each battery.

When the supply is switched off, there is the risk of a reverse bias being applied across the regulators, if there is significant inductance or capacitance in the load circuit. Diodes across the regulators prevent damage. When the power supply is switched on, the two switches do not act in unison. There is a probability that one or the other regulators will be latched hard off by the other. To prevent this, D3 and D4 are Zener diodes so that  $\pm 5$ -V rails are pulled up by the batteries until the regulators establish the correct levels.

## POWER SUPPLY FOR 25-WATT ARC LAMP

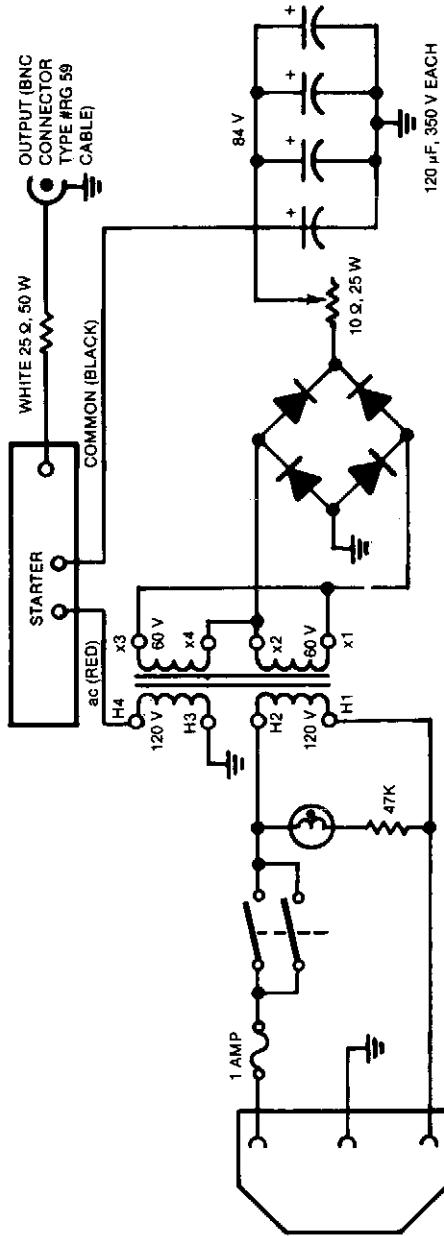


NASA

Fig. 72-15

### Circuit Notes

A dual-voltage circuitry both strikes and maintains the arc. The lamps require a starting voltage in excess of 1,000 volts. Once stabilized, the voltage drop across the lamp is near 20 volts. Power supply consists of two main sections. The first section, the low-voltage power supply section, is an 84-volt direct-current supply. This supply powers the stabilized arc. Current is limited by the 10 ohm adjustable and 25 ohm fixed resistance. The second section, the high-voltage starter circuit, is a Cockcroft-Walton voltage multiplier. With no load, the output voltage is 2,036 volts. However, when the arc is established, the heavy current drain maintains a forward bias on all of the diodes, and the circuit becomes a straight path with a voltage drop of 7.2 volts. The small value of the capacitors used in the multiplier guarantees that the diodes will be forward-biased once the arc is established.
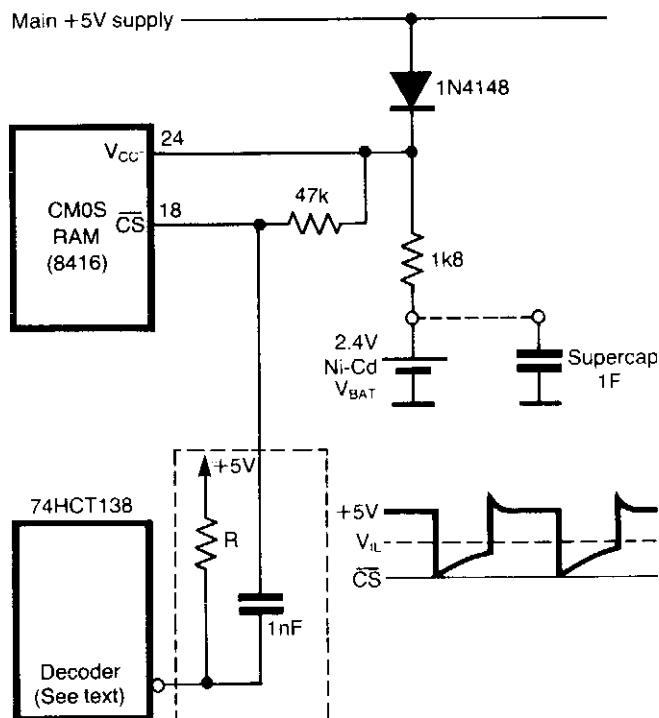
## STAND-BY POWER FOR NON-VOLATILE CMOS RAMs



ELECTRONIC ENGINEERING

**Fig. 72-16**

### Circuit Notes

To prevent loss of data when a CMOS RAM is switched from normal operation ( $V_{CC} = 5$  volts) to stand-by mode ( $V_{CC} = V_{BAT}$ ) it must be ensured that the CS pin goes near the  $V_{CC}$  rail at all times. Ac coupling to the chip select is made through capacitor C, breaking the dc current path between  $V_{CC}$  (and hence  $V_{BAT}$ ) and the decoder output. So, whatever the impedance state of the decoder in power down, the battery will provide current only for the RAM, low enough to keep the voltage at CS near to  $V_{CC}$ .

## HV REGULATOR WITH FOLDBACK CURRENT LIMITING

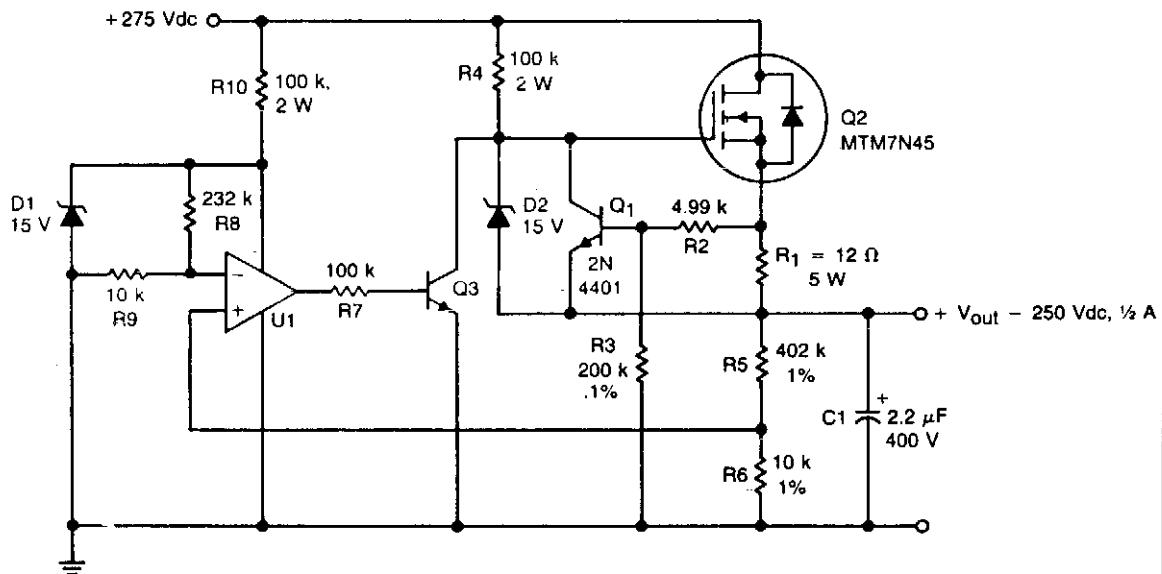


Fig. 72-17

MOTOROLA

### Circuit Notes

A TMOS MTM7N45 (Q2) is used as a series pass element in a linear high voltage supply that accepts +275-V unregulated and produces 250 V regulated with foldback current limiting.


A 15-V zener, D1, provides the dc reference for operational amplifier U1, whose other input is obtained from a fraction of the output voltage. U1 drives Q3, which drives the gate of Q2. Foldback current limiting is achieved by R1, R2, R3, R4, Q1, and D2. The formula to establish the current "knee" for limiting is:

$$I_{KNEE} = \frac{V_{OUT}(R_2/R_2 + R_3) + 0.5 \text{ V}}{R_1}$$

Short circuit current is:

$$I_{SC} = \frac{0.5 \text{ V}}{R_1}$$
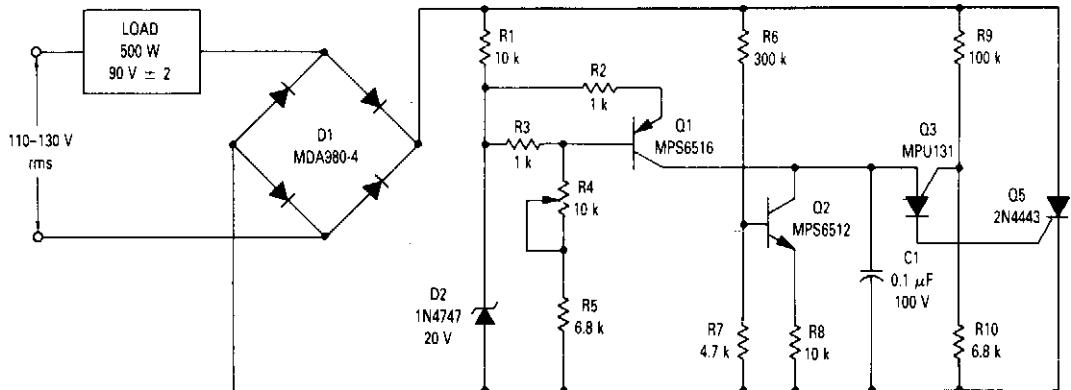
## 90 V rms VOLTAGE REGULATOR USING A PUT




MOTOROLA

**Fig. 72-18**

### Circuit Notes

The circuit is an open loop rms voltage regulator that will provide 500 watts of power at 90 V rms with good regulation for an input voltage range of 110-130 V rms. With the input voltage applied, capacitor C1 charges until the firing point of Q3 is reached causing it to fire. This turns Q5 on which allows current to flow through the load. As the input voltage increases, the voltage across R10 increases which increases the firing point of Q3. This delays the firing of Q3 because C1 now has to charge to a higher voltage before the peak-point voltage is reached. Thus the output voltage is held fairly constant by delaying the firing of Q5 as the input voltage increases. For a decrease in the input voltage, the reverse occurs.


## 12-14 V REGULATED 3 A POWER SUPPLY

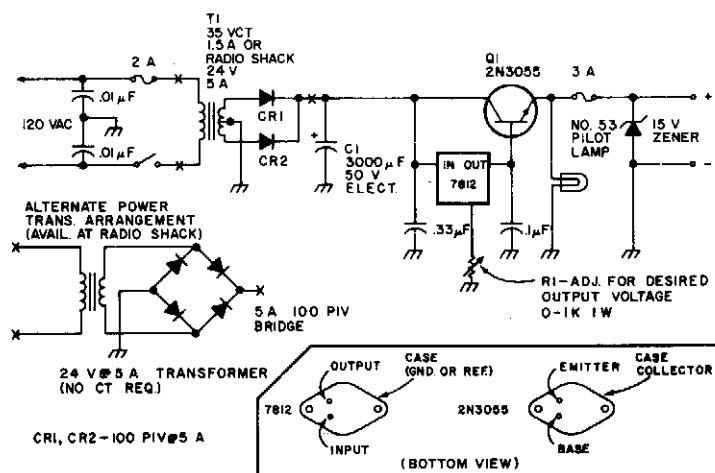

AMATEUR RADIO

Fig. 72-19

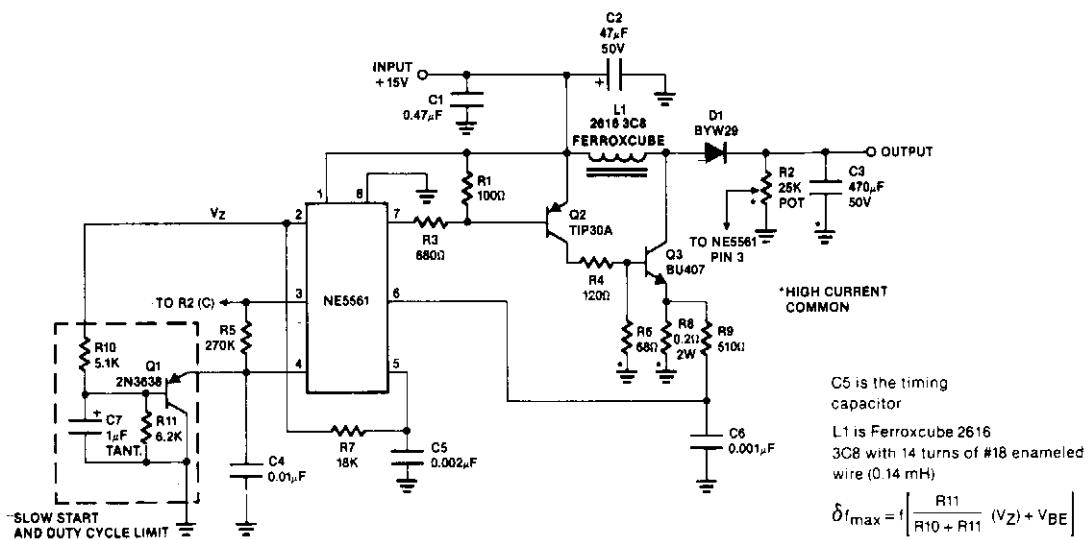
## DC-TO-DC SMPS VARIABLE 18 V TO 30 V OUT AT 0.2 A



SIGNETICS

Fig. 72-20

## OFF-LINE FLYBACK REGULATOR

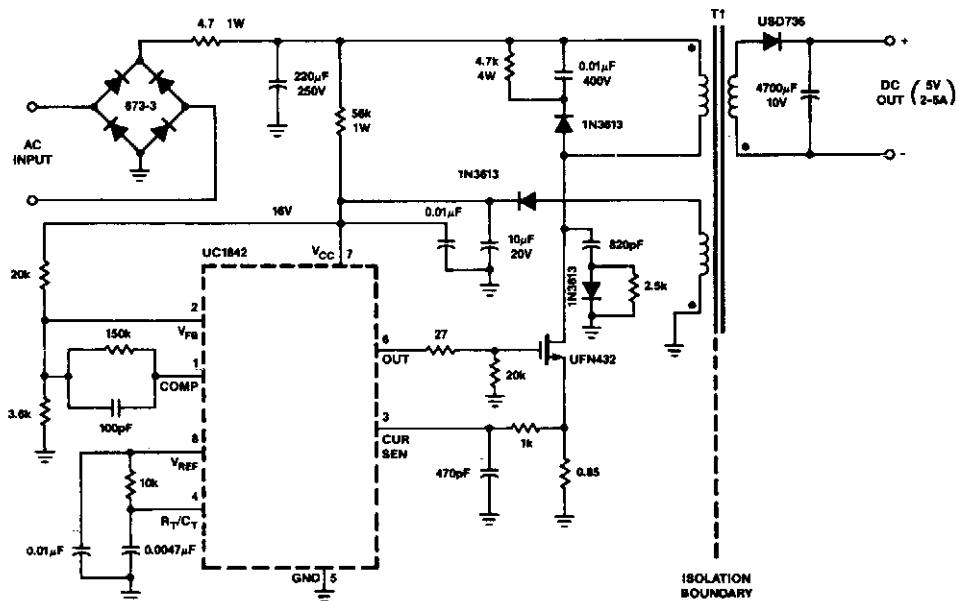

TC116903

**NOTES:**  
 T1: Coilcraft E-4140-B  
 Primary - 97 turns  
 single AWG 24  
 Secondary - 4 turns  
 4 parallel AWG 22  
 Control - 9 turns  
 3 parallel AWG 28

### SPECIFICATIONS

Input line voltage:	90V <sub>AC</sub> to 130V <sub>AC</sub>	Efficiency @ 25 W,
Input frequency:	50 or 60Hz	$V_{IN} = 90V_{AC}$ : 70%
Switching frequency:	40kHz± 10%	$V_{IN} = 130V_{AC}$ : 65%
Output power:	25W maximum	Output short-circuit current: 2.5A average
Output voltage:	5V± 5%	
Output current:	2 to 5A	
Line regulation:	0.01%/V	
Load regulation:	8%/A*	


### SIGNETICS

**Fig. 72-21**

### Circuit Notes

This circuit uses a low-cost feedback scheme in which the dc voltage developed from the primary-side control winding is sensed by the UC1842 error amplifier. Load regulation is therefore dependent on the coupling between secondary and control windings, and on transformer leakage inductance. For applications requiring better load regulation, a UC1901 Isolated Feedback Generator can be used to directly sense the output voltage.

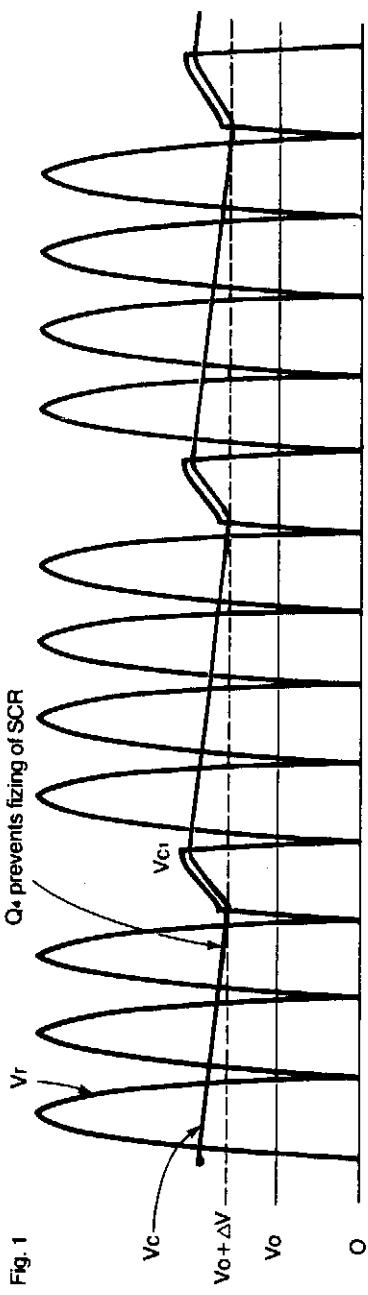**SCR PREREGULATOR FITS ANY POWER SUPPLY**



一

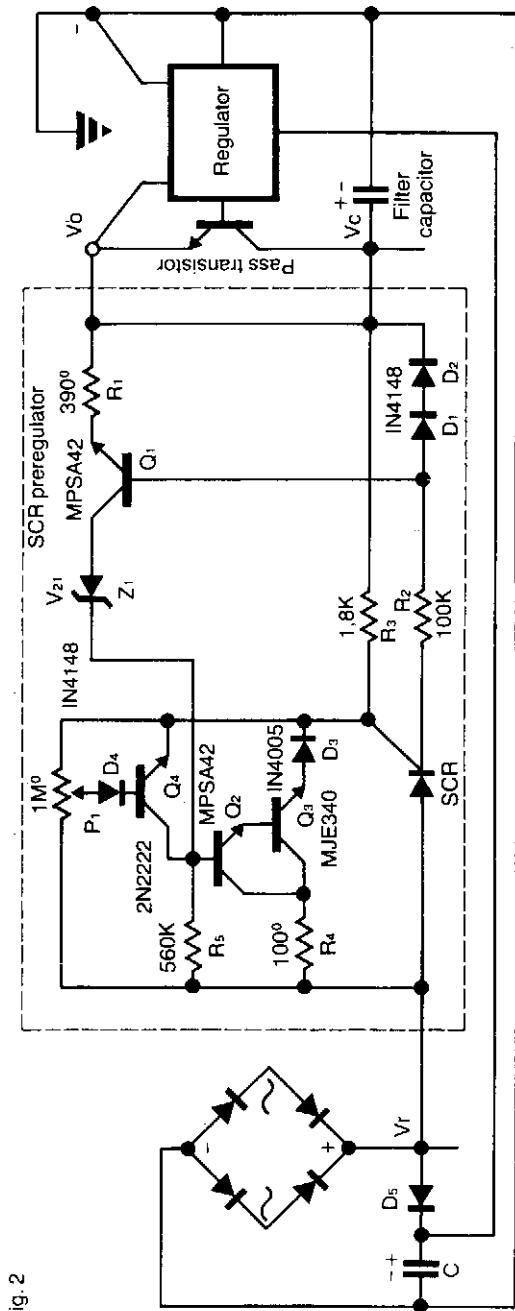


Fig. 2

ELECTRONIC ENGINEERING


Fig. 72-22

### **Circuit Notes**

This SCR pre-regulator keeps the filter capacitor  $V_c$ , in a variable output power supply, a few volts above the output voltage  $V_o$ . The benefits include: less heat dissipated by the pass transistor and therefore small heatsink, cooler operation and higher efficiency, especially at low output voltages.

Q1, R1, R2, D1 and D2 form a constant current source for zener Z1, so that the contribution to the output current is always a few mA (2 - 3 mA). The Darlington pair Q2, Q3 keeps the SCR off. The voltage  $V_c$  decreases until  $V_c = V_o = V$  at which point the Darlington pair fires the SCR, charging the filter capacitor to a higher voltage  $V_c^1$  in less than half the period of the input voltage. The component values, shown are for a 0 - 250-V, 3-A power supply.


## VOLTAGE REGULATOR

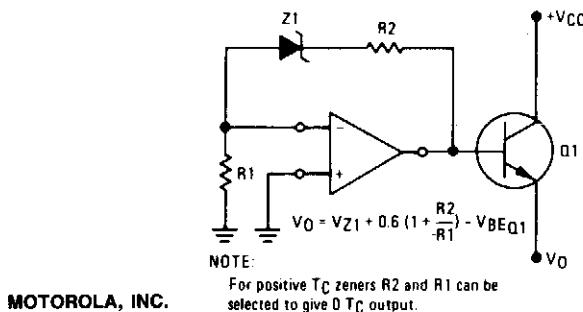

*Fig. 72-23*

MOTOROLA, INC.
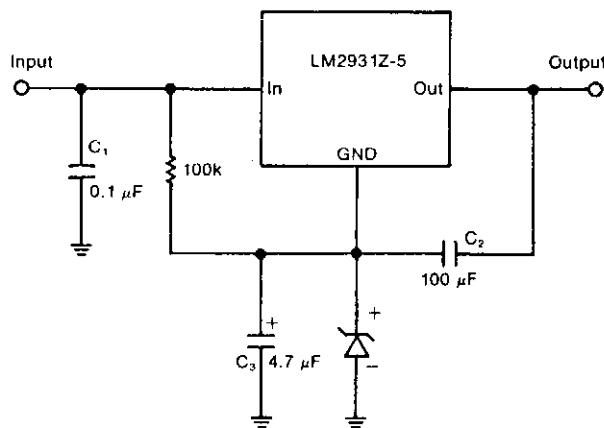
## ZENER DIODE INCREASE FIXED PNP REGULATOR'S OUTPUT VOLTAGE RATINGS




ELECTRONIC DESIGN

*Fig. 72-24*

### Circuit Notes

A zener diode in the ground lead of a fixed pnp regulator varies the voltage output of that device without a significant sacrifice in regulation. The technique also allows the regulator to operate with output voltages beyond its rated limit.
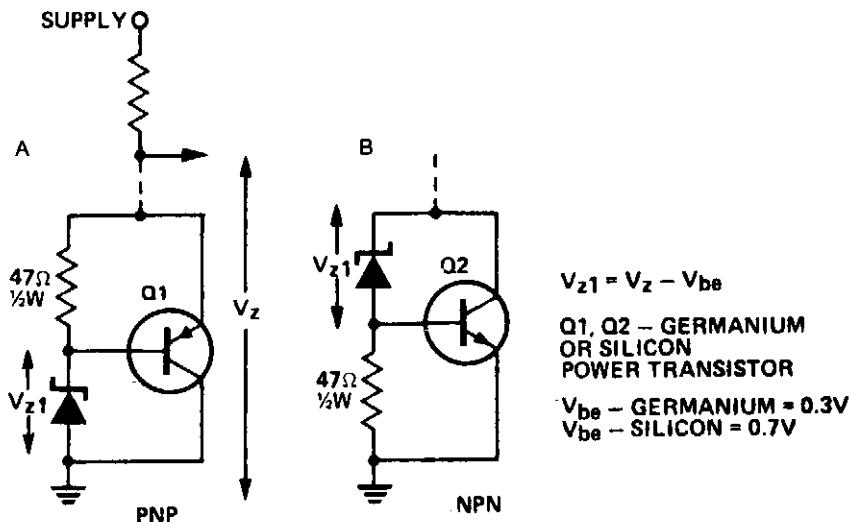
## INCREASING THE POWER RATING OF ZENER DIODES




ELECTRONICS TODAY INTERNATIONAL

Fig. 72-25

### Circuit Notes

A power transistor can be used to provide a high powered zener voltage from a low wattage zener. A 400 mW zener can be used where a 10 watt zener is required or a 1 W zener can be used where a 50 to 80 watt zener is required by using appropriate transistors for Q1 and Q2 in the circuits shown. Where low rating is required, Q1 would be an ASZ 15 (germanium) or an AY9140 (silicon). Q2 could be a 2N2955 (silicon). For higher powers, Q1 should be an ASZ18 (germanium) or a 2N2955 (silicon) and Q2 a 2N3055 (silicon) or an AY8149 (silicon). A heatsink on the transistor is required. The circuit in A has the advantage that power transistors can be bolted directly on to a chassis which may serve as a heatsink.

## MEMORY SAVE ON POWER-DOWN

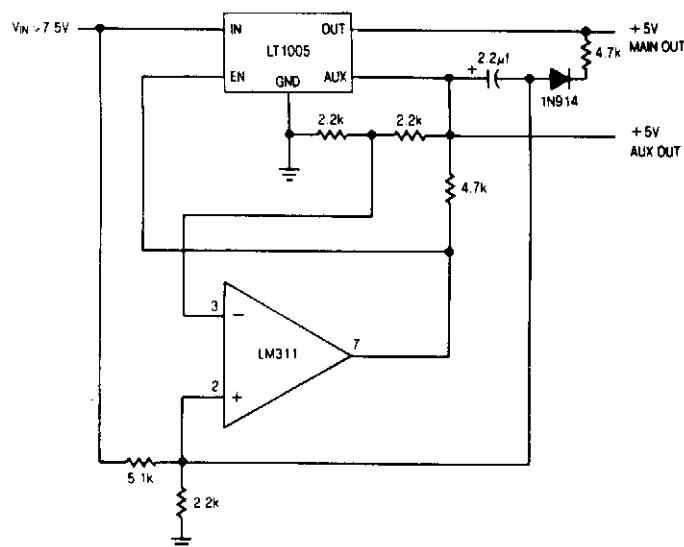

LINEAR TECHNOLOGY

Fig. 72-26

### Circuit Notes

The auxiliary output powers the memory, while the main output powers the system and is connected to the memory store pin. When power goes down, the main output goes low, commanding the memory to store. The auxiliary output then drops out.

# **73**

## **Power Supply Circuits (High Voltage)**



---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low Cost Ultra High Generator  
Simple High-Voltage Supply  
High Voltage Geiger Counter Supply  
High Voltage Supply

## LOW COST ULTRA HIGH VOLTAGE GENERATOR

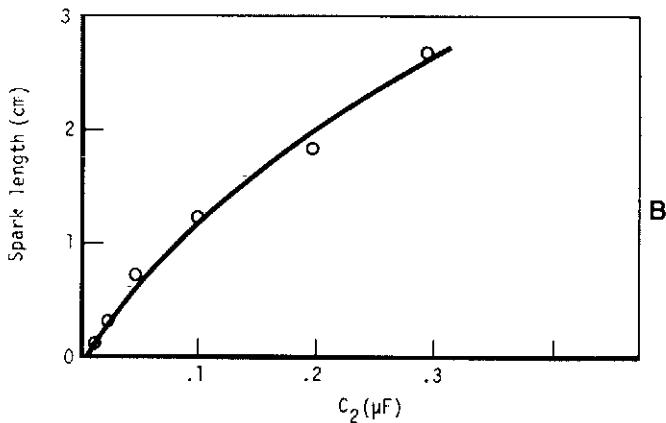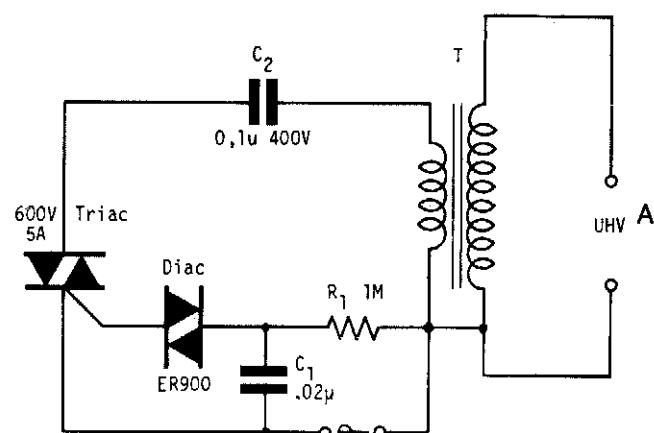


ELECTRONIC ENGINEERING

Fig. 73-1


### Circuit Notes

By repetitively charging and discharging a capacitor through the primary of an induction coil with a high voltage, an ultra high emf is induced in the secondary. Switching is performed by the triac, triggered by the disc at times set by  $C_1$  and  $R_1$ . With a 12 V car ignition coil for example, the length of sparkgap obtained is 12 mm of air for  $C_2 = 0.1 \mu\text{F}$ . If the dielectric strength of air is assumed to be 3 kV/mm, this spark-gap length corresponds to 36 kV. From the curve shown in Fig. B, care must be taken in keeping the value of  $C_2$  below 1  $\mu\text{F}$  as the coil is liable to be seriously damaged at this value of  $C_2$ . Power consumption is only about one watt.

### SIMPLE HIGH-VOLTAGE SUPPLY

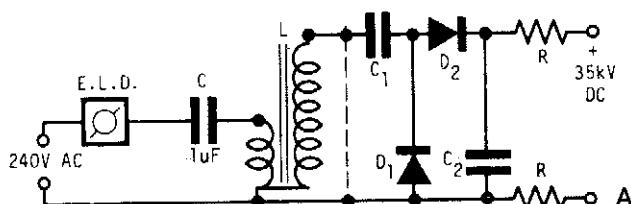

*Fig. 73-2*

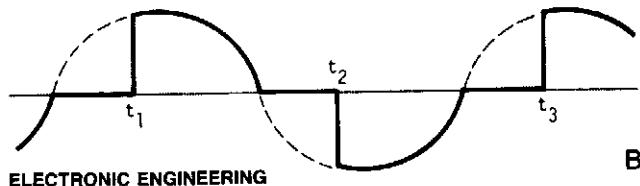


ELECTRONIC ENGINEERING

B

#### Circuit Notes

A light dimmer, a  $1 \mu\text{F}$  capacitor and a 12 V car ignition coil form the simple line powered HV generator. The current in the dimmer is shown in Fig. B. At times  $t_1$ ,  $t_2$ , . . . , set by the dimmer switch, the inner triac of the dimmer switches on, and a very high and very fast current pulse charges the capacitor through the primary of the induction coil. Then at a rate of 120 times per second for a 60 Hz line, a very high voltage pulse appears at the secondary of the coil. To obtain an HV dc output, use a voltage doubler. D1 and D2 are selenium rectifiers (TV 18 Siemens or ITT) used for the supply of television sets. High value output shock protection resistors, R, are recommended when suitable.

### HIGH VOLTAGE GEIGER COUNTER SUPPLY

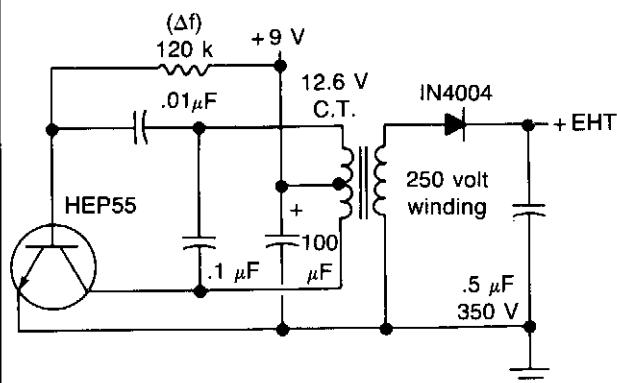


#### Circuit Notes

This circuit will generate about 300 volts dc—at a very low current, but enough for a GM tube.

POPULAR ELECTRONICS

*Fig. 73-3*

### HIGH VOLTAGE SUPPLY

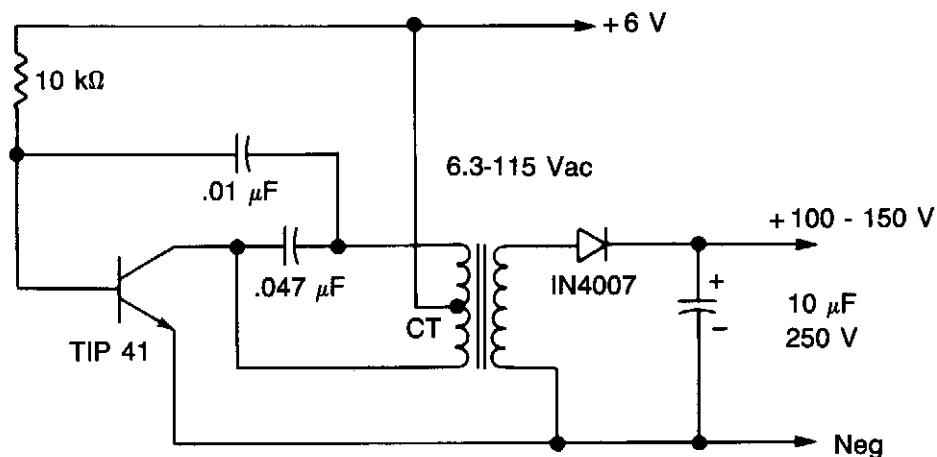

WILLIAM SHEETS

Fig. 73-4

#### Circuit Notes

A 6 V battery can provide 100-150 Vdc center-tapped at a high internal impedance (not dangerous though it can inflict an unpleasant jolt). A 6.3 V transformer is connected "in reverse" with a transistor used in a Hartley oscillator configuration. The frequency of operation may be controlled by varying the value of the 10 K ohm resistor. The 10 μF capacitor must have a working voltage of at least 250 Vdc.

## **74**

# **Power Supply Monitors**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Power Supply Monitor
- Low-Volts Alarm
- Microprocessor Power Supply Watchdog
- Overvoltage Protection Circuit (SCR Crowbar)
- Power Supply Protection Circuit

## POWER SUPPLY MONITOR


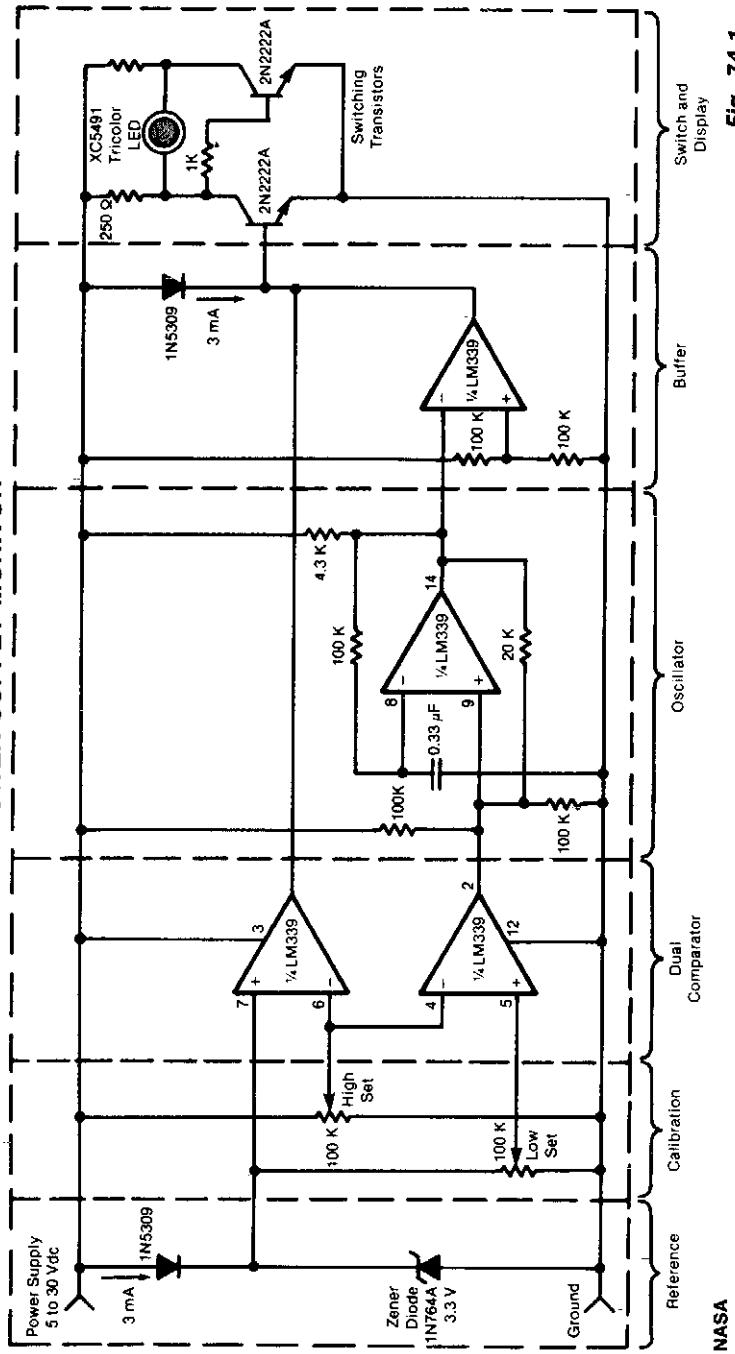


Fig. 74-1

### Circuit Notes

This circuit uses a tricolor LED display to indicate acceptable and unacceptable output voltages. One to set the upper voltage limit, the other, the lower voltage limit. When the monitored voltage is above the set maximum, the LED display turns red. Yellow turns on for voltages below the set minimum, and green turns on for voltages between the high and the low settings. The circuit does not need a separate power supply. It is powered by the voltage it monitors. The circuit can be adapted to monitor voltage differences between two power supplies. Should the monitored voltages differ by more than a set value, a visual or an audible alarm would warn the operator about the difference. The circuit can also be modified for remote monitoring and the use of a separate power supply.

## LOW-VOLTS ALARM

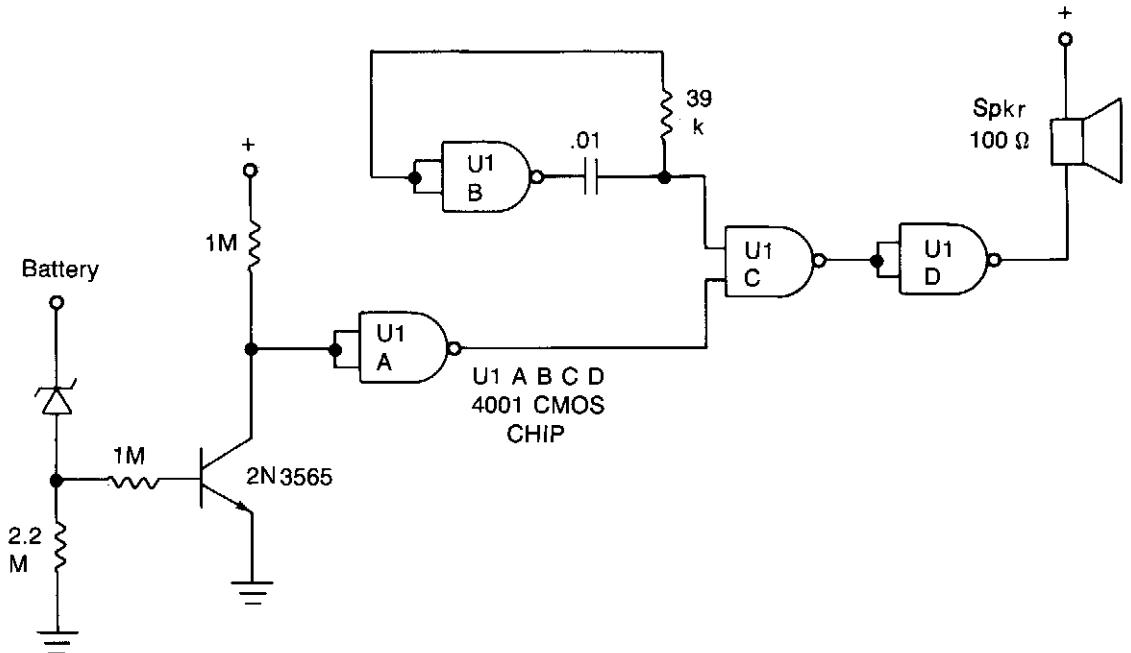

WILLIAM SHEETS


*Fig. 74-2*

### Circuit Notes

This inexpensive dc supply-voltage monitor sounds a warning when the voltage falls below a preset value. It is ideal for monitoring rechargeable batteries since it draws only a few microamperes when not sounding. The voltage at which the alarm sounds is determined by the zener diode. When the voltage falls below the zener voltage, the alarm sounds. The alarm tone is determined by the RC time constant of the 39 k resistor and 0.01 μf capacitor.

## MICROPROCESSOR POWER SUPPLY WATCHDOG

Fig 1

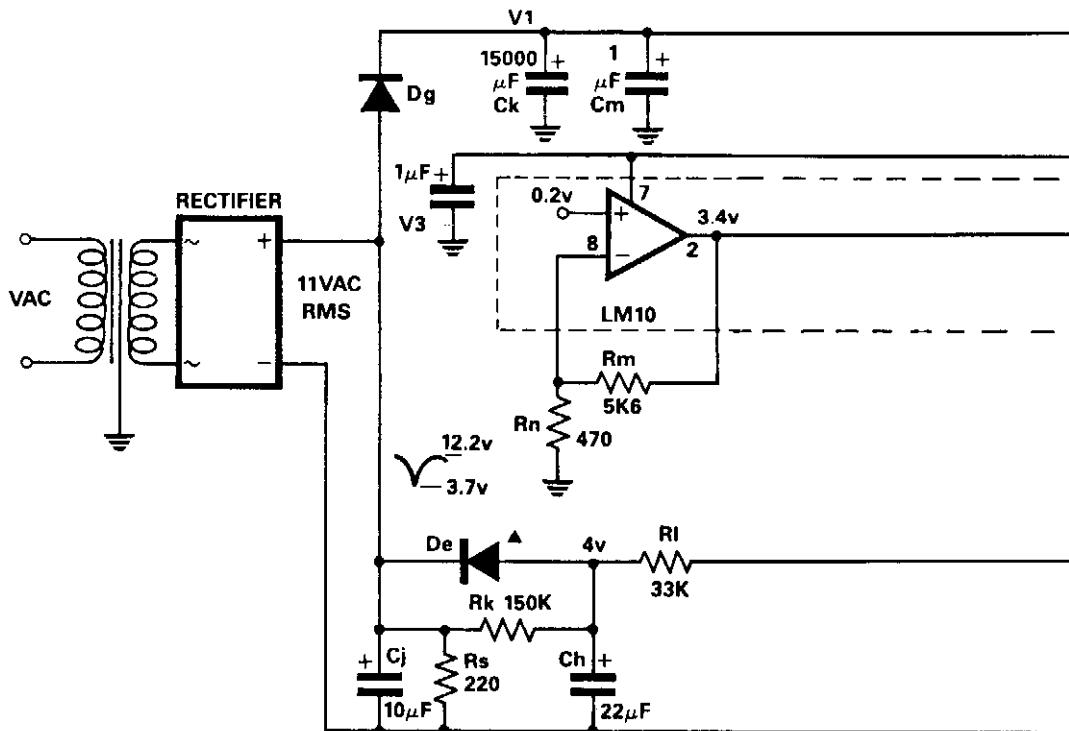


ELECTRONIC ENGINEERING

Fig. 74-3

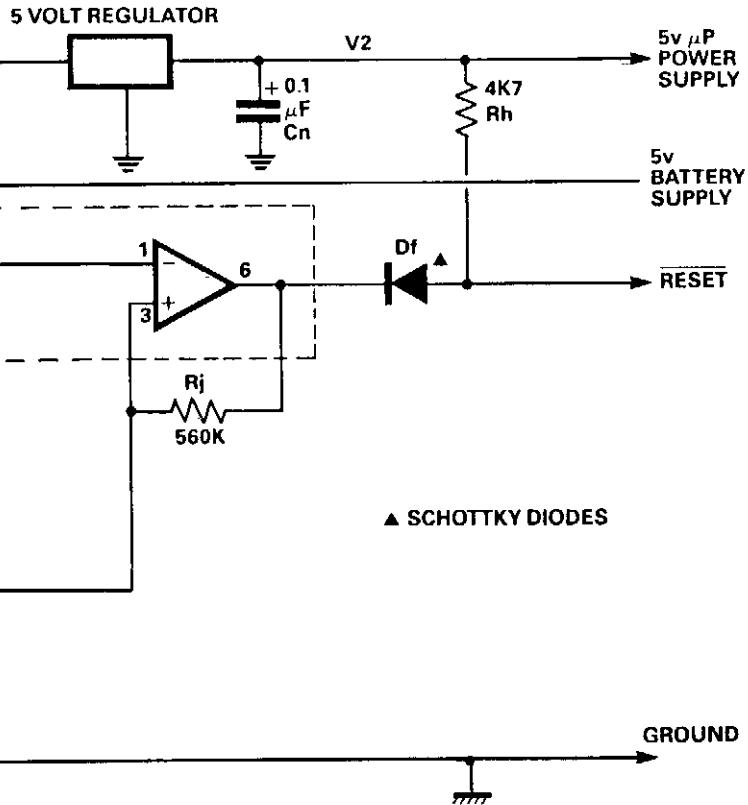
### Circuit Notes

The circuit monitors the input to the microprocessor 5 V regulated supply for voltage drops and initiates a reset sequence before supply regulation is lost. In operation, the resistor capacitor combination  $R_s$  and  $C_j$  form a short time constant smoothing network for the output of the fullwave bridge rectifier. An approximately triangular, voltage waveform appears across  $C$  and  $R_s$  and it is the minimum excursion of this that initiates



the reset. Diode Dg prevents charge sharing between capacitors Cj and Ck. Resistors Rn and Rm form a feedback network around the voltage reference section of the LM10C, setting a threshold voltage of 3.4 volts. The threshold voltage is set at 90% of the minimum voltage of the triangular wave trough, at the comparator's non-inverting input, dips below the threshold, the comparator output is driven low. This presents a reset to the microprocessor. Capacitor Ch is charged slowly through resistor Rk and discharged rapidly through diode De.
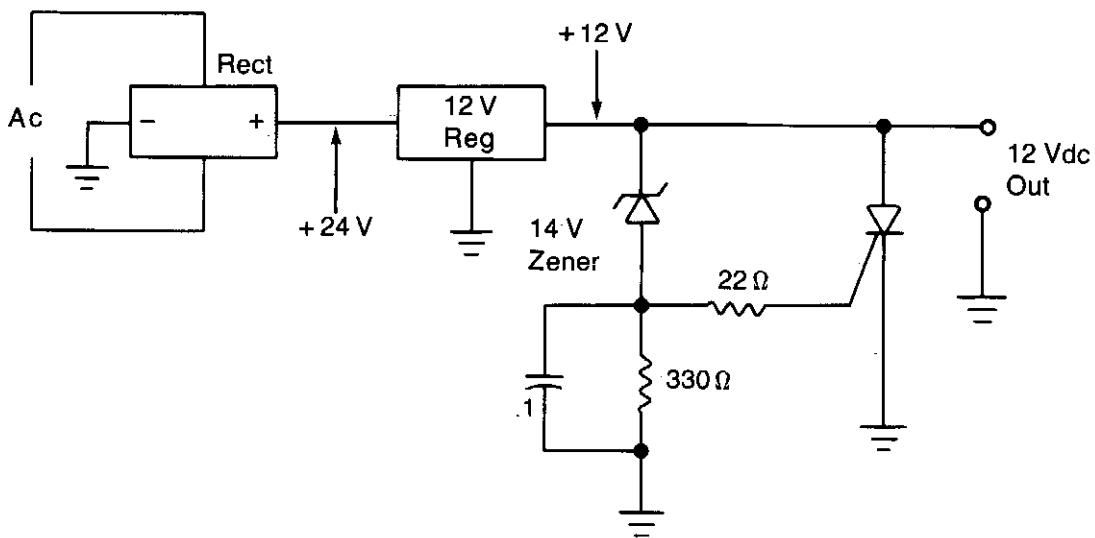
### OVERVOLTAGE PROTECTION CIRCUIT (SCR CROWBAR)




WILLIAM SHEETS

*Fig. 74-4*

#### Circuit Notes

The silicon controlled rectifier (SCR) is rated to handle at least the current of the power supply. It is connected in parallel across the 12 V dc output lines, but remains inert until a voltage appears at the gate terminal. This triggering voltage is supplied by the zener diode. At potentials less than 14 V the zener will not conduct current. But, at potentials greater than 14 Vdc the zener conducts and creates a voltage drop across the 330 ohm resistor that will fire the SCR. When the SCR turns on, the output lines of the power supply are shorted to ground. This will blow the primary fuse or burn out the transformer if there is no primary fuse.

### POWER SUPPLY PROTECTION CIRCUIT

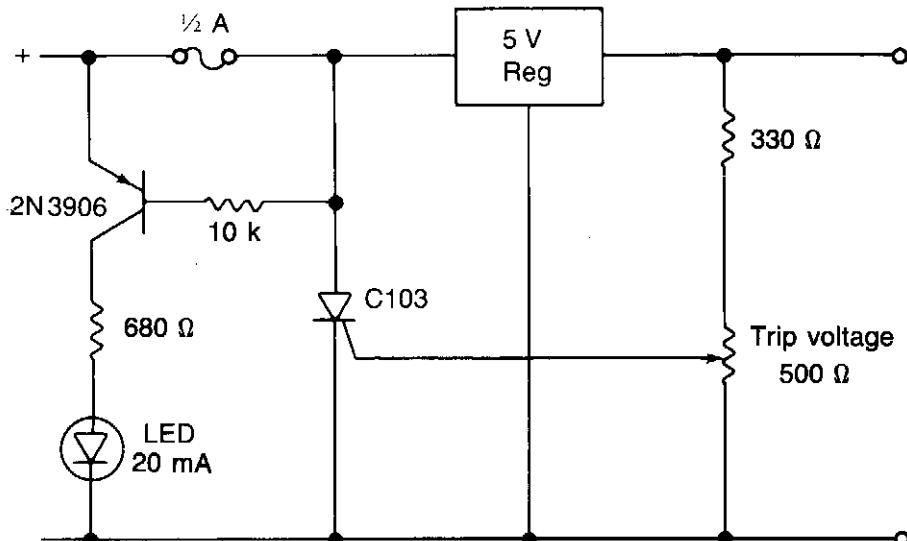

WILLIAM SHEETS

*Fig. 74-5*

#### Circuit Notes

When using a regulated supply to reduce a supply voltage there is always the danger of component failure in the supply and consequent damage to the equipment. A fuse will protect when excess current is drawn, but might be too slow to cope with overvoltage conditions. The values shown are for a 12 V supply being dropped to 5 V. The trip voltage is set to 5.7 V to protect the equipment in the event of a regulator fault. The 330 ohm resistor and the 500 ohm potentiometer form a potential divider which samples the output voltage as set by adjustment of the potentiometer. The SCR is selected to carry at least twice the fuse rating. The full supply voltage is connected to the input of the regulator. The 2N2906 is held bias off by the 10 k resistor and the SCR so that the LED is held off. If the output voltage rises above a set trip value then the SCR will conduct, the fuse will blow, and the 2N3906 will be supplied with base current via the 10 k resistor, and the LED will light up.

# **75**

## **Probes**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Microvolt Probe
- Single Injector-Tracer
- General Purpose RF Detector
- Clamp-on-Current Probe Compensator
- 650 MHz Amplifying Prescaler Probe
- Tone Probe for Testing Digital ICs

## MICROVOLT PROBE

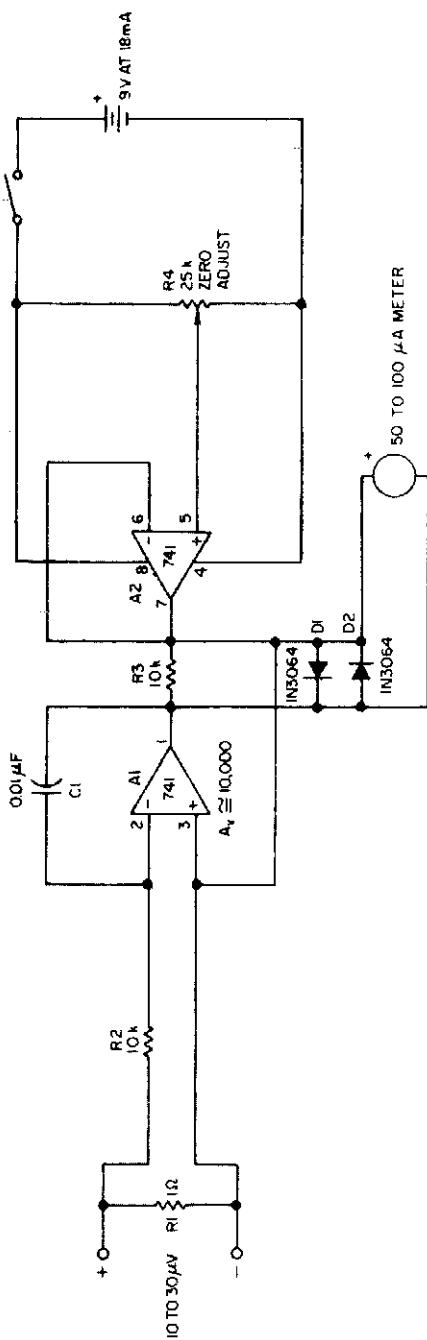


ELECTRONIC DESIGN

Fig. 75-1

### Circuit Notes

The current tracer helps locate a defective IC that is loading down the power supply. The tracer amplifies the small voltage drop caused by current flow along a fraction of an inch of PC wiring and drives an ordinary microammeter. Needle-point test probes are used to contact the edge of a PC trace and to follow the current to determine which branch the current takes. One-half of a dual 741 op amp forms a dc amplifier with ac feedback to prevent oscillations and hum-pickup problems. It drives a 50-to-100  $\mu$ A meter. The other op amp provides a center tap for the 9 V battery supply and zero adjustment with R4. Two diodes protect the meter. Resistor R1 eliminates the necessity for shorting the probes when the meter is zeroed. The value of 1 ohm is large when compared with the resistance of the meter leads plus the bridged portion of PC wiring.

### SINGLE INJECTOR-TRACER

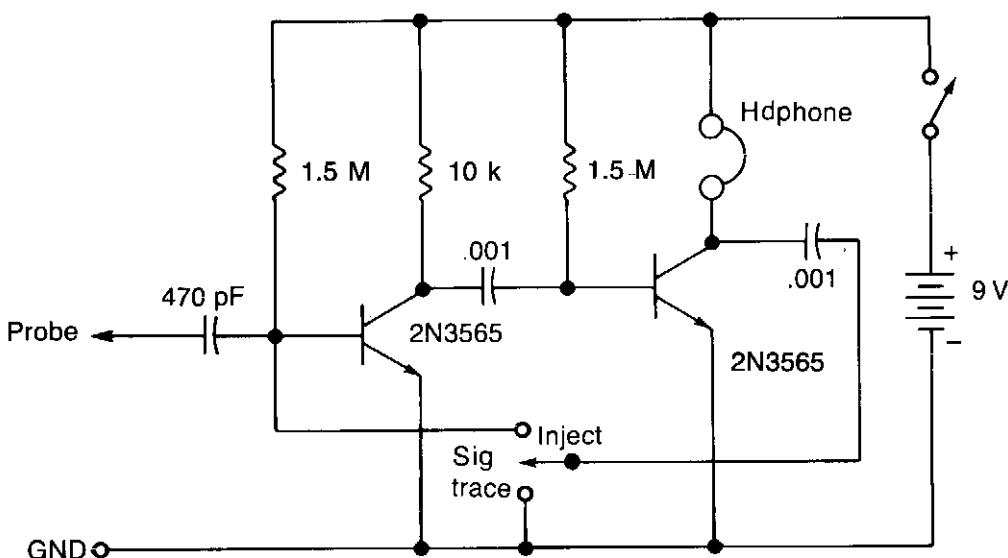


**Fig. 75-2**

WILLIAM SHEETS

### Circuit Notes

This circuit will provide a nominal square wave output in the audio range in the "Inject" mode, the harmonics of which should be heard at several MHz. In the "Trace" mode the non-linear operation of the amplifier will detect modulated rf signals which will be filtered by the .001  $\mu$ F capacitor and heard in the headphones.

### GENERAL PURPOSE RF DETECTOR

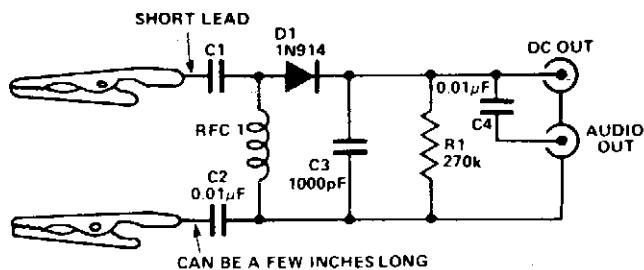


ELECTRONICS TODAY INTERNATIONAL

**Fig. 75-3**

### Circuit Notes

This circuit provides a dc output to a meter and an audio output (if necessary) for checking transmitters or modulated signals. It can be used also as a field strength meter or transmitter monitor.

## CLAMP-ON-CURRENT PROBE COMPENSATOR

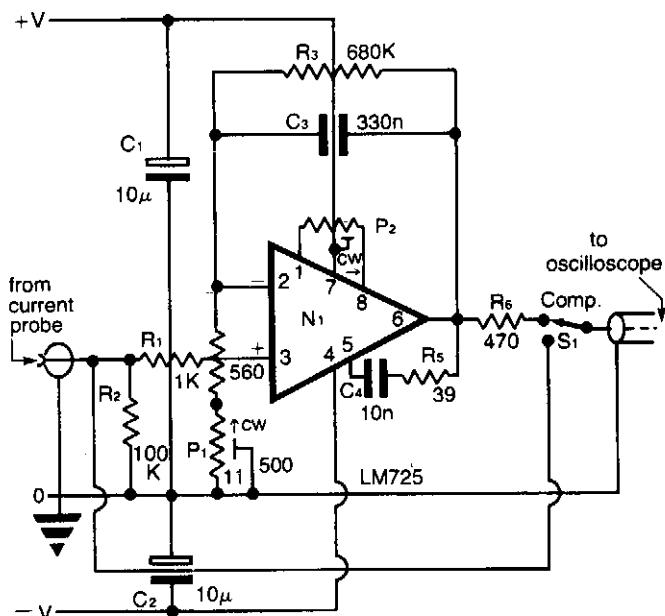

**Table**

Tek P6021, on its own	with Tek amp. 134	with compensator
120Hz to 60MHz @ 10mA/mV	12Hz to 38MHz	1Hz to 100kHz @
450Hz to 60MHz @ 2mA/mV	(switched 1mA to 1A/div for 50mV/div output)	2mA/mV

ELECTRONIC ENGINEERING


**Fig. 75-4**

### Circuit Notes

A clamp-on "current probe" such as the Tektronix P6021 is a useful means of displaying current waveforms on an oscilloscope. Unfortunately, the low-frequency response is somewhat limited, as shown in the Table.

The more sensitive range on the P6021 is 2 mA/mV, but it has a roll-off of 6 dB per octave below 450 Hz. The compensator counteracts the low-frequency attenuation, and this is achieved by means of C3 and R4 + P1 in the feedback around op amp N1. The latter is a low-noise type, such as the LM725 shown, and even so it is necessary at some point to limit the increasing gain with decreasing frequency; otherwise amplifier noise and drift will overcome the signal. The values shown for C3R3 give a lower limit below 1 Hz. A test square wave of  $\pm 10$  mA is fed to the current probe so that P1 can be adjusted for minimum droop or overshoot in the output waveform. At high frequencies, the response begins to fall off at 100 kHz.
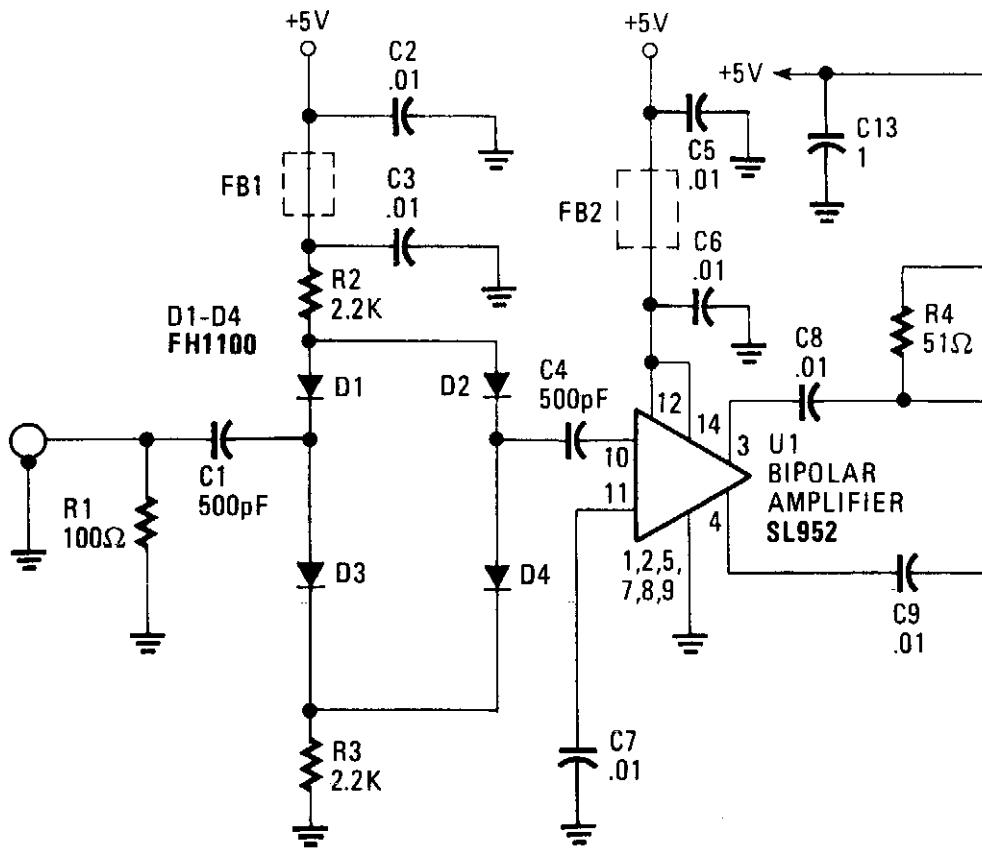
## **650 MHz AMPLIFYING PRESCALER PROBE**




## HANDS-ON ELECTRONICS

**Fig. 75-5**

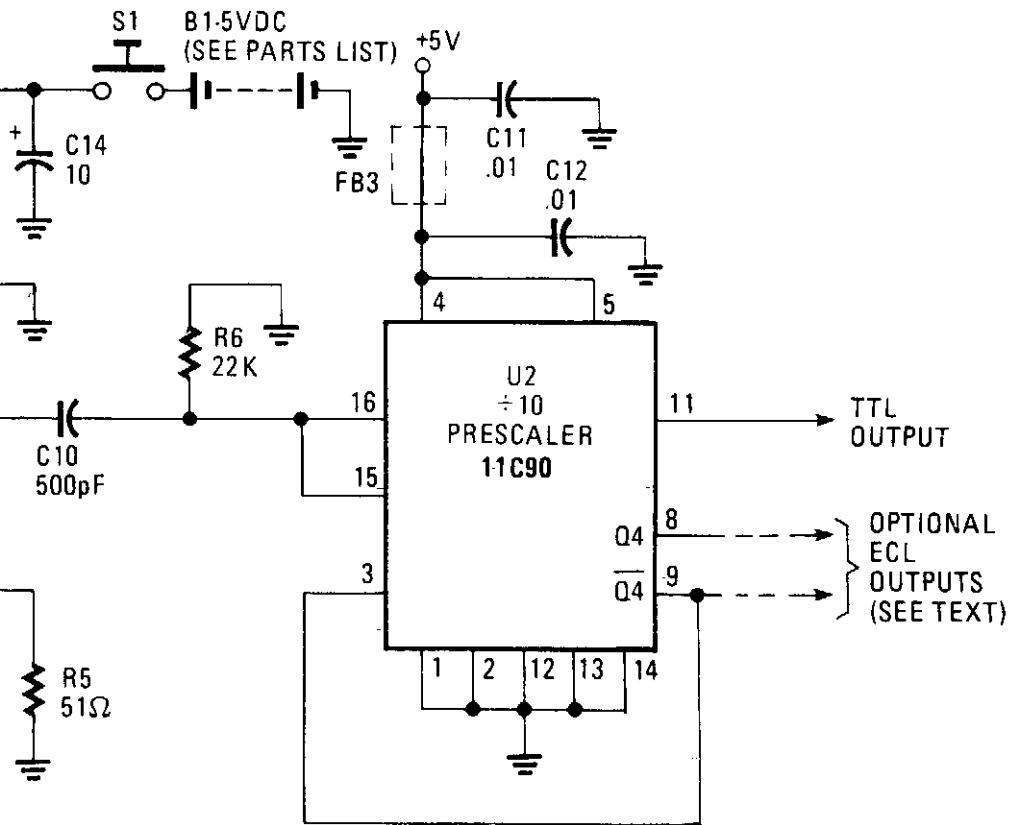**Circuit Notes**


The 650 MHz Prescaler Probe's input is terminated by resistor R1 and is fed through C1 to the diode limiter composed of D1 through D4. Those diodes are forward-biased by the + 5 volt supply for small-input signals and, in turn, feed the signal to U1. However, for larger input signals, diodes D1 through D4 will start to turn off, passing less of the signal, and, thus, attenuating it. But even in a full-off state, the FH1100-type diodes will always pass a small part of the input to U1 because of capacitive leakage within the diodes. Integrated circuit U1, a Plessey SL952 bipolar amplifier, capable of 1 GHz operation, provides 20 to 30 dB of gain. The input signal is supplied to pin 10, U1 with



the other input (pin 11) is bypassed to ground. The output signal is taken at pin 3 and pin 4, with pin 3 loaded by R4 and pin 4 by R5.

Integrated circuit 11C90, U2, is a high-speed prescaler capable of 650 MHz operation configured for a divide-by-10 format. A reference voltage internally generated appears at pin 15 and is tied to pin 16, the clock input. This centers the capacitive-coupled input voltage from U1 around the switching threshold-voltage level. An ECL-to-TTL converter in U1 provides level conversion to drive TTL input counters by tying pin 13 low. Therefore, no external ECL to TTL converter is required at the pin 11 output. On the other hand, ECL outputs are available at U2, pin 8 (Q4) and at pin 9 (Q4), if desired. In that circuit configuration, pin 13 is left open, and U2 will use less power.

## TONE PROBE FOR TESTING DIGITAL ICs

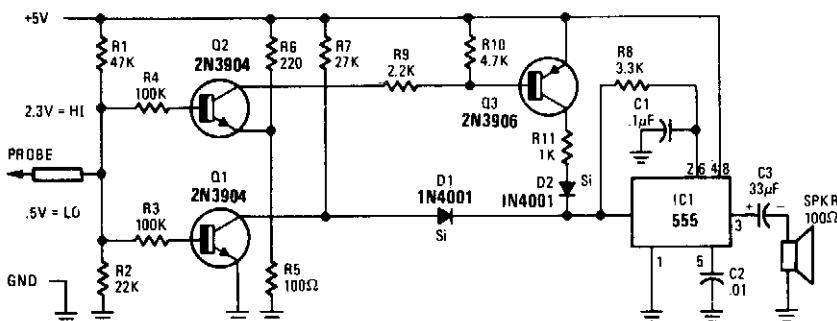

RADIO-ELECTRONICS

**Fig. 75-6**

### Circuit Notes

The tone probe uses sound to tell the status of the signal being probed. The probe's input circuit senses the condition of the signal and produces either a low-pitched tone for low-level signals (less than 0.8 V) or a high-pitched tone for high-level signals (greater than 2 V).

# **76**

## **Proximity Sensors**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Proximity Alarm  
Field Disturbance Sensor/Alarm

## PROXIMITY ALARM

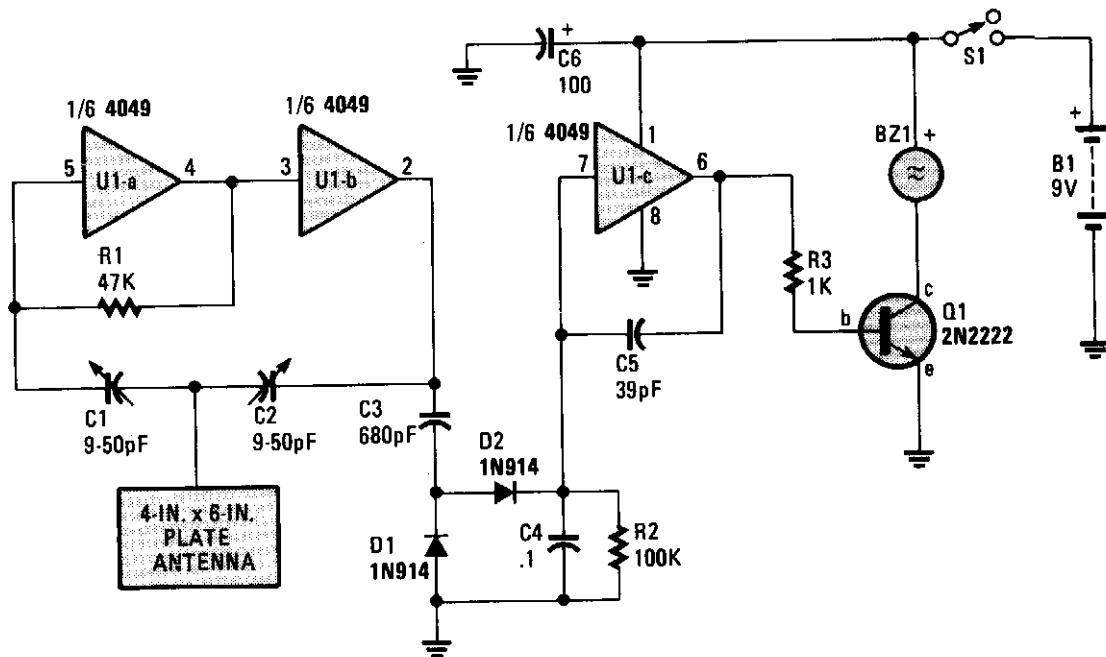


HANDS-ON ELECTRONICS

Fig. 76-1

### Circuit Notes

Inverters U1a and U1b are connected in a simple RC oscillator circuit. The frequency is determined by the values of R1, C1, C2, and the internal characteristics of the integrated circuit. As long as the circuit is oscillating, a positive dc voltage is developed at the output of the voltage-coupler circuit: C3, D1, D2 and C4. The dc voltage is applied to the input of U1c—the third inverter amplifier—keeping its output in a low state, which keeps Q1 turned off so that no sound is produced by BZ1. With C1 and C2 adjusted to the most sensitive point, the pickup plate will detect a hand 3 to 5-inches away and sound an alert. Set C1 and C2 to approximately one-half of their maximum value and apply power to the circuit. The circuit should oscillate and no sound should be heard. Using a non-metallic screwdriver, carefully adjust C1 and C2, one at a time, to a lower value until the circuit just ceases oscillation: Buzzer BZ1 should sound off. Back off either C1 or C2 just a smidgen until the oscillator starts up again—that is the most sensitive setting of the circuit.

## FIELD DISTURBANCE SENSOR/ALARM

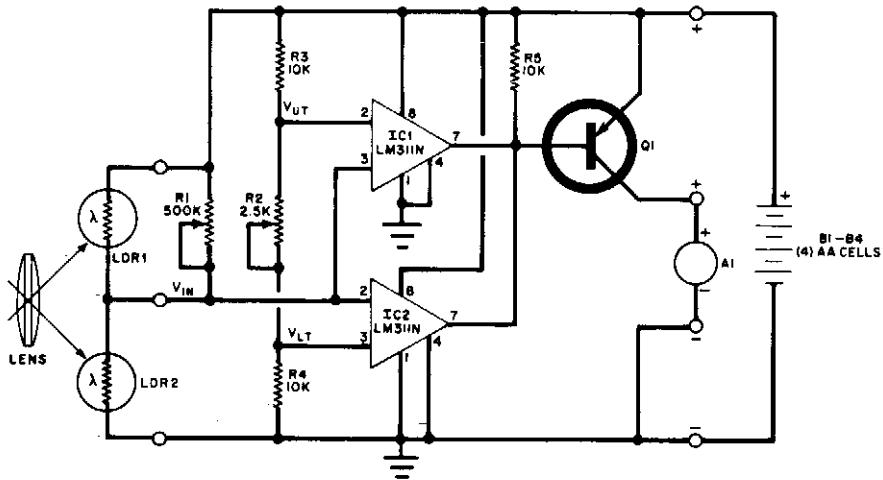

POPULAR ELECTRONICS

**Fig. 76-2**

### Circuit Notes

The change in ambient light triggers the alarm by changing resistance of LDR1 and LDR2.

Q1 = Radio Shack 276-2024

A1 = Mallory SC628P Sonalert

LDR1, LDR2 = Cadmium sulfide photocell, Radio Shack 276-116

# 77

## Pulse Generators


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Delayed Pulse Generator  
Pulse Generator (Astable Multivibrator)  
Non-Integer Programmable Pulse Divider

## DELAYED PULSE GENERATOR

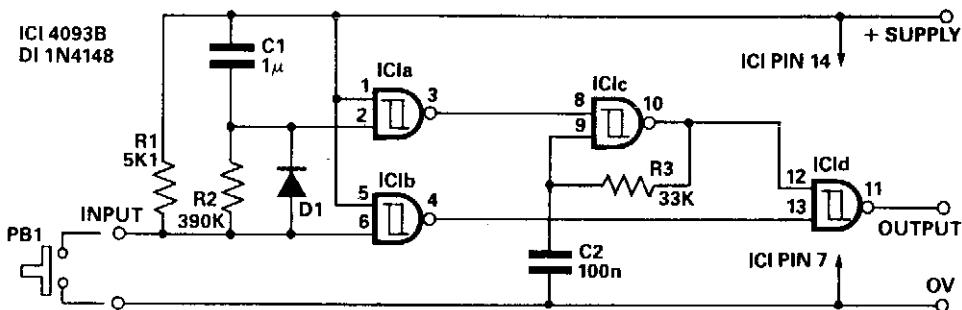


ELECTRONIC ENGINEERING

**Fig. 77-1**

### Circuit Notes

The circuit offers independent control of initial delay and pulse rate. IC1c is connected as a pulse generator whose operation is inhibited by the normally low O/P of the IC1a. When the circuit input goes low i.e., by pressing PB1, IC1b O/P goes high and the circuit O/P goes low thus replicating the input. When the input is kept low capacitor C1 charges via R2 to a point where IC1a O/P goes low. This allows the pulse generator IC1c to start and "rapid fire" pulses appear at the circuit O/P. When the circuit input returns to the high state C1 is rapidly discharged via D1 and R1. The value of R2 and C1 control the initial delay while R3 and C2 control the pulse rate. The values given will give a delay of around 0.5 seconds and a pulse rate of 200/300 Hz depending on supply voltage. PB1 may be replaced by an open collector TTL gate or a common emitter transistor stage if required.
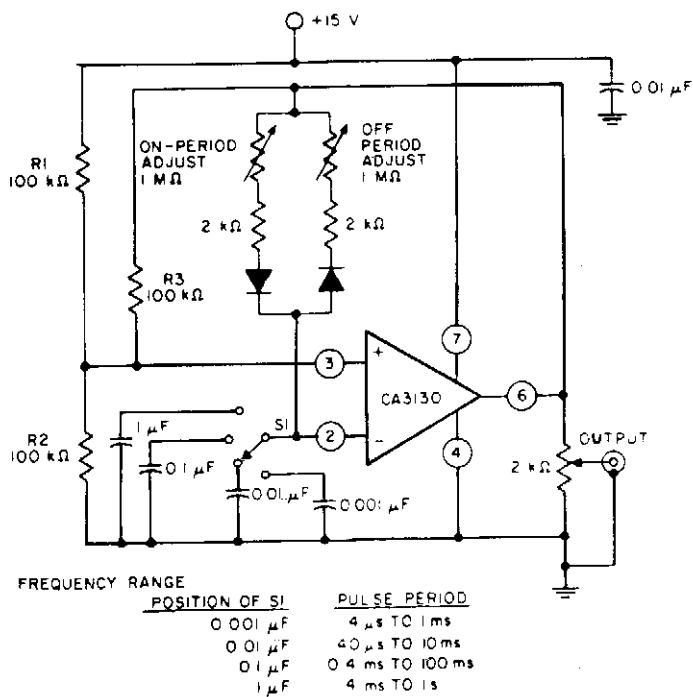
## PULSE GENERATOR (ASTABLE MULTIVIBRATOR)




RCA

Fig. 77-2

### Circuit Notes

Resistors R1 and R2 bias the CA3130 to the mid-point of the supply-voltage, and R3 is the feedback resistor. The pulse repetition rate is selected by positioning S1 to the desired position and the rate remains essentially constant when the resistors which determine on-period and off-period are adjusted.

## NON-INTEGER PROGRAMMABLE PULSE DIVIDER

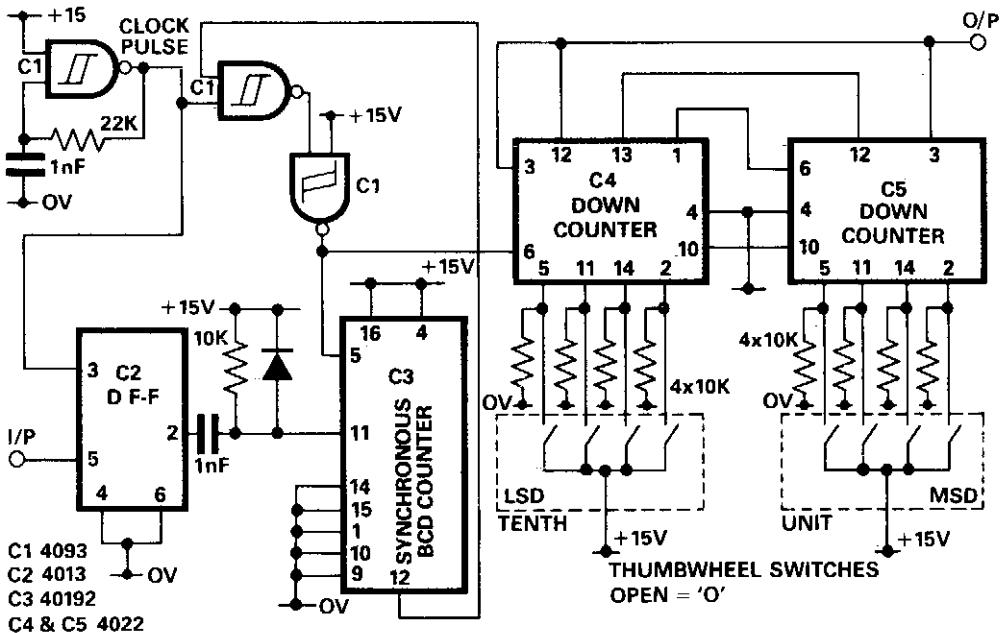

**Fig. 77-3**

ELECTRONIC ENGINEERING

### Circuit Notes

In applications where the period of the input pulses is uneven and the divider is required to cover a wide range of frequencies, the non-integer programmable pulse divider shown can be used. The purpose of the D-type flip-flop (IC2) is to synchronize the input signal with the clock pulse. When the clock pulse changes from low to high and the input is high, IC2 output goes high. Subsequently, IC3 resets to zero and starts counting up. The number of pulses at the output of IC3 is ten times the input pulse. IC4 and IC5 are cascaded to form a two decade programmable down counter.

# **78**

## **Radiation Detectors**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Micropower Radioactive Radiation Detector  
Pocket-Sized Geiger Counter  
Photomultiplier Output-Gating Circuit
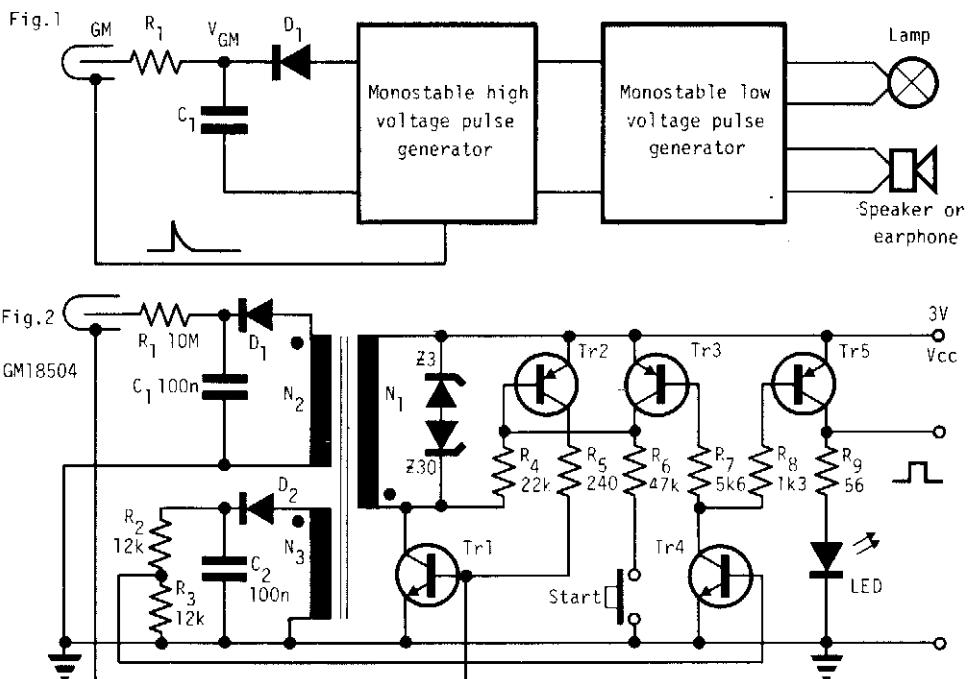
## MICROPOWER RADIOACTIVE RADIATION DETECTOR





ELECTRONIC ENGINEERING

Fig. 78-1

### Circuit Notes


In the absence of radiation, no current is drawn. At normal background radiation levels the power consumption is extremely low. The instrument may be left on for several months without changing batteries. In this way the detector is always ready to indicate an increase in radiation. An LED is used as an indicator lamp. With background radiation it draws less than  $50 \mu\text{A}$ . A ferrite pot core is used for the transformer with  $N_1 = 30$ ,  $N_2 = 550$ , and  $N_3 = 7$ . Using two 1.5V batteries with 0.5 Ah total capacity, the detector can work at background radiation levels for  $0.5 \text{ Ah} \div 50 \mu\text{A} = 10,000$  hours, which is more than a year.

## POCKET-SIZED GEIGER COUNTER

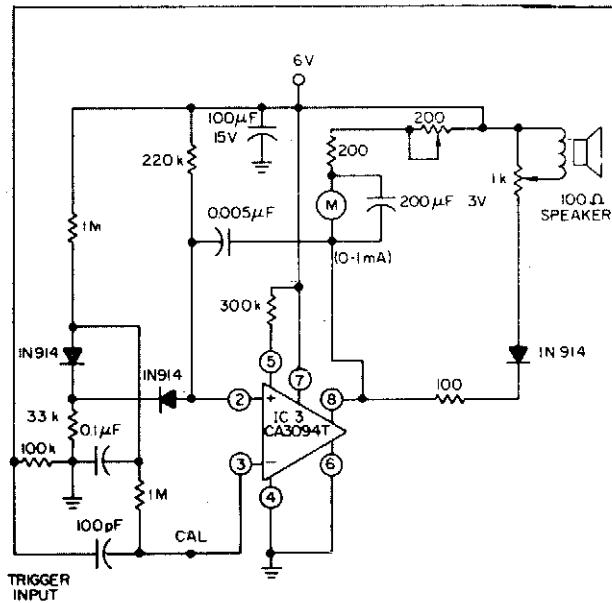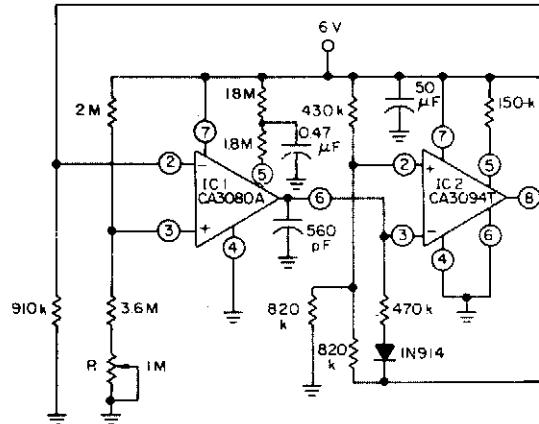

ELECTRONIC DESIGN


*Fig. 78-2*

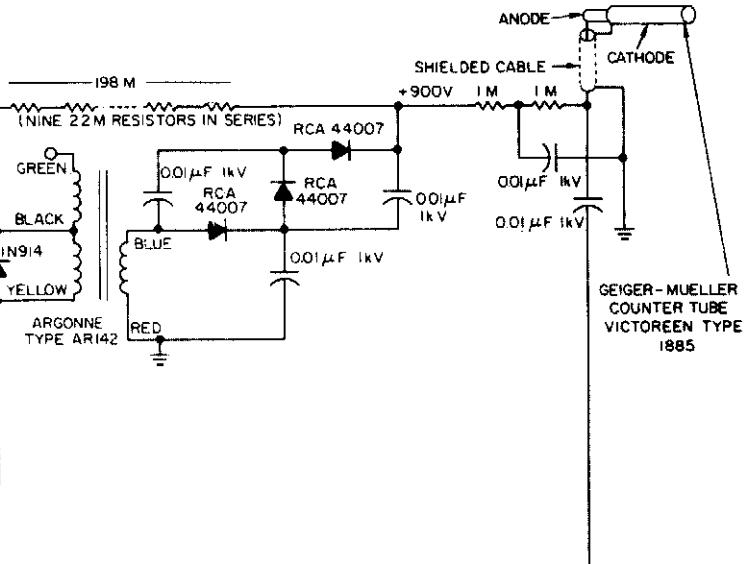

### Circuit Notes

A single 6.75 V mercury battery powers the counter, which features a 1 mA count-rate meter as well as an aural output. A regulated 900 V supply provides stable operation of the counter tube. A multivibrator, built around a differential power amplifier IC2, drives the step-up transformer. Comparator IC1 varies the multivibrator duty cycle to provide a constant 900 V. The entire regulated supply draws less than 2 mA. A one-shot multivibrator, built with IC3, provides output pulses that have constant width and amplitude. Thus the average current through the meter is directly proportional to the pulse-rate output from the counter tube. And the constant-width pulses also drive the speaker. Full-scale meter deflection (1 mA) represents 5000 counts/min, or 83.3 pulses/s. A convenient calibration checkpoint can be provided on the meter scale for 3600 ppm (60 pulses/s.).

### PHOTOMULTIPLIER OUTPUT-GATING CIRCUIT

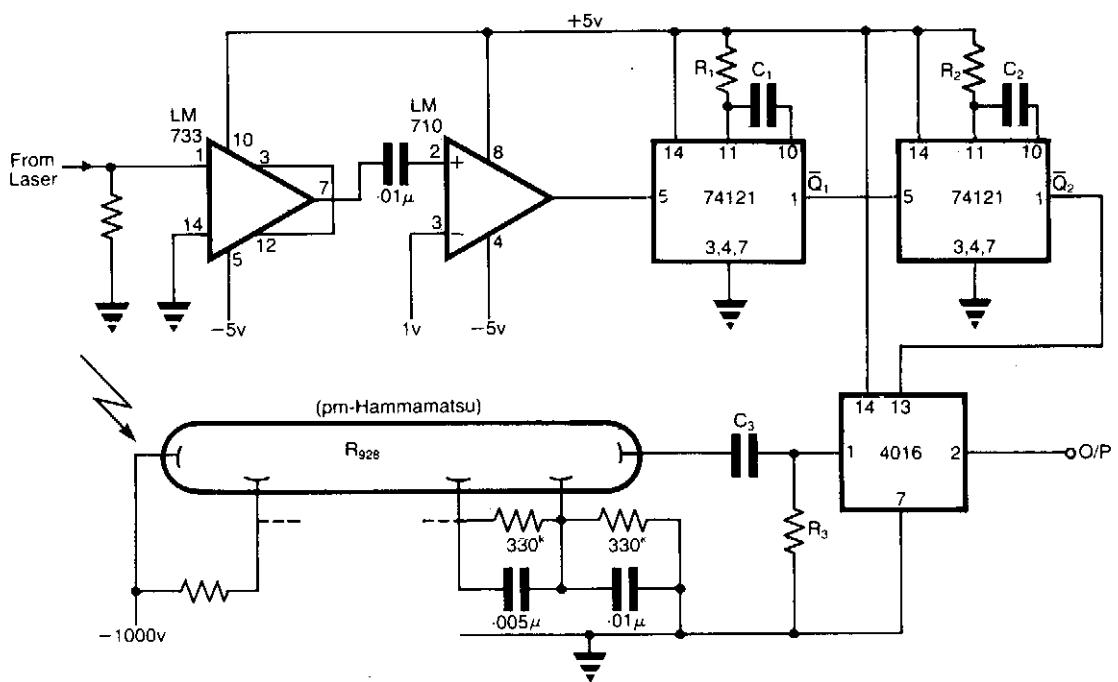

**Fig. 78-3**

ELECTRONIC ENGINEERING

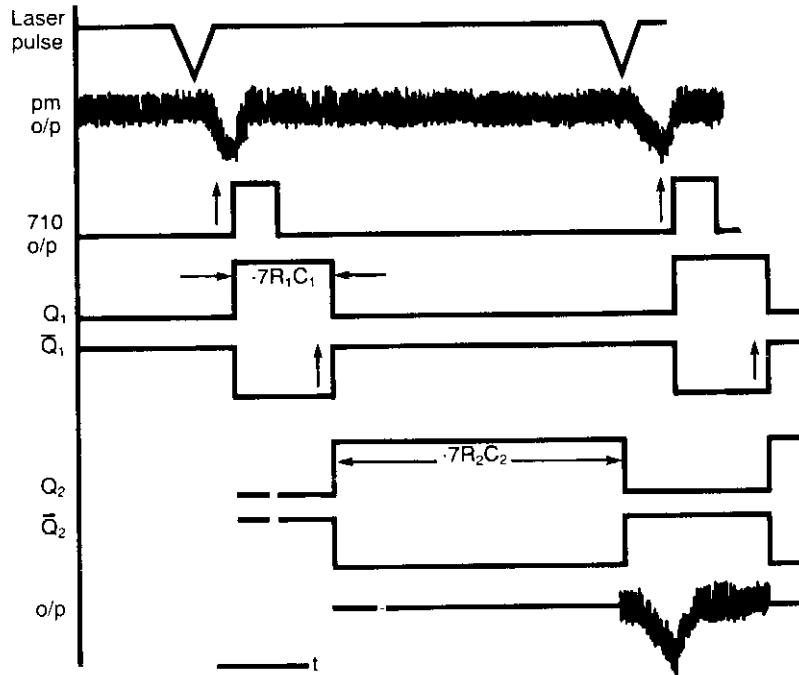


Fig 2

### Circuit Notes

The application involves observing the light pulse emerging from a thick specimen after transillumination by a laser pulse. Pulses derived from the laser source are amplified using a Video Amplifier LM733. The reference level is set to 1 V in the comparator LM 710, to provide the necessary trigger pulses for the monostable multivibrator 74121. The laser pulses have a repetition frequency of 500 Hz and suitable values are as below:

$$R_1 = 33 \text{ k ohm}, C_1 = 22 \text{ pF}$$

$$R_2 = 33 \text{ k ohm}, C_2 = 68 \text{ nF}$$

The pulse width for each monostable is approximately given by  $t_w = 0.7 RC$ . R3 and C3 is a high pass filter. The method therefore permits the use of low cost components having moderate response times for extracting the pulse of interest.

# 79

## Radar Detectors


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

One-Chip Radar Detection Circuit  
Radar Signal Detector

## ONE-CHIP RADAR DETECTION CIRCUIT

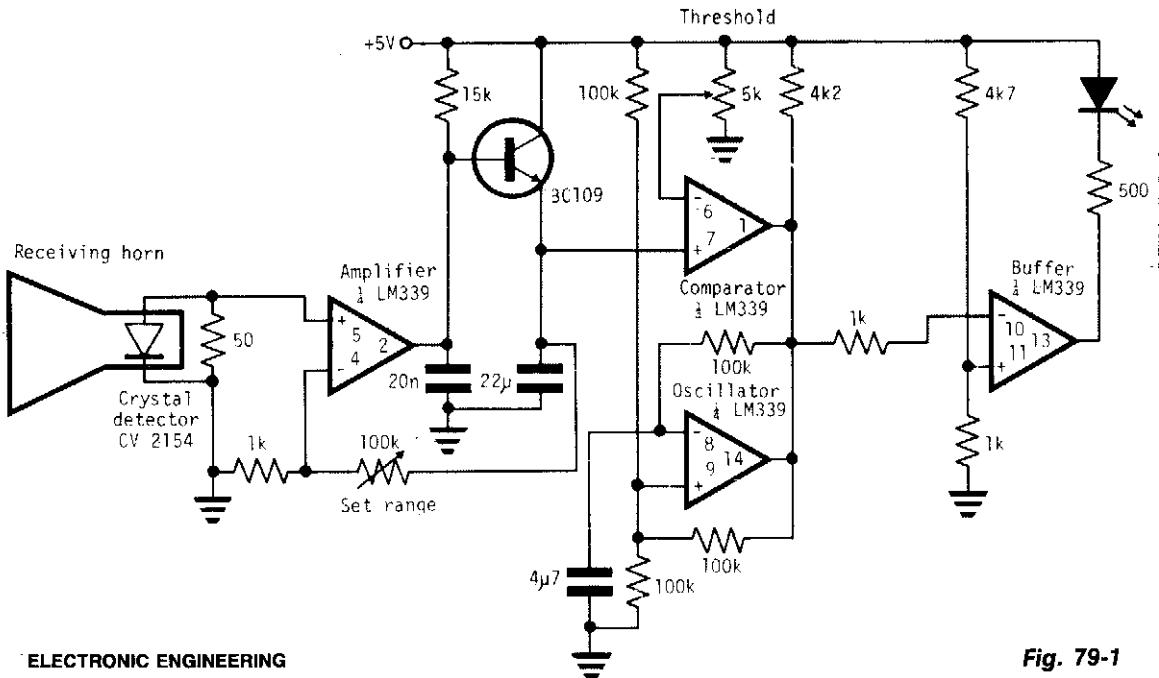

ELECTRONIC ENGINEERING

**Fig. 79-1**

### Circuit Notes

A simple X-band radar detector is capable of indicating changes in rf radiation strength at levels down to 2 mW/cm<sup>2</sup>. Radiation falling on the detector diode, produces a voltage at the input of an amplifier whose gain may be adjusted to vary the range at which the warning is given. The amplifier output drives a voltage comparator with a variable threshold set to a level that avoids false alarms. The comparator output is connected in the wired-OR configuration with the open collector output of an oscillator running at a frequency of 2 Hz. In the absence of a signal, the comparator output level is low, inhibiting the oscillator output stage and holding the buffer so the lamp is off. When a signal appears, the comparator output goes high, removing the lock from the oscillator which free-runs, switching the lamp on and off at 2 Hz.

## RADAR SIGNAL DETECTOR

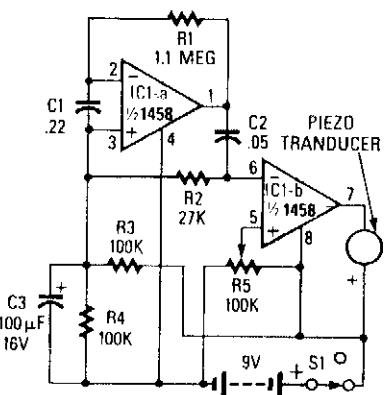


FIG. 1—THE ECONOMY RADAR DETECTOR needs only one IC and a few discrete components.

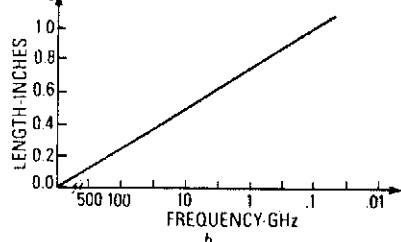
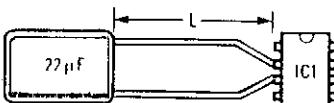


FIG. 3—VARY THE LEAD LENGTHS OF C1 to tune the input circuit.

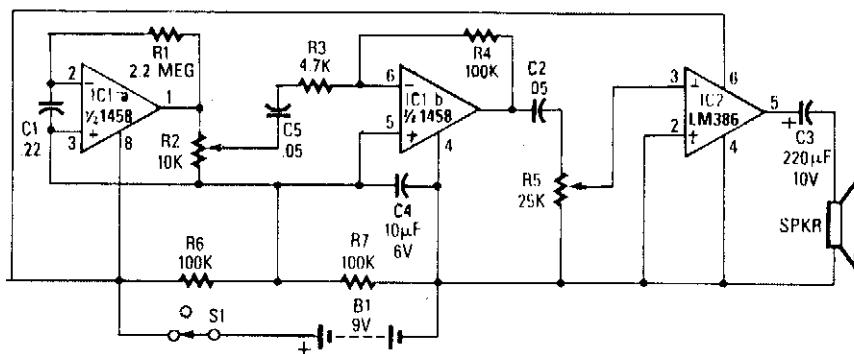


FIG. 2—DELUXE RADAR DETECTOR adds a buffer amplifier and an audio power amp to drive a speaker.

RADIO-ELECTRONICS

*Fig. 79-2*

### Circuit Notes

The circuit can be tuned to respond to signals between 50 MHz and 500 GHz. The economy model is shown in Fig. 1, and the deluxe model is shown in Fig. 2. The first op amp in each circuit functions as a current-to-voltage converter. In the economy model IC1b buffers the output to drive the piezo buzzer. The deluxe model functions in a similar manner except that IC1b is configured as a  $\times 20$  buffer amplifier to drive the LM386. In both circuits C1 functions as a "transmission line" that intercepts the incident radar signal. The response may be optimized by trimming C1's lead length for the desired frequency. Typically the capacitor's leads should be 0.5-0.6 inches long.

# **80**

## **Ramp Generators**


---

---


The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Ramp Generator  
Voltage Controlled Ramp Generator

## RAMP GENERATOR

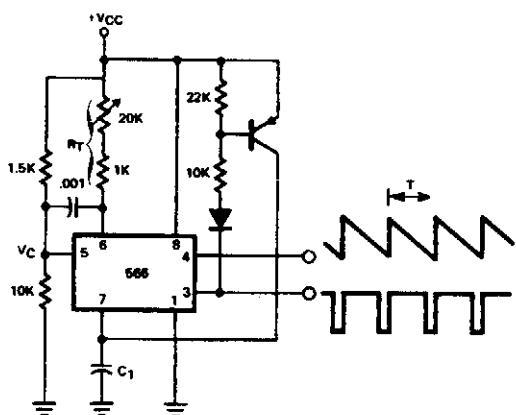

a. Negative Ramp

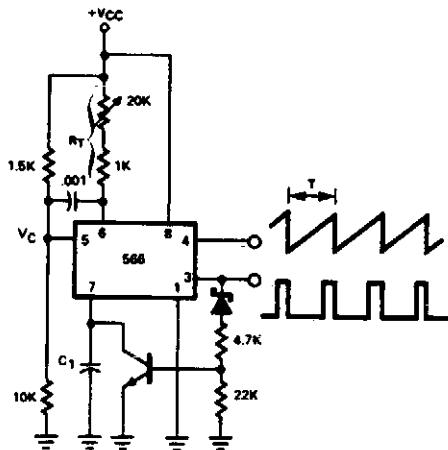

b. Positive Ramp

SIGNETICS

Fig. 80-1

### Circuit Notes

The 566 can be wired as a positive or negative ramp generator. In the positive ramp generator, the external transistor driven by the Pin 3 output rapidly discharges  $C_1$  at the end of the charging period so that charging can resume instantaneously. The pnp transistor of the negative ramp generator likewise rapidly charges the timing capacitor  $C_1$  at the end of the discharge period. Because the circuits are reset so quickly, the temperature stability of the ramp generator is excellent. The period


$$T \text{ is } \frac{1}{2f_o}$$

where  $f_o$  is the 566 free-running frequency in normal operation. Therefore,

$$T = \frac{1}{2f_o} = \frac{R_T C_1 V_{CC}}{5(V_{CC} - V_C)} \quad (1)$$


where  $V_C$  is the bias voltage at Pin 5 and  $R_T$  is the total resistance between Pin 6 and  $V_{CC}$ . Note that a short pulse is available at Pin 3. (Placing collector resistance in series with the external transistor collector will lengthen the pulse.)

## VOLTAGE CONTROLLED RAMP GENERATOR

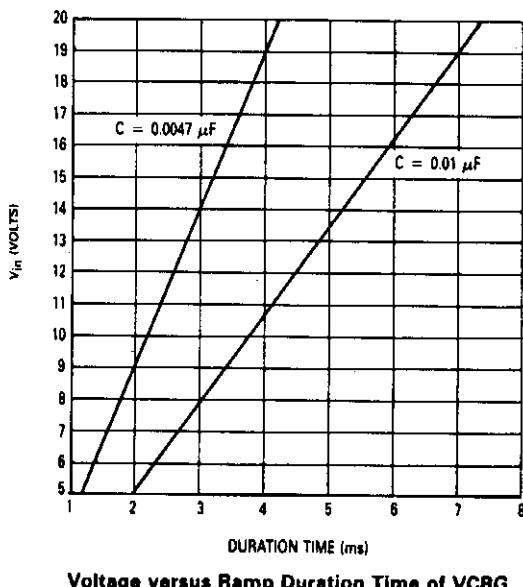

Voltage versus Ramp Duration Time of VCRG

MOTOROLA

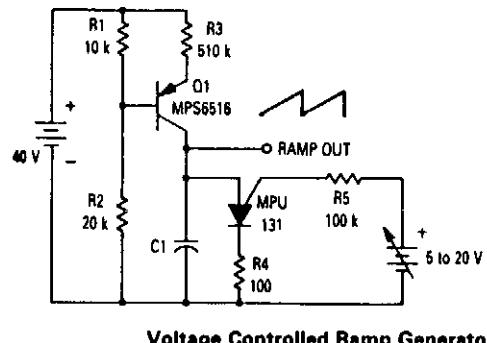

Voltage Controlled Ramp Generator  
(VCRG)

Fig. 80-2

### Circuit Notes

The current source formed by Q1 in conjunction with capacitor C1 set the duration time of the ramp. As the positive dc voltage at the gate is changed, the peak point firing voltage of the PUT is changed, which changes the duration time, i.e., increasing the supply voltage increases the peak point firing voltage causing the duration time to increase.

# **81**

## **Receivers**


---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Car Radio with Capacitive Diode Tuning and  
Electronic MW/LW Switching  
Receiver Monitor  
PLL/BC Receiver
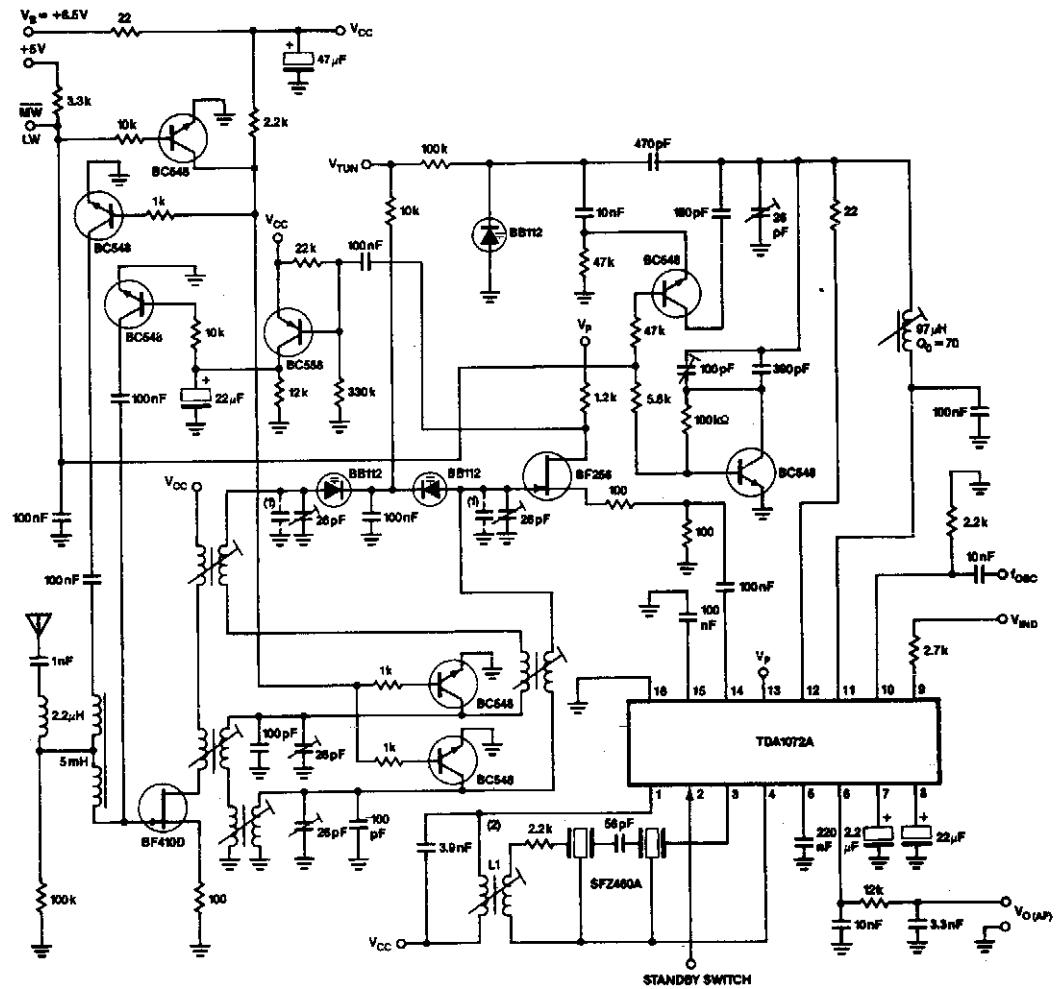
## CAR RADIO WITH CAPACITIVE DIODE TUNING AND ELECTRONIC MW/LW SWITCHING




**NOTES:**

1. Values of capacitors depend on the selected group of capacitive diodes BB112.
2. For IF filter and coil data refer to Block Diagram.
3. The circuit includes pre-stage AGC optimized for good large-signal handling.

SIGNETICS

Fig. 81-1

## RECEIVER MONITOR

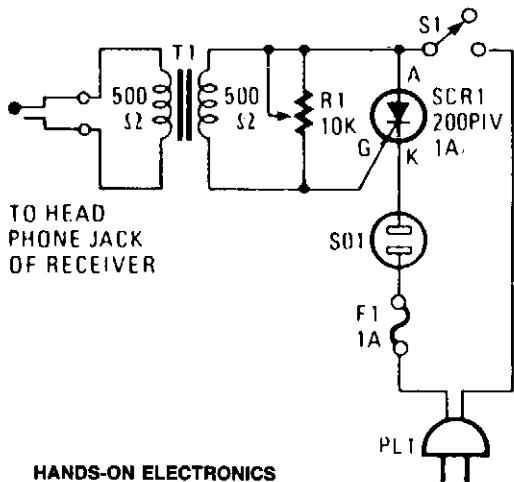


**Fig. 81-2**

## Circuit Notes

The alarm plugs into the earphone jack on a receiver. Then when a signal (normally fed to the headphones) is detected and applied to the gate of SCR1, it conducts, sounding whatever alarm is connected to SO1. The signaling device can be an audible alarm or a lamp. Variable resistor R1 functions as a sensitivity control so that background noises won't trigger the alarm.

## PLL/BC RECEIVER

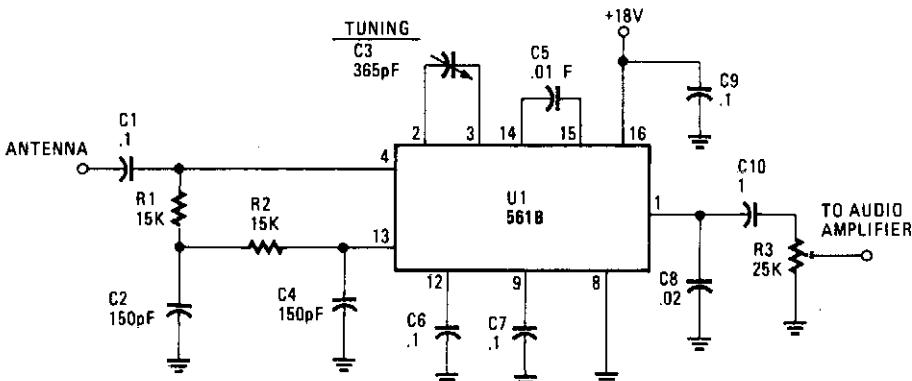

**Fig. 81-3**

## Circuit Notes

This simple AM circuit uses a 561B. There's no inductance/capacitance tuning circuit. The 365 pF capacitor connected between pins 2 and 3 does all the tuning. The circuit needs a good outside antenna and a solid ground. And if you want to further improve operation, stick a broadband amplifier in front of the receiver. Just make sure the input voltage does not climb over 0.5 volt rms.

## **82**

# **Rectifier Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Absolute-Value, "Ideal" Full-Wave Rectifier  
Half-Wave Rectifier
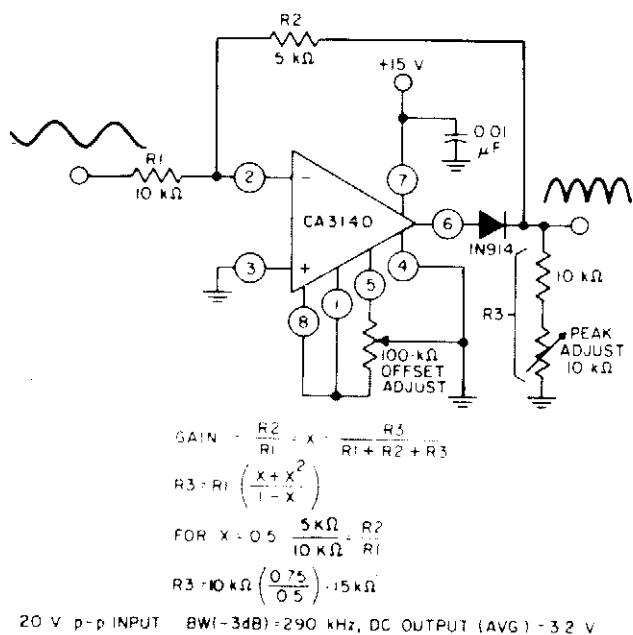
## ABSOLUTE-VALUE, "IDEAL" FULL-WAVE RECTIFIER




GENERAL ELECTRIC /RCA

**Fig. 82-1**

### Circuit Notes

The circuit uses a CA3140 BiMOS op amp in an inverting gain configuration. When equality of two equations shown in satisfied, full-wave output of circuit is symmetrical.

## HALF-WAVE RECTIFIER

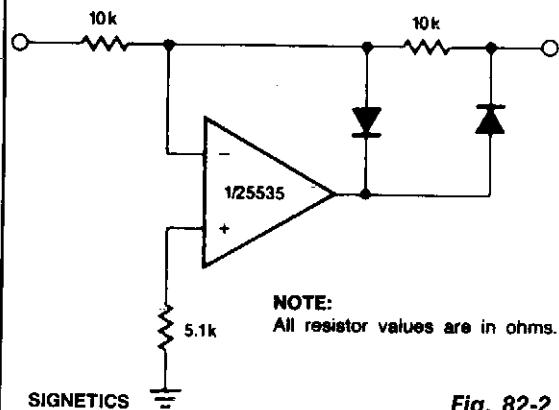

**Fig. 82-2**

### Circuit Notes

The circuit provides for accurate half-wave rectification of the incoming signal. For positive signals, the gain is 0; for negative signals, the gain is -1. By reversing both diodes, the polarity can be inverted. This circuit provides an accurate output, but the output impedance differs for the two input polarities and buffering may be needed. The output must slew through two diode drops when the input polarity reverses. The NE5535 device will work up to 10 kHz with less than 5% distortion.

## **83**

# **Relay Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Relay Driver Provides Delay and Controls Closure Time
- TRIAC Relay-Contact Protection
- TR Circuit

## RELAY DRIVER PROVIDES DELAY AND CONTROLS CLOSURE TIME

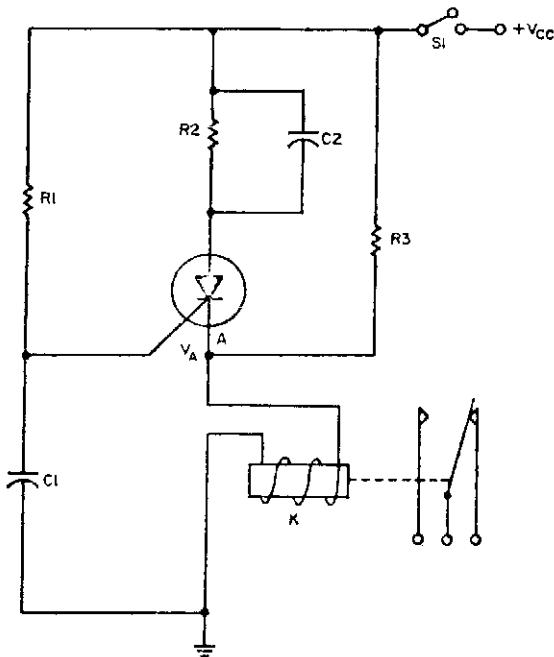



Fig. 83-1

ELECTRONIC DESIGN

### Circuit Notes

The relay operates a certain time,  $t_d$ , after power is applied to it, and then it operates for a length of time,  $t_c$ . The SCR fires when the voltage on C1 reaches  $V_A$ . This operates the relay, which stays activated until the current charging C2 drops below the dropout current. To keep the relay in its activated position indefinitely ( $t_c = \infty$ ), eliminate C2 and choose R2 just large enough to keep the relay coil current within its related limits. Typical component values for  $t_d = 30$  seconds and  $t_c = 2$  seconds are:  $R1 = 1.5$  megohms,  $R2 = 10$  k ohms,  $R3 = 3$  k ohms,  $C1 = 47 \mu F$ , and  $C2 = 100 \mu F$ . The SCR is a 2N1877 and the relay is a Potter Brumfield PW-5374. A value of 12 Vdc is assumed for  $V_{cc}$ .

## TRIAC RELAY-CONTACT PROTECTION

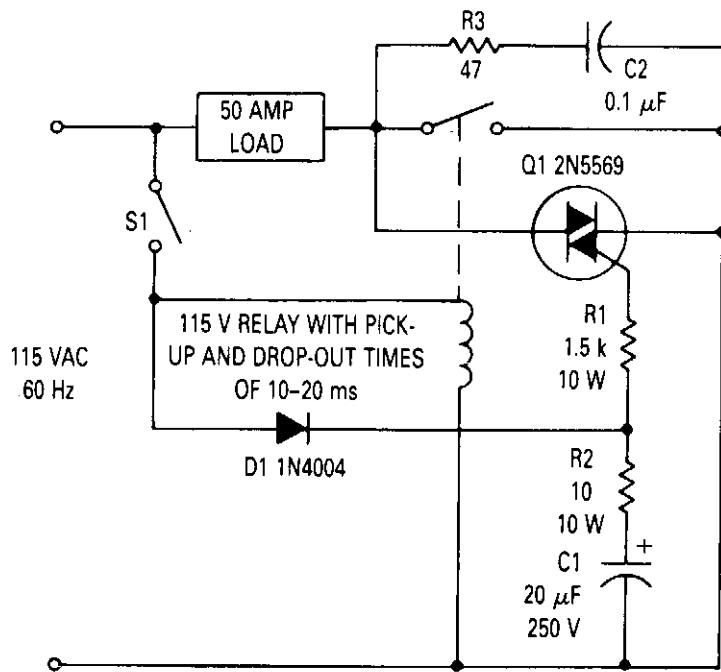

MOTOROLA


**Fig. 83-2**

### Circuit Notes

This circuit can be used to prevent relay contact arcing for loads up to 50 amperes. There is some delay between the time a relay coil is energized and the time the contacts close. There is also a delay between the time the coil is de-energized and the time the contacts open. For the relay used in this circuit both times are about 15 ms. The TRIAC across the relay contacts will turn on as soon as sufficient gate current is present to fire it. This occurs after switch S1 is closed but before the relay contacts close. When the contacts close, the load current passes through them, rather than through the TRIAC, even though the TRIAC is receiving gate current. If S1 should be closed during the negative-half cycle of the ac line, the TRIAC will not turn on immediately but will wait until the voltage begins to go positive, at which time diode D1 conducts providing gate current through R1. The maximum time that could elapse before the TRIAC turns on is 8-1/3 ms for the 60 Hz supply. This is adequate to ensure that the TRIAC will be on before the relay contact closes.

## TR CIRCUIT

EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu\text{F}$ ); OTHERS ARE IN PICOFARADS ( $\text{pF}$ ); RESISTANCES ARE IN OHMS.  $k = 1000$ ,  $M = 1000\,000$ .

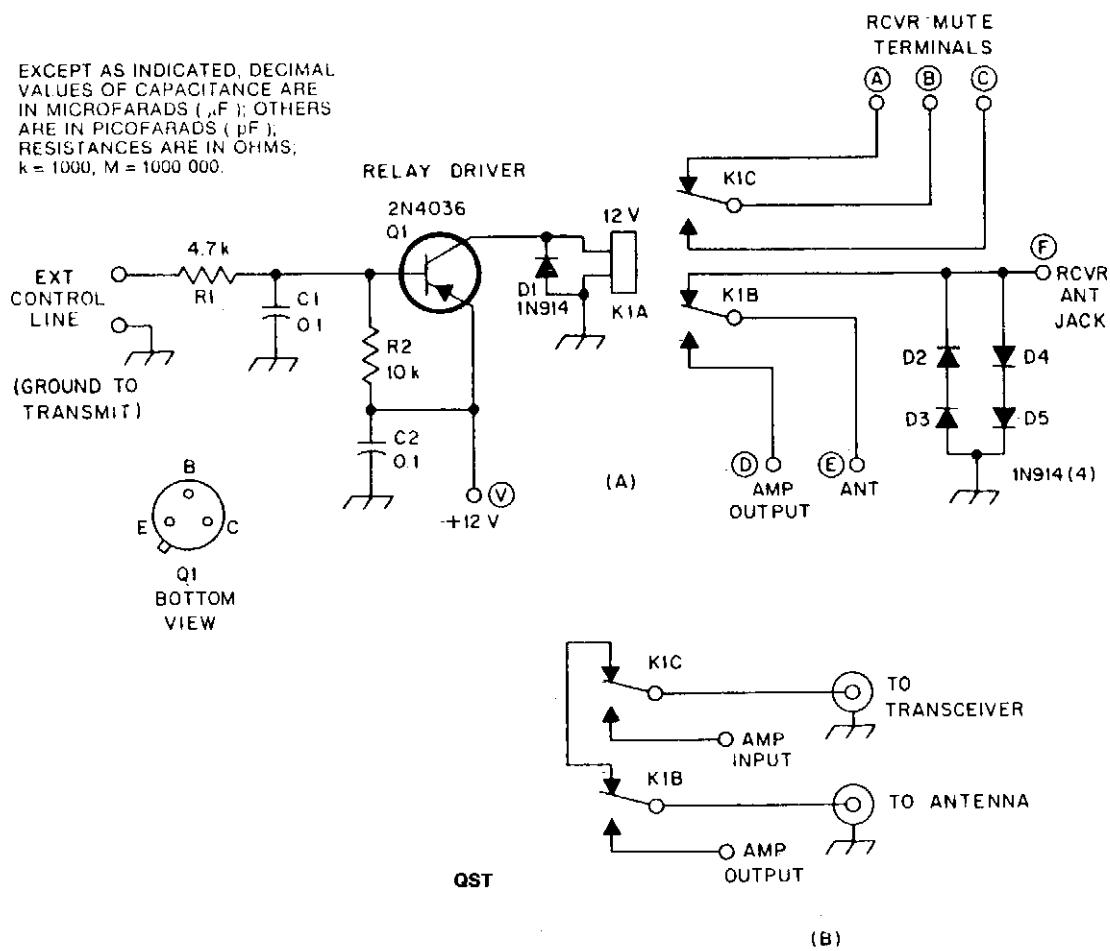

**Fig. 83-3**

### Circuit Notes

C1 and C2 are disc ceramic. R1 and R2 are  $\frac{1}{4}$  or  $\frac{1}{2}$  W carbon composition resistors. K1 is a 12 V DPDT DIP relay. Illustration A shows how to connect the relay contacts for use with a separate transmitter-receiver combination. The circuit at B is for amplifier use with a transceiver.

## **84**

# **Resistance/Continuity Meters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Single Chip Checks Resistance
- Simple Continuity Tester for PCB's
- Simple Continuity Tester
- Adjustable, Audible Continuity Tester for Delicate Circuits

## SINGLE CHIP CHECKS RESISTANCE

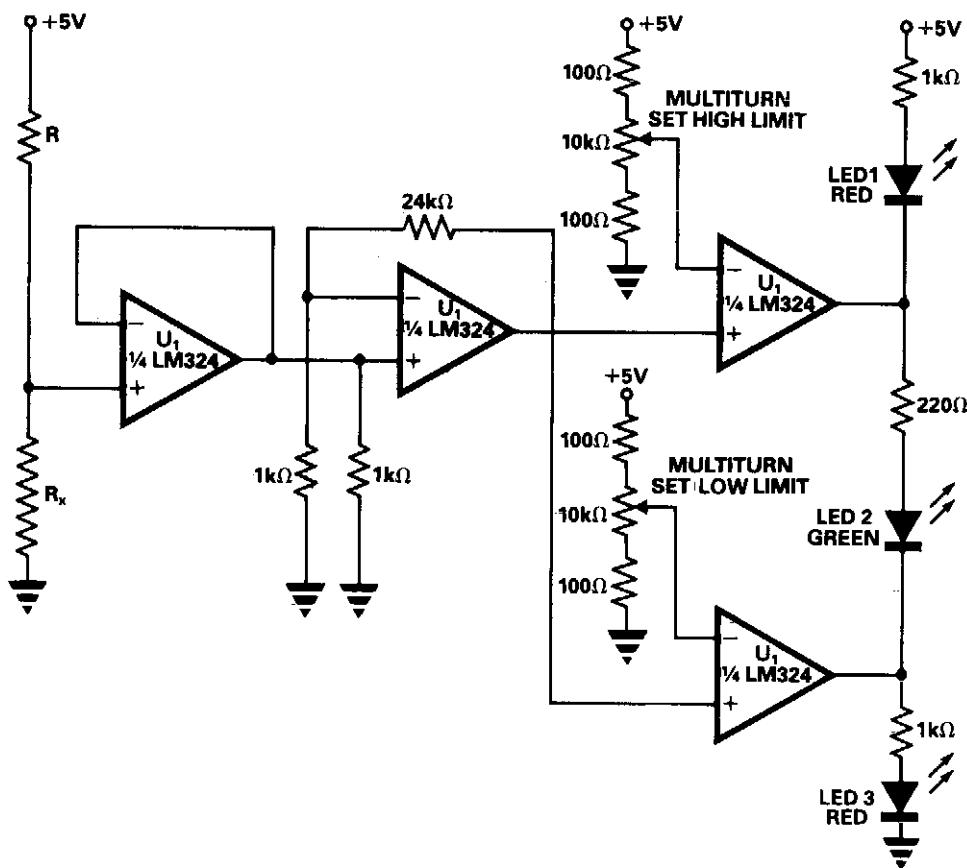


ELECTRONIC ENGINEERING

Fig. 84-1

### Circuit Notes

A simple tester can be used for routine checks for resistance on production lines of relays, coils, or similar components where frequent changes in resistance to be tested are not required. The tester is built around a single quad op amp chip, the LM324.  $R$ , which is chosen to be around 80 times the resistance to be checked, and the  $5V$  supply form the current source. The first op amp buffers the voltage generated across the resistance under test,  $R_x$ . The second op amp amplifies this voltage. The third and fourth op amps compare the amplified voltage with high and low limits. The high and low limits are set on multturn presets with high and low limit resistors connected in place of  $R_x$ . LED 1 (red) lights when the resistance is high. LED 2 (green) shows that the resistance is within limits. LED 3 (red) indicates that the resistance is low.


### SIMPLE CONTINUITY TESTER FOR PCBs

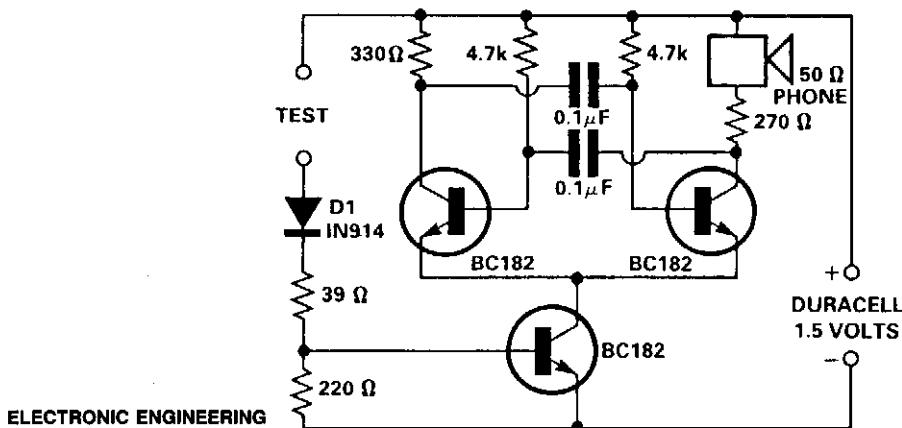

#### Circuit Notes

This tester is for tracing wiring on Printed Circuit Boards. Resistors below 50 ohms act as a short circuit; above 100 ohms as an open circuit. The circuit is a simple multivibrator switched on by transistor T3. The components in the base of T3 are D1, R1, R2, and the test resistance. With a 1.5 volt supply, there is insufficient voltage to turn on a semiconductor connected to the test terminals.


### SIMPLE CONTINUITY TESTER

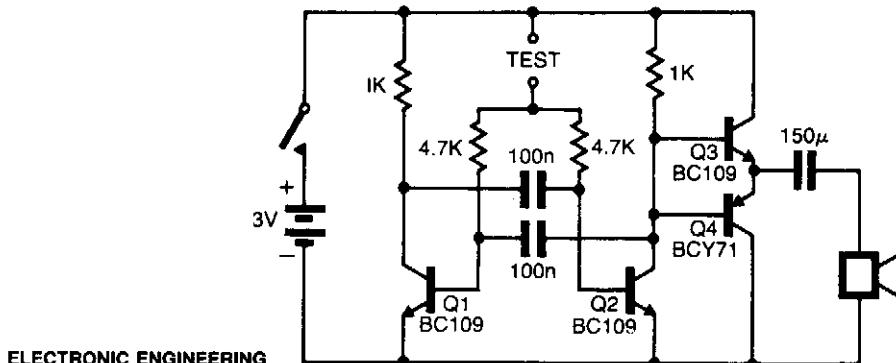

#### Circuit Notes

The pitch of the tone is dependent upon the resistance under test. The tester will respond to resistance of hundreds of kilohms, yet it is possible to distinguish differences of just a few tens of ohms in low-resistance circuits. Q1 and Q2 form a multivibrator, the frequency of which is influenced by the resistance between the test points. The output stage Q3 and Q4 will drive a small loudspeaker or a telephone earpiece.


### SIMPLE CONTINUITY TESTER FOR PCBs

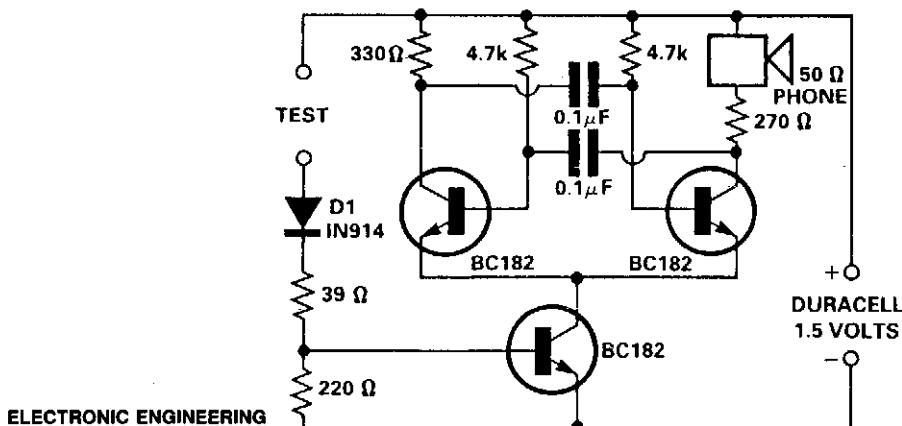

#### Circuit Notes

This tester is for tracing wiring on Printed Circuit Boards. Resistors below 50 ohms act as a short circuit; above 100 ohms as an open circuit. The circuit is a simple multivibrator switched on by transistor T3. The components in the base of T3 are D1, R1, R2, and the test resistance. With a 1.5 volt supply, there is insufficient voltage to turn on a semiconductor connected to the test terminals.


### SIMPLE CONTINUITY TESTER

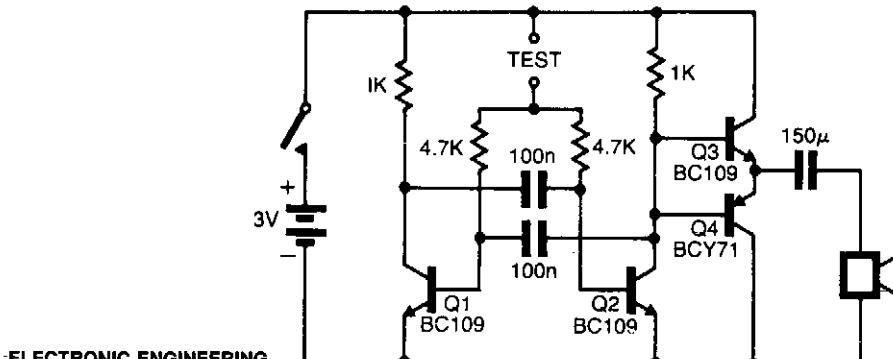

#### Circuit Notes

The pitch of the tone is dependent upon the resistance under test. The tester will respond to resistance of hundreds of kilohms, yet it is possible to distinguish differences of just a few tens of ohms in low-resistance circuits. Q1 and Q2 form a multivibrator, the frequency of which is influenced by the resistance between the test points. The output stage Q3 and Q4 will drive a small loudspeaker or a telephone earpiece.
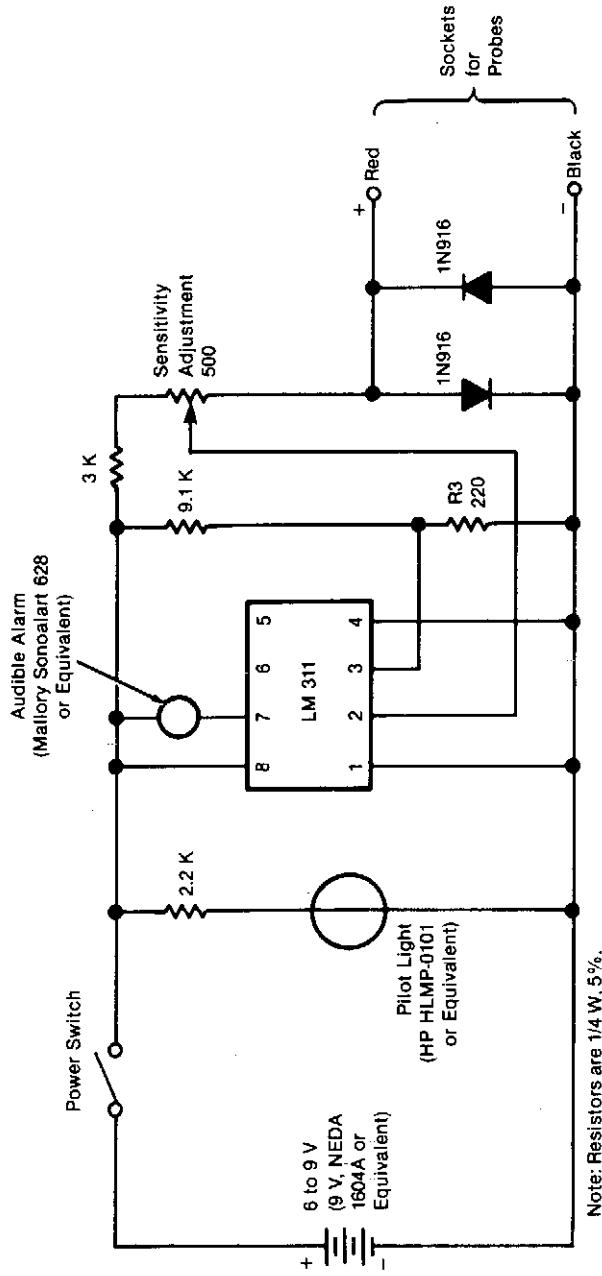
## ADJUSTABLE, AUDIBLE CONTINUITY TESTER FOR DELICATE CIRCUITS



NASA

Fig. 84-4

### Circuit Notes

The tester gives an audible indication, making it unnecessary for the user to look directly at the instrument to observe a meter reading. In addition, the current and voltage of the tester are strictly limited. It can apply no more than 0.6 volts dc and no more than 3 mA through the probes. It can therefore be used safely on circuit boards in which semiconductor components have been installed, and on complementary metal oxide/semiconductor integrated circuits, which are highly susceptible to damage during testing. The tester can be adjusted to indicate continuity below any resistance value up to 35 ohms. For example, if the user sets the tester to 30 ohms, the unit will emit an audible tone whenever the resistance between the probes is 30 ohms or less; if, for example, the resistance is 30.2 ohms, the unit will remain silent.

## **85**

# **RF Amplifiers**

---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low-Distortion 1.6 to 30 MHz SSB Driver

1 Watt, 2.3 GHz Amplifier

5-W RF Power Amplifier

6-Meter Preamplifier Provides 20 dB Gain and Low

NF

125 Watt 150 MHz Amplifier


6-Meter Kilowatt Amplifier

Broadcast-Band RF Amplifier

Improved RF Isolation Amplifier

A 10 Watt 225-400 MHz Amplifier
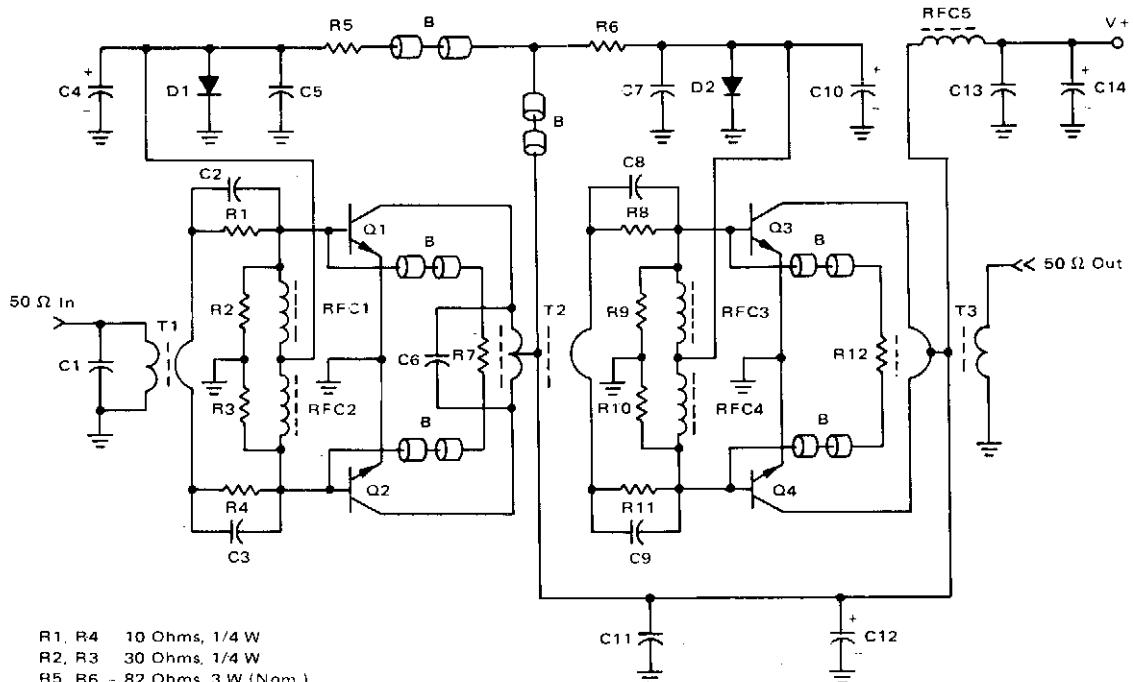
## LOW-DISTORTION 1.6 TO 30 MHz SSB DRIVER



R1, R4 - 10 Ohms, 1/4 W

R2, R3 - 30 Ohms, 1/4 W

R5, R6 - 82 Ohms, 3 W (Nom.)

R7 - 47 Ohms, 1/4 W

R8, R11 - 6.8 Ohms, 1/4 W

R9, R10 - 15 Ohms, 1/4 W

R12 - 130 Ohms, 1/4 W

C1 - 39 pF Dipped Mica

C2, C3 - 680 pF Ceramic Disc

C4, C10 - 220  $\mu$ F, 4 V, Tantalum

C5, C7, C11, C13 - 0.1  $\mu$ F Ceramic Disc

C6 - 56 pF Dipped Mica

C8, C9 - 1200 pF Ceramic Disc

C12, C14 - 10  $\mu$ F, 25 V Tantalum

RFC5 - Ferroxcube VK200 19/4B

RFC1, 2, 3, 4 - 10  $\mu$ H Molded Choke

B - Ferrite Beads (Fair-Rite Prod. Corp. #2643000101 or  
Ferroxcube #56 590 65/3B)

D1, D2 - 1N4001

Q1, Q2 - MRF476

Q3, Q4 - MRF475

T1, T2 - 4:1 Impedance Transformer

T3 - 1:4 Impedance Transformer


**MOTOROLA**

**Fig. 85-1**

### **Circuit Notes**

The amplifier provides a total power gain of about 25 dB, and the construction technique allows the use of inexpensive components throughout. The MRF476 is specified as a 3 watt device and the MRF475 has an output power of 12 watts. Both are extremely tolerant to overdrive and load mismatches, even under CW conditions. Typical IMD numbers are better than -35 dB, and the power gains are 18 dB and 12 dB, respectively, at 30 MHz. The bias currents of each stage are individually adjustable with R5 and R6. Capacitors C4 and C10 function as audio-frequency bypasses to further reduce the source impedance at the frequencies of modulation. Gain leveling across the band is achieved with simple RC networks in series with the bases, in conjunction with negative feedback. The amplitude of the out-of-phase voltages at the bases is inversely proportional to the frequency as a result of the series inductance in the feedback loop and the increasing input impedance of the transistor at low frequencies. Conversely, the negative feedback lowers the effective input impedance presented to the source (not the input impedance of the device itself) and with proper voltage slope would equalize it. With this technique, it is possible to maintain an input VSWR of 1.5:1 or less than 1.6 to 30 MHz.

## 1 WATT, 2.3 GHz AMPLIFIER

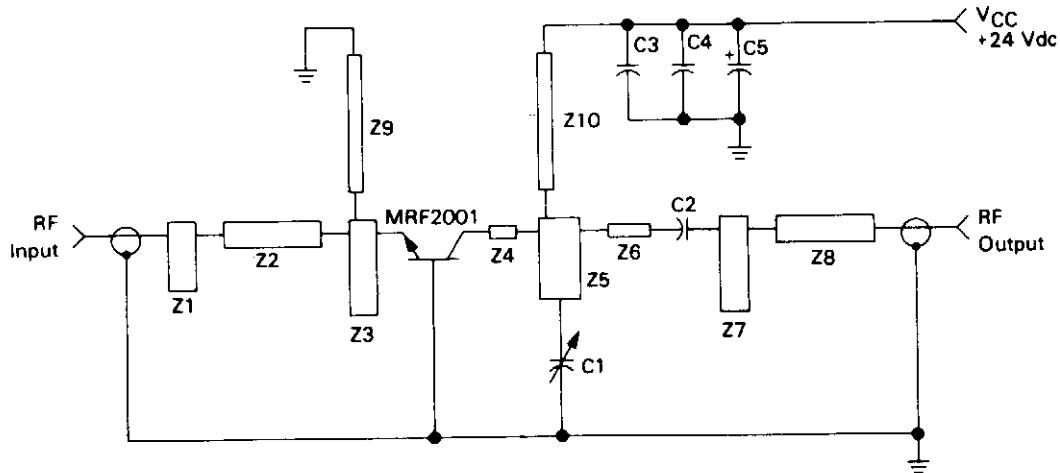

C1 — 0.4–2.5 pF Johanson 7285\*

C2, C3 — 68 pF, 50 mil ATC\*\*

C4 — 0.1  $\mu$ F, 50 V

C5 — 4.7  $\mu$ F, 50 V Tantalum

Z1-Z10 — Microstrip; see Photomaster, Figure 3

Board Material — 0.0625" 3M Glass Teflon.\*\*\*

$\epsilon_r = 2.5 \pm 0.05$

\*Johanson Manufacturing Corp., 400 Rockaway Valley Road, Boonton, NJ 07005

\*\*American Technical Ceramics, One Norden Lane, Huntington Station, NY 11746

\*\*\*Registered Trademark of Du Pont


MOTOROLA

Fig. 85-2

### **Circuit Notes**

Simplicity and repeatability are featured in this 1 watt S-band amplifier design. The design uses an MRF2001 transistor as a common base, Class C amplifier. The amplifier delivers 1 watt output with 8 dB minimum gain at 24 V, and is tunable from 2.25 to 2.35 GHz. Applications include microwave communications equipment and other systems requiring medium power, narrow band amplification. The amplifier circuitry consists almost entirely of distributed microstrip elements. A total of six additional components, including the MRF2001, are required to build a working amplifier. The input and output impedances of the transistor are matched to 50 ohms by double section low pass networks. The networks are designed to provide about 3% 1 dB power bandwidth while maintaining a collector efficiency of approximately 30%. There is one tuning adjustment in the amplifier—C1 in the output network. Ceramic chip capacitors, C2 and C3, are used for dc blocking and power supply decoupling. Additional low frequency decoupling is provided by capacitors C4 and C5.

## 5-W RF POWER AMPLIFIER

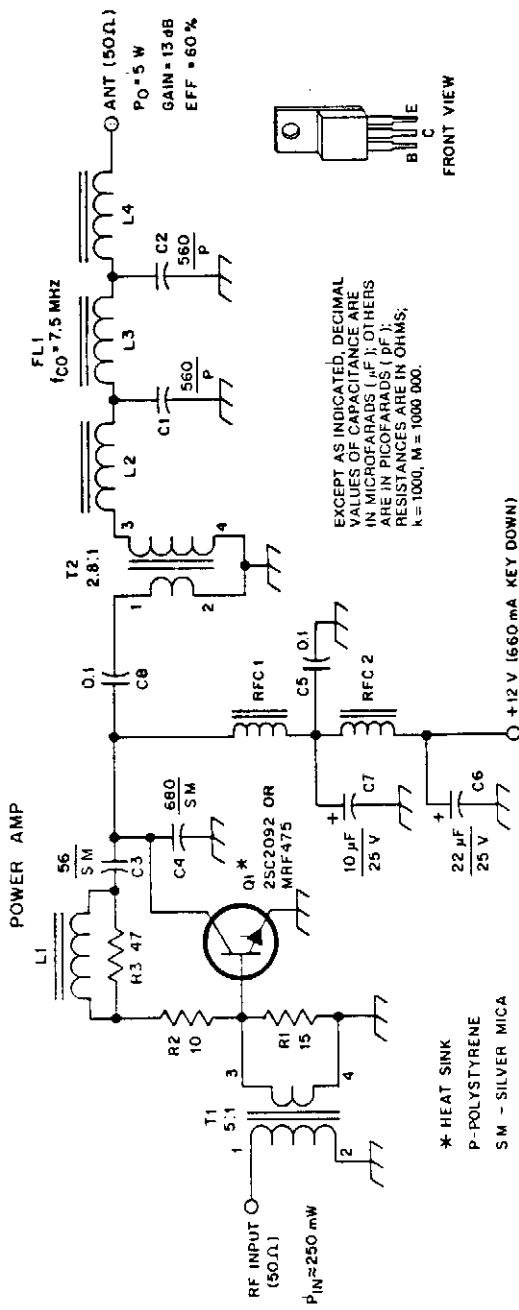

L1—0.22- $\mu\text{H}$  inductor. Small RF choke or 8 turns of no. 24 enam wire on an Amidon T-37-6 toroid.  
L2, L4—0.8- $\mu\text{H}$  inductor. 12 turns of no. 24 enam wire on an Amidon T-50-2 toroid.  
L3—1.67- $\mu\text{H}$  inductor. 18 turns of no. 24 enam wire on an Amidon T-50-2 toroid.

RFC1—2.8- $\mu\text{H}$  choke. 24 turns of no. 26 enam wire on an Amidon T-50-2 toroid.  
RFC2—42- $\mu\text{H}$  choke. 10 turns of no. 26 enam wire on an Amidon FT-37-43 toroid.  
T1—Primary has 16 turns of no. 26 enam wire on an Amidon FT-37-43 toroid.


Secondary has 6 turns of no. 26 enam wire.  
T2—Primary (Q1 side) has 9 turns of no. 24 enam wire on an Amidon FT-50-43 toroid. Secondary has 15 turns of no. 24 enam wire.

Fig. 85-3

### Circuit Notes

Numbered components are so designated for PC-board layout purposes. C5 and C8 are disc ceramic. C6 and C7 are tantalum or electrolytic. R1, R2 and R3 are  $1/2$  W carbon composition resistors. Silver-mica capacitors may be substituted for polystyrene (P) types. Impedance transformation ratios are shown above T1 and T2.
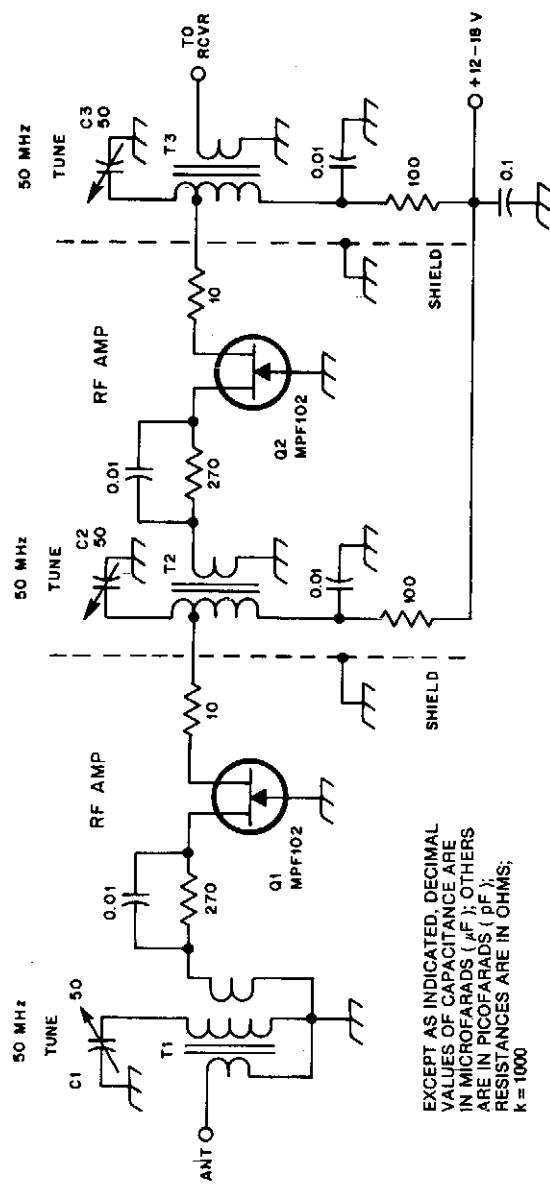
### 6-METER PREAMPLIFIER PROVIDES 20 dB GAIN AND LOW NF




QST

Fig. 85-4

#### Circuit Notes

C1, C2, and C3 are miniature ceramic or plastic trimmers. T1 (main winding) is 0.34  $\mu\text{H}$ . Use of 11 turns of no. 24 enameled wire on a T37-10 toroid core. The antenna winding has one turn, and Q1 the source winding has three turns. T2 primary consists of 11 turns of no. 24 enameled wire on a T37-10 toroid. Tap Q1 drain is three turns from C2 the end of the winding. The secondary has three turns. T3 is the same as T2, except its secondary has one turn.

## 125 WATT 150 MHz AMPLIFIER

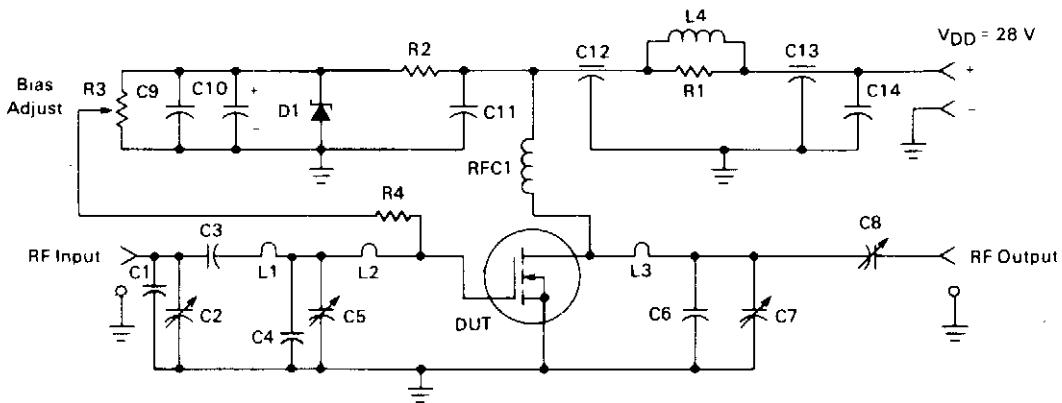

C1 — 35 pF Unilco  
 C2, C5 — Arco 462, 5-80 pF  
 C3 — 100 pF Unilco  
 C4 — 25 pF Unilco  
 C6 — 40 pF Unilco  
 C7 — Arco 461, 2.7-30 pF  
 C8 — Arco 463, 9-180 pF  
 C9, C11, C14 — 0.1  $\mu$ F Erie Redcap  
 C10 — 50  $\mu$ F, 50 V  
 C12, C13 — 680 pF Feedthru  
 D1 — 1N5925A Motorola Zener

L1 — #16 AWG, 1-1/4 Turns, 0.213" ID  
 L2 — #16 AWG, Hairpin, 0.25"  
 L3 — #14 AWG, Hairpin, 0.47", 0.062"  
 L4 — 10 Turns #16 AWG Enamelled Wire on R1  
 RFC1 — 18 Turns #16 AWG Enamelled Wire, 0.3" ID  
 R1 — 10  $\Omega$ , 2.0 W  
 R2 — 1.8 k $\Omega$ , 1/2 W  
 R3 — 10 k $\Omega$ , 10 Turn Bourns  
 R4 — 10 k $\Omega$ , 1/4 W

MOTOROLA

**Fig. 85-5**

### Circuit Notes

This amplifier operates from a 28 Vdc supply. It has a typical gain of 12 dB, and can survive operation into a 30:1 VSWR load at any phase angle with no damage. The amplifier has an AGC range in excess of 20 dB. This means that with input power held constant at the level that provides 125 watts output, the output power may be reduced to less than 1.0 watt continuously by driving the dc gate voltage negative from its  $I_{DQ}$  value.

## 6-METER KILOWATT AMPLIFIER

### Circuit Notes

The amplifier uses a grounded grid circuit with either the Eimac 3CX1000A7 or 8877, ceramic/metal triodes intended for linear service in the HF and VHF ranges. The amp provides the legal power output of 1500 watts PEP and CW service with no effort and requires a driver delivering between 50 and 80 watts at 50 MHz. With a plate voltage of 3000 volts at 0.8 amps the amplifier performs at 60 percent efficiency. The grid is grounded by means of the grid ring of the 3CX1000A7 socket providing a low-inductance path to ground. The amplifier is completely stable.


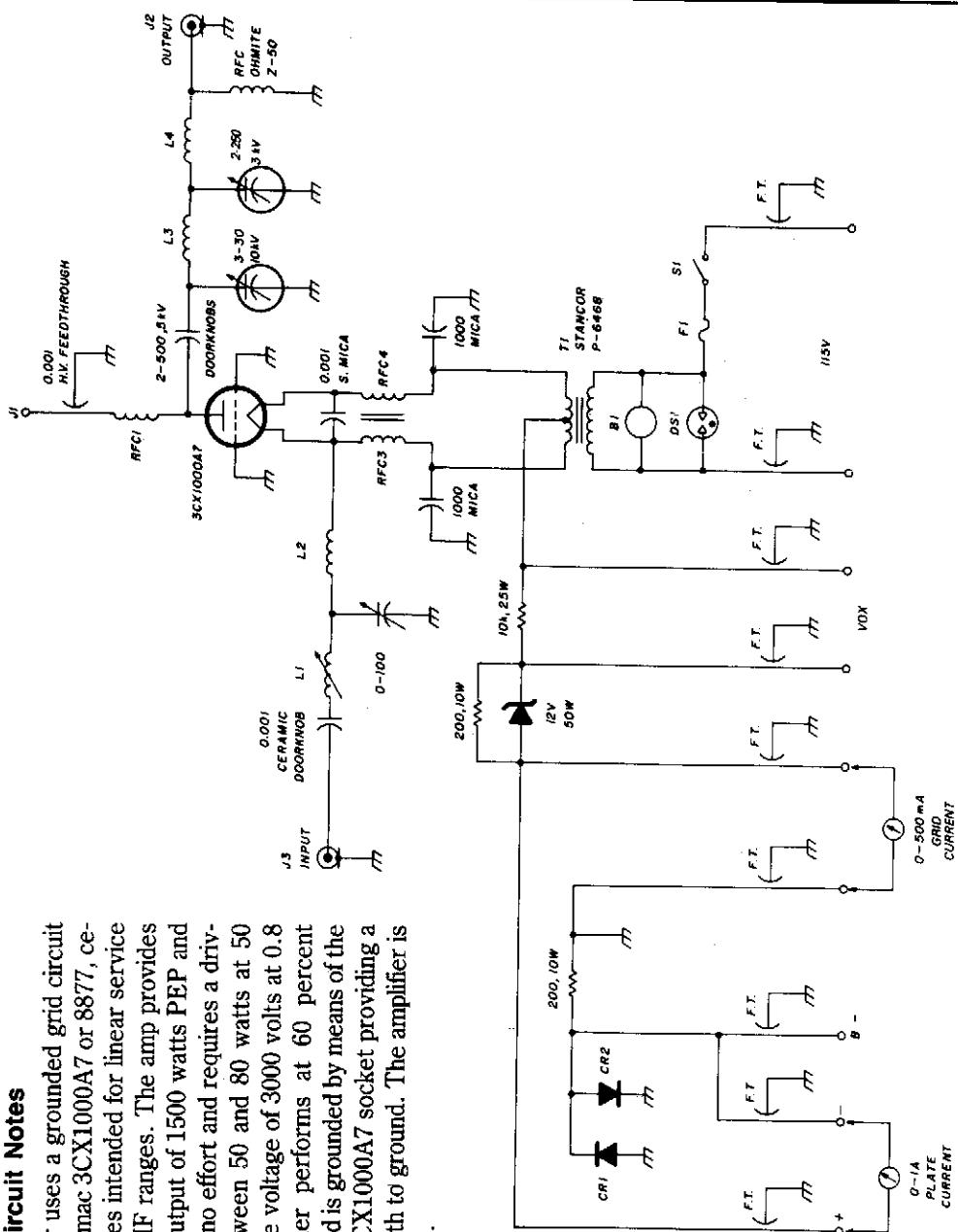


Fig. 85-6

## BROADCAST-BAND RF AMPLIFIER

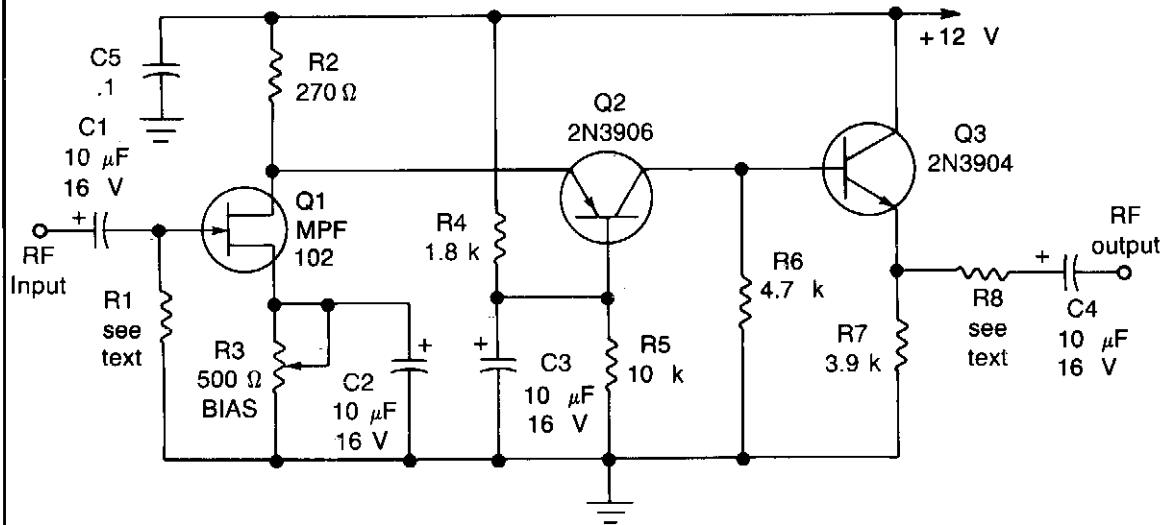


RADIO-ELECTRONICS

*Fig. 85-7*

### Circuit Notes

The circuit has a frequency response ranging from 100 Hz to 3 MHz; gain is about 30 dB. Field-effect transistor Q1 is configured in the common-source self-biased mode; optional resistor R1 sets the input impedance to any desired value. Commonly, it will be 50 ohms. The signal is then direct-coupled to Q2, a common-base circuit that isolates the input and output stages and provides the amplifier's exceptional stability. Q3 functions as an emitter follower, to provide low output impedance (about 50 ohms). For higher output impedance, include resistor R8. It will affect impedance according to this formula:  $R_8 \sim R_{out} - 50$ . Otherwise, connect output capacitor C4 directly to the emitter of Q3.

## IMPROVED RF ISOLATION AMPLIFIER

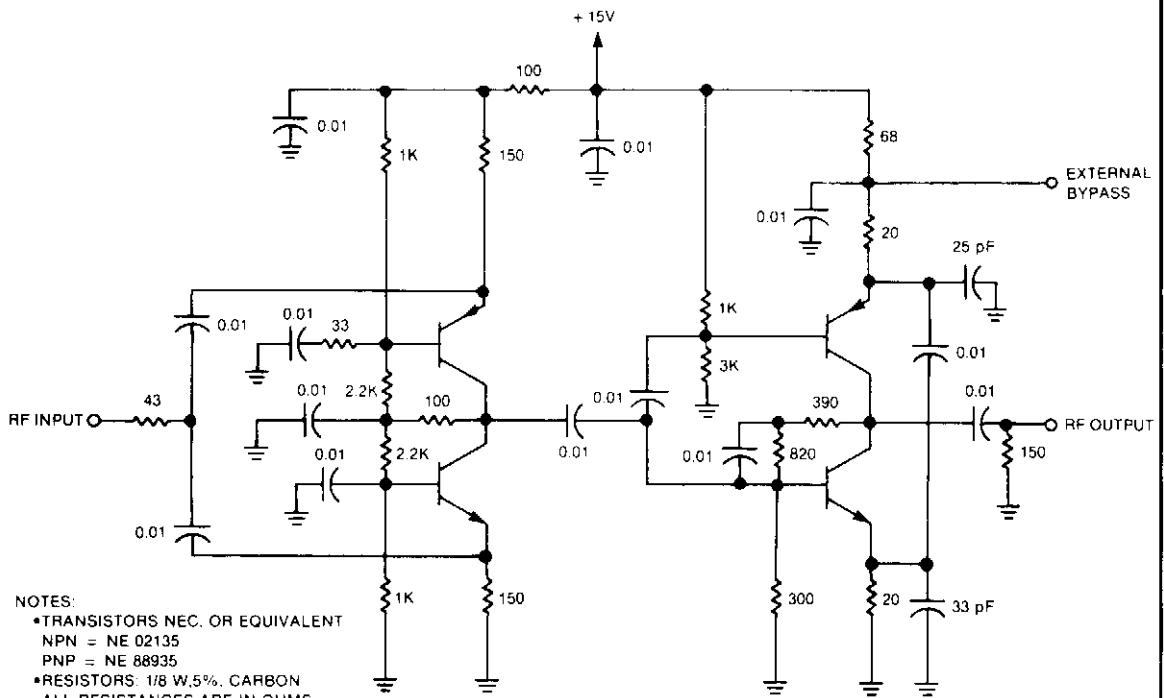


NASA

**Fig. 85-8**

### Circuit Notes

This wideband RF isolation amplifier has a frequency response of 0.5 to 400 MHz  $\pm$  0.5 dB. This two stage amplifier can be used in applications requiring high reverse isolation, such as receiver intermediate-frequency (IF) strips and frequency distribution systems. Both stages use complementary-symmetry transistor arrangements. The input stage is a common-base connection for the complementary circuit. The output stage, which supplies the positive gain, is a common-emitter circuit using emitter degeneration and collector-base feedback for impedance control.

## A 10 WATT 225-400 MHz AMPLIFIER

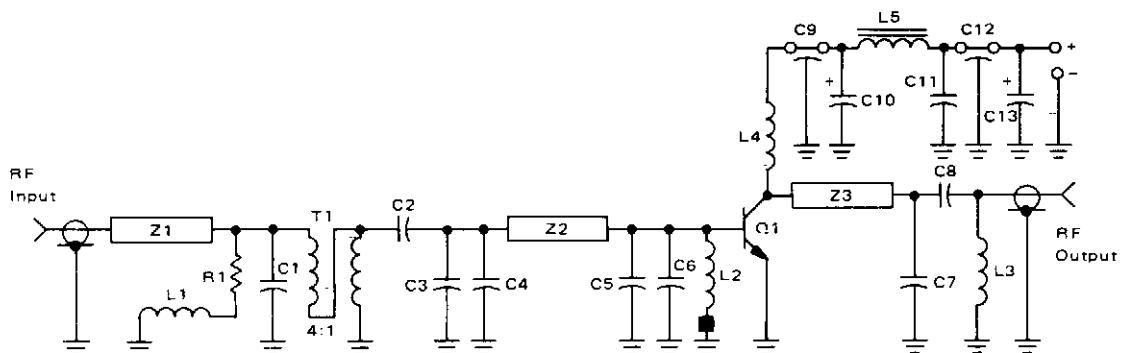

C1 - 8.2 pF Chip\*

C2 - 270 pF Chip\*

C3 - 36 pF Chip\*

C4, C7 - 15 pF Chip\*

C5, C6 - 50 pF Chip\*

C8 - 82 pF Chip\*

C9, C12 - 680 pF Feedthru

C10, C13 - 1.0  $\mu$ F 50 V Tantalum

C11 - 0.1  $\mu$ F Erie Redcap

L1, L3 - 3 Turns #22 AWG 1/8" (3.175 mm) ID

L2 - 0.15  $\mu$ H Molded Choke

L4 - 0.15  $\mu$ H Molded Choke with Ferroxcube Bead  
(Ferroxcube 56 590-65/4B on Ground End  
of Choke)

L5 - Ferroxcube VK200-19/4B

\*100 mil A.C.I. Chip Capacitors

**MOTOROLA**

R1 - 36  $\Omega$  1/4 Watt

T1 - 25  $\Omega$  Subminiature Coax (Type UT34 25) -  
1.75 inches (44.45 mm) long

Z1 - Microstrip Line

720 mils L X 162 mils W  
18.29 mm L X 4.115 mm W

Z2 - Microstrip Line

680 mils L X 162 mils W  
17.27 mm L X 4.115 mm W

Z3 - Microstrip Line


2200 mils L X 50 mils W  
55.88 mm L X 1.27 mm W

Board - 0.0625" (1.588 mm) Glass Teflon,  
 $\epsilon_r = 2.56$

Q1 - MRF331


**Fig. 85-9**

### SCHEMATIC REPRESENTATION

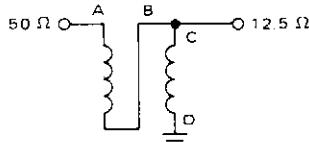

### ASSEMBLY AND PICTORIAL

Transformer Dimensions  
(not to scale)

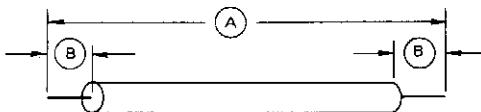


(A) - 1.75 inches (4.445 cm)

(B) - 0.1875 inch (0.476 cm)

## A 10 WATT 225-400 MHz AMPLIFIER, Continued.

Transformer Connections

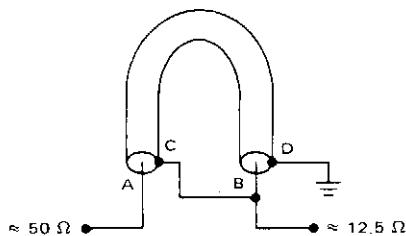

### Circuit Notes

This broadband amplifier covers the 225-400 MHz military communications band producing 10 watt RF output power and operating from a 28 volt supply. The amplifier can be used as a driver for higher power devices such as 2N6439 and MRF327. The circuit is designed to be driven by a 50 ohm source and operate into a nominal 50 ohm load. The input matching network consists of a section composed of C3, C4, Z2, C5 and C6. C2 is a dc blocking capacitor, and T1 is a 4:1 impedance ratio coaxial transformer. Z1 is a 50 ohm transmission line. A compensation network consisting of R1, C1, and L1 is used to improve the input VSWR and flatten the gain response of the amplifier. L2 and a small ferrite bead make up the base bias choke. The output network is made up of a microstrip L-section consisting of Z3 and C7, and a high pass section consisting of C8 and L3. C8 also serves as a dc blocking capacitor. Collector decoupling is accomplished through the use of L4, L5, C9, C10, C11, C12, and C13.

# **86**

## **RF Oscillators**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

5 MHz VFO

## 5 MHz VFO

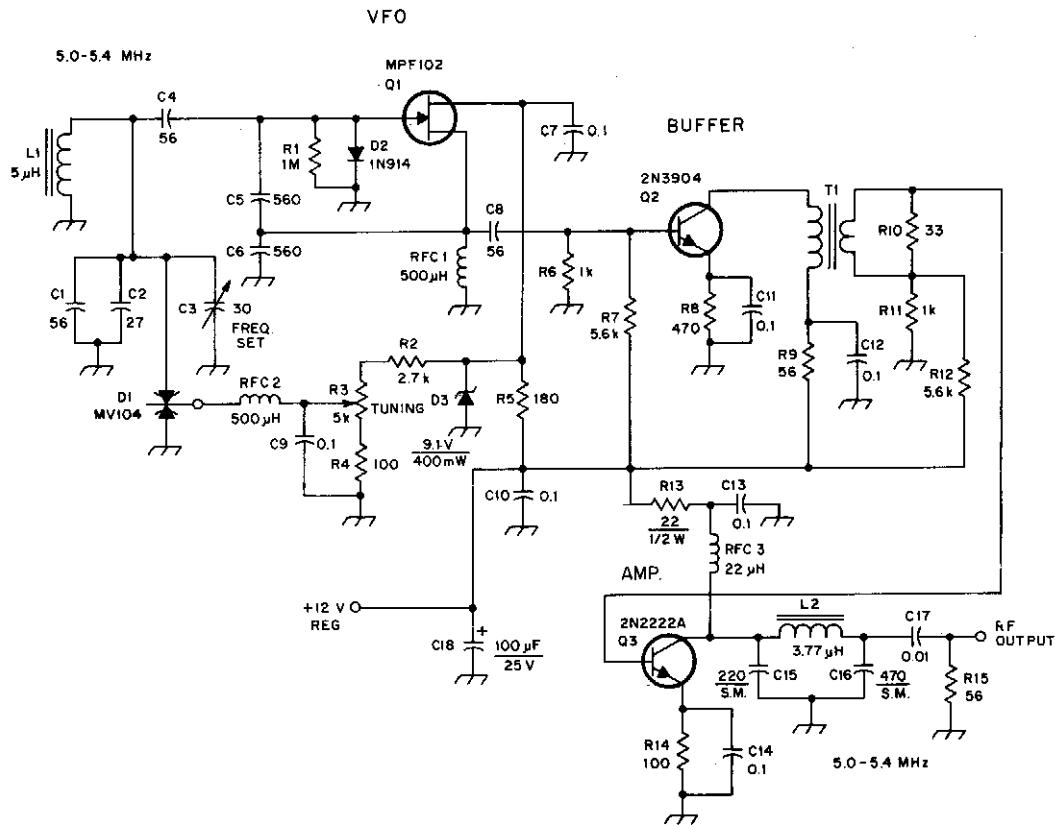

QST

**Fig. 86-1**

### Circuit Notes

A JFET (Q1) serves as the oscillator. D2 helps to stabilize the transistor by limiting positive sinewave peaks and stabilizing the bias. Output from Q1 is supplied to a class A buffer, Q2. It operates as a broadband amplifier by means of T1, which is untuned. Output amplifier Q3 is also a class A stage. A low-pass, single-section filter is used at the output of Q3 to remove some of the harmonic currents generated within the system. The filter output impedance is 50 ohms. The injection level to the mixer is 600 mV p-p.

# 87

## Sample-and-Hold Circuits



---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Sample-and-Hold Circuit
- Sample and Hold Circuit II
- Fast, Precision Sample-Hold
- High Performance Sample and Hold
- Infinite Sample and Hold Amplifier
- Charge Compensated Sample and Hold

## SAMPLE-AND-HOLD CIRCUIT

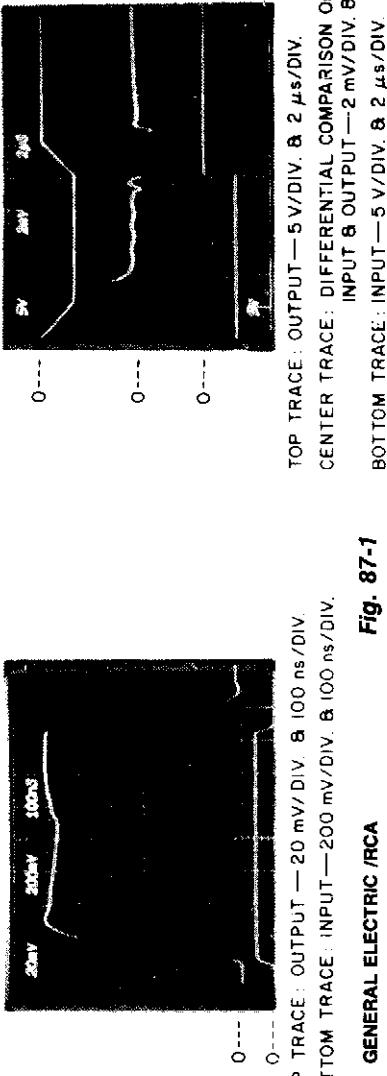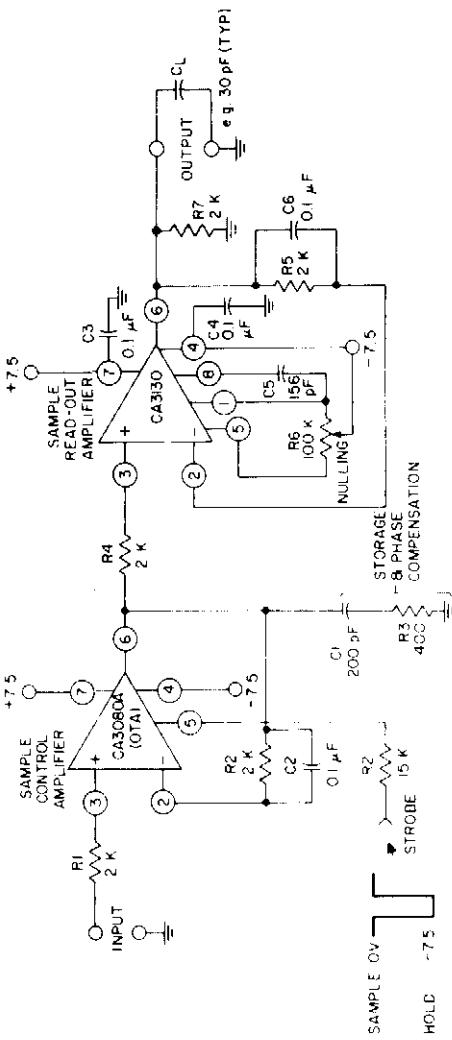

GENERAL ELECTRIC /RCA

Fig. 87-1

## Circuit Notes

The circuit uses a CA3130 BiMOS op amp as the sample-readout amplifier for the storage (sample-holding) capacitor C1, and a CA3080A as the sample-control amplifier. Applications in linear systems to temporarily store analog data include DVM systems, industrial process-control, multiplex systems, and A-D converters.

## SAMPLE AND HOLD CIRCUIT II


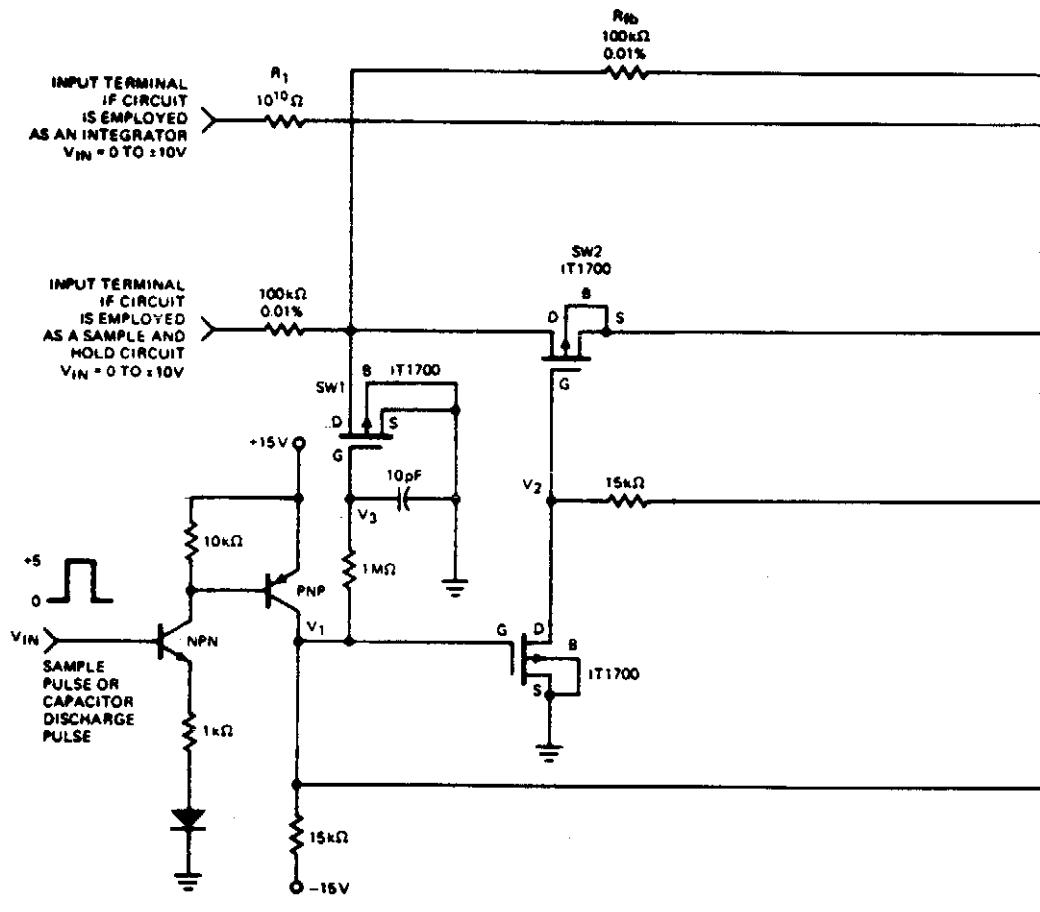


Fig. 87-2
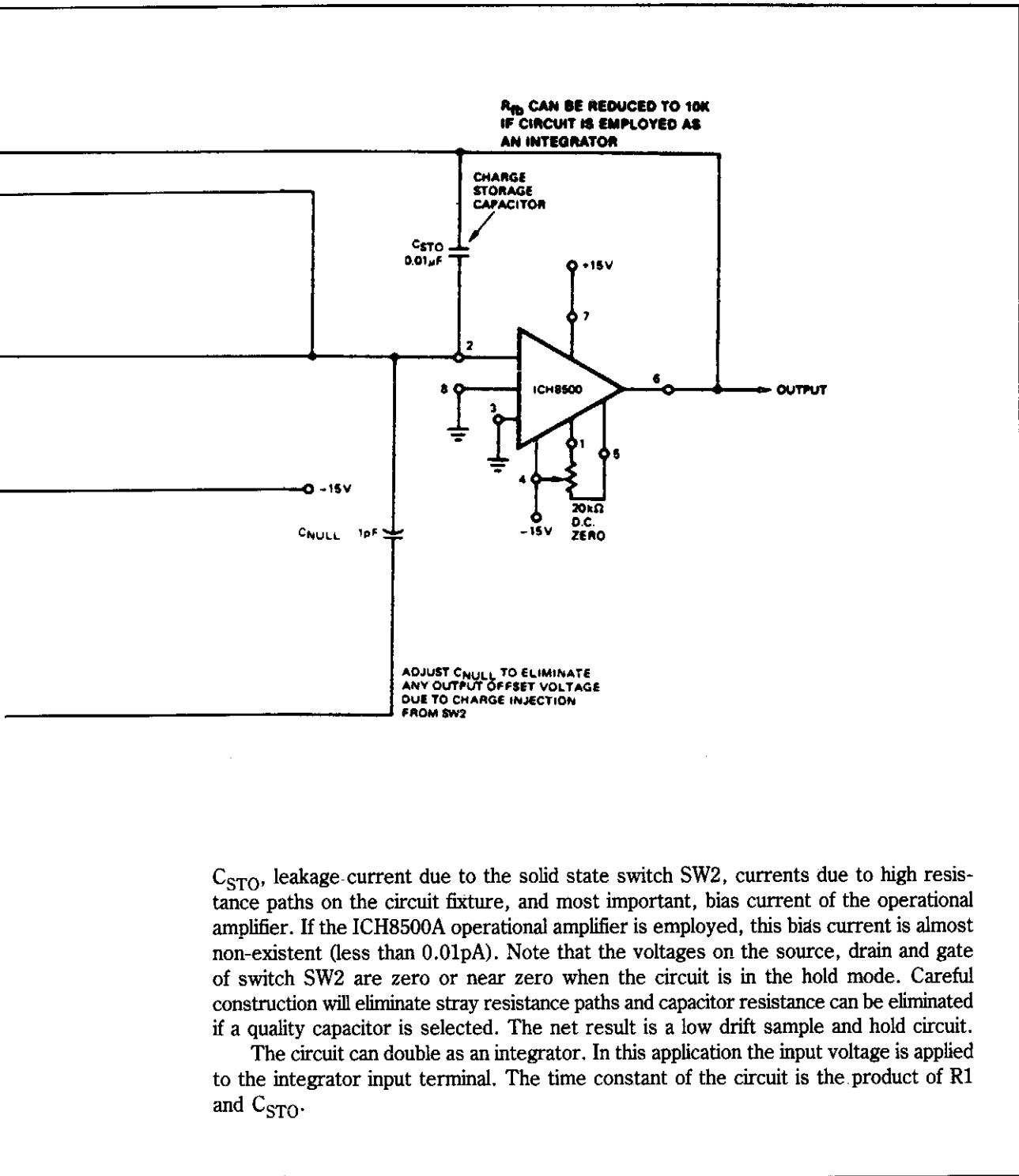
### Circuit Notes

This circuit rapidly charges capacitor  $C_{STO}$  to a voltage equal to an input signal. The input signal is then electrically disconnected from the capacitor with the charge still remaining on  $C_{STO}$ . Since  $C_{STO}$  is in the negative feedback loop of the operational amplifier, the output voltage of the amplifier is equal to the voltage across the capacitor. Ideally, the voltage across  $C_{STO}$  should remain constant causing the output of the amplifier to remain constant as well. However, the voltage across  $C_{STO}$  will decay at a rate proportional to the current being injected or taken out of the current summing node of the amplifier. This current can come from four sources: leakage resistance of



$C_{STO}$ , leakage current due to the solid state switch SW2, currents due to high resistance paths on the circuit fixture, and most important, bias current of the operational amplifier. If the ICH8500A operational amplifier is employed, this bias current is almost non-existent (less than 0.01pA). Note that the voltages on the source, drain and gate of switch SW2 are zero or near zero when the circuit is in the hold mode. Careful construction will eliminate stray resistance paths and capacitor resistance can be eliminated if a quality capacitor is selected. The net result is a low drift sample and hold circuit.

The circuit can double as an integrator. In this application the input voltage is applied to the integrator input terminal. The time constant of the circuit is the product of R1 and  $C_{STO}$ .

## FAST, PRECISION SAMPLE-HOLD


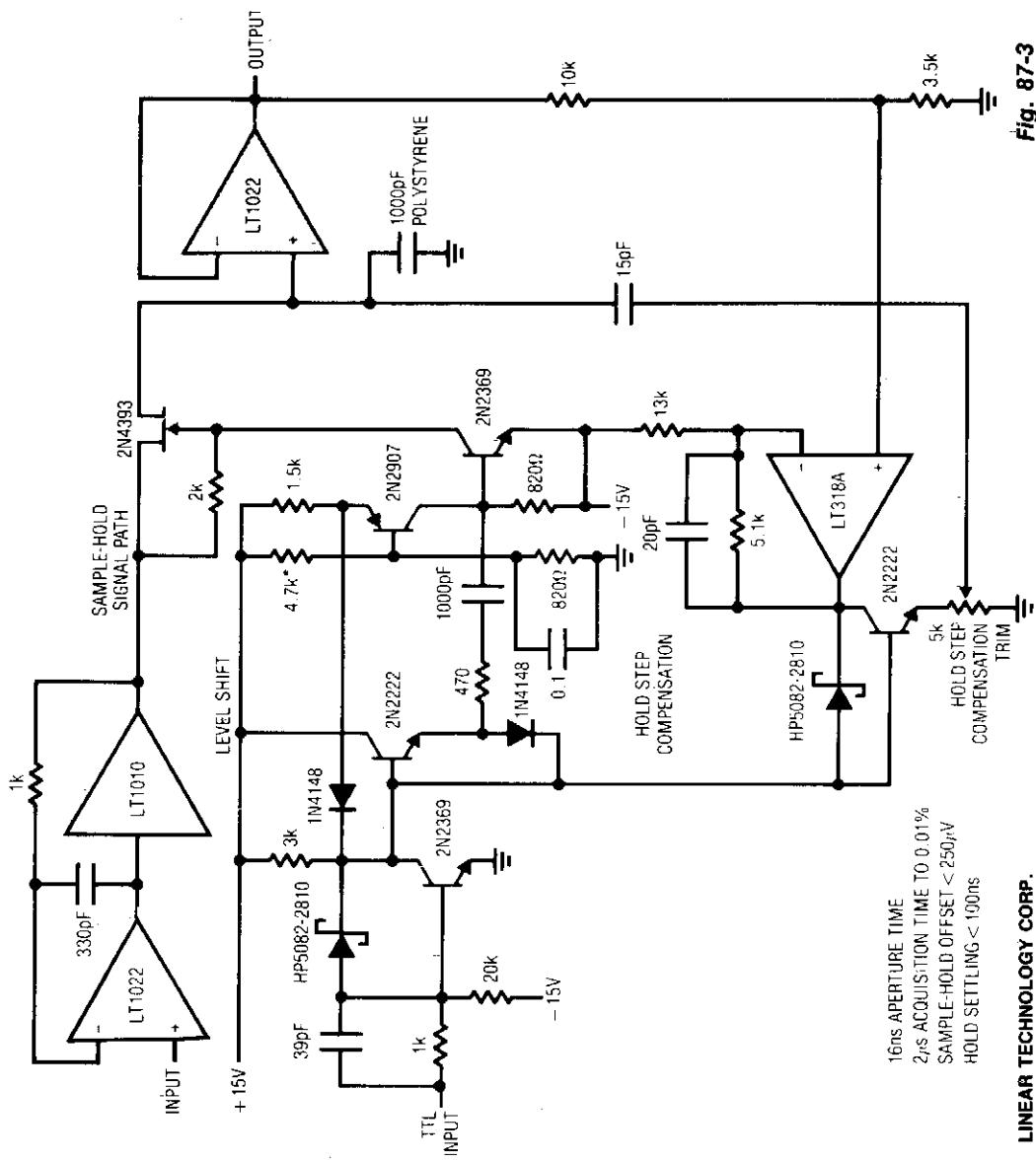



Fig. 87-3

LINEAR TECHNOLOGY CORP.

## HIGH PERFORMANCE SAMPLE AND HOLD

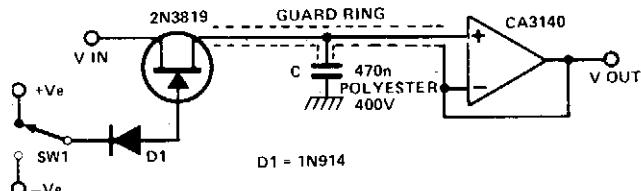

PRINTED CIRCUIT BOARD LAYOUT

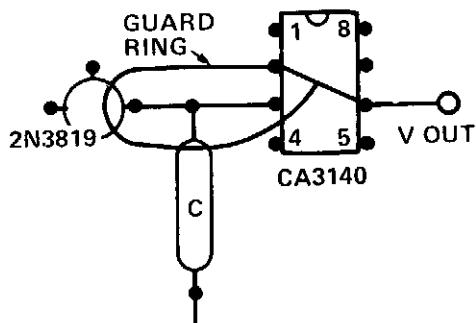

ELECTRONICS TODAY INTERNATIONAL


Fig. 87-4

### Circuit Notes

When switch SW1 is positive, the FET is turned on, and has a resistance of about 400 ohm. The input voltage charges up the capacitor through the FET. When SW1 is negative, the FET is turned off (pinched off). To get a long storage time, the op amp must have a very low input bias current. For the CA3140, this current is about 10 pico amps. The rate at which the capacitor will be discharged by this current is based on the equation,  $C \frac{dv}{dt} = i$  where  $dv/dt$  is the rate of change of voltage on the capacitor. Therefore:

$$\frac{dv}{dt} = \frac{i}{C} = \frac{10^{-11}}{0.47 \times 10^{-6}} = 22\mu\text{V/s}$$
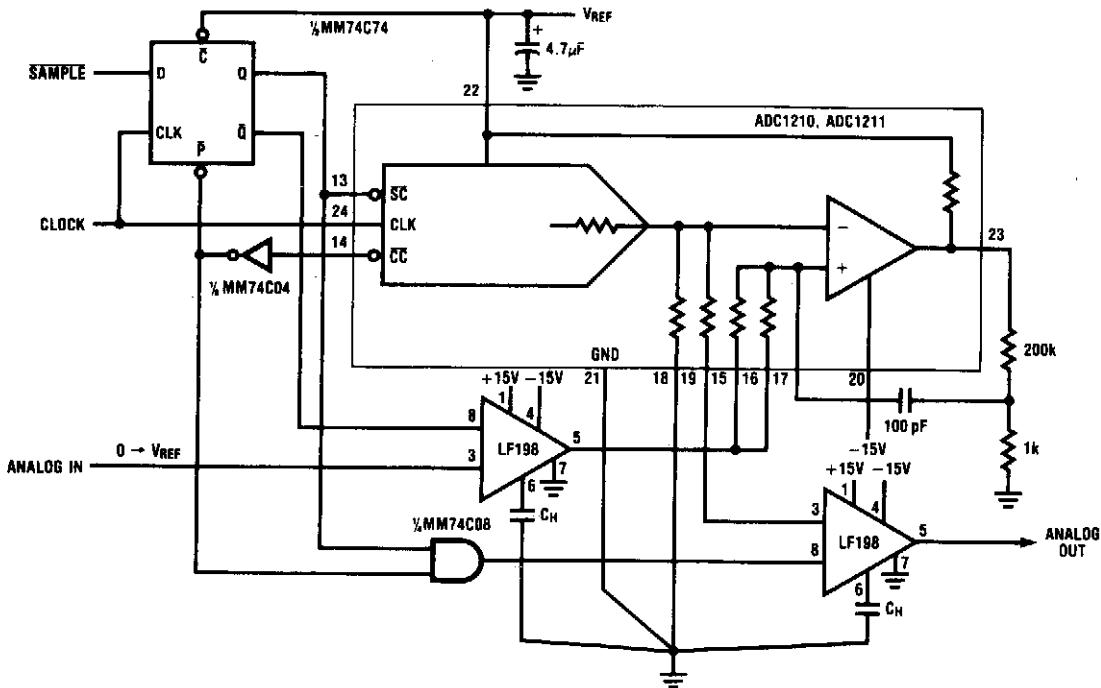
## **INFINITE SAMPLE AND HOLD AMPLIFIER**




NATIONAL SEMICONDUCTOR CORP.

*Fig. 87-5*

Circuit Notes

During normal "hold" mode, the replicated analog voltage is buffered straight through the S/H amplifier to the output. Upon issuance of a SAMPLE signal, the S/H amplifier is placed in the hold mode, holding the voltage until the new analog voltage is valid. The same SAMPLE signal triggers an update to the input sample-and-hold amplifier. The most current analog voltage is captured and held for conversion. The previously determined voltage is held stable at the output during the conversion cycle while the SAR/D-to-A converter continuously adjusts to replicate the new input voltage. At the end of the conversion, the output sample-and-hold amplifier is once again placed in the track mode. The new analog voltage is then regenerated.

## CHARGE COMPENSATED SAMPLE AND HOLD

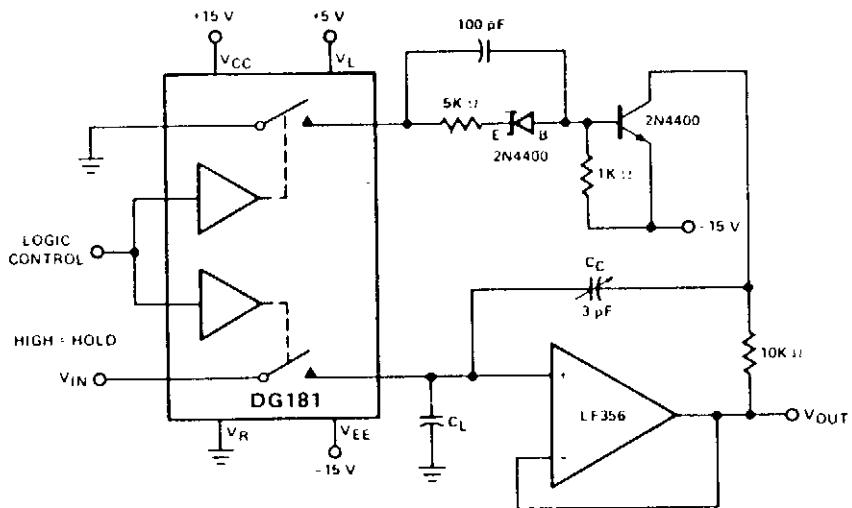

(< 5 mV of Sample to Hold Offset when  $C_L$  = 1000 pF)

SILICONIX

**Fig. 87-6**

### Circuit Notes

Less than  $\pm 5$  pC charge transfer (less than 5 mV sample-to-hold offset when  $C_L$  = 1000 pF).

# 88

## Sine-Wave Oscillators

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Sine-Wave Shaper  
Low Distortion Sine-Wave Oscillator  
Audio Oscillator  
Simple Audio Sine-Wave Generator  
Low Cost Wien Bridge Oscillator  
Modified UJT Relaxation Oscillator Produces Clean  
Audio Sinusoids

A 555 Used as an RC Audio Oscillator  
Wien Bridge Oscillator Uses CMOS Chip  
Adjustable Sine-wave Audio Oscillator  
One-IC Audio Generator  
Simple Two-Tone Generator

## SINE-WAVE SHAPER

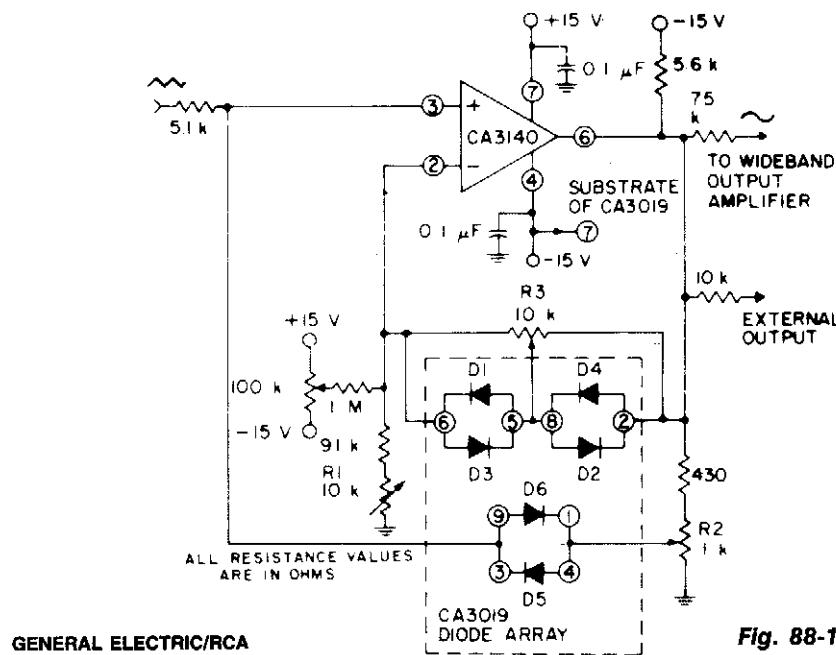


Fig. 88-1

### Circuit Notes

Uses a CA3140 BiMOS op amp as voltage follower, together with diodes from a CA3019 array, to convert a triangular signal (such as obtained from a function generator) to a sine-wave output with typical THD less than 2%.

## LOW DISTORTION SINE-WAVE OSCILLATOR


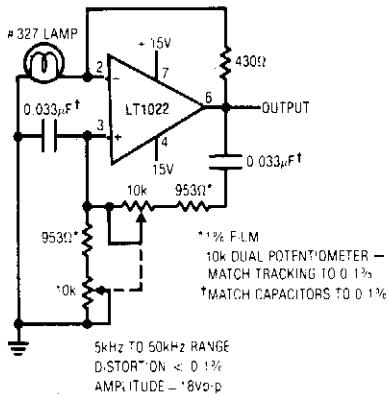


Fig. 88-2

LINEAR TECHNOLOGY CORP.

## AUDIO OSCILLATOR

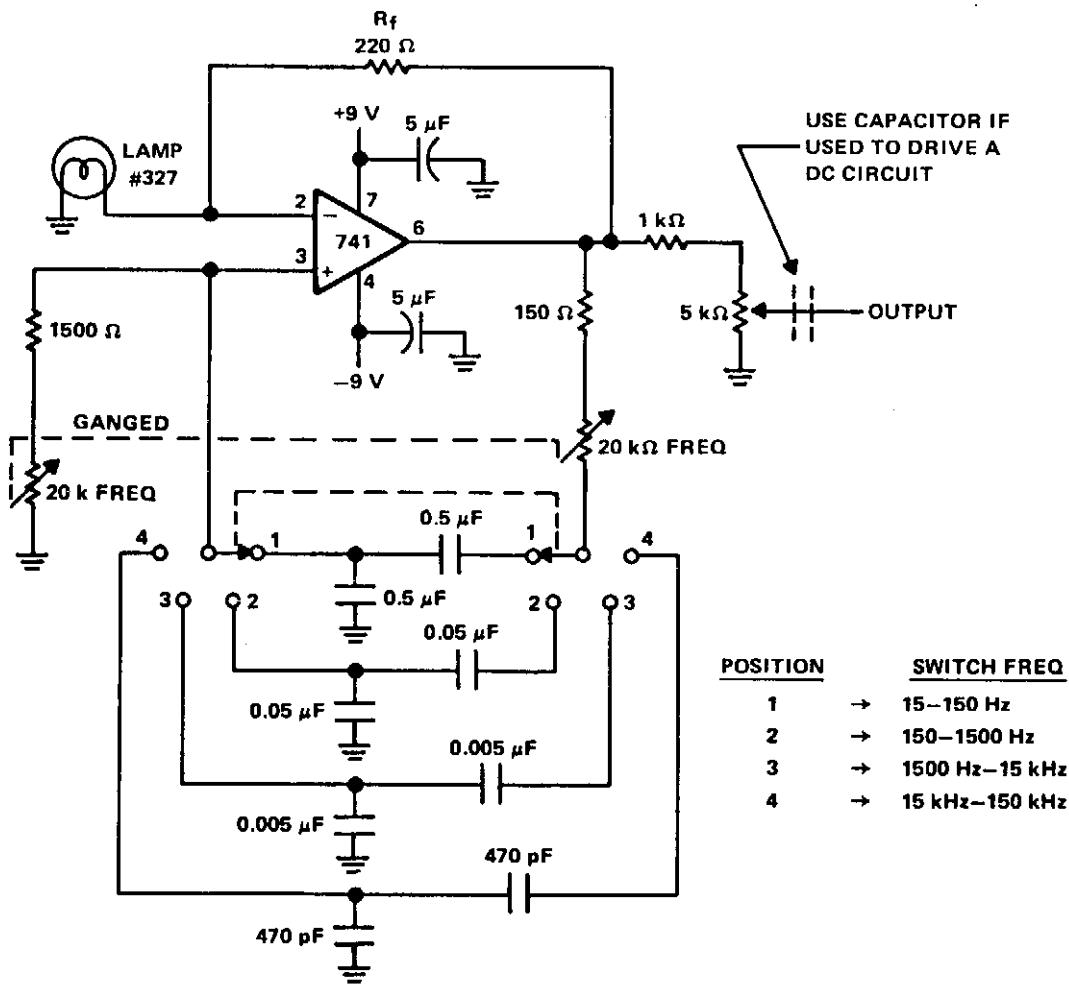


TEXAS INSTRUMENTS

Fig. 88-3

### Circuit Notes

A Wien bridge oscillator produces sine waves with very low distortion level. The Wien bridge oscillator produces zero phase shift at only one frequency ( $f = \frac{1}{2} \pi RC$ ) which will be the oscillation frequency. Stable oscillation can occur only if the loop gain remains at unity at the oscillation frequency. The circuit achieves this control by using the positive temperature coefficient of a small lamp to regulate gain ( $R_f/R_{LAMP}$ ) as the oscillator attempts to vary its output. The oscillator shown here has four frequency bands covering about 15 Hz to 150 kHz. The frequency is continuously variable within each frequency range with ganged 20 k ohm potentiometers. The oscillator draws only about 4.0 mA from the 9-V batteries. Its output is from 4 to 5 V with a 10 k ohm load and the  $R_f$  (feedback resistor) is set at about 5% below the point of clipping. As shown, the center arm of the 5 k ohm output potentiometer is the output terminal. To couple the oscillator to a dc type circuit, a capacitor should be inserted in series with the output lead.

## SIMPLE AUDIO SINE-WAVE GENERATOR

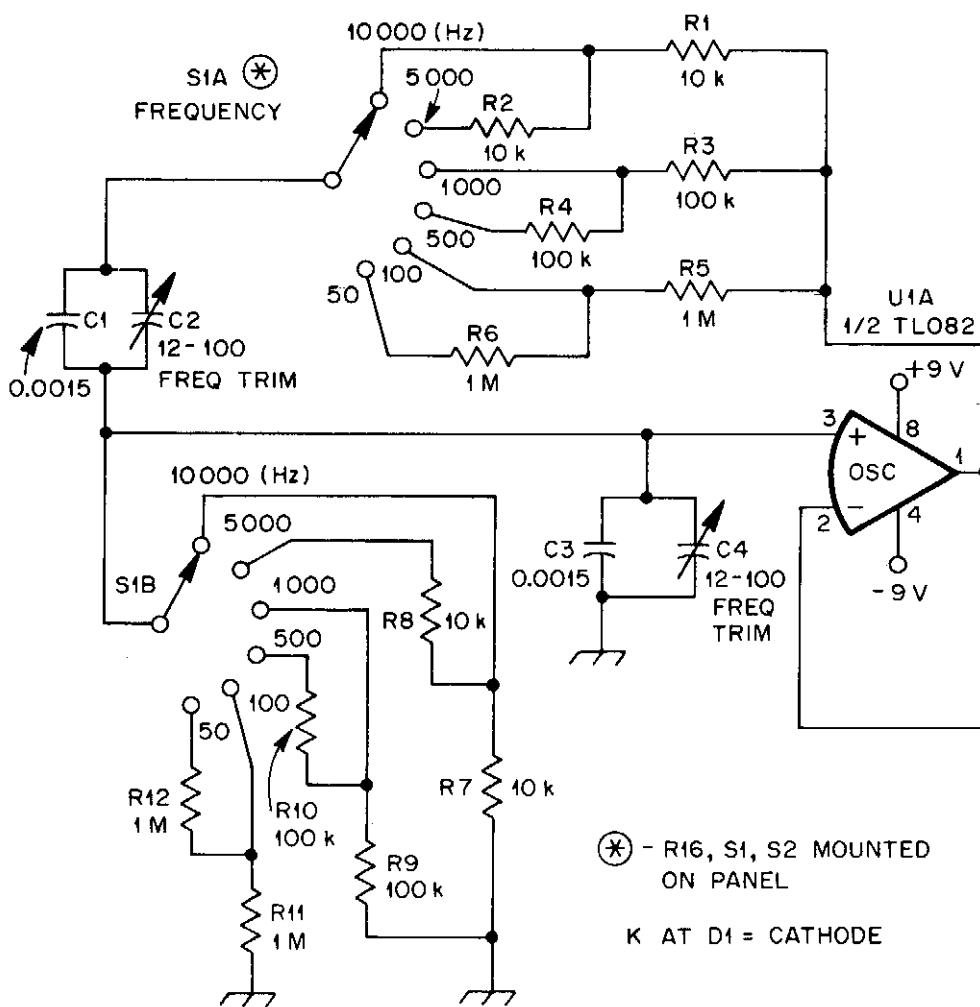


**QST**


**Fig. 88-4**
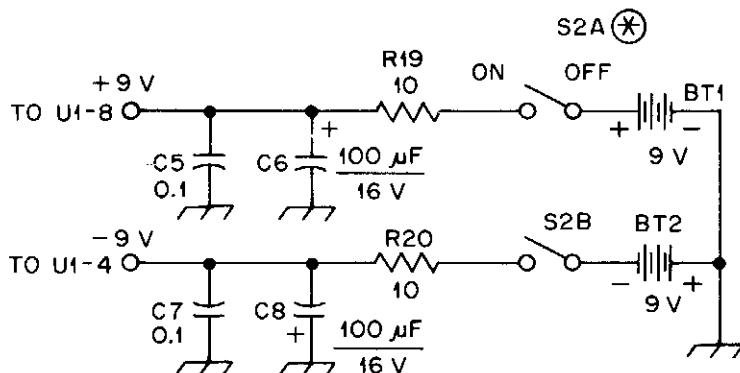
### Circuit Notes

U1A, an op amp, oscillates at the frequency at which the phase shift in the Wien bridge network is exactly zero degrees. Changing bridge component values changes the oscillator frequency. In this circuit, we need change only the two resistors to do this. S1A chooses a value among R1 through R6, and S1B similarly selects a value from R7 through R12. U1A must provide enough gain to overcome losses in the bridge, but not so much gain that oscillation builds up to the point of overload and distortion. U2 and



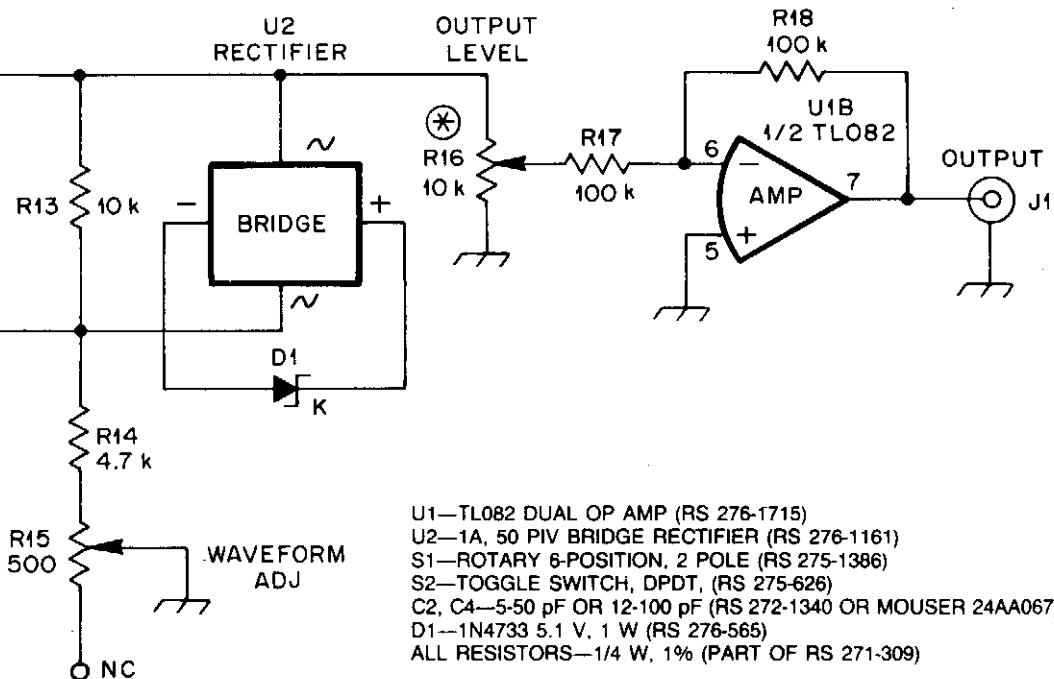
EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu\text{F}$ ); OTHERS ARE IN PICOFARADS ( $\text{pF}$ ); RESISTANCES ARE IN OHMS;  $\text{k} = 1000$ ,  $\text{M} = 1000\,000$ .



U1—TL082 DUAL OP AMP (RS 276-1715)  
 U2—1A, 50 PIV BRIDGE RECTIFIER (RS 276-1161)  
 S1—ROTARY 6-POSITION, 2 POLE (RS 275-1386)  
 S2—TOGGLE SWITCH, DPDT, (RS 275-626)  
 C2, C4—5-50  $\mu\text{F}$  OR 12-100  $\text{pF}$  (RS 272-1340 OR MOUSER 24AA067)  
 D1—1N4733 5.1 V, 1 W (RS 276-565)  
 ALL RESISTORS—1/4 W, 1% (PART OF RS 271-309)

C1 automatically regulate circuit gain to maintain oscillation. U2 places D1 across R13 with the proper polarity on both positive and negative alterations of the signal at pin 1 of U1. As the voltage at pin 1 of U1 approaches its peak value, D1 enters its Zener breakdown region, effectively shunting R13 with a resistive load. This increases the amount of negative feedback around U1, reducing its gain. R15, WAVEFORM ADJ, allows you to optimize circuit operation for lowest distortion. U1B provides isolation between oscillator and load. With the values shown for R17 and R18, U1B operates at unity gain.

## LOW COST WIEN BRIDGE OSCILLATOR

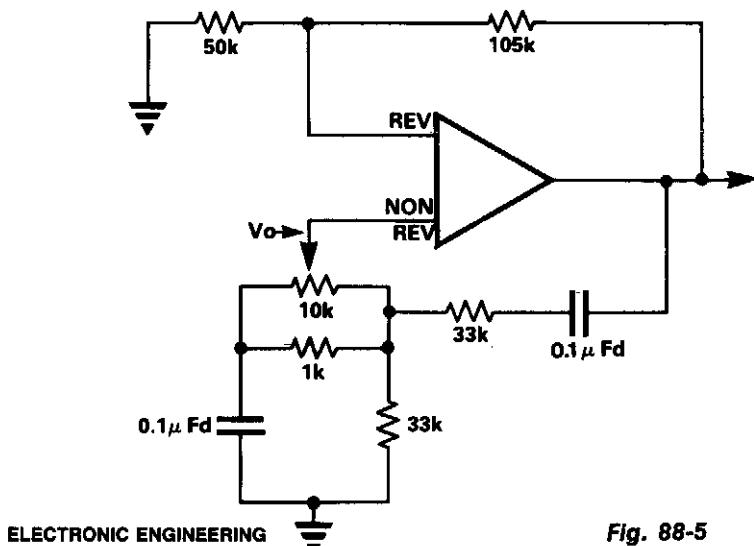


ELECTRONIC ENGINEERING

*Fig. 88-5*

### Circuit Notes

In the circuit the frequency trimming component is arranged so that the voltage across it is in quadrature with the voltage  $V_o$  from the bridge so that as it is adjusted the attenuation of the bridge only changes a little, avoiding the need for a two gang component. The range of variation of frequency is very limited. By using a high gain amplifier and metal film feedback resistors the loop gain can be set so that the unit just oscillates and the use of an automatic gain setting component, a thermistor for example, is eliminated.
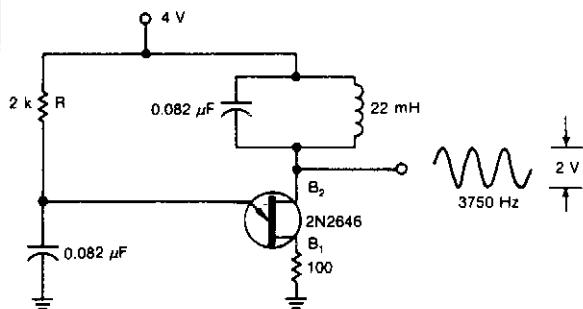
## MODIFIED UJT RELAXATION OSCILLATOR PRODUCES CLEAN AUDIO SINUSOIDS




ELECTRONIC DESIGN

### Circuit Notes

By placing a tuned circuit in the UJT oscillator's current-pulse path, a 3750-Hz sinusoid can be created at B2 with the component values shown.

*Fig. 88-6*

## A 555 USED AS AN RC AUDIO OSCILLATOR

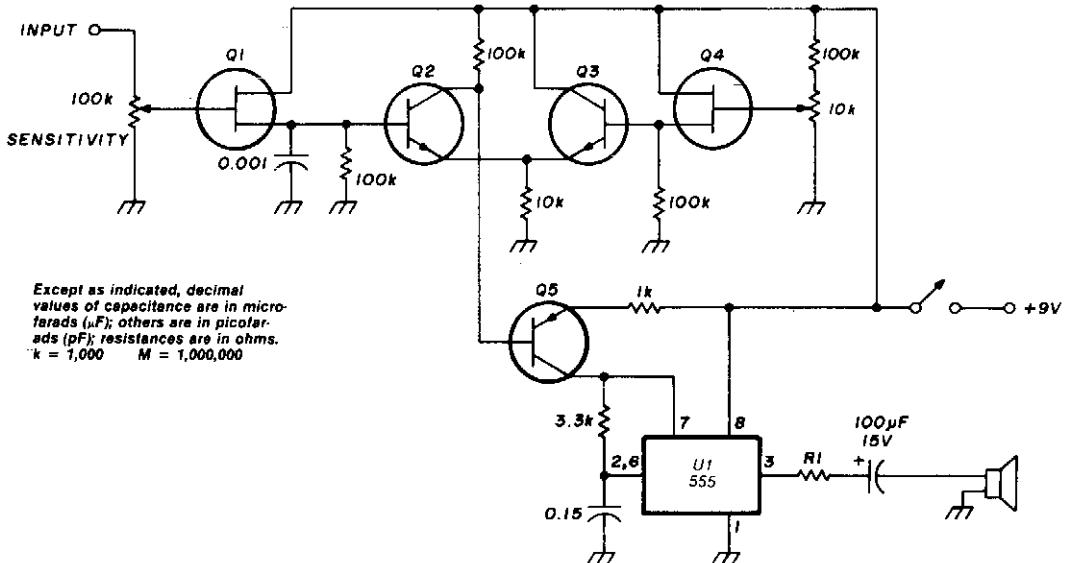


HAM RADIO

Fig. 88-7

### Circuit Notes

Transistor Q5 and the 1000 ohm resistor form the variable element needed for controlling the frequency of VCO by limiting the charging current flowing into the  $0.15 \mu\text{F}$  timing capacitor according to the forward bias being applied to Q5. As the voltage on pins 2 and 6 of U1 reach  $\frac{2}{3} V_{CC}$  (about 6 volts with a 9-volt supply) the timer will fire and pin 3 will be pulled low. Pin 7, an open collector output, goes low and begins to discharge the timing capacitor—through the 3.3 kilohm resistor. The discharge time provided by this resistor assures a reasonable, although asymmetrical, waveform for the aural signal generated by U1. At  $\frac{1}{3} V_{CC}$  the internal flip-flop resets, the output on pin 3 goes high, the open collector output on pin 7 floats, and the timing cycle begins again.


## WIEN BRIDGE OSCILLATOR USES CMOS CHIP

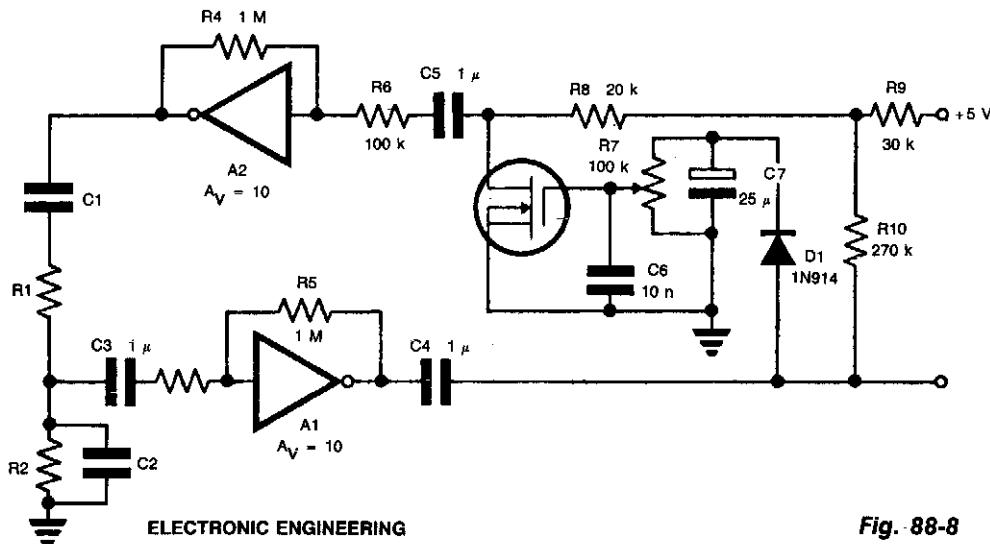

ELECTRONIC ENGINEERING

Fig. 88-8

## ADJUSTABLE SINE-WAVE AUDIO OSCILLATOR

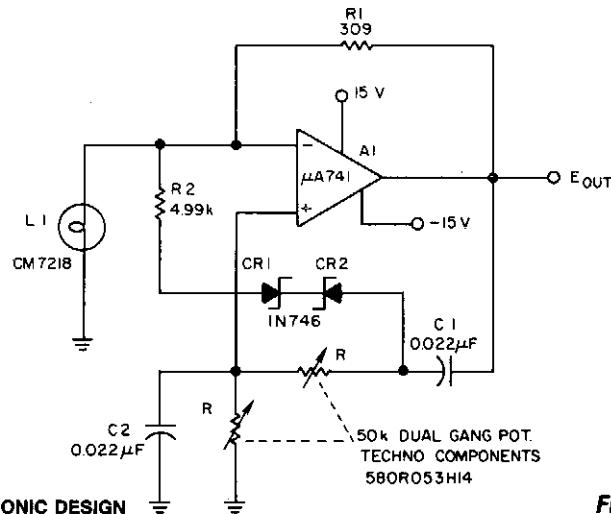

ELECTRONIC DESIGN

Fig. 88-9

### Circuit Notes

Waveform purity at low frequencies for a Wien bridge oscillator is enhanced by diode limiting. Lamp L1 stabilizes the loop gain at higher frequencies while the limiting action of R<sub>2</sub>, CR<sub>1</sub>, and CR<sub>2</sub> prevents clipping at low frequencies and increases the frequency adjustment range from about 3:1 to greater than 10:1.

## ONE-IC AUDIO GENERATOR

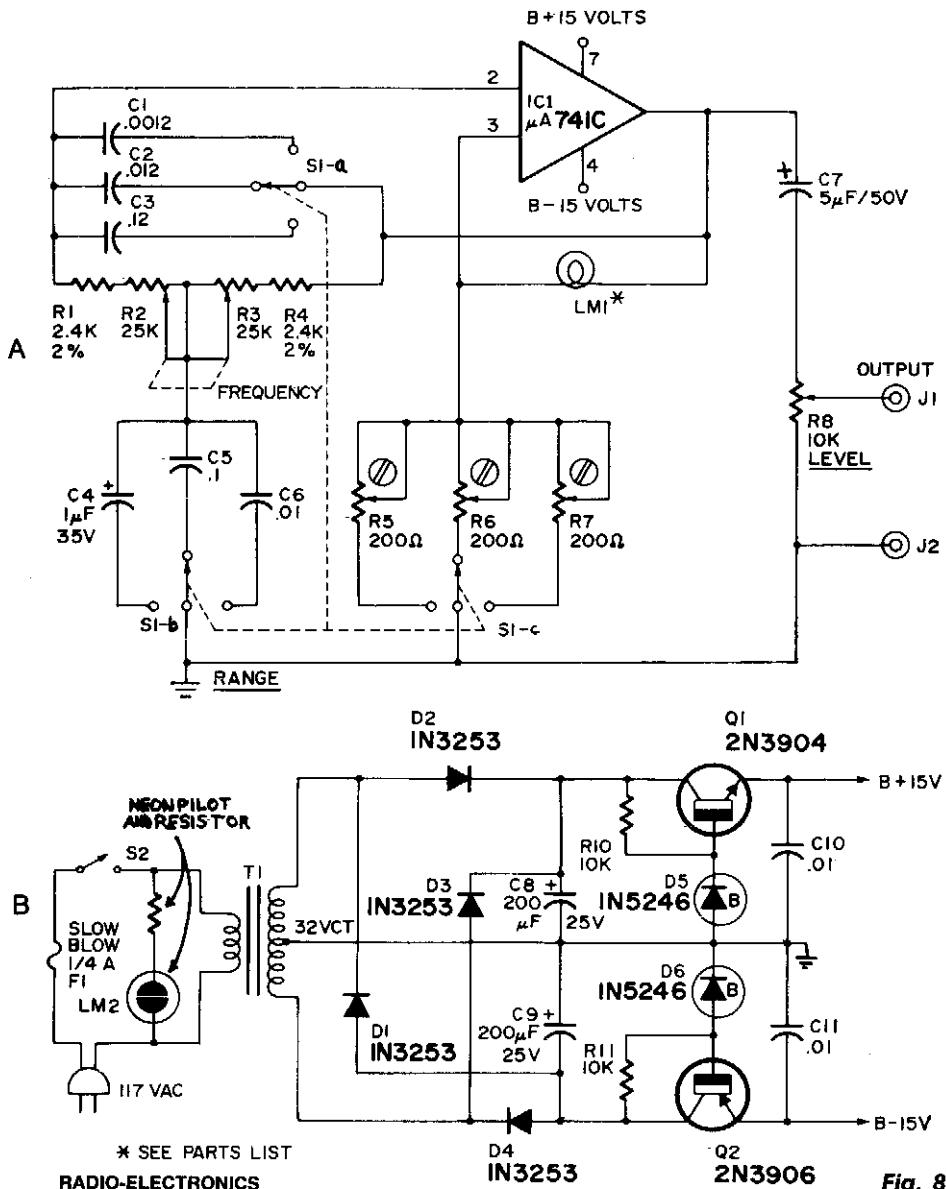


Fig. 88-10


### Circuit Notes

This high-quality low-cost generator covers 20 Hz to 20 kHz in three bands with less than 1% distortion. LM1—10 V, 14 mA (344, 1869, 914) or 10 V, 10 mA (913, 367).

A = oscillator

B = power supply

## SIMPLE TWO-TONE GENERATOR

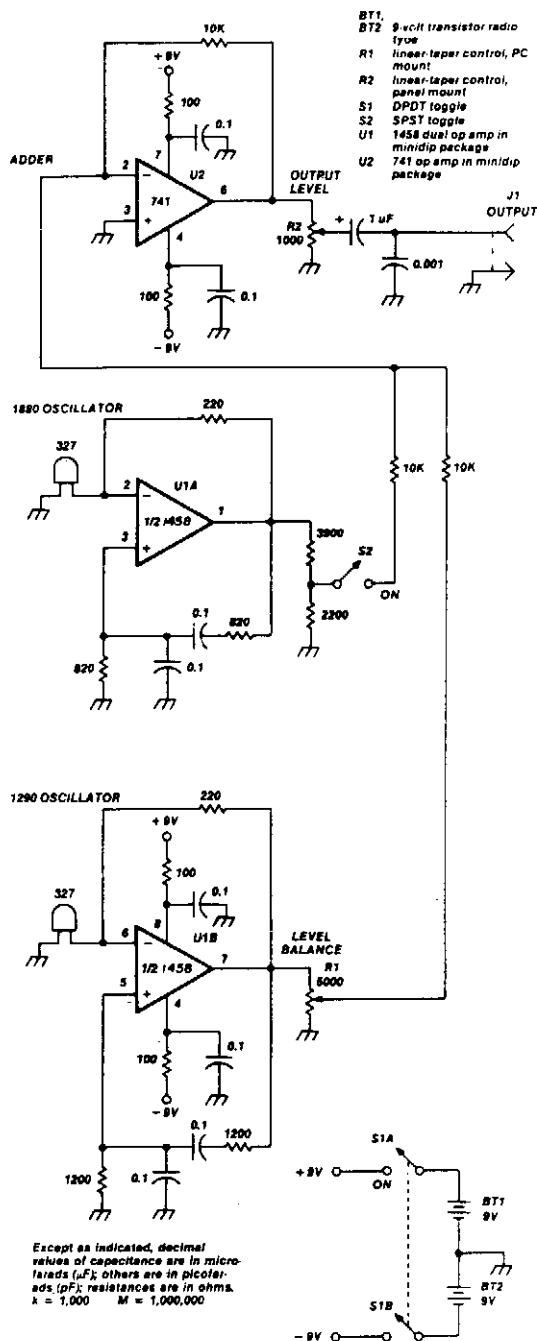

### Circuit Notes

Two 741 operational amplifiers are used for the active element in this Wien bridge oscillator. (The 1458 is the dual version of the 741.) Frequencies of the two oscillators were chosen to fit standard component values. Other frequencies between 500 and 2000 Hz can be employed. They should not be harmonically related. The output level of U1A is set by a resistive divider, while the output of U1B is adjustable through R1. The output of the two oscillators is combined in U2, an op-amp adder with unity gain. The output from U2 can be adjusted using R2.

**Fig. 88-11**

# 89

## Sirens, Warblers and Wailers

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Warble Generator  
Wailing Alarm  
Warble-Tone Alarm  
Warbling Tone Generator  
Multifunction Siren System  
7400 Siren  
Toy Siren

Siren Uses TTL Gates  
Electronic Ship Siren  
Siren Alarm Simulates Star Trek Red Alert  
Yelp Oscillator  
High Power Siren  
“Hee-Haw” Two-Tone Siren  
Varying Frequency Warning Alarm

## WARBLE GENERATOR

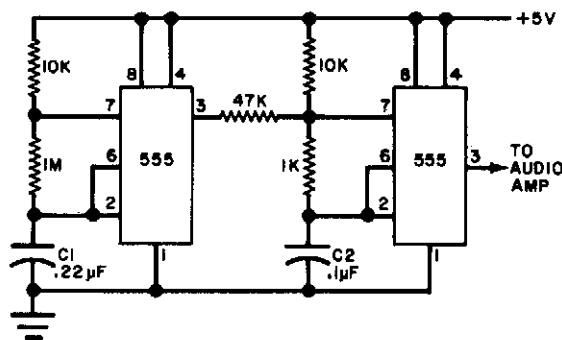


POPULAR ELECTRONICS

*Fig. 89-1*

### Circuit Notes

The circuit uses a pair of 555 timers or a single dual timer. Capacitor C1 controls the speed of the warble, while C2 determines the pitch. The values shown should produce quite a distinctive signal.

## WAILING ALARM

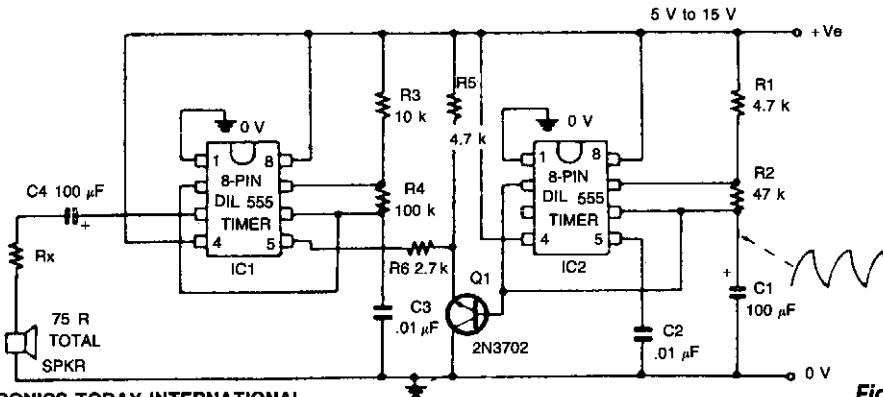


ELECTRONICS TODAY INTERNATIONAL

*Fig. 89-2*

### Circuit Notes

This circuit simulates the sound of an American police siren. IC2 is wired as a low frequency astable that has a cycling period of about 6 seconds. The slowly varying ramp waveform on C1 is fed to pnp emitter follower Q1, and is then used to frequency modulate alarm generator IC1 via R6. IC1 has a natural center frequency of about 800Hz. Circuit action is such that the alarm output signal starts at a low frequency, rises for 3 seconds to a high frequency, then falls over 3 seconds to a low frequency again, and so on ad infinitum.

## WARBLE-TONE ALARM

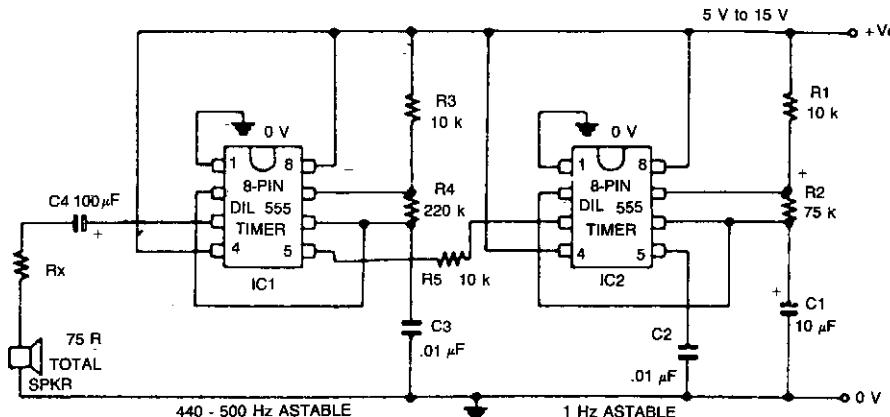


ELECTRONICS TODAY INTERNATIONAL

**Fig. 89-3**

### Circuit Notes

The circuit generates a warble-tone alarm signal that simulates the sound of a British police siren. IC1 is wired as an alarm generator and IC2 is wired as a 1 Hz astable multivibrator. The output of IC2 is used to frequency modulate IC1 via R5. The action is such that the output frequency of IC1 alternates symmetrically between 500 Hz and 440 Hz, taking one sound to complete each alternating cycle.

## WARBLING TONE GENERATOR

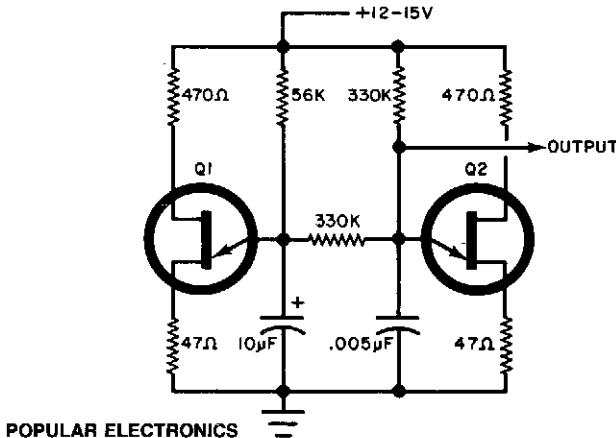

POPULAR ELECTRONICS

**Fig. 89-4**

### Circuit Notes

The circuit uses two unijunction transistors. The low-frequency sawtooth generated by Q1 modulates the high-frequency tone generated by Q2. The output should feed into a high-impedance amplifier. Q1 = Q2 = 2N4871.

## MULTIFUNCTION SIREN SYSTEM

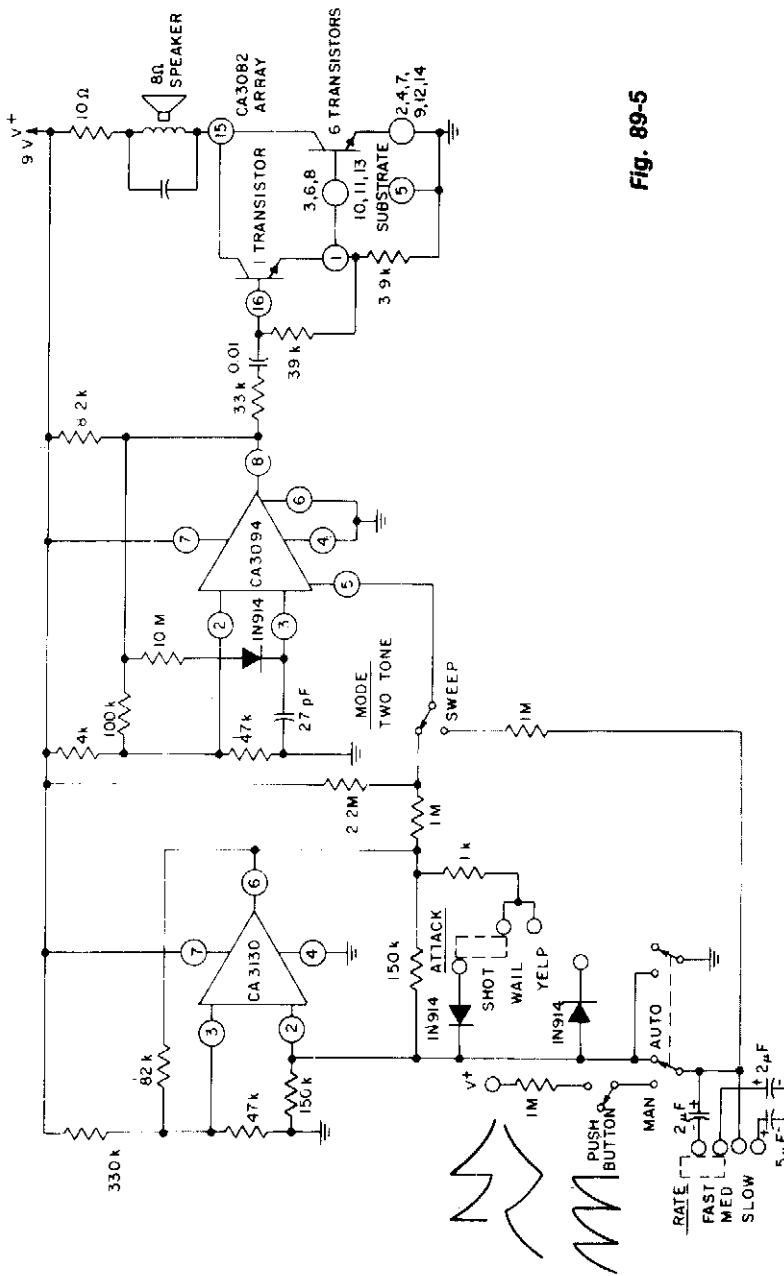



Fig. 89-5

Circuit Notes

The circuit uses a CA3130 BiMOS op amp as a multivibrator to control the siren's rate. A CA3094 used as a VCO is followed by a CA3082 transistor array used to drive a speaker. A "Manual" or "Auto" mode switch allows the user to select either intermittent or continuous siren operation, respectively. In addition, three switches are available that control "Mode", "Attack", and "Rate".

GENERAL ELECTRIC/BCA

## 7400 SIREN

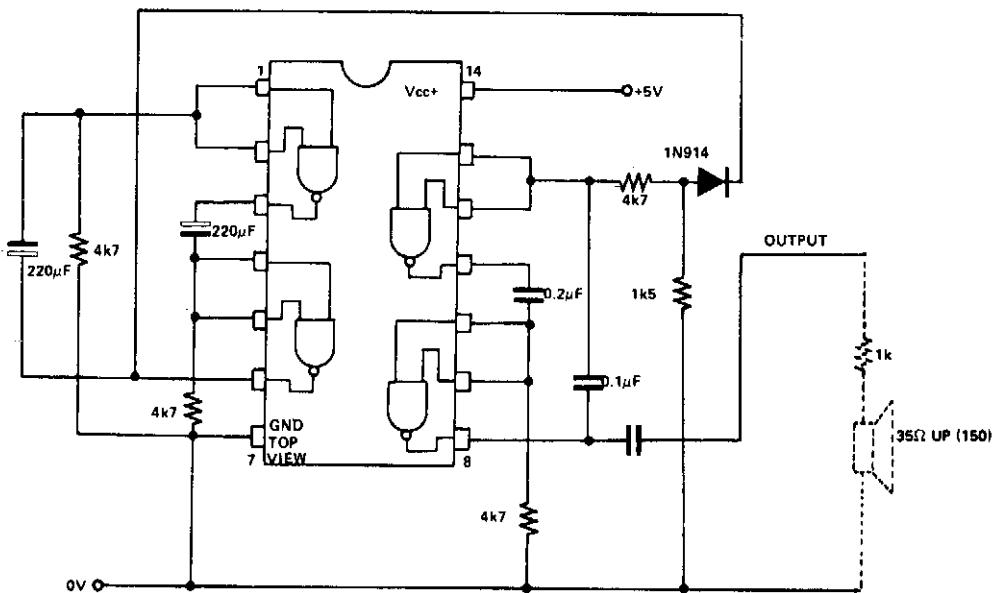


ELECTRONICS TODAY INTERNATIONAL

Fig. 89-6

### Circuit Notes

Two NAND gates are used for the oscillator, and two as the control. If the two-tone speed needs to be altered, the  $220 \mu\text{F}$  capacitors can be changed (larger for slower operation). If the frequency of the oscillator is to be changed, the  $0.2$  and  $0.1 \mu\text{F}$  capacitors can be varied and the value of R1 can be increased. To change frequency range between the two notes, alter the  $1.5 \text{ k}$  ( $1,500$ ) resistor.

## TOY SIREN

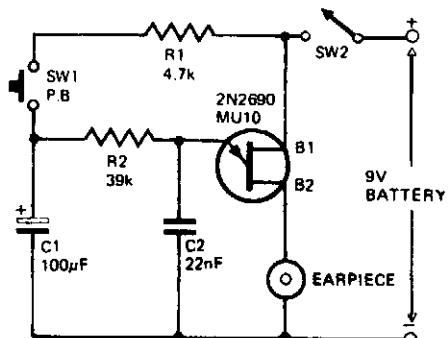

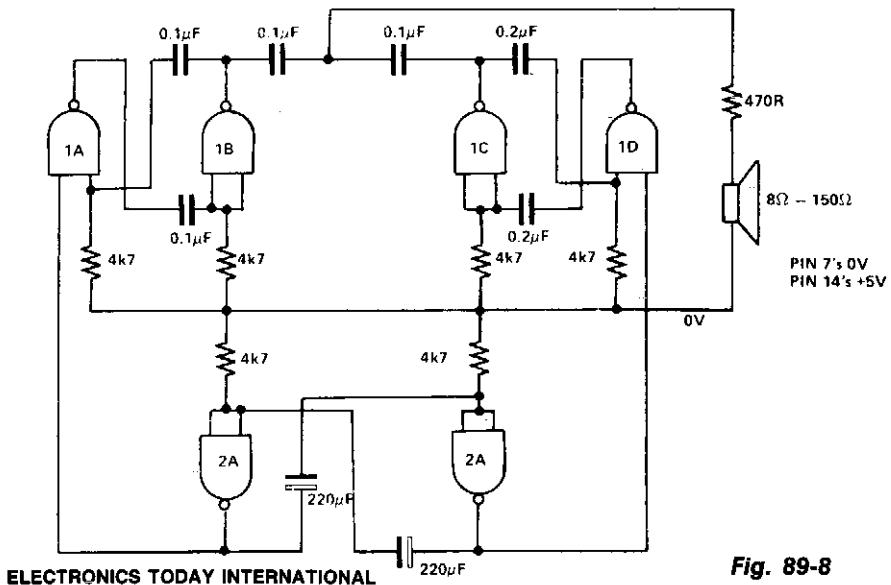
ELECTRONICS TODAY INTERNATIONAL

Fig. 89-7

### Circuit Notes

This circuit can be built small enough to fit inside a toy. The circuit consists of a relaxation oscillator utilizing one unijunction transistor (2N2646, MU10, TIS43). R2 and C2 determine the frequency of the tone. Pushing the button, SW1 charges up the capacitor and the potential at the junction of R2 and C2 rises, causing an upswing in the frequency of oscillation. On releasing the pushbutton the charge on C2 will drop slowly with a proportional reduction in the frequency of oscillation. Manual operation of the button at intervals of approximately 2 seconds will produce a siren sound.

### SIREN USES TTL GATES

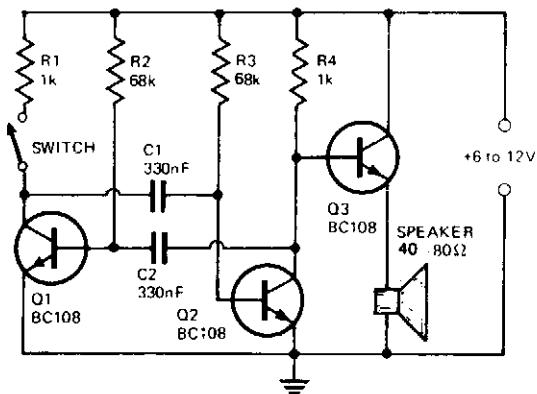


**Fig. 89-8**

### Circuit Notes

The siren consists of two oscillators which generate the tones. A third oscillator is used to switch the others on and off alternately, giving the two-tone effect. By changing the capacitor values different tones can be produced.

### ELECTRONIC SHIP SIREN




### Circuit Notes

The circuit consists of a multivibrator (Q1 & Q2), and a low power output stage Q3. The speaker should have an impedance in the region of 40 to 80 ohms. To use a low impedance speaker, connect an output transformer from the emitter of Q3 to ground. C1 and C2 determine the pitch of the siren and the values specified will provide a tone of about 300 Hz. Quiescent current is negligible. The output at the collector of Q2 can also be fed into an amplifier input via a 1 μF electrolytic, in series with a 12 k resistor.

ELECTRONICS TODAY INTERNATIONAL

**Fig. 89-9**
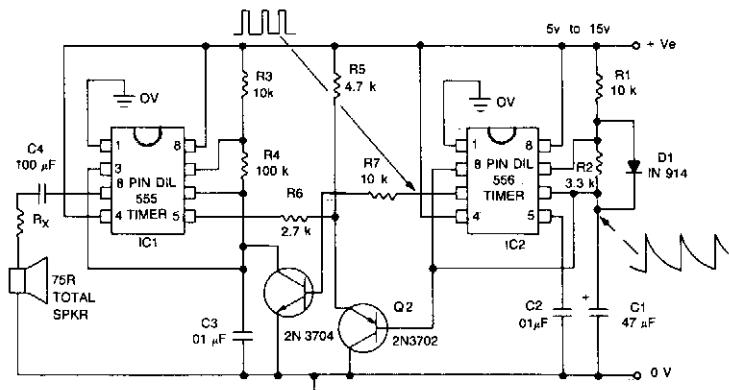
#### **SIREN ALARM SIMULATES STAR TREK RED ALERT**




ELECTRONICS TODAY INTERNATIONAL

*Fig. 89-10*

Circuit Notes

The signal starts at a low frequency, rises for about 1.15 seconds to a high frequency, ceases for about 0.35 seconds, then starts rising again from a low frequency, and so on ad infinitum.

## **YELP OSCILLATOR**

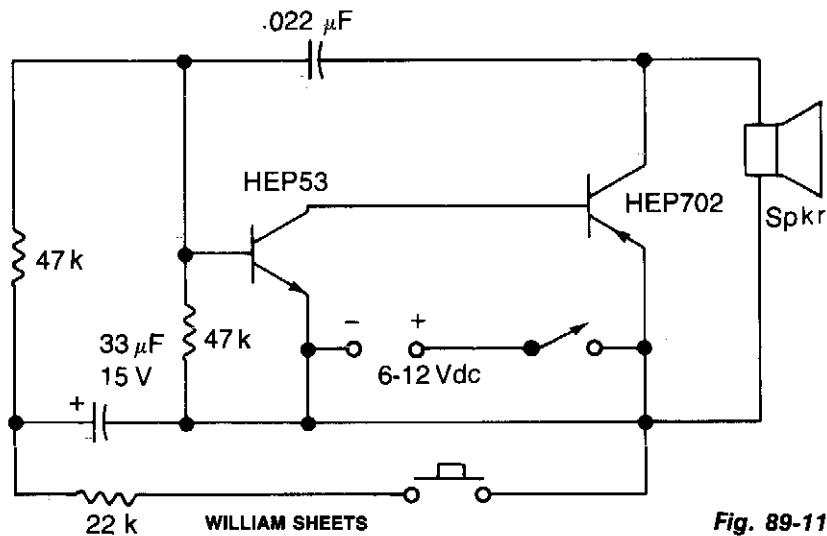


*Fig. 89-11*

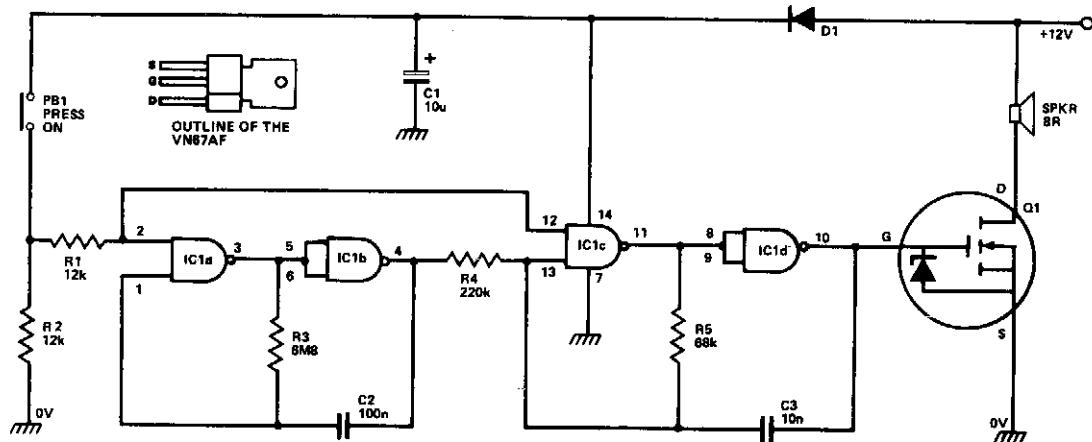**Circuit Notes**

Close the pushbutton switch and the circuit starts the siren up-shifting to a higher frequency. Release it and the tone slides down until S2 is closed again. Tone quality is adjusted by changing the  $0.022 \mu\text{F}$  capacitor.

## HIGH POWER SIREN



ELECTRONICS TODAY INTERNATIONAL


Fig. 89-12

NOTES:  
D1 IS 1N4001  
Q1 IS VN67AF  
IC1 IS CD4011B

### Circuit Notes

IC1a and IC1b are wired as a slow astable multivibrator and IC1c-IC1d are wired as a fast astable. Both are "gated" types, which can be turned on and off via PB1. The output of the slow astable modulates the frequency of the fast astable, and the output of the fast astable is fed to the external speaker via the Q1 VMOS power FET amplifier stage.

## "HEE-HAW" TWO-TONE SIREN

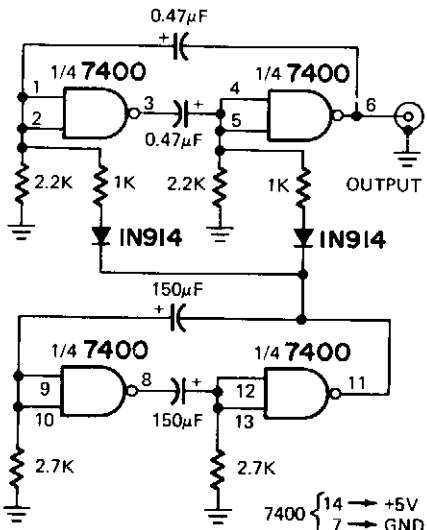

RADIO-ELECTRONICS

Fig. 89-13

### Circuit Notes

The circuit uses two gates of a 7400 IC cross-connected to form an astable multivibrator driven by the 1-pulse per second output of the digital clock IC. The hee-haw circuit has a low frequency astable modulator added to make a self-contained European-type siren. Tone and rate can be varied as desired by changing capacitor values. If the tone is too harsh, a simple R-C filter will remove the harmonic content—the multivibrator output is almost a square wave. With the resistor values shown, no start-up problems occur; but if the 2.2 k or 2.7 k resistors are changed too much, latch-up can be a problem.

### VARYING-FREQUENCY WARNING ALARM

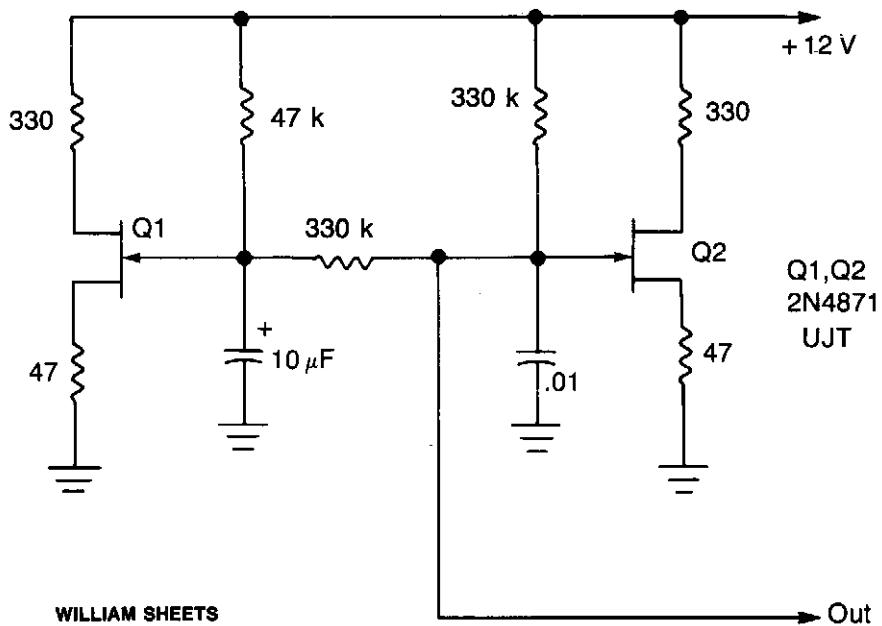


Fig. 89-14

#### Circuit Notes

The output frequency changes continuously. Low frequency oscillator (Q1) modulates high frequency oscillator Q2 and its associated timing capacitor.

# **90**

## **Sound (Audio) Operated Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Sound-Activated Switch  
Sound-Activated ac Switch  
VOX Box  
Color Organ  
Basic Color Organ

### SOUND-ACTIVATED SWITCH

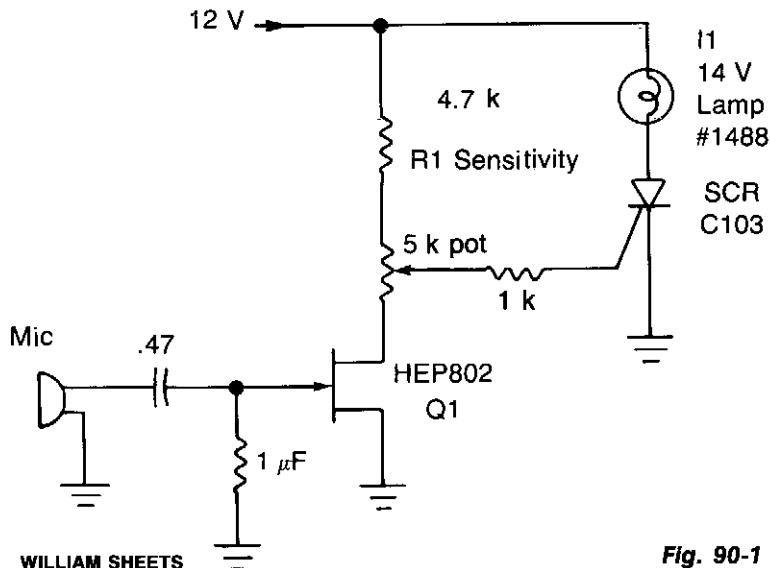


Fig. 90-1

#### Circuit Notes

The audio from Mic is amplified by Q1. Peaks of signal (adjusted by R1) greater than about 0.7 volts trigger the SCR and light lamp I1.

### SOUND-ACTIVATED ac SWITCH

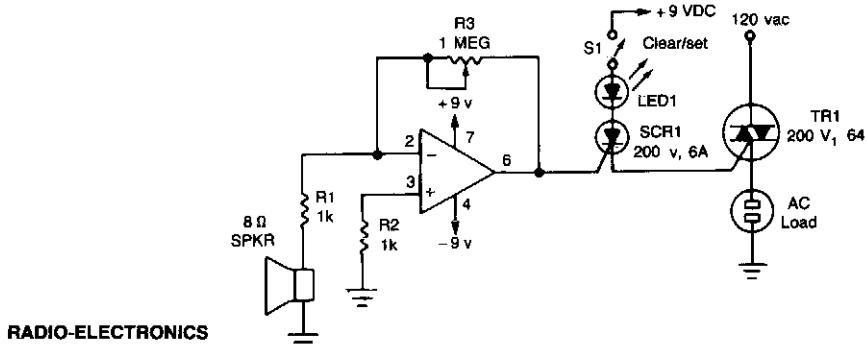


Fig. 90-2

#### Circuit Notes

The circuit uses a 741 op amp operating as an inverting amplifier to amplify the voltage produced by an 8-ohm speaker used to detect any sounds. The feedback resistor R3, a 1-megohm potentiometer used to vary the gain of the amplifier determines the sensitivity of the circuit. When S1 is closed in the (SET) position and a sound is applied to the speaker, SCR1 is turned on. It will remain in conduction until the anode voltage is removed by opening S1, putting it in its RESET position. (Once an SCR is turned on, the gate or trigger has no control over the circuit.) As long as the SCR conducts, the Triac, TR1, will remain on and supply voltage to the load.

## VOX BOX

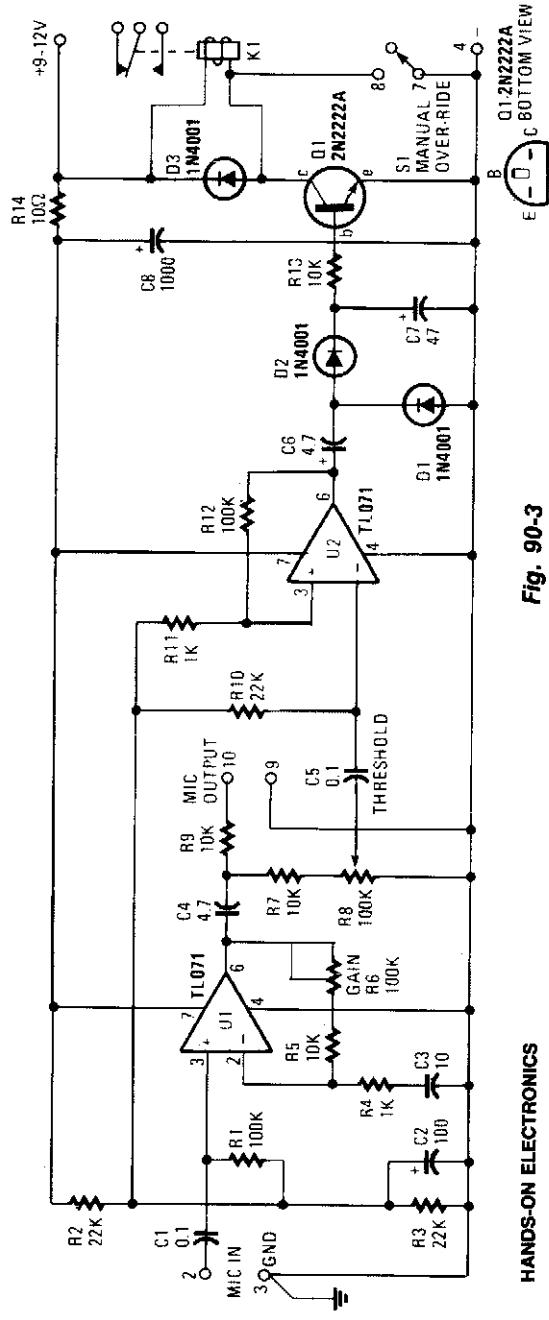
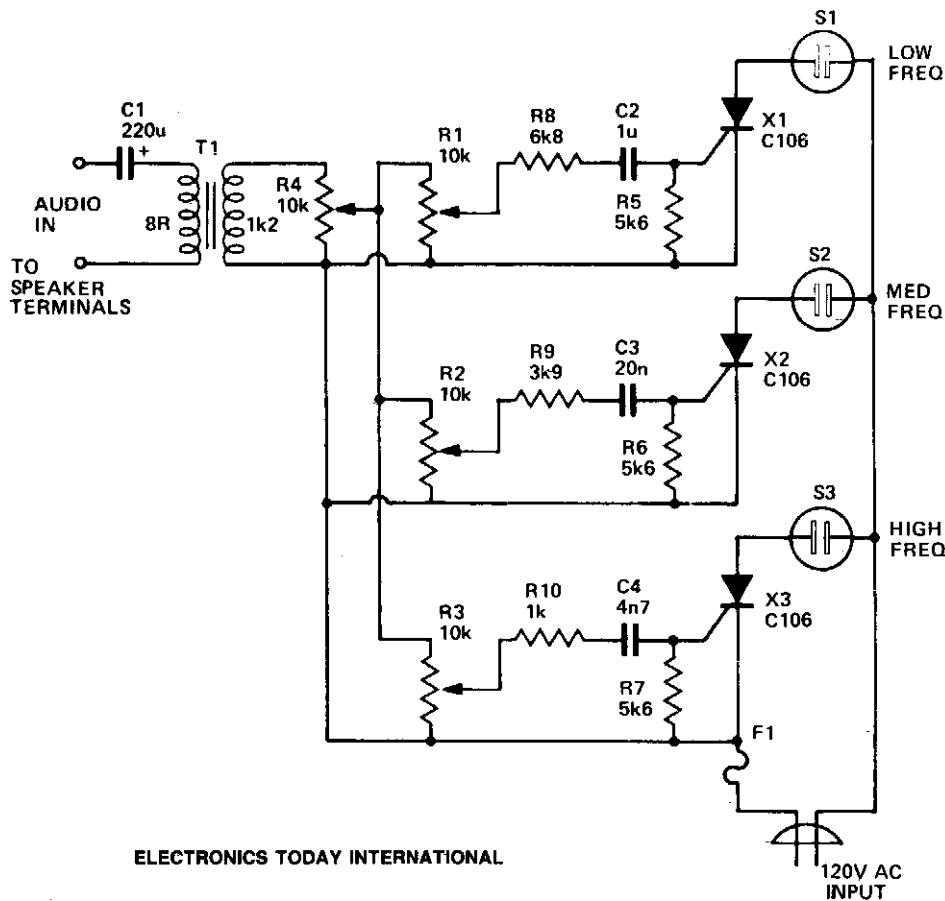


Fig. 90-3

### Circuit Notes

The electronic circuit in the VOX Box consists of three parts: a microphone preamplifier, a Schmitt trigger, and a relay driver. Input signals (MIC INPUT terminals) to the microphone preamplifier (U1) are amplified and fed to a THRESHOLD control (R8). When the preselected threshold voltage level is exceeded, the output of the Schmitt trigger (U2) immediately goes high. The signal from U2 is rectified and the voltage developed across C7 turns on the relay energizer transistor (Q1). That transistor action passes pull-down current through the coil of relay K1. The changing of the relay SPDT contacts can be used to either make or break an external ac or dc circuit.

## COLOR ORGAN

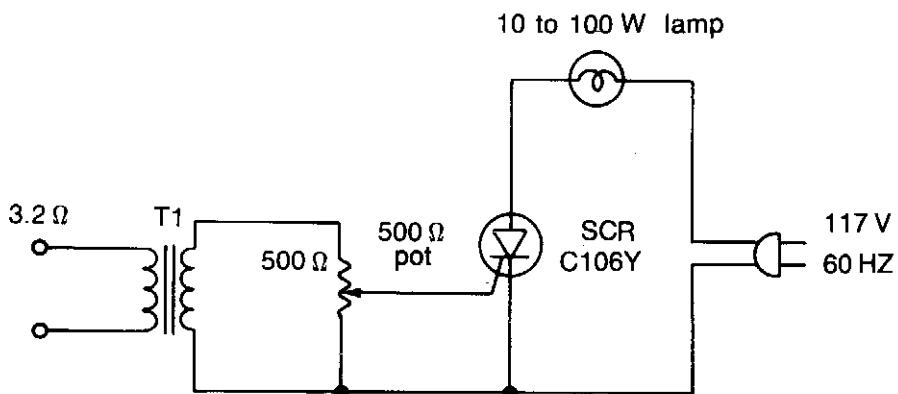


**Fig. 90-4**

### Circuit Notes

Three lights are controlled by the three channels. One light will pulse in response to the bass, another illuminates with mid-range sounds, and the last lights for high notes. Four level controls allow adjustment of overall light level and each channel individually. Up to 200 watts per channel can be handled.

## BASIC COLOR ORGAN



WILLIAM SHEETS

Fig. 90-5

### Circuit Notes

Transformer T1 can be any matching transistor type in the range of 500/500 to 2500/2500 ohms. No connections from the SCR or its components are connected to ground. For safety's sake, keep the 117-V line voltage from the amplifier connections—that is the reason for using T1. To adjust, set potentiometer R1 "off" and adjust the amplifier volume control for a normal listening level. Then adjust the potentiometer until the lamp starts to throb in step with the beat.

# 91

## Sound Effect Circuits

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Sound Effects Generator  
Electronic Bongos  
Train Chuffer  
Bird Chirp  
Steam Locomotive Whistle  
WAA-WAA Circuit

Unusual Fuzz  
Autodrum  
Twang-Twang Circuit  
Steam Train/Prop Plane  
Funk Box

## SOUND EFFECTS GENERATOR


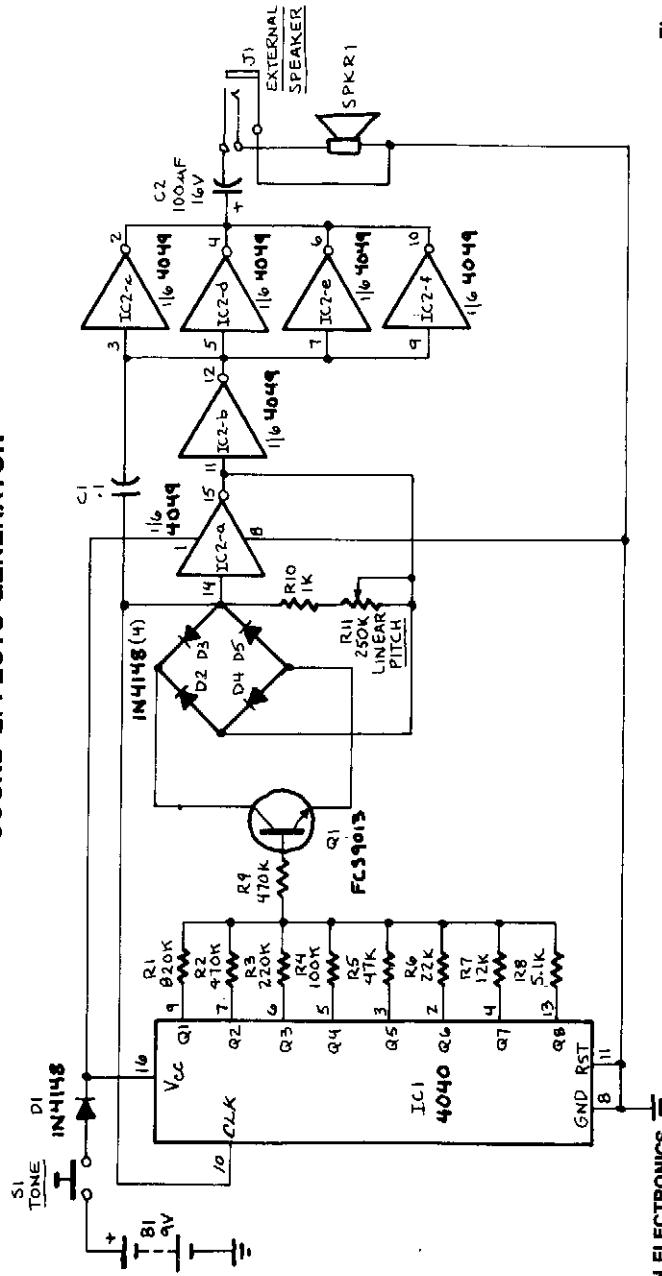


Fig. 91-1

### Circuit Notes

This circuit can generate a European police-car siren, bird noises, spaceship sounds, etc. In addition, it can be put to use as a doorbell, an alarm, etc. The circuit consists of four parts: a binary counter, a D/A converter, a VCO, and an audio output amplifier. The initial frequency of oscillation is determined by potentiometer R11. The VCO first oscillates at a relatively low frequency, and gradually picks up speed as the control voltage supplied by the D/A converter increases. The DA converter is the group of resistors R1-R8. When none of IC1's outputs is active, little current will flow into the base of Q1, so the VCO's control voltage will be low. As more and more counter outputs become active, base current increases, and thereby so does the VCO's frequency of oscillation. The VCO itself is composed of IC2-a, IC2-b, Q1, and the timing network comprising D1-D4, C1, R10, and R11. The buffer amplifier is made up of the four remaining gates from IC2, all wired in parallel.

## ELECTRONIC BONGOS

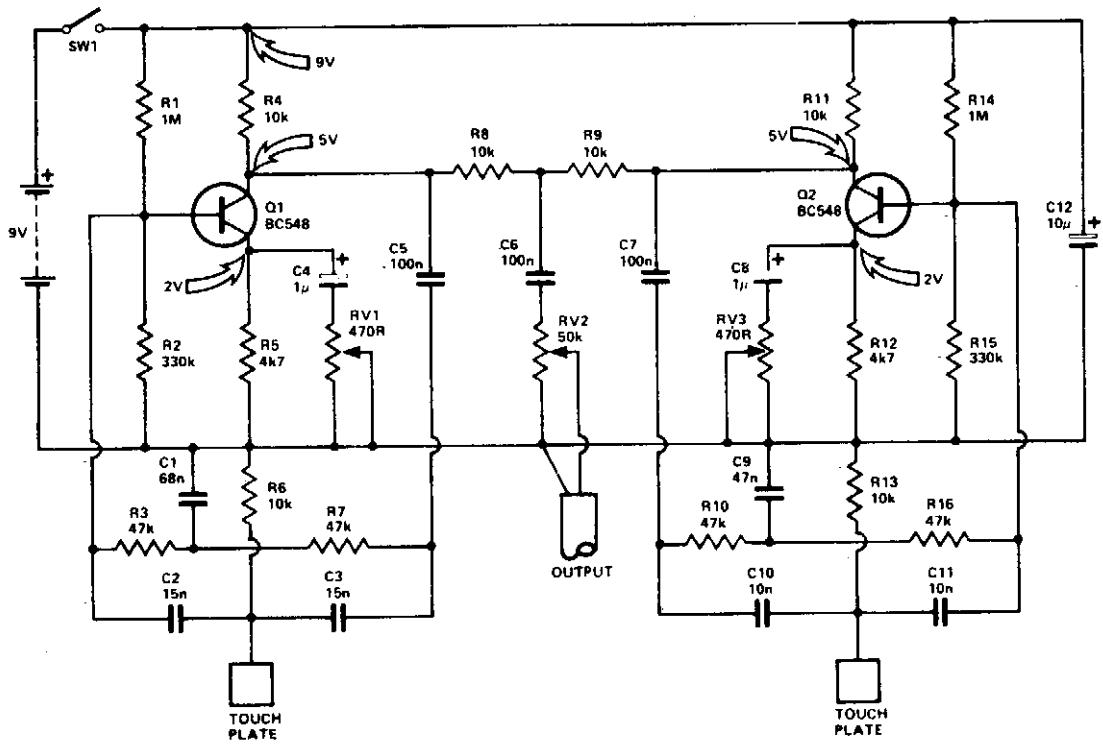


ELECTRONICS TODAY INTERNATIONAL

### Circuit Notes

This circuit consists of twin-T sine-wave oscillators. Each oscillator has a filter in the feedback loop. If the loop gain is greater than unity, the circuit will oscillate. Gain is adjusted to be just less than unity. Touching the touch plate starts the oscillator, but the moment your finger is removed from the touch plate the oscillations will die away. The rate of decay is a function of circuit gain and controlled by RV1 (and RV3).

## TRAIN CHUFFER

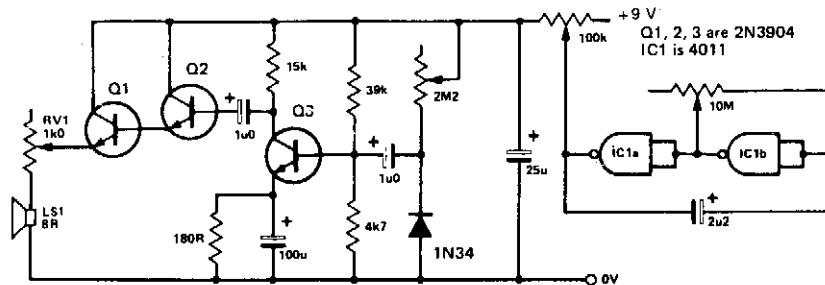


ELECTRONICS TODAY INTERNATIONAL

**Fig. 91-3**

### Circuit Notes

The circuit consists of a white noise generator which only switches on with the high part of the square wave output from the clock circuit. The frequency of the clock is adjusted with the 10 M pot and the output voltage of the clock is adjusted by the 100 k pot (rate and volume of chuff respectively). The 2M2 pot controls the amount of noise produced and the 1 k pot on the speaker controls the pitch of the average noise.

## BIRD CHIRP

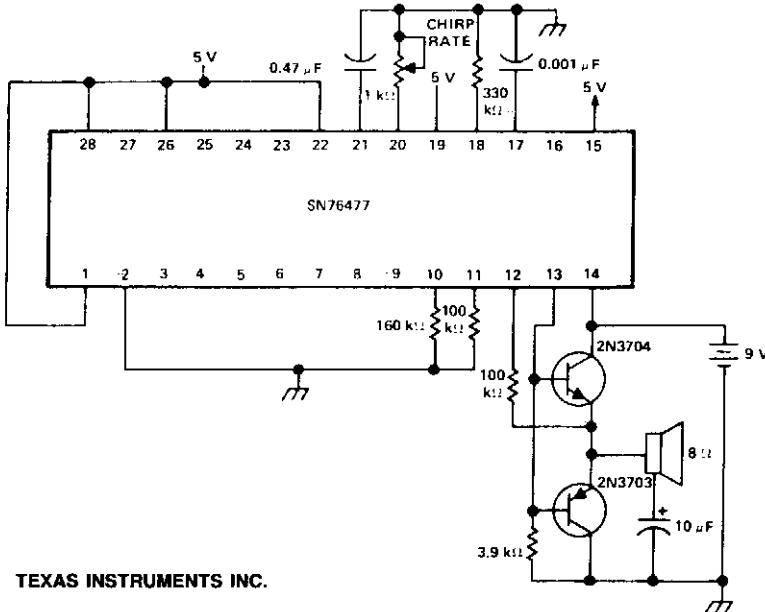


TEXAS INSTRUMENTS INC.

**Fig. 91-4**

### Circuit Notes

For a barking dog, the capacitor at pin 17 is changed to 15 pF to increase the frequency of the VCO.

## STEAM LOCOMOTIVE WHISTLE

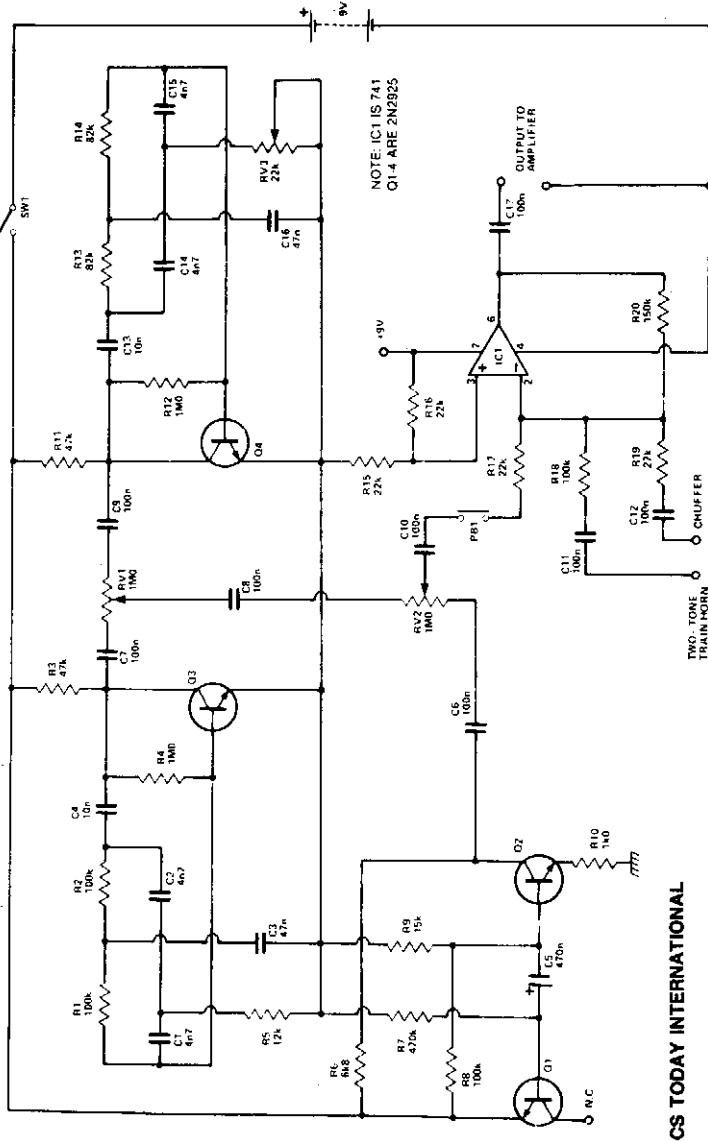

ELECTRONICS TODAY INTERNATIONAL


## Circuit Notes

The waveform of a steam whistle is a complex combination of white noise and an audio frequency oscillation. The noise generator is a transistor (Q1) biased into zener mode. The audio frequency oscillation is a straightforward mixture of two similar (but not identical) sine waves, which after their addition produce a more complex waveshape.

The sine wave generators are twin-t oscillators. Preset RV1 mixes the two sine waves so that an appropriate waveform is obtained. RV2 mixes this waveform with the white noise. Adjustment of all three presets will result in the required sound. Integrated circuit IC1 is an operational amplifier used as a simple mixer/amplifier which combines the steam whistle, chuffer, (generated elsewhere) and two-tone horn sounds into one, suitable for amplification by an external amplifier.

Fig. 91-5

## WAA-WAA CIRCUIT

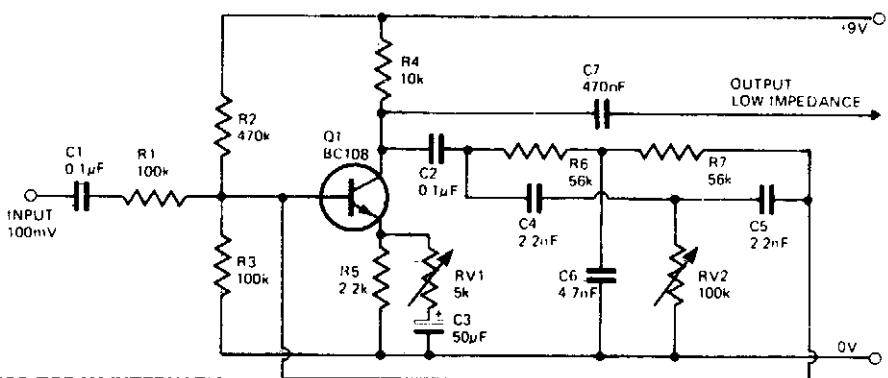


**Fig. 91-6**

ELECTRONICS TODAY INTERNATIONAL

### Circuit Notes

The waa-waa effect is achieved as certain frequencies are amplified more than others. A phase shift RC oscillator makes up the basic circuit. Negative feedback is obtained by feeding part of the signal back to the base. When adjusting initially, RV1 is turned to minimum. RV2 is adjusted to a point at which an audible whistle appears indicating oscillation. RV1 is then adjusted till the oscillation just disappears. It should be possible to set RV2 to any value without any oscillation, this should also be achieved with the minimum possible value of RV1.

## UNUSUAL FUZZ

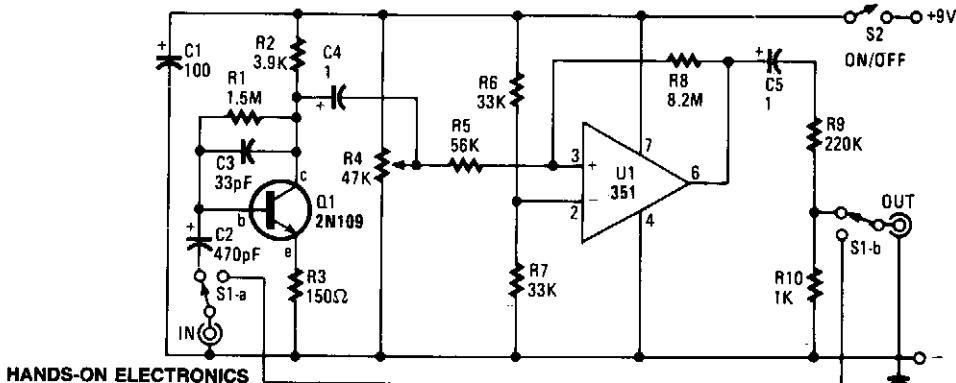


**Fig. 91-7**

HANDS-ON ELECTRONICS

### Circuit Notes

It seems that guitar fuzz boxes have been around since the beginning of rock, and have seen little improvement over the years. This one is somewhat different because rather than simply distorting the sound, it also pulses in step with the peaks of the waveform from the pickup because of the Schmitt trigger op amp circuit. Capacitor C2 requires some explanation. It should normally be a 1- or 2- $\mu$ F electrolytic capacitor. However, we show the value as 470 pF because it's recommended as an experimental value giving far out effects.

## AUTODRUM

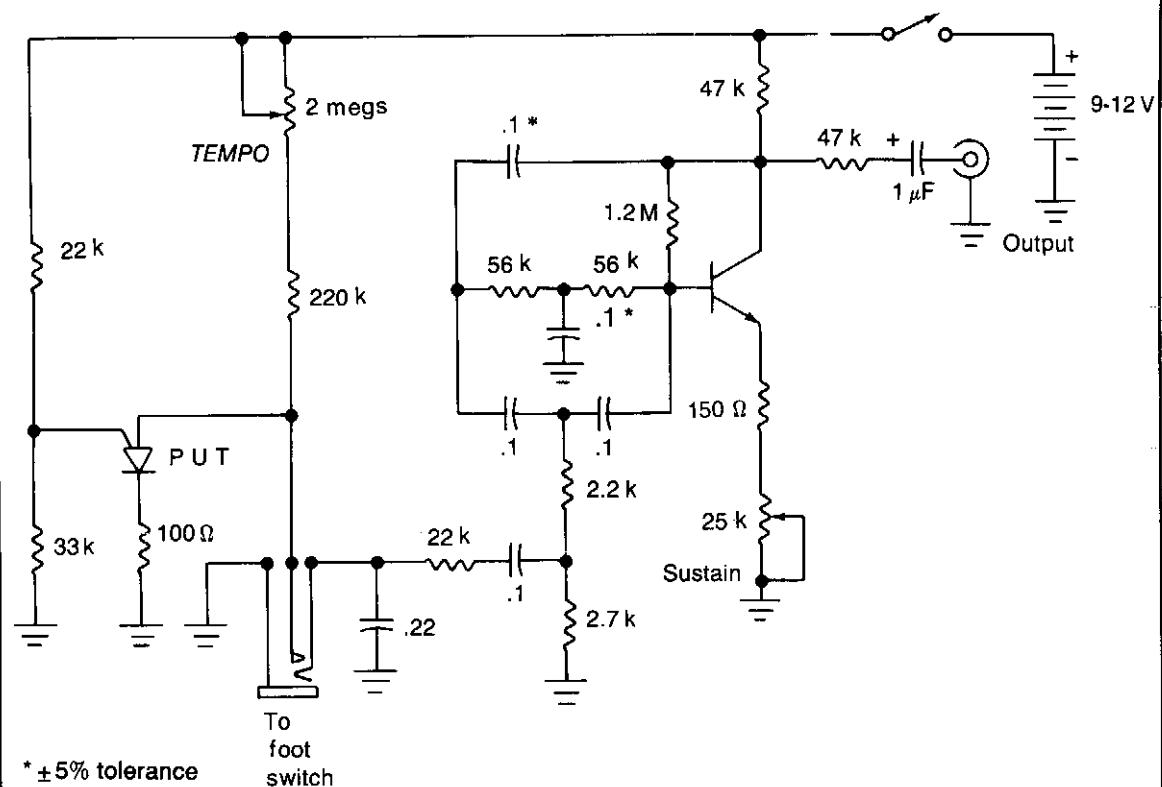


WILLIAM SHEETS

Fig. 91-8

### Circuit Notes

This unit generates a drum-like damped oscillation that sounds best when fed into a higher power amplifier. The beat rate may be determined by operating a foot pedal in much the same manner as for a real drum, or by means of an internal oscillator, the speed of which may be preset.

## TWANG-TWANG CIRCUIT

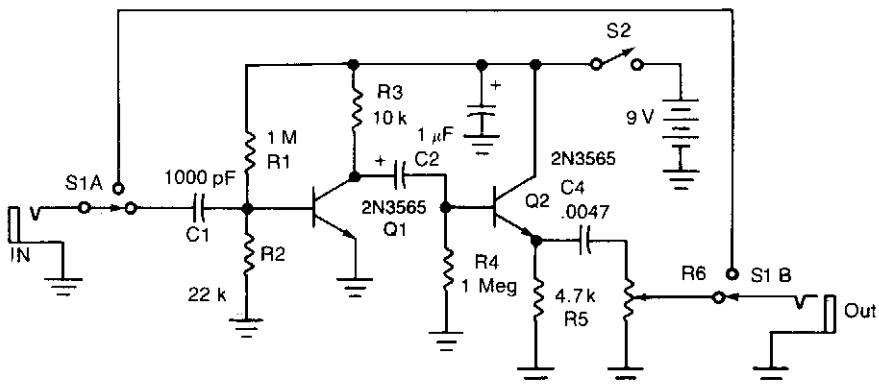


WILLIAM SHEETS

**Fig. 91-9**

### Circuit Notes

Twang is a guitar sound that more or less approximates a banjo or mandolin. The circuit produces unusual sounds from an ordinary electric guitar by cutting the bass, severely distorting the midband and highs, and then amplifying the distortion. S1 cuts the effect in and out, S2 turns the unit on and off.


## STEAM TRAIN/PROP PLANE

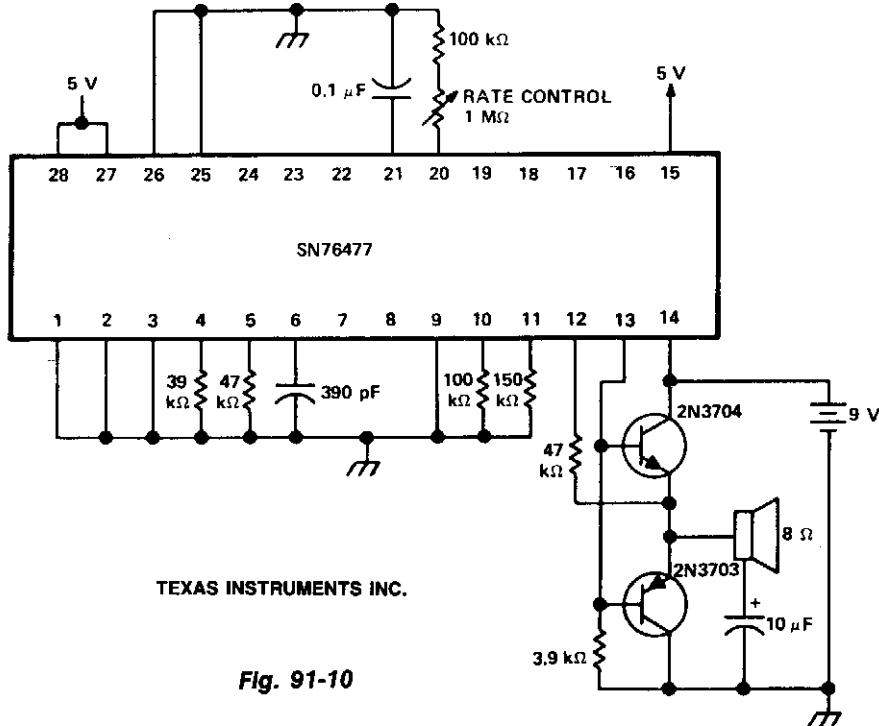

TEXAS INSTRUMENTS INC.

**Fig. 91-10**

## FUNK BOX

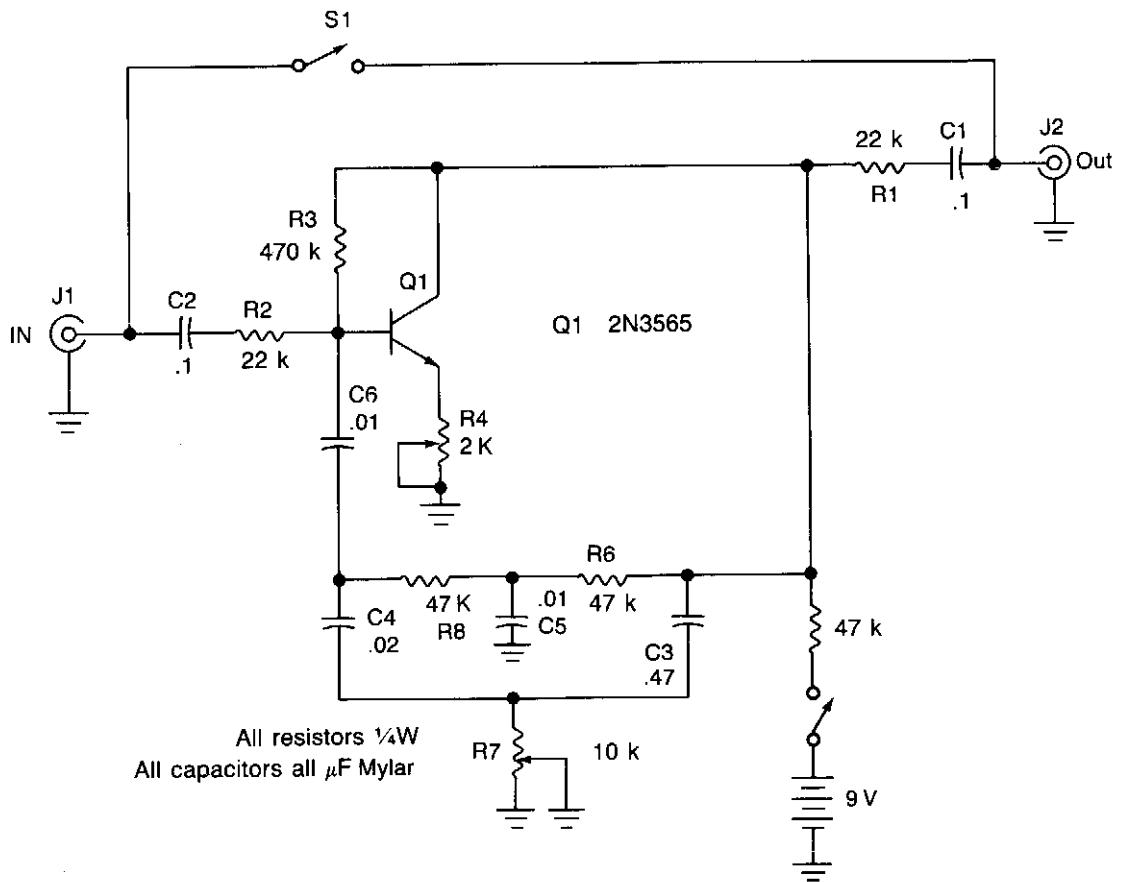

WILLIAM SHEETS

Fig. 91-11

### Circuit Notes

Adjusting potentiometer R7 adds extra twang from way down low to way up high. To set the unit, adjust potentiometer R4 until you hear a whistle (oscillation); then back off R4 until the oscillation just ceases. The effect can be varied from bass to treble by R7.

# 92

## Square-Wave Generators

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Low Frequency TTL Oscillator

Square-Wave Generator Using a 555 Timer

Oscillator with Frequency Doubled Output

CMOS 555 Astable Generates True Rail-to-Rail  
Square Waves

Square-Wave Oscillator

Astable Multivibrator


Two-MHz Square-Wave Generator Uses Two TTL  
Gates

Phase Tracking Three-Phase Generator

Line Frequency Square-Wave Generator

Three Phase Square-Wave Output Generator

## LOW FREQUENCY TTL OSCILLATOR

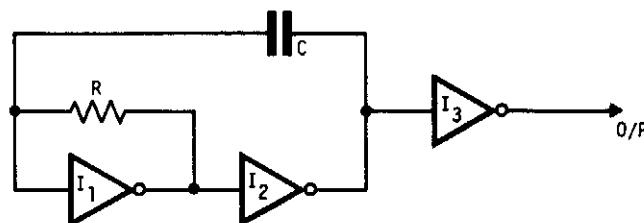


ELECTRONIC ENGINEERING

*Fig. 92-1*

### Circuit Notes

This oscillator uses standard inverters, one resistor and one capacitor, and has no minimum operating frequency. R and C must be chosen such that currents into the gates are below recommended operating limits and that leakage current into the gates and into C are small in comparison with the current in R also the output should be buffered (I3) to prevent variations in load affecting frequency. This circuit may also be used to square up slowly changing logic levels by use of multi input gates (NANDS, NORs Etc).
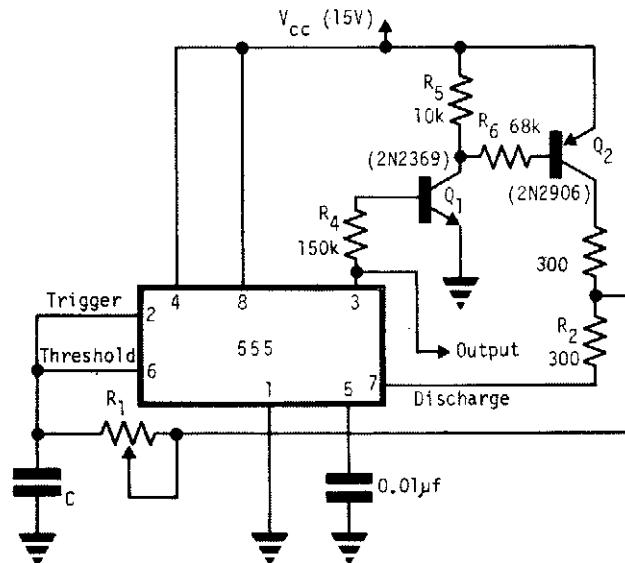
## SQUARE-WAVE GENERATOR USING A 555 TIMER




ELECTRONIC ENGINEERING

*Fig. 92-2*

### Circuit Notes

A single timing resistor ensures that the output is a square (50% duty cycle) wave at all frequency settings.
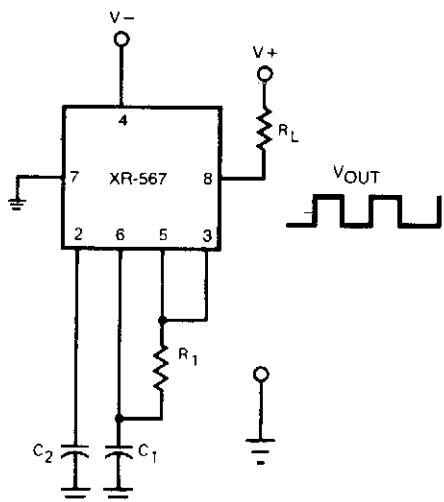
### OSCILLATOR WITH FREQUENCY DOUBLED OUTPUT




EXAR

Fig. 92-3

### Circuit Notes

The current-controlled oscillator frequency can be doubled by applying a portion of the square-wave output at pin 5 back to the input at pin 3, as shown. In this manner, the quadrature detector functions as a frequency doubler and produces an output of  $2 f_0$  at pin 8.
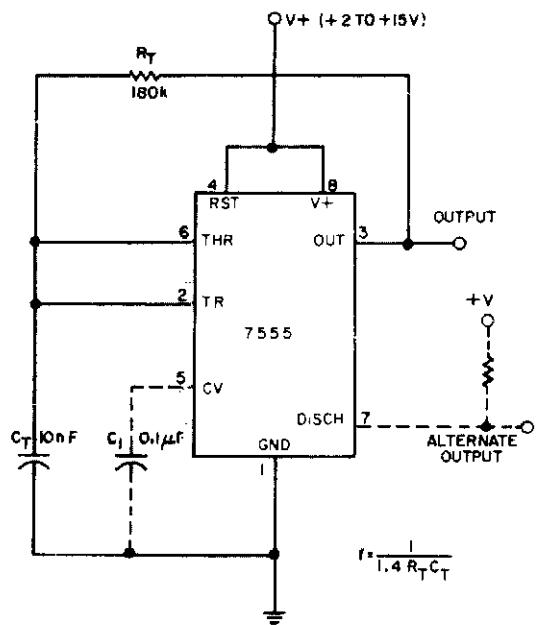
### CMOS 555 ASTABLE GENERATES TRUE RAIL-TO-RAIL SQUARE WAVES



ELECTRONIC DESIGN

Fig. 92-4

### Circuit Notes

A CMOS timer generates true square waves because, unlike the bipolar 555, its output swings from rail to rail. The component values shown give a frequency of about 400 Hz.

## SQUARE-WAVE OSCILLATOR

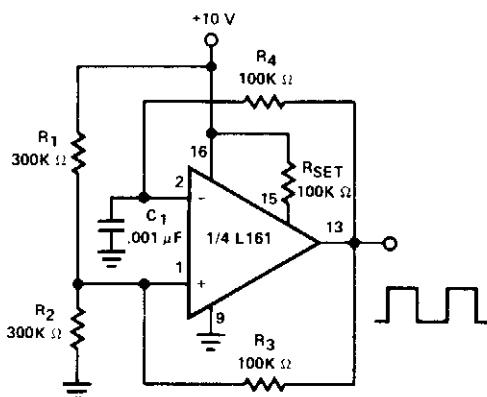


Fig. 92-5

SILICONIX

## ASTABLE MULTIVIBRATOR

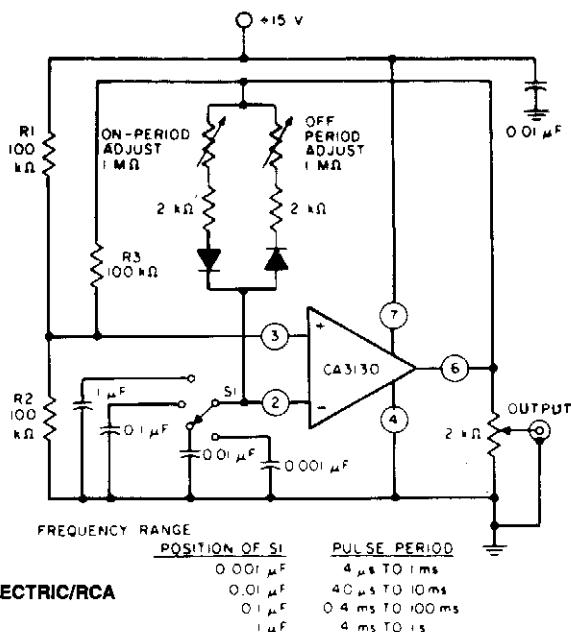



Fig. 92-6

### Circuit Notes

The circuit with independent control of "ON" and "OFF" periods uses the CA3130 BiMOS op amp for filters, oscillators, and long-duration timers. With input current at 50 pA, oscillators can utilize large-resistor/small-capacitor combinations without loading effects.

## TWO-MHz SQUARE-WAVE GENERATOR USES TWO TTL GATES

N.C. = NO CONNECTION

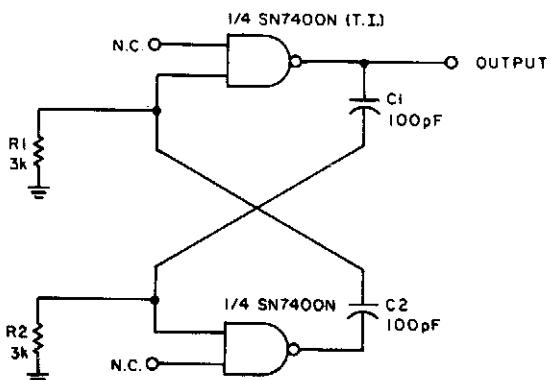


ELECTRONIC DESIGN

Fig. 92-7

### Circuit Notes

With the values shown the circuit generates a 2-MHz symmetrical square wave. Changing capacitors C1 and C2 to 0.01  $\mu$ F results in a frequency of 500 Hz. For the particular integrated circuits and power supply voltages (5.0 V), the reliable operating range of R1 = R2 is 2 k ohm to 4 k ohm.

## PHASE TRACKING THREE-PHASE GENERATOR

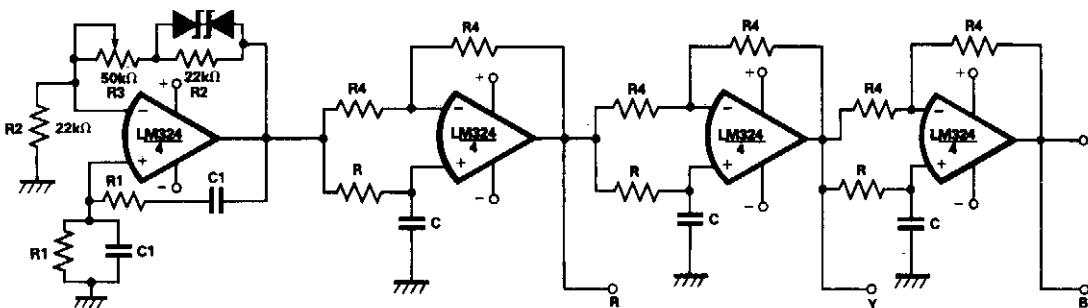


ELECTRONIC ENGINEERING

Fig. 92-8

### Circuit Notes

Using a single chip LM324 can, with active R-C networks, reduce the size of a 3-phase waveform generator, and prove useful in compact and stable 3-phase inverters. One quarter of an LM324 is used as a Wien bridge oscillator generating a pure sinusoidal waveform while the remaining parts of the LM324 are used as three 120° fixed phase shifters. Initially potentiometer R3 should be varied to adjust the loop gain of the oscillator in order to start the oscillator.

### LINE FREQUENCY SQUARE-WAVE GENERATOR

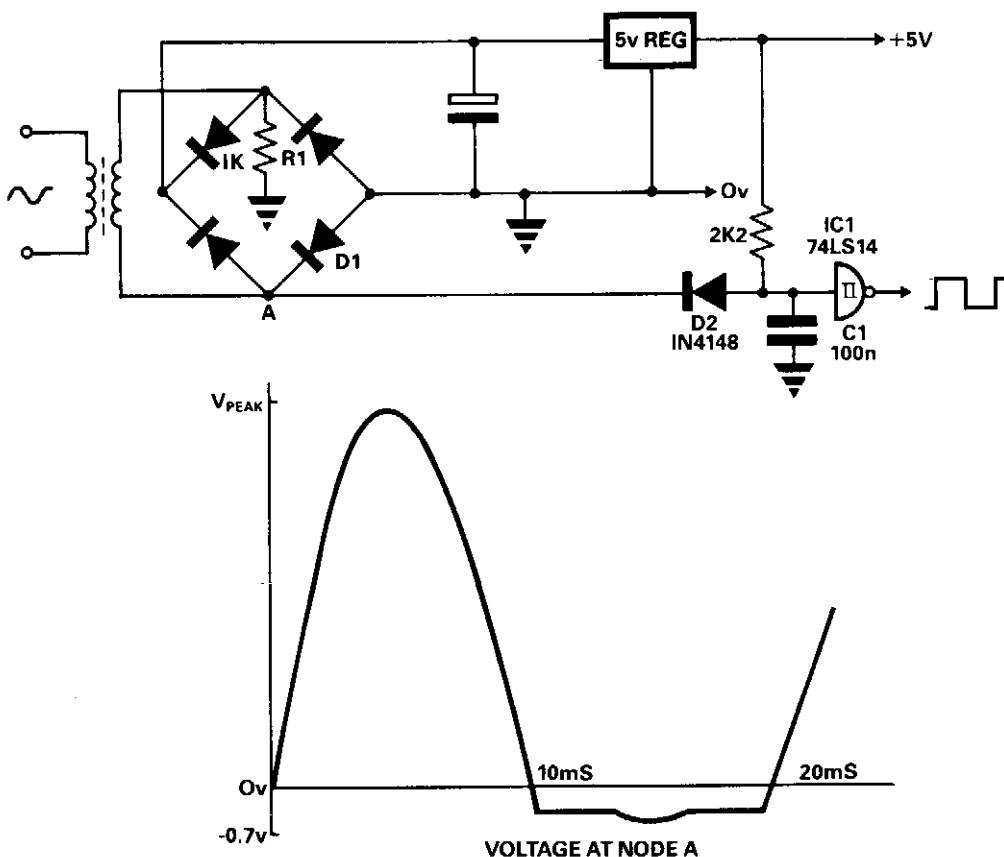

**Fig. 92-9**

ELECTRONIC ENGINEERING

#### Circuit Notes

With only three components and a buffer, a line frequency square wave having a 1:1 duty cycle may be derived from the power supply. During the alternate half-cycle, however, A is effectively clamped to  $-0.7\text{ V}$  by D1 in the bridge which offsets the forward voltage across D2 giving an input to IC1 of approximately  $0\text{ V}$ . When A rises above  $+5\text{ V}$ , D2 is reverse biased and remains at  $+5\text{ V}$ . R1 is needed to load the transformer secondary maintaining a distortion-free waveform at A during the time the diode bridge is not conducting. C1 although not essential may be required to remove transients.

### THREE PHASE SQUARE-WAVE OUTPUT GENERATOR

Fig. 1

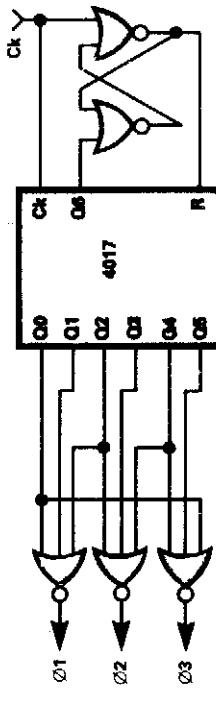


Fig. 2

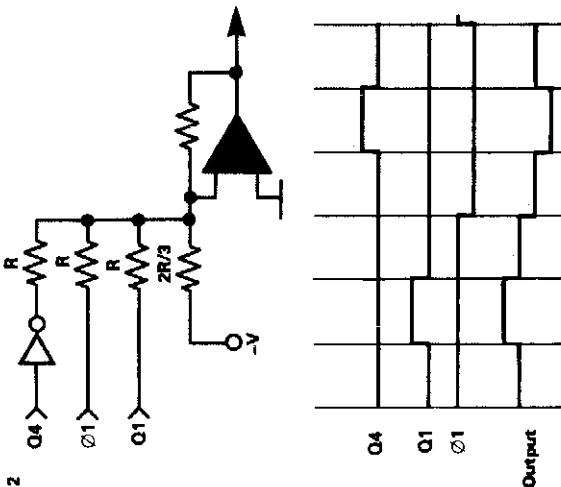


Fig. 92-10

ELECTRONIC ENGINEERING

#### Circuit Notes

This circuit gives a 3 phase square-wave output for a variable speed motor drive. Operation is straightforward, the 4017 counter is synchronously reset after six clock inputs. The six outputs are combined to give the required waveforms. It is interesting to note that although NOR gates are shown, OR gates will give effectively the same result. The circuit can be extended as shown in Fig. 2 to give pseudo-sine waves if that is required, but that will diminish the simplicity of the circuit.

## **93**

# **Staircase Generator Circuits**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Staircase Generator  
Staircase Generator II

## STAIRCASE GENERATOR

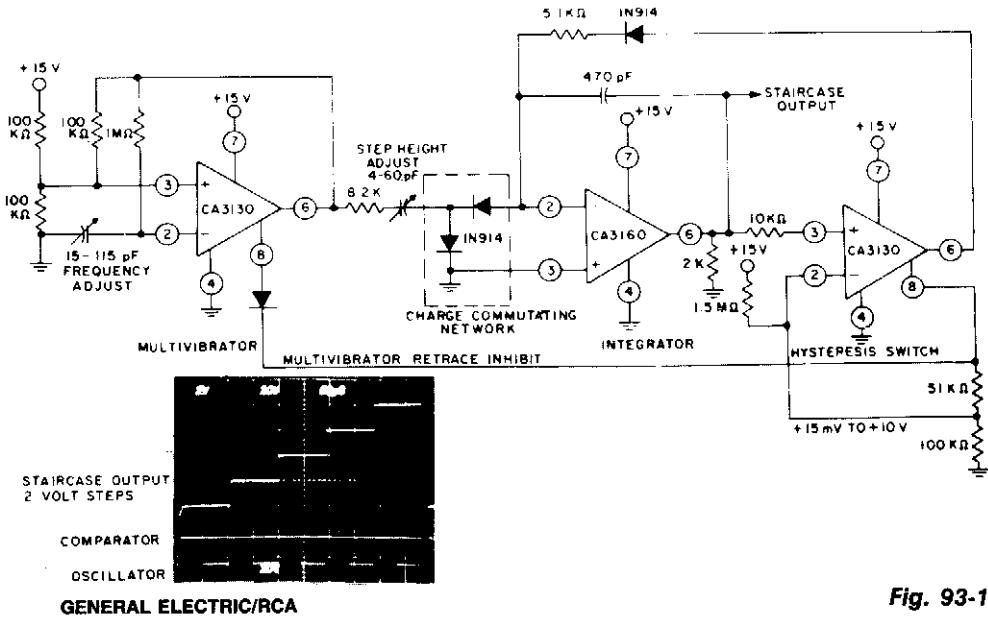


Fig. 93-1

### Circuit Notes

The circuit uses three BiMOS op amps. Two CA3130's are used, one as a multivibrator and the other as a hysteresis switch. The third amplifier, a CA3160, is used as a linear staircase generator.

## STAIRCASE GENERATOR II

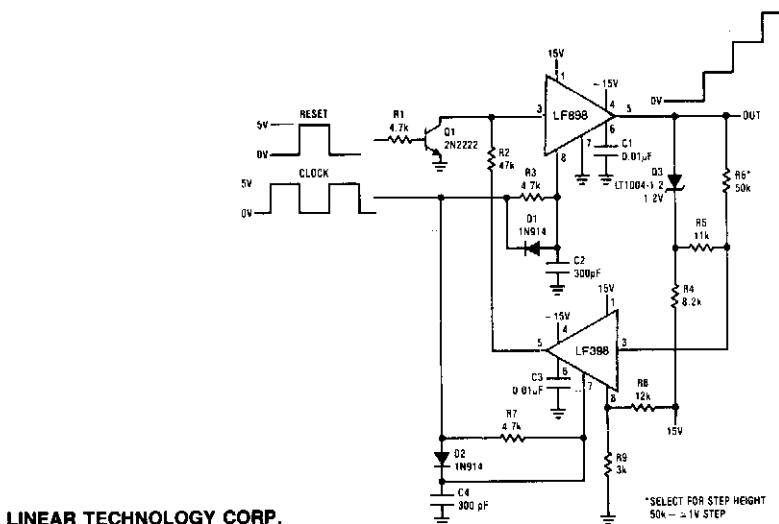


Fig. 93-2

**94**

## **Stereo Balance Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Stereo Balance Tester  
Stereo Balance Meter

## STEREO BALANCE TESTER

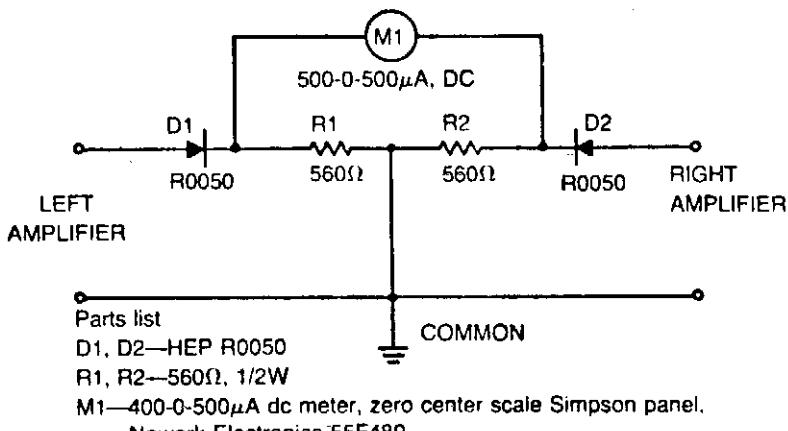


TAB BOOKS INC.

*Fig. 94-1*

### Circuit Notes

The meter will show volume and tone control balance between left and right stereo amplifiers. For maximum convenience the meter is a zero-center type. Resistors are five percent or better and the diodes a matched pair. Optimum stereo level and phase balance occurs for matched speakers when the meter indicates zero. If the meter indicates either side of zero, the levels are not matched or the wires are incorrectly phased. Check phasing by making certain the meter leads are connected to the amplifier hot terminals and the common leads go to ground.

## STEREO BALANCE METER

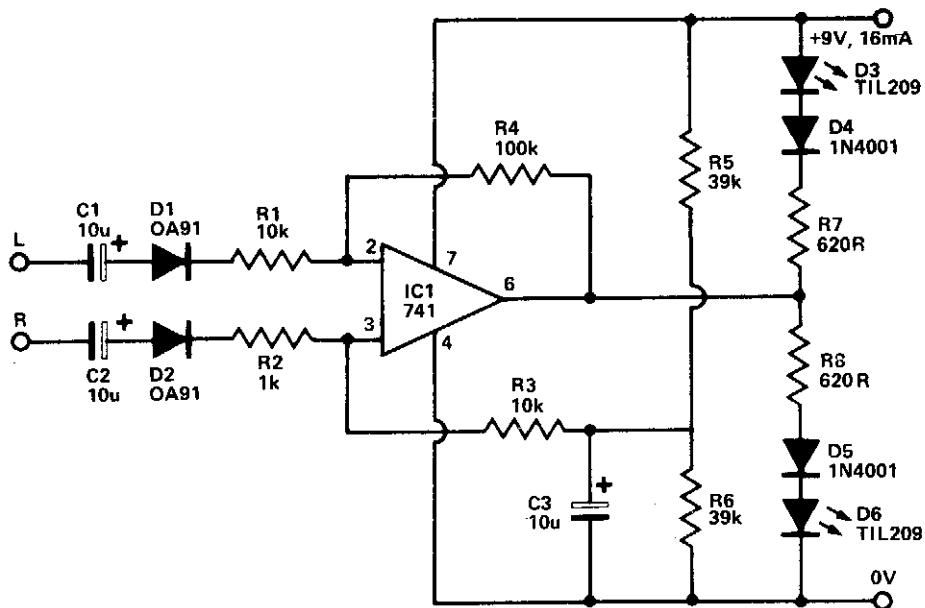

ELECTRONICS TODAY INTERNATIONAL

*Fig. 94-2*

### Circuit Notes

To use the indicator, switch the amplifier to mono mode and adjust the balance control until both LEDs are equally illuminated. The amplifier is now in perfect stereo mode balance.

# **95**

## **Strobe Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Simple Strobe  
Safety Flare  
Disco-Strobe Light

## SIMPLE STROBE

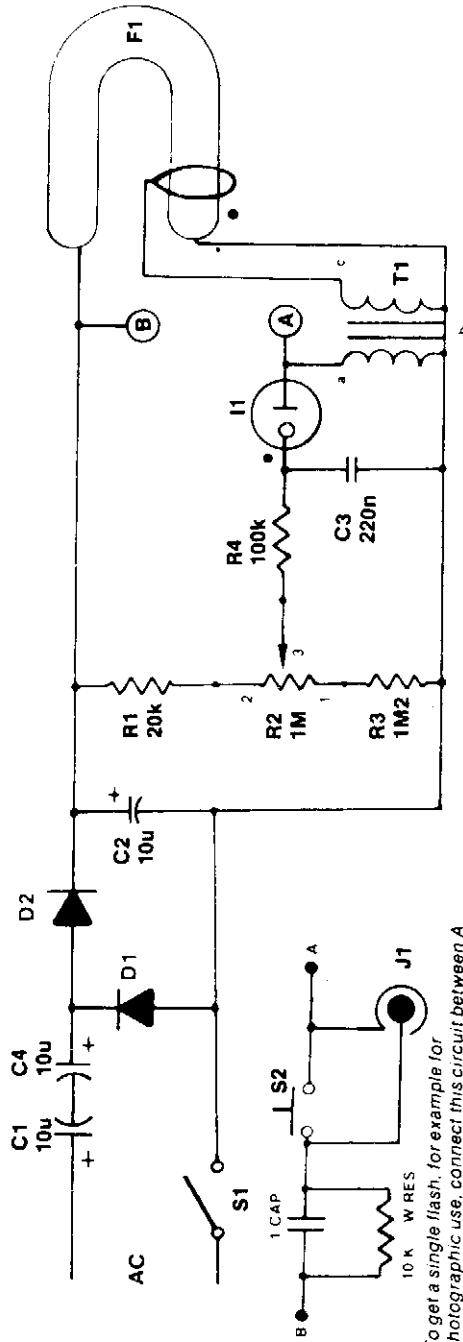


ELECTRONICS TODAY INTERNATIONAL

Fig. 95-1

### Circuit Notes

Initially the neon and xenon lamps are not conducting and act like a very high (almost infinite) resistance. Capacitors C1 and C4 in conjunction with D1 and D2 form a voltage doubler circuit, which can charge C2 up to about 300 Vdc after several ac cycles. Voltage increases as current is supplied through R1 and R2. Neon bulb II will all of a sudden start to conduct when the voltage across C3 reaches II's ionization potential. While conducting, the resistance of the bulb will be relative low. Due to this sudden conduction, a pulse of current will pass through the primary of T1. The turns ratio is such that about 400 V will be developed at the secondary. The xenon tube is similar to the neon bulb in that it produces light when the gas ionizes and conducts. However, it is designed so that an external signal (the 4 kV on the metal ring around the tube) ionizes the gas and initiates the conduction. When F1 conducts, it discharges C2. At this point, the whole cycle starts over again. The purpose of R2 is to vary the rate at which C3 charges, and hence the repetition rate of the strobe.


## SAFETY FLARE

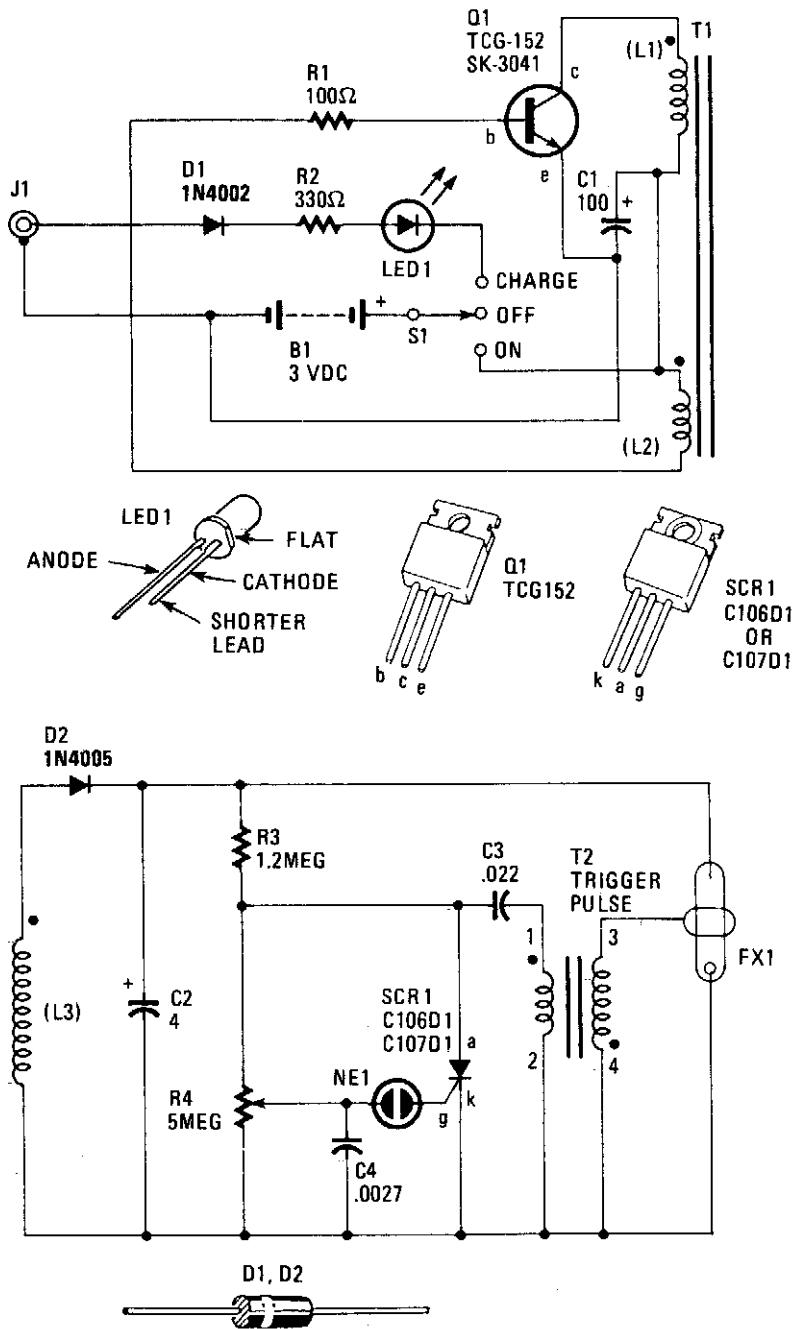

### **Circuit Notes**

When S1 is on, power is applied to an oscillator composed of Q1, R1, C1, L1, and L2. Coil L1 is the primary winding of T1, and L2 is the feedback winding. When Q1 turns on, its collector current saturates T1's ferrite core. That, in turn, removes the base drive to Q1 through L2. Transistor Q1 then turns off. As the field around L1 and L2 decays, Q1 will eventually turn on again, and the cycle repeats over, and over. Transformer T1 is a step-up, ferrite-core, potted-type unit whose secondary-winding (L3) output is rectified by D2 and filtered by C2. That capacitor charges up to around 250 to 300 volts, which is applied to the resistor divider composed of R3 and R4, along with the flash tube FX1. Capacitors C3 and C4 will charge up to around 200 and 100 volts, through R3 and R4, respectively. Flash rate is adjustable via R4. When the charge on C4 gets to around 100 volts, neon lamp NE1 fires discharging C4 into the gate circuit of silicon control rectifier SCR1. The SCR1 turns on discharging C3 into the primary winding of trigger-pulse transformer T2. Transformer T2 is another step-up, pulse-type unit providing an output of around 4 kW across transformer T2's secondary winding. The xenon gas inside FX1 is ionized and a bright flash is emitted. Finally, C3 quickly discharges through L4, and the cycle repeats over, and over.

### DISCO-STROBE LIGHT

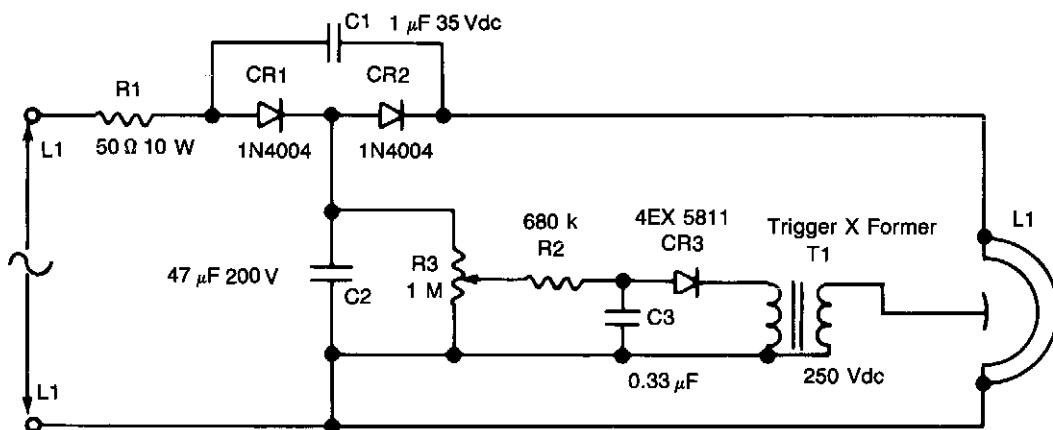

WILLIAM SHEETS

*Fig. 95-3*

#### Circuit Notes

This circuit uses a voltage doubler CR1 and CR2 to obtain about 280 V dc across C1. C2 and R3 form a voltage divider to obtain a dc voltage to change C3 thru R2. When CR3 fires, a high voltage is generated in T1, firing L1.

# **96**

## **Switch Circuits**

---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Solid State Stepping Switch  
AC-Static SPDT Switch

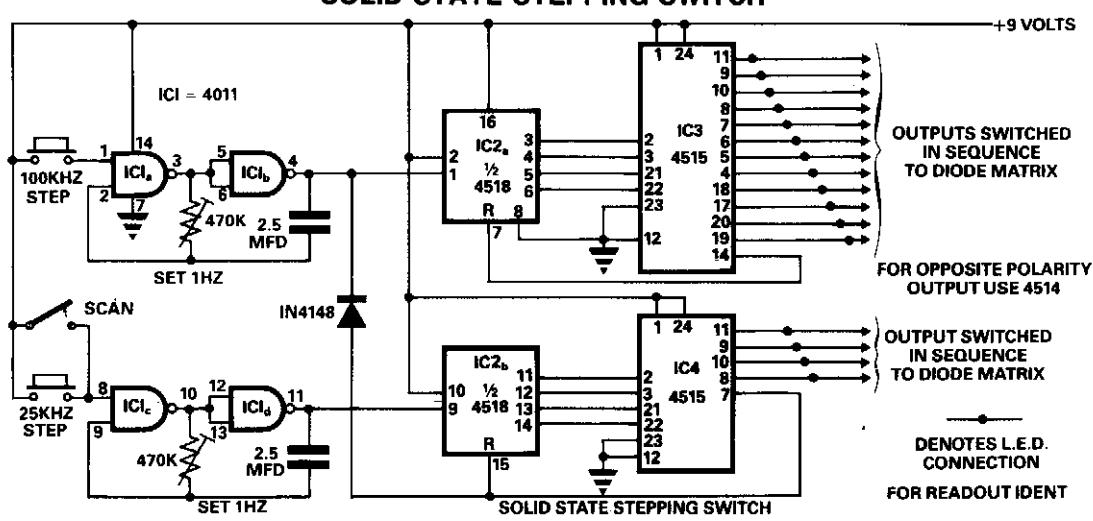


Fig. 96-1

#### Circuit Notes

This circuit was designed to make switching of a 48-channel mobile transceiver safe to operate while mobile. The oscillators allow for single-stepping or a scanning function. The scan facility allows for stepping through all 48 channels to check for occupancy or otherwise, and each output is indicated with an LED and labeled accordingly, so at-a-glance indication is possible. With full scope of this circuit it is possible to scan 256 channels and by adding more 4 to 16 line encoders etc. you could switch to any required number.

#### AC-STATIC SPDT SWITCH

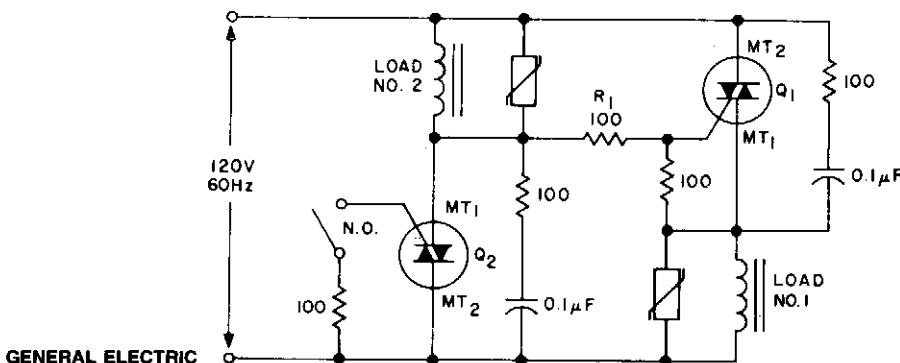


Fig. 96-2

#### Circuit Notes

An SPDT solid state relay is shown. When voltage is applied Q1 will turn on, activating load #1, because the full line voltage appears across Q2, supplying gate current through R1. When S1 is closed, Q2 turns on removing the gate drive from Q1 and activating load #2.

# **97**

## **Tape Recorder Circuits**

---

---

**T**he sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Tape Recorder Interface

Tape Recorder Position Indicator/Controller

## TAPE RECORDER INTERFACE


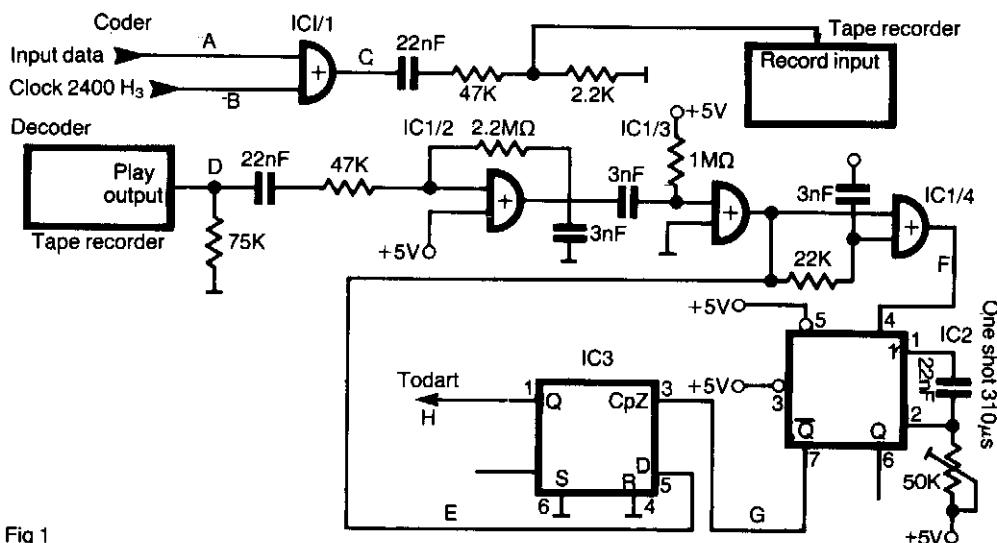


Fig 1

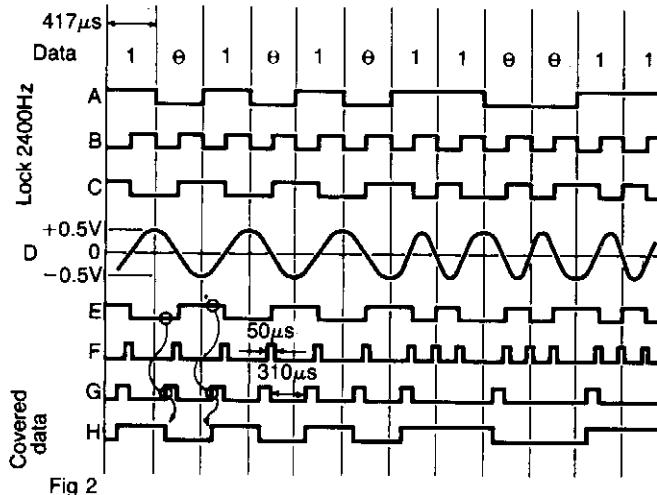

ELECTRONIC ENGINEERING

**Fig. 97-1**

### Circuit Notes


The interface allows data to be saved on an ordinary tape recorder at a speed of 2400 bit/s.

The serial stream of data Fig. 1 (A) is coded with a clock of 2400 Hz (B), by means of XOR gate IC 1/1. Logical "high" and "low" appear as shown in Fig. 2 (C). These impulses are lowered in amplitude and feed into the record input of a low cost tape recorder.

## TAPE RECORDER INTERFACE, Continued.

During the playback, pulses (D) are amplified with CMOS gate IC 1/2 connected as a linear amplifier, and providing a TTL level signal shown in (E). On both positive and negative transitions IC 1/4 forms short pulses as shown in (F) (approx. 50  $\mu$ s) that triggers one shot IC2. A monostable one shot pulse width is adjusted to be  $\frac{1}{4}$  of bit length (310  $\mu$ s). A change from "high" to "low" in a coded stream generates a "low" pulse width of one bit cell. The same is for change from "low" to "high" that generates a "high" pulse of the same width. During this pulse one shot latches the state of line E in D type flip-flop IC3 (G). When a stream consists of multiple "ones" or "zeros," the one shot is retriggered before it comes to the end of the quasistable state and the state of the flip-flop remains unchanged. The original data stream is available at the output of the flip-flop (H). Z80 the DUART that receives these pulses is programmed so that the receiver clock is 16 times the data rate (38.4 kHz).
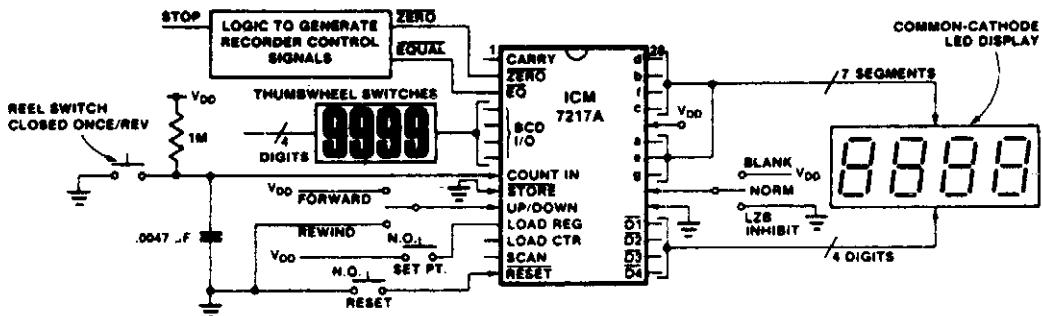
### TAPE RECORDER POSITION INDICATOR/CONTROLLER



INTERSIL

Fig. 97-2

#### Circuit Notes

This circuit is representative of the many applications of up/down counting in monitoring dimensional position. In the tape recorder application, the LOAD REGISTER, EQUAL, and ZERO outputs are used to control the recorder. To make the recorder stop at a particular point on the tape, the register can be set with the stop at a particular point on the tape, the register can be set with the stop point and the EQUAL output used to stop the recorder either on fast forward, play or rewind.

To make the recorder stop before the tape comes free of the reel on rewind, a leader should be used. Resetting the counter at the starting point of the tape, a few feet from the end of the leader, allows the ZERO output to be used to stop the recorder on rewind, leaving the leader on the reel. The 1 M ohm resistor and .0047  $\mu$ F capacitor on the COUNT INPUT provide a time constant of about 5 ms to debounce the reel switch. The Schmitt trigger on the COUNT INPUT of the ICM7217 squares up the signal before applying it to the counter. This technique may be used to debounce switchclosure inputs in other applications.

## 98

# Telephone-Related Circuits

---


---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Speech Activity Detector for Telephone Lines  
Scramble Phone  
Musical Telephone Ringer  
Dual Tone Decoding  
Automatic Telephone Recording Device  
Telephone Ringing Detector, Frequency and Volume Controlled  
Music on Hold  
Circuit Monitors Blinking Phone Lights  
Phone Light  
High Isolation Telephone Ringer

Remote Telephone Monitor  
Plug-In Remote Telephone Ringer  
Telephone Hold Button  
Telephone Blinker  
Telephone "In Use" Indicator  
Tone Ringer  
Tone Ringer II  
Speakerphone  
Speech Network  
Programmable Multi-Tone Telephone Ringer
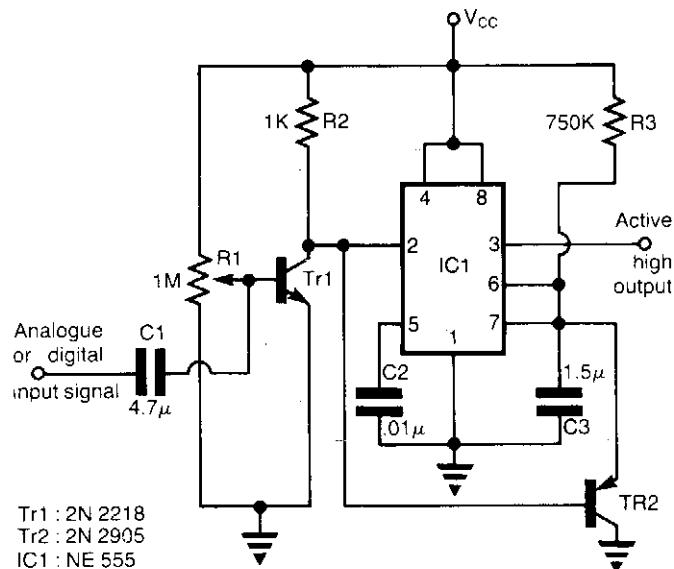
## SPEECH ACTIVITY DETECTOR FOR TELEPHONE LINES



ELECTRONIC ENGINEERING

Fig. 98-1

### Circuit Notes


The circuit can be used in telephone lines for speech activity detection purposes. This detection is very useful in the case of half-duplex conversation between two stations, in the case of simultaneous transmission of voice and data over the same pair of cables by the method of interspersion data on voice traffic, and also in echo suppressor devices. The circuit consists of a class-A amplifier in order to amplify the weak analog signals (in the range 25-400 mW of an analog telephone line).

The IC1 is connected as a retriggerable monostable multivibrator with the Tr2 discharging the timing capacitor C3, if the pulse train reaches the trigger input 2 of IC1 with period less than the time:

$$T_{\text{high}} = 1.1 (R3 C3)$$

The output 3 of IC1 is active ON when an analog or digital signal is presented at the output and it drops to low level,  $T_{\text{high}}$  seconds after the input signal has ceased to exist.

## SCRAMBLE PHONE

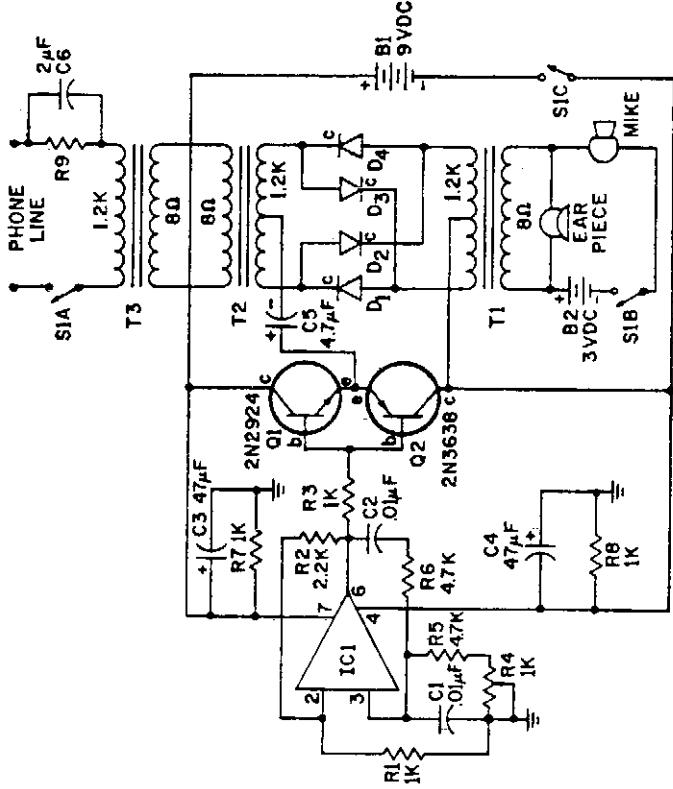

**B1**—9-volt battery, Eveready 216 or equiv.  
**B2**—3-volt battery, two AA penlight cells  
**C1**, **C2**—0.01  $\mu$ F polystyrene capacitor, 100 V  
**series**

Q2—PNP transistor, 2N3638, HEP-716  
 R1, R3, R7, R8—1000-ohm,  $\frac{1}{2}$ -watt resistor  
 R2—2,200-ohm  $\frac{1}{2}$ -watt resistor

**Misc.**—Surplus telephone (see *Lafayette*, *Radio Shack*, *ED1*, *BA catalogs*), battery holders, hardware, knob, wire, solder, etc.

Circuit Notes

IC-1 and the associated circuitry form a stable audio tone generator that feeds a buffer amplifier, Q1 and Q2. The tone output is taken from the emitters of the transistor pair to supply a carrier voltage for a balanced modulator made up of four diodes—D1 through D4—and T1 and T2. If the two transformers and the four diodes are perfectly matched (which is almost impossible to achieve and not necessary in any case) no carrier will appear at the input or output of T1 or T2. In a practical circuit, a small amount of unbalance will occur and produce a low-level carrier tone at the input and output of the balanced modulator. A telephone carbon mike and earpiece are connected to the low impedance winding of T1, with a three volt battery supplying the necessary mike current. Trim potentiometer R4 is used to make a fine frequency adjustment of the oscillator so that two scrambler units may be synchronized to the same carrier frequency.  $R_g$  limits line current to 25 mA.

Fig. 98-2

## MUSICAL TELEPHONE RINGER

### Circuit Notes

The heart of the circuit is IC1, General Instrument's AY-3-1350 melody synthesizer IC. IC2 is a TCM1512 telephone ring detector IC that is powered by the telephone line. The circuit's operation begins when IC2 senses a ringing pulse on the telephone line. The detector (internally) rectifies the ring signal and then outputs a voltage to relay RY1 (an SPST reed-type relay with 5 volt contacts), causing its contacts to close. That pulls pin 12 (the ON/OFF control) of IC1 low (logic "0"), causing it to output a signal—the selected tune—to transistor amplifier Q2. The amplified signal is then fed to the speaker. The melody continues to play either until the tune is finished (at which time IC1 returns to the standby mode), or until someone takes the phone off the hook. Taking the phone off the hook discontinues the ring pulses to IC2, which opens RY1. When the relay contacts open, pin 12 of IC1 goes high, returning the circuit to the standby mode to wait for the next incoming phone call.

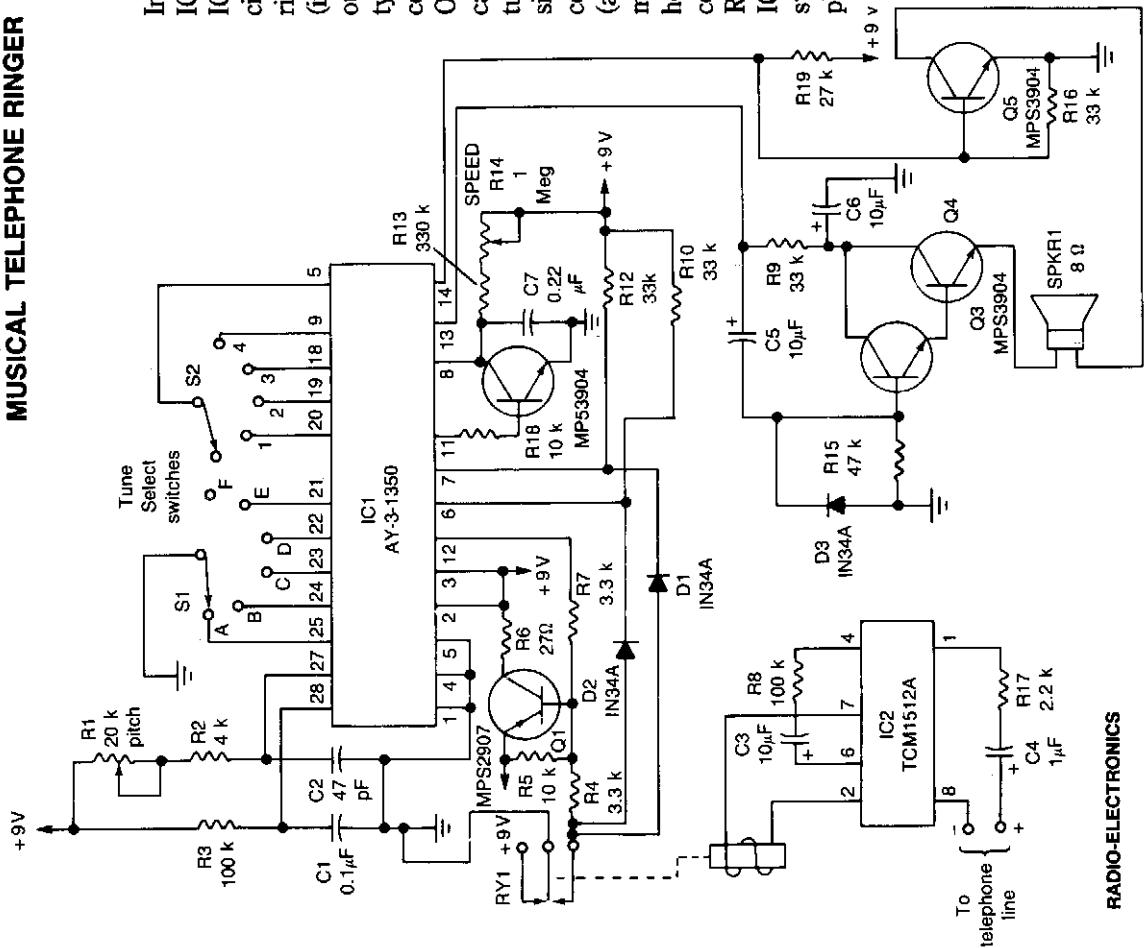


Fig. 98-3

## DUAL TONE DECODING

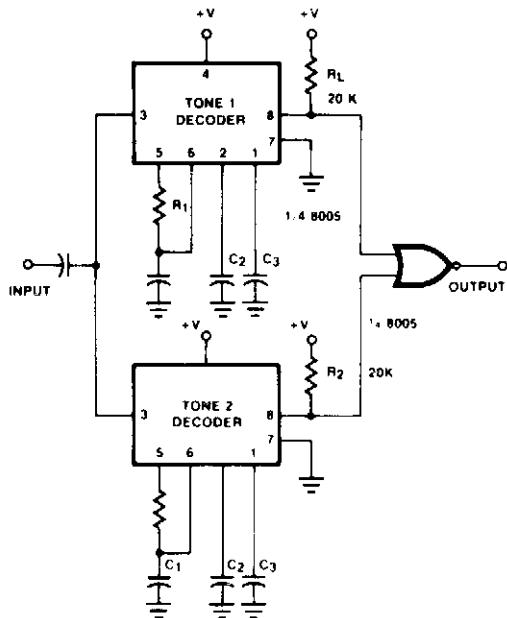


Figure 1A. Detection of Two Simultaneous or Sequential Tones

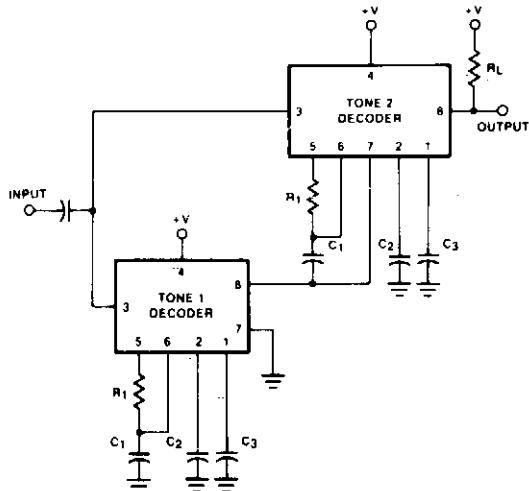


Figure 1C

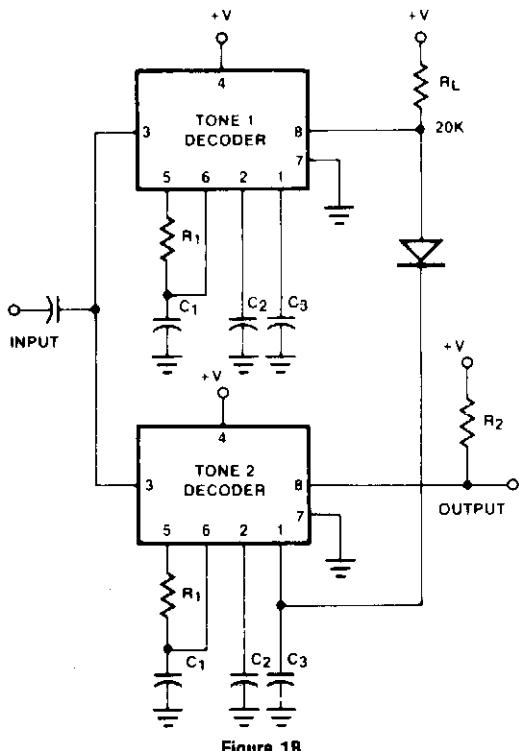


Figure 1B


EXAR

*Fig. 98-4*

### Circuit Notes

Two integrated tone decoders, XR-567 units, can be connected (as shown in Fig. 1A) to permit decoding of simultaneous or sequential tones. Both units must be on before an output is given.  $R_1C_1$  and  $R'_1C'_1$  are chosen, respectively, for Tones 1 and 2. If sequential tones (1 followed by 2) are to be decoded, then  $C_3$  is made very large to delay turn-off of Unit 1 until Unit 2 has turned on and the NOR gate is activated. Note that the wrong sequence (2 followed by 1) will not provide an output since Unit 2 will turn off before Unit 1 comes on. Figure 1B shows a circuit variation which eliminates the NOR gate. The output is taken from Unit 2, but the Unit 2 output stage is biased off by  $R_2$  and  $C_1R_1$  until activated by Tone 1. A further variation is given in Fig. 1C. Here, Unit 2 is turned on by the Unit 1 output when Tone 1 appears, reducing the standby power to half. Thus, when Unit 2 is on, Tone 1 is or was present. If Tone 2 is now present, Unit 2 comes on also and an output is given. Since a transient output pulse may appear at Unit 1 turn-on, even if Tone 2 is not present, the load must be slow in response to avoid a false output due to Tone 1 alone. The XR-267 Dual Tone Decoder can replace two integrated tone decoders in this application.

## AUTOMATIC TELEPHONE RECORDING DEVICE

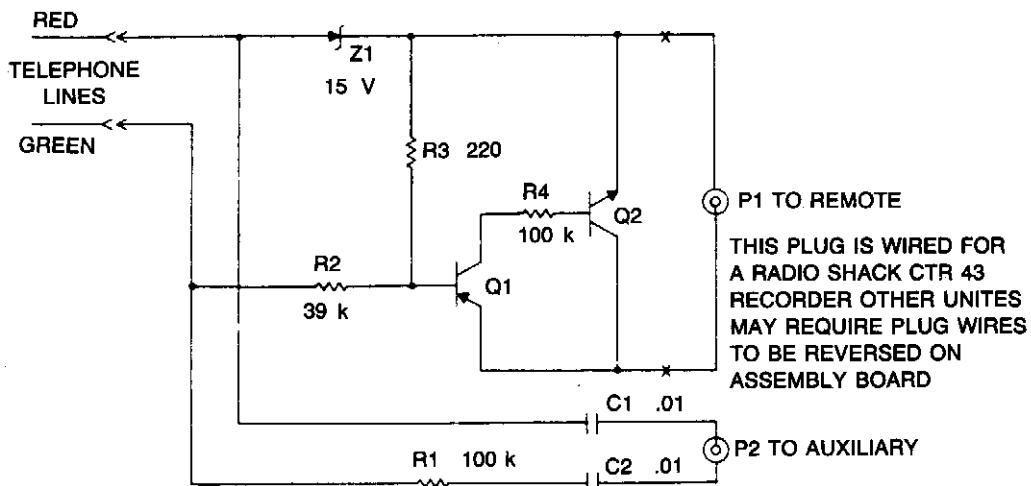

CONNECT TO ANY CONVENIENT PHONE JACK OR WHEREVER ACCESS TO WIRES IS AVAILABLE. MAY BE CONNECTED VIA ALLIGATOR CLIPS, PLUGS OR MODULAR PLUG.

SPECIAL NOTE  
SEE TEXT


TAB BOOKS, INC.

*Fig. 98-5*

### Circuit Notes

The device is a dc switch that is normally on via the forward biasing of Q1 via R3. Q1 now clamps Q2 into a forward state by biasing its complement well into a saturated state via R4. The dc switch is turned off via a negative voltage above that of the zener (D1). This voltage is usually about 48 and is the on-hook value of the phone line. This negative voltage overrides the effect of R3 and keeps the circuit "off." When the phone is off the hook, the 48 volts drops to 10 volts, that is below the zener voltage of D1 and R3 now turns the circuit on. The audio signal is via attenuator resistor R1 and dc isolating capacitors C1, C2. The device is a high impedance switch that isolates the recording controlled device from the phone line via some relatively simple electronic circuitry. It requires no battery and obtains power for operating via the remote jack that in most recorders is a source of 6 volts. When clamped to ground it initiates recorder operation. The unit interfaces with most portable cassette recorders providing they contain a remote control jack.
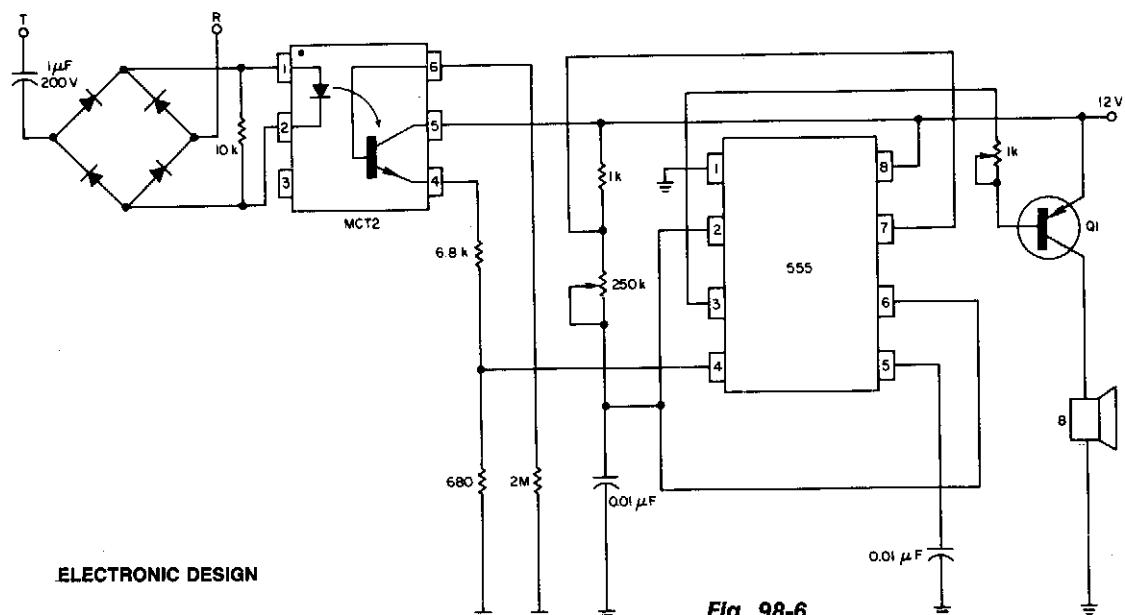
## TELEPHONE RINGING DETECTOR, FREQUENCY AND VOLUME CONTROLLED




ELECTRONIC DESIGN

**Fig. 98-6**

### Circuit Notes

With the 555 timer connected as a multivibrator and an opto-isolator, a remote speaker can be driven.

## MUSIC ON HOLD

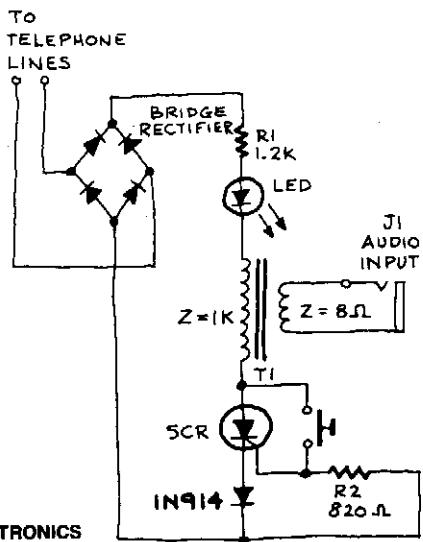


RADIO-ELECTRONICS

### Circuit Notes

With this music-on-hold device, you can answer the phone in one room, place the caller on hold, and then pick up the phone again at another location. When you pick up the phone the second time, you automatically deactivate the music-on-hold feature and can continue your conversation.

**Fig. 98-7**

## CIRCUIT MONITORS BLINKING PHONE LIGHTS

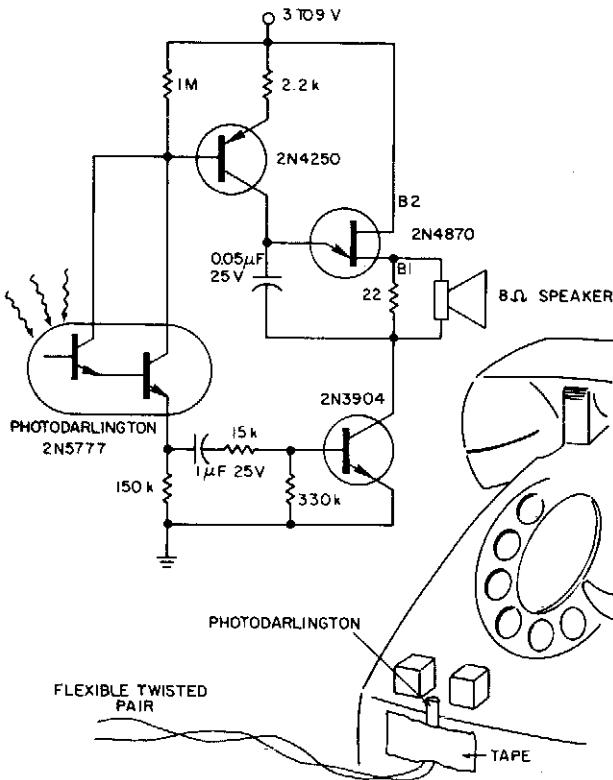


**Fig. 98-8**

ELECTRONIC DESIGN

### Circuit Notes

A 2N5777 photo-Darlington cell picks up blinking light from the transparent plastic buttons. The power is switched ON and OFF by a hi-beta 2N3904 transistor. The circuit's 9 V battery can be left continuously connected. Less than a micro-ampere is drawn—even with normal, office ambient light and the phone lights not flashing. For noisy locations, the tone can be made louder with an output transformer (ratio of 250:8) or a 100 ohm speaker that replaces the 22 ohm resistor in the output.

## PHONE LIGHT

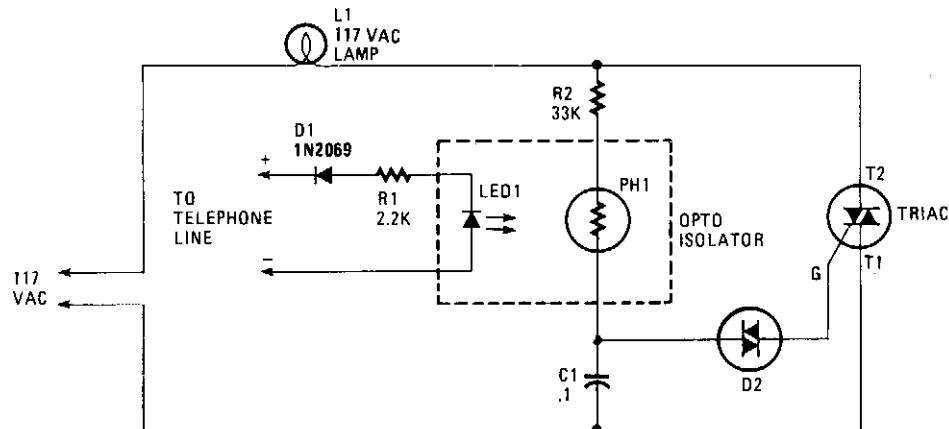


HANDS-ON ELECTRONICS

**Fig. 98-9**

### Circuit Notes

When the phone does ring the triac is triggered into conduction by a signal applied to its gate (G) through a bilateral switch (diac), D2. The triac acts as a switch, conducting only when a signal is present at the gate.

## HIGH ISOLATION TELEPHONE RINGER

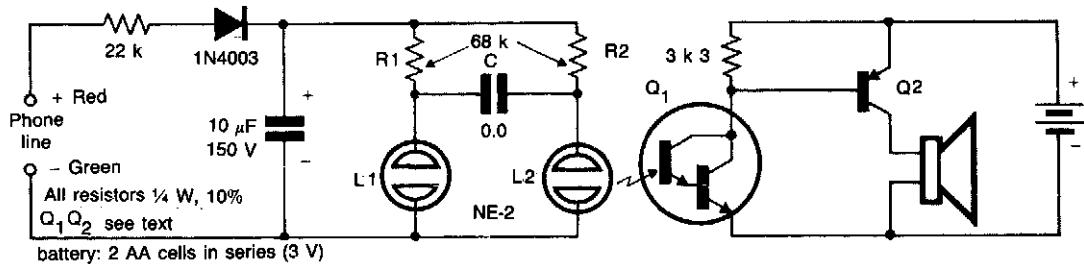


ELECTRONIC ENGINEERING

**Fig. 98-10**

### Circuit Notes

The diode rectifies the ringing signal to supply the operating power to the audio relaxation oscillator made up of L1, L2, R1, R2, and C. Moreover, L2 together with Q1 acts as an opto-isolator, totally isolating the telephone line from the rest of the circuit. The oscillator audio frequency is optically coupled to the photo-Darlington which drives Q2 and thus the speaker. The  $10 \mu\text{F}$  capacitor is not large enough to smooth the ringing ripple completely. This results in frequency modulation of the audio oscillator giving it an attention-getting warble.

## REMOTE TELEPHONE MONITOR


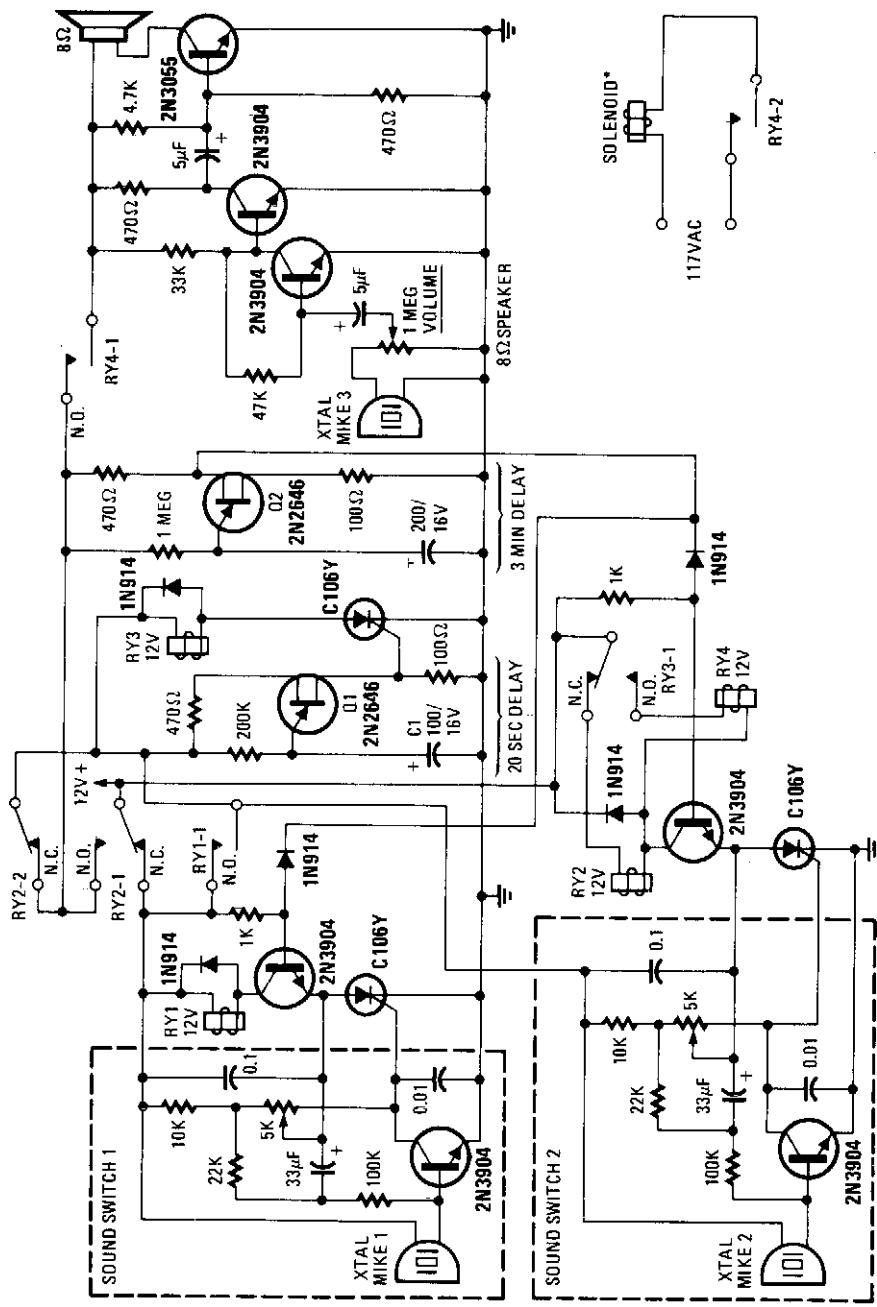


RADIO-ELECTRONICS

Circuit Notes  
Fig. 98-11

This device monitors sounds in home or office when a telephone is called from a remote location.
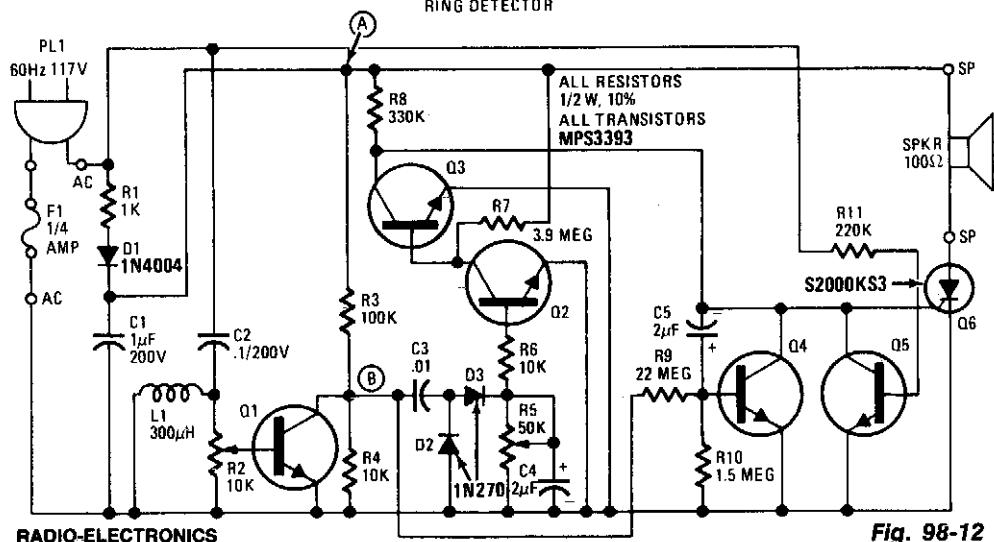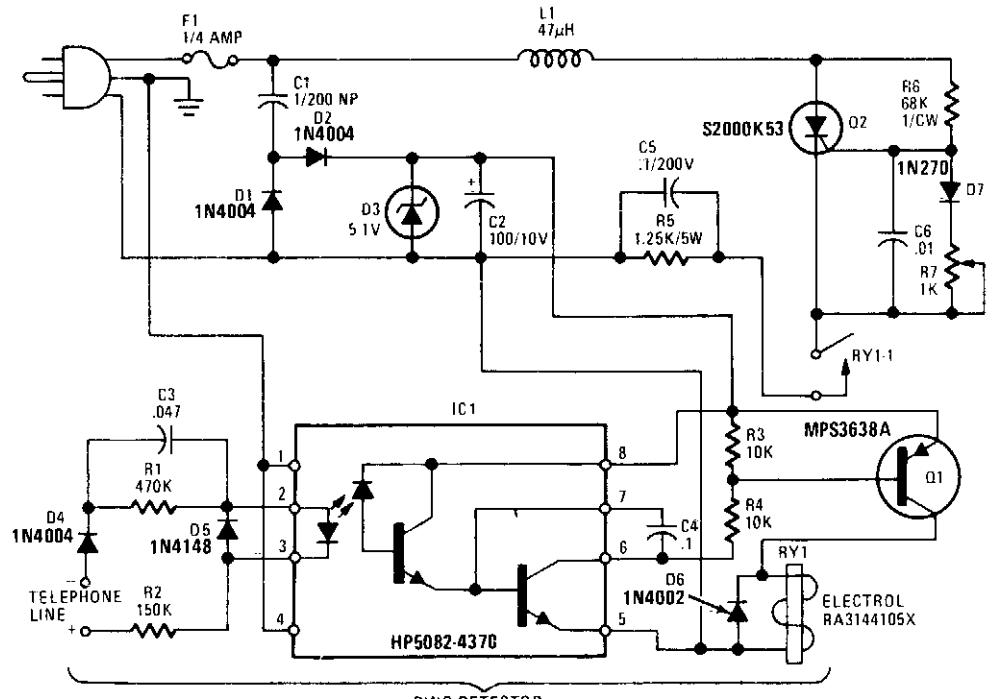
### PLUG-IN REMOTE TELEPHONE RINGER

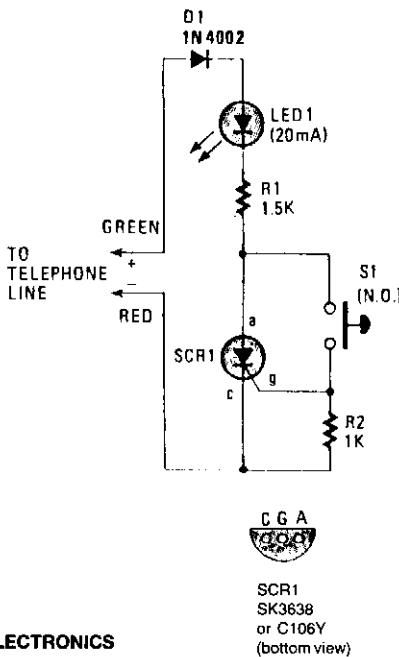


**Fig. 98-12**

#### Circuit Notes

This device consists of a ring detector connected to the telephone line. When the telephone rings, the ring detector impresses high-frequency pulses on the ac power line. A receiver placed anywhere on the same power line detects these pulses and emits an audible tone in synchronization with the telephone signal.

## TELEPHONE HOLD BUTTON




HANDS-ON ELECTRONICS

**Fig. 98-13**

### Circuit Notes

The on-hook (no load) voltage across the red-green wires will be 48 V or slightly less when all telephones are on-hook (disconnected). When any telephone goes off-hook the load current flowing in the telephone causes the voltage to fall below 5 volts dc. Although the telephone hold is connected across the red-green wires, silicon control rectifier SCR1 is open; so there is no current path across the telephone line. To hold the call, depress normally-open switch S1 and hang up the telephone (still depressing S1). When the phone goes on-hook the red-green voltage jumps to 48 volts dc. Since switch S1 is closed, a positive voltage is applied to SCR1's gate, which causes SCR1 to conduct, thereby completing the circuit across the telephone line through D1, LED1, R1, and SCR1. The current that flows through those components also causes the LED to light up—indicating that the telephone line is being held. The effective load across the red-green wires is the 1500 ohm value of R1, which is sufficient to seize the line while limiting the current through the LED to a safe value. When the telephone, or an extension, is once again placed off-hook the red-green voltage falls to 5 volts or less. But diode D1 has a normal voltage drop—called the breakdown voltage—of 0.7 volts, and the LED has a forward drop of 2.0 volts. Excluding the voltage drop across R1 there is a maximum of 2.3 volts available for SCR1, which is too low to maintain conduction; so SCR1 automatically opens the hold circuit when any telephone goes off-hook.

## TELEPHONE BLINKER

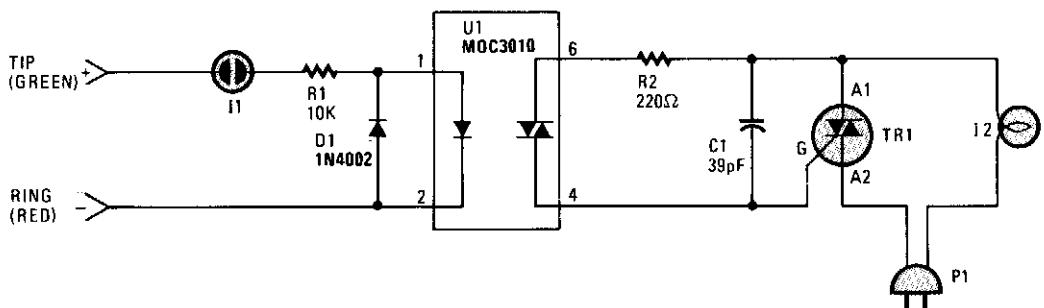


HANDS-ON ELECTRONICS

**Fig. 98-14**

### Circuit Notes

A small neon lamp is triggered into conduction by the telephone's ringing voltage, passes just enough current to activate the LED in optocoupler U1, which in turn triggers the 6-A Triac that controls I2—a 117-Vac lamp or bell. (Capacitor C1 is necessary only when the circuit is used to drive a bell.) The lamp will flash off-and-on at the ringing rate, which is normally around 20 Hz. If a 117 Vac bell is used, connect it in place of the lamp.

## TELEPHONE "IN USE" INDICATOR

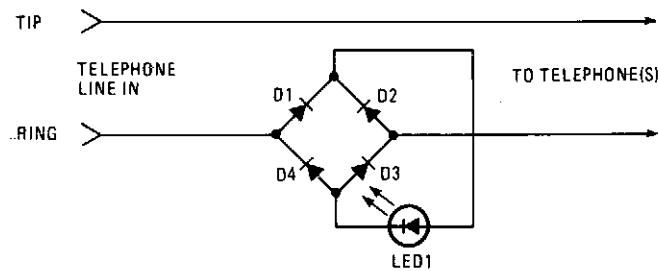


HANDS-ON ELECTRONICS

**Fig. 98-15**

### Circuit Notes

This circuit functions as a line-current sensor and can be connected in series with either of the phone lines. For the circuit to indicate an "in use" status for all phones on a single line, it must be connected in series with the phone line before, or ahead of all phones on the line. Since the power for the circuit is supplied by the phone company, a circuit could be added to each phone as an off-hook indicator.

## TONE RINGER

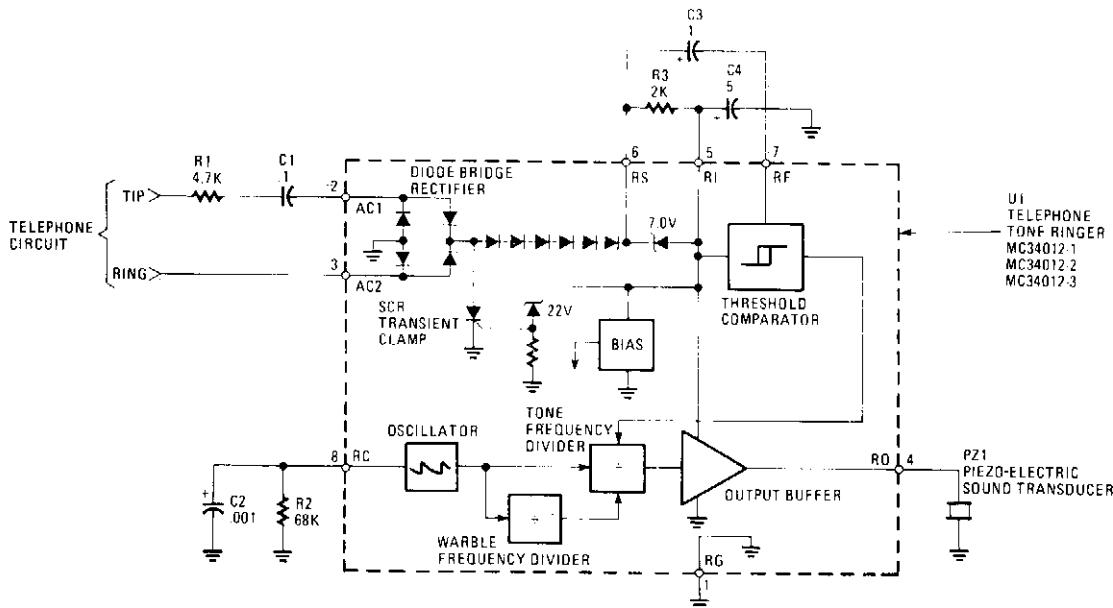



HANDS-ON ELECTRONICS

**Fig. 98-16**

### Circuit Notes

The MC34012 tone-ringer chip derives its power by rectifying the ac ringing signal. That signal is normally at 20 Hz and measures between 70 and 130 volts rms. It uses that power for the tone generator and to drive the piezoelectric transducer. The sound that is produced is a warble that varies between two frequencies,  $f_o/4$  ( $f_o - 4$ )  $f_o/5$ . The clock, or fundamental, frequency,  $f_o$ , is generated by a relaxation oscillator. That oscillator has R2 and C2 as its frequency setting components providing a selectable range of 1 kHz to 10 kHz. Selecting different values for R2 and/or C2 changes the clock frequency, which in turn varies the warble frequencies. The MC34012 chip comes in three different warble rates at which the warble frequencies ( $f_o/4$ ,  $f_o/5$ ) are varied. These warble rates are  $f_o/320$ ,  $f_o/640$ , or  $f_o/160$  and the different chips are designated as MC34012-1, -2, and -3, respectively. For example: with a 4.40 kHz oscillator frequency, the MC34012-1 produces 800 Hz and 1000 Hz tones with a 12.5 Hz warble rate. The MC34012-2 generates 1600 Hz and 2000 Hz tones with a similar 12.5 Hz warble frequency from an 8.0 kHz oscillator frequency. MC34012-3 will produce 400 Hz and 500 Hz tones with a 12.5 warble rate from a 2.0 kHz oscillator frequency.

## TONE RINGER II

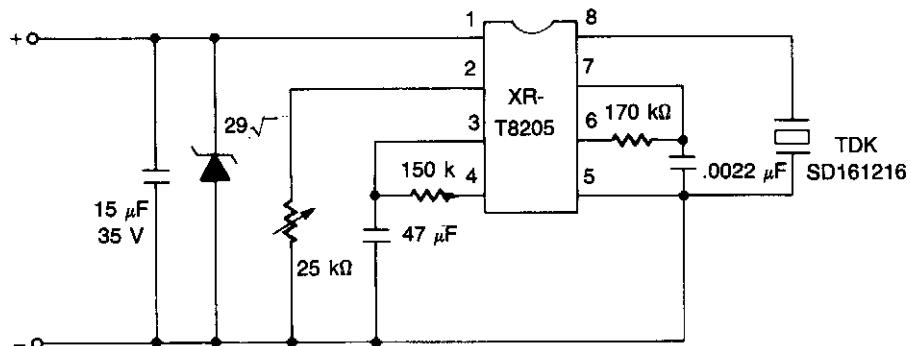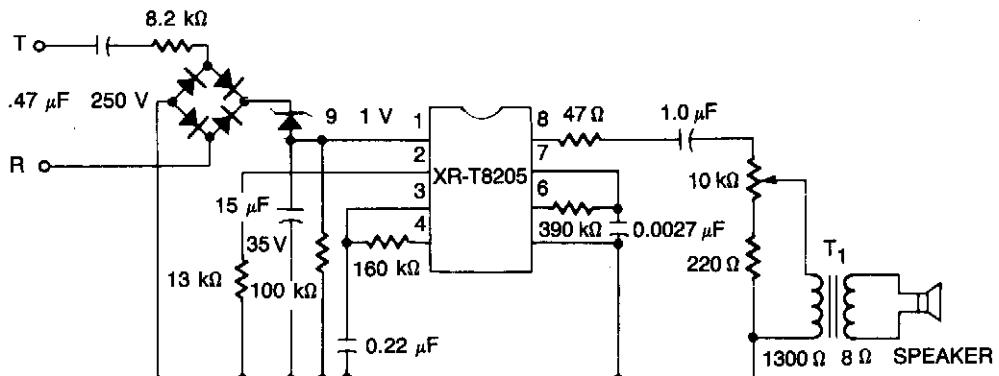


EXAR

**Fig. 98-17**

### Circuit Notes

The XR-T8205 Tone Ringer is primarily intended as a replacement for the mechanical telephone bell. The device can be powered directly from telephone ac ringing voltage or from a separate dc supply. An adjustable trigger level is provided with an external resistor. The circuit is designed for nominal 15 volt operation.

## SPEAKERPHONE

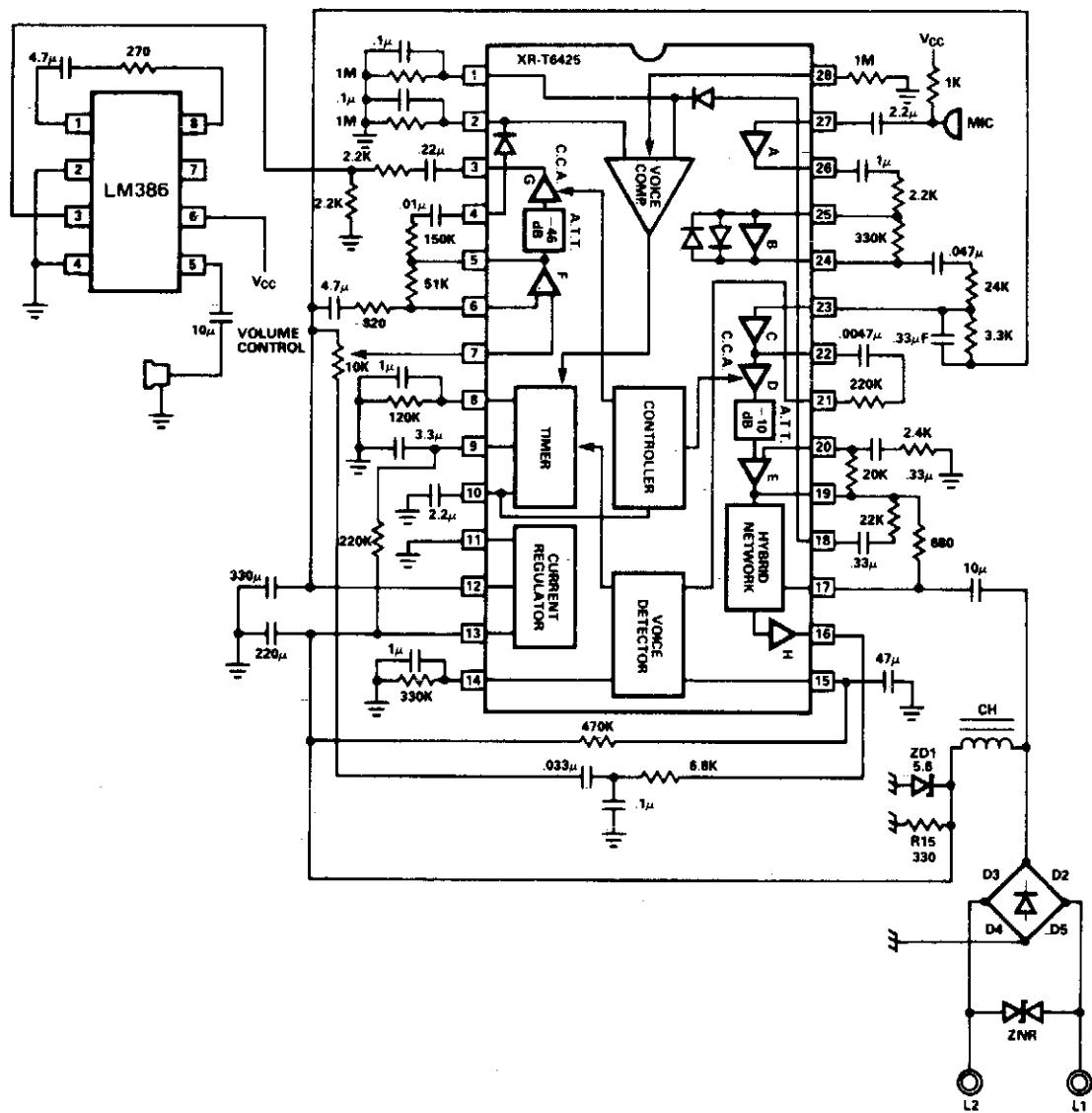

EXAR

Fig. 98-18

### Circuit Notes

The XR-T6425 Speakerphone IC makes it possible to carry on conversation without using the handset, while the user is talking into a microphone and listening from a loudspeaker. It is ideal for hands-free conference calls. The XR-T6425 contains most of the circuits to eliminate singing and excessive background noise.

## SPEECH NETWORK


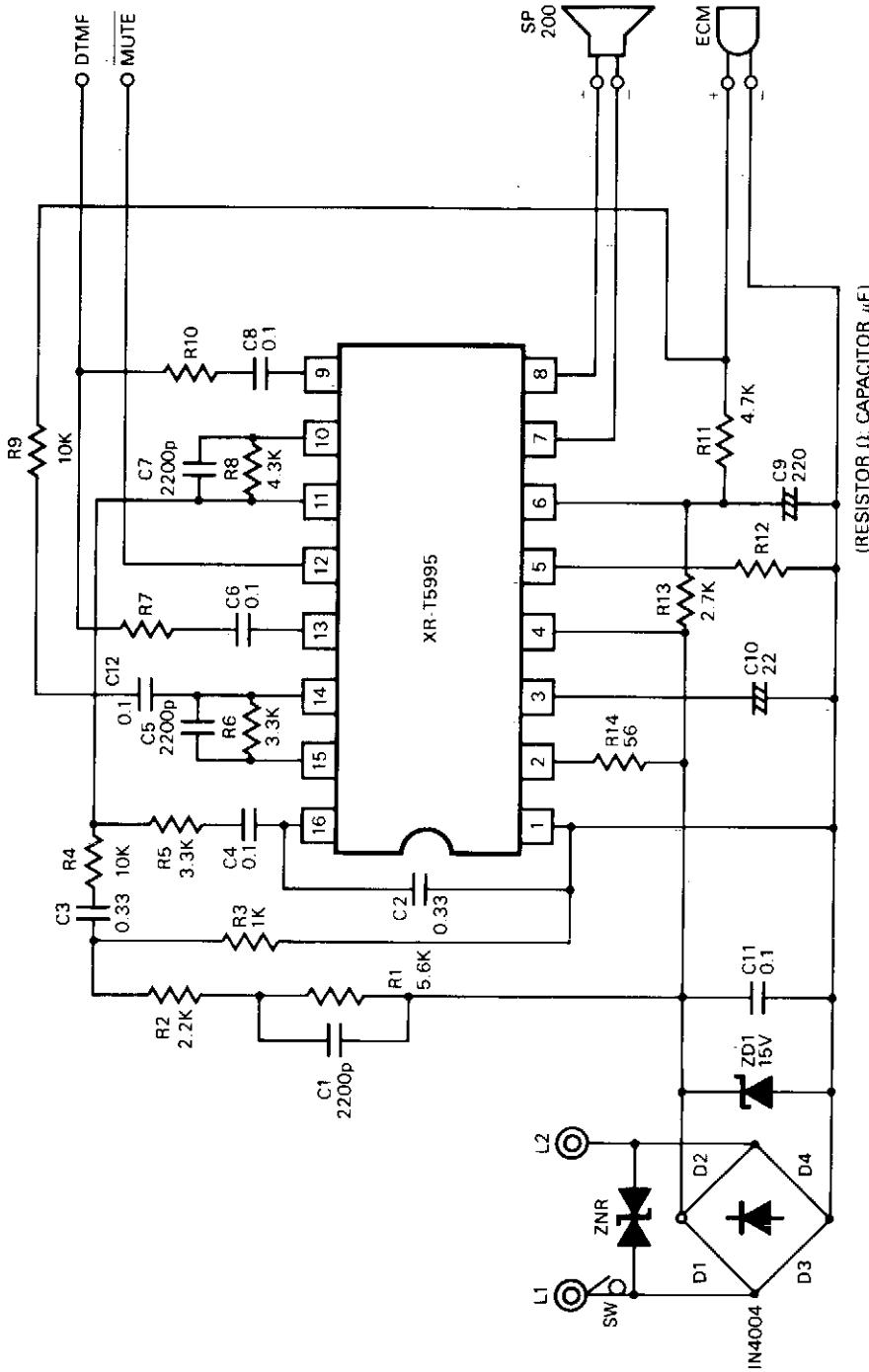


Fig. 98-19

### Circuit Notes

The XR-T5995 Speech Network is a monolithic integrated circuit specifically designed for implementing a low cost telephone circuit. It is designed to use an electrodynamic microphone and electromagnetic receiver to replace a carbon microphone and telephone network hybrid.
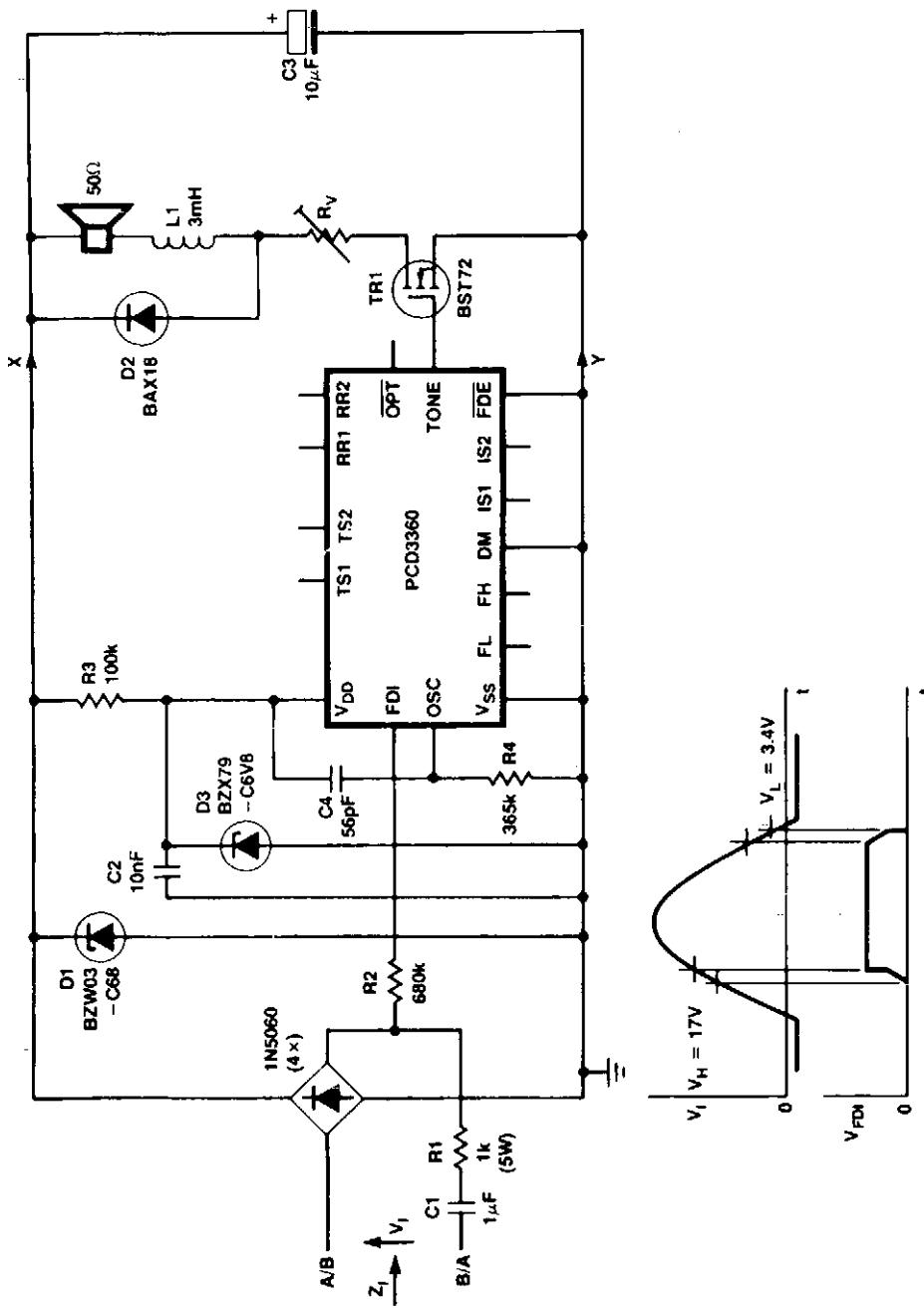
## PROGRAMMABLE MULTI-TONE TELEPHONE RINGER



Transformerless Electronic Ringer With PCD3360 and a Loudspeaker

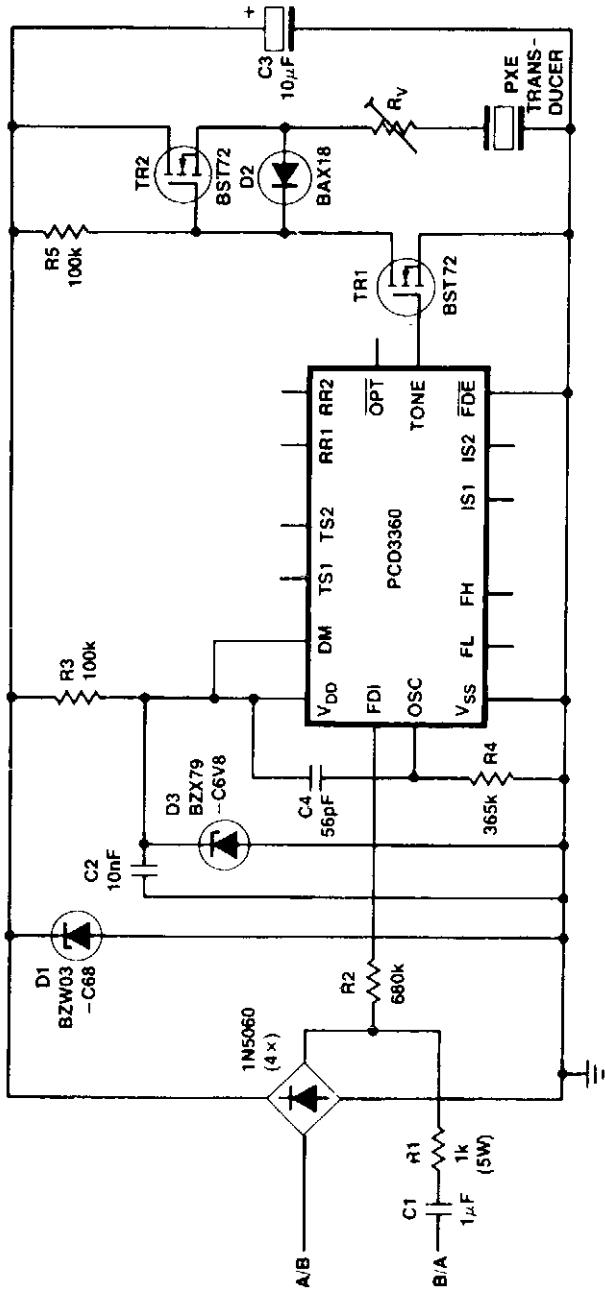


Fig. 98-20

PCD3360 Ringer With PXE Transducer

Circuit Notes

Two BST72 transistors provide an output voltage swing almost equal to the voltage at C3. Pins IS1 and IS2 are inoperative because DM = HIGH. Volume control is possible using resistor R<sub>V</sub>.

SIGNETICS

# **99**

## **Temperature Controls**

---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Temperature-Controlling Circuit

Temperature Control

Low-Cost Temperature Controller

Precision, Linearized Platinum RTD Signal Conditioner

Low Power Zero Voltage Switch Temperature Controller

Heater Element Temperature Controller

Dual-Time Chip Controls Temperature While Monitoring Liquid Level

Temperature Alarm

Adjustable Threshold Temperature Alarm

## TEMPERATURE-CONTROLLING CIRCUIT

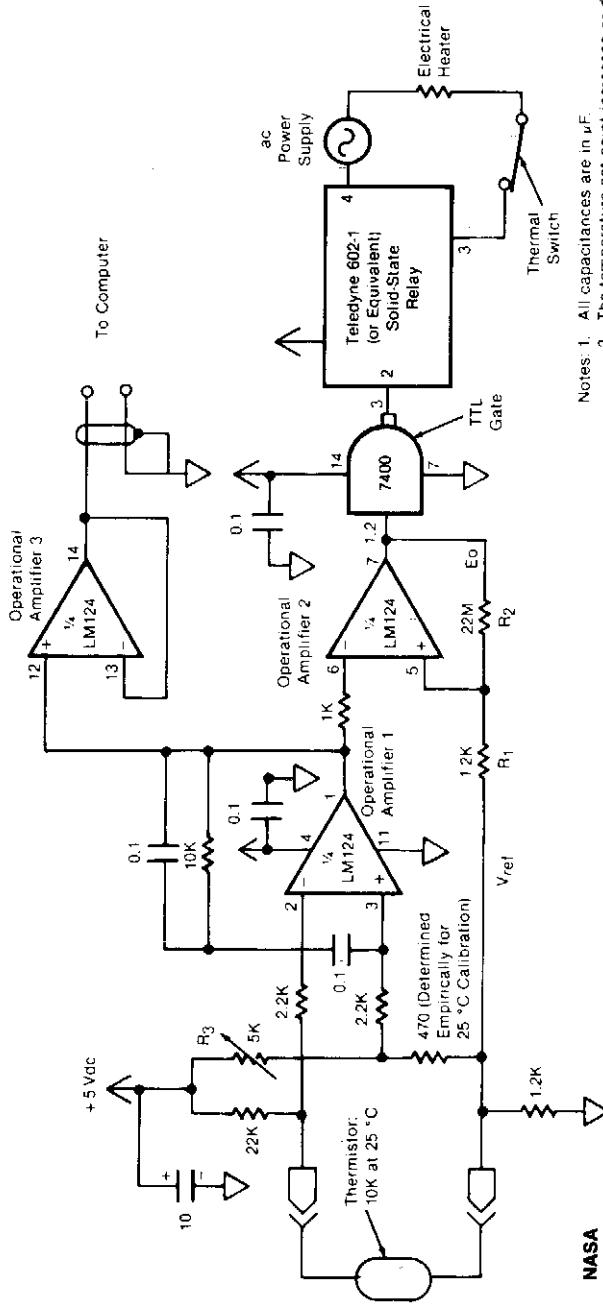


Fig. 99-1


Circuit Notes

- Notes: 1. All capacitances are in  $\mu F$ .  
 2. The temperature set point increases or decreases with  $R_3$ , which is set at 217K or 25 °C.  
 3. The upper and lower tripping voltages of operational amplifier 2 are given by  

$$V_{trip} = V_{ref} \pm E_0 R_1 / (R_1 + R_2)$$
, where  $V_{ref}$  = the reference voltage and  $E_0 =$  the output voltage of the operational amplifier

The circuit switches the current to an electrical heater on and off to maintain the temperature of a room at  $25 \pm 0.5^\circ\text{C}$ . The temperature sensor is a thermistor which provides a differential input (for reduced noise) to an operational amplifier. A 5 kilohm potentiometer is used to adjust the set point through a voltage divider; a value of 2.17 kilohms yields the  $25^\circ\text{C}$  setting. A second operational amplifier is connected as an inverting differential-input comparator. The output of operational amplifier 2 controls the electrical heater through a zero-crossing solid-state relay. A transistor/transistor-logic (TTL) gate adjusts the output to the proper level for the relay. A thermal switch is placed in series with the heater and the ac supply for safety in case of thermal runaway. A third operational amplifier monitors the output of the thermistor, providing a signal to a computer for data logging.

## TEMPERATURE CONTROL

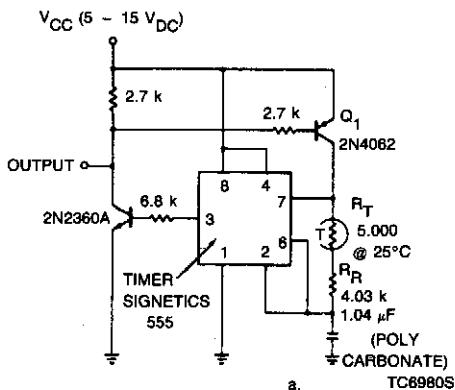

NOTE:  
All resistor values are in ohms.

SIGNETICS


b. OP03400S

**Fig. 99-2**

### Circuit Notes

A couple of transistors and a thermistor in the charging network of the 555 type timer enable this device to sense temperature and produce a corresponding frequency output. The circuit is accurate to within  $\pm 1$  Hz over a 78°F temperature range.

## LOW-COST TEMPERATURE CONTROLLER

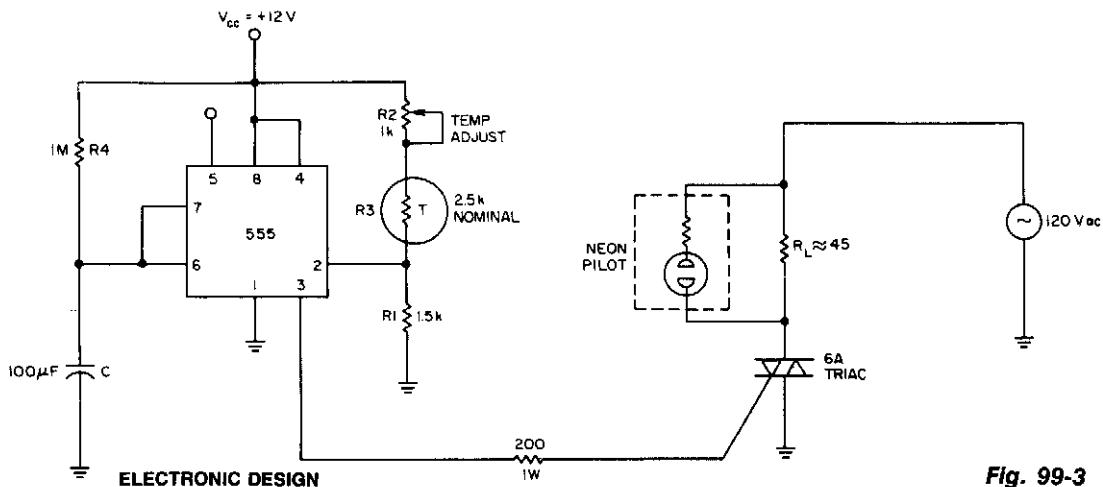


**Fig. 99-3**
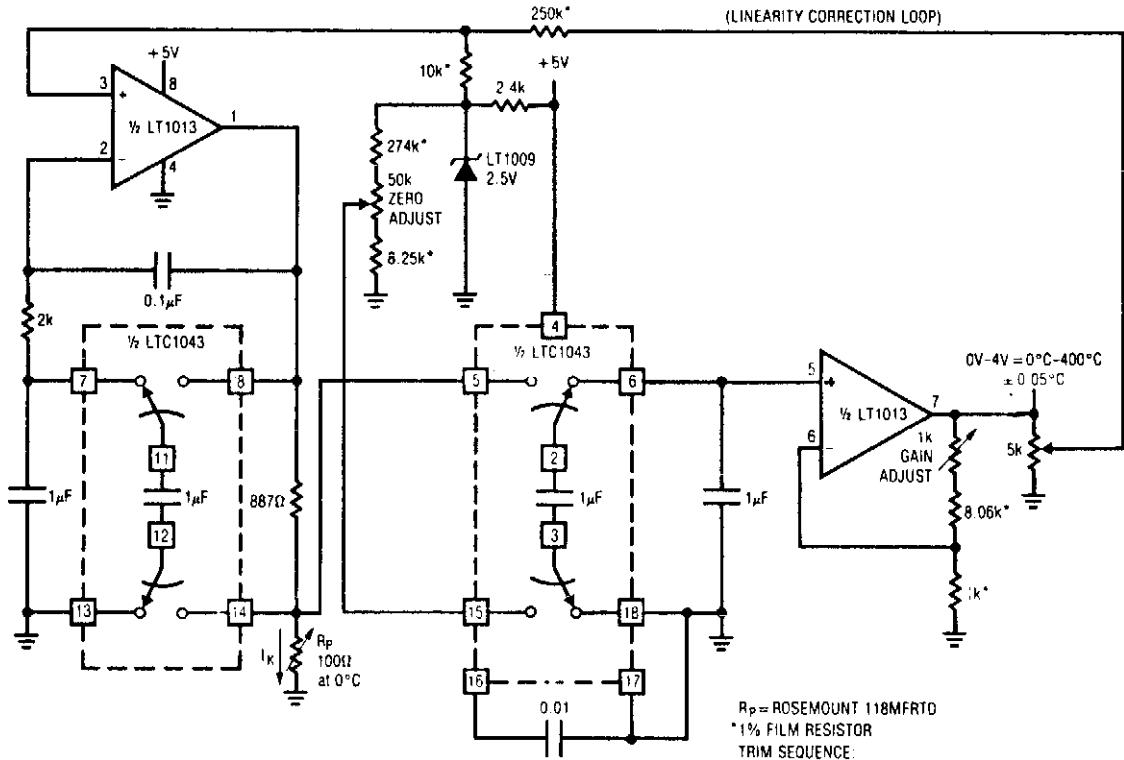
### Circuit Notes

The internal comparator of the 555 timer, combined with a thermistor, makes a low-cost temperature controller. Resistor R2 sets the temperature trip point.

## **PRECISION, LINEARIZED PLATINUM RTD SIGNAL CONDITIONER**



R<sub>P</sub>=ROSEMOUNT 118MFRTD

\*1% FILM RESISTOR

**TRIM SEQUENCE:**

SET SENSOR TO 0°C VALUE. ADJUST ZERO FOR OV OUT. SET SENSOR TO 100°C VALUE. ADJUST GAIN FOR 1.000V OUT. SET SENSOR TO 400°C VALUE. ADJUST LINEARITY FOR 4.000V OUT. REPEAT AS REQUIRED.



**LINEAR TECHNOLOGY CORPORATION**

*Fig. 99-4*

**Circuit Notes**

The circuit provides complete, linearized signal conditioning for a platinum RTD. This LTC1043 based circuit is considerably simpler than instrumentation or multi-amplifier based designs, and will operate from a single 5 V supply. A1 serves as a voltage-controlled ground referred current source by differentially sensing the voltage across the 998 ohm feedback resistor. The LTC1043 section which does this presents a single-ended signal to A1's negative input, closing a loop. The 2 k 0.1  $\mu$ F combination sets amplifier roll-off well below the LTC1043's switching frequency and the configuration is stable. Because A1's loop forces a fixed voltage across the 887 ohm resistor, the current through  $R_P$  is constant. A1's operating point is primarily fixed by the 2.5 V LT1009 voltage reference.
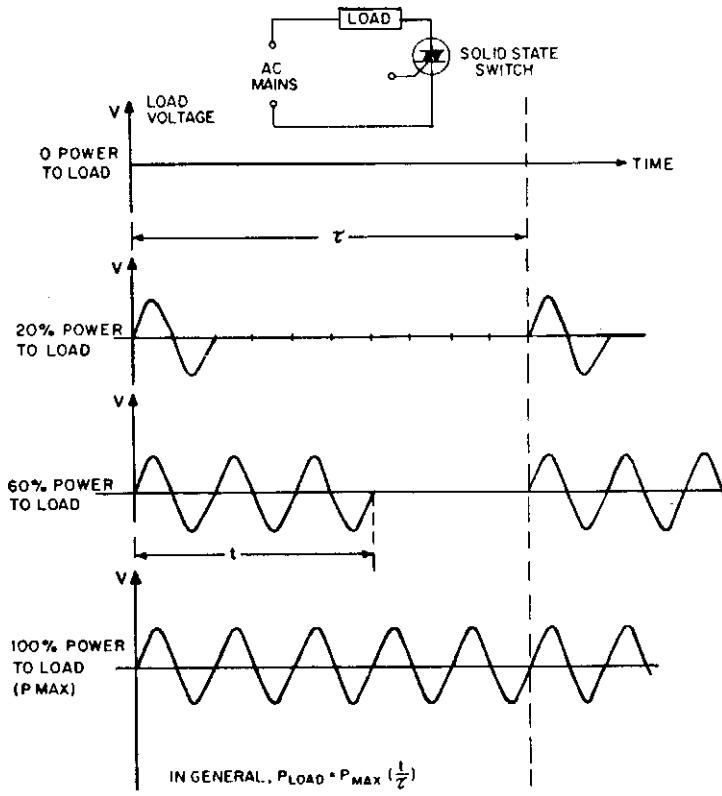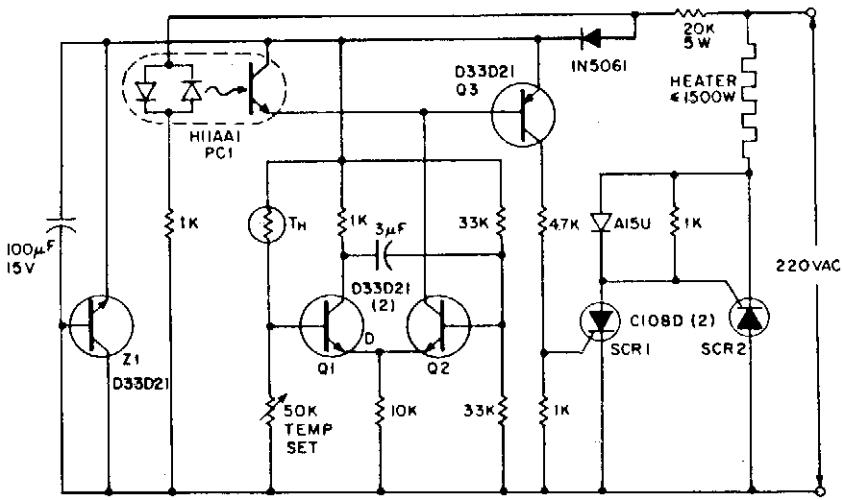
## LOW POWER ZERO VOLTAGE SWITCH TEMPERATURE CONTROLLER



GENERAL ELECTRIC

*Fig. 99-5*


### Circuit Notes

The "zero voltage switching" technique is widely used to modulate heating and similar types of ac loads where the time constant associated with the load (tens of seconds to minutes) is sufficiently long to allow smooth proportional modulation by time ratio control, using one complete cycle of the ac input voltage as the minimum switching movement. Despite its attractions, the traditional triac-based ZVS is virtually unusable for the control of very low power loads, especially from 220 volt ac inputs due to the triac's reluctance to latch-on into the near-zero instantaneous currents that flow through it and the load near the ac voltage zero crossover points. The circuit side-steps the latching problem by employing a pair of very sensitive low current reverse blocking thyristors (C106) connected in antiparallel; these are triggered by a simple thermistor modulated differential amplifier (Q1, Q2), with zero voltage logic furnished by an H11AA1 ac input optocoupler. With the NTC thermistor TH calling for heat, transistor Q1 is cut off and Q2 is on, which would normally provide continuous base drive to Q3, with consequent triggering of either SCR, or of SCR 2 via SCR1, depending on phasing of the ac input.

Note that when the ac input voltage is positive with respect to SCR 2, SCR 1 is reverse biased and, in the presence of "gate" current from Q3, behaves as a remote base transistor, whose output provides via blocking diode CR1, positive gate trigger current for SCR 2. When the ac input polarity is reversed (SCR 1's anode positive), SCR 1 behaves as a direct fired conventional thyristor. "Trigger" current to SCR 1, however, is not continuous, even when TH is calling for heat and Q2 is delivering base current to Q3. In this situation, Q3 is inhibited from conduction by the clamping action of PC1, an H11AA photocoupler, except during those brief instants when the ac input voltage is near zero and the coupler input diodes are deprived of current.

Triggering of either SCR can occur only at ac voltage crossing points, and RFI-less operation results. The proportional control feature is injected via the positive feedback action of capacitor CM, which converts the differential amplifier Q1, Q2 into a simple multivibrator, whose duty cycle varies from one to 99 percent according to the resistance of TH. Zener diode Z1 is operational, being preferred when maximum immunity from ac voltage induced temperature drift is desired.

## HEATER ELEMENT TEMPERATURE CONTROLLER

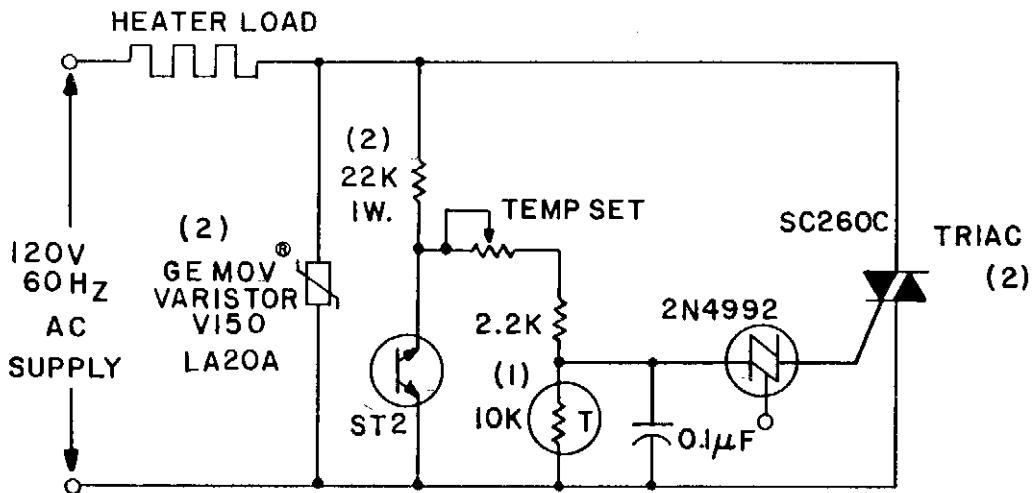

NOTES: 1. Thermistor National Lead type 1D101, or equivalent.  
 2. Component values for 220V operation:  
 Resistor - 47K, 2W  
 GE-MOV® Varistor - V275LA20A  
 Triac - SC260E


GENERAL ELECTRIC

**Fig. 99-6**
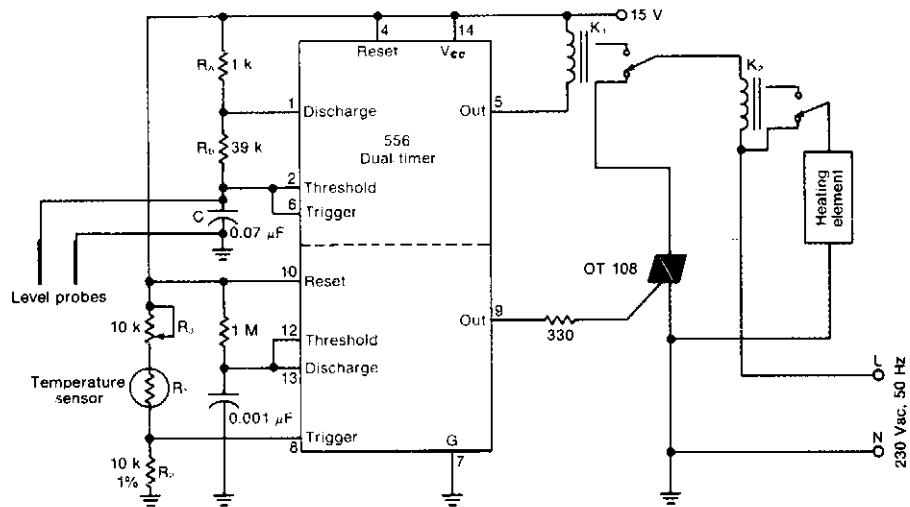
### Circuit Notes

The circuit can control up to 6 kW of heating, with moderate gain, using a 25-amp triac (SC260D). Feedback is provided by the negative temperature co-efficient (NTC) thermistor, which is mounted adjacent to the environment being temperature controlled. The temperature set potentiometer is initially adjusted to the desired heating level. As the thermistor becomes heated by the load, its resistance drops, phasing back the conduction angle of the triac, so the load voltage is reduced. The ST2 diac is used as a back-to-back zener diode. Its negative resistance region in its E-I characteristic provides a degree of line voltage stabilization. As the input line voltage increases, the diac triggers earlier in the cycle and, hence, the average charging voltage to the  $0.1 \mu\text{F}$  capacitor, decreases.

**DUAL-TIMER CHIP CONTROLS  
TEMPERATURE WHILE MONITORING LIQUID LEVEL**




ELECTRONIC DESIGN

*Fig. 99-7*

**Circuit Notes**

One-half of a 556 dual timer monitors the temperature of a liquid bath, controlling a heating element that maintains temperature within  $\pm 2^\circ\text{C}$  over a  $32^\circ - 200^\circ\text{C}$  range. The other half monitors the liquid level, disconnecting the heater when the level drops below a preset point.

## **TEMPERATURE ALARM**

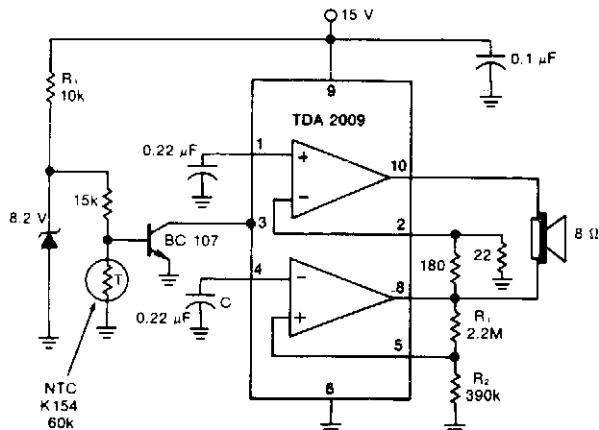


ELECTRONIC DESIGN

**Fig. 99-8**

Circuit Notes

The mute pin of this dual audio amplifier is used as the trigger for a one chip high-temperature alarm. One-half of the IC is connected as an oscillator and the other boosts the audio alarm outputs to 10W.

### ADJUSTABLE THRESHOLD TEMPERATURE ALARM

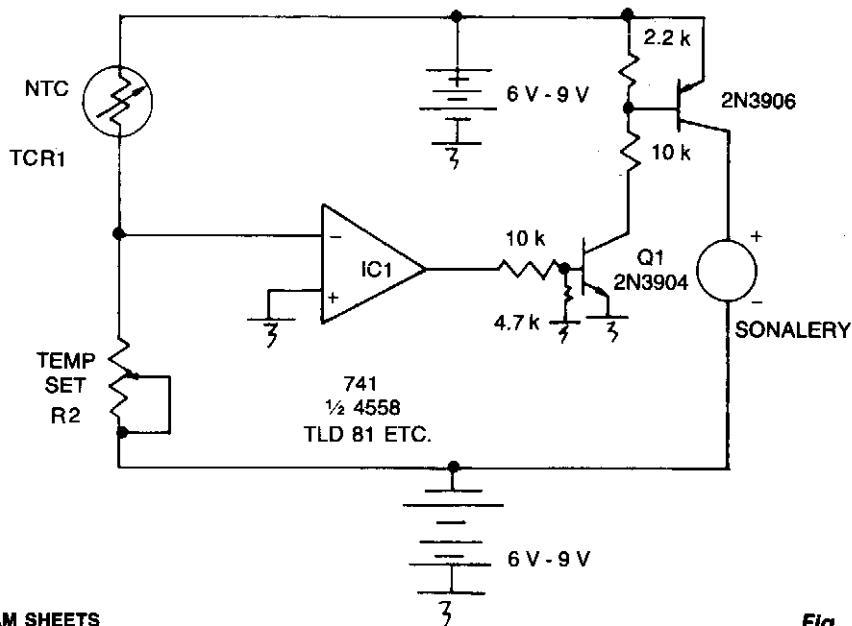

*Fig. 99-9*

#### Circuit Notes

When R1 increases as temp decreases, the output of IC1 goes positive, turning on Q1. Q1 conducts and causes Q2 to conduct, turning on the audible alarm. The threshold is set with potentiometer R2.

# 100

## Temperature Sensors


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Dual Output, Over-Under Temperature Monitor
- Temperature Sensor and DVM Interface
- Curvature Corrected Platinum RD Thermometer
- Thermocouple Amplifier with Cold Junction Compensation
- 5-V Powered, Linearized Platinum RTD Signal Conditioner
- HI LO Temperature Sensor
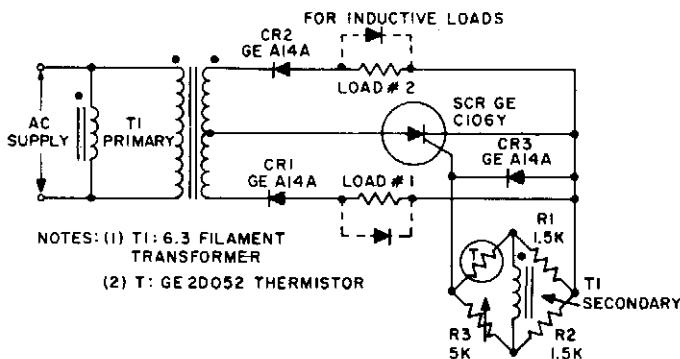
## DUAL OUTPUT, OVER-UNDER TEMPERATURE MONITOR




GENERAL ELECTRIC

Fig. 100-1

### Circuit Notes

This circuit is ideal for use as an over-under temperature monitor, where its dual output feature can be used to drive HIGH and LOW temperature indicator lamps, relays, etc. T1 is a 6.3 volt filament transformer whose secondary winding is connected inside a four arm bridge. When the bridge is balanced, ac output is zero, and C5 (or C7) receives no gate signal. If the bridge is unbalanced by raising or lowering the thermistor's ambient temperature, and ac voltage will appear across the SCR's gate cathode terminals. Depending in which sense the bridge is unbalanced, the positive gate voltage will be in phase with, or  $180^\circ$  out of phase with the ac supply. If the positive gate voltage is in phase, the SCR will deliver load current through diode CR1 to load (1), diode CR2 blocking current to load (2). Conversely, if positive gate voltage is  $180^\circ$  out of phase, diode CR2 will conduct and deliver power to load (2), CR1 being reverse biased under these conditions. With the component values shown, the circuit will respond to changes in temperature of approximately  $1-2^\circ\text{C}$ . Substitution of other variable-resistance sensors, such as cadmium sulfide light dependent resistors (LDR) or strain gauge elements, for the thermistor shown is permissible.

## TEMPERATURE SENSOR AND DVM INTERFACE

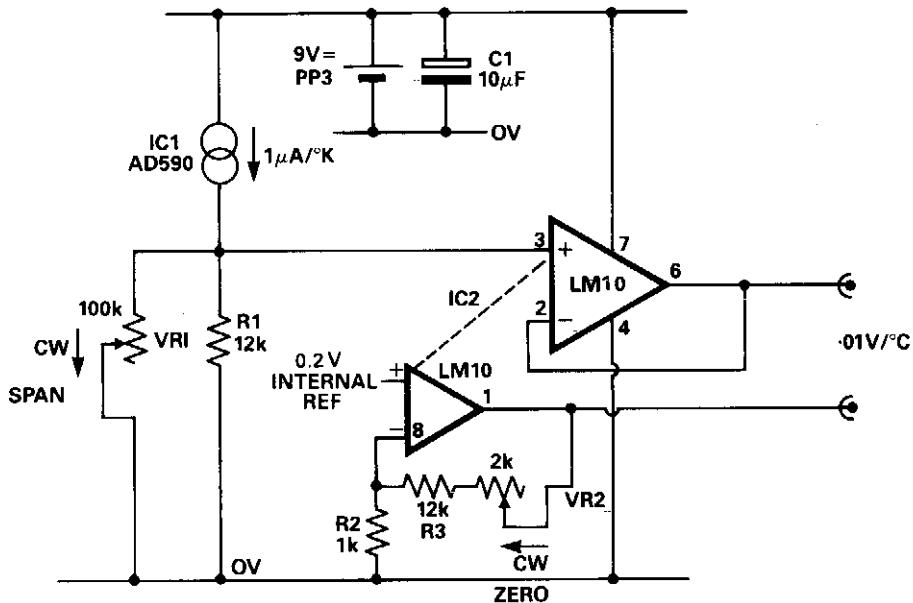

ELECTRONIC ENGINEERING


*Fig. 100-2*

### Circuit Notes

The DVM gives a direct indication of the temperature of the sensor in degrees Centigrade. The temperature sensor IC1 gives a nominal  $1\mu\text{A}$  per degree Kelvin which is converted to  $10\text{ mV}$  per degree Kelvin by R1 and VR1. IC2 is a micropower, low input drift op amp with internal voltage reference and amplifier. The main op amp in IC1 is connected as a voltage follower to buffer the sensor voltage at R1.

The second amplifier in IC1 is used to amplify the  $.2\text{ V}$  internal reference up to  $2.73\text{ V}$  in order to offset the  $273$  degrees below  $0^\circ\text{C}$ . The output voltage of the unit is the differential output of the two op amps and is thus equal to  $0.01\text{ V}$  per  $^\circ\text{C}$ .
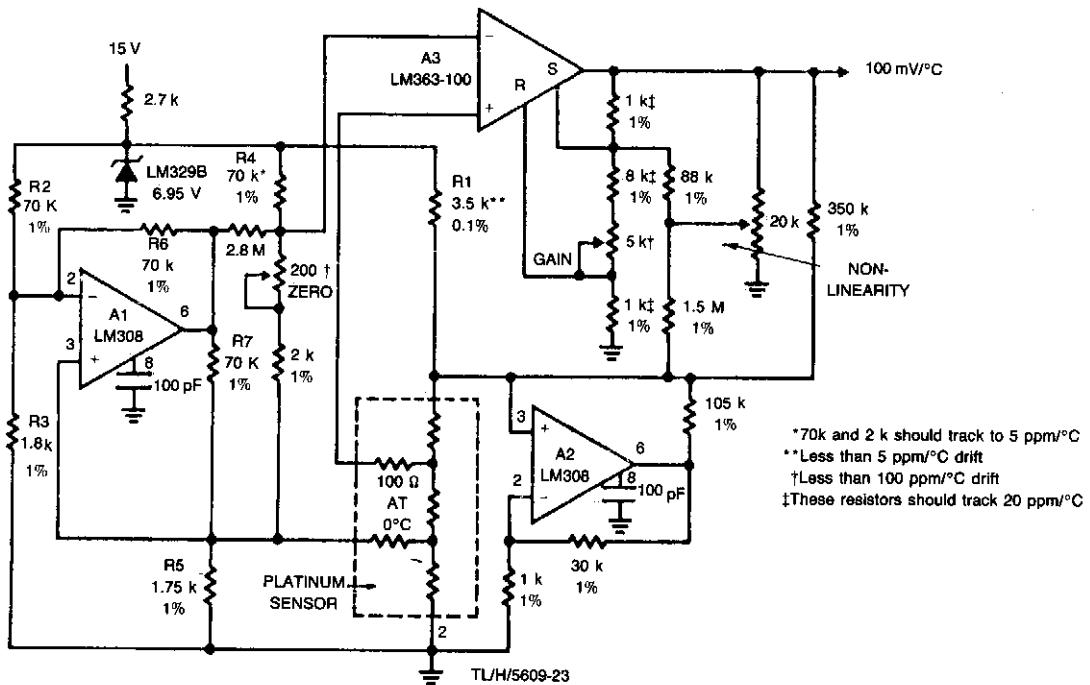
## CURVATURE CORRECTED PLATINUM RTD THERMOMETER




NATIONAL SEMICONDUCTOR CORP.

Fig. 100-3

### Circuit Notes

This thermometer is capable of 0.01°C accuracy over -50°C to +150°C. A unique trim arrangement eliminates cumbersome trim interactions so that zero gain, and nonlinearity correction can be trimmed in one even trip. Extra op amps provide full Kelvin sensing on the sensor without adding drift and offset terms found in other designs. A1 is configured as a Howland current pump, biasing the sensor with a fixed current. Resistors R2, R3, R4 and R5 form a bridge driven into balance by A1. In balance, both inputs of A2 are at the same voltage. Since R6 = R7, A1 draws equal currents from both legs of the bridge. Any loading of the R4/R5 leg by the sensor would unbalance the bridge; therefore, both bridge taps are given to the sensor open circuit voltage and no current is drawn.
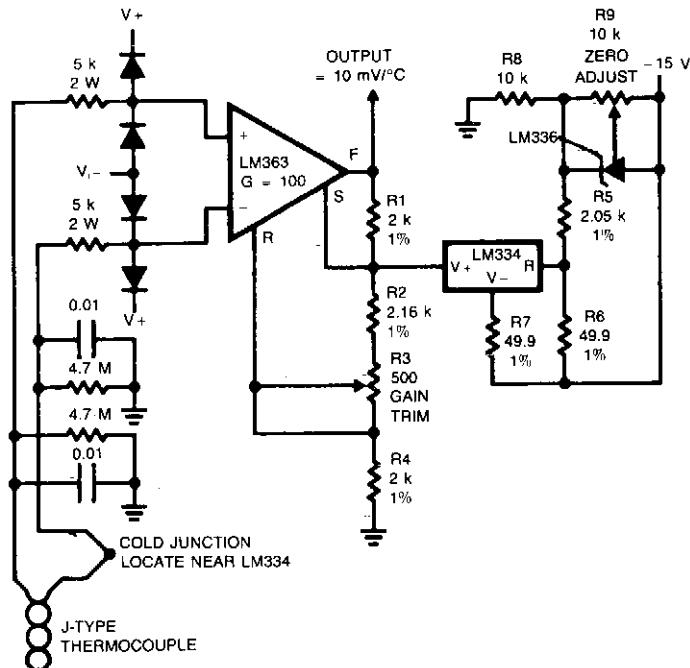
## THERMOCOUPLE AMPLIFIER WITH COLD JUNCTION COMPENSATION



NATIONAL SEMICONDUCTOR CORP.

**Fig. 100-4**

### Circuit Notes

Input protection circuitry allows thermocouple to short to 120 Vac without damaging the amplifier.

#### Calibration:

1. Apply a 50 mV signal in place of the thermocouple. Trim R3 for  $V_{OUT} = 12.25$  V.
2. Reconnect the thermocouple. Trim R9 for correct output.

## 5-V POWERED, LINEARIZED PLATINUM RTD SIGNAL CONDITIONER


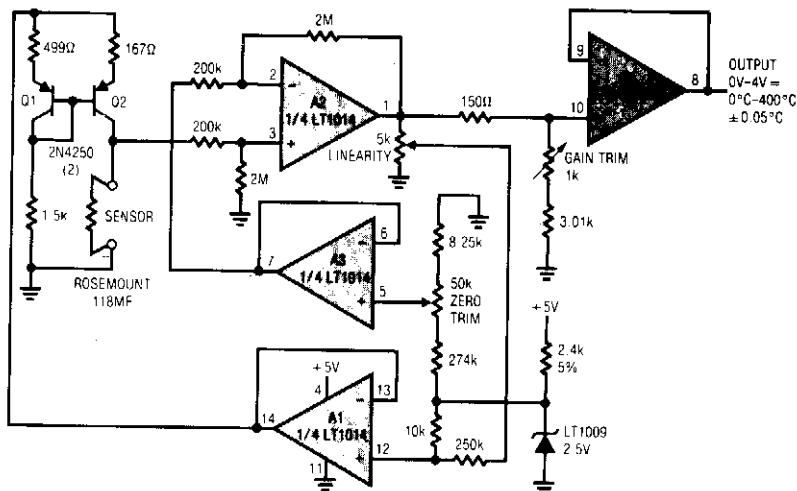


Fig. 100-5

## HI LO TEMPERATURE SENSOR

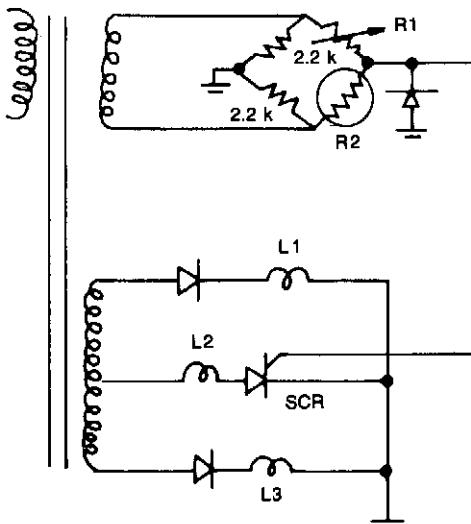

WILLIAM SHEETS

Fig. 100-6

### Circuit Notes

Resistors R1, R2, and the two 2.2 k resistors form a bridge circuit. R2 is a thermistor, and R1 sets the temperature at which L2 lights. Lower or higher temperatures light L1 or L3 to indicate an over- or under-temperature condition.

# 101

## Temperature-to-Frequency Converters


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Temperature-to-Frequency Converter  
Digital Temperature Measuring Circuit

## TEMPERATURE-TO-FREQUENCY CONVERTER

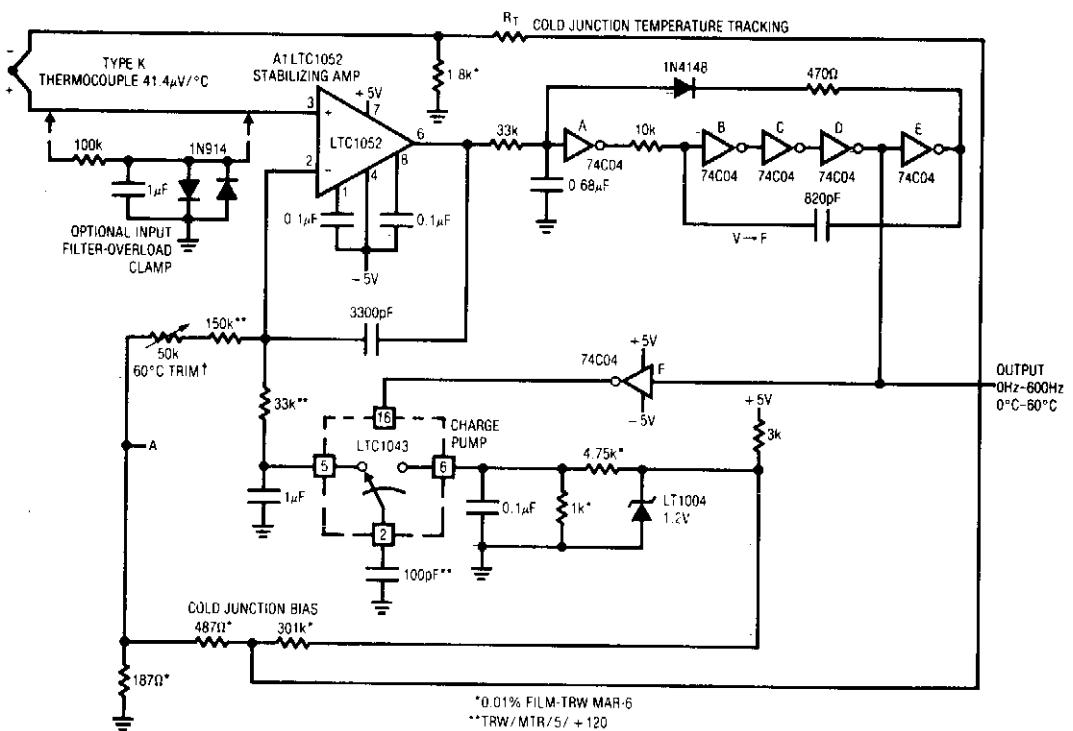


**LINEAR TECHNOLOGY CORPORATION**

**Fig. 101-1**

## Circuit Notes

A1's positive input is biased by the thermocouple. A1's output drives a crude V → F converter, comprised of the 74C04 inverters and associated components. Each V → F output pulse causes a fixed quantity of charge to be dispensed into the 1  $\mu$ F capacitor from the 100 pF capacitor via the LT1043 switch. The larger capacitor integrates the packets of charge, producing a dc voltage at A1's negative input. A1's output forces the V → F converter to run at whatever frequency is required to balance the amplifier's inputs. This feedback action eliminates drift and nonlinearities in the V → F converter as an error item and the output frequency is solely a function of the dc conditions at A1's inputs. The 3300 pF capacitor forms a dominant response pole at A1, stabilizing the loop.

## DIGITAL TEMPERATURE MEASURING CIRCUIT

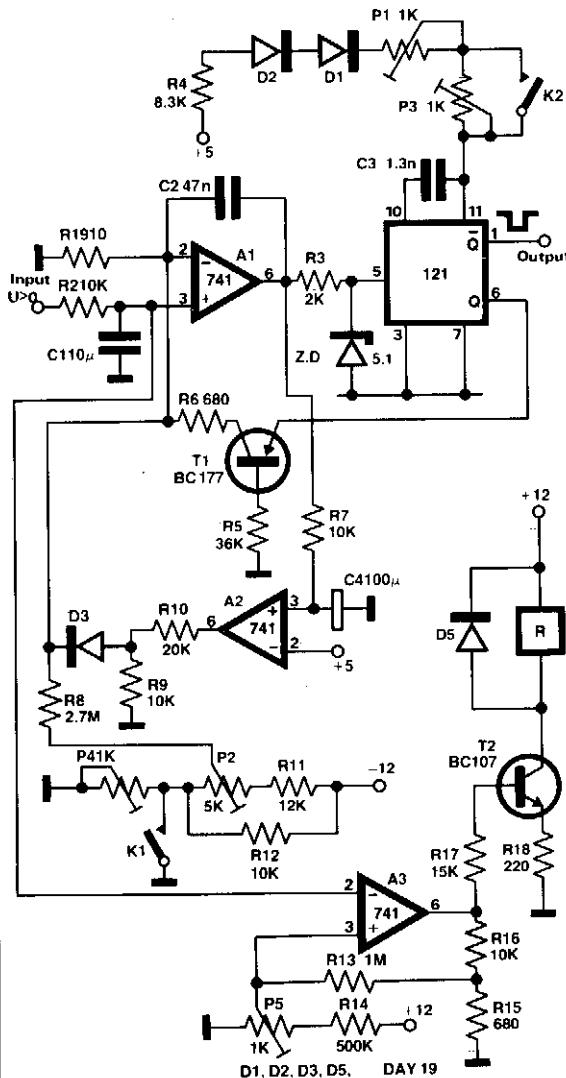

### Circuit Notes

The output voltage of a thermocouple is converted into frequency measured by a digital frequency meter. The measuring set connected with Ni-NiCr thermocouple permits you to measure the temperatures within the range of  $5^{\circ}\text{C} - 800^{\circ}\text{C}$  with  $\pm 1^{\circ}\text{C}$  error. The output thermocouple signal is proportional to the temperature difference between the hot junction and the thermostat kept at  $0^{\circ}\text{C}$ , it drives the voltage-to-frequency converter changing the analogue input signal into the output frequency with the conversion ratio adjusted in such a way, that the frequency is equal to the measured temperature in Celsius degrees, e.g., for  $350^{\circ}\text{C}$  the frequency value is 350 Hz.

# **102**


## **Theremins**

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Electronic Theremin  
Digital Theremin

## ELECTRONIC THEREMIN

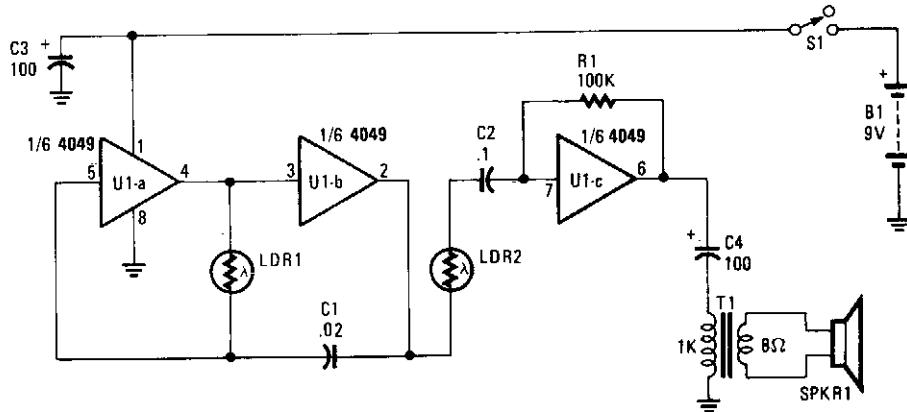


HANDS-ON ELECTRONICS

**Fig. 102-1**

### Circuit Notes

This circuit has the CMOS IC doing double-duty performance. The first two inverters operate as a digital audio oscillator; the third operates as a low-gain linear audio amplifier. As the intensity of the light falling on photoresistor LDR1 increases the oscillator's frequency increases; similarly, the illumination falling on photoresistor LDR2 determines the volume level from the loudspeaker: The more illumination the more volume. If you flop and wave your hands between the two photocells and a light source, a special kind of electronic music will be produced.

## DIGITAL THEREMIN

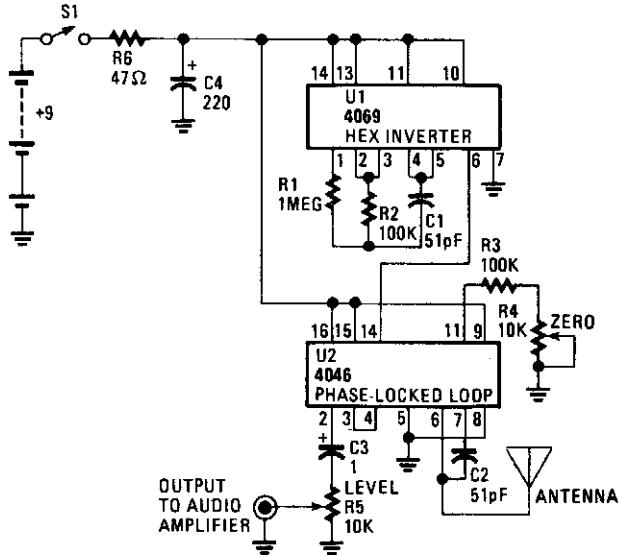

HANDS-ON ELECTRONICS

**Fig. 102-2**

### Circuit Notes

The CD4069 or 74C04 hex inverter—is used as a fixed-frequency oscillator centered around 100 kHz. U2 contains the variable frequency oscillator and balanced modulator. The CD4046 is a phase-locked loop and R3, R4, and C2 determine the center frequency of the on-chip oscillator. The antenna forms a parallel capacitance with C2, which allows the frequency to be shifted several kilohertz by bringing a hand near the antenna. R4, the ZERO control, allows the variable oscillator to be set to the same frequency as the fixed oscillator. When the difference frequency is below 15 Hz, it is below the lower frequency limit of the ear. By setting both oscillators to the same frequency, the Theremin remains silent until the performer brings his or her hand near the antenna. The oscillators are mixed by an exclusive OR gate inside the 4046. That gate acts as a digital balanced modulator, which produces the sum and difference frequencies. The output of the gate is then ac coupled by C3 to LEVEL control R5 and an output jack for connection to an audio amplifier or stereo receiver.

# **103**

## **Thermometer Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Digital Thermocouple Thermometer
- Remote Thermometer
- Electronic Thermometer
- Differential Thermometer
- Basic Digital Thermometer, Kelvin Scale with Zero  
    Adjust
- Centigrade Thermometer (0°C-100°C)

## DIGITAL THERMOCOUPLE THERMOMETER

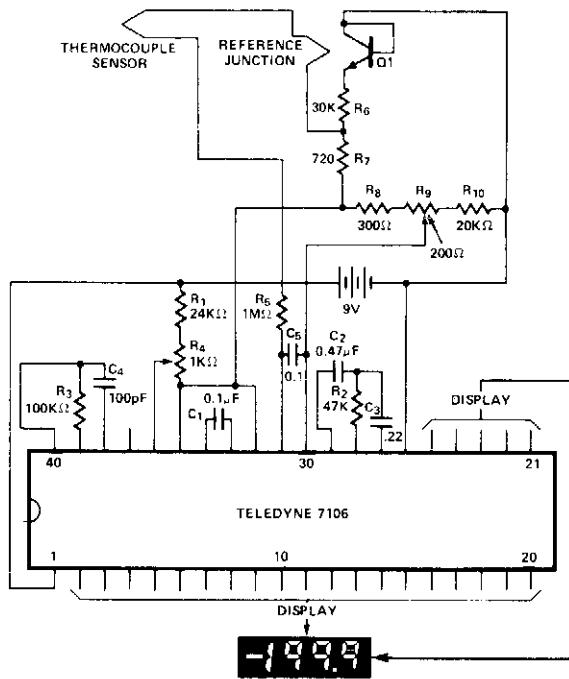


TELEDYNE SEMICONDUCTOR

*Fig. 103-1*

### Circuit Notes

This digital thermocouple thermometer uses one active component and 15 passive components. With this circuit, both type J and type K thermocouples may be used. The type J will measure over the temperature range of 10 to 530°C with a conformity of  $\pm 2^\circ\text{C}$ . The type K will measure over a temperature range of 0°C to 1000°C with a conformity of  $\pm 3^\circ\text{C}$ .

## **REMOTE THERMOMETER**

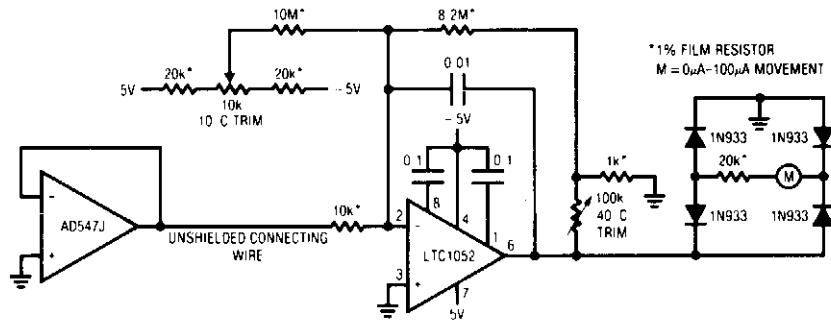


LINEAR TECHNOLOGY

**Fig. 103-2**

## Circuit Notes

The low output impedance of a closed loop op amp gives ideal line-noise immunity, while the op amp's offset voltage drift provides a temperature sensor. Using the op-amp in this way requires no external components and has the additional advantages of a hermetic package and unit-to-unit mechanical uniformity if replacement is ever required. The op amp's offset drift is amplified to drive the meter by the LTC1052. The diode bridge connection allows either positive or negative op amp temperature sensor offsets to interface directly with the circuit. In this case, the circuit is arranged for a  $+10^{\circ}\text{C}$  to  $+40^{\circ}\text{C}$  output, although other ranges are easily accommodated. To calibrate this circuit, subject the op amp sensor to a  $+10^{\circ}\text{C}$  environment and adjust the  $10^{\circ}\text{C}$  trim for an appropriate meter indication. Next, place the op amp sensor in a  $+40^{\circ}\text{C}$  environment and trim the  $40^{\circ}\text{C}$  adjustment for the proper reading. Repeat this procedure until both points are fixed. Once calibrated, this circuit will typically provide accuracy within  $\pm 2^{\circ}\text{C}$ , even in high noise environments.

## ELECTRONIC THERMOMETER

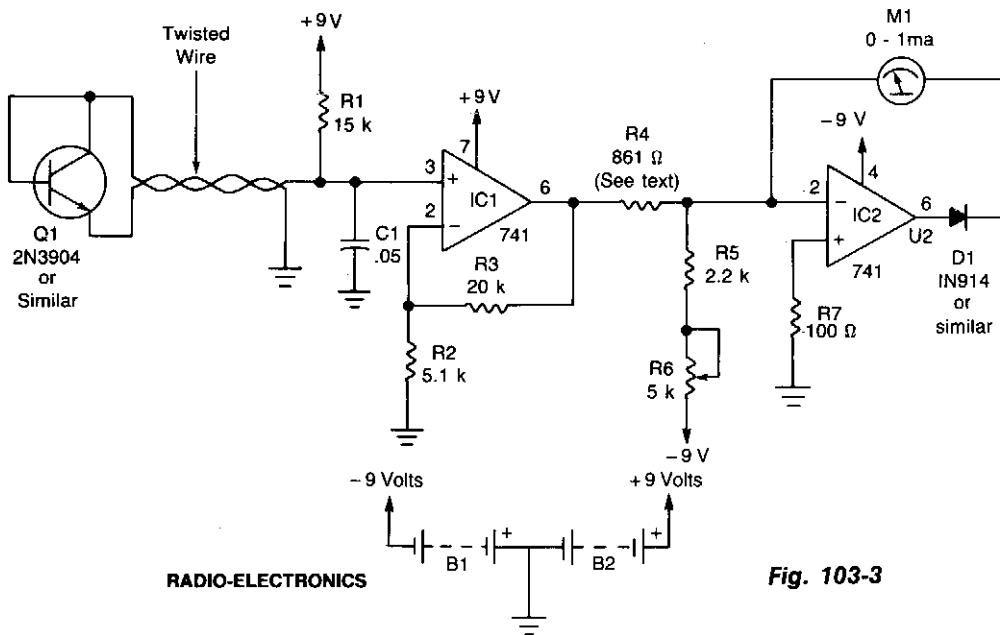


**Fig. 103-3**

### Circuit Notes

An inexpensive electronic thermometer is capable of measuring temperatures over a range of from  $-30^{\circ}\text{F}$  to  $+120^{\circ}\text{F}$ . A diode-connected 2N3904 transistor used as the temperature sensor forms a voltage divider with R1. As temperature increases, the voltage drop across the transistor changes by approximately  $-1.166 \text{ millivolts-per}^{\circ}\text{F}$ . As a result, the current at pin 3 of IC1, a 741 op amp with a gain of 5, decreases as the temperature measured by the sensor increases.

A second 741 op amp, IC2 is configured as an inverting amplifier. Resistors R5 and R6 calibrate the circuit. Calibration is also straightforward. When properly done, a temperature of  $-30^{\circ}\text{F}$  will result in a meter reading of 0 millamps, while a temperature of  $120^{\circ}\text{F}$  will result in a meter reading of 1 millamp. Divide the scale between those points into equal segments and mark the divisions with the appropriate corresponding temperatures. The calibration is completed by placing the sensor in an environment with a known temperature, such as an ice-point bath. Place the sensor in the bath and adjust R6 until you get the correct meter reading.

## DIFFERENTIAL THERMOMETER

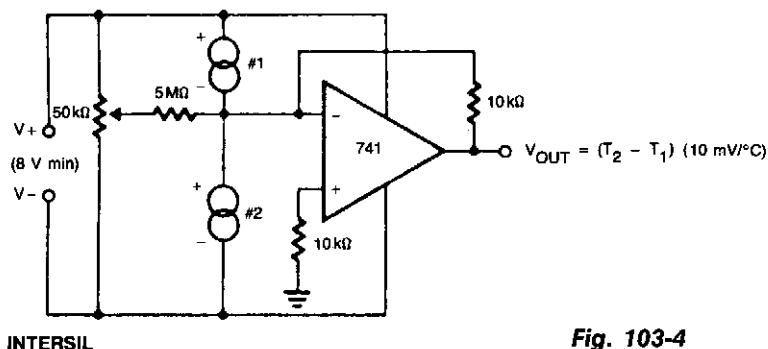


*Fig. 103-4*

### Circuit Notes

The 50 k ohm pot trims offsets in the devices whether internal or external, so it can be used to set the size of the difference interval. This also makes it useful for liquid-level detection (where there will be a measurable temperature difference).

## BASIC DIGITAL THERMOMETER, KELVIN SCALE WITH ZERO ADJUST

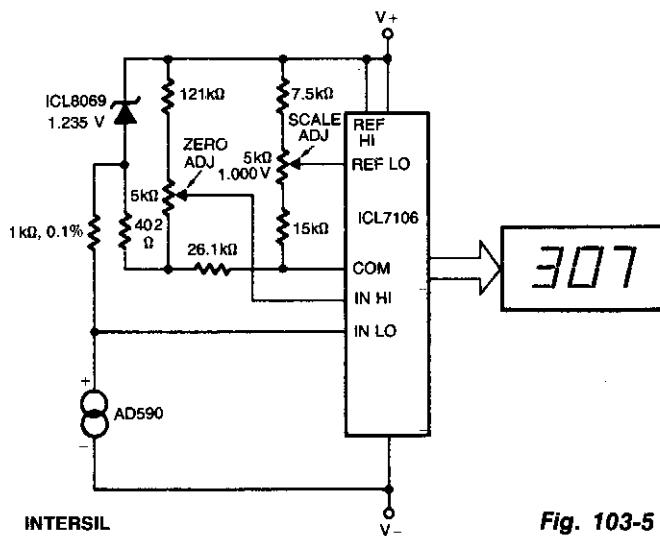


*Fig. 103-5*
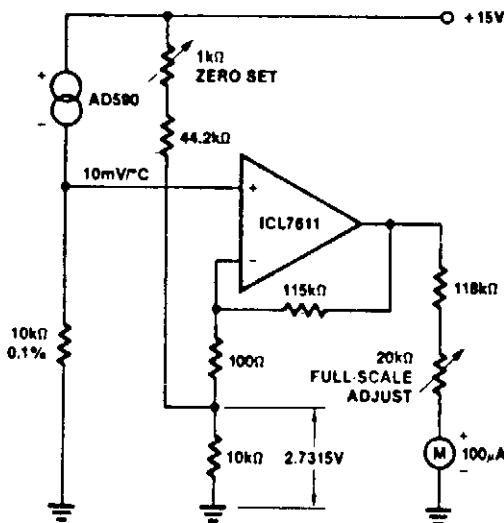
### Circuit Notes

This circuit allows "zero adjustment" as well as slope adjustment. The ICL8069 brings the input within the common-mode range, while the 5 k ohm pots trim any offset at 218° K ( $-55^{\circ}\text{C}$ ), and set the scale factor.

## CENTIGRADE THERMOMETER (0°C-100°C)



INTERSIL

Fig. 103-6

### Circuit Notes

The ultra-low bias current of the ICL7611 allows the use of large-value gain-resistors, keeping meter-current error under ½%, and therefore saving the expense of an extra meter-driving amplifier.

**104**

## **Tilt Meters**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Tiltmeter Indicates Sense of Slope  
Differential Capacitance Measurement Circuit  
Ultra-Simple Level

## TILTMETER INDICATES SENSE OF SLOPE

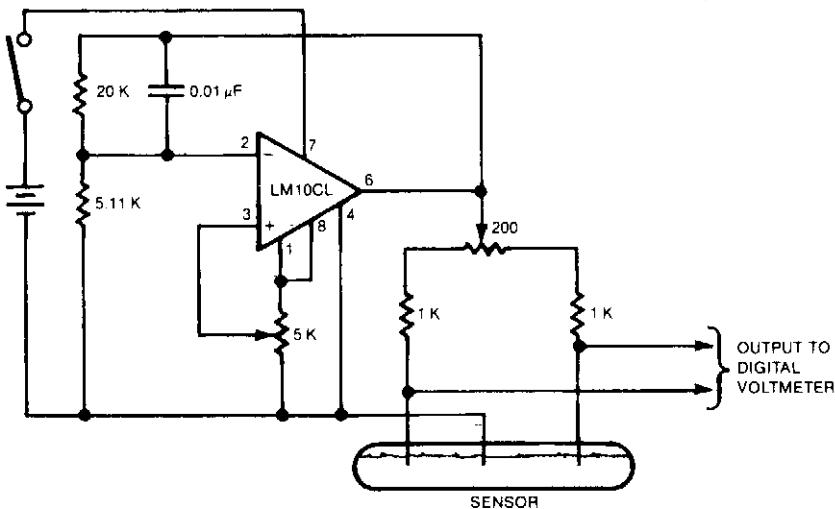



NASA

*Fig. 104-1*

### Circuit Notes

Electrodes are immersed in an electrolyte that remains level while the sensor follows the tilt of the body on which it is placed, more of one outer electrode and less of the other are immersed and their resistances fall or rise, respectively. The resistance change causes a change in the output voltage of the bridge circuit. The sensor forms the two lower legs of the bridge, and two 1000 ohm metal film resistors and a 200 ohm ceremet balance potentiometer form the two upper legs. In preparation for use, the bridge is balanced by adjusting the balance potentiometer so that the bridge output voltage is zero when the sensor is level. The bridge input voltage (dc excitation) is adjusted to provide about 10 millivolts output per degree of slope, the polarity indicating the sense of the slope. This scaling factor allows the multimeter to read directly in degrees if the user makes a mental shift of the meter decimal point. The scaling-factor calibration is done at several angles to determine the curve of output voltage versus angle.
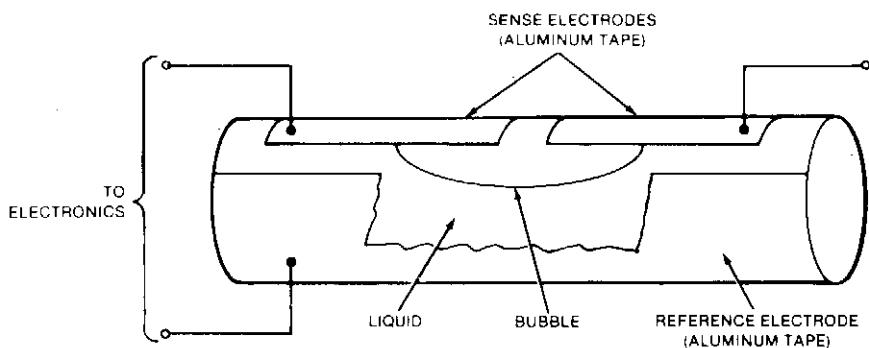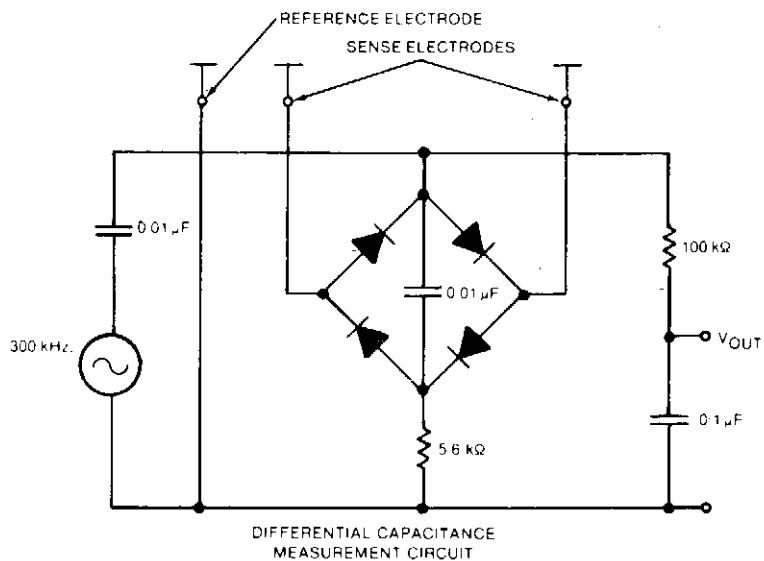
## DIFFERENTIAL CAPACITANCE MEASUREMENT CIRCUIT




NASA

**Fig. 104-2**

### Circuit Notes

A bubble vial with external aluminum-foil electrodes is the sensing element for a simple indicating tiltmeter. To measure bubble displacement, a bridge circuit detects the difference in capacitance between the two sensing electrodes and the reference electrode. Using this circuit, a tiltmeter level vial with 2 mm deflection for 5 arc-seconds of tilt easily resolves 0.05 arc-second. The four diodes are CA3039, or equivalent.

## ULTRA-SIMPLE LEVEL

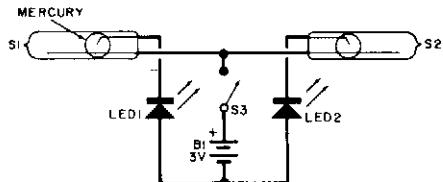

POPULAR ELECTRONICS

Fig. 104-3

### Circuit Notes

This electronic level uses two LED indicators instead of an air bubble. If the surface is tilted to the right, one LED lights; if it's tilted to the left, the other LED lights. When the surface is level, both LEDs light. It uses two unidirectional mercury switches, S1 and S2. The unidirectional mercury switch has one long electrode and one short, angled electrode. The pool of mercury "rides" on the long electrode and makes contact between the two electrodes if the unit is held in a horizontal position.

# 105


## Time-Delay Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Hour Time-Delay Sampling Circuit
- Time Delay With Constant Current Charging
- Low-Cost Integrator Multiplies 555 Timer's Delay
- Simple Time-Delay Circuit Using Two SCRs

## HOUR TIME-DELAY SAMPLING CIRCUIT

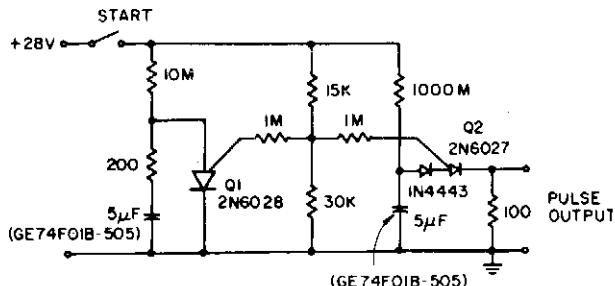


**Fig. 105-1**
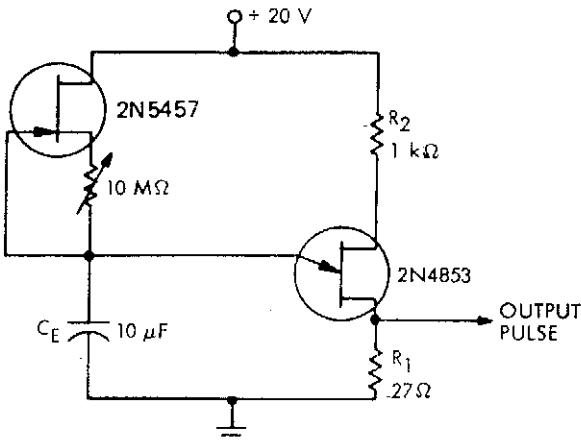
### Circuit Notes

The circuit lowers the effective peak current of the output PUT, Q2. By allowing the capacitor to charge with high gate voltage and periodically lowering gate voltage, when Q1 fires, the timing resistor can be a value which supplies a much lower current than  $I_p$ . The triggering requirement here is that minimum charge to trigger flow through the timing resistor during the period of the Q1 oscillator. This is not capacitor size dependent, only capacitor leakage and stability dependent.



## TIME DELAY WITH CONSTANT CURRENT CHARGING



**Fig. 105-2**

MOTOROLA INC.
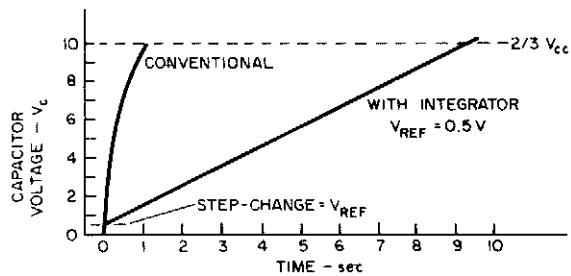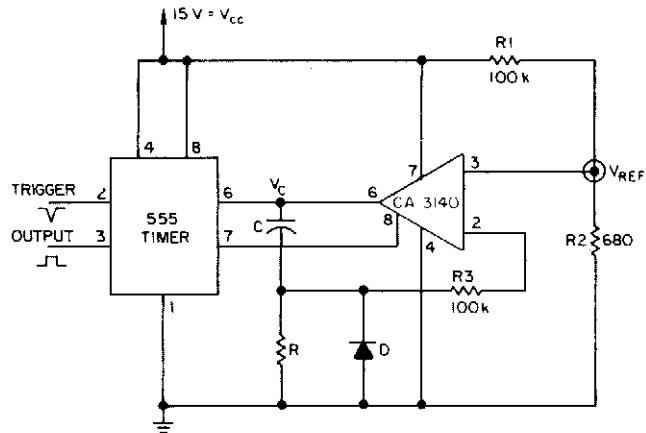
## LOW-COST INTEGRATOR MULTIPLIES 555 TIMER'S DELAY




ELECTRONIC DESIGN

*Fig. 105-3*

Circuit Notes

Long delay times can be derived from a 555 timer with reasonably sized capacitors if an integrator circuit is used. The capacitor's charging time with an integrator circuit can be much longer than with a conventional 555-timer configuration.
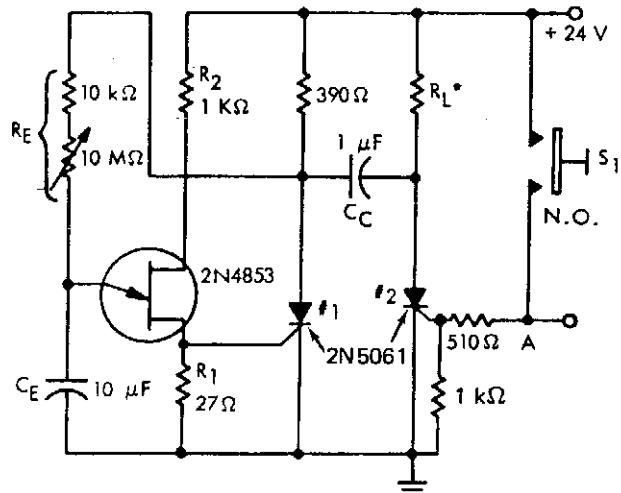
## **SIMPLE TIME-DELAY CIRCUIT USING TWO SCRs**



\*Value of  $R_L$  must be low enough to allow hold current to flow in the SCR.

**MOTOROLA INC.**

*Fig. 105-4*

# **106**

## **Timers**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Long-Term Electronic Timer
- Timer with Alarm
- Timer Circuit
- PUT Long Duration Timer
- Programmable Voltage Controlled Timer
- Low Power Microprocessor Programmable Interval Timer
- Precision Elapsed Time/Countdown Timer
- Adjustable AC Timer .2 to 10 sec.


## LONG-TERM ELECTRONIC TIMER

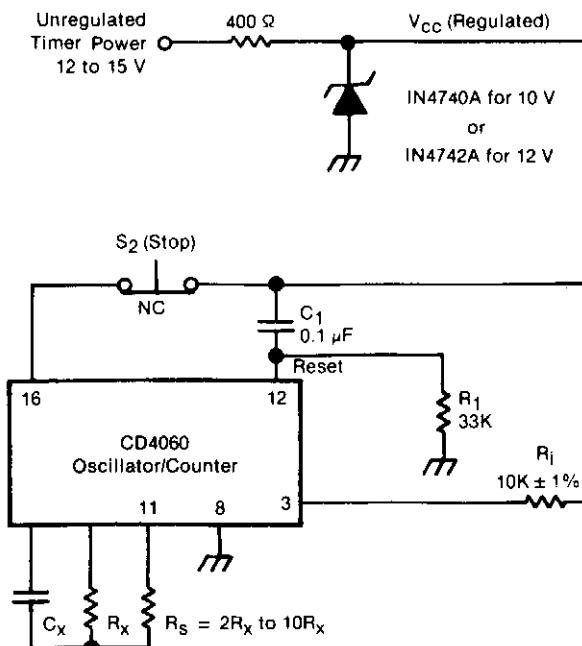

**Fig. 106-1**

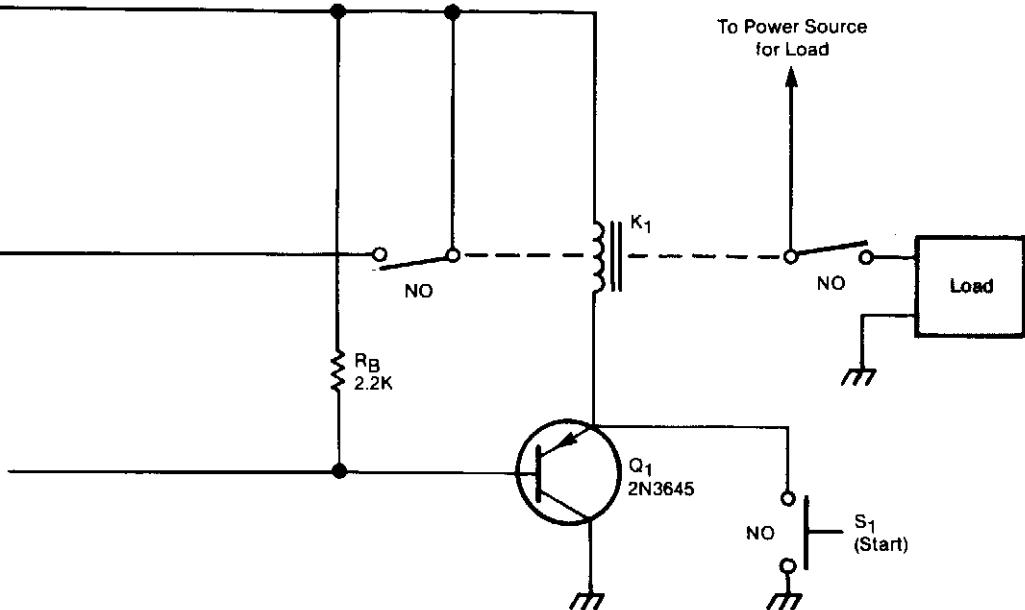
### Circuit Notes

The timer includes an oscillator and a counter in an integrated circuit. The timing interval equals the oscillator period multiplied by the number of cycles to be counted. The oscillator frequency depends upon resistor  $R_S$  and capacitor  $C_X$ . The number of oscillator cycles to be counted before the counter output changes state is determined by the selection of the counter output terminal, shown here as pin 3. The interval can be set anywhere in the range from fractions of a second to months; it is given by  $T = 0.55 R_S C_X^{2^n}$ , where  $n$  is an integer determined by the counter-output selection. Operation is initiated by the closure of momentary switch  $S_1$  (or by a command signal having a similar effect). This grounds one side of relay  $K_1$ , thereby activating the relay



and causing the closure of the switches that supply power to the timer and to the load. The turn-on of  $V_{CC}$  at the timer is coupled through  $C_1$  to the counter-reset terminal, thus resetting the counter. The initial reset voltage transient is then drained away through  $R_1$  to permit normal operation. During the first half cycle of the counter operation, the counter output voltage (at pin 3 in this case) is low. This turns on transistor  $Q_1$  so that relay  $K_1$  latches on, enabling the timer to continue running even though switch  $S_1$  has opened. The oscillator runs while the relay is on. When the number of oscillator cycles reaches the limit, the counter output voltage at pin 3 goes high. This turns off  $Q_1$ , thereby turning off the relay and returning the system to the original "power-off" state to await the next starting command. The timing cycle can also be interrupted and the system turned off by opening normally-closed switch  $S_2$ .

## TIMER WITH ALARM

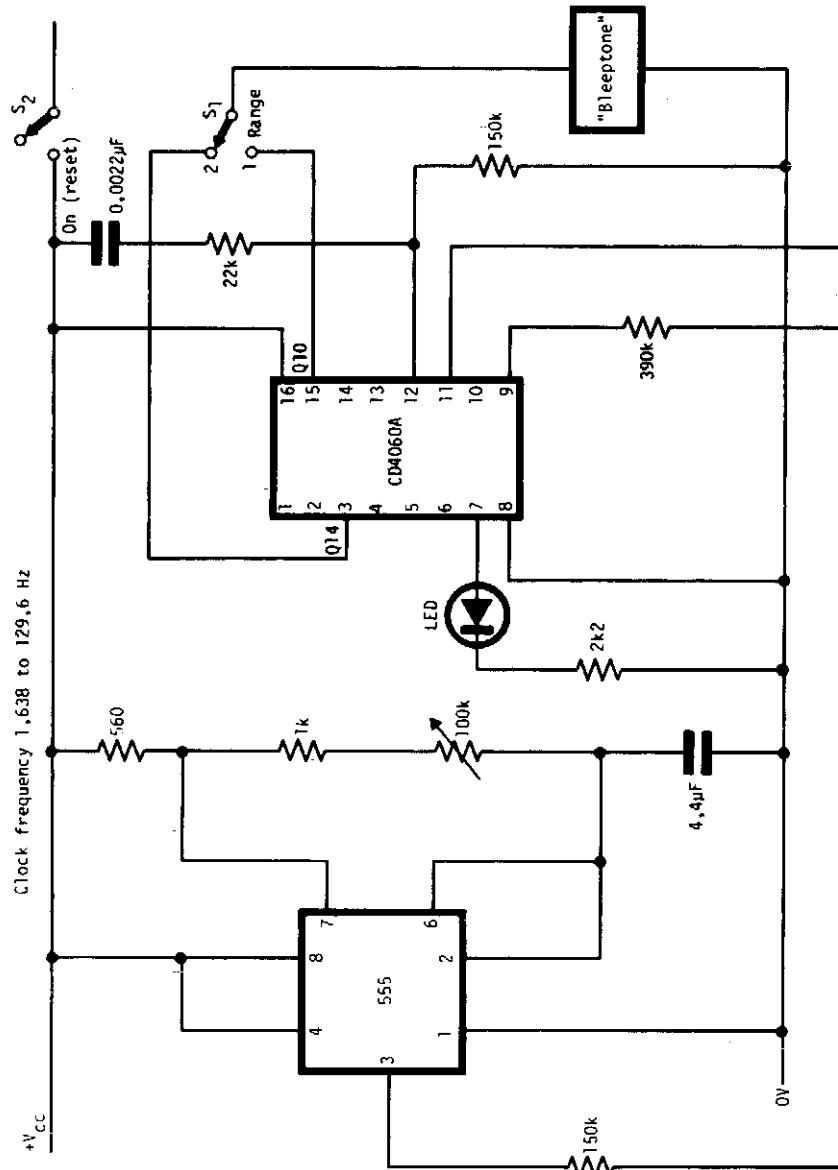


**Fig. 106-2**

Circuit Notes

The circuit has two ranges: 10 secs to 5 mins and 1 min to 80 mins. It can be powered by a 9-V battery. With the LED connected as shown a reasonable frequency of flashing occurs throughout the range of operation. This circuit is reset when S2 is closed.

ELECTRONIC ENGINEERING

## **TIMER CIRCUIT**

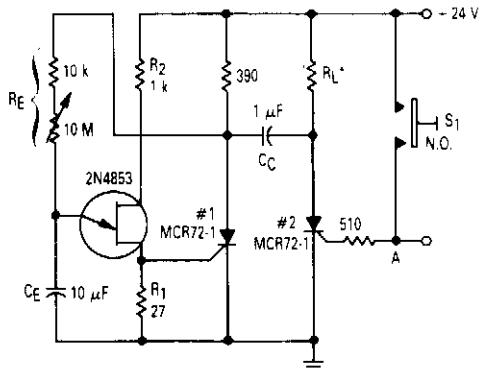

\*VALUE OF  $R_L$  MUST BE LOW ENOUGH TO ALLOW HOLD CURRENT TO FLOW IN THE SCR.


MOTOROLA

*Fig. 106-3*

Circuit Notes

After one cycle of operation, SCR 1 will be on, and a low value of voltage is applied to the UJT emitter circuit, interrupting the timing function. When pushbutton S1 is pushed, or a positive going pulse is applied at point A, SCR 2 will turn on, and SCR 1 will be turned off by commutating capacitor CC. With SCR 1 off, the supply voltage will be applied to RE and the circuit will begin timing again. After a period of time determined by the setting of RE, the UJT will fire and turn SCR 1 on and commute SCR 2 off. The time delay is determined by the charge time of the capacitor.

### **PUT LONG DURATION TIMER**

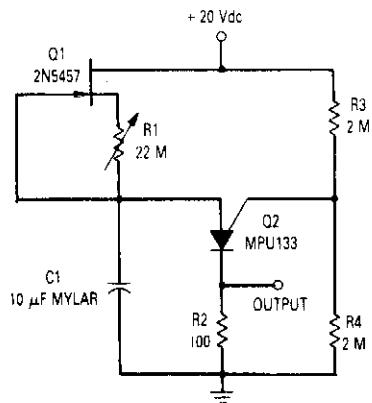


Circuit Notes

The time circuit can provide a time delay of up to 20 minutes. The circuit is a standard relaxation oscillator with a FET current source in which resistor R1 is used to provide reverse bias on the gate-to-source of the JFET. This turns the JFET off and increases the charging time of C1. C1 should be a low leakage capacitor such as a mylar type.

MOTOROLA

*Fig. 106-4*

## PROGRAMMABLE VOLTAGE CONTROLLED TIMER

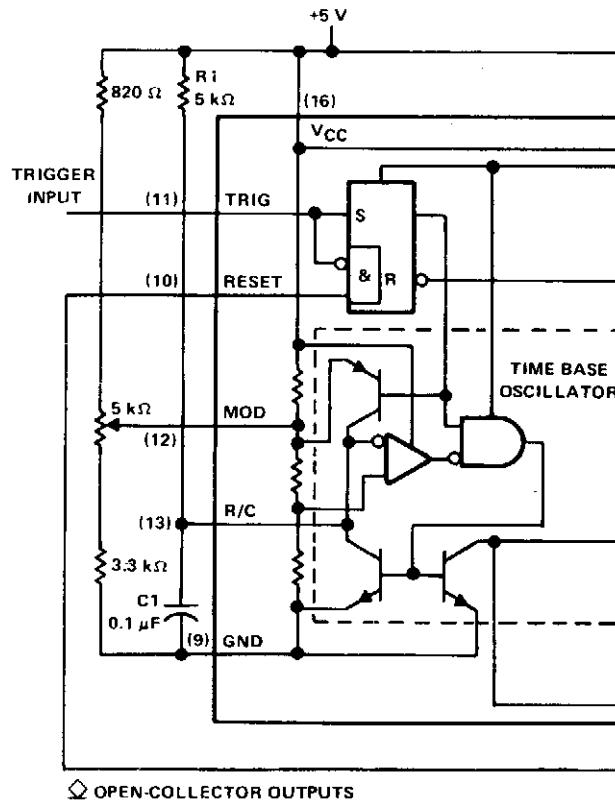


TEXAS INSTRUMENTS

*Fig. 106-5*
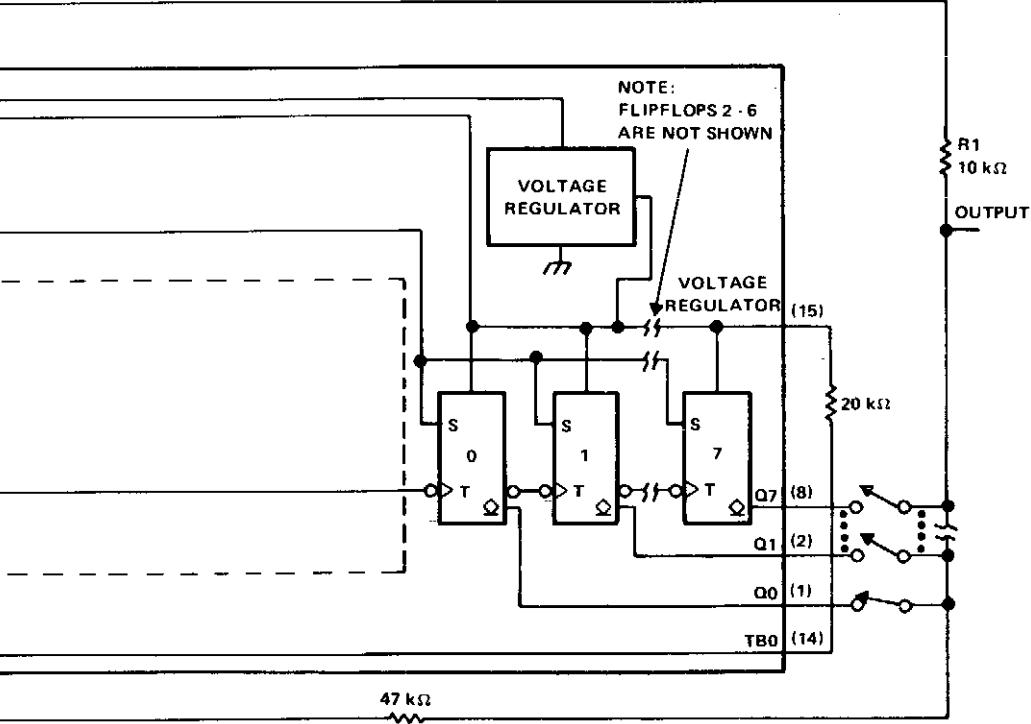
### Circuit Notes


The  $\mu$ A2240 may easily be configured as a programmable voltage controlled timer with a minimum number of external components. The modulation input (pin 12), which allows external adjustment of the input threshold level. A variable voltage is applied from the arm of a 10 k ohm potentiometer connected from  $V_{CC}$  to ground. A change in the modulation input voltage will result in a change in the time base oscillator frequency and the period of the time base output (TBO). The TBO has an open-collector output that



is connected to the regulator output via a 10 k ohm pull-up resistor. The output of the TBO drives the input to the 8-stage counter section.

At start-up, a positive trigger pulse starts the TBO and sets all counter outputs to a low state. The binary outputs are open-collector stages that may be connected together to the 10 k ohm pull-up resistor to provide a "wired-OR" output function. This circuit may be used to generate 255 discrete time delays that are integer multiples of the time-base period. The total delay is the sum of the number of time-base periods, which is the binary sum of the Q outputs connected. Delays from 200  $\mu$ s to 0.223 s are possible with this configuration.
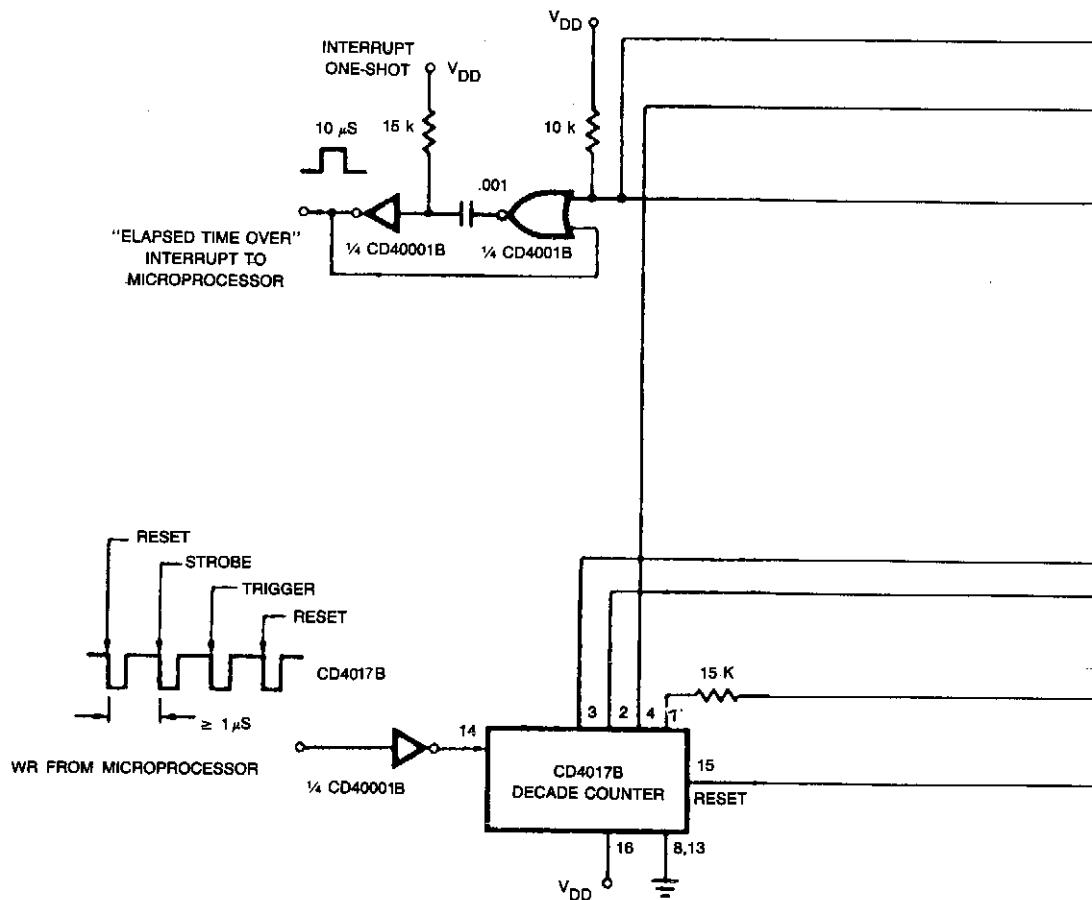
## LOW POWER MICROPROCESSOR PROGRAMMABLE INTERVAL TIMER




INTERSIL

*Fig. 106-6*
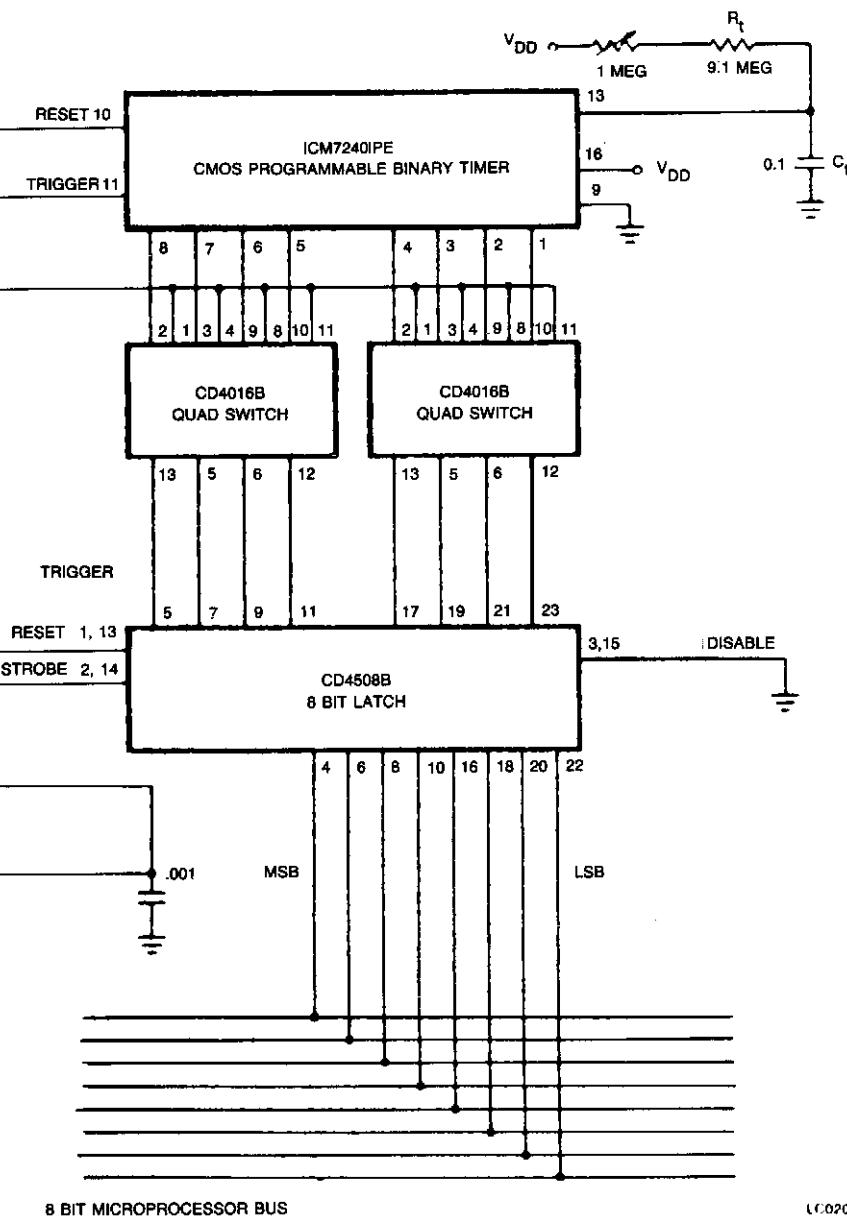
### Circuit Notes

The microprocessor sends out an 8-bit binary code on its 8-bit I/O bus (the binary value needed to program the ICM7240), followed by four WRITE pulses into the CD4017B decade counter. The first pulse resets the 8-bit latch, the second strobes the binary value into the 8-bit latch, the third triggers the ICM7240 to begin its timing cycle and the fourth resets the decade counter. The ICM7240 then counts the interval of time



determined by the R-C value on pin 13, and the programmed binary count on pins 1 through 8. At the end of the programmed time interval, the interrupt one-shot is triggered, informing the microprocessor that the programmed time interval is over. With a resistor of approximately 10 M ohm and a can capacitor of 0.1  $\mu$ F, the time base of the ICM7240 is one second. Thus, a time of 1-255 seconds can be programmed by the microprocessor, and by varying R or C, longer or shorter time bases can be selected.

## PRECISION ELAPSED TIME/COUNTDOWN TIMER

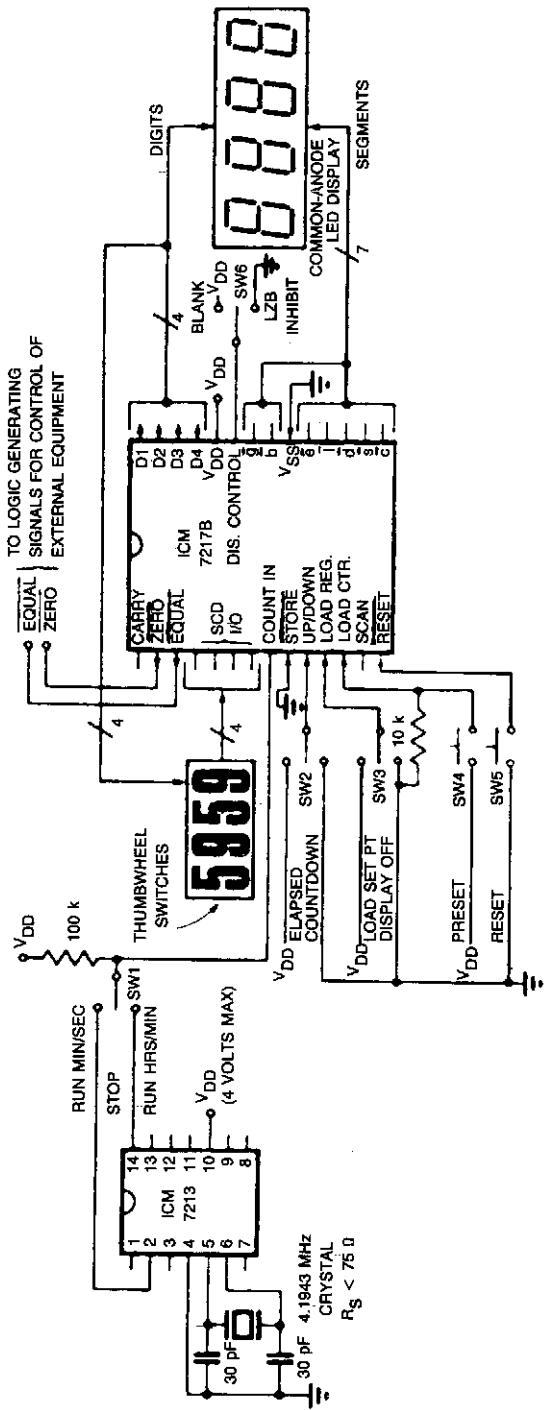



Fig. 106-7

INTERSIL

Circuit Notes

The circuit uses an ICM7213 precision one minute/one second timebase generator using a 4.1943 MHz crystal for generating pulses counted by an ICM7217B. The thumbwheel switches allow a starting time to be entered into the counter for a preset-countdown type timer, and allow the register to be set for compare functions. For instance, to make a 24-hour clock with BCD output the register can be preset with 2400 and the EQUAL output used to reset the counter. Note the 10 k resistor connected between the LOAD COUNTER terminal and ground. This resistor pulls the LOAD COUNTER input low when not loading, thereby inhibiting the BCD output drivers. This resistor should be eliminated and SW4 replaced with an SPDT center-off switch if the BCD outputs are to be used.

**ADJUSTABLE AC TIMER .2 TO 10 SEC.**

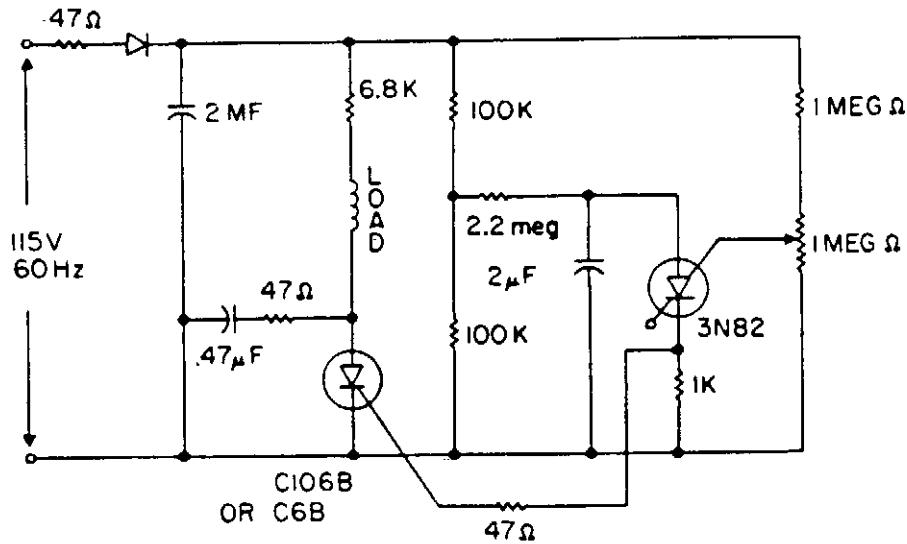

GENERAL ELECTRIC

*Fig. 106-8*

# 107


## Tone Control Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

- Guitar Treble Boost
- Tone Control
- Ten Band Graphic Equalizer, Using Active Filters
- Tone-Control Audio Amplifier
- Mike Preamp with Tone Control
- Low Cost High-Level Preamp and Tone Control Circuit
- Passive Tone-Control Circuit

## GUITAR TREBLE BOOST

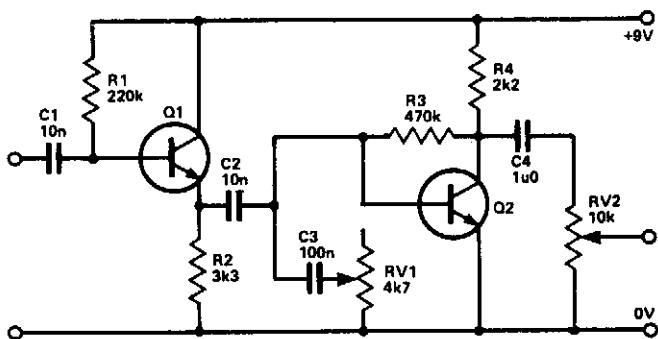



ELECTRONICS TODAY INTERNATIONAL

**Fig. 107-1**

### Circuit Notes

Q1 is connected as an emitter follower in order to present a high input impedance to the guitar. C2, being a relatively low capacitance, cuts out most of the bass, and C3 with RV1 acts as a simple tone control to cut the treble, and hence the amount of treble boost can be altered. Q2 is a simple preamp to recover signal losses in C2, C3, and RV1.

## TONE CONTROL

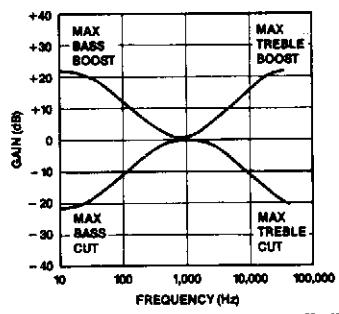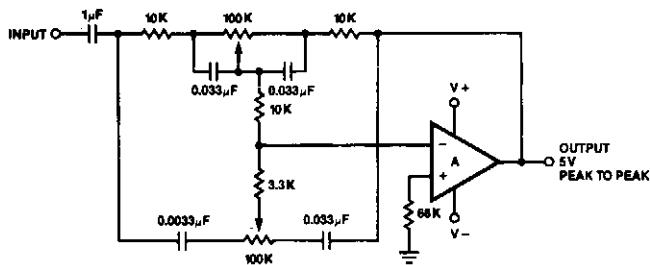

#### NOTES:

1. Amplifier A may be a NE531 or 301. Frequency compensation, as for unity gain non-inverting amplifiers, must be used.
2. Turn-over frequency — 1kHz.
3. Bass boost +20dB at 20Hz; bass cut -20dB at 20Hz, treble boost +19dB at 20Hz, treble cut -19dB at 20Hz.

All resistor values are in ohms.


**SIGNETICS**

**Fig. 107-2**
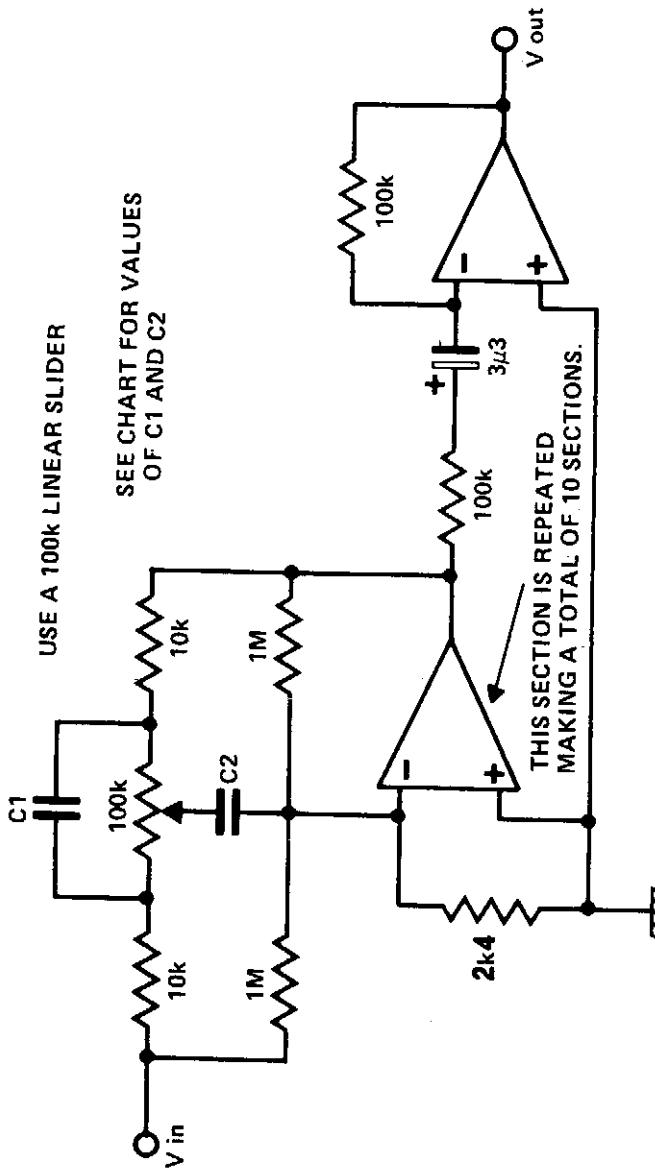
### Circuit Notes

Tone control of audio systems involves altering the flat response in order to attain more low frequencies or more high ones, dependent upon listener preference. The circuit provides 20 dB of bass or treble boost or cut as set by the variable resistance. The actual response of the circuit is shown also.


TEN BAND GRAPHIC EQUALIZER, USING ACTIVE FILTERS



ELECTRONICS TODAY INTERNATIONAL

Fig. 107-3

CHANNEL CENTRE FREQ. IN Hz	C1	C2
32	180n	18n
64	100n	10n
125	47n	4n7
250	22n	2n2
500	12n	1n2
1000	5n6	560p
2000	2n7	270p
4000	1n5	150p
8000	680p	68p
16000	360p	36p

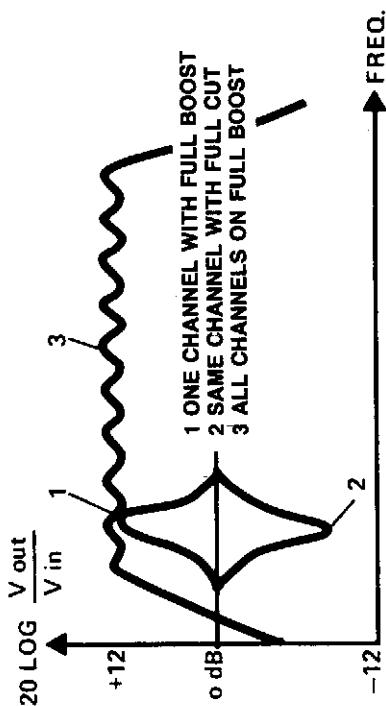

#### Circuit Notes

The above circuit is repeated ten times. Use the table to calculate values.

## TONE-CONTROL AUDIO AMPLIFIER


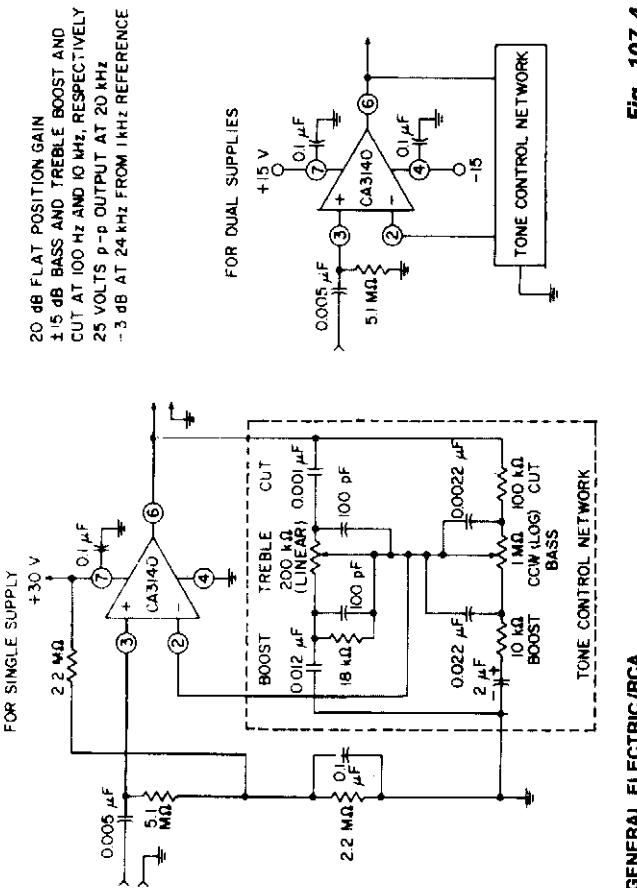


Fig. 107-4

### Circuit Notes

The circuit makes excellent use of the high slew rate, wide bandwidth, high input impedance, and high-output voltage capability of the CA3140 BiMOS op amp. The wideband gain of this circuit is equal to the ultimate boost or cut plus one, in this case a gain of eleven. For 20-dB boost or cut, input loading is essentially equal to the resistance from terminal 3 to ground.

### MIKE PREAMP WITH TONE CONTROL

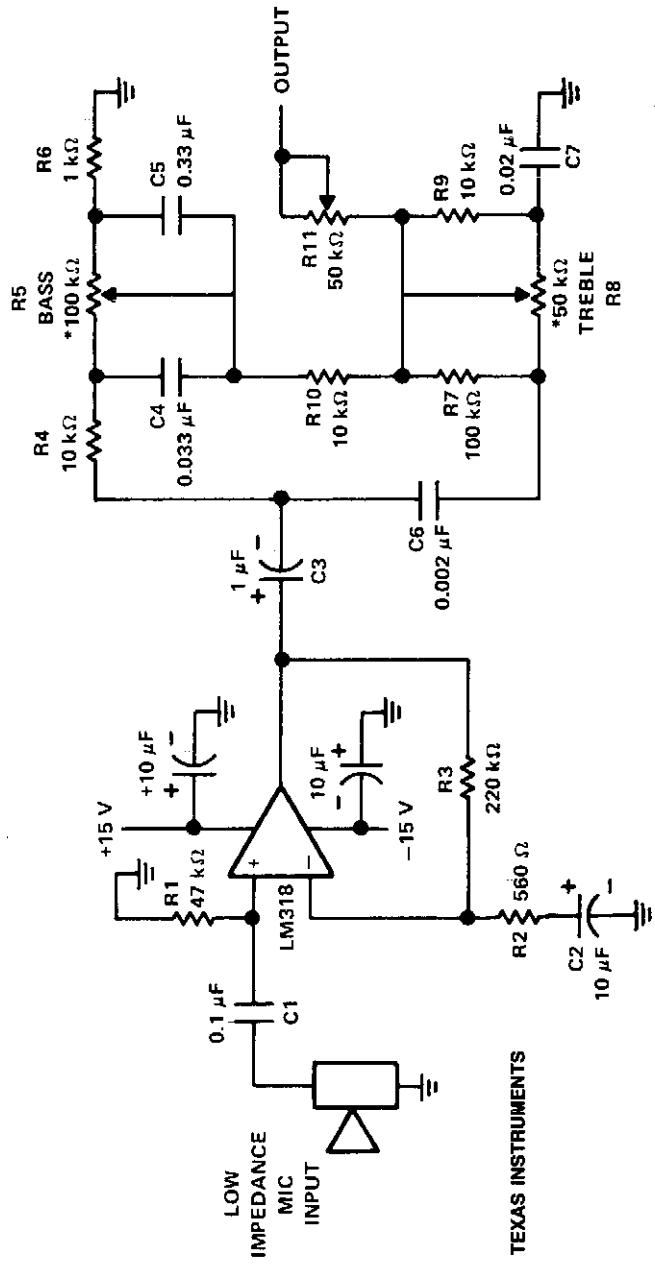


\* THE TONE CONTROLS ARE AUDIO TAPER (LOG) POTENTIOMETERS.

Fig. 107-5

### Circuit Notes

The LM318 op amp is operated as a standard non-inverting amplifier. Resistor R1 (47 k ohm) provides an input path to ground for the bias current of the non-inverting input. The combination of R2 (560 ohm) and C2 (10  $\mu$ F) provides a frequency roll-off below 30 Hz. At 30 Hz and above the gain is relatively flat at about 50 dB, set by the ratio R3/R2. R3 (200 k ohm) furnishes negative feedback from the output to the inverting input of the op amp. C3 (1.0  $\mu$ F electrolytic) ac couples the preamp to the tone control section. The top half of the tone control section is the bass control. The bottom half controls the treble frequency response. These tone controls (R5 and R8) require audio taper (logarithmic) potentiometers. The 50 k ohm potentiometer on the output can be used to set the output or gain of the preamp.
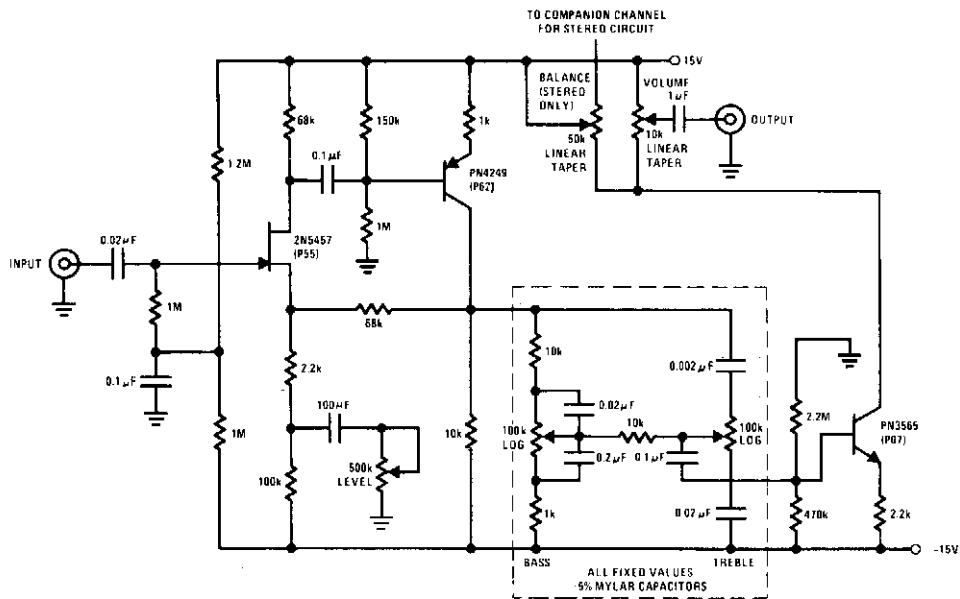
## LOW COST HIGH-LEVEL PREAMP AND TONE CONTROL CIRCUIT




NATIONAL SEMICONDUCTOR CORP.

Fig. 107-6

### Circuit Notes

This preamp and tone control uses the JFET to its best advantage; as a low noise high input impedance device. All device parameters are noncritical, yet the circuit achieves harmonic distortion levels of less than 0.05% with a S/N ratio of over 85 dB. The tone controls allow 18 dB of cut and boost; the amplifier has a 1-V output for 100-mV input at maximum level.

### PASSIVE TONE-CONTROL CIRCUIT

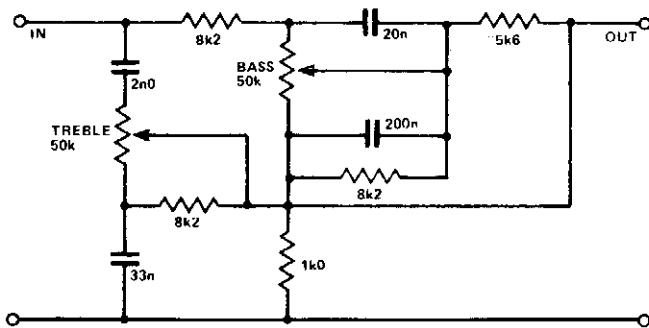

ELECTRONICS TODAY INTERNATIONAL

Fig. 107-7

#### Circuit Notes

A simple circuit using two potentiometers and easily available standard value components provides tone control. The impedance level is suitable for low-level transistor or op amp circuitry.

# **108**

## **Touch-Switch Circuits**


---

---

The sources of the following circuits are contained in the Sources section beginning on page 694. The figure number contained in the box of each circuit correlates to the source entry in the Sources section.

Touch On/Off Switch  
Touch Switch  
Touchomatic

## TOUCH ON/OFF SWITCH

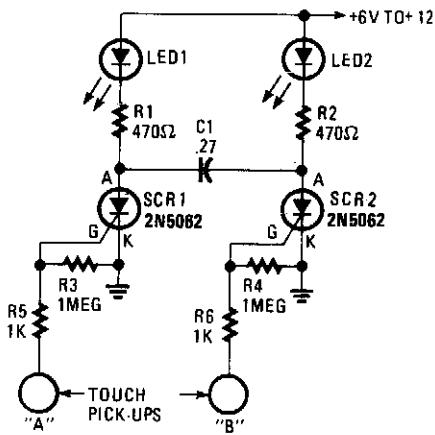


HANDS-ON ELECTRONICS

Fig. 108-1

### Circuit Notes

If a Touch On/Off Switch is desired, this circuit fills the bill. Two sensitive gate SCRs are interconnected, so that when one of the devices is turned on, the other (if on) is forced off. That toggling effect gives an on/off circuit condition for each of the LEDs in the SCR-anode circuits. To turn LED1 on and LED2 off, simply touch the "A" terminal, and to turn LED1 off and LED2 on, the "B" pick-up must be touched. It is possible to simultaneously touch both terminals, causing both SCRs to turn on together. To reset the circuit to the normal one-on/one-off condition, momentarily interrupt the circuit's dc power source. Additional circuitry can be connected to the anode circuit of either or both SCRs to be controlled by the on/off function of the touch switch.

## TOUCH SWITCH

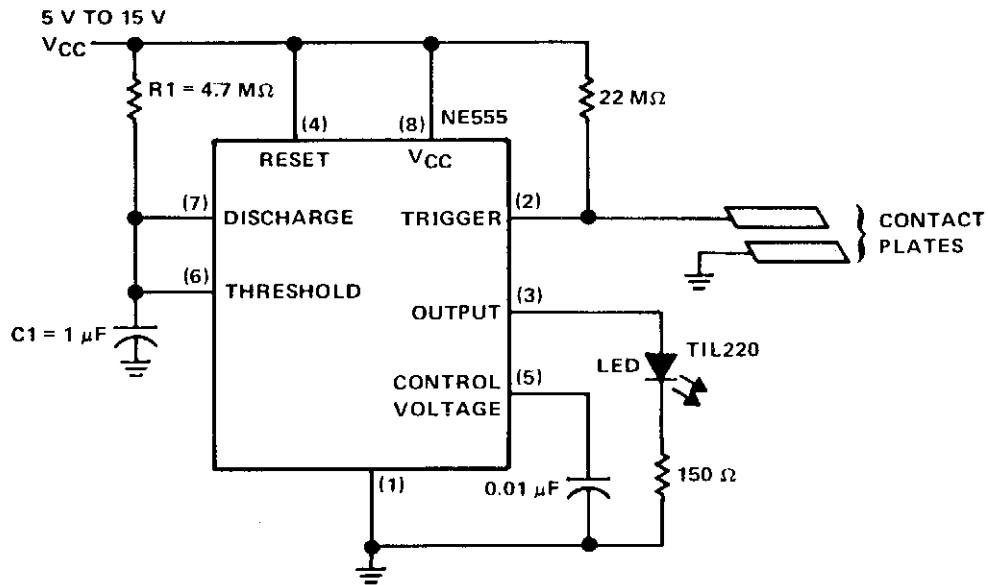


TEXAS INSTRUMENTS

*Fig. 108-2*

### Circuit Notes

The circuit is basically a NE555 monostable, the only major difference being its method of triggering. The trigger input is biased to a high value by the 22 M ohm resistor. When the contact plates are touched, the skin resistance of the operator will lower the overall impedance from pin 2 to ground. This action will reduce the voltage at the trigger input to below the  $\frac{1}{3} V_{CC}$  trigger threshold and the timer will start. The output pulse width will be  $T = 1.1 R_1 C_1$ , in this circuit about 5 seconds. A relay connected from pin 3 to ground instead of the LED and resistor could be used to perform a switching function.

## TOUCHOMATIC

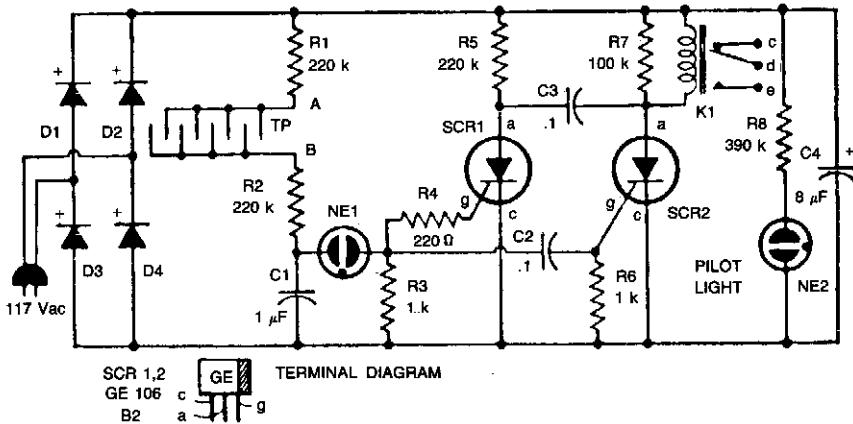

TAB BOOKS, INC.

*Fig. 108-3*

### Circuit Notes

When someone touches the touchplate (TP), the resistance of his finger across points A and B is added in series to the combination of R1 and R2, the capacitor C1 begins to charge. When the voltage across C1 is finally sufficient to fire NE1, C1 will begin to discharge. When NE1 fires, it produces a short between its terminals. Since R3 is connected across C1, they are effectively in series after NE1 fires. A voltage spike will then be passed by C2 and this will act as a positive triggering pulse. The pulse is fed to both SCR gates: SCR2 conducts, thereby closing relay K1. With a finger no longer on the touchplate, no more pulses are forthcoming because the C1 charge path is open. The next contact with the touchplate will produce a pulse which triggers SCR1. SCR2 is now off by capacitor C3 which was charged by current passing through R6 and SCR2. The firing of SCR1 in this way places a negative voltage across SCR2 which momentarily drops the relay current to a point below the holding current value of SCR2. (Holding current is the minimum current an SCR requires to remain in a conducting state once its gate voltage is removed.) With SCR2 turned off, the relay will open and SCR1 will turn off due to the large resistance in series with its anode. Starved in this way SCR1 turns off because of a forced lack of holding current.

# Sources Index

---

---

## Chapter 1

- Fig. 1-1. Signetics 1987 Linear Data Manual Vol. 2, 2/87, p.7-65.  
Fig. 1-2. General Electric Application Note 90.16, p. 25.  
Fig. 1-3. Courtesy, William Sheets.  
Fig. 1-4. General Electric Application Note 90.16, p. 25.  
Fig. 1-5. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 27.  
Fig. 1-6. R-E Experimenters Handbook, p. 157.

## Chapter 2

- Fig. 2-1. Linear Technology Corporation, Linear Applications Handbook, 1987, p. AN21-2  
Fig. 2-2. Linear Technology Corporation, Linear Databook Supplement, 1988, p. S2-34.  
Fig. 2-3. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-154.  
Fig. 2-4. Linear Technology Corp., Linear Databook, 1986, p. 2-83.

- Fig. 2-5. National Semiconductor Corp., Transistor Databook, 1982, p. 11-23.  
Fig. 2-6. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN21-1.  
Fig. 2-7. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 10/86, p. 4-260.  
Fig. 2-8. Electronic Engineering, 11/86, p. 40.  
Fig. 2-9. National Semiconductor Corp., Transistor Databook, 1982, p. 11-25.  
Fig. 2-10. Siliconix, Integrated Circuits Data Book, 3/85, p. 2-112.  
Fig. 2-11. Electronics Engineering, 9/78, p. 17.  
Fig. 2-12. Electronics Engineering, 9/84, p. 33.  
Fig. 2-13. Signetics, 1987 Linear Data Manual, Vol. 1: Communications, 8/87, p. 4-346.  
Fig. 2-14. NASA Tech Briefs, Spring 1983, p. 244.  
Fig. 2-15. Radio Electronics, 7/83, p. 74.  
Fig. 2-16. Motorola Inc., Linear Integrated Circuits, 1979, p. 6-58.  
Fig. 2-17. MR-E Experimenters Handbook, p. 158.

- Fig. 2-19. Popular Electronics, 8/68.*  
*Fig. 2-20. Ham Radio, 9/84, p. 24.*  
*Fig. 2-21. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 20.*  
*Fig. 2-22. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-2, 3-4.*  
*Fig. 2-23. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 3/87, p. 4-345.*  
*Fig. 2-24. Electronic Engineering, 11/85, p. 32.*  
*Fig. 2-25. NASA Tech Briefs, Sept/Oct 1986, p. 43.*

### Chapter 3

- Fig. 3-1. Intersil, Component Data Catalog, 1987, p. 4-43.*  
*Fig. 3-2. Linear Technology, Application Note 9, p. 16.*  
*Fig. 3-3. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 26.*  
*Fig. 3-4. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN15-2.*  
*Fig. 3-5. Linear Technology Corp., Linear Databook, 1986, p. 5-17.*  
*Fig. 3-6. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 11/86, p. 5-215.*  
*Fig. 3-7. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S5-126.*  
*Fig. 3-8. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 12/86, p. 4-67.*

### Chapter 4

- Fig. 4-1. Electronic Design, 5/82, p. 214.*  
*Fig. 4-2. R-E Experimenters Handbook, p. 160.*  
*Fig. 4-3. Popular Electronics, 11/73, p. 50.*

### Chapter 5

- Fig. 5-1. Hands-On Electronics, Summer 1984, p. 77.*  
*Fig. 5-2. Courtesy, William Sheets.*  
*Fig. 5-3. Courtesy, William Sheets.*  
*Fig. 5-4. Electronic Engineering, 5/84, p. 44.*  
*Fig. 5-5. Texas Instruments, Linear and Interface Circuits Applications, vol. 1, 1985, p. 3-13.*

- Fig. 5-6. Electronics Today International, 4/85, p. 82.*

### Chapter 6

- Fig. 6-1. Tab Books Inc., 101 Sound, Light, and Power IC Projects.*  
*Fig. 6-2. Radio Electronics, 7/70, p. 38.*  
*Fig. 6-3. Hands-On Electronics, Jul/Aug 1986, p. 16.*  
*Fig. 6-4. 73 Magazine, 12/76, p. 170.*  
*Fig. 6-5. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 21.*  
*Fig. 6-6. Ibid.*  
*Fig. 6-7. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-17.*  
*Fig. 6-8. Signetics, Analog Data Manual, 1982, p. 3-90.*

### Chapter 7

- Fig. 7-1. Motorola, TMOS Power FET Design Ideas, 1985.*  
*Fig. 7-2. Hands-On Electronics, 4/87, p. 95.*  
*Fig. 7-3. Tab Books, Inc., The Giant book of Easy-To-Build Electronics Projects, 1982, p. 196.*  
*Fig. 7-4. General Electric, Optoelectronics, Third Edition, p. 151.*  
*Fig. 7-5. Tab Books, Inc., The Build-It Book of Electronic Projects, No. 1498, p. 28.*  
*Fig. 7-6. Radio-Electronics, 6/85, p. 60.*  
*Fig. 7-7. Popular Electronics, 12/74, p. 6.*  
*Fig. 7-8. Popular Electronics, 4/75, p. 68.*  
*Fig. 7-9. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 10-21.*  
*Fig. 7-10. Texas Instruments, Linear and Interface Circuits Applications, 1985, vol. 1, p. 3-5.*  
*Fig. 7-11. Radio-Electronics, 1979.*  
*Fig. 7-12. Hands-On Electronics, 1/87, p. 30.*  
*Fig. 7-13. Electronic Engineering, 12/75, p. 9.*  
*Fig. 7-14. Electronic Design 18, 9/76, p. 114.*  
*Fig. 7-15. Radio-Electronics, 5/87, p. 10.*  
*Fig. 7-16. Hands-On Electronics, Fall 1984, p. 45.*  
*Fig. 7-17. Hands-On Electronics, 4/87, p. 92.*  
*Fig. 7-18. General Electric, Optoelectronics, Third Edition, p. 105.*

## **Chapter 8**

- Fig. 8-1. CQ, 7/82, p. 18.  
Fig. 8-2. Electronics Design, 7/76, p. 120.  
Fig. 8-3. Courtesy, William Sheets.  
Fig. 8-4. Moli Energy Limited.  
Fig. 8-5. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN6-3.  
Fig. 8-6. Courtesy, William Sheets.  
Fig. 8-7. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, p. 6-24.  
Fig. 8-8. Linear Technology Corp., Linear Databook Supplement, 1988, p. S5-11.  
Fig. 8-9. Motorola, TMOS Power FET Design Ideas, 1985, p. 8.  
Fig. 8-10. Radio Electronics, 9/85, p. 44.  
Fig. 8-11. Siliconix, MOSpower Applications Handbook, p. 6-176.

## **Chapter 9**

- Fig. 9-1. Motorola, TMOS Power FET Ideas, 1985, p. 7.  
Fig. 9-2. Electronic Engineering, 2/85, p. 45.  
Fig. 9-3. Electronic Engineering, 10/70, p. 17.  
Fig. 9-4. Electronic Engineering, Mid5/78, p. 11.  
Fig. 9-5. Moli Energy Limited, Publication MEL-126.  
Fig. 9-6. Linear Technology Corp., Linear Databook, 1986, p. 2-104.  
Fig. 9-7. Courtesy, William Sheets.  
Fig. 9-8. Tab Books, Inc., 101 Sound, Light, and Power IC Projects.

## **Chapter 10**

- Fig. 10-1. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 2/87, p. 5-367.  
Fig. 10-2. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-3, 3-4.  
Fig. 10-3. Courtesy, William Sheets.  
Fig. 10-4. General Electric/RCA, BIMOS Operational Amplifiers Circuit Ideas, 1987, p. 17.  
Fig. 10-5. Siliconix, Small-Signal FET Data Book, 1/86, p. 7-29.  
Fig. 10-6. Linear Technology Corp., Linear Databook, 1986, p. 2-83.  
Fig. 10-7. Linear Technology Corp., Linear Databook, 1986, p. 2-101.

## **Chapter 11**

- Fig. 11-1. Signetics, 1987 Linear Data Manual, Vol. 1: Communications, 2/87, p. 4-312.  
Fig. 11-2. Electronic Engineering, 5/86, p. 50.  
Fig. 11-3. Electronic Design, 9/73, p. 148.  
Fig. 11-4. Intersil, Component Data Catalog, 1987, p. 6-28.  
Fig. 11-5. Signetics, 555 Timers, 1973, p. 19.

## **Chapter 12**

- Fig. 12-1. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 7-21.  
Fig. 12-2. Electronic Engineering, 2/85, p. 34.

## **Chapter 13**

- Fig. 13-1. Hands-On Electronics, 3/87, p. 25.  
Fig. 13-2. Motorola, TMOS Power FET Design Ideas, 1985, p. 17.  
Fig. 13-3. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN13-23.  
Fig. 13-4. Intersil, Component Data Catalog, 1987, p. 5-113.  
Fig. 13-5. Courtesy, William Sheets.  
Fig. 13-6. Linear Technology Corp., Linear Databook, 1986, p. 3-23.  
Fig. 13-7. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-57.

## **Chapter 14**

- Fig. 14-1. Electronic Engineering, 3/78, p. 38.  
Fig. 14-2. Hands-On Electronics, Nov/Dec 1985, p. 4.

## **Chapter 15**

- Fig. 15-1. Linear Technology Corp., Linear Databook, 1986, p. 2-82.  
Fig. 15-2. Popular Electronics, 9/77, p. 92.  
Fig. 15-3. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 5-269.  
Fig. 15-4. Siliconix, Integrated Circuits Data Book, 3/85, p. 5-8.  
Fig. 15-5. Electronic Engineering, 2/85, p. 45.  
Fig. 15-6. Electronic Engineering, 2/84, p. 36.  
Fig. 15-7. Electronic Design 15, 7/79, p. 120.  
Fig. 15-8. Electronic Engineering, 12/78, p. 17.

- Fig. 15-9. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 23.*
- Fig. 15-10. Electronic Engineering, 11/86, p. 39.*
- Fig. 15-11. Popular Electronics, 3/79, p. 77.*
- Fig. 15-12. Electronic Engineering, 7/86, p. 27.*
- Fig. 15-13. Electronic Engineering, 1/86, p. 37.*

## Chapter 16

- Fig. 16-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 5-215.*
- Fig. 16-2. Linear Technology Corp., Linear Databook, 1986, p. 4-15.*
- Fig. 16-3. Siliconix, Integrated Circuits Data Book, 3/85, p. 2-207.*
- Fig. 16-4. Siliconix, Integrated Circuits Data Book, 3/85, p. 2-231.*
- Fig. 16-5. Intersil, Component Data Catalog, 1987, p. 13-51.*
- Fig. 16-6. Siliconix, Integrated Circuits Data Book, 3/85, p. 3-62.*
- Fig. 16-7. Datel, Data Conversion Components, p. 4-37.*

## Chapter 17

- Fig. 17-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-62.*
- Fig. 17-2. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 4-136.*
- Fig. 17-3. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 5-269.*
- Fig. 17-4. Electronic Engineering, 12/77, p. 19.*
- Fig. 17-5. Siliconix, Integrated Circuits Data Book, 3/85, p. 5-17.*
- Fig. 17-6. Linear Technology Corp., Linear Databook, 1986, p. 5-17.*
- Fig. 17-7. Analog Devices, Data Acquisition Databook, 1982, p. 4-56.*
- Fig. 17-8. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-311.*
- Fig. 17-9. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 20.*
- Fig. 17-10. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 11.*

- Fig. 17-11. Siliconix, MOSpower Applications Handbook, p. 6-178.*
- Fig. 17-12. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 5-368.*
- Fig. 17-13. National Semiconductor Corp., Transistor Databook, 1982, p. 7-27.*
- Fig. 17-14. National Semiconductor Corp., 1984 Linear Supplemental Databook, p. S5-142.*
- Fig. 17-15. Electronic Engineering, 8/83, p. 141.*

## Chapter 18

- Fig. 18-1. Intersil, Component Data catalog, 1987, p. 14-70.*
- Fig. 18-2. General Electric, Application Note 90.16, p. 29.*
- Fig. 18-3. General Electric, Application Note 90.16, p. 29.*
- Fig. 18-4. General Electric, Application Note 90.16, p. 28.*
- Fig. 18-5. Intersil, Component Data Catalog, 1987, p. 14-91.*
- Fig. 18-6. Intersil, Component Data Catalog, 1987, p. 7-96.*
- Fig. 18-7. Intersil, Component Data Catalog, 1987, p. 14-121.*
- Fig. 18-8. Intersil, Databook 1987, p. 7-47.*

## Chapter 19

- Fig. 19-1. Ham Radio, 6/85, p. 23.*
- Fig. 19-2. Siliconix, MOSpower Design Catalog, 1/83, p. 5-27.*
- Fig. 19-3. Linear Technology Corp., Linear Databook, 1986, p. 2-104.*
- Fig. 19-4. QST, 12/85, p. 38.*
- Fig. 19-5. Linear Technology Corp., Linear Applications Handbook 1987, p. AN20-12.*
- Fig. 19-6. QST, 2/88, p. 43.*
- Fig. 19-7. Ham Radio, 2/79, p. 40.*
- Fig. 19-8. Courtesy, William Sheets.*
- Fig. 19-9. Courtesy, William Sheets.*
- Fig. 19-10. Electronic Design 21, 10/75, p. 98.*
- Fig. 19-11. Ham Radio, 2/79, p. 40.*
- Fig. 19-12. Ham Radio, 2/79, p. 42.*
- Fig. 19-13. Tab Books, Inc., The Complete Handbook of Amplifiers, Oscillators, and Multivibrators, No. 1230, p. 328.*
- Fig. 19-14. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 5-269.*

- Fig. 19-15. Motorola, MECL System Design Handbook, 1983, p. 227.*  
*Fig. 19-16. Electronic Design, 11/69, p. 109.*  
*Fig. 19-17. QST, 1/86, p. 40.*  
*Fig. 19-18. R-E Experimenters Handbook, p. 157.*  
*Fig. 19-19. Electronic Design 23, 11/74, p. 148.*

## Chapter 20

- Fig. 20-1. Linear Technology Corp., 1986 Linear Databook, p. 2-57.*  
*Fig. 20-2. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-13.*  
*Fig. 20-3. Intersil, Component Data Catalog, 1987, p. 7-4.*  
*Fig. 20-4. NASA Tech Briefs, Jul/Aug 1986, p. 37.*  
*Fig. 20-5. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 17.*  
*Fig. 20-6. Linear Technology Corp., Linear Databook, 1986, p. 2-85.*  
*Fig. 20-7. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 14.*

## Chapter 21

- Fig. 21-1. EXAR, Telecommunications Databook, 1986, p. 9-23.*  
*Fig. 21-2. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 3-17.*  
*Fig. 21-3. Signetics, 1987 Linear Data Manual, Vol. 1: Communications, 2/87, p. 4-66.*  
*Fig. 21-4. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/86, p. 4-263.*

## Chapter 22

- Fig. 22-1. Radio-Electronics, 12/86, p. 57.*  
*Fig. 22-2. Radio-Electronics, 8/87, p. 63.*  
*Fig. 22-3. Radio-Electronics, 8/87, p. 53.*  
*Fig. 22-4. Radio-Electronics, 6/87, p. 12.*  
*Fig. 22-5. EXAR, Telecommunications Databook, 1986, p. 9-23.*  
*Fig. 22-6. Radio-Electronics, 3/86, p. 51.*  
*Fig. 22-7. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/86, p. 7-123.*

- Fig. 22-8. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/86, p. 7-123.*  
*Fig. 22-9. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/86, p. 4-295.*

## Chapter 23

- Fig. 23-1. General Electric, Application Note 90.16, p. 26.*  
*Fig. 23-2. Siliconix, Integrated Circuits Data Book, 3/85, p. 5-16.*  
*Fig. 23-3. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-23.*  
*Fig. 23-4. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 18.*  
*Fig. 23-5. Intersil, Component Data Catalog, 1987, p. 7-44.*  
*Fig. 23-6. Electronic Engineering, 11/86, p. 39.*  
*Fig. 23-7. General Electric, Application Note 90.16, p. 27.*  
*Fig. 23-8. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 5-367.*  
*Fig. 23-9. Intersil, Component Data Catalog, 1987, p. 5-112.*  
*Fig. 23-10. GENERAL Electric, Application Note 90.16, p. 26.*

## Chapter 24

- Fig. 24-1. Electronic Engineering, 8/85, p. 30.*  
*Fig. 24-2. Electronic Engineering, 11/86, p. 40.*

## Chapter 25

- Fig. 25-1. CQ, 1/87, p. 36.*

## Chapter 26

- Fig. 26-1. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 26.*  
*Fig. 26-2. National Semiconductor Corp., Linear Databook, 1982, p. 171.*  
*Fig. 26-3. Electronic Engineering, 9/84, p. 30.*  
*Fig. 26-4. GENERAL Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 12.*

## **Chapter 27**

- Fig. 27-1. Motorola, TMOS Power FET Design Ideas, 1985, p. 18.  
 Fig. 27-2. Electronic Design, 12/87, p. 67.  
 Fig. 27-3. General Electric/RCA, BIMOS Operational Amplifiers Circuit Ideas, 1987, p. 22.  
 Fig. 27-4. Electronic Engineering, 6/78, p. 32.  
 Fig. 27-5. Electronic Engineering, 2/83, p. 37.

## **Chapter 28**

- Fig. 28-1. Tab Books, Inc., The Giant Book of Easy-To-Build Electronic Projects, 1982, p. 53.  
 Fig. 28-2. Hands-On Electronics, 2/87, p. 38.

## **Chapter 29**

- Fig. 29-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 4-135.  
 Fig. 29-2. Linear Technology Corp., Linear Databook, 1986, p. 2-82.  
 Fig. 29-3. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/86, p. 4-135.  
 Fig. 29-4. Transistor Databook, 1982, p. 11-25.

## **Chapter 30**

- Fig. 30-1. Hands-On Electronics, May/Jun 1986, p. 52.  
 Fig. 30-2. Popular Electronics, 3/67.  
 Fig. 30-3. Courtesy, William Sheets.

## **Chapter 31**

- Fig. 31-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN13-22.  
 Fig. 31-2. General Electric, Optoelectronics, Third Edition, p. 149.  
 Fig. 31-3. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-39.

## **Chapter 32**

- Fig. 32-1. Courtesy, William Sheets.  
 Fig. 32-2. Courtesy, William Sheets.  
 Fig. 32-3. Hands-On Electronics, 8/87, p. 65.  
 Fig. 32-4. Courtesy, William Sheets.  
 Fig. 32-5. Hands-On Electronics, 3/87, p. 27.  
 Fig. 32-6. Ham Radio, 9/86, p. 67.

## **Chapter 33**

- Fig. 33-1. Electronic Engineering, 10/48, p. 45.  
 Fig. 33-2. Electronics Today International, 10/78, p. 26.  
 Fig. 33-3. Hybrid Products Databook, 1982, p. 17-131.  
 Fig. 33-4. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-62.  
 Fig. 33-5. Intersil, Component Data Catalog, 1987, p. 8-102.  
 Fig. 33-6. 73 for Radio Amateurs, 2/86, p. 10.  
 Fig. 33-7. Intersil, Component Data Catalog, 1987, p. 7-45.  
 Fig. 33-8. Linear Technology Corp., 1986 Linear Databook, p. 2-56.  
 Fig. 33-9. Electronic Engineering, 2/47, p. 47.  
 Fig. 33-10. Courtesy, William Sheets.  
 Fig. 33-11. Raytheon, Linear and Integrated Circuits, 1984, p. 6-205.  
 Fig. 33-12. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-7.  
 Fig. 33-13. Motorola, Linear Integrated Circuits, 1979, p. 3-147.  
 Fig. 33-14. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-9.

## **Chapter 34**

- Fig. 34-1. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-52.  
 Fig. 34-2. Popular Electronics, 3/81, p. 100.  
 Fig. 34-3. Hands-On Electronics, Spring 1986, p. 4.  
 Fig. 34-4. Hands-On Electronics, Fall 1984, p. 61.  
 Fig. 34-5. General Electric, SCR Manual, Fourth Edition, p. 85.  
 Fig. 34-6. Electronic Design 65, 3/73, p. 84.  
 Fig. 34-7. Electronic Design, 3/69, p. 96.  
 Fig. 34-8. Electronic Engineering, 676, p. 32.  
 Fig. 34-9. Popular Electronics, 3/75, p. 78.  
 Fig. 34-10. General Electric, Optoelectronics, Third Edition.  
 Fig. 34-11. Radio-Electronics, 2/87, p. 36.  
 Fig. 34-12. General Electric, Application Note 200.35, p. 16.  
 Fig. 34-13. General Electric, Application Note 90. 16, p. 27.

- Fig. 34-14. National Semiconductor Corp., CMOS Databook, 1981, p. 8-45.*  
*Fig. 34-15. General Electric, Application Note 90-25.*  
*Fig. 34-16. Motorola, Circuit Applications for the Transistor (AN-466), p. 11.*  
*Fig. 34-17. Siliconix, MOSpower Applications Handbook, p. 6-181.*  
*Fig. 34-18. Popular Electronics, 3/75, p. 78.*

## Chapter 35

- Fig. 35-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN5-6.*  
*Fig. 35-2. Linear Technology Corp., Linear Databook, 1986, p. 2-82.*

## Chapter 36

- Fig. 36-1. Courtesy, William Sheets.*  
*Fig. 36-2. Electronics Today International, 6/76, p. 43.*  
*Fig. 36-3. Radio-Electronics, 4/87, p. 48.*  
*Fig. 36-4. Radio-Electronics, 2/84, p. 97.*  
*Fig. 36-5. Hands-On Electronics, Sep/Oct 1986, p. 24.*  
*Fig. 36-6. Electronic Engineering, 9/86, p. 37.*  
*Fig. 36-7. R-E Experimenters Handbook, p. 162.*  
*Fig. 36-8. Linear Technology Corp., Linear Databook, 1986, p. 2-96.*

## Chapter 37

- Fig. 37-1. Electronic Design, 3/75, p. 68.*  
*Fig. 37-2. EXAR, Telecommunications Databook, 1986, p. 11-38.*

## Chapter 38

- Fig. 38-1. Electronic Design, 8/73, p. 86.*  
*Fig. 38-2. Electronic Design, 12/78, p. 98.*  
*Fig. 38-3. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-53.*  
*Fig. 38-4. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-59.*

## Chapter 39

- Fig. 39-1. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S5-143.*

## Chapter 40

- Fig. 40-1. Electronic Design, 6/79, p. 122.*  
*Fig. 40-2. Electronic Engineering, 9/84, p. 37.*  
*Fig. 40-3. NASA Tech Briefs, 6/87, p. 26.*  
*Fig. 40-4. Electronics Today International, 6/80, p. 68.*  
*Fig. 40-5. Electronic Engineering, 9/87, p. 27.*  
*Fig. 40-6. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 7-25.*  
*Fig. 40-7. Radio-Electronics, 5/70, p. 33.*  
*Fig. 40-8. Linear Technology Corp., Linear Databook, 1986, p. 5-78.*  
*Fig. 40-9. Linear Technology Corp., Linear Databook, 1986, p. 8-40.*  
*Fig. 40-10. Electronic Engineering, 2/79, p. 23.*  
*Fig. 40-11. Electronic Engineering, 7/86, p. 30.*  
*Fig. 40-12. Motorola, Application Note AN-294, p. 6.*  
*Fig. 40-13. Motorola, Linear Integrated Circuits, p. 3-139.*  
*Fig. 40-14. Hands-On Electronics, Winter 1985, p. 60.*  
*Fig. 40-15. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 7-16.*  
*Fig. 40-16. Signetics, Analog Data Manual, 1982, p. 3-39.*  
*Fig. 40-17. General Electric/RCA, BiMOS Operational Amplifier Circuit Ideas, 1987, p. 10.*  
*Fig. 40-18. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-20.*  
*Fig. 40-19. National Semiconductor, Linear Brief 23.*

## Chapter 41

- Fig. 41-1. Tab Books, Inc., 101 Sound, Light, and Power IC Projects.*  
*Fig. 41-2. Courtesy, William Sheets.*

## Chapter 42

- Fig. 42-1. Courtesy, William Sheets.*  
*Fig. 42-2. Hands-On Electronics, Sep/Oct 1986, p. 85.*  
*Fig. 42-3. Courtesy, William Sheets.*

## **Chapter 43**

*Fig. 43-1. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-8.*

*Fig. 43-2. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-10.*

## **Chapter 44**

*Fig. 44-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-7.*

## **Chapter 45**

*Fig. 45-1. Linear Technology Corp., Linear Databook Supplement, 1988, p. S2-34.*

*Fig. 45-2. Hands-On Electronics, Jul/Aug 1986, p. 86.*

*Fig. 45-3. Signetics, Linear Data Manual Vol. 3: Video, p. 5-15.*

*Fig. 45-4. Tab Books, Inc. Build Your Own Laser, Phaser, Ion Ray Gun, 1983, p. 29.*

*Fig. 45-5. Hands-On Electronics, Jul/Aug 1986, p. 86.*

*Fig. 45-6. Electronic Engineering, 8/78, p. 24.*

## **Chapter 46**

*Fig. 46-1. Hands-On Electronics, 12/86, p. 42.*

*Fig. 46-2. Linear Technology Corp., Linear Databook, 1986, p. 2-82.*

*Fig. 46-3. Electronic Engineering, 9/84, p. 33.*

*Fig. 46-4. Texas Instruments, Linear and Interface Circuits Applications Vol. 1, 1985, p. 3-18.*

*Fig. 46-5. Linear Technology Corp., Linear Databook, 1986, p. 2-83.*

## **Chapter 47**

*Fig. 47-1. Electronic Engineering, 7/86, p. 30.*

*Fig. 47-2. Signetics, Analog Data Manual, 1982, p. 3-73.*

*Fig. 47-3. National Semiconductor Corp., Data Conversion/Acquisition Databook, 1980, p. 3-30.*

## **Chapter 48**

*Fig. 48-1. Hands-On Electronics, 5/87, p. 95.*

*Fig. 48-2. Electronic Design 16, 8/76, p. 76.*

## **Chapter 49**

*Fig. 49-1. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-50.*

*Fig. 49-2. Motorola, TMOS Power FET Design Ideas, 1985, p. 20.*

*Fig. 49-3. Motorola, TMOS Power FET Design Ideas, 1985, p. 21.*

*Fig. 49-4. R-E Experimenters Handbook, p. 156.*

*Fig. 49-5. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-48.*

*Fig. 49-6. Motorola, Thyristor Device Data, Series A, 1985, 1-6-55.*

*Fig. 49-7. Electronic Engineering, 9/84, p. 38.*

*Fig. 49-8. Tab Books, Inc., 101 Sound, Light, and Power IC Projects.*

*Fig. 49-9. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-60.*

*Fig. 49-10. General Electric, Application Note 200.35, p. 17.*

## **Chapter 50**

*Fig. 50-1. Tab Books, Inc., Build Your Own Laser, Phasor, Ion Ray Gun, 1983, p. 104.*

*Fig. 50-2. Electronic Engineering, 12/84, p. 34.*

## **Chapter 51**

*Fig. 51-1. Hands-On Electronics, Sep/Oct 1986, p. 26.*

*Fig. 51-2. General Electric, Optoelectronics, Third Edition, p. 107.*

*Fig. 51-3. Courtesy, William Sheets.*

*Fig. 51-4. Courtesy, William Sheets.*

*Fig. 51-5. Electronic Engineering, 12/75, p. 15.*

*Fig. 51-6. Hands-On Electronics, 4/87, p. 94.*

*Fig. 51-7. Hands-On Electronics, 2/87, p. 87.*

*Fig. 51-8. Hands-On Electronics, 10/87, p. 92.*

*Fig. 51-9. Linear Technology Corp., Linear Databook, 1986, p. 2-83.*

*Fig. 51-10. Radio-Electronics, 11/86, p. 38.*

*Fig. 51-11. General Electric, Application Note 200.35, p. 15.*

*Fig. 51-12. Intersil, Component Data Catalog, 1987, p. 7-44.*

*Fig. 51-13. Radio Electronics, 3/86, p. 32.*

*Fig. 51-14. Electronic Design, 11/82, p. 172.*

*Fig. 51-15. Electronic Design, 6/76, p. 120.*

*Fig. 51-16. Linear Technology Corp., Linear Application Handbook, 1987, p. AN5-3.*

## **Chapter 52**

*Fig. 52-1. Siliconix, Integrated Circuit Data Book, 3/85, p. 10-85.*

- Fig. 52-2. Siliconix, *Integrated Circuit Data Book*, 3/85, p. 10-79.
- Fig. 52-3. Siliconix, *Integrated Circuit Data Book*, 3/85, p. 2-144.
- Fig. 52-4. Signetics, 1987 *Linear Data Manual*, Vol. 2: *Industrial*, 10/86, p. 4-261.
- Fig. 52-5. Siliconix, *Integrated Circuit Data Book*, 3/85, p. 2-103.

## **Chapter 53**

- Fig. 53-1. Signetics, 1987 *Linear Data Manual*, Vol. 2: *Industrial*, 2/87, p. 5-350.
- Fig. 53-2. Linear Technology Corp., *Linear Application Handbook*, 1987, p. AN3-9.

## **Chapter 54**

- Fig. 54-1. *Hands-On Electronics*, May/Jun 1986, p. 63.
- Fig. 54-2. *Electronic Design*, 10/73, p. 114.
- Fig. 54-3. *Electronic Engineering*, 7/85, p. 44.
- Fig. 54-4. *Electronics Today International*, 3/80, p. 25.
- Fig. 54-5. *Popular Electronics*, 1/82, p. 76.
- Fig. 54-6. *Electronic Engineering*, 6/87, p. 28.
- Fig. 54-7. *Popular Electronics*, 8/69, p. 71.
- Fig. 54-8. *Electronics Today International*, 1/76, p. 52.
- Fig. 54-9. *Electronic Engineering*, 9/78, p. 20.

## **Chapter 55**

- Fig. 55-1. *Electronic Engineering*, 1/85, p. 39.
- Fig. 55-2. Intersil, *Component Data Catalog*, 1987, p. 7-44.

## **Chapter 56**

- Fig. 56-1. Courtesy, William Sheets.
- Fig. 56-2. Courtesy, William Sheets.

## **Chapter 57**

- Fig. 57-1. *Popular Electronics*, 6/73.
- Fig. 57-2. Courtesy, William Sheets.
- Fig. 57-3. Courtesy, William Sheets.
- Fig. 57-4. Courtesy, William Sheets.

## **Chapter 58**

- Fig. 58-1. Unitrode Corp., 10/86, p. 332.
- Fig. 58-2. Unitrode Corp., 10/86, p. 332.
- Fig. 58-3. Radio Electronics, 8/82, p. 36.
- Fig. 58-4. *Hands-On Electronics*, Winter 1985, p. 93.
- Fig. 58-5. *Hands-On Electronics*, 9/87, p. 71.

- Fig. 58-6. *Electronic Engineering*, 10/77, p. 23.

Fig. 58-7. *Electronic Design*, 11/8/69, p. 109.

Fig. 58-8. *Radio-Electronics*, 11/82, p. 79.

Fig. 58-9. National Semiconductor Corp., *Transistor Databook*, 1982, p. 11-34.

Fig. 58-10. National Semiconductor Corp., *Data Conversion/Acquisition Databook*, 1980, p. 2-5.

Fig. 58-11. Linear Technology Corp., *Linear Databook*, 1986, p. 8-42.

Fig. 58-12. Signetics, *Linear Data Manual Vol. 3: Video*, p. 11-120.

Fig. 58-13. General Electric, *Application Note 90-16*, p. 28.

Fig. 58-14. RCA, *Digital Integrated Circuits Application Note ICAN-6346*, p. 5.

Fig. 58-15. Linear Technology Corp., *Linear Databook*, 1986, p. 5-15.

Fig. 58-16. General Electric, *SCR Manual, Sixth Edition*, 1979, p. 204.

## **Chapter 59**

Fig. 59-1. Motorola, *TMOS Power FET Design Ideas*, 1985, p. 45.

Fig. 59-2. Courtesy, William Sheets.

Fig. 59-3. Signetics, *Linear Data Manual, Vol. 3: Video*, p. 11-3.

Fig. 59-4. *Radio-Electronics*, 8/77, p. 33.

Fig. 59-5. *Electronic Design*, 3/77, p. 76.

## **Chapter 60**

Fig. 60-1. *Electronic Engineering*, 5/84, p. 43.

Fig. 60-2. General Electric, *Optoelectronics, Third Edition*, p. 114.

Fig. 60-3. Motorola, *TMOS Power FET Design Ideas*, 1985, p. 32.

Fig. 60-4. Siliconix, *MOSpower Applications Handbook*, p. 6-186.

Fig. 60-5. *Electronic Engineering*, 7/86, p. 34.

Fig. 60-6. *Electronic Engineering*, 4/85, p. 47.

Fig. 60-7. Motorola, *Thyristor Device Data, Series A*, 1985, p. 1-6-8.

Fig. 60-8. Motorola, *TMOS Power FET Design Ideas*, 1985, p. 31.

Fig. 60-9. Sprague Electric Co., *Integrated Circuits Databook WR504*, p. 4-159.

Fig. 60-10. General Electric, *Application Note 200-35*, p. 18.

Fig. 60-11. Sprague Electric Co., *Integrated Circuits Databook WR504*, p. 4-160.

- Fig. 60-12. Motorola, TMOS Power FET Design Ideas, 1985, p. 55.*
- Fig. 60-13. Motorola, TMOS Power FET Design Ideas, 1985, p. 54.*
- Fig. 60-14. Motorola, TMOS Power FET Design Ideas, 1985, p. 51.*
- Fig. 60-15. Electronic Engineering, 2/84, p. 23.*
- Fig. 60-16. National Semiconductor Corp., Linear Application Databook, p. 1066.*
- Fig. 60-17. General Electric, Optoelectronics, Third Edition, p. 113.*

## Chapter 61

- Fig. 61-1. Fairchild Corp., Linear Databook, 1982, p. 4-72.*
- Fig. 61-2. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-14.*

## Chapter 62

- Fig. 62-1. 73 Magazine, 12/76, p. 170.*
- Fig. 62-2. Electronics International Today, 1/76, p. 44.*
- Fig. 62-3. Signetics Analog Data Manual, 1983, p. 10-93.*
- Fig. 62-4. Electronics Today International, 9/75, p. 66.*
- Fig. 62-5. CQ, 5/76, p. 26.*

## Chapter 63

- Fig. 63-1. National Semiconductor Corp., Linear Applications Databook, p. 1096.*
- Fig. 63-2. EXAR, Telecommunications Databook, 1986, p. 7-24.*
- Fig. 63-3. EXAR, Telecommunications Databook, 1986, p. 7-24.*
- Fig. 63-4. Electronic Engineering, 12/84, p. 33.*
- Fig. 63-5. Electronic Engineering, 11/85, p. 31.*
- Fig. 63-6. Courtesy, William Sheets.*
- Fig. 63-7. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 2-11.*
- Fig. 63-8. Courtesy, William Sheets.*
- Fig. 63-9. Courtesy, William Sheets.*
- Fig. 63-10. Courtesy, William Sheets.*

## Chapter 64

- Fig. 64-1. Electronic Engineering, 6/83, p. 31.*
- Fig. 64-2. Electronic Design 15, 7/75, p. 68.*

## Chapter 65

- Fig. 65-1. General Electric, Optoelectronics, Third Edition, p. 135.*
- Fig. 65-2. NASA, Tech Briefs, Summer 1984, p. 446.*
- Fig. 65-3. General Electric, Optoelectronics, Third Edition, p. 140.*
- Fig. 65-4. General Electric, Optoelectronics, Third Edition, p. 121.*
- Fig. 65-5. General Electric, Optoelectronics, Third Edition, p. 120.*
- Fig. 65-6. General Electric, Optoelectronics, Third Edition, p. 139.*
- Fig. 65-7. General Electric, Optoelectronics, Third Edition, p. 120.*
- Fig. 65-8. General Electric, Optoelectronics, Third Edition, p. 134.*
- Fig. 65-9. General Electric, Optoelectronics, Third Edition, p. 112.*
- Fig. 65-10. National Semiconductor Corp., Data Conversion/Acquisition Databook, 1980, p. 13-46.*
- Fig. 65-11. General Electric, Optoelectronics, Third Edition, p. 133.*
- Fig. 65-12. Courtesy, William Sheets.*
- Fig. 65-13. General Electric, Optoelectronics, Third Edition, p. 117.*
- Fig. 65-14. Electronic Engineering, 8/86, p. 36.*
- Fig. 65-15. General Electric, Optoelectronics, Third Edition, p. 118.*

## Chapter 66

- Fig. 66-1. 73 For Radio Amateurs, 11/85, p. 32.*
- Fig. 66-2. Radio-Electronics, 5/70, p. 35.*
- Fig. 66-3. Electronics Today International, 7/78, p. 16.*
- Fig. 66-4. Electronics Today International, 12/78, p. 15.*
- Fig. 66-5. General Electric, Semiconductor Data Handbook, Third Edition, p. 513.*
- Fig. 66-6. Electronic Design, 11/29/84, p. 281.*
- Fig. 66-7. Unitrode Corp., Databook 1986, p. 51.*
- Fig. 66-8. Electronic Engineering, 5/77, p. 27.*
- Fig. 66-9. National Semiconductor Corp., Transistor Databook, 1982, p. 7-19.*
- Fig. 66-10. Courtesy, William Sheets.*
- Fig. 66-11. Electronic Design, 10/65.*

*Fig. 66-12. Hands-On Electronics, Summer 1984, p. 43.*

*Fig. 66-13. Signetics, Analog Data Manual, 1982, p. 8-10.*

## **Chapter 67**

*Fig. 67-1. Electronic Design, 5/79, p. 102.*

*Fig. 67-2. Radio-Electronics, 7/70, p. 36.*

*Fig. 67-3. Courtesy, William Sheets.*

## **Chapter 68**

*Fig. 68-1. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-18.*

*Fig. 68-2. Popular Electronics, 3/79, p. 78.*

## **Chapter 69**

*Fig. 69-1. Electronic Engineering, 2/86, p. 38.*

*Fig. 69-2. Courtesy, William Sheets.*

*Fig. 69-3. Electronic Engineering, 4/77, p. 13.*

*Fig. 69-4. Electronic Engineering, 7/85, p. 34.*

*Fig. 69-5. Electronic Design, 3/77, p. 106.*

*Fig. 69-6. Electric Engineering, 1/87, p. 25.*

## **Chapter 70**

*Fig. 70-1. Hands-On Electronics, 10/87, p. 96.*

*Fig. 70-2. Hands-On Electronics, Spring 1985, p. 82.*

*Fig. 70-3. General Electric Project G4, p. 131.*

*Fig. 70-4. Radio Electronics, 12/84, p. 77.*

*Fig. 70-5. Electronics Today International, 6/75, p. 42.*

*Fig. 70-6. Electronics Today International, 9/82, p. 42.*

## **Chapter 71**

*Fig. 71-1. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/86, p. 7-251.*

*Fig. 71-2. National Semiconductor Corp., Linear Applications Databook, p. 1065.*

*Fig. 71-3. Siliconix, MOSpower Applications Handbook, p. 6-101.*

*Fig. 71-4. Hands-On Electronics, 5/87, p. 96.*

*Fig. 71-5. Hands-On Electronics, Spring 1985, p. 36.*

*Fig. 71-6. Hands-On Electronics, Summer 1984, p. 74.*

*Fig. 71-7. Radio-Electronics, 3/86, p. 59.*

*Fig. 71-8. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 4-20.*

*Fig. 71-9. National Semiconductor Corp., Linear Databook, 1982, p. 3-187.*

*Fig. 71-10. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 11/86, p. 4-135.*

## **Chapter 72**

*Fig. 72-1. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 6-35.*

*Fig. 72-2. Motorola, TMOS Power FET Design Ideas, 1985, p. 43.*

*Fig. 72-3. Electronic Engineering, 12/84, p. 41.*

*Fig. 72-4. NASA, Tech Briefs, 9/87, p. 21.*

*Fig. 72-5. Motorola, TMOS Power FET Design Ideas, 1985, p. 37.*

*Fig. 72-6. Siliconix, MOSpower Applications Handbook, p. 6-51.*

*Fig. 72-7. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 24.*

*Fig. 72-8. Courtesy, William Sheets.*

*Fig. 72-9. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 24.*

*Fig. 72-10. Radio-Electronics, 6/86, p. 52.*

*Fig. 72-11. Siliconix, MOSpower Applications Handbook, p. 6-177.*

*Fig. 72-12. Siliconix, MOSpower Applications Handbook, p. 6-59.*

*Fig. 72-13. Linear Technology Corp., Linear Databook, 1986, p. 3-23.*

*Fig. 72-14. Electronic Engineering, 10/84, p. 38.*

*Fig. 72-15. NASA Tech Briefs, Summer 1985, p. 32.*

*Fig. 72-16. Electronic Engineering, 1/87, p. 22.*

*Fig. 72-17. Motorola, TMOS Power FET Design Ideas, 1985, p. 42.*

*Fig. 72-18. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-55.*

*Fig. 72-19. 73 Magazine, 12/70, p. 170.*

*Fig. 72-20. Signetics, Analog Data Manual, 1983, p. 12-27.*

*Fig. 72-21. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 2/87, p. 8-223.*

*Fig. 72-22. Electronic Engineering, 1/85, p. 45.*

*Fig. 72-23. Motorola, Linear Integrated Circuits, p. 3-138.*

- Fig. 72-24. Electronic Design, 11/29/84, p. 282.*
- Fig. 72-25. Electronics Today International, 1/70, p. 45.*
- Fig. 72-26. Linear Technology, 1986 Linear Databook, p. 3-22.*
- Chapter 73**
- Fig. 73-1. Electronic Engineering, 10/76, p. 17.*
- Fig. 73-2. Electronic Engineering, 7/77, p. 26.*
- Fig. 73-3. Popular Electronics, 5/74, p. 24.*
- Fig. 73-4. Courtesy, William Sheets.*
- Chapter 74**
- Fig. 74-1. NASA, Tech Briefs, Winter 1985, p. 52.*
- Fig. 74-2. Courtesy, William Sheets.*
- Fig. 74-3. Electronic Engineering, 3/86, p. 34.*
- Fig. 74-4. Courtesy, William Sheets.*
- Fig. 74-5. Courtesy, William Sheets.*
- Chapter 75**
- Fig. 75-1. Electronic Design 25, 1275, p. 90.*
- Fig. 75-2. Courtesy, William Sheets.*
- Fig. 75-3. Electronics Today International, 9/75, p. 66.*
- Fig. 75-4. Electronic Engineering, 1/85, p. 41.*
- Fig. 75-5. Hands-On Electronics, Fall 1984, p. 66.*
- Fig. 75-6. Radio-Electronics, 3/77, p. 76.*
- Chapter 76**
- Fig. 76-1. Hands-On Electronics, 11/86, p. 92.*
- Fig. 76-2. Popular Electronics, 11/77, p. 62.*
- Chapter 77**
- Fig. 77-1. Electronic Engineering, 9/86, p. 38.*
- Fig. 77-2. RCA, Design Guide for Fire Detection Systems, Publication 2M1189, p. 27.*
- Fig. 77-3. Electronic Engineering, 9/86, p. 34.*
- Chapter 78**
- Fig. 78-1. Electronic Engineering, 5/76, p. 17.*
- Fig. 78-2. Electronic Design, 4/74, p. 114.*
- Fig. 78-3. Electronic Engineering, 10/86, p. 41.*
- Chapter 79**
- Fig. 79-1. Electronic Engineering, 12/75, p. 15.*
- Fig. 79-2. Radio-Electronics, Experimenters Handbook, p. 122.*
- Chapter 80**
- Fig. 80-1. Signetics, 1987 Linear Data Manual, Vol. 1: Communications, 2/87, p. 4-310.*
- Fig. 80-2. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-52.*
- Chapter 81**
- Fig. 81-1. Signetics, 1987 Linear Data Manual, Vol. 1: Communications, 11/86, p. 7-14.*
- Fig. 81-2. Hands-On Electronics, 3/87, p. 28.*
- Fig. 81-3. Hands-On Electronics, 12/86, p. 22.*
- Chapter 82**
- Fig. 82-1. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 11.*
- Fig. 82-2. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 11/86, p. 4-135.*
- Chapter 83**
- Fig. 83-1. Electronic Design, 9/69, p. 106.*
- Fig. 83-2. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-61.*
- Fig. 83-3. QST, 7/87, p. 32.*
- Chapter 84**
- Fig. 84-1. Electronic Engineering, 4/86, p. 34.*
- Fig. 84-2. Electronic Engineering, 7/85, p. 44.*
- Fig. 84-3. Electronic Engineering, 11/86, p. 34.*
- Fig. 84-4. NASA, Tech Briefs, 1/88, p. 18.*
- Chapter 85**
- Fig. 85-1. Motorola, RF Data Manual, 1986, p. 6-141.*
- Fig. 85-2. Motorola, RF Data Manual, 1986, p. 6-240.*
- Fig. 85-3. QST, 7/87, p. 31.*
- Fig. 85-4. QST, 5-86, p. 23.*
- Fig. 85-5. Motorola, RF Data Manual, 1986, p. 6-181.*
- Fig. 85-6. Ham Radio, 7/86, p. 50.*
- Fig. 85-7. Radio Electronics, 3/87, p. 42.*
- Fig. 85-8. NASA, Tech Briefs, Spring 1984, p. 322.*
- Fig. 85-9. Motorola, RF Data Manual, 1986, p. 6-232.*

## **Chapter 86**

*Fig. 86-1. QST, 12/85, p. 39.*

## **Chapter 87**

- Fig. 87-1. General Electric/RCA, BiMOS Operational Amplifiers circuit Ideas, 1987, p. 14.*
- Fig. 87-2. Intersil, Component Data Catalog, 1987, p. 7-5.*
- Fig. 87-3. Linear Technology Corp., Linear Databook, 1986, p. 2-113.*
- Fig. 87-4. Electronics Today International, 3/78, p. 51.*
- Fig. 87-5. National Semiconductor Corp., Hybrid Products Databook, 1982, p. 17-149.*
- Fig. 87-6. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-58.*

## **Chapter 88**

- Fig. 88-1. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 8.*
- Fig. 88-2. Linear Technology Corp., Linear Databook, 1986, p. 2-113.*
- Fig. 88-3. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-15, 3-16.*
- Fig. 88-4. QST, 4/87, p. 48.*
- Fig. 88-5. Electronic Engineering, 5/85, p. 38.*
- Fig. 88-6. Electronic Design, 6/81, p. 250.*
- Fig. 88-7. Ham Radio, 1/87, p. 97.*
- Fig. 88-8. Electronic Engineering, 2/76, p. 17.*
- Fig. 88-9. Electronic Design, 2/73, p. 82.*
- Fig. 88-10. Radio-Electronics, 2/71, p. 37.*
- Fig. 88-11. Ham Radio, 6/82, p. 33.*

## **Chapter 89**

- Fig. 89-1. Popular Electronics, 12/74, p. 68.*
- Fig. 89-2. Electronics Today International, 1/77, p. 49.*
- Fig. 89-3. Electronics Today International, 1/77, p. 49.*
- Fig. 89-4. Popular Electronics, 8/74, p. 98.*
- Fig. 89-5. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 28.*
- Fig. 89-6. Electronics Today International, 11/76, p. 45.*
- Fig. 89-7. Electronics Today International, 2/75, p. 66.*

*Fig. 89-8. Electronics Today International, 1/77, p. 85.*

*Fig. 89-9. Electronics Today International, 6/75, p. 63.*

*Fig. 89-10. Electronics Today International, 1/77, p. 49.*

*Fig. 89-11. Courtesy, William Sheets.*

*Fig. 89-12. Electronics Today International, 11/80, p. 43.*

*Fig. 89-13. Radio-Electronics, 2/75, p. 42.*

*Fig. 89-14. Courtesy, William Sheets.*

## **Chapter 90**

- Fig. 90-1. Courtesy, William Sheets.*
- Fig. 90-2. Radio-Electronics, 12/83, p. 38.*
- Fig. 90-3. Hands-On Electronics, 8/87, p. 77.*
- Fig. 90-4. Electronics today International, 6/79, p. 27.*
- Fig. 90-5. Courtesy, William Sheets.*

## **Chapter 91**

- Fig. 91-1. Hands-On Electronics, 6/87, p. 40.*
- Fig. 91-2. Electronics Today International, 8/77, p. 25.*
- Fig. 91-3. Electronics Today International, 11/80.*
- Fig. 91-4. Texas Instruments, Complex Sound Generator, Bulletin No. DL-12612, p. 13.*
- Fig. 91-5. Electronics Today International, 4/82, p. 34.*
- Fig. 91-6. Electronics Today International, 2/75, p. 66.*
- Fig. 91-7. Hands-On Electronics, 12/86, p. 42.*
- Fig. 91-8. Courtesy, William Sheets.*
- Fig. 91-9. Courtesy, William Sheets.*
- Fig. 91-10. Texas Instruments, complex Sound Generator, Bulletin No. DL-S 12612, p. 11.*
- Fig. 91-11. Courtesy, William Sheets.*

## **Chapter 92**

- Fig. 92-1. Electronic Engineering, 3/82, p. 29.*
- Fig. 92-2. Electronic Engineering, 10/78, p. 17.*
- Fig. 92-3. EXAR, Telecommunications Databook, 1986, p. 9-24.*
- Fig. 92-4. Electronic Design, 5/79, p. 100.*
- Fig. 92-5. Siliconix, Integrated Circuits Data Book, 3/85, p. 5-17.*
- Fig. 92-6. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 7.*

- Fig. 92-7. *Electronic Design*, 6/69, p. 126.  
 Fig. 92-8. *Electronic Engineering*, 8/84, p. 27.  
 Fig. 92-9. *Electronic Engineering*, 12/85, p. 35.  
 Fig. 92-10. *Electronic Engineering*, 8/84, p. 29.

## Chapter 93

- Fig. 93-1. *General Electric/RCA, Operational Amplifiers Circuit Ideas*, 1987, p. 10.  
 Fig. 93-2. *Linear Technology Corp., Linear Databook*, 1986, p. 8-42.

## Chapter 94

- Fig. 94-1. *Tab Books, Inc. 303 Dynamic Electronic Circuits*, p. 169.  
 Fig. 94-2. *Electronics Today International*, 12/77, p. 86.

## Chapter 95

- Fig. 95-1. *Electronics Today International*, 10/78, p. 46.  
 Fig. 95-2. *Hands-On Electronics*, Fall 1984, p. 65.  
 Fig. 95-3. Courtesy, William Sheets.

## Chapter 96

- Fig. 96-1. *Electronic Engineering*, 6/86, p. 35.  
 Fig. 96-2. *General Electric, SCR Manual, Sixth Edition*, 1979, p. 200.

## Chapter 97

- Fig. 97-1. *Electronic Engineering*, 9/87, p. 32.  
 Fig. 97-2. *Intersil, Component Data Catalog*, 1987, p. 14-67.

## Chapter 98

- Fig. 98-1. *Electronic Engineering*, 2/87, p. 40.  
 Fig. 98-2. *Tab Books, Inc. The Giant Book of Easy-To-Build Electronic Projects*, 1982, p. 1.  
 Fig. 98-3. *Radio-Electronics*, 2/85, p. 90.  
 Fig. 98-4. *EXAR, Telecommunications Databook*, 1986, p. 11-38.  
 Fig. 98-5. *Tab Books, Inc. build Your Own Laser, Phaser, Ion gun*, 1983, p. 305.  
 Fig. 98-6. *Electronic Design*, 12/78, p. 95.  
 Fig. 98-7. *Radio-Electronics*, 11/79, p. 53.  
 Fig. 98-8. *Electronic Design*, 10/76, p. 194.  
 Fig. 98-9. *Hands-On Electronics*, 12/86, p. 22.

- Fig. 98-10. *Electronics Engineering*, 1/79, p. 17.

- Fig. 98-11. *Radio-Electronics*, 12/78, p. 67.  
 Fig. 98-12. *Radio-Electronics*, 11/77, p. 45.  
 Fig. 98-13. *Hands-On Electronics*, Summer 1985, p. 74.

- Fig. 98-14. *Hands-On Electronics*, Sep/Oct 1986, p. 88.

- Fig. 98-15. *Hands-On Electronics*, Sep/Oct 1986, p. 105.

- Fig. 98-16. *Hands-On Electronics*, Summer 1984, p. 39.

- Fig. 98-17. *EXAR, Telecommunications Databook*, 1986, p. 4-19.

- Fig. 98-18. *EXAR, Telecommunications Databook*, 1986, p. 5-14.

- Fig. 98-19. *EXAR, Telecommunications Databook*, 1986, p. 4-15.

- Fig. 98-20. *Signetics, 1987 Linear Data Manual*, Vol. 1: *Communications*, 12/2/86, p. 6-50.

## Chapter 99

- Fig. 99-1. *NASA, Tech Briefs*, 12/87, p. 28.  
 Fig. 99-2. *Signetics, 1987 Linear Data Manual*, Vol. 2: *Industrial*, 2/87, p. 7-67.  
 Fig. 99-3. *Electronic Design*, 8/75, p. 82.  
 Fig. 99-4. *Linear Technology Corp., Linear Application Handbook*, 1987, p. AN3-6.  
 Fig. 99-5. *General Electric, Optoelectronics, Third Edition*, p. 153.  
 Fig. 99-6. *General Electric, Application Note 200-85*, p. 18.  
 Fig. 99-7. *Electronic Design*, 8/82, p. 217.  
 Fig. 99-8. *Electronic Design*, 8/83, p. 230.  
 Fig. 99-9. Courtesy, William Sheets.

## Chapter 100

- Fig. 100-1. *General Electric, SCR Manual, Sixth Edition*, 1979, p. 222.  
 Fig. 100-2. *Electronic Engineering*, 9/85, p. 30.  
 Fig. 100-3. *National Semiconductor Corp., 1984 Linear Supplement Databook*, p. S1-41.  
 Fig. 100-4. *National Semiconductor Corp., 1984 Linear Supplement Databook*, p. S1-42.  
 Fig. 100-5. *Linear Technology Corp., Linear Databook*, 1986, p. 2-101.  
 Fig. 100-6. Courtesy, William Sheets.

## **Chapter 101**

*Fig. 101-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN7-2.*  
*Fig. 101-2. Electric Engineering, 7/84, p. 31.*

## **Chapter 102**

*Fig. 102-1. Hands-On Electronics, 11/86, p. 93.*  
*Fig. 102-2. Hands-On Electronics, 9/87, p. 32.*

## **Chapter 103**

*Fig. 103-1. Teledyne Semiconductor, Data & Design Manual, 1981, p. 7-17.*  
*Fig. 103-2. Linear Technology Corp., Application Note 9, p. 18.*  
*Fig. 103-3. Radio-Electronics, 9/82, p. 42.*  
*Fig. 103-4. Intersil, Component Data Catalog, 1987, p. 6-8.*  
*Fig. 103-5. Intersil, Component Data Catalog, 1987, p. 6-11.*  
*Fig. 103-6. Intersil, Component Data Catalog, 1987, p. 6-8.*

## **Chapter 104**

*Fig. 104-1. NASA, Tech Briefs, Spring 1985, p. 40.*  
*Fig. 104-2. NASA, Tech Briefs, Fall/Winter 1981, p. 319.*  
*Fig. 104-3. Popular Electronics, 12/82, p. 82.*

## **Chapter 105**

*Fig. 105-1. General Electric, Semiconductor Data Handbook, Third Edition, p. 513.*  
*Fig. 105-2. Motorola, Application Note AN294.*  
*Fig. 105-3. Electronic Design, 4/77, p. 120.*  
*Fig. 105-4. Motorola, Application Note AN294.*

## **Chapter 106**

*Fig. 106-1. NASA, Tech Briefs, Sep/Oct 1986, p. 36.*

*Fig. 106-2. Electronic Engineering, 9/77, p. 37.*

*Fig. 106-3. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-51.*

*Fig. 106-4. Motorola, Thyristor Device Data, Series A, 1985, p. 1-6-54.*

*Fig. 106-5. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 7-23.*

*Fig. 106-6. Intersil, Databook, 1987, p. 7-102.*

*Fig. 106-7. Intersil, Component Data Catalog, 1987, p. 14-67.*

*Fig. 106-8. General Electric, Application Note 90.16, p. 30.*

## **Chapter 107**

*Fig. 107-1. Electronics Today International, 11/80.*  
*Fig. 107-2. Signetics, 1987 Linear Data Manual, Vol. 2: Industrial, 2/87, p. 4-107.*  
*Fig. 107-3. Electronics Today International, 9/77, p. 55.*  
*Fig. 107-4. General Electric/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 21.*  
*Fig. 107-5. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 3-11.*  
*Fig. 107-6. National Semiconductor Corp., Transistor Databook, 1982, p. 11-35.*  
*Fig. 107-7. Electronics Today International, 6/82, p. 61.*

## **Chapter 108**

*Fig. 108-1. Hands-On Electronics, 9/87, p. 88.*  
*Fig. 108-2. Texas Instruments, Linear and Interface Circuits Applications, Vol. 1, 1985, p. 7-15.*  
*Fig. 108-3. Tab Books, Inc., The Giant book of Easy-To-Build Electronics Projects, 1982, p. 31.*

# Index

---

---

Numbers preceded by a "I," "II," "III," or "IV" are from *Encyclopedia of Electronic Circuits* Vol. I, II, III, or IV, respectively.

## A

absolute-value amplifier, I-31  
absolute-value circuit, I-37, IV-274  
absolute-value full wave rectifier, II-528  
absolute-value Norton amplifier, III-11  
ac bridge circuit, II-81  
ac flasher, III-196  
ac linear coupler, analog, II-412  
ac motor  
    control for, II-375  
    three-phase driver, II-383  
    two-phase driver, II-382  
ac sequential flasher, II-238  
ac switcher, high-voltage optically  
    coupled, III-408  
ac timer, .2 to 10 seconds, adjustable,  
    II-681  
ac-coupled amplifiers, dynamic, III-17  
ac/dc indicator, IV-214  
ac-to-dc converter, I-165  
    fixed power supplies, IV-395  
    full-wave, IV-120  
    high-impedance precision rectifier, I-  
        164  
acid rain monitor, II-245, III-361

acoustic-sound receiver/transmitter, IV-  
    311  
active antennas, III-1-2, IV-1-4  
    basic designs, IV-3  
    wideband rod, IV-4  
    with gain, IV-2  
active clamp-limiting amplifiers, III-15  
active crossover networks, I-172-173  
active filters (*see also* filter circuits)  
    band reject, II-401  
    bandpass, II-221, II-223, III-190  
    digitally tuned low power, II-218  
    five pole, I-279  
    high-pass, second-order, I-297  
    low-pass, digitally selected break  
        frequency, II-216  
    low-power, digitally selectable center  
        frequency, III-186  
    low-power, digitally tuned, I-279  
    programmable, III-185  
    RC, up to 150 kHz, I-294  
    state-variable, III-189  
    ten-band graphic equalizer using, II-  
        684  
three-amplifier, I-289  
tunable, I-294

universal, II-214  
variable-bandwidth bandpass, I-286  
active integrator, inverting buffer, II-  
    299  
adapters  
    dc transceiver, hand-held, III-461  
    program, second-audio, III-142  
traveller's shaver, I-495  
adder, III-327  
AGC, II-17  
AGC amplifiers  
    AGC system for CA3028 IF amplifier,  
        IV-458  
    rf, wideband adjustable, III-545  
    squelch control, III-33  
    wideband, III-15  
air conditioner, auto, smart clutch for,  
    III-46  
air flow detector, I-235, II-242, III-364  
air flow meter (*see* anemometer)  
air-pressure change detector, IV-144  
air-motion detector, III-364  
airplane propeller sound effect, II-592  
alarms (*see also* detectors; indicators;  
    monitors; sensors; sirens), III-3-9,  
    IV-84-87

- alarms (*cont.*)
- auto burglar, II-2, I-3, III-4, I-7, I-10, IV-53
  - auto burglar, CMOS low-current design, IV-56
  - auto burglar, horn as loudspeaker, IV-54
  - auto burglar, single-IC design, IV-55
  - auto burglar, single-IC, III-7
  - auto-arming automotive alarm, IV-50
  - automatic turn-off after 8-minute delay, automotive, IV-52
  - automatic turn-off with delay, IV-54
  - blown fuse, I-10
  - boat, I-9
  - burglar, III-8, III-9, IV-86
  - burglar, latching circuit, I-8, I-12
  - burglar, NC and NO switches, IV-87
  - burglar, NC switches, IV-87
  - burglar, one-chip, III-5
  - burglar, self-latching, IV-85
  - burglar, timed shutoff, IV-85
  - camera triggered, III-444
  - capacitive sensor, III-515
  - current monitor and, III-338
  - differential voltage or current, II-3
  - digital clock circuit with, III-84
  - door-ajar, II-284
  - door-ajar, Hall-effect circuit, III-256
  - doorbell, rain, I-443
  - fail-safe, semiconductor, III-6
  - field disturbance, II-507
  - flasher, bar display, I-252
  - flood, III-206, I-390, IV-188
  - freezer meltdown, I-13
  - headlights-on, III-52
  - high/low limit, I-151
  - home-security system, IV-87
  - ice formation, II-58
  - infrared wireless security system, IV-222-223
  - low-battery disconnect and, III-65
  - low-battery warning, III-59
  - low volts, II-493
  - mains-failure indicator, IV-216
  - motion-actuated car, I-9
  - motion-actuated motorcycle, I-9
  - multiple circuit for, II-2
  - one-chip, III-5
  - photoelectric, II-4, II-319
  - piezoelectric, I-12
  - power failure, III-511, I-581, I-582
  - printer-error, IV-106
  - proximity, II-506, III-517
  - pulsed-tone, I-11
  - purse-snatcher, capacitance operated, I-134
  - rain, I-442, I-443, IV-189
  - road ice, II-57
  - security, I-4
  - self-arming, I-2
  - shutoff, automatic, I-4
  - signal-reception, receivers, III-270
  - smoke, photoelectric, line-operated, I-596
  - smoke, SCR, III-251
  - solar powered, I-13
  - sonic defenders, IV-324
  - speed, I-95
  - Star Trek red alert, II-577
  - strobe flasher alarm, IV-180
  - tamperproof burglar, I-8
  - temperature, II-643
  - temperature, light, radiation sensitive, II-4
  - timer, II-674
  - trouble tone alert, II-3
  - varying-frequency warning, II-579
  - wailing, II-572
  - warbling, II-573
  - watchdog timer/alarm, IV-584
  - water-leakage, IV-190
  - water level, I-389
  - allophone generator, III-733
  - alternators
    - battery-alternator monitor, automotive, III-63  - AM demodulator, II-160
  - AM microphone, wireless, I-679
  - AM radio, I-544
  - AM radio
    - AM car-radio to short-wave radio converter, IV-500
    - broadcast-band signal generator, IV-302
    - envelope detector, IV-142
    - modulation monitor, IV-299
    - power amplifier for, I-77
    - receivers, III-529, IV-455
    - receivers, carrier-current, III-81
    - receivers, integrated, III-535  - AM/FM
    - clock radio, II-543, III-1
    - squelch circuit for, II-547, III-1  - amateur radio
    - linear amp, 2-30 MHz 140-W, III-260
    - receiver, III-534
    - signal-identifier, programmable, IV-326
    - transmitter, 80-M, III-675  - ambience amplifier, rear speaker, II-458
  - ammeter, I-201
    - nano, I-202
    - pico, II-154, I-202
    - pico, circuit for, II-157
    - pico, guarded input circuit, II-156
    - six decade range, II-153, II-156  - amplifiers, II-5-22, III-10-21
    - 1 watt/2.3 GHz, II-540
    - 2 to 6 W, with preamp, II-451
    - 25-watt, II-452
    - 30 MHz, I-567
    - 40 dB gain design, IV-36
    - 60 MHz, I-567
    - 135-175 MHz, I-564
    - absolute value, I-31
    - ac servo, bridge type, III-387
    - AGC, II-17
    - AGC, squelch control, III-33
    - AGC, wide-band, III-15
    - adjustable-gain, noninverting, I-91
    - ambience, rear speaker, II-458
    - amateur radio, linear, 2-30 MHz, 140W, I-555
    - AM radio power, I-77
    - attenuator, digitally controlled, I-53
    - audio (*see* audio amplifiers)
    - audio converter, two-wire to four-wire, II-14
    - audio limiter, low-distortion, II-15
    - audio power amplifiers, IV-28-33
    - audio signal amplifiers, IV-34-42
    - auto fade circuit for, II-42
    - automatic level control for, II-20
    - automotive audio amplifier, IV-66
    - balance, II-46
    - balance, loudness control, II-47, II-395
    - balancing circuit, inverting, I-33
    - bass tone control, stereo phonograph, I-670
    - bridge, I-74
    - bridge, 4W, I-79
    - bridge, 16 W, I-82
    - bridge, ac servo, I-458
    - bridge, audio power, I-81
    - bridge, high-impedance, I-353
    - bridge transducer, III-71, II-84, I-351
    - broadband, low-noise, I-562
    - broadband, PEP, 160W, I-556
    - broadband/linear, PEP, 80W, I-557
    - buffer, 10x, I-128
    - buffer, 100x, I-128
    - buffer, ac, single-supply, I-126
    - buffer, battery-powered, standard cell, I-351
    - buffer, rf amplifiers with modulator, IV-490
    - buffer, sinewave output, I-126
    - buffer, unity-gain, stable design, II-6 cascade, III-13
    - cascade, 80 MHz, I-567
    - cascode, rf amplifiers, IV-488
    - CD4049 audio signal amplifiers, IV-40
    - chopper, ± 15V, III-12
    - chopper channel, I-350

chopper stabilized, II-7  
 clamp-limiting, active, III-15  
 color video, I-34, III-724  
 common-source, 450 MHz, I-568  
 common-source, low power, II-84  
 complementary-symmetry, I-78  
 composite, II-8, III-13  
 compressor/amplifier, low-distortion, IV-24  
 constant-bandwidth, III-21  
 current-shunt, III-21  
 current collector head, II-11, II-295  
 current-to-voltage, high-speed, I-35  
 dc servo, I-457  
 dc-stabilized, fast action, III-18  
 dc-to-video log, I-38  
 detector, MC1330/MC1352, television IF, I-688  
 differential, III-14, I-38  
 differential, high-impedance, I-27, I-354  
 differential, high-input high-impedance, II-19  
 differential, instrumentation, I-347, III-283  
 differential, instrumentation, biomedical, III-282  
 differential, programmable gain, III-507  
 differential, two op amp bridge type, II-83  
 dynamic, ac-coupled, III-17  
 electrometer, overload protected, II-155  
 FET input, II-7  
 flat response, I-92, III-673  
 forward-current booster, III-17  
 four-quadrant photo-conductive detector, I-359  
 gain, 10-dB, III-543  
 gain-controlled, III-34  
 gate, I-36  
 guitars, matching audio signal amplifiers, IV-38  
 hi-fi compander, II-12  
 hi-fi expander, II-13  
 high-frequency, III-259-265  
 high-impedance/high gain/high-frequency, I-41  
 high-impedance/low capacitance, I-691  
 IF (*see* IF amplifiers)  
 input/output buffer for analog multiplexers, III-11  
 instrumentation, I-346, I-348, I-349, I-352, I-354, III-278-284, IV-229-234  
 instrumentation, differential, high-gain, I-353  
 instrumentation, high-impedance, low-drift, I-355  
 instrumentation, high-speed, I-354  
 instrumentation, low-signal/high-impedance, I-350  
 instrumentation, precision FET input, I-355  
 instrumentation, triple op-amp design, I-347  
 instrumentation, variable gain, differential input, I-349  
 instrumentation, very high-impedance, I-354  
 inverting, I-42, II-41, III-14  
 inverting, ac, high-gain, I-92  
 inverting, gain of 2, lag-lead compensation, UHF, I-566  
 inverting, power, I-79  
 inverting, unity gain, I-80  
 isolation, capacitive load, I-34  
 isolation, level-shifting, I-348  
 isolation, medical telemetry, I-352  
 isolation, rf, II-547  
 JFET bipolar cascade video, I-692  
 line amplifier, universal design, IV-39  
 linear, CMOS inverter in, II-11  
 line-operated, III-37  
 line-type, duplex, telephone, III-616  
 load line protected, 75W audio, I-73  
 logarithmic, II-8  
 logic (*see* logic amplifier)  
 log ratio, I-42  
 loudness control, II-46  
 low-noise design, IV-37  
 low-level video detector circuit, I-687  
 medical telemetry, isolation, I-352  
 meter-driver, rf, 1-MHz, III-545  
 micro-powered, high-input/high-impedance, 20 dB, II-44  
 micro-sized, III-36  
 microphone, III-34, I-87  
 microphone, electronically balanced input, I-86  
 microwave, IV-315-319  
 monostable, II-268  
 neutralized common source, 100 MHz/400MHz, I-565  
 neutralized common source, 200 MHz, I-568  
 noninverting, I-32, I-33, I-41, III-14  
 noninverting, ac power, I-79  
 noninverting, single-supply, I-75  
 noninverting, split-supply, I-75  
 Norton, absolute value, III-11  
 op amp (*see also* operational amplifiers)  
 op amp, x10, I-37  
 op amp, x100, I-37  
 op amp, clamping circuit, II-22  
 op amp, intrinsically safe-protected, III-12  
 oscilloscope sensitivity, III-436  
 output, four-channel D/A, III-165  
 phono, I-80, I-81  
 phono, magnetic pickup, I-89  
 photodiode, I-361, II-324, III-672  
 photodiode, low-noise, III-19  
 playback, tape, III-672  
 polarity-reversing low-power, III-16  
 power (*see also* power amps), II-46, II-451, III-450-456  
 power, 10-W, I-76  
 power, 12-W, low distortion, I-76  
 power, 90-W, safe area protection, II-459  
 power, GaAsFET with single supply, II-10  
 power, rf power, 600 W, I-559  
 pre-amps (*see* pre-amplifiers)  
 precision, I-40  
 programmable, II-334, III-504-508  
 programmable gain, weighted resistors, II-9  
 pulse-width proportional controller circuit, II-21  
 push-pull, PEP, 100W, 420-450 MHz, I-554  
 PWM servo, III-379  
 reference voltage, I-36  
 remote, I-91  
 rf (*see* rf amplifiers)  
 sample and hold, high-speed, I-587  
 sample and hold, infinite range, II-558  
 selectable input, programmable gain, I-32  
 servo, 400 Hz, II-386  
 servo motor, I-452  
 servo motor drive, II-384  
 signal distribution, I-39  
 sound-activated, gain-controlled amp, IV-528  
 sound mixer, II-37  
 speaker, hand-held transceivers, III-39  
 speaker, overload protector for, II-16  
 speech compressor, II-15  
 standard cell, saturated, II-296  
 stereo, Av/200, I-77  
 stereo, gain control, II-9  
 summing, I-37, III-16  
 summing, fast action, I-36  
 summing, precision design, I-36  
 switching power, I-33  
 tape playback, I-92, IV-36  
 tape recording, I-90  
 telephone, III-621, IV-555, IV-560

- amplifiers (*cont.*)
- thermocouple, I-654, III-14
  - thermocouple, cold junction compensation, II-649
  - thermocouple, high-stability, I-355
  - transducer, I-86, III-669-673
  - transformerless, 6W 8-ohm output, I-75
  - transistorized, basic design, I-85
  - transistorized, headphone, II-43
  - tremolo circuit, voltage-controlled, I-598
  - tube amplifier, high-voltage isolation, IV-426
  - TV audio, III-39
  - two-meter, 5W output, I-567
  - two-meter, 10W power, I-562
  - UHF, I-565
  - UHF, wideband, high-performance FET, I-560
  - unity gain, I-27
  - unity gain, ultra-high Z, ac, II-7
  - VHF, single-device, 80W/50-ohm, I-558
  - video, I-692, III-708-712
  - video, FET cascade, I-691
  - video, loop-through amplifier, IV-616
  - voice activated switch, I-608
  - voltage, differential-to-single-ended, III-670
  - voltage-controlled, IV-20
  - voltage-follower, signal-supply operation, III-20
  - voltage-controlled (*see* voltage-controlled amplifiers)
  - volume, II-46
  - walkman, II-456
  - weighted-resistor programmable gain, precision design, II-9
  - wideband (*see* wideband amplifiers)
  - wide frequency range, III-262
  - write, III-18
  - amplitude modulator, low distortion low level, II-370
  - analog counter circuit, II-137
  - analog delay line, echo and reverberation effects, IV-21
  - analog multiplexers
    - buffered input/output, III-396
    - single-trace to four-trace scope converter, II-431  - analog multiplier, II-392
  - 0/01 percent, II-392
  - analog-to-digital buffer, high-speed 6-bit, I-127
  - analog-to-digital converters, II-23-31, III-22-26, IV-5-6
  - 3-bit, high-speed, I-50
  - 8-bit, I-44, I-46
- 8-bit successive approximation, I-47
- 10-bit, II-28
  - 10-bit serial output, II-27
  - 12-bit, high-speed, II-29
  - 16-bit, II-26
  - board design, IV-6
  - capacitance meter, 3½ digit, III-76
  - cyclic, II-30
  - differential input system, II-31
  - fast precision, I-49
  - four-digit (10,000 count), II-25
  - half-flash, III-26
  - IC, low cost, I-50
  - LCD 3.5-digit display, I-49
  - logarithmic, three-decade, I-48
  - precision design, I-49
  - successive approximation, I-45, II-24, II-30
  - switched-capacitor, III-23
  - three-IC, low-cost, I-50
  - tracking, III-24
  - video converter, IV-610-611
  - analyzer, gas, II-281
  - AND gate, I-395
  - large fan-in, I-395
  - anemometers
    - hot-wire, III-342
    - thermally based, II-241  - angle-of-rotation detector, II-283
  - annunciators, II-32-34, III-27-28, IV-710
  - ac line-voltage, III-730
  - bell, electronic, IV-9
  - chime circuit, low-cost, II-33
  - door buzzer, IV-8
  - door buzzer, electronic, IV-8
  - electronic bell, II-33
  - large fan-in, I-395
  - SCR circuit, self-interrupting load, IV-9
  - sliding tone doorbell, II-34
  - two-door annunciator, IV-10
  - answering machines, beeper, IV-559
  - antennas, IV-11-14
    - active, III-1-2
    - active antenna, wideband rod, IV-4
    - active antenna, with gain, IV-2
    - active antennas, IV-1-4
    - loop, 3.5 MHz, IV-12-13
    - selector switch, IV-538-539
    - tuner, 1-to-30 MHz, IV-14  - antitheft device, I-7
  - arc lamp, 25W, power supply for, II-476
  - arc welding inverter, ultrasonic, 20 KHz, III-700
  - arc-jet power supply, starting circuit, III-479
  - astable flip-flop with starter, II-239
  - astable multivibrators, II-269, II-
- 510, III-196, III-233, III-238
- op amp, III-224
  - programmable-frequency, III-237
  - square wave generation with, II-597
  - attendance counter, II-138
  - attenuators, III-29-31
  - analog signals, microprocessor-controlled, III-101
  - digitally programmable, III-30
  - digitally selectable, precision design, I-52
  - programmable, I-53, III-30
  - programmable (1 to 0.00001), I-53
  - rf, IV-322
  - variable, I-52
  - voltage-controlled, II-18, III-31
  - audio amplifiers, III-32-39
  - AGC, squelch control, III-33
  - automotive stereo systems, high-power, IV-66
  - balance indicator, IV-215
  - Baxandall tone-control, IV-588
  - booster, 20 dB, III-35
  - circuit bridge load drive, III-35
  - complementary-symmetry, I-78
  - distribution, I-39, II-39
  - fixed power supplies, ± 35 V ac, IV-398
  - fixed power supplies, ± 35 V, 5 A, mobile, IV-407
  - high-slew rate power op amp, I-82
  - gain-controlled, stereo, III-34
  - line-operated, III-37
  - load line protection, 75W, I-73
  - low-power, II-454
  - micro-sized, III-36
  - microphone, III-34
  - mini-stereo, III-38
  - pre-amp, NAB tape playback, professional, III-38
  - pre-amp, phono, magnetic, III-37
  - pre-amp, RIAA, III-38
  - Q-multiplier, II-20
  - signal, II-41-47
  - speaker, hand-held transceivers, III-39
  - television type, III-39
  - tone control, II-686
  - ultra-high gain, I-87
  - volume indicator, IV-212
  - audio circuits
    - audio-rf signal tracer probe, I-527
    - automatic gain control, II-17
    - booster, II-455, III-35
    - biquad filter, III-185
    - bridge load drive, III-35
    - carrier-current transmitter, III-79
    - clipper, precise, II-394
    - compressor, II-44

- continuity tester, I-550  
 converter, two-wire to four-wire, II-14  
 distribution amplifier, II-39, I-39  
 filters (*see* audio filters)  
 frequency meter, I-311  
 generators (*see* sound generators)  
 LED bar peak program meter display, I-254  
 limiter, low distortion, II-15  
 millivoltmeter, III-767, III-769  
 mixers (*see* mixers)  
 notch filter, II-400  
 power meter, I-488  
 Q multiplier, II-20  
 sine wave generator, II-564  
 squelch, II-394  
 switching/mixing, silent, I-59  
 waveform generators, precision, III-230  
 audio effects circuits (*see* sound generators)  
 audio equalizer, IV-18  
 audio fader, IV-17  
 audio filters  
     analyzer circuit, IV-309  
     biquad filter, III-185  
     notch filter, II-400  
     tunable, IV-169  
 audio generators (*see* sound generators)  
 audio-operated circuits (*see* sound-operated circuits)  
 audio oscillators, I-64, II-24, III-427, IV-374, IV-375  
     20Hz to 20kHz, variable, I-727  
     light-sensitive, III-315  
     sine wave, II-562  
 audio power amplifier, II-451, III-454, IV-28-33  
     20-W, III-456  
     50-W, III-451  
     6-W, with preamp, III-454  
     audio amplifier, IV-32  
     audio amplifier, 8-W, IV-32  
     bridge, I-81  
     bull horn, IV-31  
     general-purpose, 5 W, ac power supply, IV-30  
     op amp, simple design, IV-33  
     receiver audio circuit, IV-31  
     stereo amp, 12-V/20-W, IV-29  
 audio scramblers, IV-25-27  
     voice scrambler/descrambler, IV-26  
     voice scrambler/disguiser, IV-27  
 audio signal amplifiers, II-41-47, IV-34-42  
     40 dB gain design, IV-36  
     audio compressor, II-44  
     auto fade, II-42  
     balance, II-46  
     balance and loudness amplifier, II-47  
     CD4049 design, IV-40  
     electric guitar, matching amplifier, IV-38  
     line amplifier, universal design, IV-39  
     loudness, II-46  
     low-noise design, IV-37  
     microphone preamp, II-45  
     micropower high-input-impedance 20-dB amplifier, II-44  
     power, II-46  
     preamplifier, 1000x, low-noise design, IV-37  
     preamplifier, general-purpose design, IV-42  
     preamplifier, impedance-matching, IV-37  
     preamplifier, low-noise, IV-41  
     preamplifier, magnetic phono cartridges, IV-35  
     preamplifier, microphone, IV-37, IV-42  
     preamplifier, microphone, low-impedance, IV-41  
     preamplifier, phono, low-noise, IV-36  
     preamplifier, phono, magnetic, ultra-low-noise, IV-36  
     stereo preamplifier, II-43, II-45  
     tape playback amplifiers, IV-36  
     transistor headphone amplifier, II-43  
     volume, II-46  
     audio-frequency doubler, IV-16-17  
     audio/video switcher circuit, IV-540-541  
     auto-advance projector, II-444  
     autodrum sound effect, II-591  
     auto-fade circuit, II-42  
     auto-flasher, I-299  
     auto-zeroing scale bridge circuits, III-69  
     automotive circuits, II-48-63, III-40-52, IV-43-67  
     alarms, automatic-arming, IV-50  
     alarms, automatic turn-off after 8-minute delay, IV-52  
     alarms, automatic turn-off with delay, IV-54  
     alarms, CMOS design, low-current, IV-56  
     alarms, horn as loudspeaker, IV-54  
     alarm, motion actuated, I-9  
     alarms, single-IC design, IV-55  
     air conditioner smart clutch, III-46  
     AM-radio to short-wave radio converter, IV-500  
     analog expanded-scale meter, IV-46  
     audio-amplifier, high-power, IV-66  
     automatic headlight dimmer, II-63  
     automobile locator, III-43  
     automotive exhaust emissions analyzer, II-51  
     back-up beeper, III-49, IV-51, IV-56  
     bar-graph voltmeter, II-54  
     battery charger, ni-cad, I-115  
     battery condition checker, I-108  
     battery current analyzer, I-104  
     battery monitor, I-106  
     battery supply circuit, ±15 V and 5 V, IV-391  
     battery-alternator monitor, III-63  
     brake lights, delayed extra, III-44  
     brake lights, flashing third, III-51  
     brake light, night-safety light for parked cars, IV-61  
     brake light, third brake light, IV-60  
     burglar alarm, I-3, I-7, I-10, II-2, III-4, III-7, IV-53  
     cassette-recorder power circuit, IV-548  
     courtesy light delay switch, III-42  
     courtesy light extender, III-50  
     delayed-action windshield wiper control, II-55  
     digi-tach, II-61  
     directional signals monitor, III-48  
     door ajar monitor, III-46  
     electric vehicles, battery saver, III-67  
     electrical tester, IV-45  
     electronic circuits, IV-63-67  
     fog light controller with delay, IV-59  
     fuel gauge, digital readout, IV-46  
     exhaust-gas emissions analyzer, II-51  
     garage stop light, II-53  
     glow plug driver, II-52  
     headlight alarm, I-109, III-52  
     headlight automatic-off controller, IV-61  
     headlight delay circuit, II-59, III-49  
     headlight dimmer, II-57  
     high-speed warning device, I-101  
     horn, III-50  
     ice formation alarm, II-58  
     ignition circuit, electronic ignition, IV-65  
     ignition cut-off, IV-53  
     ignition substitute, III-41  
     ignition timing light, II-60  
     immobilizer, II-50  
     intermittent windshield wiper with dynamic braking, II-49  
     light circuits, IV-57-62  
     lights-on warning, II-55, III-42, IV-58, IV-60, IV-62  
     night-safety light for parked cars, IV-61  
     oil-pressure gauge, digital readout, IV-44, IV-47

automotive circuits (*cont.*)  
 PTC thermistor automotive temperature indicator, II-56  
 radio, receiver for, II-525  
 read-head pre-amplifier, III-44  
 road ice alarm, II-57  
 security system, I-5, IV-49-56  
 tachometer, set point, III-47  
 tachometer/dwell meter, III-45  
 temperature gauge, digital readout, IV-48  
 temperature indicator, PTC thermistor, II-56  
 turn signals, sequential flasher, II-109, III-1  
 vacuum gauge, digital readout, IV-45  
 voltage gauge, IV-47  
 voltage regulator, III-48, IV-67  
 voltmeter, bargraph, I-99  
 water-temperature gauge, IV-44  
 wiper control, II-55, II-62  
 wiper delay, solid-state, IV-64  
 wiper interval controller, IV-67

## B

B-field measurer, IV-272  
 back-biased GaAs LED light sensor, II-321  
 back-EMF PM motor speed control, II-379  
 backup-light beeper, automotive, IV-51, IV-56  
 bagpipe sound effect, IV-521  
 balance indicator, audio amplifiers, IV-215  
 balancer, stereo, I-619  
 barricade flasher, I-299  
 battery charge/discharge indicator, I-122  
 battery charger, automatic shut-off, II-113  
 balance amplifiers, III-46  
 loudness control, II-47, II-395  
 balance indicator, bridge circuit, II-82  
 bandpass filters (*see also filter circuits*), II-222  
 0.1 to 10 Hz bandpass, I-296  
 160 Hz, I-296  
 active, II-221, II-223, III-190  
 active, with 60dB gain, I-284  
 active, 1 kHz, I-284  
 active, 20 kHz, I-297  
 active, variable bandwidth, I-286  
 biquad, RC active, I-285  
 biquad, second-order, III-188  
 Chebyshev, fourth-order, III-191  
 high Q, I-287  
 MFB, multichannel tone decoder, I-288

multiple feedback, I-285, II-224  
 multiple feedback, 1.0 kHz, I-297  
 notch, II-223  
 Sallen-Key, 500 Hz, I-291  
 second-order biquad, III-188  
 state variable, I-290  
 tunable, IV-171  
 band reject filters, active (*see also filter circuits*), II-401  
 bang-bang power controllers, IV-389  
 bar-code scanner, III-363  
 bar-expanded scale meter, II-186  
 bar graphs  
 ac signal indicator, II-187  
 voltmeter, II-54  
 voltmeter, automotive, I-99  
 barometer, IV-273  
 bass tuners, II-362  
 12 V, I-111  
 200 mA-hour, 12V ni-cad, I-114  
 automatic shutoff for, I-113  
 batteries  
 fixed power supply, 12-VDC/120-VAC, III-464  
 high-voltage generator, III-482  
 zapper, simple ni-cad, I-116  
 battery chargers, I-113, II-64, II-69, III-53-59, IV-68-72  
 12-V charger, IV-70  
 battery-life extender, lead-acid batteries, IV-72  
 constant-voltage, current limited charger, I-115  
 control for 12V, I-112  
 current limited 6V, I-118, IV-70  
 gel cell, II-66  
 lead/acid, III-55  
 lithium, II-67  
 low-battery detector, lead-acid, III-56  
 low-battery warning, III-59  
 low-cost trickle for 12V storage, I-117  
 mobile battery charger, +12-Vdc, IV-71  
 ni-cad, I-118  
 ni-cad, portable, III-57, IV-69  
 ni-cad, temperature-sensing charger, IV-77  
 ni-cad, zapper, II-66  
 power supply and, 14V, III-4A, II-73  
 PUT, III-54  
 regulator, I-117  
 simpli-cad, I-112  
 solar cell, II-71  
 thermally controlled ni-cad, II-68  
 UJT, III-56  
 universal, III-56, III-58  
 versatile design, II-72  
 voltage detector relay, II-76  
 wind powered, II-70  
 zapper, simple ni-cad, I-116  
 battery monitors, I-106, II-74-79, III-60-67, IV-73-80  
 analyzer, ni-cad batteries, III-64  
 automatic shutoff, battery-powered projects, III-61  
 battery saver, electric vehicles, III-67  
 battery-life extender, 9 V, III-62  
 battery life-extender, disconnect switch, IV-75  
 capacity tester, III-66  
 condition checker, I-108, I-121  
 converter, dc-to-dc +3-to-+5 V, IV-119  
 disconnect switch, life-extender circuit, IV-75  
 dynamic, constant current load fuel cell/battery tester, II-75  
 internal resistance tester, IV-74  
 level indicator, II-124  
 lithium battery, state of charge indicator, II-78  
 low-battery detector, III-63, IV-76  
 low-battery indicator, I-124, II-77, IV-80  
 low-battery protector, III-65  
 low-battery warning/disconnect, III-65  
 protection circuit, ni-cad batteries, III-62  
 sensor, quick-deactivating, III-61  
 splitter, III-66  
 status indicator, II-77  
 step-up switching regulator for 6V, II-78  
 temperature-sensing battery charger, ni-cad batteries, IV-77  
 test circuit, IV-78  
 test circuit, ni-cad batteries, IV-79  
 threshold indicator, I-124  
 undervoltage indicator for, I-123  
 voltage, II-79  
 voltage detector relay in, II-76  
 voltage gauge, automotive battery, IV-47  
 voltage indicator, solid-state, I-120  
 voltage measuring regulator, IV-77  
 voltage monitor, II-79  
 voltage monitor, HTS, I-122  
 voltage-level indicator, IV-80  
 battery-life extender, 9 V, III-62, IV-75  
 battery-operated equipment  
 ac power control switch, battery-triggered, IV-387  
 automatic shutoff, III-61  
 automotive battery supply, ±15 V and 5 V, IV-391  
 automotive cassette-deck power

circuit, IV-548  
 bipolar power supply for, II-475  
 buffer amplifier for standard cell, I-351  
 fence charger, II-202  
 flasher, high powered, II-229  
 lantern circuit, I-380  
 light, capacitance operated, I-131  
 On indicator, IV-217  
 undervoltage indicator for, I-123  
 warning light, II-320  
 Baxandall tone-control audio amplifier, IV-588  
 BCD-to-analog converter, I-160  
 BCD-to-parallel converter, multiplexed, I-169  
 beacon transmitter, III-683  
 beep transformer, III-555, III-566  
 beepers  
     back-up, automotive circuits, III-49  
     repeater, I-19  
 bells  
     electronic, II-33, IV-9  
     electronic phone, I-636  
 benchtop power supply, II-472  
 bicycle speedometer, IV-271, IV-282  
 bilateral current source, III-469  
 binary counter, II-135  
 biomedical instrumentation differential amplifier, III-282  
 bipolar dc-dc converter with no inductor, II-132  
 bipolar power supply, II-475  
 bipolar voltage reference source, III-774  
 biquad audio filter, I-292-293, III-185  
     second-order bandpass, III-188  
     RC active bandpass, I-285  
 bird-chirp sound effect, II-588, III-577  
 bistable multivibrator, touch-triggered, I-133  
 bit grabber, computer circuits, IV-105  
 blinks (*see* flashers and blinks)  
 blown-fuse alarm, I-10  
 boiler control, I-638  
 bongos, electronic, II-587  
 boosters  
     12ns, II-97  
     audio, III-35, II-455  
     booster/buffer for reference current boost, IV-425  
     electronic, high-speed, II-96  
     forward-current, III-17  
     LED, I-307  
     power booster, op-amp design, IV-358  
     rf amplifiers, broadcast band booster, IV-487  
     shortwave FET, I-561

bootstrapping, cable, I-34  
 brake lights  
     extra, delayed, III-44  
     flashing, extra, III-51  
 brake, PWM speed control/energy recovering, III-380  
 breakers  
     12ns, II-97  
     high-speed electronic, II-96  
 breaker power dwell meter, I-102  
 breakout box, buffer, II-120  
 breath alert alcohol tester, III-359  
 breath monitor, III-350  
 bridge balance indicator, II-82  
 bridge circuits, I-552, II-80-85, III-68-71, IV-81-83  
 ac, II-81  
 ac servo amplifier with, III-387  
 accurate null/variable gain circuit, III-69  
 air-flow sensing thermistor bridge, IV-82  
 auto-zeroing scale, III-69  
 balance indicator, II-82  
 bridge transducer amplifier, III-71  
 crystal-controlled bridge oscillator, IV-127  
 differential amplifier, two op-amp, II-83  
 inductance bridge, IV-83  
 load driver, audio circuits, III-35  
 low power common source amplifier, II-84  
 one-power supply design, IV-83  
 QRP SWR, III-336  
 rectifier, fixed power supplies, IV-398  
 remote sensor loop transmitter, III-70  
 strain gauge signal conditioner, II-85, III-71  
 transducer, amplifier for, II-84  
 Wien bridge, variable oscillator, III-424  
 Wien-bridge filter, III-659  
 Wien-bridge oscillator, III-429  
 Wien-bridge oscillator, low-distortion, thermally stable, III-557  
 Wien-bridge oscillator, low-voltage, III-432  
 Wien-bridge oscillator, single-supply, III-558  
 brightness controls, III-308  
 LED, I-250  
 low loss, I-377  
 broadband communications  
     ac active rectifier, IV-271  
 broadcast-band rf amplifier, II-546, III-264  
 buck converter, 5V/0.5A, I-494  
 buck/boost converter, III-113  
 bucking regulator, high-voltages, III-481  
 buffers, IV-88-90  
 ac, single-supply, high-speed, I-127-128  
 ADC input, high-resolution, I-127  
 A/D, 6-bit, high-speed, I-127  
 booster/buffer for reference current boost, IV-425  
 capacitance, stabilized low-input, III-502  
 input/output, for analog multiplexers, III-11  
 inverting bistable buffer, IV-90  
 oscillator buffers, IV-89  
 precision-increasing design, IV-89  
 rf amplifiers, buffer amplifier with modulator, IV-490  
 stable, high-impedance, I-128  
 unity gain, stable, good speed and high-input impedance, II-6  
 video, low-distortion, III-712  
 wideband, high-impedance/low-capacitance I-127  
 buffer amplifiers  
     10x, I-128  
     100x, I-128  
     ac, single-supply, I-126  
     battery-powered, standard cell, I-351  
     sinewave output, I-126  
     unity-gain, stable design, II-6  
 buffered breakout box, II-120  
 bug detector, III-365  
 bug tracer, III-358  
 bull horn, II-453, IV-31  
 burglar alarms (*see also* alarms)  
 burst generators (*see also* function generators; sound generators; waveform generators), II-86-90, III-72-74  
 multi-, square waveform, II-88  
 rf, portable, III-73  
 single timer IC square wave, II-89  
 single-tone, II-87  
 strobe-tone, I-725, II-90  
 tone, II-90  
 tone burst, European repeaters, III-74  
 burst power control, III-362  
 bus interface, eight bit uP, II-114  
 Butler oscillators  
     aperiodic, I-196  
     common base, I-191  
     emitter follower, II-190-191, II-194  
 Butterworth filter, high-pass, fourth-order, I-280  
 buzzers  
     door buzzer, IV-8

buzzers (*cont.*)

continuous tone 2kHz, I-11  
gated 2kHz, I-12

## C

cable bootstrapping, I-34  
cable tester, III-539  
calibrated circuit, DVM auto, I-714  
calibrated tachometer, III-598  
calibration standard, precision, I-406  
calibrators  
  crystal, 100 kHz, I-185  
  electrolytic-capacitor reforming  
    circuit, IV-276  
ESR measurer, IV-279  
oscilloscope, II-433, III-436  
portable, I-644  
square-wave, 5 V, I-423  
tester, IV-265  
wave-shaping circuits, high slew  
  rates, IV-650  
cameras (*see* photography-related  
  circuits; television-related circuits;  
  video circuits)  
canceler, central image, III-358  
capacitance buffers  
  low-input, III-498  
  low-input, stabilized, III-502  
capacitance meters, I-400, II-91-94,  
  III-75-77  
  A/D, three-and-a-half digit, III-76  
  capacitance-to-voltage, II-92  
  digital, II-94  
capacitance multiplier, I-416, II-200  
capacitance relay, I-130  
capacitance switched light, I-132  
capacitance-to-pulse width converter,  
  II-126  
capacitance-to-voltage meter, II-92  
capacitor discharge  
  high-voltage generator, III-485  
  ignition system, II-103  
capacity tester, battery, III-66  
car port, automatic light controller, II-  
  308  
cars (*see* automotive circuits)  
carrier-current circuits, III-78-82, IV-  
  91-93  
  AM receiver, III-81  
  audio transmitter, III-79  
  data receiver, IV-93  
  data transmitter, IV-92  
  FM receiver, III-80  
  intercom, I-146  
  power-line modem, III-82  
  receiver, I-143  
  receiver, single transistor, I-145  
  receiver, IC, I-146

remote control, I-146  
transmitter, I-144  
transmitter, integrated circuit, I-145  
carrier-operated relay (COR), IV-461  
carrier system receiver, I-141  
carrier transmitter with on/off 200kHz  
  line, I-142  
cascaded amplifier, III-13  
cassette bias oscillator, II-426  
cassette interface, telephone, III-618  
cassette-recorders (*see* tape-recorder  
  circuits)  
centigrade thermometer, I-655, II-648,  
  III-662  
central image canceller, III-358  
charge pool power supply, III-469  
charge pumps  
  positive input/negative output, I-418,  
    III-360  
  regulated for fixed power supplies,  
    IV-396  
chargers (*see* battery charger)  
chase circuit, I-326, III-197  
Chebyshev filters (*see also* filter cir-  
  cuits)  
  bandpass, fourth-order, III-191  
  fifth-order multiple feedback low-  
    pass, II-219  
  high-pass, fourth-order, III-191  
chime circuit, low-cost, II-33  
chopper amplifier, I-350, II-7, III-12  
checkers  
  buzz box continuity and coil, I-551  
  car battery condition, I-108  
  crystal, I-178, I-186  
  zener diode, I-406  
chroma demodulator with RGB matrix,  
  III-716  
chug-chug sound generator, III-576  
circuit breakers (*see also* protection  
  circuits)  
  12ms, II-97  
  ac, III-512  
  high-speed electronic, II-96  
  trip circuit, IV-423  
circuit protection (*see* protection cir-  
  cuits)  
clamp-on-current probe compensator,  
  II-501  
clamp-limiting amplifiers, active, III-15  
clamping circuits  
  video signal, III-726  
  video summing amplifier and, III-710  
class-D power amplifier, III-453  
clippers, II-394, IV-648  
  audio-powered noise, II-396  
  audio clipper/limiter, IV-355  
  zener-design, fast and symmetrical,  
    IV-329

clock circuits, II-100-102, III-83-85  
  60Hz clock pulse generator, II-102  
adjustable TTL, I-614  
comparator, I-156  
crystal oscillators, micropower  
  design, IV-122  
digital, with alarm, III-84  
gas discharge displays, 12-hour, I-253  
oscillator/clock generator, III-85  
phase lock, 20-Mhz to Nubus, III-  
  105  
run-down clock for games, IV-205  
sensor touch switch and clock, IV-  
  591  
single op amp, III-85  
source, clock source, I-729  
three-phase from reference, II-101  
TTL, wide-frequency, III-85  
Z80 computer, II-121  
clock generators  
  oscillator, I-615, III-85  
  precision, I-193  
  pulse generator, 60 Hz, II-102  
clock radio, I-542  
  AM/FM, I-543  
CMOS circuits  
  555 astable true rail to rail square  
    wave generator, II-596  
9-bit, III-167  
coupler, optical, III-414  
crystal oscillator, III-134  
data acquisition system, II-117  
flasher, III-199  
inverter, linear amplifier from, II-11  
mixer, I-57  
optical coupler, III-414  
oscillator, III-429, III-430  
short-pulse generator, III-523  
timer, programmable, precision, III-  
  652  
touch switch, I-137  
universal logic probe, III-499  
coaxial cable, five-transistor pulse  
  booster, II-191  
Cockcroft-Walton cascaded voltage  
  doubler, IV-635  
code-practice oscillator, I-15, I-20, I-  
  22, II-428-431, IV-373, IV-375, IV-  
  376  
coil drivers, current-limiting, III-173  
coin flipper circuit, III-244  
color amplifier, video, III-724  
color-bar generator, IV-614  
color organ, II-583, II-584  
color video amplifier, I-34  
Colpitts crystal oscillator, I-194, I-572,  
  II-147  
1-to-20 MHz, IV-123  
frequency checker, IV-301

harmonic, I-189-190  
 two-frequency, IV-127  
 combination locks  
   electronic, II-196  
   electronic, three-dial, II-195  
 commutator, four-channel, II-364  
 comparanders (*see* compressor/expander circuits)  
 comparators, I-157, II-103-112, III-86-90  
   demonstration circuit, II-109  
   diode feedback, I-150  
   display and, II-105  
   double-ended limit, I-156, II-105  
   dual limit, I-151  
   four-channel, III-90  
   frequency, II-109  
   frequency-detecting, III-88  
   high-impedance, I-157  
   high-input impedance window comparator, II-108  
   high-low level comparator with one op amp, II-108  
   latch and, III-88  
   LED frequency, II-110  
   limit, II-104, I-156  
   low-power, less than 10uV hysteresis, II-104  
   microvolt, dual limit, III-89  
   microvolt, with hysteresis, III-88  
   monostable using, II-268  
   opposite polarity input voltage, I-155  
   oscillator, tunable signal, I-69  
   power supply overvoltage, glitch detection with, II-107  
   precision, balanced input/variable offset, III-89  
   precision, photodiode, I-360, I-384  
   time-out, I-153  
   TTL-compatible Schmitt trigger, II-111  
   three-input and gate comparator, op-amp design, IV-363  
   variable hysteresis, I-149  
   voltage comparator, IV-659  
   voltage monitor, II-104  
   window, I-152, I-154, II-106, III-87, III-90, III-776-781, IV-656-658  
   with hysteresis, I-157  
   with hysteresis, inverting, I-154  
   with hysteresis, noninverting, I-153  
 compass  
   digital design, IV-147  
   Hall-effect, III-258  
 compensator, clamp-on-current probe, II-501  
 composite amplifier, II-8, III-13  
 composite-video signal text adder, III-716

compressor/expander circuits, III-91-95, IV-94-97  
 amplifier/compressor, low-distortion, IV-24  
 audio, II-44  
 audio compressor/audio-band splitter, IV-95  
 clock circuit, I-156  
 guitar, sound-effect circuit, IV-519  
 hi-fi, II-12, II-13  
 hi-fi, de-emphasis, III-95  
 hi-fi, pre-emphasis, III-93  
 low-voltage, III-92  
 protector circuit, IV-351  
 speech, II-2  
 universal design, IV-96-97  
 variable slope, III-94  
 computalarm, I-2  
 computer circuits (*see also* interfaces), II-113-122, III-96-108, IV-98-109  
   analog signal attenuator, III-101  
   alarm, I-2  
   ASCII triplex LCD, 8048/IM80C48 8-char/16-seg, II-116  
   bit grabber, IV-105  
   buffered breakout box, II-120  
   bus interface, 8-bit uP, II-114  
   clock phase lock, 20-Mhz-to-Nubus, III-105  
 CMOS data acquisition system, II-117  
 CPU interface, one-shot design, IV-239  
 data separator for floppy disks, II-122  
 deglitcher, IV-109  
 display, eight-digit, III-106  
 dual 8051s execute in lock-step circuit, IV-99  
 EEPROM pulse generator, 5V-powered, III-99  
 eight-channel mux/demux system, II-115  
 eight-digit microprocessor display, III-106  
 flip-flop inverter, spare, III-103  
 high-speed data acquisition system, II-118  
 interface, 680x, 650x, 8080 families, III-98  
 interval timer, programmable, II-678  
 keyboard matrix interface, IV-240  
 line protectors, 3 uP I/O, IV-101  
 logic-level translators, IV-242  
 logic line monitor, III-108  
 long delay line, logic signals, III-107  
 memory/protector power supply monitor, IV-425  
 memory saving power supply for, II-486  
 microprocessor selected pulse width control, II-116  
 multiple inputs detector, III-102  
 one-of-eight channel transmission system, III-100  
 oscilloscope digital-levels, IV-108  
 power supply watchdog, II-494  
 pulse width control, II-116  
 printer-error alarm, IV-106  
 reset protection, IV-100  
 reset switch, child-proof, IV-107  
 RGB blue box, III-99  
 RS-232 dataselector, automatic, III-97  
 RS-232C line-driven CMOS circuits, IV-104  
 RS-232-to-CMOS line receiver, III-102  
 RS-232C LED circuit, III-103  
 short-circuit sensor, remote data lines, IV-102  
 signal attenuator, analog, microprocessor-controlled, III-101  
 socket debugger, coprocessor, III-104  
 speech synthesizer, III-732  
 stalled-output detector, IV-109  
 switch debouncer, IV-105  
 switch debouncer, auto-repeat, IV-106  
 triac array driver, II-410  
 uninterruptible power supply, II-462  
 Vpp generator for EPROMs, II-114  
 XOR gate, IV-107  
 XOR gate up/down counter, III-105  
 Z-80 bus monitor/debugger, IV-103  
 Z80 clock, II-121  
 contact switch, I-136  
 continuity testers, II-533, II-535, III-345, III-538-540, IV-287, IV-289, IV-296  
   audible, adjustable, II-536  
   cable tester, III-539  
   latching design, IV-295  
   PCB, II-342, II-535  
 contrast meters, II-447  
   automatic, I-472  
 control circuits (*see also* alarms; detectors; indicators; monitors; motor control circuits; sensors), III-378-390  
   ac servo amplifier, bridge-type, III-387  
   boiler, I-638  
   brightness, low-loss, I-377  
   fan speed, III-382  
   feedback speed, I-447  
   floodlamp power, I-373  
   fluid level, I-387

- control circuits (*cont.*)  
   full-wave SCR, I-375  
   heater, I-639  
   hi-fi tone, high-Z input, I-676  
   high-power, sensitive contacts for, I-371  
   LED brightness, I-250  
   light-level, I-380  
   light-level, 860 W limited-range low-cost, I-376  
   light-level, brightness, low-loss, I-377  
   liquid level, I-388  
   model train and/or car, I-453, I-455  
   motor controllers (*see* motor control circuits)  
   on/off, I-665  
   phase control, hysteresis-free, I-373  
   power tool torque, I-458  
   sensitive contact, high power, I-371  
   servo system, III-384  
   single-setpoint temperature, I-641  
   speed control (*see* speed controllers)  
   switching, III-383  
   temperature, I-641-643  
   temperature-sensitive heater, I-640  
   three-phase power-factor, II-388  
   tone control (*see* tone controls)  
   voltage-control, pulse generator and, III-524  
   water-level sensing, I-389  
   windshield wiper, I-105  
 conversion and converters, I-503, II-123-132, III-109-122, IV-110-120  
   3-5 V regulated output, III-739  
   4-18 MHz, III-114  
   4-to-20-mA current loop, IV-111  
   5V-to-isolated 5V at 20mA, III-474  
   5V/0.5A buck, I-494  
   9-to-5 V converter, IV-119  
   12 V- to 9-, 7.5-, or 6-V, I-508  
   12-to-16 V, III-747  
   +50V feed forward switch mode, I-495  
   +50 V push-pull switched mode, I-494  
   100 MHz, II-130  
   100 V/10.25 A switch mode, I-501  
   ac-to-dc, I-165  
   ac-to-dc, high-impedance precision rectifier, I-164  
   analog-to-digital (*see* analog-to-digital conversion)  
   ATV rf receiver/converter, IV-420  
     MHz, low-noise, IV-496, IV-497  
   BCD-to-analog, I-160  
   BCD-to-parallel, multiplexed, I-169  
   buck/boost, III-113  
   calculator-to Stopwatch, I-153  
   capacitance-to-pulse width, II-126  
   current-to-frequency, IV-113  
   current-to-frequency, wide-range, I-164  
   current-to-voltage, I-162, I-165  
   current-to-voltage, grounded bias and sensor, II-126  
   current-to-voltage, photodiode, II-128  
   dc-dc, 3-25 V, III-744, IV-118  
   dc-to-dc, +3-to +5 V battery, IV-119  
   dc-to-dc, 1-to-5 V, IV-119  
   dc-to-dc, bipolar, no inductor, II-132  
   dc-to-dc, fixed 3- to 15-V supplies, IV-400  
   dc-to-dc, isolated +15V., III-115  
   dc-to-dc, push-pull, 400 V, 60 W, I-210  
   dc-to-dc, regulating, I-210, I-211, II-125, III-121  
   dc-to-dc, step up-step down, III-118  
   digital-to-analog (*see* digital-to-analog conversion)  
   fixed power supply, III-470  
   flyback, I-211  
   flyback, self oscillating, I-170, II-128  
   flyback, voltage, high-efficiency, III-744  
   frequency, I-159  
   frequency-to-voltage (*see* frequency-to-voltage conversion)  
   high-to-low impedance, I-41  
   intermittent converter, power-saving design, IV-112  
   light intensity-to-frequency, I-167  
   logarithmic, fast-action, I-169  
   low-frequency, III-111  
   ohms-to-volts, I-168  
   oscilloscope, I-471  
   period-to-voltage, IV-115  
   pico-ampere, 70 voltage with gain, I-170  
   PIN photodiode-to-frequency, III-120  
   polarity, I-166  
   positive-to-negative, III-112, III-113  
   peak-to-peak, ac-dc, precision, II-127  
   pulse height-to-width, III-119  
   pulse train-to-sinusoid, III-122  
   pulse width-to-voltage, III-117  
   radio beacon converter, IV-495  
   rectangular-to-triangular waveform, IV-116-117  
   regulated 15-Vout 6-V driven, III-745  
   resistance-to-voltage, I-161-162  
   RGB-composite video signals, III-714  
   RMS-to-dc, II-129, I-167  
   RMS-to-dc, 50-MHz thermal, III-117  
   RGB-to-NTSC, IV-611  
   sawtooth wave converter, IV-114  
   shortwave, III-114  
   simple LF, I-546  
   sine-to-square wave, I-170, IV-120  
   square-to-sine wave, III-118  
   square-to-triangle wave, TTL, II-125  
   temperature-to-frequency, I-168  
   temperature-to-time, III-632-633  
   triangle-to-sine wave, II-127  
   TTL-to-MOS logic, II-125, I-170  
   two-wire to four-wire audio, II-14  
   unipolar-to-dual voltage supply, III-743  
   video, a/d and d/a, IV-610-611  
   video, RGB-to-NTSC, IV-611  
   VLF, I-547  
   VLF, rf converter, IV-497  
   voltage ratio-to-frequency, III-116  
   voltage, III-742-748, III-742  
   voltage, negative voltage, uP-controlled, IV-117  
   voltage, offline, 1.5-W, III-746  
   voltage-to-current, I-166, II-124, III-110, IV-118  
   voltage-to-current, power, I-163  
   voltage-to-current, zero IB error, III-120  
   voltage-to-frequency (*see* voltage-to-frequency conversion)  
   voltage-to-pulse duration, II-124  
   WWV-to-SW rf converter, IV-499  
 coprocessor socket debugger, III-104  
 countdown timer, II-680  
 counters, II-133-139, III-123-130  
   analog circuit, II-137  
   attendance, II-138  
   binary, II-135  
   divide-by-N, CMOS programmable, I-257  
   divide-by-n, 1 + GHz, IV-155  
   divide-by-odd-number, IV-153  
   frequency, III-340, III-768, IV-300  
   frequency, 1.2 GHz, III-129  
   frequency, 10-MHz, III-126  
   frequency, 100 MHz, periodic, II-136  
   frequency, low-cost, III-124  
   frequency, preamp, III-128  
   frequency, tachometer and, I-310  
   geiger, I-536-537  
   microfarad counter, IV-275  
   odd-number divider and, III-217  
   preamplifier, oscilloscope, III-438  
   precision frequency, I-253  
   programmable, low-power wide-range, III-126  
   ring, 20 kHz, II-135  
   ring, incandescent lamp, I-301  
   ring, low cost, I-301  
   ring, low-power pulse circuit, IV-437

- ring, SCR, III-195  
 ring, variable timing, II-134  
 time base, function generators, I-1 Hz, IV-201  
 universal, 10 MHz, I-255, II-139  
 universal, 40-MHz, III-127  
 up/down, 8-digit, II-134  
 up/down, extreme count freezer, III-125  
 up/down, XOR gate, III-105  
 couplers  
     linear, ac analog, II-412  
     linear, analog, II-413  
     linear, dc, II-411  
     optical, CMOS design, III-414  
     optical, TTL design, III-416  
     photon, II-412  
     transmitter oscilloscope for CB signals, I-473  
 courtesy light delay/extender, I-98, III-42, III-50  
 CRO doubler, III-439  
 cross-fader, II-312  
 cross-hatch generator, color TV, III-724  
 crossover networks, II-35  
     5V, I-518  
     ac/dc lines, electronic, I-515  
     active, I-172  
     active, asymmetrical third order Butterworth, I-173  
     electronic circuit for, II-36  
 crowbars, I-516  
     electric, III-510  
     electronic, II-99  
     SCR, II-496  
 crystal oscillators (*see also* oscillators),  
     I-180, I-183-185, I-195, I-198, II-140-151, III-131-140, IV-121-128  
 1-to-20 MHz, TTL design, IV-127  
 1-to-4 MHz, CMOS design, IV-125  
 10 MHz, II-141  
 10-to-150 kHz, IV-125  
 10-to-80 MHz, IV-125  
 50-to-150 MHz, IV-126  
 96 MHz, I-179  
 150-to-30,000 kHz, IV-126  
 330 MHz, IV-125  
 aperiodic, parallel-mode, I-196  
 bridge, crystal-controlled, IV-127  
 Butler oscillator, I-182  
 calibrator, 100 kHz, I-185, IV-124  
 ceramic, 10 MHz, varactor tuned, II-141  
 clock, micropower design, IV-122  
 CMOS, I-187, III-134  
 CMOS, 1-to-4 MHz, IV-125  
 Colpitts, II-147  
 Colpitts, 1-to-20 MHz, IV-123  
 Colpitts, frequency checker, IV-301  
 Colpitts, two-frequency, IV-127  
 crystal-controlled oscillator as, II-147  
 crystal-stabilized IC timer for subharmonic frequencies, II-151  
 crystal tester, I-178, I-186, II-151  
 doubler and, I-184  
 easy start-up, III-132  
 FET, 1 MHz, II-144  
 fundamental-frequency, III-132  
 high-frequency, I-175, II-148  
 high-frequency signal generator as, II-150  
 IC-compatible, II-145  
 LO for SSB transmitter controlled by, II-142  
 low-frequency, I-184, II-146  
 low-frequency, 10 kHz to 150 kHz, II-146  
 low-noise, II-145  
 OF-1 HI oscillator, international, I-197  
 OF-1 LO oscillator, international, I-189  
 overtone, I-176, I-180, I-183, II-146  
 overtone, 100 MHz, IV-124  
 marker generator, III-138  
 mercury cell crystal-controlled oscillator as, II-149  
 overtone, I-176, I-177, I-180, I-186, III-146  
 Pierce, II-144  
 Pierce, 1-MHz, III-134  
 Pierce, JFET, I-198  
 Pierce, low-frequency, III-133  
 quartz, two-gate, III-136  
 reflection oscillator, crystal-controlled, III-136  
 Schmitt trigger, I-181  
 signal source controlled by, II-143  
 sine-wave oscillator, I-198  
 stable low frequency, I-198  
 standard, 1 MHz, I-197  
 temperature-compensated, I-187, III-137  
 temperature-compensated, 5V  
     driven, low-power, II-142  
 third-overtone, I-186, IV-123  
 time base, economical design, IV-128  
 TTL design, I-179  
 TTL design, 1-to-20 MHz, IV-127  
 TTL-compatible, I-197  
 transistorized, I-188  
 tube-type, I-192  
 VHF, 20-MHz, III-138  
 VHF, 50-MHz, III-140  
 VHF, 100-MHz, III-139  
 voltage-controlled, III-135, IV-124  
 crystal switching, overtone oscillator with, I-183  
 current analyzer, auto battery, I-104  
 current booster, I-30, I-35  
 current collector head amplifier, II-11, II-295  
 current loop, 4-to-20-mA converter, IV-111  
 current meters and monitors, I-203, II-152-157, III-338  
 ac current indicator, IV-290  
 current sensing in supply rails, II-153  
 electrometer amplifier with overload protection, II-155  
 Hall-effect circuit, III-255  
 Hall-sensor, IV-284  
 high-gain current sensor, IV-291  
 pico ammeter, II-154, II-157  
 pico ammeter, guarded input, II-156  
 range ammeter, six-decade, II-153, II-156  
 current readout, rf, I-22  
 current sensing, supply rails, II-153  
 current sink, I-206  
     1 mA for fixed power supplies, IV-402  
     voltage-controlled, IV-629  
 current sources, I-205, I-697  
     0-to-200-nA, IV-327  
     bilateral, III-469, I-694-695  
     bipolar, inverting, I-697  
     bipolar, noninverting, I-695  
     constant, I-697, III-472  
     fixed power supplies, bootstrapped amp, IV-406  
     fixed power supplies, differential-input, fast-acting, IV-405  
     low-current source, fixed power supplies, IV-399  
     precision, I-205  
     precision, 1mA to 1mA, I-206  
     regulator, variable power supply, III-490  
     variable power supplies, voltage-programmable, IV-420  
     voltage-controlled, grounded source/load, III-468  
 current-loop controller, SCR design, IV-387  
 current-shunt amplifiers, III-21  
 current-to-frequency converter, IV-113 wide range, I-164  
 current-to-voltage amplifier, high-speed, I-35  
 current-to-voltage converter, I-162, I-165  
     grounded bias and sensor in, II-126  
     photodiode, II-128  
 curve tracer  
     diodes, IV-274  
     FET, I-397  
 CW radio communications

CW radio communications (*cont.*)

filter, razor sharp, II-219  
keying circuits, IV-244  
offset indicator, IV-213  
SSB/CW product detector, IV-139  
transceiver, 5 W, 80-meter, IV-602  
transmitter, 1-W, III-678  
transmitter, 40-M, III-684  
transmitter, 902-MHz, III-686  
transmitter, HF low-power, IV-601  
transmitter, QRP, III-690  
cyclic A/D converter, II-30

## D

darkroom equipment (*see photography-related circuits*)  
Darlington regulator, variable power supplies, IV-421  
data-manipulation circuits, IV-129-133  
acquisition circuits, CMOS system, II-117  
acquisition circuits, four-channel, I-421  
acquisition circuits, high-speed system, II-118  
analog-signal transmission isolator, IV-133  
data-acquisition systems, IV-131  
link, IR type, I-341  
prescaler, low-frequency, IV-132  
read-type circuit, 5 MHz, phase-encoded, II-365  
receiver/message demuxer, three-wire, IV-130  
selector, RS-232, III-97  
separator, floppy disk, II-122  
data transmission  
  receiver, carrier-current circuit design, IV-93  
  transmitter, carrier-current circuit design, IV-92  
dc adapter/transceiver, hand-held, III-461  
dc generators, high-voltage, III-481  
dc restorer, video, III-723  
dc servo drive, bipolar control input, II-385  
dc static switch, II-367  
dc-to-dc converters, IV-118  
  1-to-5 V, IV-119  
  3-25 V, III-744  
bipolar, no inductor, II-132  
dual output  $\pm$  12-15 V, III-746  
fixed power supplies, 3-to-15 V, IV-400  
isolated +15 V, III-115  
push-pull, 400 V, 60 W, I-210

regulated, I-210, I-211, II-125, III-121  
step up/step down, III-118  
dc-to-dc SMPS variable power supply, II-480  
debouncer, III-592, IV-105  
  auto-repeat, IV-106  
  flip-flop, IV-108  
debugger, coprocessor sockets, III-104  
decibel level detector, audio, with meter driver, III-154  
decoders, II-162, III-141-145  
  10.8 MHz FSK, I-214  
24-percent bandwidth tone, I-215  
direction detector, III-144  
dual-tone, I-215  
encoder and, III-144  
frequency division multiplex stereo, II-169  
PAL/NTSC, with RGB input, III-717  
radio control receiver, I-574  
SCA, I-214, III-166, III-170  
second-audio program adapter, III-142  
sound-activated, III-145  
stereo TV, II-167  
time division multiplex stereo, II-168  
tone alert, I-213  
tone dial, I-631  
tone dial sequence, I-630  
tone, I-231, III-143  
tone, dual time constant, II-166  
tone, relay output, I-213  
video, NTSC-to-RGB, IV-613  
weather-alert detector/decoder, IV-140  
deglitcher circuit, computer circuits, IV-109  
delay circuits/ delay units, III-146-148  
  adjustable, III-148  
door chimes, I-218  
headlights, I-107, II-59  
leading-edge, III-147  
long duration time, I-217, I-220  
precision solid state, I-664  
pulse, dual-edge trigger, III-147  
time delay, constant-current charging, II-668  
time delay, simple design, I-668, II-220  
  windshield wiper delay, I-97, II-55  
delay line, analog, echo and reverb effects, IV-21  
delayed pulse generator, II-509  
delay relay, ultra-precise long time, II-211  
demodulators, II-158-160, III-149-150  
5V FM, I-233  
12V FM, I-233  
565 SCA, III-150  
AM, II-160  
chroma, with RGB matrix, III-716  
FM, II-161  
FM, narrow-band, carrier detect, II-159  
linear variable differential transformer driver, I-403  
LVDT circuit, III-323-324, III-323  
LVDT driver, II-337  
stereo, II-159  
telemetry, I-229  
demonstration comparator circuit, II-109  
demultiplexer, III-394  
descramblers, II-162  
  gated pulse, II-165  
outband, II-164  
sine wave, II-163  
derived center-channel stereo system, IV-23  
detect-and-hold circuit, peak, I-585  
detection switch, adjustable light, I-362  
detectors (*see also* alarms; control circuits; indicators; monitors; sensors), II-171-178, III-151-162, IV-134-145  
air flow, I-235, II-240-242  
air motion, I-222, III-364  
air-pressure change, IV-144  
amplifier, four quadrant photoconductive, I-359  
angle of rotation, II-283  
bug, III-365  
controller circuit, IV-142  
decibel level, audio, with meter driver, III-154  
direction detector, thermally operated, IV-135  
double-ended limit, I-230, I-233  
duty-cycle, IV-144  
edge, III-157, I-226  
electrostatic, III-337  
envelope detector, III-155  
envelope detector, AM signals, IV-142  
envelope detector, low-level diodes, IV-141  
flame, III-313  
flow, III-202-203  
flow, low-rate thermal, III-203  
fluid and moisture, II-243, II-248, III-204-210, IV-184-191  
frequency limit, II-177  
frequency window, III-777  
frequency, digital, III-158  
frequency-boundary, III-156

- gas, II-278, III-246-253  
 gas and smoke, I-332  
 gas and vapor, II-279  
 ground-fault Hall detector, IV-208-209  
 high-frequency peak, II-175  
 high-speed peak, I-232  
 IC product detector, IV-143  
 infrared, II-289, III-276, IV-224  
 IR, long-range objects, III-273  
 level, II-174  
 level, with hysteresis, I-235  
 lie detector, IV-206  
 light detector, IV-369  
 light interruption, I-364  
 light level, III-316  
 light level, level drop, III-313  
 line-current, optically coupled, III-414  
 liquid level, I-388, I-390  
 low-level video, video IF amplifier, I-687-689  
 low-line loading ring, I-634  
 low-voltage, I-224  
 magnet, permanent-magnet detector, IV-281  
 magnetic transducer, I-233  
 MC1330/MC1352 television IF amplifier, I-688  
 metal, II-350-352, IV-137  
 missing pulse, I-232, III-159  
 moisture, I-442  
 motion, IV-341-346  
 motion, UHF, III-516  
 multiple-input, computer circuit, III-102  
 negative peak, I-234  
 nuclear particle, I-537  
 null, I-148, III-162  
 peak program, III-771  
 peak, II-174, II-175, IV-138, IV-143  
 peak, analog, with digital hold, III-153  
 peak, digital, III-160  
 peak, high-bandwidth, III-161  
 peak, low-drift, III-156  
 peak, negative, I-225  
 peak, op amp, IV-145  
 peak, positive, III-169  
 peak, wide-bandwidth, III-162  
 peak, wide-range, III-152  
 peak voltage, precision, I-226  
 people-detector, infrared-activated, IV-225  
 pH level, probe and, III-501  
 phase, III-440-442  
 phase, 10-bit accuracy, II-176  
 photodiode level, precision, I-365  
 positive peak, I-225, I-235  
 power loss, II-175  
 product, I-223, I-861  
 proximity, I-344, II-135, II-136, IV-341-346  
 pulse coincidence, II-178  
 pulse sequence, II-172  
 pulse-width, out-of-bounds, III-158  
 radar (*see* radar detector)  
 radiation (*see* radiation detector)  
 resistance ratio, II-342  
 rf, II-500, IV-139  
 rf detector probe, IV-433  
 Schmitt trigger, III-153  
 smoke, II-278, III-246-253, IV-140  
 smoke, ionization chamber, I-332-333  
 smoke, operated ionization type, I-596  
 smoke, photoelectric, I-595  
 speech activity on phone lines, II-617, III-615  
 SSB/CW product detectors, IV-139  
 stalled computer-output detector, IV-109  
 static detector, IV-276  
 telephone ring, III-619, IV-564  
 telephone ring, optically interfaced, III-611  
 threshold, precision, III-157  
 tone, 500-Hz, III-154  
 toxic gas, II-280  
 true rms, I-228  
 TV sound IF/FM IF amplifier with quadrature, I-690  
 two-sheets in printer detector, IV-136  
 ultra-low drift peak, I-227  
 undervoltage detector, IV-138  
 video, low-level video IF amplifier, I-687-689  
 voltage level, I-8, II-172  
 weather-alert decoder, IV-140  
 window, I-235, III-776-781, IV-658  
 zero crossing, I-732, I-733, II-173  
 zero crossing, with temperature sensor, I-733  
 deviation meter, IV-303  
 dial pulse indicator, telephone, III-613  
 dialers, telephone  
 pulse-dialing telephone, III-610  
 pulse/tone, single-chip, III-603  
 telephone-line powered repertory, I-633  
 tone-dialing telephone, III-607  
 dice, electronic, I-325, III-245, IV-207  
 differential amplifiers, I-38, III-14  
 high-impedance, I-27, I-354  
 high-input high-impedance, II-19  
 instrumentation, I-347, III-283  
 instrumentation, biomedical, III-282  
 programmable gain, III-507  
 two op amp bridge type, II-83  
 differential analog switch, I-622  
 differential capacitance measurement circuit, II-665  
 differential hold, I-589, II-365  
 differential multiplexers  
 demultiplexer, I-425  
 wide band, I-428  
 differential thermometer, II-661, III-638  
 differential voltage or current alarm, II-3  
 differentiators, I-423  
 negative-edge, I-419  
 positive-edge, I-420  
 digital-capacitance meter, II-94  
 digital-IC, tone probe for testing, II-504  
 digital-frequency meter, III-344  
 digital-logic probe, III-497  
 digital audio tape (DAT)  
 ditherizing circuit, IV-23  
 digital multimeter (DMM)  
 high-resistance-measuring, IV-291  
 digital oscillator, resistance controlled, II-426  
 digital transmission isolator, II-414  
 digital voltmeters (DVM)  
 3.5-digit, common anode display, I-713  
 3.5-digit, full-scale, four-decade, III-761  
 3.75-digit, I-711  
 4.5-digit, III-760  
 4.5-digit, LCD display, I-717  
 auto-calibrate circuit, I-714  
 automatic nulling, I-712  
 interface and temperature sensor, II-647  
 digital-to-analog converters, I-241, II-179-181, III-163-169  
 0-to -5V output, resistor terminated, I-239  
 3-digit, BCD, I-239  
 8-bit, I-240-241  
 8-bit, high-speed, I-240  
 8-bit, output current to voltage, I-243  
 8-bit to 12-bit, two, II-180  
 9-bit, CMOS, III-167  
 10-bit, I-238  
 10-bit, 4-quad, offset binary coding, multiplying, I-241  
 + 10V full scale bipolar, I-242  
 + 10V full scale unipolar, I-244  
 12-bit, binary two's complement, III-166

digital-to-analog converters (*cont.*)  
   12-bit, precision, I-242  
   12-bit, variable step size, II-181  
   14-bit binary, I-237  
   16-bit binary, I-243  
   fast voltage output, I-238  
   high-speed voltage output, I-244  
   multiplying, III-168  
   output amplifier, four-channel, III-165  
   video converter, IV-610-611  
 digitizer, tilt meter, III-644-646  
 dimmers (*see* lights/light-activated and controlled circuits)  
 diode emitter driver, pulsed infrared, II-292  
 diode tester, II-343, III-402  
   go/no-go, I-401  
   zener diodes, I-406  
 diode-matching circuit, IV-280  
 dip meters, I-247, II-182-183  
   basic grid, I-247  
   dual gate IGFET, I-246  
   little dipper, II-183  
   varicap tuned FET, I-246  
 diplexer/mixer, IV-335  
 direction detector, thermally operated, IV-135  
 direction detector decoder, III-144  
 direction finders, IV-146-149  
   compass, digital design, IV-147  
   radio-signal direction finder, IV-148-149  
 direction-of-rotation circuit, III-335  
 directional-signals monitor, auto, III-48  
 disco strobe light, II-610  
 discrete current booster, II-30  
 discrete sequence oscillator, III-421  
 discriminators  
   multiple-aperture, window, III-781  
   pulse amplitude, III-356  
   pulse width, II-227  
   window, III-776-781  
 display circuits, II-184-188, III-170-171  
   3½ digit DVM common anode, II-713  
   60 dB dot mode, II-252  
   audio, LED bar peak program meter, II-254  
   bar-graph indicator, ac signals, II-187  
   brightness control, III-316  
   comparator and, II-105  
   exclamation point, II-254  
   expanded scale meter, dot or bar, II-186  
   LED bar graph driver, II-188  
   LED matrix, two-variable, III-171  
   oscilloscope, eight-channel voltage, III-435  
   dissolver, lamp, solid-state, III-304

distribution circuits, II-35  
 distribution amplifiers  
   audio, I-39, II-39  
   signal, I-39  
 dividers, IV-150-156  
   1 + GHz divide-by- $n$  counter, IV-155  
   7490-divided-by- $n$  circuits, IV-154  
   binary chain, I-258  
   counter, divide-by-odd-number, IV-153  
   divide-by-2-or-3 circuit, IV-154  
   divide-by- $n$  + ½ circuit, IV-156  
   frequency, I-258, II-254, III-213-218  
   frequency divider, clock input, IV-151  
   frequency, decade, I-259  
   frequency, divide-by-1½, III-216  
   frequency, low frequency, II-253  
   frequency divider, programmable, IV-152-153  
   mathematical, one trim, III-326  
   odd-number counter and, III-217  
   pulse, non-integer programmable, II-511, III-226  
 Dolby noise reduction circuits, III-399  
   decode mode, III-401  
   encode mode, III-400  
 door bells/chimes, I-218, I-443, IV-8  
   buzzer, two-door, IV-10  
   musical-tone, IV-522  
   rain alarm, I-443  
   single-chip design, IV-524  
   sliding tone, II-34  
 door-open alarm, II-284, III-46  
   Hall-effect circuit, III-256  
 door opener, III-366  
 dot-expanded scale meter, II-186  
 double-sideband suppressed-carrier modulator, III-377  
 double-sideband suppressed-carrier rf, II-366  
 doublers  
   0 to 1MHz, II-252  
   150 to 300 MHz, I-314  
   audio-frequency doubler, IV-16-17  
   broadband frequency, I-313  
   CRO, oscilloscope, III-439  
   crystal oscillator, I-184  
   frequency, I-313, III-215  
   frequency, digital, III-216  
   frequency, GASFET design, IV-324  
   frequency, single-chip, III-218  
   low-frequency, I-314  
   voltage, III-459  
   voltage, triac-controlled, III-468  
 downbeat-emphasized metronome, III-353-354  
 drivers and drive circuits, I-260, II-189-193, III-172-175, IV-157-160  
 50 ohm, I-262  
 bar-graph driver, transistorized, IV-213  
 BIFET cable, I-264  
 bridge loads, audio circuits, III-35  
 capacitive load, I-263  
 coaxial cable, I-266, I-560  
 coaxial cable, five-transistor pulse boost, II-191  
 coil, current-limiting, III-173  
 CRT deflection yoke, I-265  
 demodulator, linear variable differential transformer, I-403  
 fiber optic, 50-Mb/s, III-178  
 flash slave, I-483  
 glow plug, II-52  
 high-impedance meter, I-265  
 instrumentation meter, II-296  
 lamp, I-380  
 lamp, flip-flop independent, IV-160  
 lamp, low-frequency flasher/relay, I-300  
 lamp, optically coupled, III-413  
 lamp, short-circuit proof, II-310  
 laser diode, high-speed, I-263  
 LED, bar graph, II-188  
 LED, emitter/follower, IV-159  
 line signals, 600-ohm balanced, II-192  
 line, I-262  
 line, 50-ohm transmission, II-192  
 line, full rail excursions in, II-190  
 line-synchronized, III-174  
 load, timing threshold, III-648  
 LVDT demodulator and, II-337, III-323-324  
 meter-driver rf amplifier, 1-MHz, III-545  
 microprocessor triac array, II-410  
 motor drivers (*see* motor control, drivers)  
 multiplexer, high-speed line, I-264  
 neon lamp, I-379  
 op amp power driver, IV-158-159  
 optoisolated, high-voltage, III-482  
 power driver, op amp, IV-158-159  
 pulsed infrared diode emitter, II-292  
 relay, I-264  
 relay, delay and controls closure time, II-530  
 relay, with strobe, I-266  
 RS-232C, low-power, III-175  
 shift register, I-418  
 solenoid, I-265, III-571-573  
 SSB, low distortion 1.6 to 30MHz, II-538  
 stepping motor, II-376  
 totem-pole, with bootstrapping, III-175  
 two-phase motor, I-456

VCO driver, op-amp design, IV-362  
drop-voltage recovery for long-line systems, IV-328  
drum sound effect, II-591  
dual-tone decoding, II-620  
dual-tracking regulator, III-462  
duplex line amplifier, III-616  
duty-cycle detector, IV-144  
duty-cycle meter, IV-275  
duty-cycle monitor, III-329  
duty-cycle multivibrator, 50-percent, III-584  
duty-cycle oscillators  
  50-percent, III-426  
  variable, fixed-frequency, III-422  
dwell meters  
  breaker point, I-102  
  digital, III-45

**E**

eavesdropper, telephone, wireless, III-620  
echo effect, analog delay line, IV-21  
edge detector, I-266, III-157  
EEPROM pulse generator, 5V-powered, III-99  
EKG simulator, three-chip, III-350  
elapsed-time timer, II-680  
electric-fence charger, II-202  
electric-vehicle battery saver, III-67  
electrolytic-capacitor reforming circuit, IV-276  
electrometer, IV-277  
electrometer amplifier, overload protected, II-155  
electronic dice, IV-207  
electronic locks, II-194-197, IV-161-163  
  combination, I-583, II-196  
  digital entry lock, IV-162  
  keyless design, IV-163  
  three-dial combination, II-195  
electronic music, III-360  
electronic roulette, II-276, IV-205  
electronic ship siren, II-576  
electronic switch, push on/off, II-359  
electronic theremin, II-655  
electronic thermometer, II-660  
electronic wake-up call, II-324  
electrostatic detector, III-337  
emergency lantern/flasher, I-308  
emergency light, I-378, IV-250  
emissions analyzer, automotive  
  exhaust, II-51  
emulators, II-198-200  
  capacitance multiplier, II-200  
  JFET ac coupled integrator, II-200  
  resistor multiplier, II-199  
  simulated inductor, II-199

encoders  
  decoder and, III-14  
  telephone handset tone dial, I-634, III-613  
  tone, I-67, I-629  
  tone, two-wire, II-364  
engine tachometer, I-94  
enlarger timer, II-446, III-445  
envelope detectors, III-155  
  AM signals, IV-142  
  low-level diodes, IV-141  
envelope generator/modulator, musical, IV-22  
EPROM, V<sub>pp</sub> generator for, II-114  
equalizers, I-671, IV-18  
  ten-band, graphic, active filter in, II-684  
  ten-band, octave, III-658  
equipment-on reminder, I-121  
exhaust emissions analyzer, II-51  
expanded-scale meters  
  analog, III-774  
  dot or bar, II-186  
expander circuits (*see* compressor/expander circuits)  
extended-play circuit, tape-recorders, III-600  
extractor, square-wave pulse, III-584

**F**

555 timer  
  astable, low duty cycle, II-267  
  beep transformer, III-566  
  integrator to multiply, II-669  
  RC audio oscillator from, II-567  
  square wave generator using, II-595  
fader, audio fader, IV-17  
fail-safe semiconductor alarm, III-6  
fans  
  infrared heat-controlled fan, IV-226  
  speed controller, automatic, III-382  
Fahrenheit thermometer, I-658  
fault monitor, single-supply, III-495  
fax/telephone switch, remote-controlled, IV-552-553  
feedback oscillator, I-67  
fence charger, II-201-203  
  battery-powered, II-202  
  electric, II-202  
  solid-state, II-203  
FET circuits  
  dual-trace scope switch, II-432  
  input amplifier, II-7  
  probe, III-501  
  voltmeter, III-765, III-770  
fiber optics, II-204-207, III-176-181  
  driver, LED, 50-Mb/s, III-178  
  interface for, II-207  
  link, I-268, I-269, I-270, III-179

motor control, dc, II-206  
receiver, 10 MHz, II-205  
receiver, 50-Mb/s, III-181  
receiver, digital, III-178  
receiver, high-sensitivity, 30nw, I-270  
receiver, low-cost, 100-M baud rate, III-180  
receiver, low-sensitivity, 300nW, I-271  
receiver, very-high sensitivity, low speed, 3nW, I-269  
repeater, I-270  
speed control, II-206  
transmitter, III-177  
field disturbance sensor/alarm, II-507  
field-strength meters, II-208-212, III-182-183, IV-164-166  
  1.5-150 MHz, I-275  
adjustable sensitivity indicator, I-274  
high-sensitivity, II-211  
LF or HF, II-212  
microwave, low-cost, I-273  
rf sniffer, II-210  
sensitive, I-274, III-183  
signal-strength meter, IV-166  
transmission indicator, II-211  
tuned, I-276  
UHF fields, IV-165  
untuned, I-276  
filter circuits, II-213-224, III-184-192, IV-167-177  
  active (*see* active filters)  
  antialiasing/sync-compensation, IV-173  
  audio, biquad, III-185  
  audio, tunable, IV-169  
  bandpass (*see* bandpass filters)  
  band-reject, active, II-401  
  biquad, I-292-293  
  biquad, audio, III-185  
  biquad, RC active bandpass, I-285  
bridge filter, twin-T, programmable, II-221  
Butterworth, high-pass, fourth-order, I-280  
Chebyshev (*see* Chebyshev filters)  
CW, razor-sharp, II-219  
full wave rectifier and averaging, I-229  
high-pass (*see* high-pass filters)  
low-pass (*see* low-pass filters)  
networks of, I-291  
noise, dynamic, III-190  
noisy signals, III-188  
notch (*see* notch filters)  
programmable, twin-T bridge, II-221  
rejection, I-283  
ripple suppressor, IV-175

filter circuits (*cont.*)  
 rumble, III-192, IV-175  
 rumble, LM387 in, I-297  
 rumble filter, turntable, IV-170  
 rumble/scratch, III-660  
 Sallen-Key, 500 Hz bandpass, I-291  
 Sallen-key, low-pass, active, IV-177  
 Sallen-Key, low-pass, equal component, I-292  
 Sallen-Key, low-pass, second order, I-289  
 scratch, III-189, IV-175  
 scratch, LM287 in, I-297  
 speech, bandpass, 300 Hz 3kHz, I-295  
 speech filter, second-order, 300-to-3,400 Hz, IV-174  
 speech filter, two-section, 300-to-3,000 Hz, IV-174  
 state-variable, II-215  
 state-variable, multiple outputs, III-190  
 state-variable, second-order, 1kHz, Q/10, I-293  
 state-variable, universal, I-290  
 turbo, glitch free, III-186  
 twin-T bridge filter, II-221  
 Wien-bridge, III-659  
 voltage-controlled, III-187  
 voltage-controlled, 1,000:1 tuning, IV-176  
 fixed power supplies, III-457-477, IV-390-408  
 12-VDC battery-operated 120-VAC, III-464  
 +24 V, 1.5 A supply from +12 V source, IV-401  
 15 V isolated to 2,500 V supply, IV-407  
 audio amplifier supply,  $\pm$  35 V ac, IV-398  
 audio amplifier supply,  $\pm$  35 V, 5 A, mobile, IV-407  
 automotive battery supply,  $\pm$  15 V and 5 V, IV-391  
 auxiliary supply, IV-394  
 bias/reference applications, auxiliary negative dc supply, IV-404  
 bilateral current source, III-469  
 bridge rectifier, IV-398  
 charge pool, III-469  
 charge pump, regulated, IV-396  
 constant-current source, safe, III-472  
 converter, III-470  
 converter, 5V-to-isolated 5V at 20MA, III-474  
 converter, ac-to-dc, IV-395  
 converter, dc-to-dc, 3-to-15 V, IV-400

current sink, 1 mA, IV-402  
 current source, bootstrapped amp, IV-406  
 current source, differential-input, fast-acting, IV-405  
 dc adapter/transceiver, hand-held, III-461  
 dual-tracking regulator, III-462  
 GASFET power supply, IV-405  
 general-purpose, III-465  
 inverter, 12 V input, IV-395  
 isolated feedback, III-460  
 LCD display power supply, IV-392, IV-403  
 linear regulator, low cost, low dropout, III-459  
 low-current source, IV-399  
 low-power inverter, III-466  
 negative rail, GET, with CMOS gates, IV-408  
 negative supply from +12 V source, IV-401  
 negative voltage from positive supply, IV-397  
 output stabilizer, IV-393  
 portable-radio 3 V power supply, IV-397  
 positive and negative voltage power supplies, IV-402  
 pn junction regulator, zener increases voltage output, II-484  
 programmable, III-467  
 rectifier, bridge rectifier, IV-398  
 rectifier, low forward-drop, III-471  
 regulated 1 A, 12 V, IV-401  
 regulated +15V 1-A, III-462  
 regulated -15V 1-A, III-463  
 regulator, 15V slow turn-on, III-477  
 regulator, positive with PNP boost, III-471  
 regulator, positive, with NPN/PNP boost, III-475  
 regulator, switching, 3-A, III-472  
 regulator, switching, high-current inductorless, III-476  
 ripple suppressor, IV-396  
 RTTY machine current supply, IV-400  
 stabilizer, CMOS diode network, IV-406  
 switching, III-458  
 switching, 5- and  $\pm$  12 V, ac-powered, IV-404  
 switching, 50-W off-line, III-473  
 switching, positive and negative voltage, IV-403  
 switching regulator, 3 A, IV-408  
 three-rail, III-466  
 uninterruptible +5V, III-477  
 voltage doubler, III-459  
 voltage doubler, triac-controlled, III-468  
 voltage regulator, 10V, high stability, III-468  
 voltage regulator, 5-V low-dropout, III-461  
 voltage regulator, ac, III-477  
 voltage regulator, negative, III-474  
 voltage-controlled current source/grounded source/load, III-468  
 fixed-frequency generator, III-231  
 flame ignitor, III-362  
 flame monitor, III-313  
 flash/flashbulb circuits (*see* photography-related circuits)  
 flashers and blinkers (*see also* photography-related circuits), I-304, II-225, III-193-210, IV-178-183  
 1.5 V, minimum power, I-308  
 1 kW flip-flop, II-234  
 1A lamp, I-306  
 2 kW, photoelectric control in, II-232  
 3V, I-306  
 ac, III-196  
 alternating, I-307, II-227  
 astable multivibrator, III-196  
 auto, I-299  
 automatic safety, I-302  
 automotive turn signal, sequential, I-109  
 bar display with alarm, I-252  
 barricade, I-299  
 boat, I-299  
 CMOS, III-199  
 dc, adjustable on/off timer, I-305  
 dual LED CMOS, I-302  
 electronic, II-228  
 emergency lantern, I-308  
 fast-action, I-306  
 flash light, 60-W, III-200  
 flicker light, IV-183  
 flip-flop, I-299  
 four-parallel LED, I-307  
 high efficiency parallel circuit, I-308  
 high-voltage, safe, I-307  
 high-power battery operated, II-229  
 incandescent bulb, III-198, I-306  
 LED, IV-181  
 LED, alternating, III-198, III-200  
 LED, control circuit, IV-183  
 LED, multivibrator design, IV-182  
 LED, PUT used in, II-239  
 LED, ring-around, III-194  
 LED flasher, sequential, reversible-direction, IV-182  
 LED, three-year, III-194  
 LED, UJT used in, II-231  
 low-current consumption, II-231

- low-voltage, I-305, II-226  
 miniature transistorized, II-227  
 minimum-component, III-201  
 neon, I-303  
 neon, five-lamp, III-198  
 neon, two-state oscillator, III-200  
 neon, tube, I-304  
 oscillator and, high drive, II-235  
 oscillator and, low frequency, II-234  
 photographic slave-flash trigger, SCR design, IV-380, IV-382  
 photographic time-delay flash trigger, IV-380  
 relay driver, low-frequency lamp, I-300  
 SCR design, II-230, III-197  
 SCR chaser, III-197  
 SCR relaxation, II-230  
 SCR ring counter, III-195  
 sequential, II-233, IV-181  
 sequential, ac, II-238  
 sequencer, pseudorandom simulated, IV-179  
 single-lamp, III-196  
 strobe alarm, IV-180  
 telephone, II-629, IV-558, IV-559, IV-561  
 telephone-message flasher, IV-556  
 transistorized, III-200, I-303  
 transistorized, table of, II-236  
 variable, I-308  
 xenon light, IV-180  
 flashlight finder, I-300  
**flip-flops**  
 astable, with starter, II-239  
 debouncer switch, IV-108  
 flasher circuit, 1 kW, use of, II-234  
 inverter, III-103  
 SCR, II-367  
 wave-shaping circuits, S/R, IV-651  
 flood alarm, I-390, III-206, IV-188  
 flow detectors, II-240-242, III-202-203  
     air, II-242  
     low-rate thermal, III-203  
     thermally based anemometer, II-241  
 flowmeter, liquid, II-248  
 fluid and moisture detectors, I-388, I-390, I-442, II-243-248, III-204-210, IV-184-191  
 acid rain monitor, II-245  
 checker, III-209  
 control, I-388, III-206  
 cryogenic fluid-level sensor, I-386  
 dual, III-207  
 flood alarm, III-206, IV-188  
 fluid-level control, III-205  
 full-bathtub indicator, IV-187  
 full-cup detector for the blind, IV-189  
 indicator, II-244  
 liquid flow meter, II-248  
 liquid-level checker, III-209  
 liquid-level monitor, III-210  
 liquid-level sensor, IV-186  
 liquid-level, dual, III-207  
 moisture detector, IV-188  
 monitor, III-210  
 plant water, II-245, II-248  
 pump controller, single-chip, II-247  
 rain alarm, IV-189  
 rain warning beeper, II-244  
 sensor and control, II-246  
 soil moisture, III-208  
 temperature monitor, II-643, III-206  
 water-leak alarm, IV-190  
 water-level, III-206, IV-186, IV-191  
 water-level, indicator, II-244  
 water-level, sensing and control, II-246, IV-190  
 windshield-washer level, I-107  
 fluid-level controller, I-387, III-205  
 fluorescent display, vacuum, II-185  
 fluorescent lamps  
     high-voltage power supplies, cold-cathode design, IV-411  
     inverter, 8-W, III-306  
 flyback converters, I-211  
     self oscillating, I-170, II-128, III-748  
     voltage, high-efficiency, III-744  
 flyback regulator, off-line, II-481  
 FM transmissions  
     5 V, I-233  
     12 V, I-233  
     clock radio, AM/FM, I-543  
     demodulators, I-544, II-161  
     IF amplifier with quadrature detector, TV sound IF, I-690  
     generators, low-frequency, III-228  
     radio, I-545  
     receivers, carrier-current circuit, III-80  
     receivers, MPX/SCA receiver, III-530  
     receivers, narrow-band, III-532  
     receivers optical receiver/transmitter, 50 kHz, I-361  
     receivers, zero center indicator, I-338  
     snooper, III-680  
     speakers, remote, carrier-current system, I-140  
     squench circuit for AM, I-547  
     stereo demodulation system, I-544  
     transmitters, I-681  
     transmitters, infrared, voice-modulated pulse, IV-228  
     transmitters, multiplex, III-688  
     transmitters, one-transistor, III-687  
     transmitters, optical, 50 kHz center frequency, II-417  
     transmitters, optical receiver/transmitter, 50 kHz, I-361  
     transmitters, optical (PRM), I-367  
     transmitters, voice, III-678  
     tuner, I-231, III-529  
     wireless microphone, III-682, III-685, III-691  
 FM/AM clock radio, I-543  
 fog-light controller, automotive, IV-59  
 foldback current, HV regulator limiting, II-478  
 followers, III-211-212  
     inverting, high-frequency, III-212  
     noninverting, high-frequency, III-212  
     source, photodiode, III-419  
     unity gain, I-27  
     voltage, III-212  
 forward-current booster, III-17  
 free-running multivibrators  
     100 kHz, I-465  
     programmable-frequency, III-235  
 free-running oscillators, I-531  
     square wave, I-615  
 freezer, voltage, III-763  
 freezer-meltdown alarm, I-13  
 frequency comparators, II-109  
     LED, II-110  
 frequency control, telephone, II-623  
 frequency converter, I-159  
 frequency counters, III-340, III-768, IV-300  
     1.2 GHz, III-129  
     10-MHz, III-126  
     100 MHz, period and, II-136  
     low-cost, III-124  
     preamp, III-128  
     precision, I-253  
     tachometer and, I-310  
 frequency detectors, II-177, III-158  
     boundary detector, III-156  
     comparator, III-88  
 frequency dividers, I-258, II-251, II-254  
     clock input, IV-151  
     decade, I-259  
     low, II-253  
     programmable, IV-152-153  
     staircase generator and, I-730  
 frequency-division multiplex stereo decoder, II-169  
 frequency doublers, I-313  
     broadband, I-313  
     GASFET design, IV-324  
 frequency generators, fixed-frequency, III-231  
 frequency indicators, beat, I-336  
 frequency inverters, variable frequency, complementary output, III-297

- frequency meters, II-249-250, IV-282  
     audio, I-311  
     linear, I-310  
     low cost, II-250  
     power, II-250  
     power-line, I-311  
 frequency multipliers/dividers, II-251,  
     III-213-218  
     counter, odd-number, III-217  
     divide-by- $1\frac{1}{2}$ , III-216  
     doubler, III-215  
     doubler, digital, III-216  
     doubler, to 1MHz, II-252  
     doubler, single-chip, III-218  
     nonselective tripler, II-252  
     pulse-width, III-214  
 frequency-boundary detector, III-156  
 frequency-detecting comparator, III-88  
 frequency oscillator, tunable, II-425  
 frequency-ratio monitoring circuit, IV-  
     202  
 frequency-shift key (FSK) communica-  
     tions  
     data receiver, III-533  
     decoder, 10.8 MHz, I-214  
     generator, low-cost design, III-227  
     keying circuits, IV-245  
 frequency synthesizer, programmable  
     voltage controlled, II-265  
 frequency-to-voltage converter, I-318,  
     II-255-257, III-219-220  
     dc, 10kHz, I-316  
     digital meter, I-317  
     optocoupler input, IV-193  
     sample-and-hold circuit, IV-194  
     single-supply design, IV-195  
     zener regulated, I-317  
 fuel gauge, automotive, IV-46  
 full-wave rectifiers, IV-328, IV-650  
     absolute value, II-528  
     precision, I-234, III-537  
 function generators (*see also* burst  
     generators; sound generators;  
     waveform generators), I-729, II-  
     271, III-221-242, III-258-274, IV-  
     196-202  
     555 astable, low duty cycle, II-267  
     astable multivibrator, II-269, III-233,  
     III-238  
     astable multivibrator, op amp, III-224  
     astable multivibrator, programmable-  
         frequency, III-237  
     audio function generator, IV-197  
     clock generator, I-193  
     clock generator/oscillator, I-615  
     complementary signals, XOR gate,  
         III-226  
     DAC controlled, I-722  
     emitter-coupled RC oscillator, II-266  
     fixed-frequency, III-231  
     FM, low-frequency, III-228  
     free-running multivibrator, program-  
         mable-frequency, III-235  
     frequency-ratio monitoring circuit,  
         IV-202  
     frequency synthesizer, programmable  
         voltage controlled, II-265  
     FSK, low-cost, III-227  
     harmonics, III-228  
     linear ramp, II-270  
     linear triangle/square wave VCO, II-  
         263  
     monostable operation, III-235  
     monostable multivibrator, III-230  
     monostable multivibrator, linear-  
         ramp, III-237  
     monostable multivibrator, positive-  
         triggered, III-229  
     monostable multivibrator, video  
         amplifier and comparator, II-268  
     multiplying pulse width circuit, II-264  
     multivibrator, low-frequency, III-237  
     multivibrator, single-supply, III-232  
     nonlinear potentiometer outputs, IV-  
         198  
     one-shot, precision, III-222  
     one-shot, retriggerable, III-238  
     oscillator/amplifier, wide frequency  
         range, II-262  
     potentiometer-position V/F con-  
         verter, IV-200  
     precise wave, II-274  
     programmed, I-724  
     pulse divider, noninteger, program-  
         mable, III-226  
     pulse train, IV-202  
     pulse, 2-ohm, III-231  
     quad op amp, four simultaneous  
         synchronized waveform, II-259  
     ramp, variable reset level, II-267  
     sawtooth and pulse, III-241  
     signal, two-function, III-234  
     sine/cosine (0.1-10 kHz), II-260  
     single supply, II-273  
     sine-wave/square-wave oscillator,  
         tunable, III-232  
     single-control, III-238  
     timebase, 1 Hz, for readout and  
         counter applications, IV-201  
     time-delay generator, I-217-218  
     triangle-square wave, programmable,  
         III-225  
     triangle-wave, III-234  
     triangle-wave timer, linear, III-222  
     triangle-wave/square-wave, III-239  
     triangle-wave/square-wave, precision,  
         III-242  
     triangle-wave/square-wave, wide-  
         range, III-242  
     tunable, wide-range, III-241  
     UJT monostable circuit insensitive to  
         changing bias voltage, II-268  
     variable duty cycle timer output, III-  
         240  
     voltage controlled high-speed one  
         shot, II-266  
     waveform, II-269, II-272  
     waveform, four-output, III-223  
     white noise generator, IV-201  
 fuzz box, II-593  
 furnace exhaust gas/smoke detector,  
     temp monitor/low supply detection,  
         III-248  
 fuzz box, III-575  
 fuzz sound effect, II-590

## G

- GaAsFET amplifier, power, with single  
     supply, II-10  
 gain block, video, III-712  
 gain control, automatic, audio, II-17  
 gain-controlled stereo amplifier, II-9,  
     III-34  
 game feeder controller, II-360  
 game roller, I-326  
 games, II-275-277, III-243-245, IV-  
     203-207  
     coin flipper, III-244  
     electronic dice, III-245, IV-207  
     electronic roulette, II-276, IV-205  
     lie detector, II-277, IV-206  
     reaction timer, IV-204  
     run-down clock/sound generator, IV-  
         205  
     Wheel-of-Fortune, IV-206  
     who's first, III-244  
 garage stop light, II-53  
 gas analyzer, II-281  
 gas/smoke detectors (*see also* smoke  
     alarms and detectors), II-278-279,  
     III-246-253, III-246  
     analyzer and, II-281  
     furnace exhaust, temp monitor/low-  
         supply detection, III-248  
     methane concentration, linearized  
         output, III-250  
     toxic, II-280  
     SCR, III-251  
     smoke/gas/vapor detector, III-250  
 GASFET fixed power supplies, IV-405  
 gated oscillator, last-cycle completing,  
     III-427  
 gated-pulse descrambler, II-165  
 gates  
     programmable, I-394  
     XOR gate, IV-107

geiger counters, I-536-537  
     high-voltage supply, II-489  
     pocket-sized, II-514  
     gel cell charger, II-66  
     generators, electric-power  
         corona-wind generator, IV-633  
         high-voltage generator, IV-413  
         high-voltage generator, battery-powered, III-482  
         high-voltage generator, capacitor-discharge, III-485  
         high-voltage generator, dc voltage, III-481  
         high-voltage generator, negative-ions, IV-634  
         high-voltage generator, ultra-high voltages, II-488  
     glitch-detector, comparator, II-107  
     glow plug driver, II-52  
     graphic equalizer, ten-band, active filter in, II-684  
     grid-dip meter, bandswitched, IV-298  
     ground tester, II-345  
     ground-fault Hall detector, IV-208-209  
     ground-noise probe, battery-powered, III-500  
     guitars  
         compressor, sound-effect circuit, IV-519  
         matching audio signal amplifiers, IV-38  
         treble boost for, II-683  
         tuner, II-362  
     gun, laser, visible red and continuous, III-310

## H

half-duplex information transmission link, III-679  
     half-flash analog-to-digital converters, III-26  
     half-wave ac phase-controlled circuit, I-377  
     half-wave rectifiers, I-230, III-528, IV-325  
         fast, I-228  
     Hall-effect circuits, II-282-284, III-254-258  
         angle of rotation detector, II-283  
         compass, III-258  
         current monitor, III-255, IV-284  
         door open alarm, II-284  
         ground-fault detector, IV-208-209  
         security door-ajar alarm, III-256  
         switches using, III-257, IV-539  
     halogen lamps, dimmer for, III-300  
     handtalkies, I-19  
         two-meter preamplifier for, I-19

hands-free telephone, III-605  
     hands-off intercom, III-291  
     handset encoder, telephone, III-613  
     harmonic generators, I-24, III-228, IV-649  
     Hartley oscillator, I-571  
     HC-based oscillators, III-423  
     HCU/HTC-based oscillator, III-426  
     headlight alarm, III-52  
     headlight delay unit, I-107, III-49  
     headlight dimmer, II-63  
     headphones, amplifier for, II-43  
     heart rate monitor, II-348, II-349  
     heat sniffer, electronic, III-627  
     heater, induction, ultrasonic, 120-KHz 500-W, III-704  
     heater controls, I-639  
         element controller, II-642  
         protector circuit, servo-sensed, III-624  
         temperature sensitive, I-640  
     hee-haw siren, II-578, III-565  
     hi-fi circuits  
         compacker, II-12  
         compressor, pre-emphasis and, III-93  
         expander, II-13  
         expander, de-emphasis, III-95  
         tone control circuit, high Z input, I-676  
     high-frequency amplifiers, III-259-265  
         29-MHz, III-262  
         3-30 MHz, 80-W, 12.5-13.6 V, III-261  
         amateur radio, linear, 2-30 MHz 140-W, III-260  
         noninverting, 28-dB, III-263  
         RF, broadcast band, III-264  
         UHF, wideband with high-performance FETs, III-264  
         wideband, hybrid, 500 kHz-1GHz, III-265  
         wideband, miniature, III-265  
     high-frequency oscillator, III-426  
     crystal, I-175, II-148  
     high-frequency peak detector, II-175  
     high-frequency signal generator, II-150  
     high-input-high-impedance amplifiers, II-19, II-44  
     high-pass filters, I-296  
         active, I-296  
         active, second-order, I-297  
         Butterworth, fourth-order, I-280  
         Chebyshev, fourth-order, III-191  
         fourth-order, 100-Hz, IV-174  
         second-order, 100-Hz, IV-175  
         sixth-order elliptical, III-191  
         wideband two-pole, II-215  
     high-voltage power supplies (*see also* generators, electrical power), II-

487-490, III-486, IV-409-413  
     10,000 V dc supply, IV-633  
     arc-jet power supply, starting circuit, III-479  
     battery-powered generator, III-482  
     bucking regulator, III-481  
     dc generator, III-481  
     fluorescent-lamp supply, cold-cathode design, IV-411  
     geiger counter supply, II-489  
     generators (*see* generators, electrical power)  
     inverter, III-484  
     inverter, 40 W, 120 V ac, IV-410-411  
     negative-ion generator, IV-634  
     optoisolated driver, III-482  
     preregulated, III-480  
     pulse supply, IV-412  
     regulator, III-485  
     regulator, foldback-current limiting, II-478  
     solid-state, remote adjustable, III-486  
     strobe power supply, IV-413  
     tube amplifier, high-volt isolation, IV-426  
     ultra high-voltage generator, II-488  
     hobby circuits (*see* model and hobby circuits)  
     hold button, telephone, 612, II-628  
     home security systems, IV-87  
         lights-on warning, IV-250  
         monitor, I-6  
     horn, auto, electronic, III-50  
     hot-wire anemometer, III-342  
     hour/time delay sampling circuit, II-668  
     Howland current pump, II-648  
     humidity sensor, II-285-287, III-266-267  
     HV regulator, foldback current limiting, II-478  
     hybrid power amplifier, III-455

## I

IC product detectors, IV-143  
     IC timer, crystal-stabilized, subharmonic frequencies for, II-151  
     ice alarm, automotive, II-57  
     ice formation alarm, II-58  
     ice warning and lights reminder, I-106  
     ICOM IC-2A battery charger, II-65  
     IF amplifiers, I-690, IV-459  
         AGC system, IV-458  
         AGC system, CA3028-amplifiers, IV-458  
     preamp, IV-460  
     preamp, 30-MHz, IV-460  
     receiver, IV-459  
     two-stage, 60 MHz, I-563

ignition circuit, electronic, automotive, IV-65  
 ignition cut-off circuit, automotive, IV-53  
 ignition substitute, automotive, III-41  
 ignition system, capacitor discharger, I-103  
 ignition timing light, II-60  
 ignitor, III-362  
 illumination stabilizer, machine vision, II-306  
 image canceller, III-358  
 immobilizer, II-50  
 impedance converter, high to low, I-41  
 incandescent light flasher, III-198  
 indicators (*see also* alarms; control circuits; detectors; monitors; sensors), III-268-270, IV-210-218  
 ac-current indicator, IV-290  
 ac-power indicator, LED display, IV-214  
 ac/dc indicator, IV-214  
 alarm and, I-337  
 automotive-temperature indicator, PTC thermistor, II-56  
 balance indicator, IV-215  
 bar-graph driver, transistorized, IV-213  
 battery charge/discharge, I-122  
 battery condition, I-121  
 battery level, I-124  
 battery threshold, I-124  
 battery voltage, solid-state, I-120  
 beat frequency, I-336  
 CW offset indicator, IV-213  
 dial pulse, III-613  
 field-strength (*see* field-strength meters)  
 in-use indicator, telephone, II-629  
 infrared detector, low-noise, II-289  
 lamp driver, optically coupled, III-413  
 level, three-step, I-336  
 low-battery, I-124  
 low-voltage, III-769  
 mains-failure indicator, IV-216  
 On indicator, IV-217  
 on-the-air, III-270  
 overspeed, I-108  
 overvoltage/undervoltage, I-150  
 peak level, I-402  
 phase sequence, I-476  
 receiver-signal alarm, III-270  
 rf output, IV-299  
 rf-actuated relay, III-270  
 simulated, I-417  
 sound sensor, IV-218  
 stereo-reception, III-269  
 SWR warning, I-22  
 telephone, in-use indicator, II-629, IV-560, IV-563

telephone, off-hook, I-633  
 temperature indicator, IV-570  
 transmitter-output indicator, IV-218  
 undervoltage, battery operated equipment, I-123  
 visual modulation, I-430  
 visual level, III-269  
 voltage, III-758-772  
 voltage, visible, I-338, III-772  
 voltage-level, I-718, III-759  
 voltage-level, five step, I-337  
 voltage-level, ten-step, I-335  
 volume indicator, audio amplifier, IV-212  
 VU meter, LED display, IV-211  
 zero center, FM receivers, I-338  
 in-use indicator, telephone, II-629  
 induction heater, ultrasonic, 120-KHz 500-W, III-704  
 inductors  
     active, I-417  
     simulated, II-199  
 infrared circuits, II-288-292, III-271-277, IV-219-228  
 data link, I-341  
 detector, III-276, IV-224  
 detector, low-noise, II-289  
 emitter drive, pulsed, II-292  
 fan controller, IV-226  
 laser rifle, invisible pulsed, II-291  
 loudspeaker link, remote, I-343  
 low-noise detector for, II-289  
 object detector, long-range, III-273  
 people-detector, IV-225  
 proximity switch, infrared-activated, IV-345  
 receivers, I-342, II-292, III-274, IV-220-221  
 receivers, remote-control, I-342  
 remote controller, IV-224  
 remote-control tester, IV-228  
 remote-extender, IV-227  
 transmitter, I-343, II-289, II-290, III-274, III-276, III-277, IV-226-227  
 transmitter, digital, III-275  
 transmitter, remote-control, I-342  
 transmitter, voice-modulated pulse FM, IV-228  
 wireless speaker system, III-272  
 injectors  
     three-in-one set: logic probe, signal tracer, injector, IV-429  
 injector-tracers, I-522  
     single, II-500  
     signal, I-521  
 input selectors, audio, low distortion, II-38  
 input/output buffer, analog multiplexers, III-11  
 instrumentation amplifiers, I-346, I-348, I-349, I-352, II-293-295, III-278-284, IV-229-234  
 ± 100 V common mode range, III-294  
 current collector head amplifier, II-295  
 differential, I-347, I-354, III-283  
 differential, biomedical, III-282  
 differential, high-gain, I-353  
 differential, input, I-354  
 differential, variable gain, I-349  
 extended common-mode design, IV-234  
 high-impedance low drift, I-355  
 high-speed, I-354  
 low-drift/low-noise dc amplifier, IV-232  
 low-signal level/high-impedance, I-350  
 low-power, III-284  
 meter driver, II-296  
 preamp, oscilloscope, IV-230-231  
 re-amp, thermocouple, III-283  
 precision FET input, I-355  
 saturated standard cell amplifier, II-296  
 strain gauge, III-280  
 triple op amp, I-347  
 ultra-precision, III-279  
 variable gain, differential input, I-349  
 very high-impedance, I-354  
 wideband, III-281  
 instrumentation meter driver, II-296  
 integrators, II-297-300, III-285-286  
     active, inverting buffer, II-299  
     JFET ac coupled, II-200  
     gamma ray pulse, I-536  
     long time, II-300  
     low drift, I-423  
     noninverting, improved, II-298  
     photocurrent, II-326  
     programmable reset level, III-286  
     ramp generator, initial condition reset, III-527  
     resettable, III-286  
 intercoms, I-415, II-301-303, III-287-292  
     bidirectional, III-290  
     carrier current, I-146  
     hands-off, III-291  
     party-line, II-303  
     pocket pager, III-288  
     telephone-intercoms, IV-557  
     two-way, III-292  
     two-wire design, IV-235-237  
 interfaces (*see also* computer circuits), IV-238-242  
     680x, 650x, 8080 families, III-98

cassette-to-telephone, III-618  
 CPU interface, one-shot design, IV-239  
 DVM, temperature sensor and, II-647  
 FET driver, low-level power FET, IV-241  
 fiber optic, II-207  
 keyboard matrix interface, IV-240  
 logic-level translators, IV-242  
 optical sensor-to-TTL, III-314  
 process control, precision, I-30  
 tape recorder, II-614  
 interrupter, ground fault, I-580  
 interval timer, low-power, microprocessor programmable, II-678  
 inverters, III-293-298  
     dc-to-dc/ac, I-208  
     fast, I-422  
     fixed power supplies, 12 V input, IV-395  
     flip-flop, III-103  
     fluorescent lamp, 8-W, III-306  
     high-voltage, III-484  
     high-voltage power supplies, 40 W, 120 V ac, IV-410-411  
     low-power, fixed power supplies, III-466  
     on/off switch, III-594  
     picture, video circuits, III-722  
     power, III-298  
     power, 12 VDC-to-117 VAC at 60 Hz, III-294  
     power, medium, III-296  
     power, MOSFET, III-295  
     rectifier/inverter, programmable op-amp design, IV-364  
     ultrasonic, arc welding, 20 KHz, III-700  
     variable frequency, complementary output, III-297  
     voltage, precision, III-298  
 inverting amplifiers, I-41-42, III-14  
     balancing circuit in, I-33  
     low power, digitally selectable gain, II-333  
     power amplifier, I-79  
     programmable-gain, III-505  
     unity gain amplifier, I-80  
     wideband unity gain, I-35  
 inverting buffers, active integrator using, II-299  
 inverting comparators, hysteresis in, I-154  
 inverting followers, high-frequency, III-212  
 isolated feedback power supply, III-460  
 isolation amplifiers  
     capacitive load, I-34

level shifter, I-348  
 medical telemetry, I-352  
 rf, II-547  
 isolation and zero voltage switching logic, II-415  
 isolators  
     analog data-signal transmission, IV-133  
     digital transmission, II-414  
     stimulus, III-351

## J

JFET ac coupled integrator, III-200

## K

Kelvin thermometer, I-655  
     zero adjust, III-661  
 keying circuits, IV-243-245  
     automatic operation, II-15  
     automatic TTL morse code, I-25  
     CW keyer, IV-244  
     electronic, I-20  
     frequency-shift keyer, IV-245  
     negative key line keyer, IV-244

## L

lamp-control circuits (*see* lights/light-activated and controlled circuits)  
 laser circuits (*see also* lights/light-activated and controlled circuits; optical circuits), II-313-317, III-309-311  
 diode sensor, IV-321  
 discharge current stabilizer, II-316  
 gun, visible red, III-310  
 light detector, II-314  
 power supply, IV-636  
 pulsers, laser diode, III-311, I-416  
 receiver, IV-368  
 rifle, invisible IR pulsed, II-291  
 latches  
     12-V, solenoid driver, III-572  
     comparator and, III-88  
 latching relays, dc, optically coupled, III-417  
 latching switches  
     double touchbutton, I-138  
     SCR-replacing, III-593  
 LCD display, fixed power supply, IV-392, IV-403  
 lead-acid batteries  
     battery chargers, III-55  
     life-extender and charger, IV-72  
     low-battery detector, III-56  
 leading-edge delay circuit, III-147  
 LED circuits  
     ac-power indicator, IV-214

alternating flasher, III-198, III-200  
 bar graph driver, II-188  
 driver, emitter/follower, IV-159  
 flasher, IV-181  
 flasher, control circuit, IV-183  
 flasher, multivibrator design, IV-182  
 flasher, PUT, II-239  
 flasher, sequential, reversible-direction, IV-182  
 flasher, UJT, II-231  
 frequency comparator, II-110  
 matrix display, two-variable, III-171  
 millivoltmeter readout, IV-294  
 multiplexed common-cathode display ADC, III-764  
 panel meter, III-347  
 peakmeter, III-333  
 ring-around flasher, III-194  
 RS-232C, computer circuit, III-103  
 three-year flasher, III-194  
 voltmeter, IV-286  
 VU meter, IV-211  
 level, electronic, II-666, IV-329  
 level controllers/indicators/monitors, II-174  
 alarm, water, I-389  
 audio, automatic, II-20  
 cryogenic fluid, I-386  
 fluid, I-387  
 hysteresis in, I-235  
 liquid, I-388, I-389, I-390  
 meter, LED bar/dot, I-251  
 peak, I-402  
 sound, I-403  
 three-step, I-336  
 visual, III-269  
 warning, audio output, low, I-391  
 warning, high-level, I-387  
 water, I-389  
 level shifter, negative-to-positive supply, I-394  
 LF or HF field strength meter, II-212  
 LF receiver, IV-451  
 lie detector, II-277, IV-206  
 lights/light-activated and controlled circuits (*see also* laser circuits; optical circuits), II-304-312, II-318-331, III-312-319  
 860 W limited-range light control, I-376  
 ambient-light cancellation circuit, II-328  
 audio oscillator, light-sensitive, III-315  
 battery-powered light, capacitance operated, I-131  
 brightness control, lighted displays, III-316  
 carport light, automatic, II-308

- lights/light-activated and controlled circuits (*cont.*)  
 chaser lights, sequential activation, IV-251, IV-252  
 Christmas light driver, IV-254  
 complementary, I-372  
 controller, IV-252  
 cross fader, II-312  
 detectors, detection switch, adjustable, I-362  
 dimmer, I-369, II-309, IV-247, IV-249  
 dimmer, 800 W, II-309  
 dimmer, dc lamp, II-307  
 dimmer, four-quadrant, IV-248-249  
 dimmer, halogen lamps, III-300  
 dimmer, headlight, II-57, II-63  
 dimmer, low-cost, I-373  
 dimmer, soft-start, 800-W, I-376, III-304  
 dimmer, tandem, II-312  
 dimmer, triac, I-375, II-310, III-303  
 dissolver, solid-state, III-304  
 drivers, I-380  
 drivers, flip-flop independent design, IV-160  
 drivers, indicator-lamps, optical coupling, III-413  
 drivers, neon lamps, I-379  
 drivers, short-circuit-proof, II-310  
 emergency light, I-378, I-581, II-320, III-317, III-415, IV-250  
 flame monitor, III-313  
 fluorescent-lamp high-voltage power supplies, cold-cathode design, IV-411  
 indicator-lamp driver, optically coupled, III-413  
 interruption detector, I-364  
 inverter, fluorescent, 8-W, III-306  
 level controller, I-380  
 level detector, I-367, III-316  
 level detector, low-light level drop detector, III-313  
 life-extender for lightbulbs, III-302  
 light-bulb changer, "automatic" design, IV-253  
 lights-on warning, IV-58, IV-62, IV-250  
 light-seeking robot, II-325  
 logic circuit, I-393  
 machine vision illumination stabilizer, II-306  
 marker light, III-317  
 meters, light-meters, I-382, I-383  
 modulator, III-302  
 monostable photocell, self-adjust trigger, II-329  
 mooring light, automatic, II-323  
 night light, automatic, I-360, III-306  
 night light, telephone-controlled, III-604  
 on/off relay, I-366  
 on/off reminder, automotive lights, I-109  
 on/off reminder, with ice alarm, I-106  
 one-shot timer, III-317  
 phase control, II-303, II-305  
 photo alarm, II-319  
 photocell, monostable, self-adjust trigger, II-329  
 photocurrent integrator, II-326  
 photodiode sensor amplifier, II-324  
 photoelectric controller, IV-369  
 photoelectric switches, II-321, II-326, III-319  
 projector-lamp voltage regulator, II-305  
 power outage light, line-operated, III-415  
 pulse-generation interruption, I-357  
 relay, on/off, I-366  
 remote-controller, I-370  
 robot, eyes, II-327  
 robot, light-seeking robot, II-325  
 sensor, ambient-light ignoring, III-413  
 sensor, back-biased GaAs LED, II-321  
 sensor, logarithmic, I-366  
 sensor, optical sensor-to-TTL interface, III-314  
 sequencer, pseudorandom, III-301  
 short-circuit proof lamp driver, II-310  
 signal conditioner, photodiode design, II-330  
 sound-controlled lights, I-609  
 speed controller, IV-247  
 strobe, high-voltage power supplies, IV-413  
 strobe, variable, III-589-590  
 sun tracker, III-318  
 switch, II-320, III-314  
 switch, capacitance switch, I-132  
 switch, light-controlled, II-320, III-314  
 switch, photoelectric, II-321, II-326, III-319  
 switch, solar triggered, III-318  
 switch, zero-point triac, II-311  
 tarry light, I-579  
 telephone in-use light, II-625  
 three-way light control, IV-251  
 touch lamp, three-way, IV-247  
 triac switch, inductive load, IV-253  
 turn-off circuit, SCR capacitor design, IV-254  
 twilight-triggered circuit, II-322  
 voltage regulator for projection lamp, II-305  
 wake-up call light, II-324  
 warning lights, II-320, III-317  
 light-seeking robot, II-325  
 lights-on warning, automotive, II-55, III-42  
 limit alarm, high/low, I-151  
 limit comparator, I-156, III-106  
 double ended, I-156, II-105  
 limit detectors  
 double ended, I-230, I-233  
 micropower double ended, I-155  
 limiters, III-320-322, IV-255-257  
 audio, low distortion, II-15  
 audio clipper/limiter, IV-355  
 dynamic noise reduction circuit, III-321  
 hold-current, solenoid driver, III-573  
 noise, III-321, II-395  
 one-zener design, IV-257  
 output, III-322  
 power-consumption, III-572  
 transmit-time limiter/timer, IV-580  
 voltage limiter, adjustable, IV-256  
 line amplifier  
 duplex, telephone, III-616  
 universal design, IV-39  
 line drivers  
 50-ohm transmission, II-192  
 600-ohm balanced, II-192  
 full rail excursions, II-190  
 high output 600-ohm, II-193  
 video amplifier, III-710  
 line-dropout detector, II-98  
 line-frequency square wave generator, II-599  
 line receivers  
 digital data, III-534  
 low-cost, III-532  
 line-sync, noise immune 60 Hz, II-367  
 line-current detector, optically coupled, III-414  
 line-current monitor, III-341  
 line-hum touch switch, III-664  
 line-synchronized driver circuit, III-174  
 line-voltage announcer, ac, III-730  
 line-voltage monitor, III-511  
 linear amplifiers  
 2-30MHz, 140W PEP amateur radio, I-555  
 100 W PEP 420-450 MHz push-pull, I-554  
 160 W PEP broadband, I-556  
 amateur radio, 2-30 MHz 140-W, III-260  
 CMOS inverter, II-11  
 rf amplifiers, 6-m, 100 W, IV-480-481  
 rf amplifiers, 903 MHz, IV-484-485  
 rf amplifiers, ATV, 10-to-15 W, IV-481

linear couplers  
     analog, II-413  
     analog ac, II-412  
     dc, II-411  
 linear IC siren, III-564  
 linear optocoupler, instrumentation, II-417  
 linear ramp generator, II-270  
 linear regulators  
     fixed power supply, low dropout low cost, III-459  
     radiation-hardened 125A, II-468  
 link, fiber optic, III-179  
 liquid flowmeter, II-248  
 liquid-level detectors (*see* fluid and moisture detectors)  
 lithium batteries  
     charger for, II-67  
     state of charge indicator for, II-78  
 little dipper dip meter, II-183  
 locator, lo-parts treasure, I-409  
 locks, electronic, II-194-197, IV-161-163  
     combination, I-583, II-196  
     digital entry lock, IV-162  
     keyless design, IV-163  
     three-dial combination, II-195  
 locomotive whistle, II-589  
 logarithmic amplifiers, I-29, I-35, II-8  
     dc to video, I-38  
     log-ratio amplifier, I-42  
 logarithmic converter, fast, I-169  
 logarithmic light sensor, I-366  
 logarithmic sweep VCO, III-738  
 logic/logic circuits  
     audible pulses, II-345  
     four-state, single LED indicator, II-361  
     isolation and zero voltage switching, II-415  
     light-activated, I-393  
     line monitor, III-108  
     overvoltage protection, I-517  
     probes (*see* logic probes)  
     pulse generator for logic-troubleshooting, IV-436  
     pulser, III-520  
     signals, long delay line for, III-107  
     tester, audible, III-343  
     tester, TTL, I-527  
     translators, logic-level translators, IV-242  
 logic amplifiers, II-332-335  
     low power binary, to 10n gain low frequency, II-333  
     low power inverting, digitally selectable gain, II-333  
     low power noninverting, digitally selectable input and gain, II-334

precision, digitally programmable  
     input and gain, II-335  
     programmable amplifier, II-334  
 logic converter, TTL to MOS, I-170  
 logic level shifter, negative-to-positive supply, I-394  
 logic probes, I-520, I-525, I-526, IV-430-431, IV-434  
     CMOS, I-523, I-526, III-499  
     digital, III-497  
     four-way operation, IV-432  
     memory-tester, installed, I-525  
     single-IC design, IV-433  
     three-in-one test set: probe, signal tracer, injector, IV-429  
 long-duration timer, PUT, II-675  
 long-range object detector, III-273  
 long-term electronic timer, II-672  
 long-time integrator, II-300  
 long-time timer, III-653  
 loop antenna, 3.5 MHz, IV-12-13  
 loop transmitter, remote sensors, III-70  
 loop-thru video amplifier, IV-616  
 loudness amplifier, II-46  
 loudness control, balance amplifier with, II-395  
 loudspeaker coupling circuit, I-78  
 low-current measurement system, III-345  
 low-distortion audio limiter, II-15  
 low-distortion input selector for audio use, II-38  
 low-distortion low level amplitude modulator, II-370  
 low-distortion sine wave oscillator, II-561  
 low-frequency oscillators, III-428  
     crystal, I-184, II-146  
     oscillator/flasher, II-234  
     Pierce oscillator, III-133  
     TTL oscillator, II-595  
 low-pass filters, I-287  
     active, digitally selected break frequency, II-216  
     Chebyshev, fifth-order, multi-feedback, II-219  
     pole-active, I-295  
     fast-response, fast settling, IV-168-169  
     fast-settling, precision, II-220  
     precision, fast settling, II-220  
     Sallen-Key, 10 kHz, I-279  
     Sallen-key, active, IV-177  
     Sallen-Key, equal component, I-292  
     low-voltage alarm/indicator, II-493, III-769  
     low-voltage power disconnector, II-97  
     LVDT circuits, II-336-339, III-323-324

driver demodulator, II-337  
 signal conditioner, II-338

## M

machine vision, illumination stabilizer for, II-306  
 magnetic current low-power sensor, III-341  
 magnetic phono preamplifier, I-91  
 magnetic pickup phone preamplifier, I-89  
 magnetometer, II-341  
 magnets, permanent-magnet detector, IV-281  
 mains-failure indicator, IV-216  
 marker generator, III-138  
 marker light, III-317  
 mathematical circuits, III-325-327, IV-258-263  
     adder, III-327  
     adder, binary, fast-action, IV-260-261  
     divide/multiply, one trim, III-326  
     multiplier, precise commutating amp, IV-262-263  
     slope integrator, programmable, IV-259  
     subtractor, III-327  
 measurement/test circuits (*see also* detectors; indicators; meters), II-340, III-328-348, IV-264-311  
     3-in-1 test set, III-330  
     absolute-value circuit, IV-274  
     acoustic-sound receiver, IV-311  
     acoustic-sound transmitter, IV-311  
     anemometer/, hot-wire, III-342  
     audible logic tester, III-343  
     automotive electrical tester, IV-45  
     B-field measure, IV-272  
     barometer, IV-273  
     battery internal-resistance, IV-74  
     battery tester, IV-78  
     battery tester, ni-cad batteries, IV-79  
     breath alert alcohol tester, III-359  
     broadband ac active rectifier, IV-271  
     cable tester, III-539  
     capacitor tester, IV-265  
     capacitor-ESR measurer, IV-279  
     continuity tester, I-550, I-551, II-342, III-345, III-540, IV-287, IV-289, IV-296  
     continuity tester, latching, IV-295  
     crystal tester, II-151  
     current indicator, ac current, IV-290  
     current monitor, Hall-sensor, IV-284  
     current monitor/alarm, III-338  
     current sensor, high-gain, IV-291  
     deviation meter, IV-303  
     digital frequency meter, III-344

measurement/test circuits (*cont.*)  
   digital multimeter (DMM), high-resistance measuring, IV-291  
   diode, I-402, II-343  
   direction-of-rotation circuit, III-335  
   diode-curve tracer, IV-274  
   diode-matching circuit, IV-280  
   duty-cycle measurer, IV-265  
   duty-cycle meter, IV-275  
   duty-cycle monitor, III-329  
   E, T, and R measurement/test circuits, IV-283-296  
   electrolytic-capacitor reforming circuit, IV-276  
   electrometer, IV-277  
   electrostatic detector, III-337  
   filter analyzer, audio filters, IV-309  
   frequency checker, crystal oscillator, precision design, IV-301  
   frequency counter, III-340, IV-300  
   frequency meter, IV-282  
   frequency shift keyer tone generator, I-723  
   go/no-go, diode, I-401  
   go/no-go, dual-limit, I-157  
   grid-dip meter, bandswitched, IV-298  
   ground, I-580, II-345  
   injectors, IV-429  
   high-frequency and rf, IV-297-303  
   LC checker, III-334  
   LED panel meter, III-347  
   line-current monitor, III-341  
   logic probes (*see* logic probes)  
   logic-pulses, slow pulse test, II-345  
   low-current measurement, III-345  
   low-ohms adapter, IV-290  
   magnet, permanent-magnet detector, IV-281  
   magnetic current sensor, low-power, III-341  
   magnetic-field meter, IV-266  
   magnetometer, II-341  
   measuring gauge, linear variable differential transformer, I-404  
   meter tester, IV-270  
   microammeter, dc, four-range, IV-292  
   microfarad counter, IV-275  
   millivoltmeter, dc, IV-295  
   millivoltmeter, four-range, IV-289  
   millivoltmeter, LED readout, IV-294  
   modulation monitor, IV-299  
   mono audio-level meter, IV-310  
   motion sensor, unidirectional, II-346  
   motor hour, III-340  
   multiconductor-cable tester, IV-288  
   multimeter shunt, IV-293  
   noise generator, IV-308  
   ohmmeter, linear, III-540  
   ohmmeter, linear-scale, five-range, IV-290  
   oscilloscope adapter, four-trace, IV-267  
   paper sheet discriminator, copying machines, III-339  
   peak-dB meter, III-348  
   peakmeter, LED, III-333  
   phase difference from 0 to 180 degrees, II-344  
   phase meter, digital VOM, IV-277  
   picommeter, III-338  
   power gain, 60 MHz, I-489  
   power supply test load, constant-current, IV-424  
   probes, 4-to-220 V, III-499  
   pulse-width, very short, III-336  
   QRP SWR bridge, III-336  
   remote-control infrared device, IV-228  
   resistance measurement, synchronous system, IV-285  
   resistance ratio detector, II-342  
   resistance/continuity meters, III-538-540  
   rf output indicator, IV-299  
   rf power, wide-range, III-332  
   SCR tester, III-344  
   shutter, I-485  
   signal generator, AM broadcast-band, IV-302  
   signal generator, AM/IF, 455 kHz, IV-301  
   signal strength (S), III-342  
   signal tracer, IV-429  
   sound-level meter, III-346, IV-305, IV-307  
   sound-test circuits (*see also* sound generators), IV-304  
   speedometer, bike, IV-271, IV-282  
   static detector, IV-276  
   stereo audio-level meter, IV-310  
   stereo audio-power meter, IV-306  
   stereo power meter, III-331  
   stud finder, III-339  
   SWR meter, IV-269  
   tachometer, III-335, III-340  
   tachometer, optical pick-up, III-347  
   tachometer, analog readout, IV-280  
   tachometer, digital readout, IV-278  
   tachometer, digital, IV-268-269  
   temperature measurement, transistorized, IV-572  
   test probe, 4-220 V, III-499  
   thermometers, III-637-643  
   three-in-one set, logic probe, signal tracer, injector, IV-429  
   three-phase tester, II-440  
   transistor, I-401, IV-281  
   TTL logic, I-527  
   universal test probe, IV-431  
   UHF source dipper, IV-299  
   voltmeter, digital LED readout, IV-286  
   VOM, phase meter, digital readout, IV-277  
   VOR signal simulator, IV-273  
   water-level measurement circuit, IV-191  
   wavemeter, tuned RF, IV-302  
   wideband test amplifier, IV-303  
   wire tracer, II-343  
   zener, I-400  
 medical electronic circuits, II-347-349, III-349-352  
 biomedical instrumentation differential amp, III-282  
 breath monitor, III-350  
 EKG simulator, three-chip, III-350  
 heart rate monitor, II-348, II-349  
 preamplifier for, II-349  
 stimulator, constant-current, III-352  
 stimulus isolator, III-351  
 thermometer, implantable/ingestible, III-641  
 melody generator, single-chip design, IV-520  
 memory-related circuits  
   EEPROM pulse generator, 5V-powered, III-99  
   memory protector/power supply monitor, IV-425  
   memory-saving power supply, II-486  
 metal detectors, II-350-352, IV-137  
   micropower, I-408  
 meters (*see also* measurement/test circuits)  
   ac voltmeters, III-765  
   analog, expanded-scale, IV-46  
   analog, expanded-scale, voltage reference, III-774  
   anemometer/, hot-wire, III-342  
   audio frequency, I-311  
   audio millivolt, III-767, III-769  
   audio power, I-488  
   automatic contrast, I-479  
   basic grid dip, I-247  
   breaker point dwell, I-102  
   capacitance, I-400  
   dc voltmeter, III-763  
   dc voltmeter, high-input resistance, III-762  
   deviation meter, IV-303  
   digital frequency, III-344  
   digital multimeter (DMM), high-resistance measuring, IV-291  
   dip, I-247  
   dip, dual-gate IGFET in, I-246

dosage rate, I-534  
duty-cycle meter, IV-275  
electrometer, IV-277  
extended range VU, I-715, III-487  
FET voltmeter, III-765, III-770  
field-strength meters (*see* field-strength meters)  
flash exposure, I-484, III-446  
frequency meter, IV-282  
grid-dip meter, bandswitched, IV-298  
LED bar/dot level, I-251  
LED panel, III-347  
light, I-383  
linear frequency, I-310  
linear light, I-382  
logarithmic light, I-382  
magnetic-field meter, IV-266  
meter-driver rf amplifier, 1-MHz, III-545  
microammeter, dc, four-range, IV-292  
microwave field strength, I-273  
millivoltmeter, dc, IV-295  
millivoltmeter, four-range, IV-289  
millivoltmeter, LED readout, IV-294  
mono audio-level meter, IV-310  
motor hour, III-340  
multimeter shunt, IV-293  
ohmmeter, linear, III-540  
ohmmeters, linear-scale, five-range, IV-290  
peak decibels, III-348  
peak, LED, III-333  
pH, I-399  
phase, I-406  
picammeter, III-338  
power line frequency, I-311  
power, I-489  
resistance/continuity, III-538-540  
rf power, I-16  
rf power, wide-range, III-332  
rf voltmeter, III-766  
signal strength (S), III-342, IV-166  
soil moisture, III-208  
sound-level meter, IV-305, IV-307  
sound level, telephone, III-614  
sound level, III-346  
speedometer, bicycle, IV-271, IV-282  
stereo audio-level meter, IV-310  
stereo audio-power meter, IV-306  
stereo balance, I-618-619  
stereo power, III-331  
suppressed zero, I-716  
SWR power, I-16, IV-269  
tachometer, III-335, III-340, III-347  
tachometer, analog readout, IV-280  
tachometer, digital readout, IV-278  
temperature, I-647  
tester, IV-270

thermometers, III-637-643  
tilt meter, III-644-646  
varicap tuned FET DIP, I-246  
vibration, I-404  
voltage, III-758-77  
voltmeters, ac wide-range, III-772  
voltmeters, digital, 3.5-digit, full-scale four-decade, III-761  
voltmeters, digital, 4.5-digit, III-760  
voltmeters, high-input resistance, III-768  
VOM field strength, I-276  
VOM/phase meter, digital readout, IV-277  
wavemeter, tuned RF, IV-302  
methane concentration detector, linearized output, III-250  
metronomes, I-413, II-353-355, III-353-354, IV-312-314  
ac-line operated unijunction, II-355  
accentuated beat, I-411  
downbeat-emphasized, III-353-354  
electronic, IV-313  
low-power design, IV-313  
novel design, IV-314  
sight and sound, I-412  
simple, II-354  
version II, II-355  
microammeter, dc, four-range, IV-292  
microcontroller, musical organ, preprogrammed single-chip, I-600  
micro-sized amplifiers, III-36  
microphone circuits  
amplifiers for, I-87, III-34  
amplifiers for, electronic balanced input, I-86  
FM wireless, III-682, III-685, III-691  
mixer, II-37  
preamp for, II-45, IV-37, IV-42  
preamp, low-impedance design, IV-41  
preamp for, low-noise transformer-less balanced, I-88  
preamp for, tone control in, I-675, II-687  
wireless, IV-652-654  
wireless AM, I-679  
microprocessors (*see* computer circuits)  
microvolt comparators  
dual limit, III-89  
hysteresis-including, III-88  
microvolt probe, II-499  
microwave amplifier circuits, IV-315-319  
5.7 GHz, IV-317  
bias supply for preamp, IV-318  
preamplifier, 2.3 GHz, IV-316  
preamplifier, 3.4 GHz, IV-316  
preamplifier, single-stage, 10 GHz, IV-317  
preamplifiers, bias supply, IV-318  
preamplifiers, two-stage, 10 GHz, IV-319  
Miller oscillator, I-193  
millivoltmeters (*see also* meters; voltmeters)  
ac, I-716  
audio, III-767, III-769  
high-input impedance, I-715  
mini-stereo audio amplifiers, III-38  
mixers, III-367-370, IV-330-336  
1-MHz, I-427  
audio, I-23, II-35, IV-335  
audio, one-transistor design, I-59  
CMOS, I-57  
common-source, I-427  
digital mixer, IV-334  
diplexer, IV-335  
doubly balanced, I-427  
dynamic audio mixer, IV-331  
four-channel, I-60, III-369, IV-333  
four-channel, four-track, II-40  
four-channel, high level, I-56  
four-input, stereo, I-55  
four-input, unity-gain, IV-334  
HF transceiver/mixer, IV-457  
hybrid, I-60  
input-buffered, III-369  
microphone, II-37  
multiplexer, I-427  
one-transistor design, I-59  
passive, I-58  
preamplifier with tone control, I-58  
signal combiner, III-368  
silent audio switching, I-59  
sound amplifier and, II-37  
stereo mixer, pan controls, IV-332  
unity-gain, four-input, IV-334  
utility-design mixer, IV-336  
universal stage, III-370  
video, high-performance operation, IV-609  
mobile equipment, 8-amp regulated power supply, II-461  
model and hobby circuits, IV-337-340  
controller, model-train and/or slot-car, IV-338-340  
model rocket launcher, II-358  
modems, power-line, carrier-current circuit, III-82  
modulated light beam circuit, ambient light effect cancellation with, II-328  
modulated readback systems, disc/tape phase, I-89  
modulation indicator/monitor, I-430  
CB, I-431

modulators, I-437, II-368-372, III-371-377  
 + 12V dc single supply, balanced, I-437  
 AM, I-438  
 amplitude, low-distortion low level, II-370  
 balanced, III-376  
 balanced, phase detector-selector/sync rectifier, III-441  
 double-sideband suppressed-carrier, III-377  
 linear pulse-width, I-437  
 monitor for, III-375  
 musical envelope generator, I-601  
 pulse-position, I-435, III-375  
 pulse-width, I-435, I-436, I-438-440, III-376, IV-326  
 rf, I-436, III-372, III-374  
 rf, double sideband, suppressed carrier, II-369  
 saw oscillator, III-373  
 TTL oscillator for television display, II-372  
 TV, I-439, II-433, II-434  
 VHF, I-440, III-684  
 video, I-437, II-371, II-372  
 moisture detector (*see* fluid and moisture detectors)  
 monitors (*see also* alarms; control circuits; detectors; indicators; sensors), III-378-390  
 acid rain, III-361  
 battery, III-60-67  
 battery-alternator, automotive, III-63  
 blinking phone light, II-624  
 breath monitor, III-350  
 current, alarm and, III-338  
 directional signals, auto, III-48  
 door-ajar, automotive circuits, III-46  
 duty cycle, III-329  
 flames, III-313  
 home security system, I-6  
 line-current, III-341  
 line-voltage, III-511  
 logic line, III-108  
 modulation, III-375  
 overvoltage, III-762  
 power monitor, SCR design, IV-385  
 power-supply monitors (*see* power-supply monitors)  
 power-line connections, ac, III-510  
 precision battery voltage, HTS, I-122  
 receiver, II-526  
 sound level, telephone, III-614  
 telephone status, optoisolator in, I-625  
 telephone, remote, II-626  
 thermal monitor, IV-569  
 undervoltage, III-762  
 voltage, III-767  
 voltage, III-758-772  
 monostable circuit, I-464, II-460  
 monostable multivibrators, I-465, III-230, III-235  
 input lockout, I-464  
 linear-ramp, III-237  
 positive-triggered, III-229  
 monostable photocell, self-adjust trigger, II-329  
 monostable TTL, I-464  
 monostable UJT, I-463  
 mooring light, automatic, II-323  
 MOSFETs  
 power control switch, IV-386  
 power inverter, III-295  
 mosquito repelling circuit, I-684  
 motion sensors  
 acoustic Doppler motion detector, IV-343  
 auto alarm, I-9  
 low-current-drain design, IV-342-343  
 motorcycle alarm, I-9  
 UHF, III-516, IV-344  
 unidirectional, II-346  
 motor control circuits, IV-347-353  
 400 Hz servo amplifier, II-386  
 ac motors, II-375  
 bidirectional proportional, II-374  
 compressor protector, IV-351  
 direction control, dc motors, I-452  
 direction control, series-wound motors, I-448  
 direction control, shunt-wound motors, I-456  
 direction control, stepper motor, IV-350  
 driver control, ac, three-phase, II-383  
 driver control, ac, two-phase, II-382  
 driver control, constant-speed, III-386  
 driver control, dc, fixed speed, III-387  
 driver control, dc, servo, bipolar control input, II-385  
 driver control, dc, speed-controlled reversible, III-388  
 driver control, N-phase motor, II-382  
 driver control, reversing, dc control signals, II-381  
 driver control, servo motor amplifier, I-452, II-384  
 driver control, stepper motors, III-390  
 driver control, stepper motor, half-step, IV-349  
 driver control, stepper motor, quadrature-step, IV-350  
 driver control, two-phase, II-456  
 fiber-optic, dc, variable, II-206  
 hours-in-use meter, III-340  
 induction motor, I-454  
 load-dependent, universal motor, I-451  
 mini-drill control, IV-348  
 power brake, ac, II-451  
 power-factor controller, three-phase, II-388  
 PWM motor controller, III-389  
 PWM servo amplifier, III-379  
 PWM speed control, II-376  
 PWM speed control/energy-recovering brake, III-380  
 self-timing control, built-in, universal motor, I-451  
 servo motor amplifier, I-452, II-384  
 speed control (*see* speed controllers)  
 start-and-run motor circuit, III-382  
 stepper motors, half-step, IV-349  
 stepper motors, quarter-step, IV-350  
 stepper motors, speed and direction, IV-350  
 tachometer feedback control, II-378  
 tachometer feedback control, closed loop, II-390  
 motorcycle alarm, motion actuated, II-9  
 multiburst generator, square waveform, II-88  
 multimeters, shunt, IV-293  
 multiple-input detector, III-102  
 multiplexed common-cathode LED-display ADC, III-764  
 multiplexers, III-391-397  
 1-of-8 channel transmission system, III-395  
 analog, II-392  
 analog, 0/01-percent, II-392  
 analog, buffered input and output, III-396  
 analog, input/output buffer for, III-11  
 analog, single- to four-trace converter, II-431  
 capacitance, II-200, II-416  
 de-, III-394  
 four-channel, low-cost, III-394  
 frequency, III-213-218  
 mathematical, one trim, III-326  
 oscilloscopes, add-on, III-437  
 pulse-width, III-214  
 resistor, II-199  
 sample-and-hold, three-channel, III-396  
 two-level, III-392  
 video, 1-of-15 cascaded, III-393  
 wideband differential, II-428  
 multipliers, low-frequency multiplier, IV-325

multiplying D/A converter, III-168  
 multiplying pulse width circuit, II-264  
 multivibrators  
     100 kHz free running, II-485  
     astable, I-461, II-269, II-510, III-196, III-224, III-233, III-238  
     astable, digital-control, II-462  
     astable, dual, II-463  
     astable, programmable-frequency, III-237  
     bistable, II-465  
     bistable, touch-triggered, I-133  
     car battery, II-106  
     CB modulation, II-431  
     current, II-203  
     duty-cycle, 50-percent, III-584  
     free-running, programmable-frequency, III-235  
     low-frequency, III-237  
     low-voltage, II-123  
     modulation, II-430  
     monostable, II-465, III-229, III-230, III-235, III-237  
     monostable, input lock-out, II-464  
     one-shot, II-465  
     oscilloscope, II-474  
     single-supply, III-232  
     sound level, II-403  
     square-wave generators, IV-536  
     telephone line, II-628  
     wideband radiation, II-535  
 music circuits (*see* sound generators)  
 musical envelope generator/modulator, IV-22  
 mux/demux systems  
     differential, I-425  
     eight-channel, I-426, II-115

## N

N-phase motor drive, III-382  
 NAB preamps  
     record, III-673  
     two-pole, III-673  
 NAB tape playback pre-amp, III-38  
 nano ammeter, I-202  
 narrow-band FM demodulator, carrier detect in, II-159  
 negative-ion generator, IV-634  
 neon flashers  
     five-lamp, III-198  
     two-state oscillator, III-200  
 networks  
     filter, I-291  
     speech, telephone, II-633  
 ni-cad batteries  
     analyzer for, III-64  
     charger, I-112, I-116, III-57  
     charger, 12 v, 200 mA per hour, I-114

charger, current and voltage limiting, I-114  
 charger, fast-acting, I-118  
 charger, portable, IV-69  
 charger, temperature-sensing, IV-77  
 charger, thermally controlled, II-68  
 packs, automotive charger for, I-115  
 protection circuit, III-62  
 test circuit, IV-79  
 zappers, I-6, II-68  
 night lights (*see* lights/light-activated and controlled circuits)  
 noise generators (*see* sound generators)  
 noise reduction circuits, II-393-396, III-398-401, IV-354-356  
 audio clipper/limiter, IV-355  
 audio shunt noise limiter, IV-355  
 audio squelch, II-394  
 balance amplifier with loudness control, II-395  
 blunker, IV-356  
 clipper, II-394  
 clipper, audio-powered, III-396  
 Dolby B, decode mode, III-401  
 Dolby B, encode mode, III-400  
 Dolby B/C, III-399  
 dynamic noise reduction, III-321  
 filter, III-188  
 filter, dynamic filter, III-190  
 limiter, II-395, III-321  
 noninverting amplifiers, I-41, III-14  
 adjustable gain, I-91  
 comparator with hysteresis in, I-153  
 high-frequency, 28-dB, III-263  
 hysteresis in, I-153  
 low power, digitally selectable input and gain, II-334  
 power, I-79  
 programmable-gain, III-505  
 single supply, I-74  
 split supply, I-75  
 noninverting integrator, improved design, II-298  
 noninverting voltage followers, I-33  
     high-frequency, III-212  
 nonselective frequency tripler, transistor saturation, II-252  
 Norton amplifier, absolute value, III-11  
 notch filters (*see also* filter circuits), I-283, II-397-403, III-402-404  
     4.5 MHz, I-282  
     550 Hz, II-399  
     1800 Hz, II-398  
     active band reject, II-401  
     adjustable Q, II-398  
     audio, II-400  
     bandpass and, II-223  
     high-Q, III-404  
     selectable bandwidth, I-281

three-amplifier design, I-281  
 tunable, II-399, II-402  
 tunable, passive-bridged differentiator, II-403  
 tunable, hum-suppressing, I-280  
 tunable, op amp, II-400  
 twin-T, III-403  
 Wien bridge, II-402  
 NTSC-to-RGB video decoder, IV-613  
 null circuit, variable gain, accurate, III-69  
 null detector, I-148, III-162

## O

ohmmeters, I-549  
     linear, III-540  
     linear scale, I-549  
     linear-scale, five-range, IV-290  
 ohms-to-volts converter, I-168  
 oil-pressure gauge, automotive, IV-44, IV-47  
 on/off inverter, III-594  
 on/off touch switches, II-691, III-663  
 one-of-eight channel transmission system, III-100  
 one-shot function generators, I-465  
     digitally controlled, I-720  
     precision, III-222  
     retriggerable, III-238  
 one-shot timers, III-654  
     light-controlled, III-317  
     voltage-controlled high-speed, II-266  
 op amps, II-404-406, III-405-406, IV-357-364  
     x10, I-37  
     x100, I-37  
 astable multivibrator, III-224  
 audio amplifier, IV-33  
 bidirectional compound op amp, IV-361  
 clamping for, II-22  
 clock circuit using, III-85  
 comparator, three-input and gate comparator, IV-363  
 compound op-amp, IV-364  
 feedback-stabilized amplifier, IV-360  
 gain-controlled op amp, IV-361  
 intrinsically safe protected, III-12  
 inverter/rectifier, programmable, IV-364  
 on/off switch, transistorized, IV-546  
 power booster, IV-358  
 power driver circuit, IV-158-159  
 quad, simultaneous waveform generator using, II-259  
 single potentiometer to adjust gain over bipolar range, II-406  
 swing rail-ray, LM324, IV-363

op amps (*cont.*)  
     tunable notch filter with, II-400  
     variable gain and sign, II-405  
     VCO driver, IV-362  
     video op amp circuits, IV-615  
     optical circuits (*see also* lasers; lights/  
         light-activated and controlled cir-  
         cuits), II-407-419, IV-365-369  
     50 kHz center frequency FM trans-  
         mitter, II-417  
     ac relay, III-418  
     ac relay using two photon couplers,  
         II-412  
     ac switcher, high-voltage, III-408  
     ambient light ignoring optical sensor,  
         III-413  
     CMOS coupler, III-414  
     communication system, II-416  
     dc linear coupler, II-411  
     dc latching relay, III-417  
     digital transmission isolator, II-414  
     high-sensitivity, NO, two-terminal  
         zero voltage switch, II-414  
     indicator lamp driver, III-413  
     integrated solid state relay, II-408  
     interruption sensor, IV-366  
     isolation and zero voltage switching  
         logic, II-415  
     light-detector, IV-369  
     line-current detector, III-414  
     linear ac analog coupler, II-412  
     linear analog coupler, II-413  
     linear optocoupler for instrumenta-  
         tion, II-417  
     microprocessor triac array driver, II-  
         410  
     optoisolator relay circuit, IV-475  
     paper tape reader, II-414  
     photoelectric light controller, IV-369  
     power outage light, line-operated, III-  
         415  
     probe, IV-369  
     receiver, 50 kHz FM optical trans-  
         mitter, II-418  
     receiver, light receiver, IV-367  
     receiver, optical or laser light, IV-368  
     relays, dc solid-state, open/closed,  
         III-412  
     source follower, photodiode, III-419  
     stable optocoupler, II-409  
     telephone ring detector, III-611  
     transmitter, light transmitter, IV-368  
     triggering SCR series, III-411  
     TTL coupler, optical, III-416  
     zero-voltage switching, closed half-  
         wave, III-412  
     zero-voltage switching, solid-state,  
         III-410  
     zero-voltage switching, solid-state  
         relay, III-416

optical communication system, I-358,  
     II-416  
 optical pyrometer, I-654  
 optical receiver, I-364, II-418  
 optical Schmitt trigger, I-362  
 optical sensor, ambient light ignoring,  
     III-413  
 optical sensor-to-TTL interface, III-  
     314  
 optical transmitters, I-363  
     FM (PRM), I-367  
 optocouplers  
     linear, instrumentation, II-417  
     stable, II-409  
 optoisolators, IV-475  
     driver, high-voltage, III-482  
     telephone status monitor using, I-626  
 OR gate, I-395  
 organ, musical, I-415  
     preprogrammed single chip microcon-  
         troller for, I-600  
     stylus, I-420  
 oscillators, II-420-429, III-420-432, IV-  
     370-377  
     1 kHz, II-427  
     1.0 MHz, I-571  
     2MHz, II-571  
     5-V, III-432  
     50 kHz, I-727  
     400 MHz, I-571  
     500 MHz, I-570  
     800 Hz, I-68  
     adjustable over 10:1 range, II-423  
     astable, I-462  
     audio, I-245, III-427, IV-374, IV-375  
     audio, light-sensitive, III-315  
     beat-frequency audio generator, IV-  
         371  
     buffer circuits, IV-89  
     Butler, aperiodic, I-196  
     Butler, common base, I-191  
     Butler, emitter follower, II-190-191,  
         II-194  
     cassette bias, II-426  
     clock generator, I-615, III-85  
     CMOS, I-615  
     CMOS, 1 MHz to 4MHz, I-199  
     CMOS, crystal, I-187  
     code practice, I-15, I-20, I-22, II-  
         428, III-431, IV-373, IV-375, IV-  
         376  
     Colpitts, I-194, I-572, II-147  
     Colpitts, harmonic, I-189-190  
     crystal (*see* crystal oscillators)  
     double frequency output, I-314  
     discrete sequence, III-421  
     duty-cycle, 50-percent, III-426  
     emitter-coupled, big loop, II-422  
     emitter-coupled, RC, II-266  
     exponential digitally controlled, I-728

feedback, I-67  
 flasher and, high drive, II-235  
 flasher and, low frequency, II-234  
 free-running, I-531  
 free-running, square wave, I-615  
 frequency doubled output from, II-  
     596  
 gated, I-728  
 gated, last-cycle completing, III-427  
 Hartley, I-571  
 hc-based, III-423  
 HCU/HCT-based, III-426  
 high-current, square-wave generator,  
     III-585  
 high-frequency, III-426  
 high-frequency, crystal, I-175, II-148  
 load-switching, 100 mA, I-730  
 low-distortion, I-570  
 low-duty-cycle pulse circuit, IV-439  
 low-frequency, III-428  
 low-frequency, crystal, I-184, II-146  
 low-frequency, TTL, II-595  
 low-noise crystal, II-145  
 Miller, I-193  
 neon flasher, two-state, III-200  
 one-second, 1 kHz, II-423  
 one-shot, voltage-controlled high-  
     speed, II-266  
 overtone, 50 MHz to 100 MHz, I-  
     181  
 overtone, crystal, I-176, I-180, II-  
     146, IV-123  
 overtone, crystal switching, I-183  
 overtone, fifth overtone, I-182  
 phase-locked, 20-MHz, IV-374  
 Pierce, I-195  
 Pierce, crystal, II-144  
 Pierce, harmonic, I-199, II-192  
 quadrature, III-428  
 quadrature-output, I-729  
 quadrature-output, square-wave  
     generator, III-585  
 R/C, I-612  
 reflection, crystal-controlled, III-136  
 relaxation, IV-376  
 relaxation, SCR, III-430  
 resistance-controlled digital, II-426  
 rf (*see also* rf oscillator), II-550, I-572  
 rf-genie, II-421  
 rf-powered sidetone, I-24  
 RLC, III-423  
 sawtooth wave, modulator, III-373  
 Schmitt trigger crystal, I-181  
 sine-wave (*see* sine-wave oscillators)  
 sine-wave/square wave, easily tuned,  
     I-65  
 sine-wave/square-wave, tunable, III-  
     232  
 single op amp, I-529  
 square-wave, II-597, I-613-614, II-

- 616, IV-532, IV-533  
 square-wave, 0.5 Hz, I-616  
 square-wave, 1kHz, I-612  
 start-stop oscillator pulse circuit, IV-438  
 switching, 20 ns, I-729  
 temperature-compensated, low power 5v-driven, II-142  
 temperature-stable, II-427  
 temperature-compensated crystal, I-187  
 timer, 500 timer, I-531  
 tone-burst, decoder and, I-726  
 transmitter and, 27 MHz and 49 MHz rf, I-680  
 triangle/square wave, I-616, II-422  
 TTL, I-179, I-613  
 TTL, 1MHz to 10MHz, I-178  
 TTL, television display using, II-372  
 TTL-compatible crystal, I-197  
 tube type crystal, I-192  
 tunable frequency, II-425  
 tunable single comparator, I-69  
 varactor tuned 10 MHz ceramic resonator, II-141  
 variable, II-421  
 variable, audio, 20Hz to 20kHz, II-727  
 variable, four-decade, single control for, II-424  
 variable, wide range, II-429  
 variable-duty cycle, fixed-frequency, III-422  
 voltage-controlled (*see* voltage-controlled oscillators)  
 wide-frequency range, II-262  
 wide-range, I-69, III-425  
 wide-range, variable, I-730  
 Wien-bridge (*see* Wien-bridge oscillators)  
 XOR-gate, III-429  
 yelp, II-577  
 oscilloscopes, II-430-433, III-433-439  
 analog multiplexer, single- to four-trace scope converter, II-431  
 beam splitter, I-474  
 calibrator, II-433, III-436  
 converter, I-471  
 CRO doubler, III-439  
 eight-channel voltage display, III-435  
 extender, III-434  
 FET dual-trace switch for, II-432  
 four-trace oscilloscope adapter, IV-267  
 monitor, I-474  
 multiplexer, add-on, III-437  
 preamplifier, III-437  
 preamplifier, counter, III-438  
 preamplifier, instrumentation amplifiers, IV-230-231  
 sensitivity amplifier, III-436  
 triggered sweep, III-438  
 voltage-level dual readout, IV-108  
 outband descrambler, II-164  
 out-of-bounds pulse-width detector, III-158  
 output limiter, III-322  
 output-gating circuit, photomultiplier, II-516  
 output-stage booster, III-452  
 over/under temperature monitor, dual output, II-646  
 overload protector, speaker, II-16  
 overspeed indicator, I-108  
 overtone crystal oscillators, II-146  
 50 MHz to 100 MHz, I-181  
 100 MHz, IV-124  
 crystal, I-176, I-180, II-146  
 crystal switching, I-183  
 fifth overtone, I-182  
 third-overtone oscillator, IV-123  
 overvoltage detection and protection, IV-389  
 comparator to detect, II-107  
 monitor for, III-762  
 protection circuit, II-96, II-496, III-513  
 undervoltage and, indicator, I-150
- P**
- pager, pocket-size, III-288  
 PAL/NTSC decoder, RGB input, III-717  
 palette, video, III-720  
 panning circuit, two-channel, I-57  
 paper-sheet discriminator, copying machines, III-339  
 paper-tape reader, II-414  
 parallel connections, telephone, III-611  
 party-line intercom, II-303  
 passive bridge, differentiator tunable notch filter, II-403  
 passive mixer, II-58  
 PCB continuity tester, II-342  
 peak decibel meter, III-348  
 peak detectors, II-174, II-175, II-434-436, IV-138, IV-143  
 analog, with digital hold, III-153  
 digital, III-160  
 high-bandwidth, III-161  
 high-frequency, II-175  
 high-speed, I-232  
 low-drift, III-156  
 negative, I-225, I-234  
 op amp, IV-145  
 positive, I-225, I-235, II-435, III-169  
 ultra-low drift, I-227  
 voltage, precision, I-226  
 wide-bandwidth, III-162  
 wide-range, III-152
- peak meter, LED, III-333  
 peak program detector, III-771  
 peak-to-peak converter, precision ac/dc, II-127  
 people-detector, infrared-activated, IV-225  
 period counter, 100 MHz, frequency and, II-136  
 period-to-voltage converter, IV-115  
 pest-repeller, ultrasonic, III-699, III-706, III-707, IV-605-606  
 pH meter, I-399  
 pH probe, I-399, III-501  
 phase detectors, III-440-442  
 10-bit accuracy, II-176  
 phase selector/sync rectifier/balanced modulator, III-441  
 phase sequence, III-441  
 phase difference, 0- to 180-degree, II-344  
 phase indicator, II-439  
 phase meter, I-406  
 digital VOM, IV-277  
 phase selector, detector/sync rectifier/balanced modulator, III-441  
 phase sequence circuits, II-437-442  
 detector, II-439, II-441, II-442, III-441  
 indicator, I-476, II-439  
 rc circuit, phase sequence reversal detection, II-438  
 reversal, rc circuit to detect, II-438  
 three-phase tester, II-440  
 phase shifters, IV-647  
 0-180 degree, I-477  
 0-360 degree, I-477  
 single transistor, I-476  
 phase splitter, precision, III-582  
 phase tracking, three-phase square wave generator, II-598  
 phasor gun, I-606, IV-523  
 phono amplifiers, I-80-81  
 magnetic pickup, I-89  
 stereo, bass tone control, I-670  
 phone preamps, I-91  
 equalized, III-671  
 LM382, I-90  
 low-noise design, IV-36  
 magnetic, I-91, III-37  
 magnetic, ultra-low-noise, IV-36  
 photo-conductive detector amplifier, four quadrant, I-359  
 photo memory switch for ac power control, I-363  
 photo stop action, I-481  
 photocell, monostable, self-adjust trigger, II-329  
 photocurrent integrator, II-326  
 photodiode circuits  
 amplifier, III-672

photodiode circuits amplifier (*cont.*)  
     amplifier, low-noise, III-19  
     current-to-voltage converter, II-128  
     sensor amplifier, II-324  
     amplifier, I-361  
     comparator, precision, I-360  
     level detector, precision, I-365  
     PIN, thermally stabilized signal conditioner with, II-330  
     PIN-to-frequency converters, III-120  
     source follower, III-419  
 photoelectric circuits  
     ac power switch, III-319  
     alarm system, II-4  
     controlled flasher, II-232  
     light controller, IV-369  
     smoke alarm, line operated, I-596  
     smoke detector, I-595  
     switch, II-321  
     switch, synchronous, II-326  
 photoflash, electronic, III-449  
 photography-related circuits, II-443-449, III-443-449, IV-378-382  
 auto-advance projector, II-444  
 camera alarm trigger, III-444  
 camera trip circuit, IV-381  
 contrast meter, II-447  
 darkroom enlarger timer, III-445  
 electronic flash trigger, II-448  
 enlarger timer, II-446  
 exposure meter, I-484  
 flash meter, III-446  
 flash slave driver, I-483  
 flash trigger, electronic, II-448  
 flash trigger, remote, I-484  
 flash trigger, sound-triggered, II-449  
 flash trigger, xenon flash, III-447  
 photo-event timer, IV-379  
 photoflash, electronic, III-449  
 shutter speed tester, II-445  
 slave-flash unit trigger, SCR design, IV-380, IV-382  
 slide projector auto advance, IV-381  
 slide timer, III-448  
 slide-show timer, III-444  
 sound trigger for flash unit, II-449, IV-382  
 time-delay flash trigger, IV-380  
 timer, I-485  
 xenon flash trigger, slave, III-447  
 photomultiplier output-gating circuit, II-516  
 picoometers, I-202, II-154, III-338  
     circuit for, II-157  
     guarded input circuit, II-156  
 picture fixer/inverter, III-722  
 Pierce crystal oscillator, I-195, II-144  
     1-MHz, III-134  
     harmonic, I-199, II-192  
     low-frequency, III-133

piezoelectric alarm, I-12  
 piezoelectric fan-based temperature controller, III-627  
 PIN photodiode-to-frequency converters, III-120  
 pink noise generator, I-468  
 plant watering gauge, II-248  
 plant watering monitor, II-245  
 plant waterer, I-443  
 playback amplifier, tape, I-77  
 PLL/BC receiver, II-526  
 pocket pager, III-288  
 polarity converter, I-166  
 polarity-protection relay, IV-427  
 polarity-reversing amplifiers, low-power, III-16  
 portable-radio 3 V fixed power supplies, IV-397  
 position indicator/controller, tape recorder, II-615  
 positive input/negative output charge pump, III-360  
 positive peak detector, II-435  
 positive regulator, NPN/PNP boost, III-475  
 power amps, II-450-459, III-450-456  
     2- to 6-watt audio amplifier with preamp, II-451  
     10 W, I-76  
     12 W low distortion, I-76  
     25 W, II-452  
     90 W, safe area protection, II-459  
     am radio, I-77  
     audio, II-451, III-454, IV-28-33  
     audio, 20-W, III-456  
     audio, 50-W, III-451  
     audio, 6-W, with preamp, III-454  
     audio, booster, II-455  
     bridge audio, I-81  
     bull horn, II-453  
     class-D, III-453  
     hybrid, III-455  
     inverting, I-79  
     low-distortion, 12 W, I-76  
     low-power audio, II-454  
     noninverting, I-79  
     noninverting, ac, I-79  
     output-stage booster, III-452  
     portable, III-452  
     rear speaker ambience amplifier, II-458  
     rf, 1296-MHz solid state, III-542  
     rf, 5W, II-542  
     switching, I-33  
     two-meter 10 W, I-562  
     walkman amplifier, II-456  
 power booster, I-28, I-33  
 power control, burst, III-362  
 power disconnector, low-voltage, II-97  
 power factor controller, three-phase, II-388  
 power failure alarm, I-581-582  
 power gain test circuit, 60 MHz, I-489  
 power inverters, III-298  
     12 VDC-to-117 VAC at 60 Hz, III-294  
     medium, III-296  
     MOSFET, III-295  
 power loss detector, II-175  
 power meters, I-489  
     audio, I-488  
     frequency and, II-250  
     rf, I-16  
     SWR, I-16  
 power op amp/audio amp, high slew rate, I-82  
 power outage light, line-operated, III-415  
 power pack for battery operated devices, I-509  
 power protection circuit, I-515  
 power reference, 0-to-20 V, I-694  
 power supplies, II-460-486, III-464  
     5V including momentary backup, II-464  
     5V, 0.5A, I-491  
     8-amp regulated, mobile equipment operation, II-461  
     10 A regulator, current and thermal protection, II-474  
     12-14 V regulated 3A, II-480  
     90 V rms voltage regulator with PUT, II-479  
     500 kHz switching inverter for 12V, II-474  
     2,000 V low-current supply, IV-636-637  
     adjustable current limit and output voltage, I-505  
     arc lamp, 25W, II-476  
     arc-jet, starting circuit, III-479  
     backup supply, drop-in main-activated, IV-424  
     balance indicator, III-494  
     battery charger and, 14V, 4A, II-73  
     bench top, II-472  
     benchtop, dual output, I-505  
     bipolar, battery instruments, II-475  
     charge pool, III-469  
     dc-to-dc SMPS variable 18V to 30 V out at 0.2A, II-480  
     dual polarity, I-497  
     fault monitor, single-supply, III-495  
     fixed power supplies (*see* fixed power supplies)  
     general-purpose, III-465  
     glitches in, comparator to detect, II-107

- high-voltage (*see* high-voltage power supplies)  
 increasing zener diode power rating, II-485  
 isolated feedback, III-460  
 laser power supply, voltage multiplier circuits, IV-636  
 low-ripple, I-500  
 low-volts alarm, II-493  
 memory save on power-down, II-486  
 micropower bandgap reference, II-470  
 microprocessor power supply watchdog, II-494  
 monitors (*see* power-supply monitors)  
 off-line flyback regulator, II-481  
 overvoltage protection circuit, II-496  
 overvoltages in, comparator to detect, II-107  
 power-switching circuit, II-466  
 programmable, III-467  
 protection circuit, II-497  
 protection circuit, fast acting, I-518  
 push-pull, 400V/60W, II-473  
 radiation-hardened 125A linear regulator, II-468  
 regulated, +15V 1-A, III-462  
 regulated, -15V 1-A, III-463  
 regulated, split, I-492  
 SCR preregulator for, II-482  
 single supply voltage regulator, II-471  
 split, I-512  
 stand-by, non-volatile CMOS RAMs, II-477  
 switching, II-470, III-458  
 switching, 50-W off-line, III-473  
 switching, variable, 100-KHz multiple-output, III-488  
 three-rail, III-466  
 uninterruptible, +5V, III-477  
 uninterruptible, personal computer, II-462  
 variable (*see* variable power supplies)  
 voltage regulator, II-484  
 power-consumption limiters, III-572  
 power-control circuits, IV-383-389  
     ac switch, battery-triggered, IV-387  
     bang-bang controllers, IV-389  
     current-loop control, SCR design, IV-387  
     high-side switches, 5 V supplies, IV-384, IV-385  
     monitor, SCR design, IV-385  
     MOSFET switch, IV-386  
     overvoltage protector, IV-389  
     power controller, universal design, IV-388  
     pushbutton switch, IV-388  
     power-down protection
- alarm, III-511  
 memory save power supply for, II-486  
 protection circuit, II-98  
 power-line connections monitor, ac, III-510  
 power-line modem, III-82  
 power-on reset, II-366  
 power-supply monitors, II-491-497, III-493-495, IV-422-427  
 backup supply, drop-in main-activated, IV-424  
 balance monitor, III-494  
 booster/buffer, boosts reference current, IV-425  
 circuit breaker, trip circuit, IV-423  
 fault monitor, single-supply, III-495  
 memory protector/supply monitor, IV-425  
 polarity-protection relay, IV-427  
 test load, constant-current, IV-424  
 triac for ac-voltage control, IV-426  
 tube amplifier, high-voltage isolation, IV-426  
 voltage sensor, IV-423  
 power-switching circuit, II-466  
     complementary ac, I-379  
 power/frequency meter, II-250  
 preamplifiers, I-41  
     6-meter, 20 dB gain and low NF, II-543  
     1000x, low-noise design, IV-37  
     audio amplifier, 2- to 6-watt, II-451  
     audio amplifier, 6-W and, III-454  
     equalized, for magnetic phono cartridges, III-671  
 frequency counter, III-128  
 general purpose, I-84  
 general-purpose design, audio signal amplifiers, IV-42  
 handtalkies, two-meter, I-19  
 IF, 30 MHz, IV-460  
 impedance-matching, IV-37  
 LM382 phono, I-91  
 low-noise, IV-41  
 low-noise 30MHz, I-561  
 low-noise transformerless balanced microphone, I-88  
 magnetic phono, I-91, III-673, IV-35  
 medical instrument, II-349  
 microphone, II-45, IV-37, IV-42  
 microphone, low-impedance, IV-41  
 microphone, tone control for, II-687  
 microphone, transformerless, unbalanced input, I-88  
 microwave, 2.3 GHz, IV-316  
 microwave, 3.4 GHz, IV-316  
 microwave, bias supply, IV-318  
 microwave, single-stage, 10 GHz, IV-317
- microwave, two-stage, 10 GHz, IV-319  
 NAB, tape playback, professional, III-38  
 NAB, record, III-673  
 NAB, two-pole, III-673  
 oscilloscope, III-437  
 oscilloscope, instrumentation amplifiers, IV-230-231  
 oscilloscope/counter, III-438  
 phono, I-91  
 phono, low-noise, IV-36  
 phono, magnetic, ultra-low-noise, IV-36  
 phono, magnetic, III-37  
 read-head, automotive circuits, III-44  
 RIAA, III-38  
 RIAA/NAB compensation, I-92  
 stereo, II-43, II-45  
 tape, I-90  
 thermocouple instrumentation amplifier, III-283  
 tone control, I-675  
 tone control, high-level, II-688  
 tone control, IC, I-673, III-657  
 tone control, mixer, I-58  
 UHF-TV, III-546  
 ultra-low leakage, I-38, II-7  
 VHF, I-560  
 precision amplifier, I-40  
     digitally programmable input and gain, II-335  
 preregulators  
     high-voltage power supplies, III-480  
     tracking, III-492  
 prescaler, data circuits, low-frequency, IV-132  
 prescaler probe, amplifying, 650 MHz, II-502  
 preselectors  
     rf amplifiers, JFET, IV-485  
     rf amplifiers, JFET, double-tuned, IV-483  
     rf amplifiers, varactor-tuned, IV-488  
 printer-error alarm, computer circuits, IV-106  
 printers  
     printer-error alarm, IV-106  
     two-sheets in printer detector, IV-136  
 probes, II-498-504, III-496-503, IV-428-434  
     100 K megaohm dc, I-524  
     ac hot wire, I-581  
     audible TTL, I-524  
     audio-rf signal tracer, I-527  
     capacitance buffer, low-input, III-498  
     capacitance buffer, stabilized low-input, III-502

- probes (*cont.*)
- clamp-on-current compensator, II-501
  - CMOS logic, I-523
  - FET, III-501
  - general purpose rf detector, II-500
  - ground-noise, battery-powered, III-500
  - logic probes (*see* logic probes)
  - microvolt, II-499
  - optical light probe, IV-369
  - pH, I-399, III-501
  - prescaler, 650 MHz amplifying, II-502
  - rf, I-523, III-498, III-502, IV-433
  - single injector-tracer, II-500
  - test, 4-220V, III-499
  - three-in-one test set: logic probe, signal tracer, injector, IV-429
  - tone, digital IC testing, II-504
  - universal test probe, IV-431
  - process control interface, I-30
  - processor, CW signal, I-18
  - product detector, I-223
  - programmable amplifiers, II-334, III-504-508
  - differential-input, programmable gain, III-507
  - inverting, programmable-gain, III-505
  - noninverting, programmable-gain, III-505
  - precision, digital control, III-506
  - precision, digitally programmable, III-506
  - programmable-gain, selectable input, I-32
  - variable-gain, wide-range digital control, III-506
  - projectors (*see* photography-related circuits)
  - proportional temperature controller, III-626
  - protection circuits, II-95-99, III-509-513
  - 12ns circuit breaker, II-97
  - automatic power down, II-98
  - circuit breaker, ac, III-512
  - circuit breaker, electronic, high-speed, II-96
  - compressor protector, IV-351
  - crowbars, electronic, II-99, III-510
  - heater protector, servo-sensed, III-624
  - line protectors, computer I/O, 3 uP, IV-101
  - line dropout detector, II-98
  - line-voltage monitor, III-511
  - low-voltage power disconnector, II-97
  - overvoltage, II-96, IV-389
  - overvoltage, fast, III-513
  - overvoltage, logic, I-517
  - polarity-protection relay for power supplies, IV-427
  - power-down, II-98
  - power-failure alarm, III-511
  - power-line connections monitor, ac, III-510
  - power supply, II-497, I-518
  - reset-protection for computers, IV-100
  - proximity sensors, I-135-136, I-344, II-505-507, III-514-518, IV-341-346
  - alarm for, II-506
  - capacitive, III-515
  - field disturbance sensor/alarm, II-507
  - infrared-reflection switch, IV-345
  - relay-output, IV-345
  - SCR alarm, III-517
  - self-biased, changing field, I-135
  - switch, III-517
  - UHF movement detector, III-516
  - pseudorandom sequencer, III-301
  - pulse circuits, IV-435-440
  - amplitude discriminator, III-356
  - coincidence detector, II-178
  - counter, ring counter, low-power, IV-437
  - delay, dual-edge trigger, III-147
  - detector, missing-pulse, III-159
  - divider, non-integer programmable, III-226, II-511
  - extractor, square-wave, III-584
  - generator, 555-circuit, IV-439
  - generator, delayed-pulse generator, IV-440
  - generator, free-running, IV-438
  - generator, logic troubleshooting applications, IV-436
  - generator, transistorized design, IV-437
  - height-to-width converters, III-119
  - oscillator, fast, low duty-cycle, IV-439
  - oscillator, start-stop, stable design, IV-438
  - pulse train-to-sinusoid converters, III-122
  - sequence detector, II-172
  - stretcher, IV-440
  - stretcher, negative pulse stretcher, IV-436
  - stretcher, positive pulse stretcher, IV-438
  - pulse generators, II-508-511
  - 2-ohm, III-231
  - 300-V, III-521
  - astable multivibrator, II-510
  - clock, 60Hz, II-102
  - CMOS short-pulse, III-523
  - delayed, II-509
  - EEPROM, 5V-powered, III-99
  - interrupting pulse-generation, I-357
  - logic, III-520
  - programmable, I-529
  - sawtooth-wave generator and, III-241
  - single, II-175
  - two-phase pulse, I-532
  - unijunction transistor design, I-530
  - very low duty-cycle, III-521
  - voltage-controller and, III-524
  - wide-ranging, III-522
  - pulse supply, high-voltage power supplies, IV-412
  - pulse-dialing telephone, III-610
  - pulse-position modulator, III-375
  - pulse-width-to-voltage converters, III-117
  - pulse-width modulators (PWM), IV-326
  - brightness controller, III-307
  - control, microprocessor selected, II-116
  - modulator, III-376
  - motor speed control, II-376, III-389
  - multiplier circuit, II-264, III-214
  - out-of-bounds detector, III-158
  - proportional-controller circuit, II-21
  - servo amplifier, III-379
  - speed control/energy-recovering brake, III-380
  - very short, measurement circuit, III-336
  - pulse/tone dialer, single-chip, III-603
  - pulsers, laser diode, III-311
  - pump circuits
  - controller, single chip, II-247
  - positive input/negative output charge, I-418
  - push switch, on/off, electronic, II-359
  - push-pull power supply, 400V/60W, II-473
  - pushbutton power control switch, IV-388
  - PUT battery chargers, III-54
  - PUT long-duration timer, II-675
  - pyrometer, optical, I-654

## Q

- Q-multipliers
- audio, II-20
- transistorized, I-566
- QRP CW transmitter, III-690
- QRP SWR bridge, III-336
- quad op amp, simultaneous waveform generator using, II-259
- quadrature oscillators, III-428
- square-wave generator, III-585
- quartz crystal oscillator, two-gate, III-136

quick-deactivating battery sensor, III-61

## R

race-car motor/crash sound generator, III-578  
radar detectors, II-518-520, IV-441-442  
one-chip, II-519  
radiation detectors, II-512-517  
alarm, II-4  
micropower, II-513  
monitor, wideband, I-535  
photomultiplier output-gating circuit, II-516  
pocket-sized Geiger counter, II-514  
radiation-hardened 125A linear regulator, II-468  
radio  
AM car-radio to short-wave radio converter, IV-500  
AM demodulator, II-160  
AM radio, power amplifier, I-77  
AM radio, receivers, III-81, III-529, III-535  
AM/FM, clock radio, I-543  
AM/FM, squelch circuit, II-547, III-1  
amateur radio, III-260, III-534, III-675  
automotive, receiver for, II-525  
clock, I-542  
direction finder, radio signals, IV-148-149  
FM (*see FM transmissions*)  
portable-radio 3 V fixed power supplies, IV-397  
radio beacon converter, IV-495  
receiver, AM radio, IV-455  
receiver, old-time design, IV-453  
receiver, reflex radio receiver, IV-452  
receiver, short-wave receiver, IV-454  
receiver, TRF radio receiver, IV-452  
radio beacon converter, IV-495  
radio-control circuits  
audio oscillator, II-567, III-555  
motor speed controller, I-576  
phase sequence reversal by, II-438  
oscillator, emitter-coupled, II-266  
receiver/decoder, I-574  
single-SCR design, II-361  
radioactivity (*see radiation detectors*)  
rain warning beeper, II-244, IV-189  
RAM, non-volatile CMOS, stand-by power supply, II-477  
ramp generators, I-540, II-521-523, III-525-527, IV-443-447  
accurate, III-526  
integrator, initial condition reset, III-527

linear, II-270  
variable reset level, II-267  
voltage-controlled, II-523  
ranging system, ultrasonic, III-697  
reaction timer, IV-204  
read-head pre-amplifier, automotive circuits, III-44  
readback system, disc/tape phase modulated, I-89  
readout, rf current, I-22  
receiver audio circuit, IV-31  
receivers and receiving circuits (*see also transceivers; transmitters*), II-524-526, III-528-535, IV-448-461  
50kHz FM optical transmitter, I-361  
acoustic-sound receiver, IV-311  
AGC system for CA3028 IF amplifier, IV-458  
AM, III-529, IV-455  
AM, carrier-current circuit, III-81  
AM, integrated, III-535  
analog, I-545  
ATV rf receiver/converter, 420 MHz, low-noise, IV-496, IV-497  
car radio, capacitive diode tuning/ electronic MW/LW switching, II-525  
carrier current, I-143, I-146  
carrier current, single transistor, I-145  
carrier system, I-141  
carrier-operated relay (COR), IV-461  
CMOS line, I-546  
data receiver/message demuxer, three-wire design, IV-130  
fiber optic, 10 MHz, II-205  
fiber optic, 50-Mb/s, III-181  
fiber optic, digital, III-178  
fiber optic, high-sensitivity, 30nW, I-270  
fiber optic, low-cost, 100-M baud rate, III-180  
fiber optic, low-sensitivity, 300nW, I-271  
fiber optic, very high-sensitivity, low speed 3nW, I-269  
FM, carrier-current circuit, III-80  
FM, MPX/SCA, III-530  
FM, narrow-band, III-532  
FM, tuner, III-529  
FM, zero center indicator, I-338  
FSK data, III-533  
ham-band, III-534  
IF amplifier, IV-459  
IF amplifier, preamp, 30 MHz, IV-460  
IF amplifier/receiver, IV-459  
infrared, I-342, II-292, III-274, IV-220-221  
laser, IV-368  
LF receiver, IV-451  
line-type, digital data, III-534  
line-type, low-cost, III-532  
monitor for, II-526  
optical, I-364, II-418  
optical light receiver, IV-367, IV-368  
PLL/BC, II-526  
pulse-frequency modulated, IV-453  
radio control, decoder and, I-574  
radio receiver, AM, IV-455  
radio receiver, old-time design, IV-453  
radio receiver, reflex, IV-452  
radio receiver, TRF, IV-452  
regenerative receiver, one-transistor design, IV-449  
RS-232 to CMOS, III-102  
short-wave receiver, IV-454  
signal-reception alarm, III-270  
superheterodyne receiver, 3.5-to-10 MHz, IV-450-451  
tracer, III-357  
transceiver/mixer, HF, IV-457  
ultrasonic, III-698, III-705  
zero center indicator for FM, I-338  
recording amplifier, I-90  
recording devices (*see tape-recorder circuits*)  
rectangular-to-triangular waveform converter, IV-116-117  
rectifiers, II-527-528, III-536-537  
absolute value, ideal full wave, II-528  
averaging filter, I-229  
bridge rectifier, fixed power supplies, IV-398  
broadband ac active, IV-271  
diodeless, precision, III-537  
full-wave, I-234, III-537, IV-328, IV-650  
half-wave, I-230, II-528, IV-325  
half-wave, fast, I-228  
high-impedance precision, for ac/dc converter, I-164  
inverter/rectifier, programmable op-amp design, IV-364  
low forward-drop, III-471  
precision, I-422  
synchronous, phase detector-selector/balanced modulator, III-441  
redial, electronic telephone set with, III-606  
reference voltages, I-695, III-773-775  
± 10V, I-696  
± 3V, I-696  
± 5V, I-696  
0- to 20 V power, I-694, I-699  
amplifier, I-36  
bipolar output, precision, I-698

- reference voltages (*cont.*)  
 dual tracking voltage, precision, I-698  
 high-stability, I-696  
 low-noise buffered, precision, I-698  
 low-power regulator, I-695  
 micropower 10 V, precision, I-697  
 square wave voltage, precision, I-696  
 standard cell replacement, precision,  
 I-699  
 variable-voltage reference source, IV-  
 327
- reference clock, three phase clock  
 from, II-101
- reference supply, low-voltage adjustable, I-695
- reflection oscillator, crystal-controlled,  
 III-136
- reflectometer, I-16
- regenerative receiver, one-transistor  
 design, IV-449
- registers, shift, I-380, II-366  
 driver, I-418
- regulated power supplies  
 8-amp, II-461  
 12 to 14V at 3 A, II-480  
 +15V 1-A, III-462  
 -15V 1-A, III-463  
 split power supplies, I-492
- regulators (*see* voltage regulators)
- rejection filter, I-283
- relaxation oscillator, III-430, IV-376
- relays, II-529-532, IV-471-475  
 ac, optically coupled, III-418  
 ac, photon coupler in, II-412  
 ac, solid-state latching, IV-472  
 audio operated, I-608  
 bidirectional switch, IV-472  
 capacitance, I-130  
 carrier operated, I-575  
 carrier-operated relay (COR), IV-461  
 dc latching, optically coupled, III-417  
 delay-off circuit, IV-473  
 driver, delay and controls closure  
 time, II-530  
 light-beam operated on/off, I-366  
 monostable relay, low-consumption  
 design, IV-473  
 optically coupled, ac, III-418  
 optically coupled, dc latching, III-417  
 optoisolator, IV-475  
 polarity-protection for power supplies, IV-427  
 rf-actuated, III-270  
 ringer, telephone, III-606  
 solid-state, III-569-570, IV-474  
 solid-state, 10 A 25 Vdc, I-623  
 solid-state, ac, III-570  
 solid-state, ac, latching, IV-472
- solid-state, dc, normally open/closed,  
 III-412
- solid-state, integrated, II-408
- solid-state, light-isolated, I-365
- solid-state, ZVS, antiparallel SCR  
 output, III-416
- sound actuated, I-576, I-610
- telephone, I-631
- time delayed, I-663
- time delayed, ultra-precise, I-219
- tone actuated, I-576
- TR circuit, II-532
- triac, contact protection, II-531
- remote control devices  
 amplifier, I-99  
 carrier, current, I-146  
 drop-voltage recovery for long-line  
 systems, IV-328
- extender, infrared, IV-227
- fax/telephone switch, IV-552-553
- infrared circuit, IV-224
- lamp or appliance, I-370
- loudspeaker via IR link, I-343
- on/off switch, I-577
- ringer, telephone, III-614
- sensor, temperature transducer, I-  
 649
- servo system, I-575
- telephone monitor, II-626
- temperature sensor, II-654
- tester, infrared, IV-228
- thermometer, II-659
- transmitter/receiver, IR, I-342
- video switch, IV-619-621
- repeaters  
 European-type, tone burst generator  
 for, III-74
- fiber optic link, I-270
- telephone, III-607
- repeater beeper, I-19
- reset buttons  
 child-proof computer reset, IV-107
- power-on, II-366
- protection circuit for computer, IV-  
 100
- resistance/continuity meters, II-533,  
 III-538-540
- cable tester, III-539
- continuity tester, III-540
- ohmmeter, linear, III-540
- resistance-ratio detector, II-342
- single chip checker, II-534
- resistance measurement, low parts  
 count ratiometric, I-550
- resistance-to-voltage converter, I-161-  
 162
- resistor multiplier, II-199
- resonator oscillator, varactor tuned 10  
 MHz ceramic, II-141
- restorer, video dc, III-723
- reverb effect, analog delay line, IV-21
- reverb system, stereo, I-602, I-606
- reversing motor drive, dc control  
 signal, II-381
- rf amplifiers, II-537-549, III-542-547,  
 IV-476-493  
 1 W, 2.3 GHz, II-540  
 10 W, 225-400 MHz, II-548  
 10 dB-gain, III-543  
 2- to 30 MHz, III-544  
 4 W amp for 900 MHz, IV-477  
 5 W 150-MHz, III-546  
 5 W power, II-542  
 6-meter kilowatt, II-545  
 6-meter preamp, 20dB gain and low  
 NE, II-543  
 60 W 225-400 MHz, III-547  
 125 W, 150 MHz, II-544  
 500 MHz, IV-491  
 1,296 MHz, IV-486  
 1,500 W, IV-478-479
- AGC, wideband adjustable, III-545
- broadcast-band, III-264, II-546
- broadcast-band booster, IV-487
- buffer amplifier with modulator, IV-  
 490
- cascode amplifier, IV-488
- common-gate, 450-MHz, III-544
- isolation amplifier, II-547
- linear amplifier, 903 MHz, IV-484-  
 485
- linear amplifier, 6-m, 100 W, IV-480-  
 481
- linear amplifier, ATV, 10-to-15 W, IV-  
 481
- low distortion 1.6 to 30MHz SSB  
 driver, II-538
- meter-driver, 1-MHz, III-545
- MOSFET rf-amp stage, dual-gate,  
 IV-489
- power, 600 W, I-559
- power amp, 1296-MHz solid-state,  
 III-542
- preselector, JFET, IV-485
- preselector, JFET, double-tuned, IV-  
 483
- preselector, varactor-tuned, IV-488
- UHF-TV preamp, III-546
- UHF TV-line amplifier, IV-482, IV-  
 483
- wideband amplifier, IV-479, IV-489,  
 IV-490
- wideband amplifier, HF, IV-492
- wideband amplifier, JFET, IV-493
- wideband amplifier, MOSFET, IV-492
- wideband amplifier, two-CA3100 op

- amp design, IV-491  
 rf circuits  
   attenuator, IV-322  
   burst generators, portable, III-73  
   converters, IV-494-501  
   converters, ATV receiver/converter,  
     420 MHz, low-noise, IV-496, IV-  
     497  
   converters, radio beacon converter,  
     IV-495  
   converters, receiver frequency-  
     converter stage, IV-499  
   converters, SW converter for AM car  
     radio, IV-500  
   converters, two-meter, IV-498  
   converters, up-converter, TVRO  
     subcarrier reception, IV-501  
   converters, VLF converter, IV-497  
   converters, WWV-to-SW converter,  
     IV-499  
   converters,receiving converter, 220  
     MHz, IV-500  
   current readout, I-22  
   detector, II-500  
   detector probe, IV-433  
   genie, II-421  
   measurement/test circuits, IV-297-  
     303  
   modulators, I-436, III-372, III-374  
   modulators, double sideband sup-  
     pressed carrier, II-369  
   oscillators, I-550-551, I-572  
   oscillators, 5 MHz VFO, II-551  
   oscillators, transmitter and, 27MHz  
     and 49MHz, I-680  
   output indicator, IV-299  
   power meter, I-16  
   power meter, sidetone oscillator, I-24  
   power meter, switch, III-592  
   power meter, wide-range, III-332  
   probe, I-523, III-498, III-502  
   signal tracer probe, audio, I-527  
   sniffer, II-210  
   switch, low-cost, III-361  
   VHF/UHF diode switch, IV-544  
   voltmeter, I-405, III-766  
 RGB video amplifier, III-709  
 RGB-composite video signal converter,  
   III-714  
 RGB-to-NTSC converter, IV-611  
 ring counters  
   20 kHz, II-135  
   incandescent lamps, I-301  
   low cost, I-301  
   pulse circuit, low-power, IV-437  
   SCR, III-195  
   variable timing, II-134  
 ring detectors
- low line loading, I-634  
 telephone, II-623, III-619  
 telephone, auto-answer, I-635  
 telephone, optically interfaced, III-  
   611  
 ring-around flasher, LED, III-194  
 ringers, telephone, I-628, IV-556  
   extension-phone ringer, IV-561  
   high isolation, II-625  
   multi-tone, remote programmable, II-  
     634  
   musical, II-619  
   piezoelectric, I-636  
   plug-in, remote, II-627  
   relay, III-606  
   remote, II-627, III-614, IV-562  
   silencer, IV-557  
   tone, I-627, I-628, II-630, II-631  
 ripple suppressor, IV-175  
   fixed power supplies, IV-396  
 RLC oscillator, III-423  
 rms-to-dc converter, I-167, II-129  
   thermal, 50-MHz, III-117  
 road ice alarm, II-57  
 robots  
   eyes for, II-327  
   light-seeking, II-325  
 rocket launcher, II-358  
 rotation detector, II-283  
 roulette, electronic, II-276, IV-205  
 RS-232 interface  
   CMOS-to, line receiver, III-102  
   dataselector, automatic, III-97  
   drive circuit, low-power, III-175  
   LED circuit, III-103  
   line-driven CMOS circuits, IV-104  
 RS flip-flop, I-395  
 RTD signal conditioners  
   5V powered linearized platinum, II-  
     650  
   precision, linearized platinum, II-639  
 RTTY machines, fixed current supply,  
   IV-400  
 rumble filters, I-297, III-192, III-660,  
   IV-170, IV-175
- S**  
 S meter, III-342  
 safe area protection, power amplifier  
   with, III-459  
 safety flare, II-608  
 Sallen-Key filters  
   500 Hz bandpass, I-291  
   low-pass, active, IV-177  
   low-pass, equal component, I-292  
   low-pass, second order, I-289  
 sample-and-hold circuits, I-590, II-552-  
   559, III-548-553, IV-502-503  
   x 1000, I-589  
 charge-compensated, II-559  
 fast and precise, II-556  
 filtered, III-550  
 frequency-to-voltage conversion, IV-  
   194  
 high-accuracy, I-590  
 high-performance, II-557  
 high-speed amplifier, I-587  
 high-speed, I-587-588, I-590, III-550  
 infinite, II-558  
 inverting, III-552  
 JFET, I-586  
 low-drift, I-586  
 offset adjustment for, I-588  
 three-channel multiplexer with, III-396  
 track-and-hold, III-552  
 track-and-hold, basic, III-549  
 sampling circuit, hour time delay, II-668  
 saturated standard cell amplifier, II-296  
 sawtooth waves  
   converter, IV-114  
   generator, digital design, IV-444, IV-  
     446  
   oscillator modulator, III-373  
   pulse generator and, III-241  
 SCA decoder, I-214, II-166, II-170  
 SCA demodulator, II-150, III-565  
 scale, digital weight, I-398  
 scaler, inverse, I-422  
 scanner, bar codes, III-363  
 Schmitt triggers, I-593, III-153  
   crystal oscillator, I-181  
   programmable hysteresis, I-592  
   TTL-compatible, II-111  
   without hysteresis, I-592  
 SCR circuits  
   annunciator, self-interrupting load,  
     IV-9  
   chaser, III-197  
   crowbar, II-496  
   flasher, III-197  
   flip-flop, II-367  
   gas/smoke detector, III-251  
   preregulator, II-482  
 proximity alarm, III-517  
   radio control using, II-361  
   relaxation flasher, II-230  
   relaxation oscillator, III-430  
   ring counter, III-195  
   tester, III-344  
   time delay circuit with, II-670  
   triggering series, optically coupled,  
     III-411  
 scramblers, audio (*see also* sound  
   generators; voice-activated cir-  
   cuits), IV-25-27

- scramblers, audio (*cont.*)  
     telephone, II-618  
     voice scrambler/descrambler, IV-26  
     voice scrambler/disguiser, IV-27  
 scratch filters, III-189, IV-175  
     LM287 in, I-297  
 second-audio program adapter, III-142  
 security circuits, I-4, III-3-9  
     automotive security system, I-5, IV-49-56  
 home system, I-6, IV-87  
     infrared, wireless, IV-222-223  
 sense-of-slope tilt meter, II-664  
 sensors (*see also* alarms; control circuits; detectors; indicators; monitors)  
     0-50 C, four-channel temperature, I-648  
     air-flow sensor, thermistor bridge, IV-82  
     ambient light ignoring optical, III-413  
     capacitive, alarm for, III-515  
     cryogenic fluid level, I-386  
     differential temperature, I-655  
     humidity, II-285-287, III-266-267  
     IC temperature, I-649  
     isolated temperature, I-651  
     light level, I-367  
     light, back-biased GaAs LED, II-321  
     logarithmic light, I-366  
     magnetic current, low-power, III-341  
     motion, IV-341-346  
     motion, unidirectional, II-346  
     nanoampere, 100 megohm input impedance, I-203  
     optical interruption sensor, IV-366  
     photodiode amplifier for, II-324  
     precision temperature transducer with remote, I-649  
     proximity, II-505, III-514-518, IV-341-346  
     remote, loop transmitter for, III-70  
     remote temperature, I-654  
     self-biased proximity, detected changing field, I-135  
     short-circuit sensor, computer remote data lines, IV-102  
     simple differential temperature, I-654  
     temperature (*see also* temperature sensor), II-645, I-648, I-657  
     temperature, III-629-631, III-629  
     voltage regulators, LM317 design, IV-466  
     voltage sensor, power supplies, IV-423  
     voltage-level, III-770  
     water level, I-389  
     zero crossing detector with temperature, I-733
- sequence indicator, phase, I-476  
 sequencer, pseudorandom, III-301  
 sequential flasher, II-233  
     ac, II-238  
     automotive turn signals, I-109  
 sequential timer, III-651  
 series connectors, telephone, III-609  
 servo amplifiers  
     400 Hz, II-386  
     bridge type ac, I-458  
     dc, I-457  
 servo motor drive amplifier, II-384  
 servo systems  
     controller, III-384  
     remote control, I-575  
 shaper, sine wave, II-561  
 shift registers, I-380, II-366  
     driver for, I-418  
 shifter, phase (*see* phase shifter)  
 ship siren, electronic, II-576  
 short-circuit proof lamp driver, II-310  
 shortwave transmissions  
     converters, III-114  
     converter, AM car radio, IV-500  
     FET booster, I-561  
     receiver, IV-454  
 short-circuit sensor, computer remote data lines, IV-102  
 shunt, multimeter shunt, IV-293  
 shutoff, automatic, battery-powered projects, III-61  
 shutter speed tester, II-445  
 sidetone oscillator, rf-powered, I-24  
 signal amplifiers, audio, IV-34-42  
 signal attenuator, analog, microprocessor-controlled, III-101  
 signal combiner, III-368  
 signal conditioners, IV-649  
     5V powered linearized platinum RTD, II-650  
     bridge circuit, strain gauge, II-85  
     linearized RTD, precision design, II-639  
     LVDT, II-338  
     thermally stabilized PIN photodiode, II-330  
 signal distribution amplifier, I-39  
 signal generators (*see also* function generators; sound generators; waveform generators)  
     AM broadcast-band, IV-302  
     AM/IF, 455 kHz, IV-301  
     high-frequency, II-150  
     square-wave, III-583-585  
     staircase, III-586-588  
     two-function, III-234  
 signal injectors, III-554-555  
 signal sources, crystal-controlled, II-143
- signal tracer, three-in-one set: logic probe, signal tracer, injector, IV-429  
 signal-strength meters, III-342, IV-166  
 signal-supply, voltage-follower amplifiers, III-20  
 simulated inductor, II-199  
 simulators  
     EKG, three-chip, III-350  
     VOR signals, IV-273  
 sine-to-square wave converter, IV-120  
 sine-wave descrambler, II-163  
 sine-wave generators, square-wave and, tunable oscillator, III-232  
 sine-wave oscillators, I-65, II-560-570, III-556-559, III-560, IV-504-513  
     555 used as RC audio oscillator, II-567  
     adjustable, II-568  
     audio, II-562  
     audio, generator, III-559  
     audio, simple generator for, II-564  
     generator, IV-505  
     generator, LC sine-wave, IV-507  
     generator, LF, IV-512  
     generator, pure sine-wave, IV-506  
     generator, VLF audio tone, IV-508  
 generators, 60 Hz, IV-507  
 LC oscillator, low-frequency, IV-509  
 low distortion, II-561  
 one-IC audio generator, II-569  
 phase-shift, audio ranging, IV-510  
 programmable-frequency, III-424  
 relaxation, modified UJT for clean audio sinusoids, II-566  
 sine wave shaper, II-561  
 sine/square wave TTL oscillator, IV-512  
 two-tone generator, II-570  
 two-transistor design, IV-508  
 variable, super low-distortion, III-558  
 very-low distortion design, IV-509  
 Wien bridge, I-66, I-70, II-566, IV-511  
 Wien bridge, CMOS chip in, II-568  
 Wien-bridge, low-distortion, thermal stable, III-557  
 Wien-bridge, single-supply, III-558  
 Wien-bridge, three-decade 15 Hz to 15 kHz, IV-510  
 Wien-bridge, very-low distortion, IV-513  
 sine-wave output buffer amplifier, I-126  
 sine-wave to square-wave converter, I-170  
 sine/cosine generator, 0.1 to 10 kHz, II-260  
 sine/square wave oscillators, I-65  
     easily tuned, I-65  
     TTL design, IV-512

- tunable, III-232
- single-pulse generator, II-175
- single-sideband (SSB) communications
- CW/SSB product detector, IV-139
  - driver, low distortion 1.6 to 30MHz, II-538
- generators, IV-323
- transmitter, crystal-controlled LO for, II-142
- sirens (*see also* alarms; sound generators), I-606, II-571, III-560-568
- alarm using, II-572, II-573, IV-514-517
- 7400, II-575
- adjustable-rate programmable-frequency, III-563
- electronic, III-566, IV-515, IV-517
- generator for, II-572
- hee-haw, III-565, II-578
- high power, II-578
- linear IC, III-564
- low-cost design, IV-516
- multipurpose system for, II-574
- ship, electronic, II-576
- sonic defender, IV-324
- Star Trek red alert, II-577
- tone generator, II-573
- toy, II-575
- TTL gates in, II-576
- two-state, III-567
- two-tone, III-562
- varying frequency warning alarm, II-579
- wailing, III-563
- warble-tone siren, 6 W, IV-516
- warble-tone siren, alternate tone, IV-515
- whooper, IV-517
- yelp oscillator, II-577, III-562
- slave-flash trigger, IV-380, IV-382
- slide timer, III-448
- slide-show timer, III-444
- sliding tone doorbell, II-34
- smart clutch, auto air conditioner, III-46
- smoke alarms and detectors, II-278, III-246-253
- gas, I-332
- ionization chamber, I-332-333
- line-operated, IV-140
- operated ionization type, I-596
- photoelectric, I-595, I-596
- sniffers (*see also* detectors; monitors)
- heat, electronic, III-627
  - rf, II-210
- snooper, FM, III-680
- socket debugger, coprocessor, III-104
- soldering station, IR-controlled, IV-225
- soil moisture meter, III-208
- solar-powered battery charger, II-71
- solar-triggered switch, III-318
- solenoid drivers, III-571-573
- 12-V latch, III-572
  - hold-current limiter, III-573
  - power-consumption limiter, III-572
- solid-state devices
- ac relay, III-570
  - electric fence charger, II-203
  - high-voltage supply, remote adjustable, III-486
  - relays, III-569-570
  - stepping switch, II-612
  - switch, line-activated, telephone, III-617
- sonic defender, IV-324
- sound-activated circuits (*see* sound-operated circuits)
- sound generators (*see also* burst generators; function generators; sirens; waveform generators), I-605, II-585-593, III-559-568, III-575, IV-15-24, IV-518-524
- amplifier, voltage-controlled, IV-20
- amplifier/compressor, low-distortion, IV-24
- allophone, III-733
- audio tone generator, VLF, IV-508
- autodrum, II-591
- bagpipes, electronic, III-561, IV-521
- beat-frequency, IV-371
- bird chirp, I-605, II-588, III-577
- bongos, II-587
- chime generator, II-604
- chime generator, single-chip design, IV-524
- chug-chug, III-576
- dial tone, I-629, III-609
- ditherizing circuit, digital audio use, IV-23
- doorbell, musical tones, IV-522
- doubler, audio-frequency doubler, IV-16-17
- echo and reverb, analog delay line, IV-21
- electronic, III-360
- envelope generator/modulator, II-601
- equalizer, IV-18
- fader, IV-17
- frequency-shift keyer, tone-generator test circuit, I-723
- funk box, II-593
- fuzz box, III-575
- guitar compressor, IV-519
- harmonic generator, I-24, IV-649
- high-frequency signal, III-150
- hold for telephone, II-623
- melody generator, single-chip design, IV-520
- music maker circuit, IV-521
- musical chimes, I-640
- musical envelope, modulator, I-601, IV-22
- noise generators, I-467, I-468, I-469, IV-308
- octave-shifter for musical effects, IV-523
- one-IC design, II-569
- phasor sound generator, IV-523
- pink noise, I-468
- portable, I-625
- race-car motor/crash, III-578
- run-down clock for games, IV-205
- sound effects, III-574-578
- steam locomotive whistle, II-589, III-568
- steam train/prop plane, II-592
- stereo system, derived center-channel, IV-23
- super, III-564
- synthesizer, II-599
- telephone call-tone generator, IV-562
- telephone ringer, II-619
- tone generator, burst, I-604
- tone generator, portable design, I-625
- Touchtone dial-tone, telephone, III-609
- train chuffer, II-588
- tremolo circuits, III-692-695, IV-589
- twang-twang, II-592
- two-tone, II-570
- ultrasonic sound source, IV-605
- unusual fuzz, II-590
- warbling tone, II-573
- white noise, IV-201
- very-low frequency, I-64
- vocal eliminator, IV-19
- voice circuits, III-729-734
- waa-waa circuit, II-590
- white noise, IV-201
- sound-level meters, III-346, IV-305, IV-307
- meter/monitor, telephone, III-614
- sound-operated circuits (*see also* ultrasonic circuits; voice-operated circuits), II-580-584, III-579-580, IV-525-528
- amplifier, gain-controlled, IV-528
- color organ, II-583, II-584
- decoder, III-145
- flash triggers, I-481, II-449, IV-382
- lights, I-609
- noise clipper, I-396
- relay, I-608, I-610
- switch, II-581, III-580, III-600, III-601, IV-526-527
- switch, ac, II-581

- sound-operated circuits (*cont.*)  
 switch, two-way, I-610  
 switch, voice-operated, III-580  
 switch, voice-activated, microphone-controlled, IV-527  
 speech activity detector, telephone, III-615  
 voice-operated switch, III-580  
 vox box, II-582  
 sources (*see* current sources; voltage sources)  
 source follower, photodiode, III-419  
 SPDT switch, ac-static, II-612  
 space war, I-606  
 speaker systems  
   FM carrier current remote, I-140  
   hand-held transceiver amplifiers, III-39  
   overload protector for, II-16  
   wireless, IR, III-272  
 speakerphone, II-611, III-608  
 speech-activity detector, II-617, III-619  
 speech compressor, II-15  
 speech filter  
   300 Hz-3kHz bandpass, I-295  
   second-order, 300-to-3,400 Hz, IV-174  
   two-section, 300-to-3,000 Hz, IV-174  
 speech network, II-633  
 speed alarm, I-95  
 speed controllers, I-450, I-453, II-378, II-379, II-455  
   back EMF PM, II-379  
   cassette-deck motor speed calibrator, IV-353  
   closed-loop, III-385  
   fans, automatic, III-382  
   dc motors, I-452, I-454, III-377, III-380  
   dc motor, direction control and, I-452  
   dc variable, fiber optic, II-206  
   feedback, I-447  
   fixed, III-387  
   high-efficiency, III-390  
   high-torque motor, I-449  
   light-activated/controlled, IV-247  
   load-dependent, I-451  
   model trains and/or cars, I-455, IV-338-340  
   motor, I-450, I-453  
   motor, dc, reversible, driver and, III-388  
   motor, high-efficiency, III-390  
   PWM, II-376  
   PWM, energy-recovering brake, III-380  
   radio-controlled, I-576  
   series-wound motors, I-448, II-456  
   shunt-wound motors, II-456
- stepper motors, direction and speed control, IV-350  
 switched-mode, III-384  
 tachless, III-386  
 tachometer, II-378, II-389  
 tachometerless, IV-349  
 tools and appliances, I-446  
 universal motors, I-457  
 universal motors, load-dependent, II-451  
 speed warning device, I-96, I-101  
 speedometers, bicycle, IV-271, IV-282  
 splitters, III-581-582  
   battery, III-66  
   phase, precision, III-582  
   precision phase, I-477  
   voltage, III-738, III-743  
   wideband, III-582  
 squarer, precision, I-615  
 square-wave generators, II-594-600, III-583-585, IV-529-536  
   1 kHz, IV-536  
   2 MHz using two TTL gates, II-598  
   555 timer, II-595  
   astable circuit, IV-534  
   astable multivibrator, II-597  
   CMOS 555 astable, true rail-to-rail, II-596  
   duty-cycle multivibrator, III-50-percent, III-584  
   four-decade design, IV-535  
   high-current oscillator, III-585  
   line frequency, II-599  
   low-frequency TTL oscillator, II-595  
   multiburst generator, II-88  
   multivibrator, IV-536  
   oscillator, II-597, IV-532, IV-533  
   oscillator, with frequency doubled output, II-596  
   phase-tracking, three-phase, II-598  
   pulse extractor, III-584  
   quadrature-outputs oscillator, III-585  
   sine-wave, tunable oscillator, III-232  
   three-phase, II-600  
   tone-burst generator, single timer IC, II-89  
   triangle-wave, III-239  
   triangle-wave, precision, III-242  
   triangle-wave, programmable, III-225  
   triangle-wave, wide-range, III-242  
   TTL, LSTTL, CMOS designs, IV-530-532  
   variable duty-cycle, IV-533  
   variable-frequency, IV-535  
 square-wave oscillators, I-613-614, II-597, II-616, IV-532, IV-533  
   0.5 Hz, I-616  
   1kHz, I-612  
   square-to-sine wave converters, III-118
- squelch circuits, II-394  
 AM/FM, I-547  
 voice-activated circuits, IV-624  
 squib firing circuits, II-357  
 stabilizer  
   fixed power supplies, CMOS diode network, IV-406  
   fixed power supplies, output stabilizer, IV-393  
 staircase generators, (*see also* waveform generators), II-601-602, III-586-588, IV-443-447  
 UA2240, III-587  
 stand-by power supply, non-volatile CMOS RAMs, II-477  
 standard, precision calibration, I-406  
 standard-cell amplifier, saturated, II-296  
 standing wave ratio (SWR) meter, IV-269  
 power meter, I-16  
 QRP bridge, III-336  
 warning indicator, I-22  
 Star Trek red alert siren, II-577  
 start-and-run motor circuit, III-382  
 state-of-charge indicator, lithium battery, II-78  
 state-variable filters, II-215, III-189  
   multiple outputs, III-190  
   second-order, 1kHz, Q/10, I-293  
   universal, I-290  
 steam locomotive sound effects, II-589, II-592, III-568  
 static detector, IV-276  
 step-up switching regulator, 6V battery, II-78  
 step-up/step-down dc-dc converters, III-118  
 stepping motor driver, II-376, III-390  
 stepping switch, solid state, II-612  
 stereo circuits  
   amplifier, 12-V/20-W, IV-29  
   amplifier, Av/200, I-77  
   amplifier, bass tone control, I-670  
   audio-level meter, IV-310  
   audio-power meter, IV-306  
   balance circuit, II-603-605  
   balance meter, II-605, I-618-619  
   balance tester, II-604  
   decoder, frequency division multiplex, II-169  
   decoder, time division multiplex, II-18  
   decoder, TV-stereo, II-167  
   demodulator, II-159  
   demodulator, FM, I-544  
   derived center-channel system, IV-23  
   mixer, four-input, I-55  
   power meter, III-331

- preamplifier, II-43, II-45  
 reception indicator, III-269  
 reverb systems, I-602, I-606  
 reverb systems, gain control in, II-9  
 TV-stereo decoder, II-167  
 stimulator, constant-current, III-352  
 stimulus isolator, III-351  
 stop light, garage, II-53  
 strain gauges  
     bridge excitation, III-71  
     bridge signal conditioner, II-85  
     instrumentation amplifier, III-280  
 strobe circuits, II-606-610  
     disco-, II-610  
     high-voltage power supplies, IV-413  
     safety flare, II-608  
     simple, II-607  
     tone burst generator, II-90  
     trip switch, sound activated, I-483  
     variable strobe, III-589-590  
 stud finder, III-339  
 subharmonic frequencies, crystal-stabilized IC timer, II-151  
 subtractor circuit, III-327  
 successive-approximation A/D converter, II-24, II-30  
 summing amplifiers, III-16  
     precision design, I-36  
     video, clamping circuit and, III-710  
 sun tracker, III-318  
 superheterodyne receiver, 3.5-to-10 MHz, IV-450-451  
 supply rails, current sensing in, II-153  
 suppressed-carrier, double-sideband, modulator, III-377  
 sweep generators  
     10.7 MHz, I-472  
     add-on triggered, I-472  
     oscilloscope-triggered, III-438  
 switches and switching circuits, II-611-612, III-591-594, IV-537  
 ac switch, battery-triggered, IV-387  
 analog, buffered, DTL-TTL-controlled, I-621  
 analog, differential, I-622  
 analog, high-toggle/high-frequency, I-621  
 analog, one MOSPOWER FET, III-593  
 antenna selector, electronic, IV-538-539  
 audio/video switcher circuit, IV-540-541  
 auto-repeat switch, bounce-free, IV-545  
 bidirectional relay switch, IV-472  
 bistable switch, mechanically controlled, IV-545  
 contact, I-136  
 dc static, II-367  
 debouncer, III-592  
 debouncer, computer switches, IV-105  
 debouncer, computer switches, auto-repeat, IV-106  
 debouncer, computer switches, flip-flop, IV-108  
 delay, auto courtesy light, III-42  
 DTL-TTL controlled buffered analog, I-621  
 fax/telephone switch, IV-552-553  
 FET dual-trace (oscilloscope), II-432  
 Hall-effect, III-257, IV-539  
 high-frequency, I-622  
 high-side power control switch, 5 V supply, IV-384, IV-385  
 infrared-activated, IV-345  
 latching, SCR-replacing, III-593  
 light-operated, II-320, III-314  
 light-operated, adjustable, I-362  
 MOSFET power control switch, IV-386  
 on/off inverter, III-594  
 on/off switch, IV-543  
 on/off switch, transistorized op-amp  
     on/off switch, IV-546  
 optically coupled, high-voltage ac, III-408  
 optically coupled, zero-voltage, solid-state, III-410  
 over-temperature switch, IV-571  
 photocell memory, ac power control, I-363  
 photoelectric, II-321  
 photoelectric, ac power, II-326  
 photoelectric, synchronous, II-326  
 proximity, III-517  
 push on/off, II-359  
 pushbutton power control switch, IV-388  
 remote, on/off, I-577  
 remote, ring extender, I-630  
 rf, low-cost, III-361  
 rf, power switch, III-592  
 satellite TV audio switcher, IV-543  
 solar-triggered, III-318  
 solid-state stepping, II-612  
 sonar transducer, III-703  
 sound-activated, II-581, III-580, III-600, III-601, IV-526-527  
 sound-activated, two-way, I-610  
 speed, I-104  
 SPDT, ac-static, II-612  
 switching controller, III-383  
 temperature control, low-power, zero-voltage, II-640  
 tone switch, narrowband, IV-542  
 touch switches (*see* touch switches)  
 touchomatic, II-693  
 triac, inductive load, IV-253  
 triac, zero point, II-311  
 triac, zero voltage, I-623  
 two-channel, I-623  
 ultrasonic, I-683  
 under-temperature switch, IV-570  
 VHF/UHF diode rf switch, IV-544  
 video, IV-618-621  
 video, automatic, III-727  
 video, general purpose, III-725  
 video, high-performance, III-728  
 video, very-high off isolation, III-719  
 voice-operated, I-608, III-580  
 voice-operated, microphone-controlled, IV-527  
 zero crossing, I-732  
 zero point, I-373, II-311  
 zero-voltage switching, closed contact half-wave, III-412  
 zero-voltage switching, solid-state, optically coupled, III-410  
 zero-voltage switching, triac design, I-623  
 switched-mode power supplies, II-470, III-458  
     50 W, off-line, III-473  
     100 kHz, multiple-output, III-488  
     converter, +50V push pull, I-494  
 switched light, capacitance, I-132  
 switching inverter, 500 kHz, 12 V systems, II-474  
 switching power amplifier, I-33  
 switching regulators  
     3 A, III-472  
     5 V, 6 A, 25 uHz, separate ultrastable reference, I-497  
     6 A variable output, I-513  
     200 kHz, I-491  
     application circuit, 3W, I-492  
     fixed power supplies, 3 A, IV-408  
     high-current inductorless, III-476  
     low-power, III-490  
     multiple output MPU, I-513  
     positive, I-498  
     step-down, I-493  
     step-up, 6V battery, II-78  
 switching/mixing, silent audio, I-59  
 sync separators  
     single-supply wide-range, III-715  
 video circuits, IV-616  
 synthesizers  
     four-channel, I-603  
     frequency, programmable voltage-controlled, II-265  
     music, I-599

## T

- tachometers, I-100, I-102, II-175, III-335, III-340, III-595-598

tachometers (*cont.*)  
analog readout, IV-280  
calibrated, III-598  
closed-loop, feedback control, II-390  
digital, II-61, III-45, IV-268-269, IV-278  
frequency counter, I-310  
gasoline engine, I-94  
low-frequency, III-596  
minimum component, I-405  
motor speed control, II-378, II-389  
optical pick-up, III-347  
set point, III-47  
tandem dimmer, II-312  
tap, telephone, III-622  
tape-recorder circuits, I-21, I-419, III-599-601, IV-547-548  
amplifier, I-90  
amplifier, playback mode, IV-36  
audio-powered controller, IV-548  
automatic tape-recording switch, I-21, II-21  
automotive-battery power circuit, IV-548  
cassette-deck motor speed calibrator, IV-353  
extended-play circuit, III-600  
flat-response amplifier, III-673  
interface for, II-614  
playback amplifier, III-672, IV-36  
position indicator/controller, II-615  
preamplifier, I-90  
sound-activated switch, III-600, III-601  
starter switch, telephone-activated, I-632  
telephone-activated starter switch, I-632, II-622, III-616  
telephone-to-cassette interface, III-618  
telemetry demodulator, I-229  
telephone-related circuits, II-616-635, III-602-622, IV-549-564  
amplifier, III-621, IV-560  
answering machine beeper, IV-559  
auto answer and ring indicator, I-635  
automatic recording device, II-622  
blinking phone light monitor, II-624, II-629  
call-tone generator, IV-562  
cassette interface, III-618  
decoder, touch-tone, IV-555  
dial pulse indicator, III-613  
dialed-phone number vocalizer, III-731  
dialer, pulse/tone, single-chip, III-603  
dual tone decoding, II-620  
duplex audio link, IV-554  
duplex line amplifier, III-616

eavesdropper, wireless, III-620  
fax-machine switch, remote-controlled, IV-552-553  
flasher, phone-message, IV-556  
flasher, tell-a-bell, IV-558  
flasher, visual ring indicator, IV-559, IV-561  
frequency and volume controller, II-623  
hands-free telephone, III-605  
handset encoder, I-634, III-613  
hold button, II-628, III-612  
in-use indicator, II-629, IV-560, IV-563  
intercom, IV-557  
light for, II-625  
line interface, autopatch, I-635  
line monitor, I-628  
message-taker, IV-563  
musical hold, II-623  
musical ringer, II-619  
night light, telephone controlled, III-604  
off-hook indicator, I-633  
optoisolator status monitor, I-626  
parallel connection, III-611  
piezoelectric ringer, I-636  
power switch, ac, IV-550  
pulse-dialing, III-610  
recording calls, I-632, III-616  
recording calls, auto-record switch, IV-558  
recording calls, telemonitor, IV-553  
redial, III-606  
relay, I-631  
remote monitor for, II-626  
repeater, III-607  
repertory dialer, line powered, I-633  
ring detector, II-623, III-619, IV-564  
ring detector, optically interfaced, III-611  
ringers, IV-556  
ringers, extension-phone ringer, IV-561  
ringers, high isolation, II-625  
ringers, multi-tone, remote programmable, II-634  
ringers, musical, II-619  
ringers, piezoelectric, I-636  
ringers, plug-in, remote, II-627  
ringers, relay, III-606  
ringers, remote, II-627, III-614, IV-562  
ringers, tone, I-627, I-628, II-630, II-631  
scrambler, II-618  
series connection, III-609  
silencer, IV-557  
sound level meter monitor, III-614  
speaker amplifier, IV-555  
speakerphone, II-632, III-608  
speech activity detector, II-617, III-615  
speech network, II-633  
status monitor using optoisolator, I-626  
switch, solid-state, line-activated, III-617  
tap, III-622  
tape-recorder starter controlled by, I-632  
toll-totalizer, IV-551  
tone-dialing, III-607  
tone ringers, I-627, I-628, II-630, II-631  
Touchtone generator, III-609  
touch-tone decoder, IV-555  
vocalizer, dialed-phone number, III-731  
television-related circuits (*see also video circuits*)  
amplifier, audio, III-39  
amplifier, IF detector, MC130/MC1352, I-688  
amplifier, IF/FM IF, quadrature, I-690  
amplifier, RF, UHF TV-line amplifier, IV-482, IV-483  
audio/video switcher circuit, IV-540-541  
automatic turn-off, I-577  
cross-hatch generator, III-724  
data interface, TTL oscillator, II-372  
decoder, stereo TV, II-167  
IF detector, amplifier, MC130/MC1352, I-688  
modulators, I-439, II-433, II-434  
preamplifier, UHF, III-546  
rf up-converter for TVRO subcarrier reception, IV-501  
satellite TV audio switcher, IV-543  
stereo-sound decoder, II-167  
transmitter, III-676  
transmitter, amateur TV, IV-599  
temperature-related circuits (*see also thermometers*), IV-565-572  
alarms, II-4, II-643  
alarms, adjustable threshold, II-644  
automotive temperature indicator, II-56, IV-48  
automotive water-temperature gauge, IV-44  
Centigrade thermometer, II-648  
control circuits, I-641-643, II-636-644, III-623-628, IV-567  
control circuits, defrost cycle, IV-566  
control circuits, heater element, II-642

- control circuits, heater protector, servo-sensed, III-624  
 control circuits, heat sniffer, electronic, III-627  
 control circuits, liquid-level monitor, II-643  
 control circuits, low-power, zero-voltage switch, II-640  
 control circuits, piezoelectric fan-based, III-627  
 control circuits, proportional, III-626  
 control circuits, signal conditioners, II-639  
 control circuits, single setpoint, I-641  
 control circuits, thermocoupled, IV-567  
 control circuits, zero-point switching, III-624  
 converters, temperature-to-frequency, I-646, I-168, I-656, II-651-653  
 converters, temperature-to-time, III-632-633  
 defrost cycle and control, IV-566  
 heater control, I-640, II-642, III-624  
 heat sniffer, III-627  
 hi/lo sensor, II-650  
 indicator, IV-570  
 indicator, automotive temperature, PTC thermistor, II-56  
 measuring circuit, digital, II-653  
 measuring sensor, transistorized, IV-572  
 meter, I-647  
 monitor, III-206  
 monitor, thermal monitor, IV-569  
 oscillators, crystal, temperature-compensated, I-187  
 oscillators, temperature-stable, II-427  
 over-temperature switch, IV-571  
 over/under sensor, dual output, II-646  
 remote sensors, I-649, I-654  
 sensors, I-648, I-657, II-645-650, III-629-631, IV-568-572  
 sensors, 0-50-degree C four channel, I-648  
 sensors, 0-63 degrees C, III-631  
 sensors, 5 V powered linearized platinum RTD signal conditioner, II-650  
 sensors, automotive-temperature indicator, PTC thermistor, II-56  
 sensors, Centigrade thermometer, II-648  
 sensors, coefficient resistor, positive, I-657  
 sensors, differential, I-654, I-655  
 sensors, over/under, dual output, II-646  
 sensors, DVM interface, II-647  
 sensors, hi/lo, II-650  
 sensors, integrated circuit, I-649  
 sensors, isolated, I-651, III-631  
 sensors, remote, I-654  
 sensors, thermal monitor, IV-569  
 sensors, thermocouple amplifier, cold junction compensation, II-649  
 sensors, thermocouple multiplex system, III-630  
 sensors, zero-crossing detector, I-733  
 signal conditioners, II-639  
 thermocouple amplifier, cold junction compensation, II-649  
 thermocouple control, IV-567  
 thermocouple multiplex system, III-630  
 transconductor, temperature-to-frequency, linear, I-646  
 transducer, temperature-transducer with remote sensor, I-649  
 under-temperature switch, IV-570  
 zero-crossing detector, I-733  
 temperature-to-frequency converter, I-168, I-656, II-651-653  
 temperature-to-frequency transconductor, linear, I-646  
 temperature-to-time converters, III-632-633  
 ten-band graphic equalizer, active filter, II-684  
 Tesla coils, III-634-636  
 test circuits (*see* measurement/test circuits)  
 text adder, composite-video signal, III-716  
 theremins, II-654-656  
     digital, II-656  
     electronic, II-655  
 thermal flowmeter, low-rate flow, III-203  
 thermocouple circuits  
     digital thermometer using, II-658  
     multiplex, temperature sensor system, III-630  
     pre-amp using, III-283  
     thermometer, centigrade calibrated, I-650  
 thermocouple amplifiers, I-654, II-14  
     cold junction compensation, II-649  
     high stability, I-355  
 thermometers, II-657-662, III-637-643, IV-573-577  
     0-50 degree F, I-656  
     0-100 degree C, I-656  
 adapter, III-642  
 add-on for DMM digital voltmeter, III-640  
 centigrade, I-655, II-648, II-662  
 centigrade, calibrated, I-650  
 centigrade, ground-referred, I-657  
 differential, I-652, II-661, III-638  
 digital, I-651, I-658  
 digital, temperature-reporting, III-638  
 digital, thermocouple, II-658  
 digital, uP controlled, I-650  
 electronic, II-660, III-639, IV-575, IV-576  
 Fahrenheit, I-658  
 Fahrenheit, ground-referred, I-656  
 high-accuracy design, IV-577  
 implantable/ingestible, III-641  
 kelvin, zero adjust, I-653, II-661  
 kelvin, ground-referred, I-655  
 linear, III-642, IV-574  
 low-power, I-655  
 meter, trimmed output, I-655  
 remote, II-659  
 single-dc supply, IV-575  
 variable offset, I-652  
 thermostats  
     electronic, remote ac, two-wire, I-639  
     electronic, three-wire, I-640  
 three-in-one test set, III-330  
 three-minute timer, III-654  
 three-rail power supply, III-466  
 threshold detectors, precision, III-157  
 tilt meter, II-663-666, III-644-646  
     differential capacitance measurement circuit, II-665  
     sense-of-slope, II-664  
     ultra-simple level, II-666  
 time base  
     crystal oscillator, III-133, IV-128  
     function generators, 1 Hz, for read-out and counter applications, IV-201  
 time delays, I-668, II-220, II-667-670, III-647-649  
     precision solid state, I-664  
     constant current charging, II-668  
     electronic, III-648  
     generator, I-218  
     hour sampling circuit, II-668  
     integrator to multiply 555 timers, low-cost, II-669  
     long-duration, I-220  
     relay, I-663  
     relay, ultra precise long, I-219  
     timing threshold and load driver, III-648  
     two-SCR design, II-670  
 time division multiplex stereo decoder, II-168

timers, I-666, I-668, II-671-681, III-650-655, IV-578-586  
 0.1 to 90 second, I-663  
 741 timer, I-667  
 adjustable, IV-585  
 adjustable ac .2 to 10 seconds, II-681  
 alarm, II-674  
 appliance-cutoff timer, IV-583  
 CMOS, programmable precision, III-652  
 circuit, II-675  
 darkroom, I-480  
 elapsed time/counter timer, II-680  
 electronic egg, I-665  
 IC, crystal-stabilized, II-151  
 interval, programmable, II-678  
 interval, programmable, thumbwheel, I-660  
 long-delay, PUT, I-219  
 long-duration, PUT, II-675  
 long-duration, time delay, IV-585  
 long-interval, programmable, IV-581, IV-582  
 long-interval, RC, I-667  
 long-term electronic, II-672  
 long-time, III-653  
 mains-powered, IV-579  
 one-shot, III-654  
 photographic, I-485  
 photographic, darkroom enlarger, III-445  
 photographic, photo-event timer, IV-379  
 reaction timer, game circuit, IV-204  
 SCR design, IV-583  
 sequential, I-661-662, I-663, III-651  
 sequential UJT, I-662  
 slide-show, III-444  
 slides, photographic, III-448  
 solid-state, industrial applications, I-664  
 ten-minute ID timer, IV-584  
 three-minute, III-654  
 thumbwheel-type, programmable interval, I-660  
 time-out circuit, IV-586  
 transmit-time limiter, IV-580  
 triangle-wave generator, linear, III-222  
 variable duty-cycle output, III-240  
 voltage-controlled, programmable, II-676  
 washer, I-668  
 watchdog timer/alarm, IV-584  
 timing light, ignition, II-60  
 timing threshold and load driver, III-648  
 tone alert decoder, I-213  
 tone annunciator, transformerless, III-27-28

tone burst generators, I-604, II-90  
 European repeaters, III-74  
 tone controls (*see also* sound generators), I-677, II-682-689, III-656-660, IV-587-589  
 active bass and treble, with buffer, I-674  
 active control, IV-588  
 audio amplifier, II-686  
 Baxandall tone-control audio amplifier, IV-588  
 equalizer, ten-band octave, III-658  
 equalizer, ten-band graphic, active filter, II-684  
 guitar treble booster, II-683  
 high-quality, I-675  
 high-z input, hi fi, I-676  
 microphone preamp, I-675, II-687  
 mixer preamp, I-58  
 passive circuit, II-689  
 preamplifier, high-level, II-688  
 preamplifier, IC, I-673, III-657  
 preamplifier, microphone, I-675, II-687  
 preamplifier, mixer, I-58  
 rumble/scratch filter, III-660  
 three-band active, I-676, III-658  
 three-channel, I-672  
 tremolo circuit, IV-589  
 Wien-bridge filter, III-659  
 tone decoders, I-231, III-143  
 dual time constant, II-166  
 24 percent bandwidth, I-215  
 relay output, I-213  
 tone-dial decoder, I-631  
 tone detectors, 500-Hz, III-154  
 tone-dial decoder, I-630, I-631  
 tone-dial encoder, I-629  
 tone-dial generator, I-629  
 tone-dialing telephone, III-607  
 tone encoder, I-67  
 subaudible, I-23  
 tone-dial encoder, I-629  
 two-wire, II-364  
 tone generators (*see* sound generators)  
 tone probe, digital IC testing with, II-504  
 tone ringer, telephone, II-630, II-631  
 totem-pole driver, bootstrapping, III-175  
 touch circuit, I-137  
 touch switches, I-131, I-135-136, II-690-693, III-661-665, IV-590-594  
 CMOS, I-137  
 bistable multivibrator, touch-triggered, I-133  
 double-button latching, I-138  
 hum-detecting touch sensor, IV-594  
 lamp control, three-way, IV-247  
 low-current, I-132  
 On/Off, II-691, III-663, IV-593  
 line-hum, III-664  
 momentary operation, I-133  
 negative-triggered, III-662  
 positive-triggered, III-662  
 sensor switch and clock, IV-591  
 time-on touch switch, IV-594  
 touchomatic, II-693  
 two-terminal, III-663  
 Touchtone generator, telephone, III-609  
 toxic gas detector, II-280  
 toy siren, II-575  
 TR circuit, II-532  
 tracers  
 audio reference signal, probe, I-527  
 bug, III-358  
 closed-loop, III-356  
 receiver, III-357  
 track-and-hold circuits, III-667  
 sample-and-hold circuit, III-549, III-552  
 signal, III-668  
 tracking circuits, III-666-668  
 positive/negative voltage reference, III-667  
 preregulator, III-492  
 track-and-hold, III-667  
 track-and-hold, signal, III-668  
 train chuffer sound effect, II-588  
 transceivers (*see also* receivers; transmitters), IV-595-603  
 CE, 20-m, IV-596-598  
 CW, 5 W, 80-meter, IV-602  
 hand-held, dc adapter, III-461  
 hand-held, speaker amplifiers, III-39  
 HF transceiver/mixer, IV-457  
 ultrasonic, III-702, III-704  
 transducer amplifiers, III-669-673  
 flat-response, tape, III-673  
 NAB preamp, record, III-673  
 NAB preamp, two-pole, III-673  
 photodiode amplifier, III-672  
 preamp, magnetic phono, III-671, III-673  
 tape playback, III-672  
 voltage, differential-to-single-ended, III-670  
 transducers, I-86  
 bridge type, amplifier, II-84, III-71  
 detector, magnetic transducer, I-233  
 sonar, switch and, III-703  
 temperature, remote sensor, I-649  
 transistors and transistorized circuits  
 flashers, II-236, III-200  
 frequency tripler, nonselective, saturated, II-252  
 headphone amplifier, II-43

on/off switch for op amp, IV-546  
 pulse generator, IV-437  
 sorter, I-401  
 tester, I-401, IV-281  
 transmission indicator, II-211  
 transmitters (*see also* receivers; transceivers), III-674-691, IV-595-603  
 2-meter, IV-600-601  
 acoustic-sound transmitter, IV-311  
 amateur radio, 80-M, III-675  
 amateur TV, IV-599  
 beacon, III-683, IV-603  
 broadcast, 1-to-2 MHz, I-680  
 carrier current, I-144, I-145, III-79  
 computer circuit, 1-of-8 channel, III-100  
 CW, 1 W, III-678  
 CW, 10 W, one-tube, I-681  
 CW, 40 M, III-684  
 CW, 902 MHz, III-686  
 CW, HF low-power, IV-601  
 CW, QRP, III-690  
 fiber optic, II-177  
 FM, I-681  
 FM, infrared, voice-modulated pulse, IV-228  
 FM, multiplex, III-688  
 FM, one-transistor, III-687  
 FM, (PRM) optical, I-367  
 FM, snooper, III-680  
 FM, voice, III-678  
 FM, wireless microphone, III-682, III-685, III-691  
 half-duplex information transmission link, low-cost, III-679  
 HF, low-power, IV-598  
 infrared, I-343, II-289, II-290, III-277, IV-226-227  
 infrared, digital, III-275  
 infrared, FM, voice-modulated pulse, IV-228  
 infrared, remote control with receiver, I-342  
 line-carrier, with on/off, 200 kHz, I-142  
 low-frequency, III-682  
 multiplexed, 1-of-8 channel, III-395  
 negative key-line keyer, IV-244  
 optical, I-363, IV-368  
 optical, FM, 50 kHz center frequency, II-417  
 optical, receiver for, II-418  
 oscillator and, 27 and 49 MHz, I-680  
 output indicator, IV-218  
 remote sensors, loop-type, III-70  
 television, III-676  
 ultrasonic, 40 kHz, I-685  
 VHF, modulator, III-684  
 VHF, tone, III-681

treasure locator, lo-parts, I-409  
 treble booster, guitar, II-683  
 tremolo circuits, I-59, III-692-695, IV-589  
 voltage-controlled amplifier, I-598  
 triac circuits  
 ac-voltage controller, IV-426  
 contact protection, II-531  
 dimmer switch, II-310, III-303  
 dimmer switch, 800W, I-375  
 drive interface, direct dc, I-266  
 microprocessor array, II-410  
 relay-contact protection with, II-531  
 switch, inductive load, IV-253  
 trigger, I-421  
 voltage doubler, III-468  
 zero point switch, II-311  
 zero voltage, I-623  
 triangle-to-sine converter, II-127  
 triangle/square wave oscillator, II-422  
 triangle-wave generators, III-234  
 square-wave, III-225, III-239  
 square-wave, precision, III-242  
 square-wave, wide-range, III-242  
 timer, linear, III-222  
 trickle charger, 12 V battery, I-117  
 triggers  
 50-MHz, III-364  
 camera alarm, III-444  
 flash, photography, xenon flash, III-447  
 optical Schmitt, I-362  
 oscilloscope-triggered sweep, III-438  
 remote flash, I-484  
 SCR series, optically coupled, III-411  
 sound/light flash, I-482  
 triac, I-421  
 triggered sweep, add-on, I-472  
 tripler, nonselective, transistor saturation, II-252  
 trouble tone alert, II-3  
 TTL circuits  
 clock, wide-frequency, III-85  
 coupler, optical, III-416  
 gates, siren using, II-576  
 Morse code keyer, II-25  
 square wave to triangle wave converter, II-125  
 TTL to MOS logic converter, II-125  
 TTL oscillators, I-179, I-613  
 1MHz to 10MHz, I-178  
 television display using, II-372  
 crystal, I-197  
 sine/square wave oscillator, IV-512  
 tube amplifier, high-voltage isolation, IV-426  
 tuners  
 antenna tuner, 1-to-30 MHz, IV-14  
 FM, I-231

guitar and bass, II-362  
 turbo circuits, glitch free, III-186  
 twang-twang circuit, II-592  
 twilight-triggered circuit, II-322  
 twin-T notch filters, III-403  
 two-state siren, III-567  
 two-tone generator, II-570  
 two-tone siren, III-562  
 two-way intercom, III-292  
 two's complement, D/A conversion system, binary, 12-bit, III-166

## U

UA2240 staircase generator, III-587  
 UHF transmissions  
 field-strength meters, IV-165  
 rf amplifiers, UHF TV-line amplifier, IV-482, IV-483  
 source dipper, IV-299  
 TV preamplifier, III-546  
 VHF/UHF rf diode switch, IV-544  
 wideband amplifier, high performance FETs, III-264  
 UJT circuits  
 battery chargers, III-56  
 metronome, II-355  
 monostable circuit, bias voltage change insensitive, II-268  
 ultrasonic circuits (*see also* sound-operated circuits), III-696-707, IV-604-606  
 arc welding inverter, 20 KHz, III-700  
 induction heater, 120-KHz 500-W, III-704  
 pest-controller, III-706, III-707  
 pest-repeller, I-684, II-685, III-699, IV-605-606  
 ranging system, III-697  
 receiver, III-698, III-705  
 sonar transducer/switch, III-703  
 sound source, IV-605  
 switch, I-683  
 transceiver, III-702, III-704  
 transmitter, I-685  
 undervoltage detector, IV-138  
 undervoltage monitor, III-762  
 uninterruptible power supply, II-462  
 + 5V, III-477  
 unity-gain amplifiers  
 inverting, I-80  
 inverting, wideband, I-35  
 ultra high Z, ac, II-7  
 unity-gain buffer  
 stable, with good speed and high-input impedance, II-6  
 unity-gain follower, I-27  
 universal counters  
 10 MHz, II-139

universal counters (*cont.*)

  40-MHz, III-127

universal mixer stage, III-370

universal power supply, 3-30V, III-489

up/down counter, extreme count  
  freezer, III-125

## V

vacuum fluorescent display circuit, II-  
  185

vacuum gauge, automotive, IV-45

vapor detector, II-279

varactor-tuned 10 MHz ceramic reso-  
  nator oscillator, II-141

variable current source, 100 mA to 2A,  
  II-471

variable duty-cycle oscillator, fixed-  
  frequency, III-422

variable-frequency inverter, comple-  
  mentary output, III-297

variable-gain amplifier, voltage-con-  
  trolled, I-28-29

variable-gain and sign op amp, II-405

variable-gain circuit, accurate null and,  
  III-69

variable oscillators, II-421

  audio, 20Hz to 20kHz, II-727

  four-decade, single control for, II-424

  sine-wave oscillator, super low-  
    distortion, III-558

  wide range, II-429

variable power supplies, III-487-492,  
  IV-414-421

  adjustable 10-A regulator, III-492

  current source, voltage-programma-  
    ble, IV-420

  dc supply, SCR variable, IV-418

  dc supply, step variable, IV-418

  dual universal supply, 0-to-50 V, 5 A,  
    IV-416-417

  regulated supply, 2.5 A, 1.25-to-25 V

regulator, Darlington, IV-421

regulator, variable, 0-to-50 V, IV-421

regulator/current source, III-490

switch-selected fixed-voltage supply,  
  IV-419

switching regulator, low-power, III-  
  490

switching, 100-KHz multiple-output,  
  III-488

tracking preregulator, III-492

transformerless supply, IV-420

universal 3-30V, III-489

variable current source, 100mA to  
  2A, II-471

voltage regulator, III-491

vehicles (*see* automotive circuits)

VFO, 5 MHz, II-551

VHF transmissions

crystal oscillator, 20-MHz, III-138

crystal oscillator, 50-MHz, III-140

crystal oscillator, 100-MHz, III-139

modulator, I-440, III-684

tone transmitter, III-681

VHF/UHF diode rf switch, IV-544

video amplifiers, III-708-712

  75-ohm video pulse, III-711

  buffer, low-distortion, III-712

  color, I-34, III-724

  dc gain-control, III-711

  FET cascade, I-691

  gain block, III-712

  IF, low-level video detector circuit, I-  
    689, II-687

  JFET bipolar cascade, I-692

  line driving, III-710

  log amplifier, I-38

  RGB, III-709

  summing, clamping circuit and, III-  
    710

video circuits (*see also* television-  
  related circuits), III-713-728, IV-  
  607-621

audio/video switcher circuit, IV-540-  
  541

camera-image tracker, analog volt-  
  age, IV-608-609

camera link, wireless, III-718

chroma demodulator with RGB  
  matrix, III-716

color amplifier, III-724

color-bar generator, IV-614

composite-video signal text adder,  
  III-716

converter, RGB-to-NTSC, IV-611

converter, video a/d and d/a, IV-610-  
  611

cross-hatch generator, color TV, III-  
  724

dc restorer, III-723

decoder, NTSC-to-RGB, IV-613

high-performance video switch, III-  
  728

line pulse extractor, IV-612

loop-thru amplifier, IV-616

mixer, high-performance video mixer,  
  IV-609

modulators, I-437, II-371, II-372

monitors, RGB, blue box, III-99

monochrome-pattern generator, IV-  
  617

multiplexer, cascaded, 1-of-15, III-  
  393

PAL/NTSC decoder with RGB input,  
  III-717

palette, III-720

picture fixer/inverter, III-722

RGB-composite converter, III-714

signal clamp, III-726

switching circuits, IV-618-621

switching circuits, remote selection  
  switch, IV-619

switching circuits, remote-controlled  
  switch, IV-619-621

sync separator, IV-616

sync separator, single-supply wide-  
  range, III-715

video op amp circuits, IV-615

video switch, automatic, III-727

video switch, general purpose, III-  
  725

video switch, very-high off isolation,  
  III-719

wireless camera link, III-71

vocal eliminator, IV-19

voice scrambler/descrambler, IV-26

voice scrambler/disguiser, IV-27

voice substitute, electronic, III-734

voice-activated circuits (*see also* sound-  
  operated circuits), III-729-734, IV-  
  622-624

ac line-voltage announcer, III-730

allophone generator, III-733

amplifier/switch, I-608

computer speech synthesizer, III-732

dialed phone number vocalizer, III-  
  731

scanner voice squelch, IV-624

switch, III-580

switch, microphone-controlled, IV-  
  527

switch/amplifier, I-608

voice substitute, electronic, III-734

VOX circuit, IV-623

voltage amplifiers

  differential-to-single-ended, III-670

  reference, I-36

voltage-controlled amplifier, I-31, I-598

  attenuator for, II-18

  tremolo circuit, I-598

  variable gain, I-28-29

  voltage-controlled filter, III-187

  1,000:1 tuning, IV-176

  voltage-controlled high-speed one shot,  
    II-266

voltage-controlled ramp generator, II-  
  523

voltage-controlled resistor, I-422

voltage-controlled timer, programma-  
  ble, II-676

voltage-controlled amplifier, IV-20

  tremolo circuit or, I-598

voltage-controlled oscillators, I-702-  
  704, II-702, III-735, IV-625-630

3-5 V regulated output converter, III-  
  739

10Hz to 10kHz, I-701, III-735-741

555-VCO, IV-627  
 audio-frequency VCO, IV-626  
 crystal oscillator, III-135, IV-124  
 current sink, voltage-controlled, IV-629  
 driver, op-amp design, IV-362  
 linear, I-701, IV-628  
 linear triangle/square wave, II-263  
 logarithmic sweep, III-738  
 precision, I-702, III-431  
 restricted-range, IV-627  
 stable, IV-372-373  
 supply voltage splitter, III-738  
 three-decade, I-703  
 TMOS, balanced, III-736  
 two-decade, high-frequency, I-704  
 varactorless, IV-630  
 variable-capacitance diode-sparked, III-737  
 VHF oscillator, voltage-tuned, IV-628  
 waveform generator, III-737  
 wide-range, IV-629  
 wide-range, biphasic, IV-629  
 wide-range, gate, IV-627  
 voltage-controller, pulse generator, III-524  
 voltage converters, III-742-748  
     12-to-16 V, III-747  
     dc-to-dc, 3-25 V, III-744  
     dc-to-dc, dual output  $\pm$  12-15 V, III-746  
     flyback, high-efficiency, III-744  
     flyback-switching, self-oscillating, III-748  
     negative voltage, uP-controlled, IV-117  
     offline, 1.5-W, III-746  
     regulated 15-Vout 6-V driven, III-745  
     splitter, III-743  
     unipolar-to-dual supply, III-743  
 voltage detector relay, battery charger, II-76  
 voltage followers, I-40, III-212  
     fast, I-34  
     noninverting, I-33  
     signal-supply operation, amplifier, III-20  
 voltage inverters, precision, III-298  
 voltage meters/monitors/indicators, III-758-772  
     ac voltmeter, III-765  
     ac voltmeter, wide-range, III-772  
     audio millivoltmeter, III-767, III-769  
     automotive battery voltage gauge, IV-47  
     battery-voltage measuring regulator, IV-77  
     comparator and, II-104  
     dc voltmeter, III-763

dc voltmeter, resistance, high-input, III-762  
 DVM, 3.5-digit, full-scale 4-decade, III-761  
 DVM, 4.5-digit, III-760  
 FET voltmeter, III-765, III-770  
 five-step level detector, I-337  
 frequency counter, III-768  
 high-input resistance voltmeter, III-768  
 HTS, precision, I-122  
 level detectors, I-338, II-172, III-759, III-770  
 low-voltage indicator, III-769  
 multiplexed common-cathode LED ADC, III-764  
 over/under monitor, III-762  
 peak program detector, III-771  
 rf voltmeter, III-766  
 solid-state battery, I-120  
 ten-step level detector, I-335  
 visible, I-338, III-772  
 voltage freezer, III-763  
 voltage multipliers, IV-631-637  
     2,000 V low-current supply, IV-636-637  
     10,000 V dc supply, IV-633  
     corona wind generator, IV-633  
     doublers, III-459, IV-635  
     doubler, cascaded, Cockcroft-Walton, IV-635  
     doublers, triac-controlled, III-468  
     laser power supply, IV-636  
     negative-ion generator, high-voltage, IV-634  
     tripler, low-current, IV-637  
     voltage ratio-to-frequency converter, III-116  
 voltage references, III-773-775  
     bipolar source, III-774  
     digitally controlled, III-775  
     expanded-scale analog meter, III-774  
     positive/negative, tracker for, III-667  
     variable-voltage reference source, IV-327  
 voltage regulators, I-501, I-511, II-484  
     0- to 10-V at 3A, adjustable, I-511  
     0- to 22-V, I-510  
     0- to 30-V, I-510  
     5 V, low-dropout, III-461  
     5 V, 1 A, I-500  
     6 A, variable output switching, I-513  
     10 A, I-510  
     10 A, adjustable, III-492  
     10 V, high stability, III-468  
     15 V, 1 A, remote sense, I-499  
     15 V, slow turn-on, III-477  
         -15 V negative, I-499  
     45 V, 1 A switching, I-499  
 100 Vrms, I-496  
 ac, III-477  
 adjustable output, I-506, I-512  
 automotive circuits, III-48, IV-67  
 battery charging, I-117  
 bucking, high-voltage, III-481  
 common hot-lead regulator, IV-467  
 constant voltage/constant current, I-508  
 current and thermal protection, 10 amp, II-474  
 dual-tracking, III-462  
 efficiency-improving switching, IV-464  
 fixed pnp, zener diode increases output, II-484  
 fixed-current regulator, IV-467  
 fixed-voltages, IV-462-467  
 flyback, off-line, II-481  
 high- or low-input regulator, IV-466  
 high-stability, I-499  
 high-stability, 1 A, I-502  
 high-stability, 10 V, III-468  
 high-voltage, III-485  
 high-voltage, foldback-current limiting, II-478  
 high-voltage, precision, I-509  
 low-dropout, 5-V, III-461  
 low-voltage, I-502, I-511  
 linear, low-dropout, III-459  
 linear, radiation-hardened 125 A, II-468  
 mobile, I-498  
 negative, III-474, IV-465  
 negative, -15 V, I-499  
 negative, floating, I-498  
 negative, switching, I-498  
 negative, voltage, I-499  
 positive, floating, I-498  
 positive, switching, I-498  
 positive, with NPN/PNP boost, III-475  
 positive, with PNP boost, III-471  
 pre-, SCR, II-482  
 pre-, tracking, III-492  
 projection lamp, II-305  
 PUT, 90 V rms, II-479  
 remote shutdown, I-510  
 negative, IV-465  
 sensor, LM317 regulator sensing, IV-466  
 short-circuit protection, low-voltage, I-502  
 single-ended, I-493  
 single-supply, II-471  
 slow turn-on 15 V, I-499  
 switch-mode, IV-463  
 switching, 3-A, III-472  
 switching, 3 W, application circuit, I-492

voltage regulators (*cont.*)  
 switching, 5 V, 6 A 25kHz, separate  
 ultrastable reference, I-497  
 switching, 6 A, variable output, I-513  
 switching, 200 kHz, I-491  
 switching, multiple output, for use  
 with MPU, I-513  
 switching, step down, I-493  
 switching, high-current inductorless,  
 III-476  
 switching, low-power, III-490  
 variable, III-491, IV-468-470  
 variable, current source, III-490  
 zener design, programmable, IV-470  
 voltage sources  
 millivolt, zenerless, I-696  
 programmable, I-694  
 voltage splitter, III-738  
 voltage-to-current converter, I-166, II-  
 124, III-110, IV-118  
 power, I-163  
 zero IB error, III-120  
 voltage-to-frequency converters, I-707,  
 III-749-757, IV-638-642  
 1 Hz-to-10MHz, III-754  
 1 Hz-to-30 MHz, III-750  
 1Hz-to-1.25 MHz, III-755  
 5 KHz-to-2MHz, III-752  
 10Hz to 10-kHz, I-706, III-110  
 accurate, III-756  
 differential-input, III-750  
 function generators, potentiometer-  
 position, IV-200  
 low-cost, III-751  
 low-frequency converter, IV-641  
 negative input, I-708  
 optocoupler, IV-642  
 positive input, I-707  
 precision, II-131  
 preserved input, III-753  
 ultraprecision, I-708  
 wide-range, III-751, III-752  
 voltage-to-pulse duration converter, II-  
 124  
 voltmeters  
 3½ digit, I-710  
 3½ digital true rms ac, I-713  
 5-digit, III-760  
 ac, III-765  
 ac, wide-range, III-772  
 add-on thermometer for, III-640  
 bar-graph, I-99, II-54  
 dc, III-763  
 dc, high-input resistance, III-762  
 digital, III-4  
 digital, 3.5-digit, full-scale, four-  
 decade, III-761  
 digital, LED readout, IV-286  
 FET, I-714, III-765, III-770

high-input resistance, III-768  
 millivoltmeters (*see* millivoltmeters)  
 rf, I-405, III-766  
 wide-band ac, I-716  
 voltohmometer, phase meter, digital  
 readout, IV-277  
 volume amplifier, II-46  
 volume control circuits, IV-643-645  
 telephone, II-623  
 volume indicator, audio amplifier, IV-  
 212  
 VOR signal simulator, IV-273  
 vox box, II-582, IV-623  
 Vpp generator, EPROM, II-114  
 VU meters  
 extended range, II-487, I-715  
 LED display, IV-211

**W**

waa-waa circuit, II-590  
 wailers (*see* alarms; sirens)  
 wake-up call, electronic, II-324  
 walkman amplifier, II-456  
 warblers (*see* alarms; sirens)  
 warning devices  
 auto lights-on warning, II-55  
 high-level, I-387  
 high-speed, I-101  
 light, III-317  
 light, battery-powered, II-320  
 low-level, audio output, I-391  
 speed, I-96  
 varying-frequency alarm, II-579  
 water-level sensors (*see* fluid and  
 moisture detectors)  
 water-temperature gauge, automotive,  
 IV-44  
 wattmeter, I-17  
 wave-shaping circuits (*see also* wave-  
 form generators), IV-646-651  
 capacitor for high slew rates, IV-650  
 clipper, glitch-free, IV-648  
 flip-flop, S/R, IV-651  
 harmonic generator, IV-649  
 phase shifter, IV-647  
 rectifier, full-wave, IV-650  
 signal conditioner, IV-649  
 waveform generators (*see also* burst  
 generators; function generators;  
 sound generators; square-wave  
 generators; wave-shaping circuits),  
 II-269, II-272  
 audio, precision, III-230  
 four-output, III-223  
 harmonic generator, IV-649  
 high-speed generator, I-723  
 precise, II-274  
 ramp generators, IV-443-447

sawtooth generator, digital, IV-444,  
 IV-446  
 sine-wave, IV-505, IV-506  
 sine-wave, 60 Hz, IV-507  
 sine-wave, audio, II-564  
 sine-wave, LC, IV-507  
 sine-wave, LF, IV-512  
 sine-wave oscillator, audio, III-559  
 staircase generators, IV-443-447  
 staircase generator/frequency  
 divider, I-730  
 stepped waveforms, IV-447  
 triangle and square waveform, I-726  
 VCO and, III-737  
 wavemeter, tuned RF, IV-302  
 weather-alert decoder, IV-140  
 weight scale, digital, II-398  
 Wheel-of-Fortune game, IV-206  
 whistle, steam locomotive, II-589, III-  
 568  
 who's first game circuit, III-244  
 wide-range oscillators, I-69, III-425  
 variable, I-730  
 wide-range peak detectors, III-152  
 hybrid, 500 kHz-1 GHz, III-265  
 instrumentation, III-281  
 miniature, III-265  
 UHF amplifiers, high-performance  
 FETs, III-264  
 wideband amplifiers  
 low-noise/low drift, I-38  
 two-stage, I-689  
 rf, IV-489, IV-490, IV-491  
 rf, HF, IV-492  
 rf, JFET, IV-493  
 rf, MOSFET, IV-492  
 rf, two-CA3100 op amp design, IV-  
 491  
 unity gain inverting, I-35  
 wideband signal splitter, III-582  
 wideband two-pole high pass filter, II-  
 215  
 Wien-bridge filter, III-659  
 notch filter, II-402  
 Wien-bridge oscillators, I-62-63, I-70,  
 III-429, IV-371, IV-377, IV-511  
 CMOS chip in, II-568  
 low-distortion, thermally stable, III-  
 557  
 low-voltage, III-432  
 sine wave, I-66, I-70, II-566  
 sine-wave, three-decade, IV-510  
 sine-wave, very-low distortion, IV-  
 513  
 single-supply, III-558  
 variable, III-424  
 wind-powered battery charger, II-70  
 windicator, I-330  
 window circuits, II-106, III-90, III-776-

781, IV-655-659  
comparator, IV-658  
comparator, low-cost design, IV-656-657  
comparator, voltage comparator, IV-659  
detector, IV-658  
digital frequency window, III-777  
discriminator, multiple-aperture, III-781  
generator, IV-657  
high-input-impedance, II-108  
windshield wiper circuits  
control circuit, I-103, I-105, II-62  
delay circuit, II-55  
delay circuit, solid-state, IV-64  
hesitation control unit, I-105  
intermittent, dynamic braking, II-49  
interval controller, IV-67  
slow-sweep control, II-55  
windshield washer fluid watcher, I-107  
wire tracer, II-343

wireless microphones (*see* microphones), IV-652  
wireless speaker system, IR, III-272  
write amplifiers, III-18

## X

xenon flash trigger, slave, III-447  
XOR gates, IV-107  
complementary signals generator, III-226  
oscillator, III-429  
up/down counter, III-105

## Y

yelp oscillator/siren, II-577, III-562

## Z

280 clock, II-121

zappers, battery, II-64  
ni-cad battery, II-66  
ni-cad battery, version II, II-68  
zener diodes  
clipper, fast and symmetrical, IV-329  
increasing power rating, I-496, II-485  
limiter using one-zener design, IV-257  
tester, I-400  
variable, I-507  
voltage regulator, programmable, IV-470  
zero-crossing detector, II-173  
zero meter, suppressed, I-716  
zero-point switches  
temperature control, III-624  
triac, II-311  
zero-voltage switches  
closed contact half-wave, III-412  
solid-state, optically coupled, III-410  
solid-state, relay, antiparallel SCR output, III-416

---

## Other Bestsellers of Related Interest

---

### ENCYCLOPEDIA OF ELECTRONIC CIRCUITS

Vol. 1—Rudolf F. Graf

“...schematics that encompass virtually the entire spectrum of electronics technology... This is a well worthwhile book to have handy.” —*Modern Electronics*

Discover hundreds of the most versatile electronic and integrated circuit designs, all available at the turn of a page. You'll find circuit diagrams and schematics for a wide variety of practical applications. Many entries also include clear, concise explanations of the circuit configurations and functions. 768 pages, 1,762 illustrations. Book No. 1938, \$32.95 paperback, \$60.00 hardcover

### THE ILLUSTRATED DICTIONARY OF ELECTRONICS—5th Edition

—Rufus P. Turner and Stan Gibilisco

This completely revised and updated edition defines more than 27,000 practical electronics terms, acronyms, and abbreviations. Find up-to-date information on basic electronics, computers, mathematics, electricity, communications, and state-of-the-art applications—all discussed in a nontechnical style. The author also includes 360 new definitions and 125 illustrations and diagrams. 736 pages, 650 illustrations. Book No. 3345, \$26.95 paperback

### ELECTRONIC CONVERSIONS:

#### Symbols and Formulas—2nd Edition

—Rufus P. Turner and Stan Gibilisco

This revised and updated edition supplies all the formulas, symbols, tables, and conversion factors commonly used in electronics. Exceptionally easy to use, the material is organized by subject matter. Its format is ideal and you can save time by directly accessing specific information. Topics cover only the most-needed facts about the most often used conversions, symbols, formulas, and tables. 280 pages, 94 illustrations. Book No. 2865, \$14.95 paperback only

### ELECTRONIC DATABOOK—4th Edition

—Rudolf F. Graf

If it's electronic, it's here—current, detailed, and comprehensive! Use this book to broaden your electronics information base. Revised and expanded to include all up-to-date information, this fourth edition makes any electronic job easier and less time-consuming. You'll find information that will aid in the design of local area networks, computer interfacing structure, and more! 528 pages, 131 illustrations. Book No. 2958, \$24.95 paperback only

### BUILD YOUR OWN TEST EQUIPMENT

—Homer L. Davidson

Build more than 30 common electronic testing devices, ranging from simple continuity and polarity testers to signal injectors and power supplies. Also learn how test instruments work, how they are used, and how to save money. Each project includes a complete parts list with exact part numbers. 300 pages, 324 illustrations. Book No. 3475, \$17.95 paperback, \$27.95 hardcover

### ELECTRONIC SIGNALS AND SYSTEMS:

#### Television, Stereo, Satellite TV, and

Automotive—Stan Prentiss

Study signal analysis as it applies to the operation and signal-generating capabilities of today's most advanced electronic devices with this handbook. It explains the composition and use of a wide variety of test instruments, transmission media, satellite systems, stereo broadcast and reception facilities, antennas, television equipment, and even automotive electrical systems. You'll find coverage of C- and Ku-band video, satellite master TV systems, high-definition television, C-QUAM® AM stereo transmission and reception, and more. 328 pages, 186 illustrations. Book No. 3557, \$19.95 paperback, \$29.95 hardcover

**Prices Subject to Change Without Notice.**

---

**Look for These and Other TAB Books at Your Local Bookstore**

---

**To Order Call Toll Free 1-800-822-8158**

(in PA, AK, and Canada call 717-794-2191)

or write to TAB Books, Blue Ridge Summit, PA 17294-0840.

---

Title	Product No.	Quantity	Price

Check or money order made payable to TAB Books                              Subtotal \$ \_\_\_\_\_

Charge my  VISA  MasterCard  American Express                              Postage and Handling

Acct. No. \_\_\_\_\_ Exp. \_\_\_\_\_ (\$3.00 in U.S., \$5.00 outside U.S.) \$ \_\_\_\_\_

Signature: \_\_\_\_\_ Add applicable state and local sales tax \$ \_\_\_\_\_

Name: \_\_\_\_\_ TOTAL \$ \_\_\_\_\_

Address: \_\_\_\_\_ TAB Books catalog free with purchase; otherwise send \$1.00 in check or money order and receive \$1.00 credit on your next purchase.

City: \_\_\_\_\_ Orders outside U.S. must pay with international money in U.S. dollars

State: \_\_\_\_\_ Zip: \_\_\_\_\_ TAB Guarantee: If for any reason you are not satisfied with the book(s) you order, simply return it (them) within 15 days and receive a full refund.

BC